

SCHAUM'S  
*ouTlines*

# BASIC ELECTRICITY

MILTON GUSSOW

The perfect aid for better grades

Covers all course fundamentals and  
supplements any class text

600 fully worked problems

Teaches effective problem-  
solving

Ideal for independent study

**MORE THAN  
30 MILLION  
SCHAUM'S  
OUTLINES  
SOLD**

Use with these courses: ✓ Basic Electricity ✓ Electric Circuits  
✓ Application of Electric Circuits

*SCHAUM'S OUTLINE OF*

**THEORY AND PROBLEMS**

OF

**BASIC ELECTRICITY**

•

by

**MILTON GUSSOW, M.S.**

*Senior Engineer  
Applied Physics Laboratory  
The Johns Hopkins University*

**McGraw-Hill**

New York San Francisco Washington, D.C. Auckland Bogotá  
Caracas Lisbon London Madrid Mexico City Milan  
Montreal New Delhi San Juan Singapore  
Sydney Tokyo Toronto

*To Libbie, Myra, and Susan*

**MILTON GUSSOW** is a senior engineer at Johns Hopkins University Applied Physics Laboratory. He received his B.S. (1949) from the U.S. Naval Academy, his B.S.E.E. (1956) from the U.S. Navy Postgraduate School, and his M.S. (1957) from Massachusetts Institute of Technology. He is an Adjunct Professor at American University and George Washington University where he teaches courses in mathematics and electrical engineering. Mr. Gussow was formerly Senior Vice President for Education at the McGraw-Hill Continuing Education Center. He is the author of over fifty technical papers.

**Schaum's Outline of Theory and Problems of  
BASIC ELECTRICITY**

Copyright © 1983 by The McGraw-Hill Companies, Inc. All rights reserved. Printed in the United States of America. Except as permitted under the Copyright Act of 1976, no part of this publication may be reproduced or distributed in any form or by any means, or stored in a data base or retrieval system, without the prior written permission of the publisher.

16 17 18 19 20 BAW 9 9

**ISBN 0-07-025240-8**

Sponsoring Editor, John Aliano  
Consulting Editor, Gordon Rockmaker  
Editing Supervisor, Marthe Grice  
Production Manager, Nick Monti

**Library of Congress Cataloging in Publication Data**

Gussow, Milton.  
Schaum's outline of theory and problems of basic  
electricity.

(Schaum's outline series)

Includes index.

1. Electricity. I. Title.

TK146.G974 1983 621.3'02'02 82-4671

ISBN 0-07-025240-8

**McGraw-Hill**

*A Division of The McGraw-Hill Companies*



## Preface

This book is intended as a basic text to cover the fundamentals of electricity and electric circuits. It may be used by beginning students in high schools, technical institutes, and colleges who have no experience in electricity.

Explanations and step-by-step solutions are deliberately detailed so that the text can stand alone. Thus it also may be used as a home-study or reference book. A knowledge of basic algebra and trigonometry is assumed. Designed to provide a broad and deep background in the nature of electricity and the operation and application of electric circuits, the text uses numerous and easy-to-follow examples accompanied by diagrams. Starting with the physics of electric current flow, the book describes and analyzes both direct-current and alternating-current electric circuits, generators and motors, transformers, and measuring instruments. To assure correlation to modern practice and design, illustrative problems are presented in terms of commonly used voltages and current ratings, covering circuits and equipments typical of those found in today's electrical systems.

There are several special features of this book. One is the use of the International System of Units (SI) throughout. A second is the prolific use of equation numbers for reference so that the reader will always know the source of each equation used. Other features include simplified ways to solve problems on three-phase transformer windings, series and parallel resonance, and *RL* and *RC* circuit waveforms.

I wish to thank John Aliano, Gordon Rockmaker, and Marthe Grice of the McGraw-Hill Book Company for their many constructive criticisms and continuing efforts to get this book published.

MILTON GUSSOW

*This page intentionally left blank*

## CONTENTS

<b>Chapter 20</b>	<b>ELECTRICAL MEASUREMENTS .....</b>	<b>411</b>
	Basic Measuring Instruments .....	411
	Ammeters .....	411
	Voltmeters .....	414
	Ohmmeters .....	416
	Multimeters .....	419
	Alternating-Current Meters .....	419
	Wattmeters and Watthour Meters .....	425
	Analog Electronic Meters .....	427
	Digital Meters .....	429
<hr/>		
	<b>INDEX .....</b>	<b>447</b>

# Contents

<b>Chapter 1</b>	<b>THE NATURE OF ELECTRICITY .....</b>	<b>1</b>
	Structure of the Atom .....	1
	The Electric Charge .....	3
	The Coulomb .....	4
	The Electrostatic Field .....	4
	Potential Difference .....	5
	Current .....	5
	Current Flow .....	6
	Sources of Electricity .....	7
	Direct and Alternating Currents and Voltages .....	8
<hr/>		
<b>Chapter 2</b>	<b>ELECTRICAL STANDARDS AND CONVENTIONS .....</b>	<b>15</b>
	<b>Units</b>	
	Introduction .....	15
	Metric Prefixes .....	15
	Powers of 10 .....	16
	Scientific Notation .....	20
	Rounding Off Numbers .....	20
	<b>Graphical Symbols and Electrical Diagrams</b>	
	Schematic Diagram .....	27
	One-Line Diagram .....	28
	Block Diagram .....	31
	Wiring Diagram .....	31
	Electric Plan .....	31
<hr/>		
<b>Chapter 3</b>	<b>OHM'S LAW AND POWER .....</b>	<b>38</b>
	The Electric Circuit .....	38
	Resistance .....	39
	Fixed Resistors .....	39
	Variable Resistors .....	40
	Ohm's Law .....	41
	Electric Power .....	42
	Horsepower .....	43
	Electrical Energy .....	44
<hr/>		
<b>Chapter 4</b>	<b>DIRECT-CURRENT SERIES CIRCUITS .....</b>	<b>50</b>
	Voltage, Current, and Resistance in Series Circuits .....	50
	Polarity of Voltage Drops .....	53
	Conductors .....	53
	Total Power in a Series Circuit .....	57
	Voltage Drop by Proportional Parts .....	58

---

## CONTENTS

<b>Chapter 5</b>	<b>DIRECT-CURRENT PARALLEL CIRCUITS</b> .....	<b>69</b>
	Voltage and Current in a Parallel Circuit .....	69
	Resistances in Parallel .....	71
	Open and Short Circuits .....	74
	Division of Current in Two Parallel Branches .....	75
	Conductances in Parallel .....	75
	Power in Parallel Circuits .....	77
<hr/>		
<b>Chapter 6</b>	<b>BATTERIES</b> .....	<b>88</b>
	The Voltaic Cell .....	88
	Series and Parallel Cells .....	89
	Primary and Secondary Cells .....	90
	Types of Batteries .....	90
	Battery Characteristics .....	94
<hr/>		
<b>Chapter 7</b>	<b>KIRCHHOFF'S LAWS</b> .....	<b>101</b>
	Kirchhoff's Voltage Law (KVL) .....	101
	Kirchhoff's Current Law (KCL) .....	103
	Mesh Currents .....	104
	Node Voltages .....	106
<hr/>		
<b>Chapter 8</b>	<b>NETWORK CALCULATIONS</b> .....	<b>116</b>
	Y and Delta Networks .....	116
	Superposition .....	120
	Thevenin's Theorem .....	122
	Norton's Theorem .....	124
	Series-Parallel Circuits .....	126
	Wheatstone Bridge Circuit .....	128
	Maximum Power Transfer .....	129
	Line-Drop Calculations .....	130
	Three-Wire Distribution Systems .....	131
<hr/>		
<b>Chapter 9</b>	<b>MAGNETISM AND ELECTROMAGNETISM</b> .....	<b>162</b>
	The Nature of Magnetism .....	162
	Magnetic Materials .....	163
	Electromagnetism .....	164
	Magnetic Units .....	167
	<i>BH</i> Magnetization Curve .....	168
	Magnetic Circuits .....	170
	Electromagnetic Induction .....	172
	International System of Units .....	174
<hr/>		



## CONTENTS

<b>Chapter 10</b>	<b>DIRECT-CURRENT GENERATORS AND MOTORS</b> .....	<b>184</b>
	Motors and Generators .....	184
	Simple DC Generator .....	185
	Armature Windings .....	186
	Field Excitation .....	187
	DC Generator Equivalent Circuit .....	188
	Generator Voltage Equations and Voltage Regulation .....	189
	Losses and Efficiency of a DC Machine .....	189
	Direct-Current Motor .....	191
	DC Motor Equivalent Circuit .....	192
	Speed of a Motor .....	193
	Motor Types .....	194
	Starting Requirements for Motors .....	196
<hr/>		
<b>Chapter 11</b>	<b>PRINCIPLES OF ALTERNATING CURRENT</b> .....	<b>205</b>
	Generating an Alternating Voltage .....	205
	Angular Measurement .....	205
	Sine Wave .....	206
	Alternating Current .....	207
	Frequency and Period .....	208
	Phase Relationships .....	209
	Phasors .....	209
	Characteristic Values of Voltage and Current .....	211
	Resistance in AC Circuits .....	213
<hr/>		
<b>Chapter 12</b>	<b>INDUCTANCE, INDUCTIVE REACTANCE, AND INDUCTIVE CIRCUITS</b> .....	<b>225</b>
	Induction .....	225
	Characteristics of Coils .....	226
	Inductive Reactance .....	227
	Inductors in Series or Parallel .....	228
	Inductive Circuits .....	231
	Q of a Coil .....	237
	Power in RL Circuits .....	237
<hr/>		
<b>Chapter 13</b>	<b>CAPACITANCE, CAPACITIVE REACTANCE, AND CAPACITIVE CIRCUITS</b> .....	<b>251</b>
	Capacitor .....	251
	Capacitance .....	252
	Types of Capacitors .....	254
	Capacitors in Series and Parallel .....	254
	Capacitive Reactance .....	256
	Capacitive Circuits .....	257
	Power in RC Circuits .....	262
<hr/>		

## CONTENTS

<b>Chapter 14</b>	<b>SINGLE-PHASE CIRCUITS</b> .....	<b>275</b>
	The General RLC Circuit .....	275
	RLC in Series .....	275
	RLC in Parallel .....	278
	RL and RC Branches in Parallel .....	280
	Power and Power Factor .....	282
<hr/>		
<b>Chapter 15</b>	<b>ALTERNATING-CURRENT GENERATORS AND MOTORS</b> .....	<b>300</b>
	Alternators .....	300
	Paralleling Generators .....	302
	Ratings .....	303
	Losses and Efficiency .....	303
	Polyphase Induction Motors .....	303
	Synchronous Motors .....	306
	Single-Phase Motors .....	310
<hr/>		
<b>Chapter 16</b>	<b>TRANSFORMERS</b> .....	<b>322</b>
	Ideal Transformer Characteristics .....	322
	Transformer Ratings .....	325
	Impedance Ratio .....	326
	Autotransformer .....	326
	Transformer Losses and Efficiency .....	327
	No-Load Condition .....	328
	Coil Polarity .....	329
<hr/>		
<b>Chapter 17</b>	<b>THREE-PHASE SYSTEMS</b> .....	<b>339</b>
	Characteristics of Three-Phase Systems .....	339
	Three-Phase Transformer Connections .....	340
	Power in Balanced Three-Phase Loads .....	342
	Unbalanced Three-Phase Loads .....	346
<hr/>		
<b>Chapter 18</b>	<b>SERIES AND PARALLEL RESONANCE</b> .....	<b>362</b>
	Series Resonance .....	362
	Q of Series Circuit .....	365
	Parallel Resonance .....	366
	Q of Parallel Circuit .....	369
	Bandwidth and Power of Resonant Circuit .....	370
<hr/>		
<b>Chapter 19</b>	<b>WAVEFORMS AND TIME CONSTANTS</b> .....	<b>384</b>
	RL Series Circuit Waveforms .....	384
	RL Time Constants .....	388
	RC Series Circuit Waveforms .....	390
	RC Time Constants .....	393
	Calculation for Time $t$ .....	394
<hr/>		

*This page intentionally left blank*

## The Nature of Electricity

### STRUCTURE OF THE ATOM

*Matter* is anything that has mass and occupies space. Matter is composed of very small particles called *atoms*. All matter can be classified into either one of two groups: *elements* or *compounds*. In an element, all the atoms are the same. Examples of elements are aluminum, copper, carbon, germanium, and silicon. A compound is a combination of elements. Water, for example, is a compound consisting of the elements hydrogen and oxygen. The smallest particle of any compound that retains the original characteristics of that compound is called a *molecule*.

Atoms are composed of subatomic particles of *electrons*, *protons*, and *neutrons* in various combinations. The electron is the fundamental negative charge ( $-$ ) of electricity. Electrons revolve about the nucleus or center of the atom in paths of concentric "shells," or *orbits* (Fig. 1-1). The proton is the fundamental positive ( $+$ ) charge of electricity. Protons are found in the nucleus. The number of protons within the nucleus of any particular atom specifies the atomic number of that atom. For example, the silicon atom has 14 protons in its nucleus so the atomic number of silicon is 14. The neutron, which is the fundamental neutral charge of electricity, is also found in the nucleus.

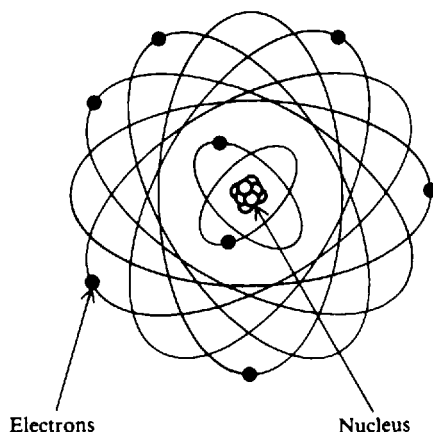


Fig. 1-1 Electrons and nucleus of an atom

Atoms of different elements differ from one another in the number of electrons and protons they contain (Fig. 1-2). In its natural state, an atom of any element contains an equal number of electrons and protons. Since the negative ( $-$ ) charge of each electron is equal in magnitude to the positive ( $+$ ) charge of each proton, the two opposite charges cancel. An atom in this condition is electrically neutral, or in balance (Fig. 1-2).

**Example 1.1** Describe the two simplest atoms.

The simplest atom is the hydrogen atom, which contains 1 proton in its nucleus balanced by 1 electron orbiting the nucleus (Fig. 1-2a). The next simplest atom is helium, which has 2 protons in its nucleus balanced by 2 electrons orbiting the nucleus (Fig. 1-2b).

A stable (neutral) atom has a certain amount of energy, which is equal to the sum of the energies of its electrons. Electrons, in turn, have different energies called *energy levels*. The energy level of an electron is proportional to its distance from the nucleus. Therefore, the energy levels of electrons in shells farther from the nucleus are higher than those of electrons in shells

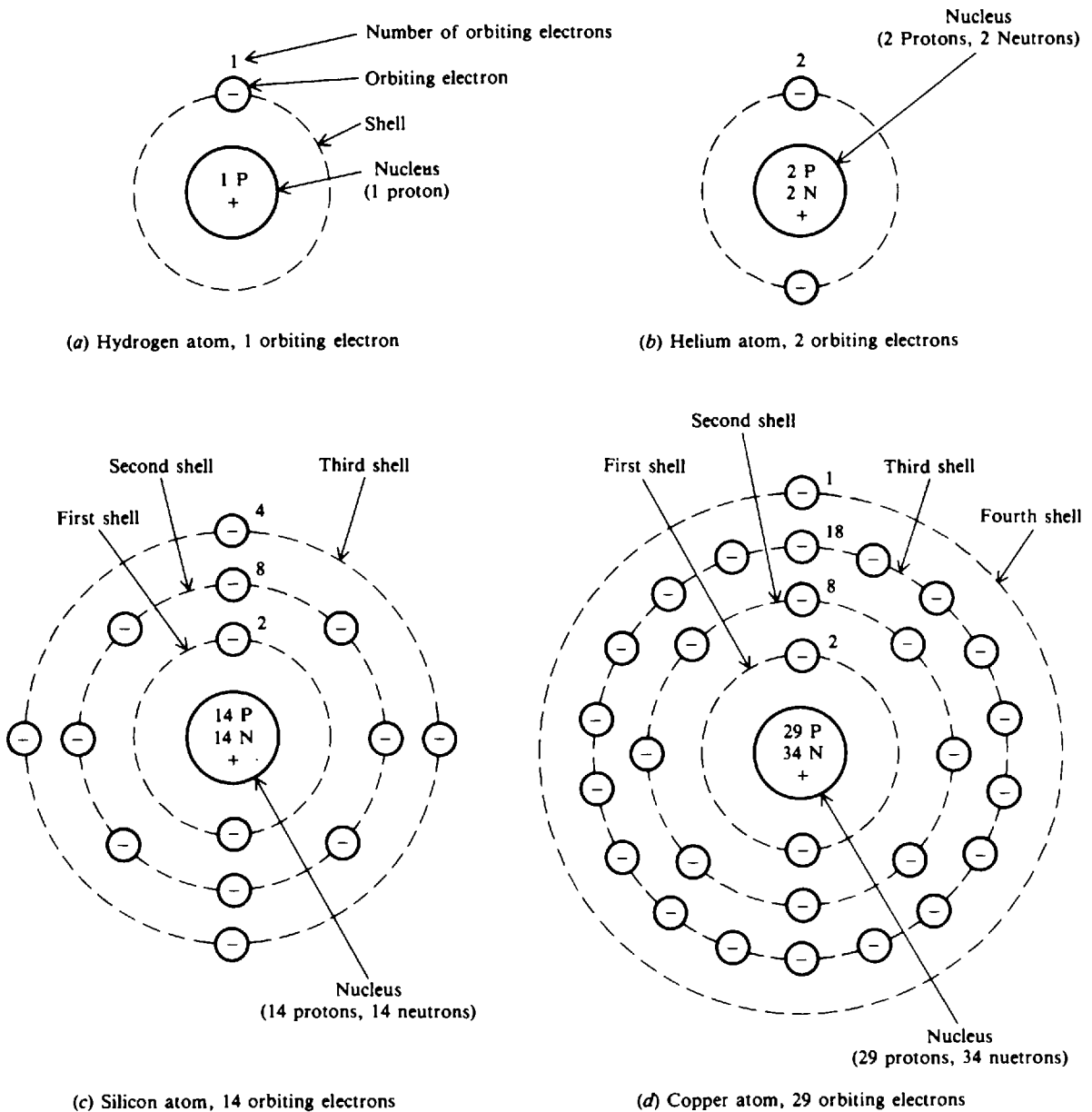


Fig. 1-2 Atomic structure of four common elements

nearer the nucleus. The electrons in the outermost shell are called *valence* electrons. When external energy such as heat, light, or electric energy is applied to certain materials, the electrons gain energy. This may cause the electrons to move to a higher energy level. An atom in which this has occurred is said to be in an *excited state*. An atom in an excited state is *unstable*.

When an electron has moved to the outermost shell of its atom, it is least attracted by the positive charges of the protons within the nucleus of its atom. If enough energy is then applied to the atom, some of the outermost shell or valence electrons will leave the atom. These electrons are called *free* electrons. It is the movement of free electrons that provides electric current in a metal conductor.

Each shell of an atom can contain only a certain maximum number of electrons. This number is called the *quota* of a shell. The orbiting electrons are in successive shells designated K, L, M, N, O, P, and Q at increasing distances outward from the nucleus. Each shell has a maximum number of electrons for stability (Fig. 1-3). After the K shell has been filled with 2 electrons, the L

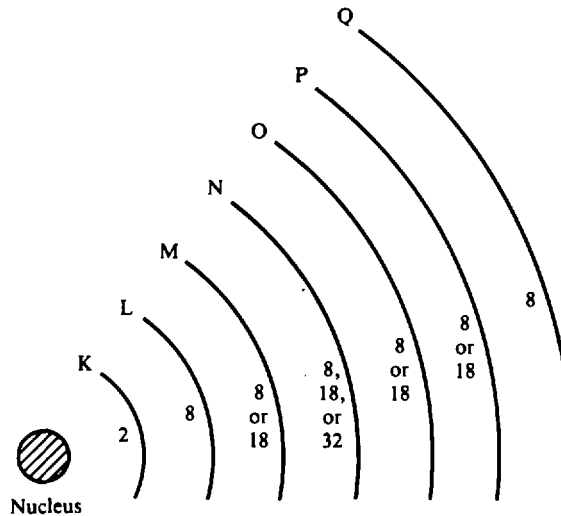


Fig. 1-3 Energy shells and the quota of electrons for each shell

shell can take up to 8 electrons. The maximum number of electrons in the remaining shells can be 8, 18, or 32 for different elements. The maximum for an outermost shell, though, is always 8.

**Example 1.2** Structure the copper atom by identifying its energy shells (Fig. 1-2d).

In the copper atom there are 29 protons in the nucleus balanced by 29 orbiting electrons. The 29 electrons fill the K shell with 2 electrons and the L shell with 8 electrons. The remaining 19 electrons then fill the M shell with 18 electrons, and the net result is 1 electron in the outermost N shell.

If the quota is filled in the outermost shell of an atom, an element made up of such atoms is said to be *inert*. When the K shell is filled with 2 electrons, we have the inert gas helium (Fig. 1-2b). When the outer shell of an atom lacks its quota of electrons, it is capable of gaining or losing electrons. If an atom loses one or more electrons in its outer shell, the protons outnumber the electrons so that the atom carries a net positive electric charge. In this condition, the atom is called a *positive ion*. If an atom gains electrons, its net electric charge becomes negative. The atom then is called a *negative ion*. The process by which atoms either gain or lose electrons is called *ionization*.

**Example 1.3** Describe what happens to the copper atom when it loses an electron from its outermost shell. The copper atom becomes a positive ion with a net charge of +1.

## THE ELECTRIC CHARGE

Since some atoms can lose electrons and other atoms can gain electrons, it is possible to cause a transfer of electrons from one object to another. When this takes place, the equal distribution of the positive and negative charges in each object no longer exists. Therefore, one object will contain an excess number of electrons and its charge must have a negative, or minus (−), electric polarity. The other object will contain an excess number of protons and its charge must have a positive, or plus (+), polarity.

When a pair of objects contains the same charge, that is, both positive (+) or both negative (−), the objects are said to have like charges. When a pair of bodies contains different charges, that is, one body is positive (+) while the other body is negative (−), they are said to have unlike or opposite charges. The law of electric charges may be stated as follows:

Like charges repel each other; unlike charges attract each other.

If a negative (–) charge is placed next to another negative (–) charge, the charges will repel each other (Fig. 1-4a). If a positive (+) charge is placed next to a negative (–) charge, they will be drawn together (Fig. 1-4c).

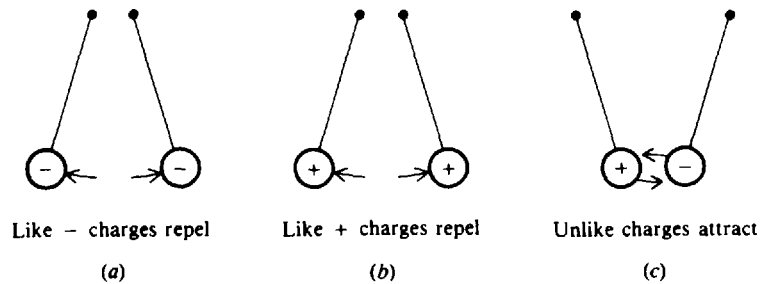


Fig. 1-4 Force between charges

### THE COULOMB

The magnitude of electric charge a body possesses is determined by the number of electrons compared with the number of protons within the body. The symbol for the magnitude of the electric charge is  $Q$ , expressed in units of coulombs (C). A charge of one negative coulomb,  $-Q$ , means a body contains a charge of  $6.25 \times 10^{18}$  more electrons than protons.\*

**Example 1.4** What is the meaning of  $+Q$ ?

A charge of one positive coulomb means a body contains a charge of  $6.25 \times 10^{18}$  more protons than electrons.

**Example 1.5** A dielectric material has a negative charge of  $12.5 \times 10^{18}$  electrons. What is its charge in coulombs?

Since the number of electrons is double the charge of 1 C ( $1 \text{ C} = 6.25 \times 10^{18}$  electrons),  $-Q = 2 \text{ C}$ .

### THE ELECTROSTATIC FIELD

The fundamental characteristic of an electric charge is its ability to exert a force. This force is present within the electrostatic field surrounding every charged object. When two objects of opposite polarity are brought near each other, the electrostatic field is concentrated in the area between them (Fig. 1-5). The electric field is indicated by lines of force drawn between the two objects. If an electron is released at point A in this field, it will be repelled by the negative charge

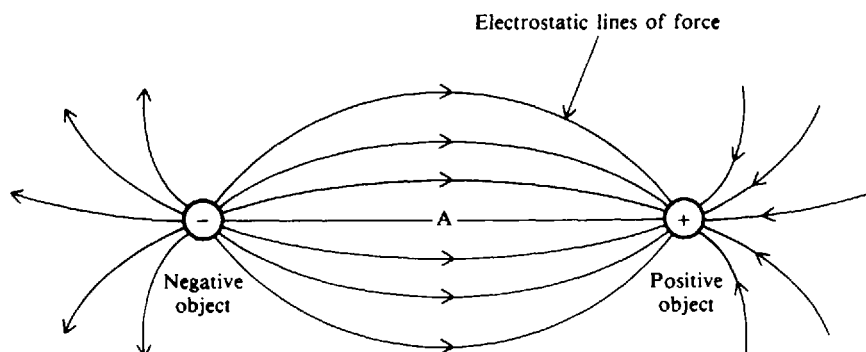



Fig. 1-5 The electrostatic field between two charges of opposite polarity

\*See page 16 for an explanation of how to use powers of 10.

and will be attracted to the positive one. Thus both charges will tend to move the electron in the direction of the lines of force between the two objects. The arrowheads in Fig. 1-5 indicate the direction of motion that would be taken by the electron if it were in different areas of the electrostatic field.

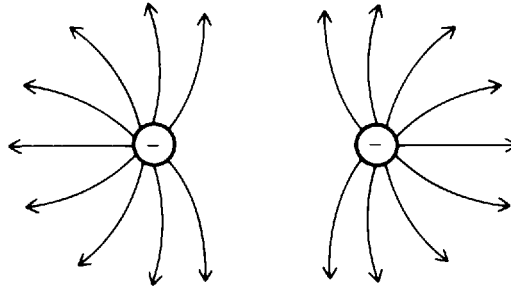**Example 1.6** Draw the electrostatic field that would exist between two negatively charged objects.

When two like charges are placed near each other, the lines of force repel each other as shown below.



A charged object will retain its charge temporarily if there is no immediate transfer of electrons to or from it. In this condition, the charge is said to be *at rest*. Electricity at rest is called *static* electricity.

## POTENTIAL DIFFERENCE

Because of the force of its electrostatic field, an electric charge has the ability to do the work of moving another charge by attraction or repulsion. The ability of a charge to do work is called its *potential*. When one charge is different from the other, there must be a difference in potential between them.

The sum of the differences of potential of all the charges in the electrostatic field is referred to as *electromotive force* (emf).

The basic unit of potential difference is the *volt* (V). The symbol for potential difference is *V*, indicating the ability to do the work of forcing electrons to move. Because the volt unit is used, potential difference is called *voltage*.

**Example 1.7** What is the meaning of a battery voltage output of 6 V?

A voltage output of 6 V means that the potential difference between the two terminals of the battery is 6 V. Thus, voltage is fundamentally the potential difference between two points.

## CURRENT

The movement or the flow of electrons is called *current*. To produce current, the electrons must be moved by a potential difference. Current is represented by the letter symbol *I*. The basic unit in which current is measured is the ampere (A). One ampere of current is defined as the movement of one coulomb past any point of a conductor during one second of time.

**Example 1.8** If a current of 2 A flows through a meter for 1 minute (min), how many coulombs pass through the meter?

1 A is 1 C per second (C/s). 2 A is 2 C/s. Since there are 60 s in 1 min,  $60 \times 2 \text{ C} = 120 \text{ C}$  pass through the meter in 1 min.

The definition of current can be expressed as an equation:

$$I = \frac{Q}{T} \quad (1-1)$$



where  $I$  = current, A  
 $Q$  = charge, C  
 $T$  = time, s

or 
$$Q = I \times T = IT \quad (1-2)$$

Charge differs from current in that  $Q$  is an accumulation of charge, while  $I$  measures the intensity of moving charges.

**Example 1.9** Find the answer to Example 1.8 by using Eq. (1-2).

Write down the known values:

$$I = 2 \text{ A} \quad T = 60 \text{ s}$$

Write down the unknown:

$$Q = ?$$

Use Eq. (1-2) to solve for the unknown:

$$Q = I \times T$$

Substitute  $I = 2 \text{ A}$  and  $T = 60 \text{ s}$ :


$$Q = (2 \text{ A}) \times (60 \text{ s})$$

Solve for  $Q$ :

$$Q = 120 \text{ C} \quad \text{Ans.}$$
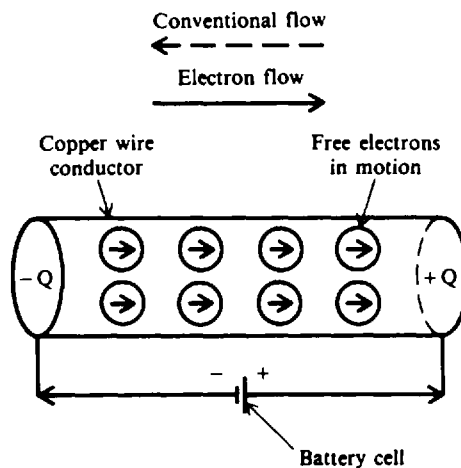
## CURRENT FLOW

In a conductor, such as copper wire, the free electrons are charges that can be forced to move with relative ease by a potential difference. If a potential difference is connected across two ends of a copper wire (Fig. 1-6), the applied voltage (1.5 V) forces the free electrons to move. This current is a drift of electrons from the point of negative charge,  $-Q$ , at one end of the wire, moving through the wire, and returning to the positive charge,  $+Q$ , at the other end. The direction of the electron drift is from the negative side of the battery, through the wire, and back to the positive side of the battery. The direction of electron flow is from a point of negative potential to a point of positive potential. The solid arrow (Fig. 1-6) indicates the direction of current in terms of



Potential difference = 1.5 V

**Fig. 1-6** Potential difference across two ends of a wire conductor causes electric current

electron flow. The direction of moving positive charges, opposite from electron flow, is considered the *conventional flow* of current and is indicated by the dashed arrow (Fig. 1-6). In basic electricity, circuits are usually analyzed in terms of conventional current because a positive potential is considered before a negative potential. Therefore, the direction of conventional current is the direction of positive charges in motion. Any circuit can be analyzed by either electron flow or conventional flow in the opposite direction. In this book current is always considered as conventional flow.

## SOURCES OF ELECTRICITY

### Chemical Battery

A voltaic chemical cell is a combination of materials which are used for converting chemical energy into electric energy. A battery is formed when two or more cells are connected. A chemical reaction produces opposite charges on two dissimilar metals, which serve as the negative and positive terminals (Fig. 1-7). The metals are in contact with an electrolyte.

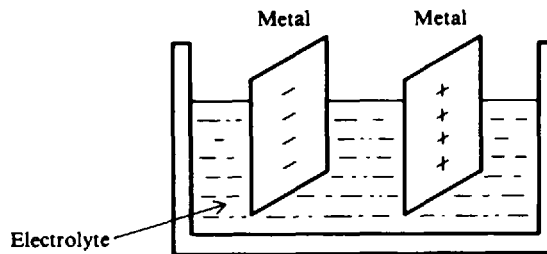


Fig. 1-7 Voltaic chemical cell

### Generator

The generator is a machine in which electromagnetic inductance is used to produce a voltage by rotating coils of wire through a stationary magnetic field or by rotating a magnetic field through stationary coils of wire. Today more than 95 percent of the world's energy is produced by generators.

### Thermal Energy

The production of most electric energy begins with the formation of heat energy. Coal, oil, or natural gas can be burned to release large quantities of heat. Once heat energy is available, conversion to mechanical energy is the next step. Water is heated to produce steam, which is then used to turn the turbines that drive the electric generators. A *direct* conversion from heat energy to electric energy will increase efficiency and reduce thermal pollution of water resources and the atmosphere.

### Magnetohydrodynamic (MHD) Conversion

In an MHD converter, gases are ionized by very high temperatures, approximately 3000 degrees Fahrenheit (3000°F), or 1650 degrees Celsius (1650°C). The hot gases pass through a strong magnetic field with current resulting. The exhausted gases are then moved back to the heat source to form a complete cycle (Fig. 1-8). MHD converters have no mechanical moving parts.

### Thermionic Emission

The thermionic energy converter is a device that consists of two electrodes in a vacuum. The emitter electrode is heated and produces free electrons. The collector electrode is maintained at a much lower temperature and receives the electrons released at the emitter.

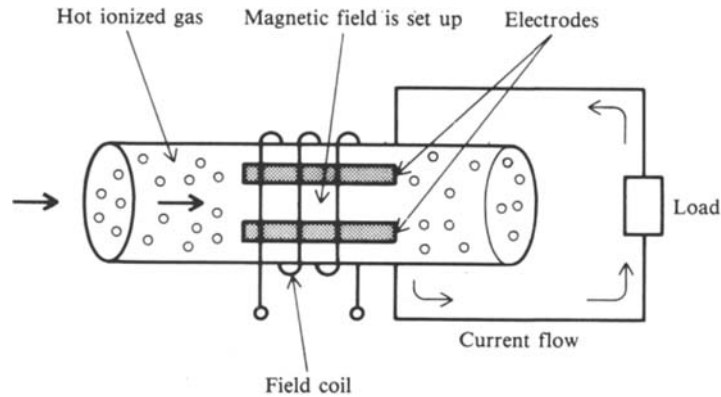


Fig. 1-8 Principles of MHD converter

### Solar Cells

Solar cells convert light energy directly into electric energy. They consist of semiconductor material like silicon and are used in large arrays in spacecraft to recharge batteries. Solar cells are also used in home heating.

### Piezoelectric Effect

Certain crystals, such as quartz and Rochelle salts, generate a voltage when they are vibrated mechanically. This action is known as the *piezoelectric effect*. One example is the crystal phonograph cartridge, which contains a Rochelle salt crystal to which a needle is fastened. As the needle moves in the grooves of a record, it swings from side to side. This mechanical motion is applied to the crystal, and a voltage is then generated.

### Photoelectric Effect

Some materials, such as zinc, potassium, and cesium oxide, emit electrons when light strikes their surfaces. This action is known as the *photoelectric effect*. Common applications of photoelectricity are television camera tubes and photoelectric cells.

### Thermocouples

If wires of two different metals, such as iron and copper, are welded together and the joint is heated, the difference in electron activity in the two metals produces an emf across the joint. Thermocouple junctions can be used to measure the amount of current because current acts to heat the junction.

## DIRECT AND ALTERNATING CURRENTS AND VOLTAGES

Direct current (dc) is current that moves through a conductor or circuit in one direction only (Fig. 1-9a). The reason for the unidirectional current is that voltage sources such as cells and batteries maintain the same polarity of output voltage (Fig. 1-9b). The voltage supplied by these sources is called *direct-current voltage*, or simply *dc voltage*. A dc voltage source can change the amount of its output voltage, but if the same polarity is maintained, direct current will flow in one direction only.


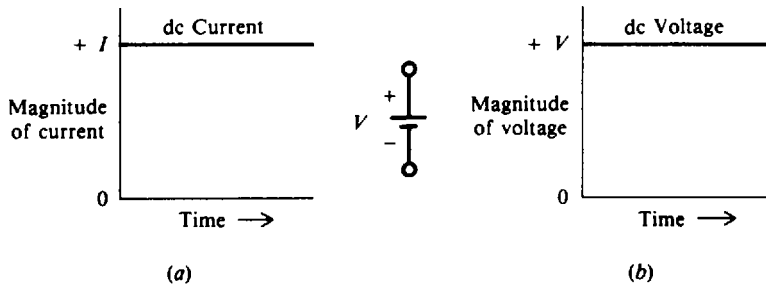


Fig. 1-9 Waveforms of a constant dc current and dc voltage

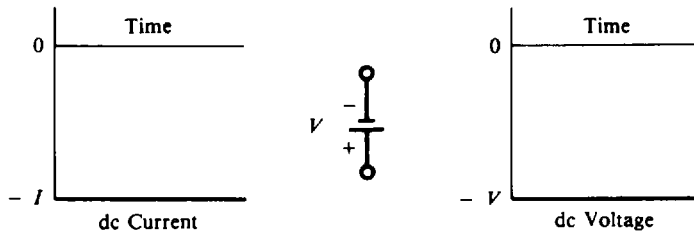**Example 1.10** Assuming the polarity of the battery were reversed in Fig. 1-9b, draw the new curves of current and voltage.

With polarity reversed, the current will now flow in the opposite direction. The curves would then appear as follows:



An alternating-current voltage (ac voltage) source periodically reverses or alternates in polarity (Fig. 1-10a). Therefore, the resulting alternating current also periodically reverses direction (Fig. 1-10b). In terms of conventional flow, the current flows from the positive terminal of the voltage source, through the circuit, and back to the negative terminal, but when the generator alternates in polarity, the current must reverse its direction. The ac power line used in most homes is a common example. The voltage and current direction go through many reversals each second in these systems.

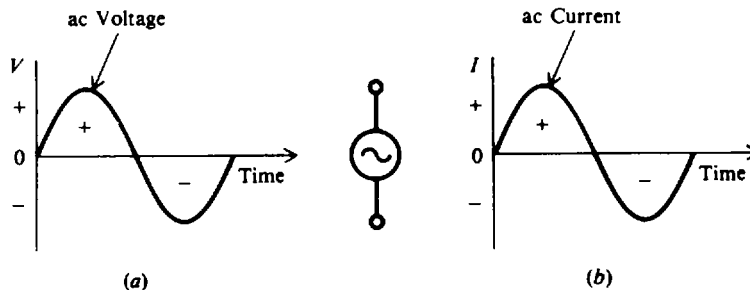


Fig. 1-10 Waveforms of ac voltage and ac current

### Solved Problems

1.1 Match each term in column 1 to its closest meaning in column 2.

Column 1	Column 2
1. Electron	(a) Positive charge
2. Neutron	(b) Same number of electrons and protons
3. Compound	(c) Electrons in first shell
4. Neutral	(d) Released electrons
5. Valence electrons	(e) Neutral charge
6. Atomic number	(f) Electrons in outermost shell
7. Free electrons	(g) Quota filled in outermost shell
8. K shell	(h) Number of electrons in nucleus
9. Ion	(i) Negative charge
10. Inert	(j) Quota of 2 electrons
	(k) Combined elements
	(l) Number of protons in nucleus
	(m) Charged atom

Ans. 1. (i) 2. (e) 3. (k) 4. (b) 5. (f) 6. (l) 7. (d) 8. (j) 9. (m) 10. (g)

1.2 Show the atomic structure of the element aluminum with atomic number 13. What is its electron valence?

Because aluminum has 13 protons in the nucleus, it must have 13 orbiting electrons to be electrically neutral. Starting with the innermost shells (Fig. 1-3), we have

K shell	2 electrons
L shell	8 electrons
M shell	3 electrons
Total	13 electrons

The atomic structure for aluminum then is shown in Fig. 1-11. Its electron valence is  $-3$  because it has 3 valence electrons.

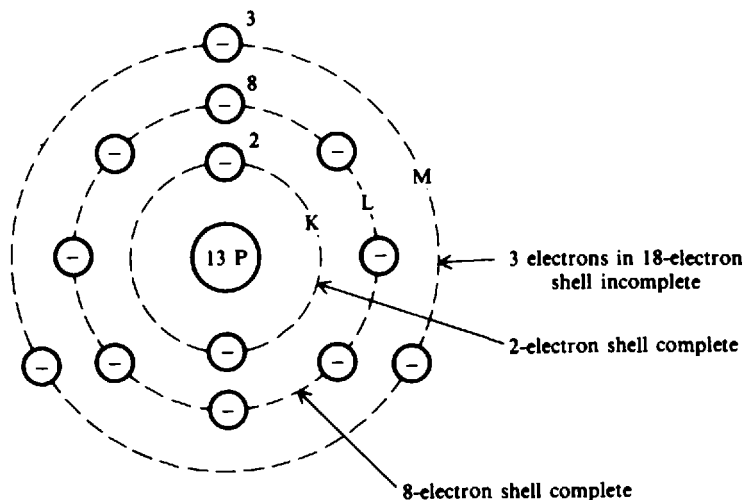


Fig. 1-11

- 1.3 In observing the maximum number of electrons in shells K, L, M, and N in Fig. 1-3, you will find that they are 2, 8, 18, and 32 electrons, respectively. Develop a formula that describes this relationship, where  $n$  is the shell number in sequential order outward from the nucleus.

The formula is  $2n^2$  because the maximum number of electrons in the

K or first shell ( $n = 1$ ) is  $2(1^2) = 2(1) = 2$

L or second shell ( $n = 2$ ) is  $2(2^2) = 2(4) = 8$

M or third shell ( $n = 3$ ) is  $2(3^2) = 2(9) = 18$

N or fourth shell ( $n = 4$ ) is  $2(4^2) = 2(16) = 32$

This relationship is true for most elements.

- 1.4 What is the net charge of a body that contains 8 protons and 4 electrons?

The numerical value of the net charge is found by subtracting the number of one type of charge from the number of the other type. So a positive charge of 8 (+8) and a negative charge of 4 (-4) yields a positive charge of 4 (+4).

- 1.5 A charged insulator has a deficiency of  $50 \times 10^{18}$  electrons. Find its charge in coulombs with polarity.

Since  $1 \text{ C} = 6.25 \times 10^{18}$  electrons,  $8 \text{ C} = 50 \times 10^{18}$  electrons. Deficiency of electrons means an excess of protons. So the insulator has a positive charge of 8 C, or  $+Q = 8 \text{ C}$ .

- 1.6 Write the word which most correctly completes each of the following statements:

- (a) A rubber rod repels a second rubber rod, so both rods have \_\_\_\_\_ charges.  
 (b) Glass rubbed with silk attracts rubber rubbed with fur. If the rubber rod is negative, the glass rod must be \_\_\_\_\_.

(a) like (law of charges); (b) positive (law of charges)

- 1.7 Find the current needed to charge a dielectric so that it will accumulate a charge of 20 C after 4 s.

Known values:  $Q = 20 \text{ C}$ ;  $T = 4 \text{ s}$

Unknown:  $I = ?$

Use Eq. (1-1) to find  $I$ :

$$I = \frac{Q}{T} = \frac{20 \text{ C}}{4 \text{ s}} = 5 \text{ A} \quad \text{Ans.}$$

- 1.8 A current of 8 A charges an insulator for 3 s. How much charge is accumulated?

Known values:  $I = 8 \text{ A}$ ;  $T = 3 \text{ s}$

Unknown:  $Q = ?$

Use Eq. (1-2) to find  $Q$ :

$$Q = IT = (8 \text{ A})(3 \text{ s}) = 24 \text{ C} \quad \text{Ans.}$$

- 1.9 Write the word or words which most correctly complete each of the following statements.

- (a) The ability of a charge to do work is its \_\_\_\_\_.

- (b) When one charge is different from the other, there is a \_\_\_\_\_ of \_\_\_\_\_.
- (c) The unit of potential difference is the \_\_\_\_\_.
- (d) The sum of potential differences of all charges is called \_\_\_\_\_.
- (e) The movement of charges produces \_\_\_\_\_.
- (f) A greater amount of moving charges means a \_\_\_\_\_ value for the current.
- (g) When the potential difference is zero, the value of current is \_\_\_\_\_.
- (h) The rate of flow of charge is called \_\_\_\_\_.
- (i) The direction of the conventional flow of current is from a point of \_\_\_\_\_ potential to a point of \_\_\_\_\_ potential.
- (j) Electron flow is opposite in direction to \_\_\_\_\_ flow.
- (k) Direct current (dc) has just \_\_\_\_\_ direction.
- (l) A \_\_\_\_\_ is an example of a dc voltage source.
- (m) An alternating current (ac) \_\_\_\_\_ its polarity.

- Ans. (a) potential (h) current  
 (b) difference, potential (i) positive, negative  
 (c) volt (j) conventional  
 (d) electromotive force (k) one  
 (e) current (l) battery  
 (f) higher (m) reverses  
 (g) zero

**1.10 Match each device in column 1 to its closest principle in column 2.**

Column 1	Column 2
1. Battery	(a) Electromagnetic induction
2. Generator	(b) Free electrons
3. TV camera tube	(c) Ionized gases
4. Vacuum tube	(d) Chemical reaction
5. Phonograph needle	(e) Thermal energy
	(f) Photoelectricity
	(g) Mechanical motion

- Ans. 1. (d) 2. (a) 3. (f) 4. (b) 5. (g)

## Supplementary Problems

1.11 Match each term in column 1 to its closest meaning in column 2.

Column 1	Column 2
1. Proton	(a) Negative charge
2. Molecule	(b) Quota of 8 electrons
3. Quota	(c) Excited state
4. L shell	(d) Maximum number of electrons in a shell
5. Element	(e) Atom negatively charged
6. Unstable	(f) Positive charge
7. Shell	(g) Mass and volume
8. Copper	(h) Atomic number is 29
9. Negative ion	(i) Quota of 18 electrons
10. Matter	(j) Orbit
	(k) Smallest particle having same characteristics
	(l) Atomic number is 14
	(m) All atoms the same

*Ans.* 1. (f) 2. (k) 3. (d) 4. (b) 5. (m) 6. (c) 7. (j) 8. (h) 9. (e) 10. (g)

1.12 Write the word or words which most correctly complete each of the following statements.

- (a) Electrons move about the nucleus of an atom in paths which are called \_\_\_\_\_.
- (b) The nucleus of an atom consists of particles called \_\_\_\_\_ and \_\_\_\_\_.
- (c) The number of protons in the nucleus of an atom is known as the \_\_\_\_\_ of that atom.
- (d) When all the atoms within a substance are alike, the substance is called a chemical \_\_\_\_\_.
- (e) A \_\_\_\_\_ is the smallest particle of a compound which retains all the properties of that compound.
- (f) The energy \_\_\_\_\_ of an electron is determined by its distance from the nucleus of an atom.
- (g) If a neutral atom gains electrons, it becomes a \_\_\_\_\_ ion.
- (h) If a neutral atom loses electrons, it becomes a \_\_\_\_\_ ion.
- (i) Unlike charges \_\_\_\_\_ each other, while like charges \_\_\_\_\_ each other.
- (j) A charged object is surrounded by an \_\_\_\_\_ field.

*Ans.* (a) shells or orbits (f) level  
 (b) protons, neutrons (g) negative  
 (c) atomic number (h) positive  
 (d) element (i) attract, repel  
 (e) molecule (j) electrostatic

1.13 Show the atomic structure of the element phosphorus, which has an atomic number of 15. What is its electron valence? *Ans.* See Fig. 1-12. Electron valence is  $-5$ .

1.14 Show the atomic structure of the element neon, which has an atomic number of 10. What is its electron valence? *Ans.* See Fig. 1-13. Electron valence is 0. Thus, neon is inert.

1.15 What is the net charge if 13 electrons are added to 12 protons? *Ans.*  $-1$  electron



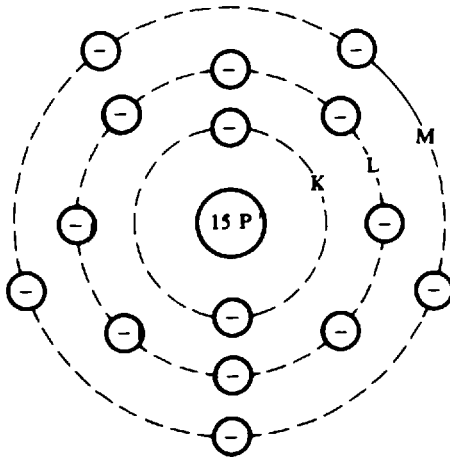


Fig. 1-12

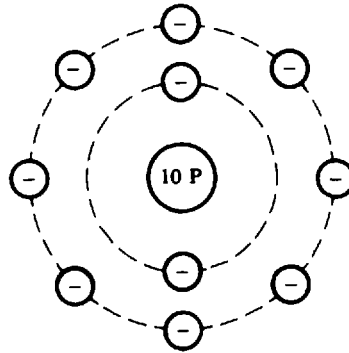


Fig. 1-13

- 1.16 What becomes of the silicon atom when it loses all the orbiting electrons in its outermost shell?  
*Ans.* It becomes a negative ion with a net charge of  $-4$ . See Fig. 1-2c.
- 1.17 A charged insulator has an excess of  $25 \times 10^{18}$  electrons. Find its charge in coulombs with polarity.  
*Ans.*  $-Q = 4 \text{ C}$
- 1.18 A material with an excess of  $25 \times 10^{18}$  electrons loses  $6.25 \times 10^{18}$  electrons. The excess electrons are then made to flow past a given point in 2 s. Find the current produced by the resultant electron flow. *Ans.*  $I = 1.5 \text{ A}$
- 1.19 A charge of 10 C flows past a given point every 2 s. What is the current? *Ans.*  $I = 5 \text{ A}$
- 1.20 How much charge is accumulated when a current of 5 A charges an insulator for 5 s?  
*Ans.*  $Q = 25 \text{ C}$
- 1.21 Match each item in section 1 with its application in section 2.

## Section 1

1. Water
2. Cesium oxide
3. Silicon
4. Quartz
5. Carbon-zinc
6. Iron-copper

## Section 2

- (a) Solar cell
- (b) Generator
- (c) Battery
- (d) Crystal oscillator
- (e) Photoelectric cell
- (f) Turbine
- (g) MHD converter
- (h) Thermocouple

*Ans.* 1. (f) 2. (e) 3. (a) 4. (d) 5. (c) 6. (h)

- 1.22 Fill in the missing quantity:

	$I, \text{ A}$	$Q, \text{ C}$	$T, \text{ s}$
(a)	?	10	2
(b)	5	?	4
(c)	?	9	2
(d)	7	?	3
(e)	2	6	?

*Ans.*

	$I, \text{ A}$	$Q, \text{ C}$	$T, \text{ s}$
(a)	5	....	....
(b)	....	20	....
(c)	4.5	....	....
(d)	....	21	....
(e)	....	....	3

# Chapter 2

## Electrical Standards and Conventions

### Units

#### INTRODUCTION

The international metric system of units or dimensions, commonly called SI, is used in electricity. The abbreviation SI stands for *système internationale*. The seven base units of SI are length, mass, time, electric current, thermodynamic temperature, light intensity, and amount of substance (Table 2-1). Formerly the MKS metric system was used, where M stands for meter (length), K for kilogram (mass), and S for seconds (time). The two supplementary units of SI are plane angle and solid angle (Table 2-2).

**Table 2-1 Base Units of the International Metric System**

Quantity	Base Unit	Symbol
Length	meter	m
Mass	kilogram	kg
Time	second	s
Electric current	ampere	A
Thermodynamic temperature	kelvin	K
Light intensity	candela	cd
Amount of substance	mole	mol

**Table 2-2 Supplementary SI Units**

Quantity	Unit	Symbol
Plane angle	radian	rad
Solid angle	steradian	sr

Other common units can be derived from the base and supplementary units. For example, the unit of charge is the coulomb, which is derived from the base units of second and ampere. Most of the units that are used in electricity are derived ones (Table 2-3).

#### METRIC PREFIXES

In the study of basic electricity, some electrical units are too small or too large to express conveniently. For example, in the case of resistance, we often use values in thousands or millions of ohms ( $\Omega$ ). The prefix *kilo* (denoted by the letter k) is a convenient way of expressing a thousand. Thus, instead of saying a resistor has a value of 10 000  $\Omega$ , we normally refer to it as a 10-kilohm (10-k $\Omega$ ) resistor. In the case of current, we often use values in thousandths or millionths of an ampere. We use expressions such as milliamperes and microamperes. The prefix

*milli* is a short way of saying a thousandth and *micro* is a short way of saying a millionth. Thus 0.012 A becomes 12 milliamperes (mA) and 0.000 005 A becomes 5 microamperes ( $\mu$ A). Table 2-4 lists the metric prefixes commonly used in electricity and their numerical equivalents.

**Table 2-3 Derived SI Units**

Quantity	Unit	Symbol
Energy	joule	J
Force	newton	N
Power	watt	W
Electric charge	coulomb	C
Electric potential	volt	V
Electric resistance	ohm	$\Omega$
Electric conductance	siemens	S
Electric capacitance	farad	F
Electric inductance	henry	H
Frequency	hertz	Hz
Magnetic flux	weber	Wb
Magnetic flux density	tesla	T

**Table 2-4 Metric Prefixes Used in Electricity**

Prefix (Letter Symbol)	Value		Pronunciation
mega (M)	million	1 000 000	as in <i>megaphone</i>
kilo (k)	thousand	1 000	kill'oh
milli(m)	thousandth	0.001	as in <i>military</i>
micro ( $\mu$ )	millionth	0.000 001	as in <i>microphone</i>
nano (n)	thousand-millionth	0.000 000 001	nan'oh
pico (p)	million-millionth	0.000 000 000 001	peek'oh

**Example 2.1** A resistor has a value of 10 M stamped on its case. How many ohms of resistance does this resistor have?

The letter M denotes mega, or million. Thus the resistor has a value of 10 megohms (M $\Omega$ ) or 10 million ohms.

**Example 2.2** A power station has a capacity of delivering 500 000 watts (W). What is the capacity in kilowatts (kW)?

Refer to Table 2-4. Kilo stands for 1000. Thus, 500 000 W = 500 kW.

## POWERS OF 10

We have seen that it is often necessary or desirable to convert one unit of measurement to another unit that may be larger or smaller. In the previous section we did this by substituting a metric prefix for certain values. Another way would be to convert the number to a power of 10. Powers of 10 are often termed the "engineer's shorthand." Examples of expressing numbers as powers of 10 are shown in Table 2-5.

Table 2-5 Powers of 10

Number	Power of 10	Commonly Read As
0.000 001 =	$10^{-6}$	10 to the minus sixth
0.000 01 =	$10^{-5}$	10 to the minus fifth
0.000 1 =	$10^{-4}$	10 to the minus fourth
0.001 =	$10^{-3}$	10 to the minus third
0.01 =	$10^{-2}$	10 to the minus second
0.1 =	$10^{-1}$	10 to the minus one
1 =	$10^0$	10 to the zero
10 =	$10^1$	10 to the first
100 =	$10^2$	10 squared
1 000 =	$10^3$	10 cubed
10 000 =	$10^4$	10 to the fourth
100 000 =	$10^5$	10 to the fifth
1 000 000 =	$10^6$	10 to the sixth

**Rule 1:** To express numbers *larger* than 1 as a small number times a power of 10, move the decimal point to the *left* as many places as desired. Then multiply the number obtained by 10 to a power which is equal to the number of places moved.

**Example 2.3**

$$\begin{aligned}
 3000 &= \underbrace{3.000}_{\leftarrow} && \text{(Decimal point is moved three places to the left.)} \\
 &= 3 \times 10^3 && \text{(Therefore the power, or exponent, is 3.)} \\
 6500 &= \underbrace{65.00}_{\leftarrow} && \text{(Decimal point is moved two places to the left.)} \\
 &= 65 \times 10^2 && \text{(Therefore the exponent is 2.)} \\
 880\,000 &= \underbrace{88.0000}_{\leftarrow} && \text{(Decimal point is moved left four places.)} \\
 &= 88 \times 10^4 && \text{(Therefore the exponent is 4.)} \\
 42.56 &= \underbrace{4.2}_{\leftarrow}56 && \text{(Decimal point is moved left one place.)} \\
 &= 4.256 \times 10 && \text{(Therefore the exponent is 1.)}
 \end{aligned}$$

**Rule 2:** To express numbers *less* than 1 as a whole number times a power of 10, move the decimal point to the *right* as many places as desired. Then multiply the number obtained by 10 to a *negative* power which is equal to the number of places moved.

**Example 2.4**

$$\begin{aligned}
 0.006 &= \underbrace{0.006}_{\rightarrow} && \text{(Decimal point is moved three places to the right.)} \\
 &= 6 \times 10^{-3} && \text{(Therefore the power or exponent is } -3\text{.)} \\
 0.435 &= \underbrace{0.435}_{\rightarrow} && \text{(Decimal point is moved one place to the right.)} \\
 &= 4.35 \times 10^{-1} && \text{(Therefore the exponent is } -1\text{.)} \\
 0.000\,92 &= \underbrace{0.000\,92}_{\rightarrow} && \text{(Decimal point is moved right five places.)} \\
 &= 92 \times 10^{-5} && \text{(Therefore the exponent is } -5\text{.)} \\
 0.578 &= \underbrace{0.578}_{\rightarrow} && \text{(Decimal point is moved right two places.)} \\
 &= 57.8 \times 10^{-2} && \text{(Therefore the exponent is } -2\text{.)}
 \end{aligned}$$

**Rule 3:** To convert a number expressed as a positive power of 10 to a decimal number, move the decimal point to the *right* as many places as the value of the exponent.

**Example 2.5**

$$0.615 \times 10^3 = \underline{0.615}_{\circlearrowright 3} \quad (\text{The exponent is 3. Therefore move the decimal point three places to the right.})$$

$$= 615$$

$$0.615 \times 10^6 = \underline{0.615\ 000}_{\circlearrowright 6} \quad (\text{Move the decimal point six places to the right.})$$

$$= 615\ 000$$

$$0.0049 \times 10^3 = \underline{0.0049}_{\circlearrowright 3} \quad (\text{Move decimal point right three places.})$$

$$= 4.9$$

$$84 \times 10^2 = \underline{84.00}_{\circlearrowright 2} \quad (\text{Move decimal point right two places.})$$

$$= 8400$$

**Rule 4:** To convert a number expressed as a negative power of 10 to a decimal number, move the decimal point to the *left* as many places as the value of the exponent.

**Example 2.6**

$$70 \times 10^{-3} = \underline{0.070}_{\circlearrowleft 3} \quad (\text{The exponent is } -3. \text{ Therefore move the decimal point three places to the left.})$$

$$= 0.07$$

$$82.4 \times 10^{-2} = \underline{0.824}_{\circlearrowleft 2} \quad (\text{Move decimal point left two places.})$$

$$= 0.824$$

$$60\ 000 \times 10^{-6} = \underline{0.060\ 000}_{\circlearrowleft 6} \quad (\text{Move decimal point left six places.})$$

$$= 0.06$$

$$0.5 \times 10^{-3} = \underline{0.0005}_{\circlearrowleft 3} \quad (\text{Move decimal point left three places.})$$

$$= 0.0005$$

**Rule 5:** To multiply two or more numbers expressed as powers of 10, *multiply* the coefficients to obtain the new coefficient and *add* the exponents to obtain the new exponent of 10.

**Example 2.7**

$$10^2 \times 10^4 = 10^{2+4} = 10^6 \quad \text{Ans.}$$

$$10^{-1} \times 10^4 = 10^{-1+4} = 10^3 \quad \text{Ans.}$$

$$(40 \times 10^3)(25 \times 10^2) = 40 \times 25 \times 10^3 \times 10^2 \quad (40 \times 25 = 1000, 3 + 2 = 5)$$

$$= 1000 \times 10^5 \quad (\text{But } 1000 = 10^3)$$

$$= 10^3 \times 10^5$$

$$= 10^8 \quad \text{Ans.}$$

$$(2 \times 10^{-2})(50 \times 10^2) = 2 \times 50 \times 10^{-2} \times 10^2$$

$$= 100 \times 10^0 \quad (\text{But } 100 = 10^2)$$

$$= 10^2 \times 1 \quad (10^0 = 1)$$

$$= 10^2 \quad \text{Ans.}$$

$$(3 \times 10^{-4})(6 \times 10^6) = 3 \times 6 \times 10^{-4} \times 10^6$$

$$= 18 \times 10^2 \quad \text{Ans.}$$

**Rule 6:** To divide by powers of 10, use the formula

$$\frac{1}{10^n} = 1 \times 10^{-n}$$

We therefore can transfer any power of 10 from numerator to denominator, or vice versa, simply by changing the sign of the exponent.

**Example 2.8**

$$\frac{15}{10^{-1}} = 15 \times 10^1 = 150 \qquad \frac{1500}{10^4} = 1500 \times 10^{-4} = 0.15$$

$$\frac{15}{10^{-3}} = 15 \times 10^3 = 15\,000 \qquad \frac{0.25 \times 4}{10^{-2}} = 1.0 \times 10^2 = 100$$

The prefixes in Table 2-4 are expressed as powers of 10 in Table 2-6.

**Table 2-6 Metric Prefixes Expressed as Powers of 10**

Metric Prefix	Power of 10
mega (M)	$10^6$
kilo (k)	$10^3$
milli (m)	$10^{-3}$
micro ( $\mu$ )	$10^{-6}$
nano (n)	$10^{-9}$
pico (p)	$10^{-12}$

**Example 2.9** Problem answers can be expressed in different but equivalent units. For example, 3 000 000  $\Omega$  is different but equivalent to 3 M $\Omega$ .

(a) Express 2.1 V in millivolts (mV).

$$1\text{ V} = 10^3\text{ mV}$$

$$2.1\text{ V} = 2.1 \times 10^3 = 2100\text{ mV} \qquad \text{Ans.}$$

(b) Express 0.006 A in milliamperes (mA).

$$1\text{ A} = 10^3\text{ mA}$$

$$0.006\text{ A} = 0.006 \times 10^3 = 6\text{ mA} \qquad \text{Ans.}$$

(c) Change 356 mV to volts (V).

$$1\text{ mV} = 10^{-3}\text{ V}$$

$$356\text{ mV} = 356 \times 10^{-3} = 0.356\text{ V} \qquad \text{Ans.}$$

(d) Change 500 000  $\Omega$  to megohms (M $\Omega$ ).

$$1\text{ } \Omega = 10^{-6}\text{ M}\Omega$$

$$500\,000\text{ } \Omega \times 10^{-6} = 0.5\text{ M}\Omega \qquad \text{Ans.}$$

(e) Change 20 000 000 picofarads (pF) into farads (F).

$$1\text{ pF} = 10^{-12}\text{ F}$$

$$20\,000\,000\text{ pF} \times 10^{-12} = 0.000\,02\text{ F} \qquad \text{Ans.}$$

## SCIENTIFIC NOTATION

In scientific notation, the coefficient of the power of 10 is always expressed with one decimal place and the required power of 10. Several examples will make the procedure clear.

**Example 2.10** Express the following numbers in scientific notation.

$$300\,000 = \underbrace{3.000\,00}_{\text{}} \times 10^5 \quad (\text{Move decimal point left five places—power is 5 by Rule 1})$$

$$= 3 \times 10^5$$

$$871 = \underbrace{8.71}_{\text{}} \times 10^2 \quad (\text{Move decimal point left two places—power is 2 by Rule 1})$$

$$= 8.71 \times 10^2$$

$$7425 = \underbrace{7.425}_{\text{}} \times 10^3 \quad (\text{Move decimal point left three places—power is 3 by Rule 1})$$

$$= 7.425 \times 10^3$$

$$0.001 = \underbrace{0.001}_{\text{}} \times 10^{-3} \quad (\text{Move decimal point right three places—power is } -3 \text{ by Rule 2})$$

$$= 1 \times 10^{-3}$$

$$0.015 = \underbrace{0.015}_{\text{}} \times 10^{-2} \quad (\text{Move decimal point right two places—power is } -2 \text{ by Rule 2})$$

$$= 1.5 \times 10^{-2}$$

## ROUNDING OFF NUMBERS

A number is rounded off by dropping one or more digits at its right. If the digit to be dropped is *less than 5*, we leave the digit as it is. For example, 4.1632, if rounded to four digits, would be 4.163; if rounded to three digits, 4.16. If the digit to be dropped is *greater than 5*, we increase the digit to its left by 1. For example, 7.3468, if rounded to four digits, would be 7.347; if rounded to three digits, 7.35. If the digit to be dropped is *exactly 5* (that is, 5 followed by nothing but zeros), we increase the digits to its left by 1 if it is an odd number and we leave the digit to the left as it is if it is an even number. For example, 2.175, when rounded to three digits, becomes 2.18. The number 2.185 would also round to the same value, 2.18, if rounded to three digits.

Any digit that is needed to define the specific value is said to be *significant*. For example, a voltage of 115 V has three significant digits: 1, 1, and 5. When rounding off numbers, zero is not counted as a significant digit if it appears immediately after the decimal point and is followed by other significant digits. Such zeros must be retained and the count of significant digits must begin at the first significant digit beyond them. For example, 0.000 12 has two significant digits, 1 and 2, and the preceding zeros don't count. However, 18.0 has three significant digits; in this case zero is significant because it is not followed by other significant digits. In electricity, specific values are usually expressed in three significant digits.

**Example 2.11** Round off the following numbers to three significant digits.

We look at the fourth significant digit to the right and observe whether this digit is less than 5, greater than 5, or equal to 5.

$$5.6428 = 5.64$$

$$0.016\,95 = 0.0170$$

$$49.67 = 49.7$$

$$2078 = 2080$$

$$305.42 = 305$$

$$1.003 \times 10^{-3} = 1.00 \times 10^{-3}$$

$$782.51 = 783$$

$$12.46 \times 10^5 = 12.5 \times 10^5$$

$$0.003\,842 = 0.003\,84$$

$$1.865 \times 10^2 = 1.86 \times 10^2$$

Scientific notation is a convenient way to work problems in electricity. Often we express a numerical answer in terms of a prefix rather than leave the answer in scientific notation.

**Example 2.12** Express each of the following first in scientific notation and then with a prefix.

(a) 0.000 53 A to milliamperes (mA)

$$\begin{aligned} 0.000\ 53\ \text{A} &= 5.3 \times 10^{-4}\ \text{A} \\ &= 0.53 \times 10^{-3}\ \text{A} \\ &= 0.53\ \text{mA} \end{aligned}$$

(b) 2500 V to kilovolts (kV)

$$\begin{aligned} 2500\ \text{V} &= 2.5 \times 10^3\ \text{V} \\ &= 2.5\ \text{kV} \end{aligned}$$

(c) 0.000 000 1 F to microfarads ( $\mu\text{F}$ )

$$\begin{aligned} 0.000\ 000\ 1\ \text{F} &= 1 \times 10^{-7}\ \text{F} \\ &= 10 \times 10^{-6}\ \text{F} \\ &= 10\ \mu\text{F} \end{aligned}$$

## Solved Problems

Express each of the following in the units indicated.

**2.1** 2 A to milliamperes

$$1\ \text{A} = 1000\ \text{mA} = 10^3\ \text{mA}$$

Multiply 2 by 1000 to get 2000 mA. *Ans.*

or

Multiply 2 by  $10^3$  to get  $2 \times 10^3$  mA, which is 2000 mA.

**2.2** 1327 mA to amperes

$$1\ \text{mA} = 0.001\ \text{A} = 10^{-3}\ \text{A}$$

Multiply 1327 by 0.001 to get 1.327 A. *Ans.*

or

Multiply 1327 by  $10^{-3}$  to get  $1327 \times 10^{-3}$  A, which is 1.327 A.

**2.3** 8.2 k $\Omega$  to ohms

$$1\ \text{k}\Omega = 1000\ \Omega = 10^3\ \Omega$$

Multiply 8.2 by 1000 to get 8200  $\Omega$ . *Ans.*

or

Multiply 8.2 by  $10^3$  to get  $8.2 \times 10^3$   $\Omega$  which is 8200  $\Omega$ .

**2.4** 680 k $\Omega$  to megohms

Use two steps.

**Step 1:** Convert to ohms.

Multiply 680 by 1000 to get 680 000  $\Omega$ .



**Step 2:** Convert to megohms.

Multiply 680 000  $\Omega$  by 0.000 001 to get 0.68 M $\Omega$ .      *Ans.*

**2.5** 10 000  $\mu\text{F}$  to farads

$$1 \mu\text{F} = 0.000\ 001 \text{ F} = 10^{-6} \text{ F}$$

Multiply 10 000 by 0.000 001 to get 0.01 F.      *Ans.*

or Multiply 10 000 by  $10^{-6}$  to get  $10\ 000 \times 10^{-6}$ , which is 0.01 F.

**2.6** 0.000 000 04 s to nanoseconds (ns)

$$1 \text{ s} = 1\ 000\ 000\ 000 \text{ ns} = 10^9 \text{ ns}$$

Multiply 0.000 000 04 by 1 000 000 000 to get 40 ns.      *Ans.*

or Multiply 0.000 000 04 by  $10^9$  to get  $0.000\ 000\ 04 \times 10^9$  ns, which is equal to  $4 \times 10^1$  or 40 ns.

Express the following numbers as decimal numbers.

**2.7**  $0.75 \times 10^3$

Move decimal point right three places—Rule 3:

$$0.75 \times 10^3 = \underbrace{0.750}_{\uparrow} = 750 \quad \textit{Ans.}$$

**2.8**  $0.75 \times 10^{-3}$

Move decimal point left three places—Rule 4:

$$0.75 \times 10^{-3} = \underbrace{0.000}_{\uparrow}75 = 0.000\ 75 \quad \textit{Ans.}$$

**2.9**  $(2.1 \times 10^{-1})(4 \times 10^2)$

$$\begin{aligned} (2.1 \times 10^{-1})(4 \times 10^2) &= 2.1 \times 4 \times 10^{-1} \times 10^2 \\ &= 8.4 \times 10^1 \quad (\text{Rule 5}) \\ &= 84 \quad (\text{Rule 3}) \quad \textit{Ans.} \end{aligned}$$

**2.10** Express 4160 in scientific notation.

Move decimal point left three places—Rule 1:

$$4160 = \underbrace{4.160}_{\uparrow} \times 10^3 = 4.160 \times 10^3 \quad \textit{Ans.}$$

Express each quantity in the following problems in scientific notation and then perform the indicated arithmetic calculation.

**2.11**  $0.072 \times 1000$

Express       $0.072 = 7.2 \times 10^{-2}$       (Move decimal point right two places—Rule 2)

$$\begin{aligned} \text{Then} \quad 0.072 \times 1000 &= (7.2 \times 10^{-2})(1 \times 10^3) \\ &= (7.2 \times 1)(10^{-2} \times 10^3) \\ &= 7.2 \times 10 \quad (\text{Rule 5}) \\ &= 72 \quad (\text{Rule 3}) \quad \textit{Ans.} \end{aligned}$$

2.12  $0.0045 \times 100$ 

Express  $0.0045 = 4.5 \times 10^{-3}$  (Move decimal point right three places—Rule 2)  
 $100 = 1 \times 10^2$  (Move decimal point left two places—Rule 1)

Then  $0.0045 \times 100 = (4.5 \times 10^{-3})(1 \times 10^2)$   
 $= (4.5 \times 1)(10^{-3} \times 10^2)$   
 $= 4.5 \times 10^{-1}$  (Rule 5)  
 $= 0.45$  (Rule 4) *Ans.*

2.13  $7500 \div 100$ 

Express  $7500 = 7.5 \times 10^3$  (Move decimal point left three places—Rule 1)  
 $100 = 1 \times 10^2$  (Move decimal point left two places—Rule 1)

Then  $\frac{7500}{100} = \frac{7.5 \times 10^3}{1 \times 10^2}$   
 $= 7.5(10^3 \times 10^{-2})$  ( $1/10^2 = 10^{-2}$ )  
 $= 7.5 \times 10^1$  (Rule 5)  
 $= 75$  (Rule 3) *Ans.*

2.14  $\frac{4000}{2000}$ 

Express  $4000 = 4 \times 10^3$  (Move decimal point left three places—Rule 1)  
 $2000 = 2 \times 10^3$  (Move decimal point left three places—Rule 1)

$$\frac{4000}{2000} = \frac{4 \times 10^3}{2 \times 10^3} = 2 \quad \text{Ans.}$$

Note that any factor divided by itself cancels out to 1. That is,  $10^3/10^3 = 10^{3-3} = 10^0 = 1$ .

2.15  $\frac{1000 \times 0.008}{0.002 \times 500}$ 

Express  $1000 = 1 \times 10^3$  (Move decimal point left three places—Rule 1)  
 $0.008 = 8 \times 10^{-3}$  (Move decimal point right three places—Rule 2)  
 $0.002 = 2 \times 10^{-3}$  (Move decimal point right three places—Rule 2)  
 $500 = 5 \times 10^2$  (Move decimal point left two places—Rule 1)

Then  $\frac{1000 \times 0.008}{0.002 \times 500} = \frac{(1 \times 10^3)(8 \times 10^{-3})}{(2 \times 10^{-3})(5 \times 10^2)}$   
 $= \frac{1 \times 8 \times 10^3 \times 10^{-3}}{2 \times 5 \times 10^{-3} \times 10^2}$   
 $= \frac{8 \times 10^0}{10 \times 10^{-1}}$  (Rule 5)  
 $= \frac{8 \times 1}{10^0}$  (Rule 5)  
 $= 8$  *Ans.*

$$2.16 \quad \frac{1}{4 \times 100\,000 \times 0.000\,05}$$

Express  $4 = 4$

$$100\,000 = 1 \times 10^5 \quad (\text{Move decimal point left five places—Rule 1})$$

$$0.000\,05 = 5 \times 10^{-5} \quad (\text{Move decimal point right five places—Rule 2})$$

$$\begin{aligned} \text{Then} \quad \frac{1}{4 \times 100\,000 \times 0.000\,05} &= \frac{1}{4(1 \times 10^5)(5 \times 10^{-5})} \\ &= \frac{1}{(4 \times 5)(10^5 \times 10^{-5})} \\ &= \frac{1}{20 \times 10^0} \quad (\text{Rule 5}) \\ &= \frac{1}{2 \times 10 \times 1} \quad (\text{Rule 1}) \\ &= \frac{10^{-1}}{2} \quad (\text{Rule 6, } 1/10 = 10^{-1}) \\ &= 0.5 \times 10^{-1} \\ &= 0.05 \quad (\text{Rule 4}) \quad \text{Ans.} \end{aligned}$$

2.17 We might read 220 V on a certain type of voltmeter, but a precision instrument might show that voltage to be 220.4 V, and a series of precise measurements might show the voltage to be 220.47 V. How many significant digits does each measurement have?

220 V, three significant digits

220.4 V, four significant digits

220.47 V, five significant digits

If the accuracy of measurement required is five places, then the instrument must measure to at least five significant digits.

In Problems 2.18–2.20, perform the indicated operations. Round off the figures in the results, if necessary, and express answers to three significant digits as a number from 1 through 10 and the proper power of 10.

$$2.18 \quad \frac{0.256 \times 338 \times 10^{-9}}{865\,000}$$

Express  $0.256 = 2.56 \times 10^{-1}$

$$338 = 3.38 \times 10^2$$

$$865\,000 = 8.65 \times 10^5$$

$$\begin{aligned} \text{Then} \quad \frac{0.256 \times 338 \times 10^{-9}}{865\,000} &= \frac{(2.56 \times 10^{-1})(3.38 \times 10^2)(10^{-9})}{8.65 \times 10^5} \\ &= \frac{2.56 \times 3.38}{8.65} (10^{-1} \times 10^2 \times 10^{-9} \times 10^{-5}) \\ &= (1.00)(10^{-13}) \\ &= 1.00 \times 10^{-13} \quad \text{Ans.} \end{aligned}$$

$$2.19 \quad \frac{2800 \times 75.61}{0.000\,900\,5 \times 0.0834}$$

Express

$$2800 = 2.8 \times 10^3$$

$$75.61 = 7.561 \times 10^1$$

$$0.000\,900\,5 = 9.005 \times 10^{-4}$$

$$0.0834 = 8.34 \times 10^{-2}$$

Then

$$\begin{aligned} \frac{2800 \times 75.61}{0.000\,900\,5 \times 0.0834} &= \frac{(2.8 \times 10^3)(7.561 \times 10^1)}{(9.005 \times 10^{-4})(8.34 \times 10^{-2})} \\ &= \frac{2.8 \times 7.561}{9.005 \times 8.34} \frac{10^3 \times 10^1}{10^{-4} \times 10^{-2}} = \frac{21.17}{75.10} \frac{10^4}{10^{-6}} \\ &= 0.2819 \times 10^{10} \\ &= 2.819 \times 10^{-1} \times 10^{10} \\ &= 2.82 \times 10^9 \quad \text{Ans.} \end{aligned}$$

$$2.20 \quad \frac{1}{6.28 \times 400 \times 10^6 \times 25 \times 10^{-12}}$$

Then

$$\begin{aligned} \frac{1}{6.28(4 \times 10^2)(10^6)(2.5 \times 10^1)(10^{-12})} &= \frac{1}{(6.28 \times 4 \times 2.5)(10^2 \times 10^6 \times 10^1 \times 10^{-12})} \\ &= \frac{1}{62.80 \times 10^{-3}} = 0.0159 \times 10^3 = 1.59 \times 10^{-2} \times 10^3 \\ &= 1.59 \times 10^1 = 15.9 \quad \text{Ans.} \end{aligned}$$

### Supplementary Problems

Express each of the following in the units indicated (use powers of 10 where applicable).

- 2.21 5 600 000  $\Omega$  in megohms    *Ans.* 5.6 M $\Omega$
- 2.22 2.2 M $\Omega$  in ohms    *Ans.* 2 200 000  $\Omega$  or  $2.2 \times 10^6 \Omega$
- 2.23 0.330 M $\Omega$  in kilohms    *Ans.* 330 k $\Omega$
- 2.24 0.013 kV in volts    *Ans.* 13 V
- 2.25 0.24 A in milliamperes    *Ans.* 240 mA
- 2.26 20 000  $\mu$ A in amperes    *Ans.* 0.02 A
- 2.27 0.25 mA in microamperes    *Ans.* 250  $\mu$ A
- 2.28 10 000 V in kilovolts    *Ans.* 10 kV
- 2.29 4 000 000 W in megawatts (MW)    *Ans.* 4 MW
- 2.30 5 000 kW in megawatts    *Ans.* 5 MW
- 2.31 200 ns in seconds    *Ans.* 0.000 000 2 s or  $2 \times 10^{-7}$  s

Express each of the following as decimal numbers.

2.32  $0.006 \times 10^2$     *Ans.* 0.6

2.33  $43.41 \times 100$     *Ans.* 4341

2.34  $0.0053 \times 10^3$     *Ans.* 5.3

2.35  $400/10^3$     *Ans.* 0.4

2.36  $3 \times 10^{-2}$     *Ans.* 0.03

2.37  $100\,000 \times 10^{-4}$     *Ans.* 10

2.38  $(0.5 \times 0.03)/10^{-2}$     *Ans.* 1.5

2.39  $(3.1 \times 10^{-1})(2 \times 10^{-3})$     *Ans.* 0.0062

2.40  $600/(5 \times 10^2)$     *Ans.* 1.2

Express each of the following in scientific notation, that is, as a number from 1 to 10 and the proper power of 10.

2.41 120 000    *Ans.*  $1.2 \times 10^5$

2.42 0.006 45    *Ans.*  $6.45 \times 10^{-3}$

2.43 2 300 000    *Ans.*  $2.3 \times 10^6$

2.44  $550 \times 10^{-4}$     *Ans.*  $5.5 \times 10^{-2}$

2.45  $0.0008 \times 10^3$     *Ans.*  $8 \times 10^{-1}$

Perform the indicated operations. Express the answer in scientific notation.

2.46  $\frac{2000 \times 0.008}{0.02 \times 10^3}$     *Ans.*  $8 \times 10^{-1}$

2.47  $\frac{1}{(4 \times 10^4)(0.5 \times 10^{-5})}$     *Ans.* 5

2.48  $\frac{(3.2 \times 10^2)(1.4 \times 10^{-1})}{(2 \times 10^{-3})(4 \times 10^5)}$     *Ans.*  $5.6 \times 10$

2.49  $\frac{400\,000}{2 \times 10^7}$     *Ans.*  $2 \times 10^{-2}$

2.50  $\frac{300(4 \times 10^{-5})(10^3)}{12 \times 10^2}$     *Ans.*  $1 \times 10^{-3}$

Round off the following numbers to three significant digits.

2.51 3.824    *Ans.* 3.82

2.52 3.825    *Ans.* 3.82



cell. The schematic components represent the pictorial components in a simplified manner. A schematic diagram then is one that shows by means of graphic symbols the electrical connections and the functions of the different parts of a circuit.

The standard graphic symbols for the commonly used electrical and electronic components are given in Fig. 2-2.

Examples of common letter symbols used to denote various circuit components are given in Table 2-7.

**Table 2-7 Examples of Letter Symbols for Circuit Components**

Part	Letter	Example
Resistor	<i>R</i>	$R_3, 120\text{ k}\Omega$
Capacitor	<i>C</i>	$C_5, 20\text{ pF}$
Inductor	<i>L</i>	$L_1, 25\text{ mH}$
Rectifier (metallic or crystal)	<i>CR</i>	$CR_2$
Transformer	<i>T</i>	$T_2$
Transistor	<i>Q</i>	$Q_5, 2N482\text{ Detector}$
Tube	<i>V</i>	$V_3, 6AU6\text{ 1st IF amp}$
Jack	<i>J</i>	$J_1$

A schematic diagram of a two-transistor radio receiver is shown in Fig. 2-3. The circuit diagram in Fig. 2-3 shows the components in the order from left to right in which they are used to convert radio waves into sound waves. With the use of the diagram, it is then possible to trace the operation of the circuit from the incoming signal at the antenna to the output at the headphones. The components in a schematic diagram are identified by letter symbols such as *R* for resistors, *C* for capacitors, *L* for inductors, and *Q* for transistors (Table 2-7). Symbols are further identified by letter-number combinations such as  $R_1$ ,  $R_2$ , and  $R_3$  (sometimes written as  $R1$ ,  $R2$ ,  $R3$ ) to prevent confusion when more than one type of component is used (Fig. 2-3). The letters *B*, *C*, and *E* near the transistor symbols indicate the base, collector, and emitter of the transistors (Fig. 2-3). The numerical values of components are often indicated directly in the schematic diagram, such as  $220\text{ k}\Omega$  for  $R_1$  and  $0.022\text{ }\mu\text{F}$  for  $C_2$  (Fig. 2-3). When these values are not given in this way, they are stated in the parts list or the notes which accompany the diagram.

A schematic diagram does not show the physical location of the components or the wires which connect the components.

## ONE-LINE DIAGRAM

A one-line, or single-line, diagram shows the component parts of a circuit by means of single lines and appropriate graphical symbols. The single lines represent the two or more conductors that are connected between the components in the actual circuit. The one-line diagram shows the necessary basic information about the sequence of a circuit but does not give the detailed information that is found in a schematic diagram. One-line diagrams are generally used to show complex electrical systems without the individual conductors to the various loads.

**Example 2.13** Draw a one-line diagram showing the major equipment, switching devices, and connecting circuits of an electric power substation.

See Fig. 2-4. The single line running down represents three lines in this three-wire system. The power path can be traced from the shielded aluminum cable steel reinforced (ACSR) downward past a grounded lightning arrester, through a disconnect switch, fused disconnect switches, and a step-down transformer. It continues downward through an oil circuit breaker, disconnect switch, past another lightning arrester, and out through the ACSR line.












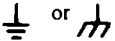
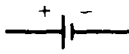















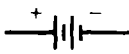








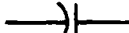

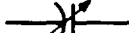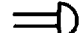





Ammeter		Generator (dc)		Switch	
Antenna		Ground		Semiconductor diode	
Appliance		Headphones		Transformer (general)	
Arc lamp		Inductor (air-core)		Transformer (iron-core)	
Battery cell		Inductor (iron-core)		Transistor (NPN)	
Battery		Inductor (tapped)		Transistor (PNP)	
Bell		Lamp		Vacuum-tube cathode	
Buzzer		Lightning arrester		Vacuum-tube filament	
Capacitor (fixed)		Loudspeaker		Vacuum-tube grid	
Capacitor (variable)		Microphone		Vacuum-tube plate	
Circuit breaker		Motor (ac)		Voltmeter	
Crystal		Motor (dc)		Wattmeter	
Fuse		Resistor (fixed)		Wires (connected)	
Galvanometer		Resistor (variable)		Wires (unconnected)	
Generator (ac)		Rheostat		Zener diode	

Fig. 2-2 Standard circuit symbols



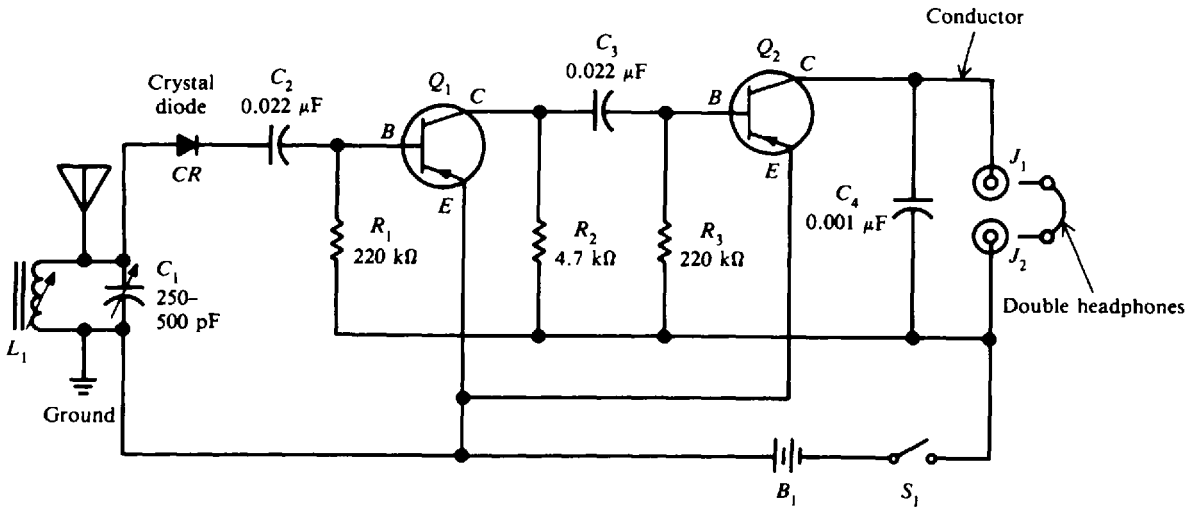


Fig. 2-3 Schematic diagram of a two-transistor radio

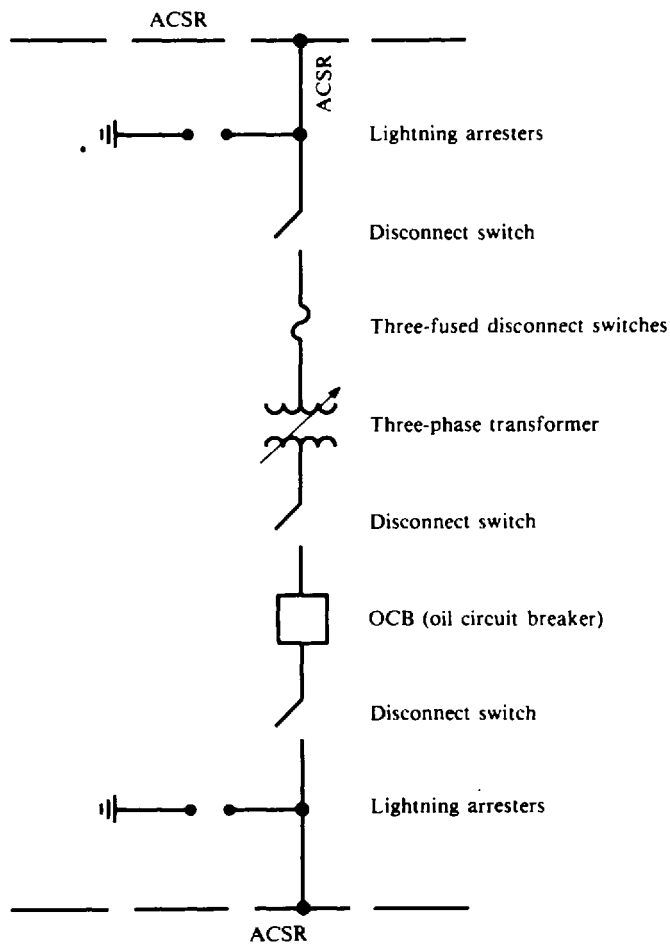


Fig. 2-4 A one-line diagram of a substation

## BLOCK DIAGRAM

The block diagram is used to show the relationship between the various component groups or stages in the operation of a circuit. It shows in block form the path of a signal through a circuit from input to output (Fig. 2-5). The blocks are drawn in the shape of squares or rectangles that are joined by single lines. Arrowheads placed at the terminal ends of the lines show the direction of the signal path from input to output as the diagram is read from left to right. As a general rule, the necessary information to describe the components or stages is placed within the block. On some block diagrams, devices such as antennas and loudspeakers are shown by standard symbols instead of by blocks (Fig. 2-5).

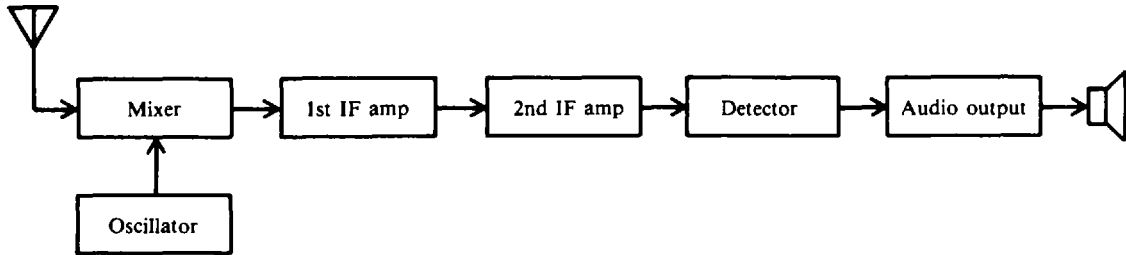


Fig. 2-5 Block diagram of a typical transistor radio receiver circuit

Because a block diagram shows the functions of the various stages of a circuit and uses single lines, it is a type of functional one-line diagram. The block diagram gives no information about specific components or wiring connections. Therefore, it is limited in use but does give a simple way of illustrating the overall features of a circuit. For this reason, block diagrams are frequently used by electricians, electronic technicians, and engineers as a first step in designing and laying out new equipment.

To show how easy it is to understand a circuit's operation by means of a block diagram, look at Fig. 2-5. The signal comes through the antenna and then progresses through the mixer circuit, through the intermediate-frequency (IF) amplifier stages and the detector stage, and finally to the output stage and speaker. The oscillator is in an auxiliary circuit, and so it is not shown in the main signal path.

## WIRING DIAGRAM

The wiring, or connection, diagram is used to show wiring connections in a simple, easy-to-follow way. They are very commonly used with home appliances and electrical systems of automobiles (Fig. 2-6). The typical wiring diagram shows the components of a circuit in a pictorial manner. The components are identified by name. Such a diagram also often shows the relative location of the components within a given space. A color-coding scheme may be used to identify certain wires or leads (Fig. 2-6).

## ELECTRICAL PLAN

An integral part of any set of drawings for the construction of a building is the wiring plan or layout. Architects, electrical designers, and contractors use floor-plan diagrams to locate components of the building's electrical system, such as receptacle outlets, switches, lighting fixtures, and other wiring devices. These devices and wiring arrangements are represented by means of symbols (Fig. 2-7). The living-room plan (Fig. 2-7) show two three-way switching arrangements. In one arrangement a ceiling outlet is switched from two door locations. Similarly, two receptacle outlets on the north wall are switched from two separate locations. The connection between switch and ceiling outlet is drawn with a medium-weight solid line, indicating that the connection (conduit or cable) is to be concealed in the walls or ceiling above. The cross lines indicate the conductors in the conduit or cable. If cross lines are omitted, two wires are understood to be in the connection.

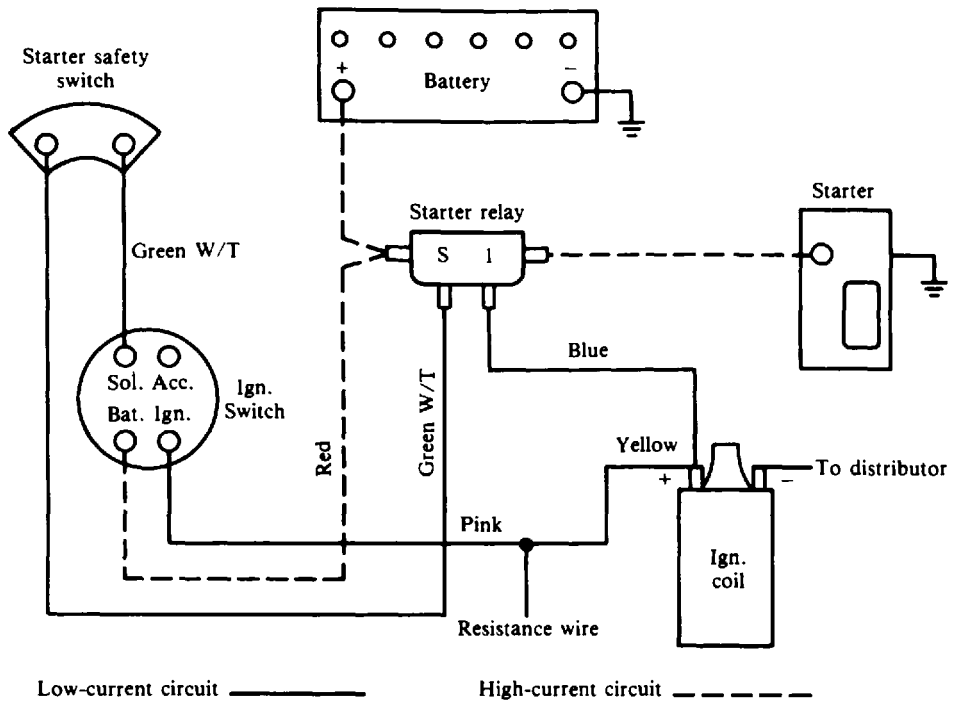


Fig. 2-6 Wiring diagram of an automobile starting circuit

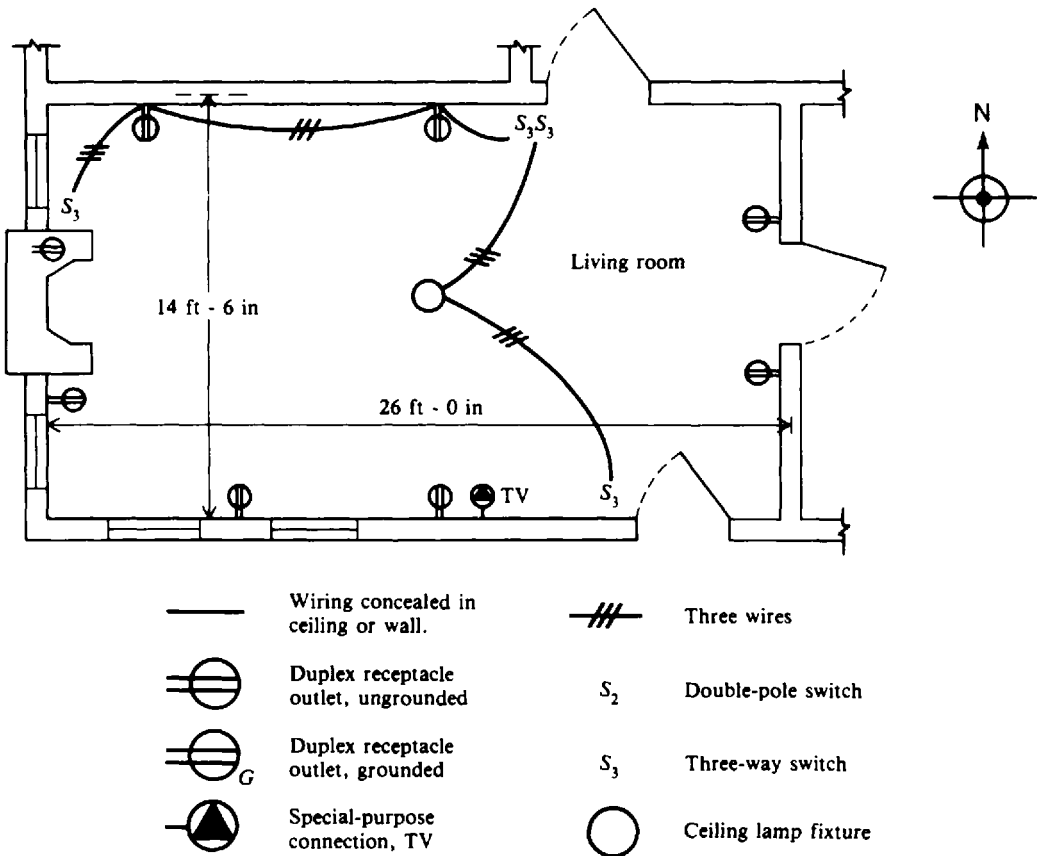


Fig. 2-7 Floor plan of a room with fixtures, outlets, and switches. Standard wiring symbols are shown.




### Solved Problems

2.63 Write the word or words which most correctly complete the following statements.

- (a) A picture showing the actual parts of a circuit and their connections is called a \_\_\_\_\_ diagram.
- (b) On a schematic diagram, the components are represented by \_\_\_\_\_.
- (c) Schematic diagrams are often drawn with the input on the \_\_\_\_\_ and the output on the \_\_\_\_\_.
- (d) Examples of letter symbols to identify components on a schematic diagram are \_\_\_\_\_ for diodes, \_\_\_\_\_ for capacitors, and \_\_\_\_\_ for inductors.
- (e) A single-line diagram is also called a \_\_\_\_\_ diagram.
- (f) Color coding is shown on a \_\_\_\_\_ diagram.

Ans. (a) pictorial; (b) symbols; (c) left, right; (d) CR, C, L; (e) one-line; (f) wiring or connection

2.64 In Fig. 2-3, identify the following symbols:

- |                     |   |   |
|---------------------|---|---|
| (a) $C_1$           | (g)  | (k) $B_1$   |
| (b) $C_2, C_3, C_4$ | (h)  | (l)  |
| (c) CR              | (i) $R_1, R_2, R_3$   |   |
| (d) $Q_1$ and $Q_2$ | (j) $L_1$   |   |
| (e) $J_1$ and $J_2$ |   |   |
| (f) $S_1$           |   |   |

- |                                     |  |
|-------------------------------------|--|
| (a) Variable capacitor              | (g) Conductors crossing but not connected      |
| (b) Fixed capacitors                | (h) Conductors electrically connected          |
| (c) Crystal rectifier (CR) diode    | (i) Fixed resistors                            |
| (d) PNP transistors                 | (j) Variable iron-core inductor (antenna coil) |
| (e) Jacks                           | (k) Battery                                    |
| (f) Single-pole single-throw switch | (l) Antenna                                    |

2.65 Using the circuit symbols in Fig. 2-2, draw a schematic circuit containing an ac generator, a switch, an ammeter, a bell, and a buzzer. Label the diagram carefully.

See Fig. 2-8.

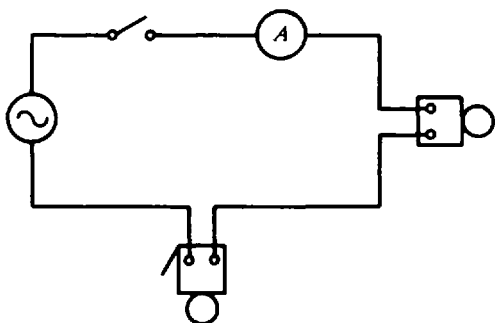


Fig. 2-8



Fig. 2-9

**2.66** Identify the symbols for transformers shown in Fig. 2-9.

1. Air-core transformer; 2. Iron-core transformer; 3. Iron-core variable transformer. The heavy lines between the coils represent an iron core. The iron core is simply a piece of iron around which the coils are wrapped. An arrow running through the coils of a transformer means the transformer is variable.

**2.67** Since an electric circuit is a path for current to flow through, a break in this path would stop current flow. Switches are simply ways to break this path or to control the flow of current. Some more symbols for switches are shown in Fig. 2-10. To remember these switches, think of the number of poles as the number of wires coming to either side of the switch. The throws can be thought of as the number of *on* positions. Answer the following questions:

- (a) The number of wires coming to each side of a double-pole switch is \_\_\_\_\_.
- (b) The number of *on* positions a DPST switch has is \_\_\_\_\_.
- (c) The number of *on* positions a DPDT switch has is \_\_\_\_\_.
- (a) two; (b) one; (c) two

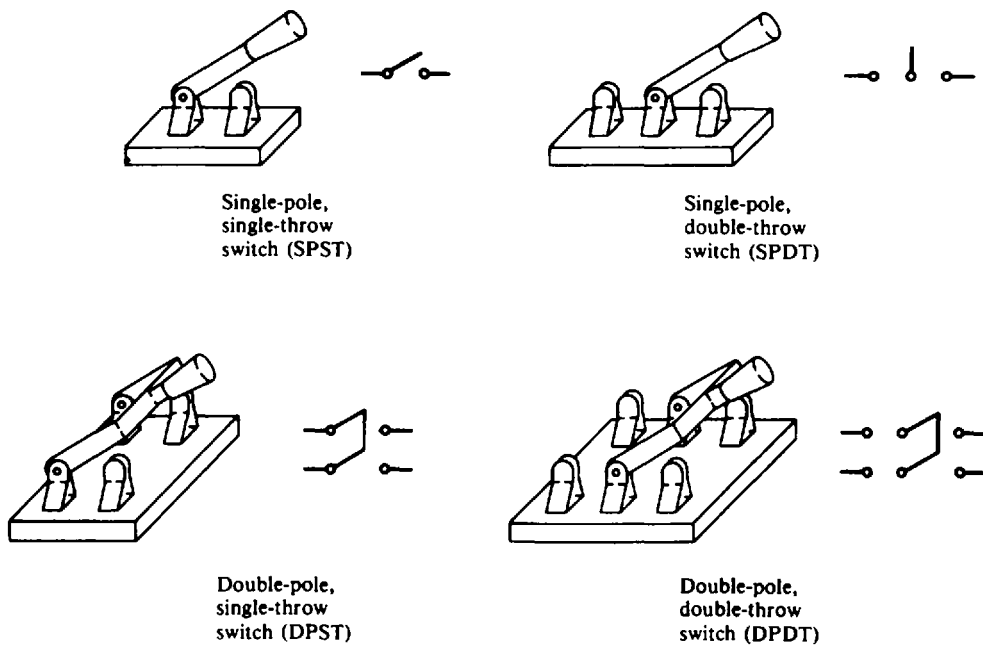


Fig. 2-10

**2.68** The ground symbol is often used in schematic diagrams. Some components are grounded to the frame or chassis of the equipment in which they are located. Aircraft, automobiles, and TV sets are grounded in this fashion. A frame or other ground must be a good conductor. The ground (frame) is the return path for current back to the power source. For the circuit shown in Fig. 2-11, complete the circuit by putting in the ground symbols:

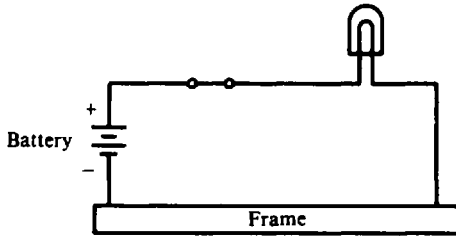


Fig. 2-11

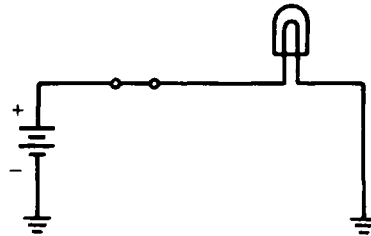


Fig. 2-12

See Fig. 2-12. In this circuit, current flows from the plus terminal of the battery, through the switch, to the lamp to ground, and then to the negative terminal of the battery. Since both the battery and the lamp are grounded to the frame, there is a complete circuit.

### Supplementary Problems

2.69 Write the words which correctly complete the following statements.

- (a) The use of a schematic diagram makes it possible to trace the function of a circuit from \_\_\_\_\_ to \_\_\_\_\_.
- (b) Examples of letter symbols to identify components on a schematic diagram are \_\_\_\_\_ for transformers, \_\_\_\_\_ for resistors, and \_\_\_\_\_ for transistors.
- (c) The \_\_\_\_\_ symbol is used to show that wires are electrically \_\_\_\_\_ at that point.
- (d) The \_\_\_\_\_ diagram is most often used to show complex electrical systems.
- (e) The \_\_\_\_\_ diagram is an easy way to show the relationships of various parts of a circuit.
- (f) Floor-plan diagrams are used with electrical \_\_\_\_\_ systems.

Ans. (a) input, output; (b) T, R, Q; (c) dot, connected; (d) one-line or single-line; (e) block; (f) wiring

2.70 Draw a schematic diagram showing a dc generator, a switch, a fuse, an arc lamp, and a resistor. Label the diagram carefully. Ans. See Fig. 2-13.

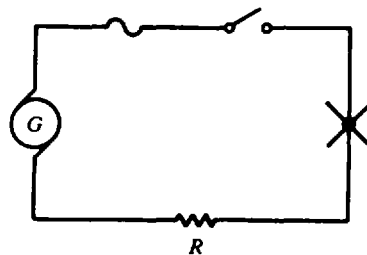






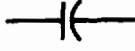


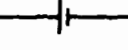


Fig. 2-13

2.71 A rectifier is a device that changes alternating current to direct current. Show a symbol for the rectifier.

Ans.

2.72 Match each symbol with its respective component.

- |  |   |               |
|--|---|---------------|
| 1.  | 6.   | (a) Voltmeter |
| 2.  | 7.   | (b) Resistor  |
| 3.  | 8.   | (c) Cell      |
| 4.  | 9.   | (d) Ammeter   |
| 5.  | 10.  | (e) Battery   |

Ans. 1. (j) 2. (e) 3. (a) 4. (k) 5. (g) 6. (i) 7. (d) 8. (h) 9. (f) 10. (c)

2.73 Place a ground symbol wherever one is needed in the diagram of Fig. 2-14. Ans. See Fig. 2-15.

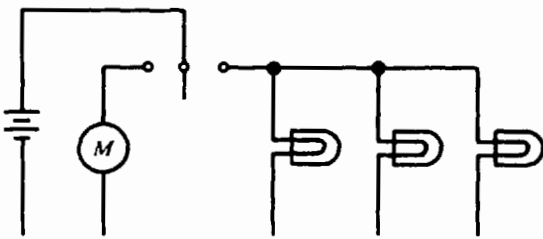


Fig. 2-14

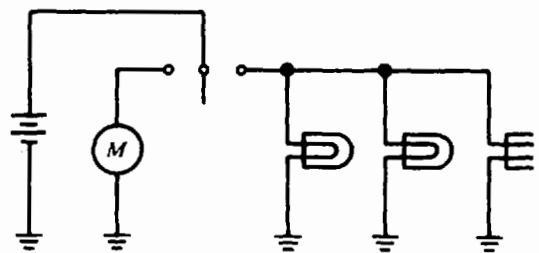






Fig. 2-15

2.74 For the wire connections shown below, identify each as "connection" or "no connection."

- (a) 
- (b) 
- (c) 
- (d) 

Ans. (a) No connection; (b) connection; (c) connection; (d) no connection

2.75 A fuse is a safety device which operates as a switch to turn a circuit off when the current exceeds a specific value. A circuit breaker performs the same protective function as a fuse, but unlike a fuse it can be reset. Show the symbols for a fuse and circuit breaker.

Ans. Fuse:  Circuit breaker: 

2.76 Match the name of each component with its respective symbol.

- |                         |     |     |
|-------------------------|-----|-----|
| 1. Unconnected wire     | (a) | (h) |
| 2. Ground               | (b) | (i) |
| 3. Lamp                 | (c) | (j) |
| 4. Voltmeter            | (d) | (k) |
| 5. Zener diode          | (e) | (l) |
| 6. PNP transistor       | (f) | (m) |
| 7. Circuit breaker      | (g) |     |
| 8. Variable capacitor   |     |     |
| 9. Air-core transformer |     |     |
| 10. Connected wire      |     |     |

Ans. 1. (b) 2. (g) 3. (m) 4. (e) 5. (j) 6. (d) 7. (a) 8. (c) 9. (h) 10. (f)

2.77 An elementary radio receiver consists of four major stages: an antenna, a tunable resonant circuit, a detector circuit, and headphones. Draw a block diagram of this elementary receiver.

Ans. See Fig. 2-16.



Fig. 2-16

2.78 Match each symbol with its meaning used in architectural floor-plan diagrams.

- | Symbol   | Meaning                                    |
|----------|--|
| 1. $S_2$ | (a) Special-purpose connection, dishwasher |
| 2.       | (b) Duplex receptacle outlet               |
| 3.       | (c) Four wires                             |
| 4.       | (d) Range outlet                           |
| 5.       | (e) Three wires                            |
|          | (f) Double-pole switch                     |

Ans. 1. (f) 2. (c) 3. (d) 4. (a) 5. (b)



## Ohm's Law and Power

### THE ELECTRIC CIRCUIT

A practical electric circuit has at least four parts: (1) a source of electromotive force, (2) conductors, (3) a load, and (4) a means of control (Fig. 3-1). The emf is the battery, the conductors are wires that connect the various parts of the circuit and conduct the current, the resistor is the load, and the switch is the control device. The most common sources of emf are batteries and generators. Conductors are wires which offer low resistance to a current. The load resistor represents a device that uses electric energy, such as a lamp, bell, toaster, radio, or a motor. Control devices might be switches, variable resistances, fuses, circuit breakers, or relays.

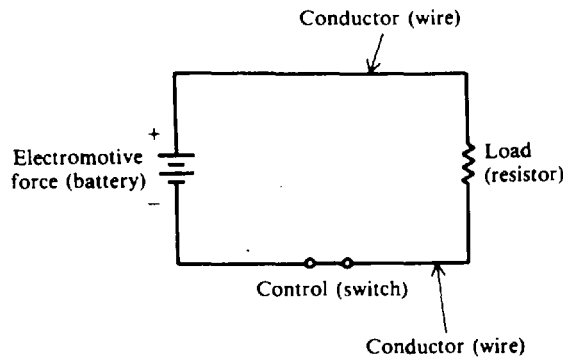


Fig. 3-1 Closed circuit

A complete or *closed circuit* (Fig. 3-1) is an unbroken path for current from the emf, through a load, and back to the source. A circuit is called *incomplete* or *open* (Fig. 3-2a) if a break in the circuit does not provide a complete path for current.

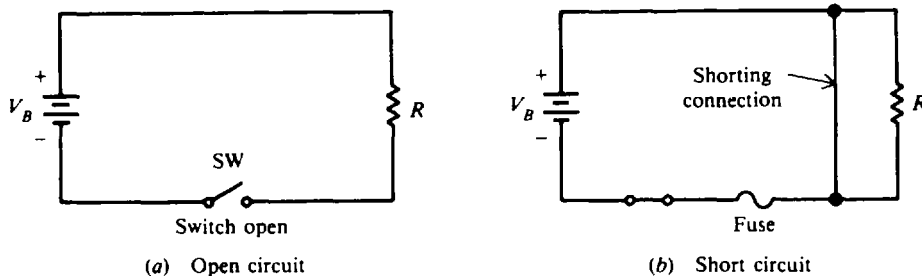


Fig. 3-2 Open and short circuits

To protect a circuit, a fuse is placed directly into the circuit (Fig. 3-2b). A fuse will open the circuit whenever a dangerously large current starts to flow. A fuse will permit currents smaller than the fuse value to flow but will melt and therefore break or open the circuit if a larger current flows. A dangerously large current will flow when a "short circuit" occurs. A short circuit is usually caused by an accidental connection between two points in a circuit which offers very little resistance (Fig. 3-2b).

A ground symbol is often used to show that a number of wires are connected to a common point in a circuit. For example, in Fig. 3-3a, conductors are shown making a complete circuit, while in Fig. 3-3b, the same circuit is shown with two ground symbols at G1 and G2. Since the ground symbol means that the two points are connected to a common point, electrically the two circuits (Fig. 3-3a and 3b) are exactly the same.

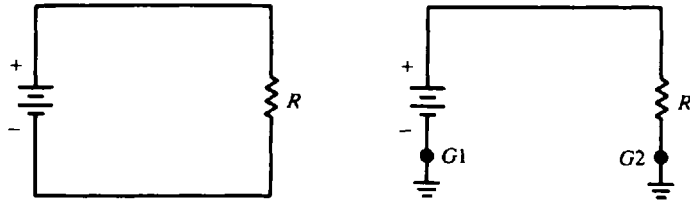


Fig. 3-3 Closed circuits *a* and *b* are the same

**Example 3.1** Replace with ground symbols the return wire of the closed circuit (in Fig. 3-4a). See Fig. 3-4b.

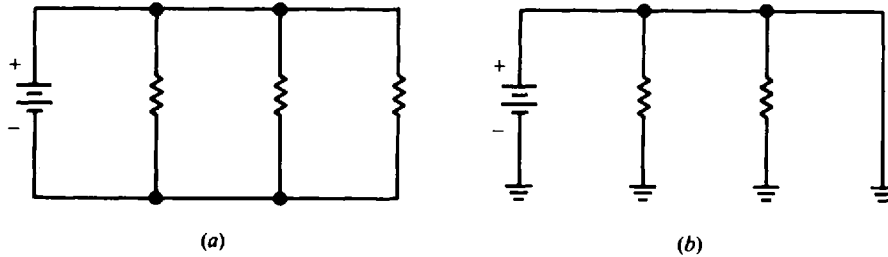


Fig. 3-4

## RESISTANCE

Resistance is the opposition to current flow. To add resistance to a circuit, electrical components called resistors are used. A *resistor* is a device whose resistance to current flow is a known, specified value. Resistance is measured in ohms and is represented by the symbol  $R$  in equations. One ohm is defined as that amount of resistance that will limit the current in a conductor to one ampere when the voltage applied to the conductor is one volt.

Resistors are common components of many electrical and electronic devices. Some frequent uses for resistors are to establish the proper value of circuit voltage, to limit current, and to provide a load.

### FIXED RESISTORS

A *fixed resistor* is one that has a single value of resistance which remains constant under normal conditions. The two main types of fixed resistors are carbon-composition and wire-wound resistors.

#### Carbon-Composition Resistors

The resistance element is primarily graphite or some other form of solid carbon carefully made to provide the desired resistance. These resistors generally are inexpensive and have resistance values that range from  $0.1\ \Omega$  to  $22\ \text{M}\Omega$ .

#### Wire-Wound Resistors

The resistance element is usually nickel-chromium wire wound on a ceramic rod. The entire assembly is normally covered with a ceramic material or a special enamel. They have resistance values from  $1\ \Omega$  to  $100\ \text{k}\Omega$ .

The actual resistance of a resistor may be greater or less than its rated or nominal value. The limit of actual resistance is called *tolerance*. Common tolerances of carbon-composition resistors are  $\pm 5\%$ ,  $\pm 10\%$ , and  $\pm 20\%$ . For example, a resistor having a rated resistance of  $100\ \Omega$  and a tolerance of  $\pm 10\%$  may have an actual resistance of any value between  $90\ \Omega$  and  $110\ \Omega$ , that is,  $10\ \Omega$  less or more than the rated value of  $100$ . Wire-wound resistors usually have a tolerance of  $\pm 5\%$ .


Resistors having high tolerances of  $\pm 20$  percent can still be used in many electric circuits. The advantage of using a high-tolerance resistor in any circuit where it is permissible is that it is less expensive than a low-tolerance resistor.

The *power rating* of a resistor (sometimes called the “wattage” rating) indicates how much heat a resistor can dissipate, or throw off, before being damaged. If more heat is generated than can be dissipated, the resistor will be damaged. The power rating is specified in watts. Carbon-composition resistors have wattage ratings which range from 1/16 to 2 W, while wire-wound resistors have ratings from 3 W to hundreds of watts.

The physical size of a resistor is no indication of its resistance. A tiny resistor can have a very low or a very high resistance. The physical size, however, gives some indication of its power rating. For a given value of resistance, the physical size of a resistor increases as the power rating increases.

**VARIABLE RESISTORS**


Variable resistors are used to vary or change the amount of resistance in a circuit. Variable resistors are called *potentiometers* or *rheostats*. Potentiometers generally consist of carbon-composition resistance elements, while the resistance element in a rheostat is usually made of resistance wire. In both devices, a sliding arm makes contact with the stationary resistance element (Fig. 3-5).

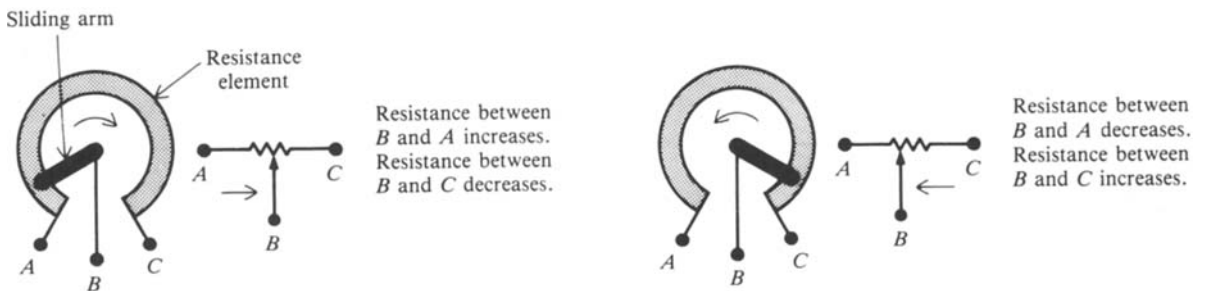


**Fig. 3-5** When the sliding arm of a variable resistor is moved, the resistance between the center terminal and end terminals changes.

As the sliding arm rotates, its point of contact on the resistance element changes, thus changing the resistance between the sliding arm terminal and the terminals of the stationary resistance (Fig. 3-5).

Rheostats are often used to control very high currents such as those found in motor and lamp loads (Fig. 3-6).

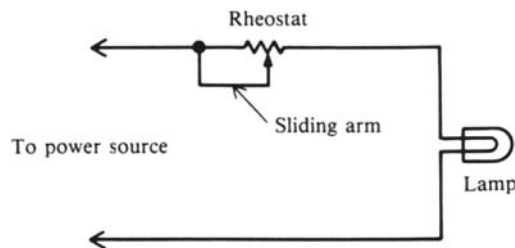

**Fig. 3-6** Use of rheostat to control current in a lamp circuit

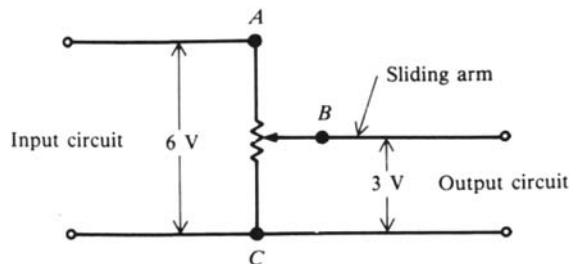

**Fig. 3-7** Use of potentiometer to change voltage

Potentiometers can be used to vary the value of voltage applied to a circuit (Fig. 3-7). In this circuit, the input voltage is applied across the terminals AC of the stationary resistance. By varying the position of the sliding arm (terminal B), the voltage across terminals BC will

change. As the sliding arm moves closer to terminal C, the voltage of the output circuit decreases. As the sliding arm moves closer to terminal A, the output voltage of the circuit increases. Potentiometers as control devices are found in amplifiers, radios, television sets, and electrical instruments. The rating of a variable resistor is the resistance of the entire stationary resistance element from one end terminal to the other.

**OHM'S LAW**

Ohm's law defines the relationship between current, voltage, and resistance. There are three ways to express Ohm's law mathematically.

1. The current in a circuit is equal to the voltage applied to the circuit divided by the resistance of the circuit:

$$I = \frac{V}{R} \tag{3-1}$$

2. The resistance of a circuit is equal to the voltage applied to the circuit divided by the current in the circuit:

$$R = \frac{V}{I} \tag{3-2}$$


3. The applied voltage to a circuit is equal to the product of the current and the resistance of the circuit:

$$V = I \times R = IR \tag{3-3}$$

where  $I$  = current, A  
 $R$  = resistance,  $\Omega$   
 $V$  = voltage, V

If you know any two of the quantities  $V$ ,  $I$ , and  $R$ , you can calculate the third.

The Ohm's law equations can be memorized and practiced effectively by using an Ohm's law circle (Fig. 3-8a). To find the equation for  $V$ ,  $I$ , or  $R$  when two quantities are known, cover the unknown third quantity with your finger.

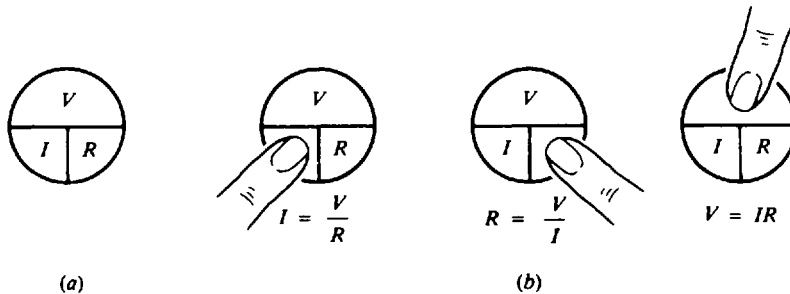


**Fig. 3-8** The Ohm's law circle

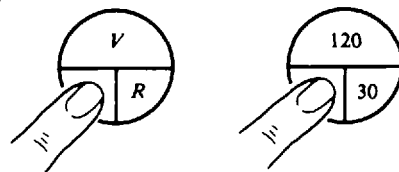The other two quantities in the circle will indicate how the covered quantity may be found (Fig. 3-8b).


**Example 3.2** Find  $I$  when  $V = 120\text{ V}$  and  $R = 30\ \Omega$ . Use Eq. (3-1) to find the unknown  $I$ .

$$\begin{aligned}
 I &= \frac{V}{R} \\
 &= \frac{120}{30} = 4\text{ A} \quad \text{Ans.}
 \end{aligned}$$




**Example 3.3** Find  $R$  when  $V = 220$  V and  $I = 11$  A. Use Eq. (3-2) to find the unknown  $R$ .

$$R = \frac{V}{I} \\ = \frac{220}{11} = 20 \Omega \quad \text{Ans.}$$

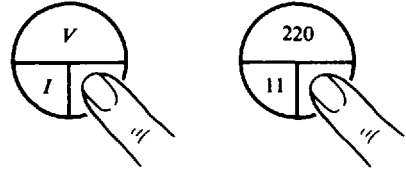

**Example 3.4** Find  $V$  when  $I = 3.5$  A and  $R = 20 \Omega$ . Use Eq. (3-3) to find the unknown  $V$ .

$$V = IR = 3.5(20) = 70 \text{ V} \quad \text{Ans.}$$

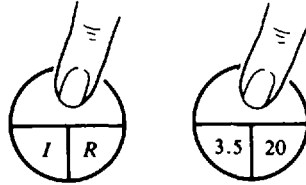

**Example 3.5** An electric light bulb draws 1.0 A when operating on a 120-V dc circuit. What is the resistance of the bulb?

The first step in solving a circuit problem is to sketch a schematic diagram of the circuit itself, labeling each of the parts and showing the known values (Fig. 3-9).

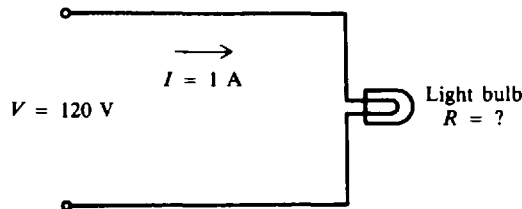


Fig. 3-9

Since  $I$  and  $V$  are known, we use Eq. (3-2) to solve for  $R$ .

$$R = \frac{V}{I} = \frac{120}{1} = 120 \Omega \quad \text{Ans.}$$

### ELECTRIC POWER

The electric power  $P$  used in any part of a circuit is equal to the current  $I$  in that part multiplied by the voltage  $V$  across that part of the circuit. Its formula is

$$P = VI \quad (3-4)$$

where  $P$  = power, W  
 $V$  = voltage, V  
 $I$  = current, A

Other forms for  $P = VI$  are  $I = P/V$  and  $V = P/I$ .

If we know the current  $I$  and the resistance  $R$  but not the voltage  $V$ , we can find the power  $P$  by using Ohm's law for voltage, so that substituting

$$V = IR \quad (3-3)$$

into (3-4) we have

$$P = IR \times I = I^2R \quad (3-5)$$

In the same manner, if we know the voltage  $V$  and the resistance  $R$  but not the current  $I$ , we can find the power  $P$  by using Ohm's law for current, so that substituting

$$I = \frac{V}{R} \quad (3-1)$$

into (3-4) we have

$$P = V \frac{V}{R} = \frac{V^2}{R} \quad (3-6)$$

If you know any two of the quantities, you can calculate the third.

**Example 3.6** The current through a 100- $\Omega$  resistor to be used in a circuit is 0.20 A. Find the power rating of the resistor.

Since  $I$  and  $R$  are known, use Eq. (3-5) to find  $P$ .

$$P = I^2 R = (0.20)^2(100) = 0.04(100) = 4 \text{ W} \quad \text{Ans.}$$

To prevent a resistor from burning out, the power rating of any resistor used in a circuit should be twice the wattage calculated by the power equation. Hence, the resistor used in this circuit should have a power rating of 8 W.

**Example 3.7** How many kilowatts of power are delivered to a circuit by a 240-V generator that supplies 20 A to the circuit?

Since  $V$  and  $I$  are given, use Eq. (3-4) to find  $P$ .

$$P = VI = 240(20) = 4800 \text{ W} = 4.8 \text{ kW} \quad \text{Ans.}$$

**Example 3.8** If the voltage across a 25 000- $\Omega$  resistor is 500 V, what is the power dissipated in the resistor?

Since  $R$  and  $V$  are known, use Eq. (3-6) to find  $P$ .

$$P = \frac{V^2}{R} = \frac{500^2}{25\,000} = \frac{250\,000}{25\,000} = 10 \text{ W} \quad \text{Ans.}$$

## HORSEPOWER

A motor is a device which converts electric power into the mechanical power of a rotating shaft. The electric power supplied to a motor is measured in watts or kilowatts; the mechanical power delivered by a motor is measured in horsepower (hp). One horsepower is equivalent to 746 W of electric power. The metric system will be used to express horsepower in watts. For most calculations, it is sufficiently accurate to consider 1 hp = 750 W or 1 hp = 3/4 kW. To convert between horsepower and kilowatt ratings, use the following equations.

$$\text{hp} = \frac{1000 \times \text{kW}}{750} = \frac{4}{3} \times \text{kW} \quad (3-7)$$

$$\text{kW} = \frac{750 \times \text{hp}}{1000} = \frac{3}{4} \times \text{hp} \quad (3-8)$$

**Example 3.9** Change the following units of measurement: (a) 7.5 kW to horsepower, and (b) 3/4 hp to watts.

(a) Use Eq. (3-7):

$$\text{hp} = \frac{4}{3} \times \text{kW} = \frac{4}{3}(7.5) = 10 \quad \text{Ans.}$$

(b) Use Eq. (3-8):

$$\begin{aligned} \text{kW} &= \frac{3}{4} \times \text{hp} = \frac{33}{44} = \frac{9}{16} = 0.563 \\ 1 \text{ kW} &= 1000 \text{ W} \\ \text{W} &= 1000(0.563) = 563 \quad \text{Ans.} \end{aligned}$$

## ELECTRIC ENERGY

Energy and work are essentially the same and are expressed in identical units. Power is different, however, because it is the time rate of doing work. With the watt unit for power, one watt used during one second equals the work of one joule, or one watt is one joule per second. The joule (J) is a basic practical unit of work or energy (see Table 2-3).

The kilowatthour (kWh) is a unit commonly used for large amounts of electric energy or work. The amount of kilowatthours is calculated as the product of the power in kilowatts (kW) and the time in hours (h) during which the power is used.

$$\text{kWh} = \text{kW} \times \text{h} \quad (3-9)$$

**Example 3.10** How much energy is delivered in 2 h by a generator supplying 10 kW?

Write Eq. (3-9) and substitute given values.

$$\begin{aligned} \text{kWh} &= \text{kW} \times \text{h} = 10(2) = 20 \\ \text{Energy delivered} &= 20 \text{ kWh} \quad \text{Ans.} \end{aligned}$$

## Solved Problems

3.1 Write the word or words which most correctly complete the following statements.

- The four basic parts of a complete circuit are the \_\_\_\_\_, \_\_\_\_\_, \_\_\_\_\_, and \_\_\_\_\_.
- A fixed resistor is one which has a \_\_\_\_\_ resistance value.
- In a carbon-film resistor, a film of \_\_\_\_\_ is deposited upon a ceramic core.
- The \_\_\_\_\_ rating of a resistor indicates how much current the resistor can conduct before becoming \_\_\_\_\_.
- The physical size of a resistor has no relationship to its \_\_\_\_\_.
- The two most common types of variable resistors are called \_\_\_\_\_ and \_\_\_\_\_.
- The rated resistance of a variable resistor is the resistance between its \_\_\_\_\_ terminals.
- \_\_\_\_\_ are used as current-limiting devices.
- If the voltage applied to a circuit is doubled and the resistance remains the same, the current in the circuit will increase to \_\_\_\_\_ the original value.
- If the current through a conductor is doubled and the resistance is constant, the power consumed by the conductor will increase to \_\_\_\_\_ times the original amount.

- Ans. (a) voltage source, conductors, load, control device (f) rheostats, potentiometers  
 (b) specific or single (g) end  
 (c) carbon (h) Rheostats  
 (d) wattage or power, overheated or damaged (i) twice ( $I = V/R$ )  
 (e) resistance (j) four ( $P = I^2R$ )

- 3.2 In Fig. 3-10, the resistor limits the current in the circuit to 5 A when connected to a 10-V battery. Find its resistance.

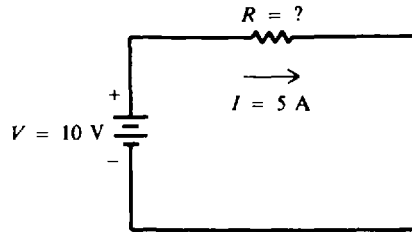


Fig. 3-10

Since  $I$  and  $V$  are known, solve for  $R$  by Ohm's law.

$$R = \frac{V}{I} \tag{3-2}$$

$$= \frac{10}{5} = 2 \Omega \quad \text{Ans.}$$

- 3.3 Figure 3-11 shows a doorbell circuit. The bell has a resistance of  $8 \Omega$  and requires a 1.5 A current to operate. Find the voltage required to ring the bell.

Since  $R$  and  $I$  are known, solve for  $V$  by Ohm's law.

$$V = IR \tag{3-3}$$

$$= 1.5(8) = 12 \text{ V} \quad \text{Ans.}$$

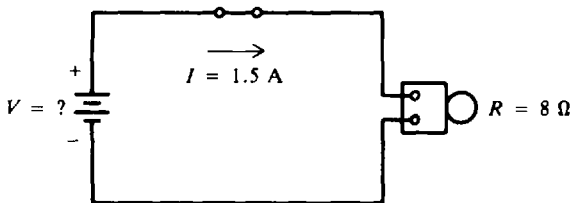


Fig. 3-11

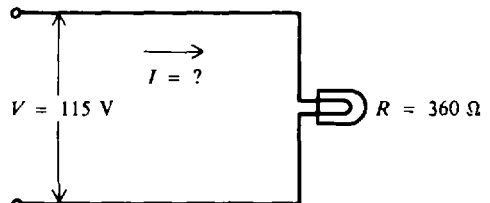


Fig. 3-12

- 3.4 What current will flow through a lamp when it has a resistance of  $360 \Omega$  and is connected to an ordinary house voltage of 115 V as shown in Fig. 3-12?

Since  $R$  and  $V$  are given, calculate  $I$  by Ohm's law.

$$I = \frac{V}{R} \tag{3-1}$$

$$= \frac{115}{360} = 0.319 \text{ A} \quad \text{Ans.}$$

Values generally will be computed to three significant figures.

- 3.5 Find the current drawn by a 60-W incandescent lamp rated for 120-V operation. Also find the current drawn by a 150-W, 120-V lamp and a 300-W, 120-V lamp. As the wattage increases, what happens to the current?

$P$  and  $V$  are known and we wish to find  $I$ . Solving for  $I$  in Eq. (3-4),

$$I = \frac{P}{V}$$



For the 60-W, 120-V lamp:

$$I = \frac{60}{120} = 0.5 \text{ A} \quad \text{Ans.}$$

For the 150-W, 120-V lamp:

$$I = \frac{150}{120} = 1.25 \text{ A} \quad \text{Ans.}$$

For the 300-W, 120-V lamp:

$$I = \frac{300}{120} = 2.5 \text{ A} \quad \text{Ans.}$$

We see that if  $V$  remains unchanged, the greater the value of  $P$ , the greater will be the value of  $I$ . That is to say, higher wattages draw higher currents for the same voltage rating.

- 3.6 Find the power consumed by a fixed 25- $\Omega$  resistor for each of the following currents: 3 A, 6 A, and 1.5 A. What effect does a change in current have on the amount of power dissipated by a fixed resistor?

$I$  and  $R$  are known and we wish to find  $P$ .

$$P = I^2 R \quad (3-5)$$

at 3 A:  $P = 3^2(25) = 225 \text{ W} \quad \text{Ans.}$

6 A:  $P = 6^2(25) = 900 \text{ W} \quad \text{Ans.}$

1.5 A:  $P = (1.5)^2(25) = 56.2 \text{ W} \quad \text{Ans.}$

If the current is doubled to 6 A from 3 A, the power will increase by  $2^2$ , or 4, so  $900 \text{ W} = 4 \times 225 \text{ W}$ . If the current is halved to 1.5 A from 3 A, the power will decrease by  $(1/2)^2$ , or  $1/4$ , so  $56.2 \text{ W} = 1/4 \times 225 \text{ W}$ . We see that if  $R$  does not change, power will change according to the square of the change in current.

- 3.7 The efficiency of a motor is calculated by dividing its output by its input. The output is measured in horsepower, while the input is measured in watts or kilowatts. Before the efficiency can be calculated, the output and the input must be expressed in the same units of measurement. Find the efficiency of a motor which receives 4 kW and delivers 4 hp.

Step 1. Express all measurements in the same units.

$$\text{Input} = 4 \text{ kW}$$

$$\text{Output} = \frac{3}{4} \times \text{hp} = \frac{3}{4} 4 = 3 \text{ kW} \quad (3-8)$$

Step 2. Find the efficiency by dividing output by input.

$$\text{Efficiency} = \frac{\text{output}}{\text{input}} = \frac{3 \text{ kW}}{4 \text{ kW}} = 0.75$$

Efficiency is not expressed in any units. To change the decimal efficiency into a percent efficiency, move the decimal point two places to the right and add a percent sign (%).

$$\text{Efficiency} = 0.75 = 75\% \quad \text{Ans.}$$

- 3.8 The motor in a washing machine uses 1200 W. How much energy in kilowatthours is used in a week by a laundromat with eight washers if they are all in use 10 hours per day (h/day) for a 6-day week?

Change 1200 W to 1.2 kW.

For one motor:  $\text{Energy} = 1.2 \text{ kW} \times \frac{10 \text{ h}}{\text{day}} \times 6 \text{ days} = 72 \text{ kWh}$

For eight motors:  $\text{Energy} = 8 \times 72 \text{ kWh} = 576 \text{ kWh}$       *Ans.*

- 3.9** A radio receiver draws 0.9 A at 110 V. If the set is used 3 h/day, how much energy does it consume in 7 days?

Find the power.

$$P = VI = 110(0.9) = 99 \text{ W} = 0.099 \text{ kW}$$

Then find the energy.

$$\text{Energy} = 0.099 \text{ kW} \times \frac{3 \text{ h}}{\text{day}} \times 7 \text{ days} = 2.08 \text{ kWh} \quad \text{Ans.}$$

- 3.10** Electric utility companies establish their rates at a given number of cents per kilowatt-hour. Rates for electric energy in the United States depend upon the method by which the electricity is generated, the type and complexity of the transmission and distribution systems, the maintenance cost, and many other factors. By knowing the amount of energy you use (from the meter readings) and the cost per kilowatt-hour of energy in your area, you can calculate your own monthly electric bill.

One residence used 820 kWh of electric energy in one month. If the utility rate is 6 cents per kilowatt-hour, what was the owner's electrical bill for the month?

A convenient formula for calculating the total cost is:

$$\begin{aligned} \text{Total cost} &= \text{kWh} \times \text{unit cost} \\ &= 820 \times 6 \text{ cents} = 4920 \text{ cents} = \$49.20^* \quad \text{Ans.} \end{aligned}$$

---

\*Here we are using an average unit cost. Most utility rates are stepped according to blocks of kilowatt-hour usage plus minimum charges, not to mention full adjustment charges and taxes.

## Supplementary Problems

- 3.11** Write the word or words which most correctly complete the following statements.
- Common sources of energy used in electric circuits are \_\_\_\_\_ and \_\_\_\_\_.
  - In a circuit, an incandescent lamp is treated as a \_\_\_\_\_ load.
  - The resistance element of a wire-wound resistor is made of \_\_\_\_\_ wire.
  - The amount by which the actual resistance of a resistor may vary from its rated value is called its \_\_\_\_\_.
  - A large resistor of a given type has a higher \_\_\_\_\_ rating than a smaller resistor of the same type.
  - A common resistor defect is an open or burned-out condition caused by excessive \_\_\_\_\_ through a resistor.
  - The amount of resistance can be changed in a circuit by a \_\_\_\_\_ resistor.
  - A variable resistor used to change the value of voltage applied to a circuit is the \_\_\_\_\_.
  - If the resistance of a circuit is doubled and the current remains unchanged, the voltage will increase to \_\_\_\_\_ its original value.
  - If a toaster rated at 1000 W is operated for 30 min, the energy used is \_\_\_\_\_ kWh.

*Ans.* (a) batteries, generators; (b) resistive; (c) nickel-chromium; (d) tolerance; (e) wattage or power; (f) current; (g) variable; (h) potentiometer; (i) twice ( $V = IR$ ); (j) 0.5

3.12 Use Ohm's law to fill in the indicated quantity.

	V	I	R
(a)	?	2 A	3 $\Omega$
(b)	120 V	?	2400 $\Omega$
(c)	120 V	24 A	?
(d)	?	8 mA	5 k $\Omega$
(e)	60 V	?	12 k $\Omega$
(f)	110 V	2 mA	?
(g)	?	2.5 A	6.4 $\Omega$
(h)	2400 V	?	1 M $\Omega$

*Ans.*

	V	I	R
(a)	6 V	....	....
(b)	....	0.05 A	....
(c)	....	....	5 $\Omega$
(d)	40 V	....	....
(e)	....	5 mA	....
(f)	....	....	55 k $\Omega$
(g)	16 V	....	....
(h)	....	2.4 mA	....

- 3.13 A circuit consists of a 6-V battery, a switch, and a lamp. When the switch is closed, 2 A flows in the circuit. What is the resistance of the lamp? *Ans.* 3  $\Omega$
- 3.14 Suppose you replace the lamp in Prob. 3.13 with another one, requiring the same 6 V across it but drawing only 0.04 A. What is the resistance of the new lamp? *Ans.* 150  $\Omega$
- 3.15 A voltage of 20 V is measured across a 200- $\Omega$  resistor. What is the current flowing through the resistor? *Ans.* 0.10 A or 100 mA
- 3.16 If the resistance of the air gap in an automobile spark plug is 2500  $\Omega$ , what voltage is needed to force 0.20 A through it? *Ans.* 500 V
- 3.17 The filament of a television tube has a resistance of 90  $\Omega$ . What voltage is required to produce the tube's rated current of 0.3 A? *Ans.* 27 V
- 3.18 A 110-V line is protected with a 15-A fuse. Will the fuse "carry" a 6- $\Omega$  load? *Ans.* No
- 3.19 A sensitive dc meter takes 9 mA from a line when the voltage is 108 V. What is the resistance of the meter? *Ans.* 12 k $\Omega$
- 3.20 An automobile dashboard ammeter shows 10.8 A of current flowing when the headlights are lit. If the current is drawn from the 12-V storage battery, what is the resistance of the headlights? *Ans.* 1.11  $\Omega$
- 3.21 A 160- $\Omega$  telegraph relay coil operates on a voltage of 6.4 V. Find the current drawn by the relay. *Ans.* 0.04 A
- 3.22 What is the power used by a soldering iron taking 3 A at 110 V? *Ans.* 330 W
- 3.23 A 12-V battery is connected to a lamp that has a 10- $\Omega$  resistance. How much power is delivered to the load? *Ans.* 14.4 W
- 3.24 An electric oven uses 35.5 A at 118 V. Find the wattage generated by the oven. *Ans.* 4190 W
- 3.25 A 12- $\Omega$  resistor in a power supply circuit carries 0.5 A. How many watts of power are dissipated in the resistor? What must be the wattage rating of the resistor in order to dissipate this power safely as heat? *Ans.* 3 W, 6 W

3.26 Find the power used by a 10-kΩ resistor drawing 0.01 A.    *Ans.* 1 W

3.27 Find the current through a 40-W lamp at 110 V.    *Ans.* 0.364 A

3.28 An electric dryer requires 360 W and draws 3.25 A. Find its operating voltage.    *Ans.* 111 V

3.29 Fill in the indicated quantity.

	hp	kW	W
(a)	$2\frac{1}{2}$	?	?
(b)	?	8.75	?
(c)	?	?	1000

*Ans.*

	hp	kW	W
(a)	....	1.69	1690
(b)	$11\frac{2}{3}$	....	8750
(c)	$1\frac{1}{3}$	1 kW	....

3.30 A motor delivers 2 hp and receives 1.8 kW of energy. Find its efficiency (See Prob. 3.7).  
*Ans.* 83.3 percent

3.31 A generator receives 7 hp and supplies 20 A at 220 V. Find the power supplied by the generator and its efficiency.    *Ans.* 4400 W, 83.8 percent

3.32 A 4-hp lathe motor runs 8 h/day. Find the electric energy in kilowatthours used in a day.  
*Ans.* 24 kWh

3.33 How much power and energy is drawn from a 110-V line by a 22-Ω electric iron in 3 h?  
*Ans.* 550 W, 1.65 kWh

3.34 What does it cost to operate a 5.5-kW electric range for  $3\frac{1}{2}$  h at 3.8 cents per kilowatthour?  
*Ans.* 73 cents

3.35 In a certain community, the average rate of electric energy is 4.5 cents per kilowatthour. Find the cost of operating a 200-W stereo receiver in this community for 12 h.    *Ans.* 11 cents

# Chapter 4

## Direct-Current Series Circuits

### VOLTAGE, CURRENT, AND RESISTANCE IN SERIES CIRCUITS

A *series circuit* is a circuit in which there is only one path for current to flow along. In the series circuit (Fig. 4-1), the current  $I$  is the same in all parts of the circuit. This means that the current flowing through  $R_1$  is the same as the current through  $R_2$ , is the same as the current through  $R_3$ , and is the same as the current supplied by the battery.

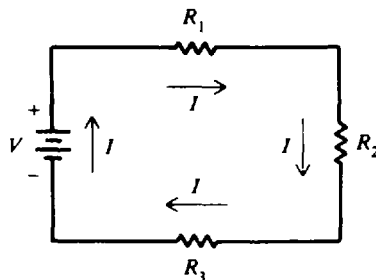


Fig. 4-1 A series circuit

When resistances are connected in series (Fig. 4-1), the total resistance in the circuit is equal to the sum of the resistances of all the parts of the circuit, or

$$R_T = R_1 + R_2 + R_3 \quad (4-1)$$

where  $R_T =$  total resistance,  $\Omega$   
 $R_1, R_2,$  and  $R_3 =$  resistances in series,  $\Omega$

**Example 4.1** A series circuit has a 50- $\Omega$ , a 75- $\Omega$ , and a 100- $\Omega$  resistor in series (Fig. 4-2). Find the total resistance of the circuit.

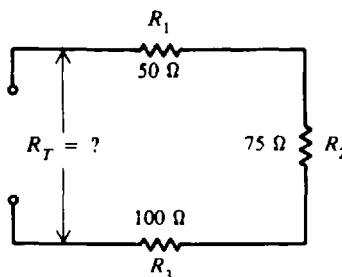


Fig. 4-2

Use Eq. (4-1) and add the values of the three resistors in series.

$$R_T = R_1 + R_2 + R_3 = 50 + 75 + 100 = 225 \Omega \quad \text{Ans.}$$

The total voltage across a series circuit is equal to the sum of the voltages across each resistance of the circuit (Fig. 4-3), or

$$V_T = V_1 + V_2 + V_3 \quad (4-2)$$

where  $V_T$  = total voltage, V  
 $V_1$  = voltage across resistance  $R_1$ , V  
 $V_2$  = voltage across resistance  $R_2$ , V  
 $V_3$  = voltage across resistance  $R_3$ , V

Although Eqs. (4-1) and (4-2) were applied to circuits containing only three resistances, they are applicable to any number of resistances  $n$ ; that is,

$$R_T = R_1 + R_2 + R_3 + \cdots + R_n \quad (4-1a)$$

$$V_T = V_1 + V_2 + V_3 + \cdots + V_n \quad (4-2a)$$

Ohm's law may be applied to an entire series circuit or to the individual parts of the circuit. When it is used on a particular part of a circuit, the voltage across that part is equal to the current in that part multiplied by the resistance of that part. For the circuit shown in Fig. 4-3,

$$V_1 = IR_1$$

$$V_2 = IR_2$$

$$V_3 = IR_3$$

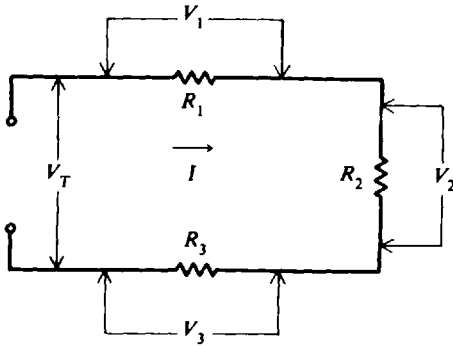


Fig. 4-3

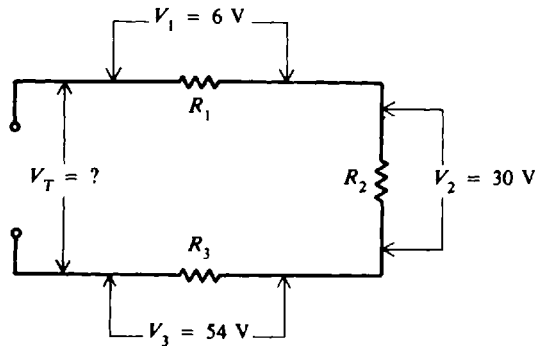


Fig. 4-4

**Example 4.2** A series circuit has 6 V across  $R_1$ , 30 V across  $R_2$ , and 54 V across  $R_3$  (Fig. 4-4). What is the total voltage across the circuit?

Write Eq. (4-2) and add the voltage across each of the three resistances.

$$V_T = V_1 + V_2 + V_3 = 6 + 30 + 54 = 90 \text{ V} \quad \text{Ans.}$$

To find the total voltage across a series circuit, multiply the current by the total resistance, or

$$V_T = IR_T \quad (4-3)$$

where  $V_T$  = total voltage, V  
 $I$  = current, A  
 $R_T$  = total resistance,  $\Omega$

Remember that in a series circuit the same current flows in every part of the circuit. Do not add the currents in each part of the circuit to obtain  $I$  in the Eq. (4-3).

**Example 4.3** A resistor of  $45 \Omega$  and a bell of  $60 \Omega$  are connected in series (Fig. 4-5). What voltage is required across this combination to produce a current of 0.3 A?

**Step 1.** Find the current  $I$ . The value of the current is the same in each part of a series circuit.

$$I = 0.3 \text{ A} \quad (\text{Given})$$

**Step 2.** Find the total resistance  $R_T$ . Add the two resistances.

$$\begin{aligned} R_T &= R_1 + R_2 \\ &= 45 + 60 = 105 \Omega \end{aligned} \quad (4-1)$$

**Step 3.** Find the total voltage  $V_T$ . Use Ohm's law.

$$\begin{aligned} V_T &= IR_T \\ &= 0.3(105) = 31.5 \text{ V} \end{aligned} \quad \text{Ans.} \quad (4-3)$$

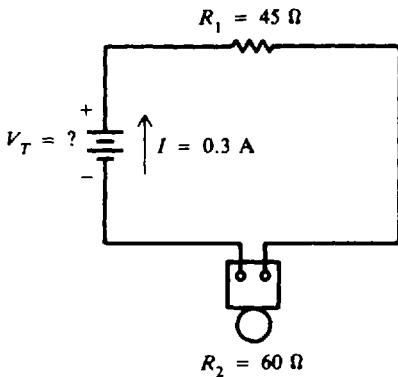


Fig. 4-5

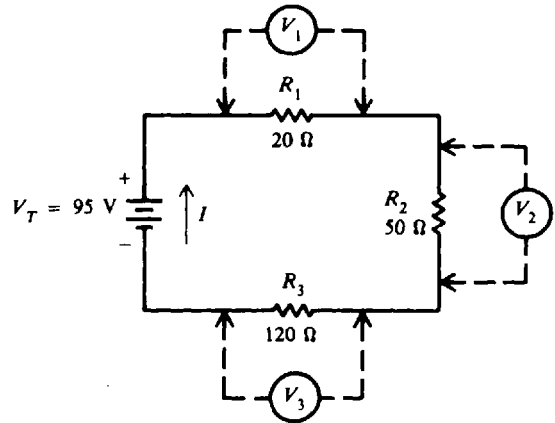


Fig. 4-6

**Example 4.4** A 95-V battery is connected in series with three resistors: 20  $\Omega$ , 50  $\Omega$ , and 120  $\Omega$  (Fig. 4-6). Find the voltage across each resistor.

**Step 1.** Find the total resistance  $R_T$ .

$$\begin{aligned} R_T &= R_1 + R_2 + R_3 \\ &= 20 + 50 + 120 = 190 \Omega \end{aligned} \quad (4-1)$$

**Step 2.** Find the current  $I$ . Write Ohm's law,

$$V_T = IR_T \quad (4-3)$$

from which we get

$$I = \frac{V_T}{R_T} = \frac{95}{190} = 0.5 \text{ A}$$

**Step 3.** Find the voltage across each part. In a series circuit, the current is the same in each part; that is,  $I = 0.5 \text{ A}$  through each resistor.

$$\begin{aligned} V_1 &= IR_1 = 0.5(20) = 10 \text{ V} && \text{Ans.} \\ V_2 &= IR_2 = 0.5(50) = 25 \text{ V} && \text{Ans.} \\ V_3 &= IR_3 = 0.5(120) = 60 \text{ V} && \text{Ans.} \end{aligned}$$

The voltages  $V_1$ ,  $V_2$ , and  $V_3$  found in Example 4.4 are known as *voltage drops* or *IR drops*. Their effect is to reduce the voltage that is available to be applied across the rest of the components in the circuit. The sum of the voltage drops in any series circuit is always equal to the voltage that is applied to the circuit. This relationship is expressed in Eq. (4-2), where the total voltage  $V_T$  is the same as the applied voltage, and can be verified in Example 4.4.

$$\begin{aligned} V_T &= V_1 + V_2 + V_3 \\ 95 &= 10 + 25 + 60 \\ 95 \text{ V} &= 95 \text{ V} \quad \text{Check} \end{aligned}$$

**POLARITY OF VOLTAGE DROPS**

When there is a voltage drop across a resistance, one end must be more positive or more negative than the other end. The polarity of the voltage drop is determined by the direction of conventional current from a positive to a more negative potential. Current direction is through  $R_1$  from point  $A$  to  $B$  (Fig. 4-7). Therefore the end of  $R_1$  connected to point  $A$  has a more positive potential than point  $B$ . We say that the voltage across  $R_1$  is such that point  $A$  is more positive than point  $B$ . Similarly, the voltage of point  $C$  is positive with respect to point  $D$ . Another way to look at polarity between any two points is that the one nearer to the positive terminal of the voltage source is more positive; also, the point nearer to the negative terminal of the applied voltage is more negative. Therefore, point  $A$  is more positive than  $B$ , while  $D$  is more negative than  $C$  (Fig. 4-7).

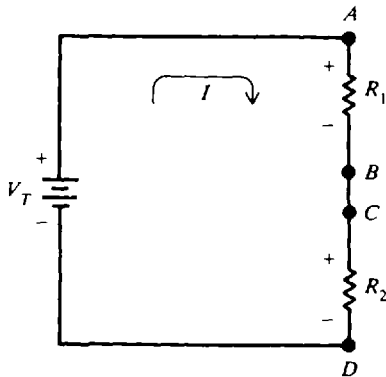


Fig. 4-7 Polarity of voltage drops

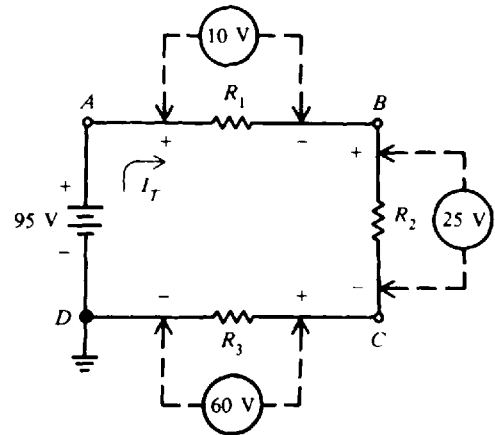


Fig. 4-8

**Example 4.5** Refer to Example 4.4. Ground the negative terminal of the 95-V battery (Fig. 4-6). Mark the polarity of voltage drops in the circuit (Fig. 4-8), and find the voltage values at points  $A$ ,  $B$ ,  $C$ , and  $D$  with respect to ground.

Trace the complete circuit in the direction of current from the positive terminal of the battery to  $A$ ,  $A$  to  $B$ ,  $B$  to  $C$ ,  $C$  to  $D$ , and  $D$  to the negative terminal. Mark plus (+) where current enters each resistor and minus (-) where current leaves each resistor (Fig. 4-8).

The voltage drops calculated in Example 4.4 are indicated (Fig. 4-8). Point  $A$  is the nearest point to the positive side of the terminal, so voltage at  $A$  is

$$V_A = +95 \text{ V} \quad \text{Ans.}$$

There is a voltage drop of 10 V across  $R_1$ , so voltage at  $B$  is

$$V_B = 95 - 10 = +85 \text{ V} \quad \text{Ans.}$$

There is a voltage drop of 25 V across  $R_2$ , so voltage at  $C$  is

$$V_C = 85 - 25 = +60 \text{ V} \quad \text{Ans.}$$

There is a voltage drop of 60 V across  $R_3$ , so voltage at  $D$  is

$$V_D = 60 - 60 = 0 \text{ V} \quad \text{Ans.}$$

Since we grounded the circuit at  $D$ ,  $V_D$  must equal 0 V. If on tracing the voltage values, we find that  $V_D$  is not equal to 0 V, then we have made an error.

**CONDUCTORS**

A conductor is a material having many free electrons. Three good electrical conductors are copper, silver, and aluminum. Generally most metals are good conductors. Copper is the most



common material used in electrical conductors. Second to copper is aluminum. Certain gases are also used as conductors under special conditions. For example, neon gas, mercury vapor, and sodium vapor are used in various kinds of lamps.

Conductors have very low resistance. A typical value for copper wire is less than  $1\ \Omega$  for 10 feet (ft). The function of the wire conductor is to connect a source of applied voltage to a load resistance with a minimum  $IR$  voltage drop in the conductor so that most of the applied voltage can produce current in the load resistance.

**Example 4.6** The resistance of two 10-ft lengths of copper wire conductors is about  $0.05\ \Omega$ , which is very small compared with the  $150\text{-}\Omega$  resistance of the tungsten filament in the bulb shown in Fig. 4-9a. The conductors should have minimum resistance to light the bulb with full brilliance. When the current of  $0.8\ \text{A}$  flows in the bulb and series conductors, the  $IR$  voltage drop across the conductors is  $0.04\ \text{V}$ , with  $109.96\ \text{V}$  across the bulb (Fig. 4-9b). Practically all the applied voltage of  $110\ \text{V}$  is across the filament of the bulb.

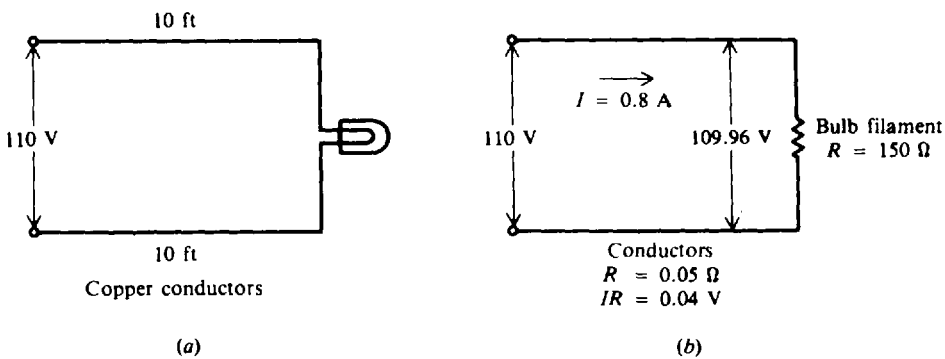


Fig. 4-9

### Wire Measurement

Table 4-1 lists the standard wire sizes which correspond to the American Wire Gauge (AWG). The gauge numbers specify the size of round wire in terms of its diameter and cross-sectional circular area. Note the following:

1. As the gauge numbers increase from 1 to 40, the diameter and circular area decrease. Higher gauge numbers mean smaller wire sizes. Thus, No. 12 is a smaller wire than No. 4.
2. The circular area doubles for every three gauge sizes. For example, No. 12 wire has about twice the area of No. 15 wire.
3. The higher the gauge number and the smaller the wire, the greater the resistance of the wire for any given length. Therefore, for 1000 ft of wire, No. 12 has a resistance of  $1.62\ \Omega$  while No. 4 has  $0.253\ \Omega$ .

In typical house wiring applications, No. 14 or No. 12 wire is used for circuits where the current is not expected to exceed  $15\ \text{A}$ . Hookup wire for radio receiver circuits with current in milliamperes is about No. 22 wire. For this size,  $0.5$  to  $1\ \text{A}$  is the maximum current the wire can carry without excessive heating.

The cross-sectional area of round wire is measured in circular mils (abbreviated cmil or CM). A mil is one-thousandth of an inch ( $0.001\ \text{in}$ ). One circular mil is the cross-sectional area of a wire having a diameter of one mil. The number of circular mils in any circular area is equal to the square of the diameter in mils, or

$$\text{cmil} = \text{CM} = d^2 \quad (4-4)$$

Table 4-1 Copper Wire Table

Gauge No.	Diameter, <i>d</i> , mil	Circular-mil Area, <i>d</i> <sup>2</sup>	Ohms per 1000 ft of Copper Wire at 25°C*	Gauge No.	Diameter, <i>d</i> , mil	Circular-mil Area, <i>d</i> <sup>2</sup>	Ohms per 1000 ft of Copper Wire at 25°C*
1	289.3	83 690	0.1264	21	28.46	810.1	13.05
2	257.6	66 370	0.1593	22	25.35	642.4	16.46
3	229.4	52 640	0.2009	23	22.57	509.5	20.76
4	204.3	41 740	0.2533	24	20.10	404.0	26.17
5	181.9	33 100	0.3195	25	17.90	320.4	33.00
6	162.0	26 250	0.4028	26	15.94	254.1	41.62
7	144.3	20 820	0.5080	27	14.20	201.5	52.48
8	128.5	16 510	0.6405	28	12.64	159.8	66.17
9	114.4	13 090	0.8077	29	11.26	126.7	83.44
10	101.9	10 380	1.018	30	10.03	100.5	105.2
11	90.74	8 234	1.284	31	8.928	79.70	132.7
12	80.81	6 530	1.619	32	7.950	63.21	167.3
13	71.96	5 178	2.042	33	7.080	50.13	211.0
14	64.08	4 107	2.575	34	6.305	39.75	266.0
15	57.07	3 257	3.247	35	5.615	31.52	335.0
16	50.82	2 583	4.094	36	5.000	25.00	423.0
17	45.26	2 048	5.163	37	4.453	19.83	533.4
18	40.30	1 624	6.510	38	3.965	15.72	672.6
19	35.89	1 288	8.210	39	3.531	12.47	848.1
20	31.96	1 022	10.35	40	3.145	9.88	1069

\*20 to 25°C or 68 to 77°F is considered average room temperature.

**Example 4.7** Find the area in circular mils of a wire with a diameter of 0.004 in.

First, convert the diameter to mils: 0.004 in = 4 mil. Then use Eq. (4-4) to find the cross-sectional area.

$$CM = d^2 = (4 \text{ mil})^2 = 16 \quad \text{Ans.}$$

To prevent the conductors from short-circuiting to each other or to some other metal in the circuit, the wires are insulated. The insulator material should have very high resistance, be tough, and age without becoming brittle.

**Resistivity**

For any conductor, the resistance of a given length depends upon the resistivity of the material, the length of the wire, and the cross-sectional area of the wire according to the formula

$$R = \rho \frac{l}{A} \tag{4-5}$$

- where *R* = resistance of the conductor, Ω
- l* = length of the wire, ft
- A* = cross-sectional area of the wire, CM
- ρ* = specific resistance or resistivity, CM · Ω/ft

The factor  $\rho$  (Greek letter rho, pronounced “roe”) permits different materials to be compared for resistance according to their nature without regard to different lengths or areas. Higher values of  $\rho$  mean more resistance.

Table 4-2 lists resistance values for different metals having the standard wire size of a 1-ft length with a cross-sectional area of 1 CM. Since silver, copper, gold, and aluminum have the lowest values of resistivity, they are the best conductors. Tungsten and iron have a much higher resistivity.

**Table 4-2 Properties of Conducting Materials\***

Material	$\rho$ = Specific Resistance, at 20°C, CM · Ω/ft	Temperature Coefficient, Ω per °C, $\alpha$
Aluminum	17	0.004
Carbon	†	-0.0003
Constantan	295	0 (average)
Copper	10.4	0.004
Gold	14	0.004
Iron	58	0.006
Nichrome	676	0.0002
Nickel	52	0.005
Silver	9.8	0.004
Tungsten	33.8	0.005

\*Listings approximate only, since precise values depend on exact composition of material.

†Carbon has about 2500 to 7500 times the resistance of copper. Graphite is a form of carbon.

**Example 4.8** What is the resistance of 500 ft of No. 20 copper wire?

From Table 4-1, the cross-sectional area for No. 20 wire is 1022 CM. From Table 4-2,  $\rho$  for copper is 10.4 CM · Ω/ft. Use Eq. (4-5) to find the resistance of 500 ft of wire.

$$R = \rho \frac{l}{A} = (10.4) \times \left( \frac{500}{1022} \right) = 5.09 \Omega \quad \text{Ans.}$$

**Example 4.9** What is the resistance of 500 ft of No. 23 copper wire?

From Table 4-1,

$$A = 509.5 \text{ CM}$$

From Table 4-2,

$$\rho = 10.4 \text{ CM} \cdot \Omega/\text{ft}$$

Substituting into Eq. (4-5),

$$R = \rho \frac{l}{A} = (10.4) \times \left( \frac{500}{509.5} \right) = 10.2 \Omega \quad \text{Ans.}$$

Note from Examples 4.8 and 4.9 that the increase in gauge size of 3 from No. 20 to No. 23 gives one-half the circular area and doubles the resistance for the same wire length.

**Temperature Coefficient**

The temperature coefficient of resistance,  $\alpha$  (Greek letter alpha), indicates how much the resistance changes for a change in temperature. A positive value for  $\alpha$  means  $R$  increases with

temperature; a negative  $\alpha$  means  $R$  decreases; and a zero  $\alpha$  means  $R$  is constant, not varying with changes in temperature. Typical values of  $\alpha$  are listed in Table 4-2.

Although for a given material  $\alpha$  may vary slightly with temperature, an increase in wire resistance caused by a rise in temperature can be approximately determined from the equation

$$R_t = R_0 + R_0(\alpha \Delta T) \quad (4-6)$$

where  $R_t$  = higher resistance at higher temperature,  $\Omega$   
 $R_0$  = resistance at 20°C,  $\Omega$   
 $\alpha$  = temperature coefficient,  $\Omega/^\circ\text{C}$   
 $\Delta T$  = temperature rise above 20°C,  $^\circ\text{C}$

Note that carbon has a negative temperature coefficient (Table 4-2). In general,  $\alpha$  is negative for all semiconductors such as germanium and silicon. A negative value for  $\alpha$  means less resistance at higher temperatures. Therefore, the resistance of semiconductor diodes and transistors can be reduced considerably when they become hot with normal load current. Observe also that constantan has a value of zero for  $\alpha$  (Table 4-2). Thus it can be used for precision wire-wound resistors, which do not change resistance when the temperature increases.

**Example 4.10** A tungsten wire has a 10- $\Omega$  resistance at 20°C. Find its resistance at 120°C.  
 From Table 4-2,

$$\alpha = 0.005 \Omega/^\circ\text{C}$$

The temperature rise is

$$\Delta T = 120 - 20 = 100^\circ\text{C}$$

Substituting into Eq. (4-6),

$$R_t = R_0 + R_0(\alpha \Delta T) = 10 + 10(0.005 \times 100) = 10 + 5 = 15 \Omega \quad \text{Ans.}$$

Because of the 100°C rise in temperature, the wire resistance is increased by 5  $\Omega$ , or 50 percent of its original value of 10  $\Omega$ .

## TOTAL POWER IN A SERIES CIRCUIT

We found that Ohm's law could be used for total values in a series circuit as well as for individual parts of the circuit. Similarly, the formula for power may be used for total values.

$$P_T = IV_T \quad (4-7)$$

where  $P_T$  = total power, W  
 $I$  = current, A  
 $V_T$  = total voltage, V

The total power  $P_T$  produced by the source in a series circuit can also be expressed as the sum of the individual powers used in each part of the circuit.

$$P_T = P_1 + P_2 + P_3 + \cdots + P_n \quad (4-8)$$

where  $P_T$  = total power, W  
 $P_1$  = power used in first part, W  
 $P_2$  = power used in second part, W  
 $P_3$  = power used in third part, W  
 $P_n$  = power used in  $n$ th part, W

**Example 4.11** In the circuit shown (Fig. 4-10), find the total power  $P_T$  dissipated by  $R_1$  and  $R_2$ .

**Step 1.** Find  $I$  by Ohm's law.

$$I = \frac{V_T}{R_T} = \frac{V_T}{R_1 + R_2} = \frac{60}{5 + 10} = 4 \text{ A}$$

**Step 2.** Find the power used in  $R_1$  and  $R_2$ .

$$P_1 = I^2 R_1 = 4^2(5) = 80 \text{ W}$$

$$P_2 = I^2 R_2 = 4^2(10) = 160 \text{ W}$$

**Step 3.** Find the total power  $P_T$  by adding  $P_1$  and  $P_2$ .

$$P_T = P_1 + P_2 = 80 + 160 = 240 \text{ W} \quad \text{Ans.}$$

An alternative method is to use Eq. (4-7) directly.

$$P_T = IV_T$$

$$I = 4 \text{ A}$$

$$P_T = 4(60) = 240 \text{ W} \quad \text{Ans.}$$

Calculated either way, the total power produced by the battery is 240 W and equals the power used by the load.

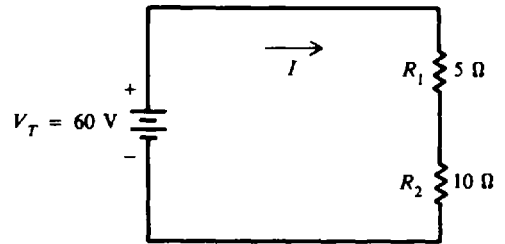


Fig. 4-10

### VOLTAGE DROP BY PROPORTIONAL PARTS

In a series circuit, each resistance provides a voltage drop  $V$  equal to its proportional part of the applied voltage. Stated as an equation,

$$V = \frac{R}{R_T} V_T \quad (4-9)$$

where  $V$  = voltage, V  
 $R$  = resistance,  $\Omega$   
 $R_T$  = total resistance,  $\Omega$   
 $R/R_T$  = proportional part of resistance  
 $V_T$  = total voltage, V

A higher resistance  $R$  has a greater voltage drop than a smaller resistance in the same series circuit. Equal resistances have equal voltage drops.

**Example 4.12** The circuit (Fig. 4-11) is an example of a proportional voltage divider. Find the voltage drop across each resistor by the method of proportional parts.

Write the formulas, using Eq. (4-9).

$$V_1 = \frac{R_1}{R_T} V_T \quad V_2 = \frac{R_2}{R_T} V_T \quad V_3 = \frac{R_3}{R_T} V_T$$

Find  $R_T$ .

$$R_T = R_1 + R_2 + R_3 = 20 + 30 + 50 = 100 \text{ k}\Omega$$

Substitute values.

$$V_1 = \frac{20}{100} 100 = 20 \text{ V} \quad \text{Ans.}$$

$$V_2 = \frac{30}{100} 100 = 30 \text{ V} \quad \text{Ans.}$$

$$V_3 = \frac{50}{100} 100 = 50 \text{ V} \quad \text{Ans.}$$

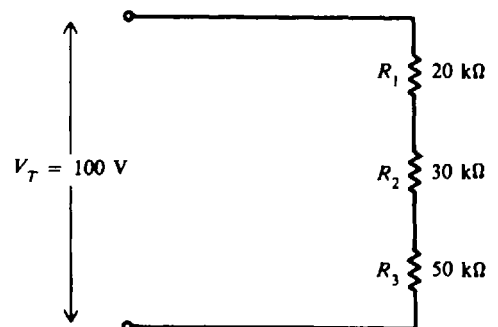


Fig. 4-11

The formula for the proportional method is derived from Ohm's law. For example, add  $V_1$ ,  $V_2$ , and  $V_3$  to obtain

$$V_1 + V_2 + V_3 = \frac{R_1}{R_T} V_T + \frac{R_2}{R_T} V_T + \frac{R_3}{R_T} V_T$$

Factor the right side of the equation.

$$V_1 + V_2 + V_3 = \frac{V_T}{R_T} (R_1 + R_2 + R_3)$$

Use the relationships

$$V_T = V_1 + V_2 + V_3$$

$$R_T = R_1 + R_2 + R_3$$

and substitute.

$$V_T = \frac{V_T}{R_T} R_T = V_T \quad \text{Check}$$

### Solved Problems

4.1 Find the voltage needed so that a current of 10 A will flow through the series circuit shown in Fig. 4-12a.

Step 1. Find total resistance.

$$R_T = R_1 + R_2 + R_3 = 2 + 3 + 5 = 10 \Omega \tag{4-1}$$

Step 2. Find the voltage (we show the series circuit with  $R_T$  in Fig. 4-12b).

$$V_T = IR_T = 10(10) = 100 \text{ V} \quad \text{Ans.} \tag{4-3}$$

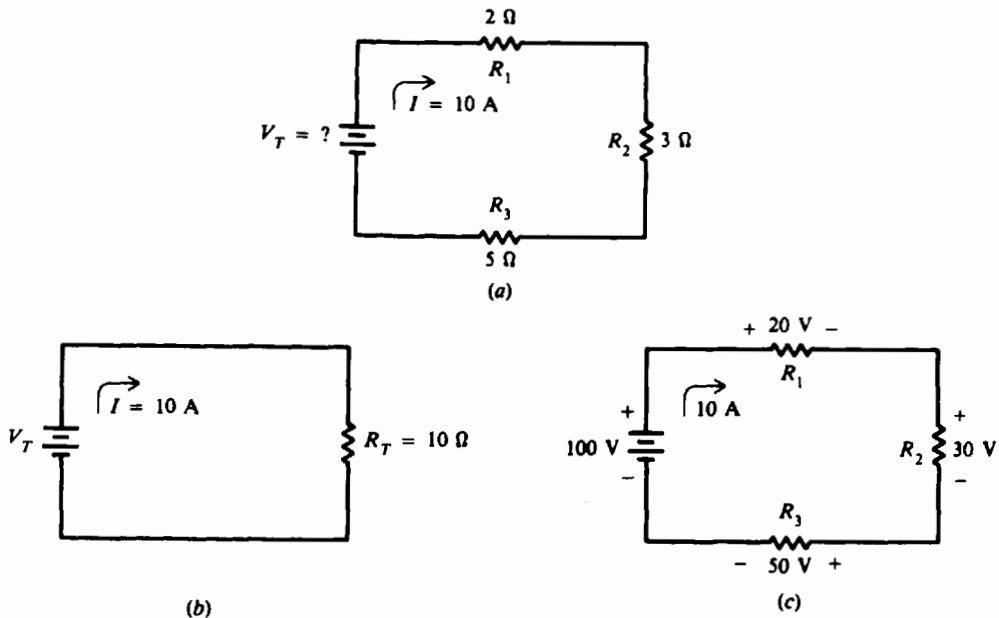


Fig. 4-12

- 4.2 Find the voltage across each resistor in the circuit of Fig. 4-12a. Show that the sum of the voltage drops equals the applied voltage of 100 V.

$$V_1 = IR_1 = 10(2) = 20 \text{ V} \quad \text{Ans.}$$

$$V_2 = IR_2 = 10(3) = 30 \text{ V} \quad \text{Ans.}$$

$$V_3 = IR_3 = 10(5) = 50 \text{ V} \quad \text{Ans.}$$

See Fig. 4-12c. Remember that the polarity signs next to the resistors indicate the direction of voltage drops not current direction as the + and - next to the source indicate.

Sum of voltage drops = applied voltage

$$V_1 + V_2 + V_3 = V_T \quad (4-2)$$

$$20 + 30 + 50 = 100$$

$$100 \text{ V} = 100 \text{ V} \quad \text{Check}$$

- 4.3 In Fig. 4-13, a 12-V battery supplies a current of 2 A. If  $R_2 = 2 \Omega$ , find  $R_1$  and  $V_1$ .

Step 1. Find  $R_T$ . By Ohm's law,

$$R_T = \frac{V_T}{I} = \frac{12}{2} = 6 \Omega$$

Step 2. Find  $R_1$ .

$$R_T = R_1 + R_2 \quad (4-1)$$

Transposing,

$$R_1 = R_T - R_2 = 6 - 2 = 4 \Omega \quad \text{Ans.}$$

Step 3. Find  $V_1$ .

$$V_1 = IR_1 = 2(4) = 8 \text{ V} \quad \text{Ans.}$$

An alternative method of solution is using voltage drops.

Step 1. Find  $V_1$ .

$$V_T = V_1 + V_2$$

Transposing,

$$V_1 = V_T - V_2 = 12 - V_2$$

But

$$V_2 = IR_2$$

so

$$V_1 = 12 - IR_2 = 12 - 2(2) = 12 - 4 = 8 \text{ V} \quad \text{Ans.}$$

Step 2. Find  $R_1$ .

$$R_1 = \frac{V_1}{I} = \frac{8}{2} = 4 \Omega \quad \text{Ans.}$$

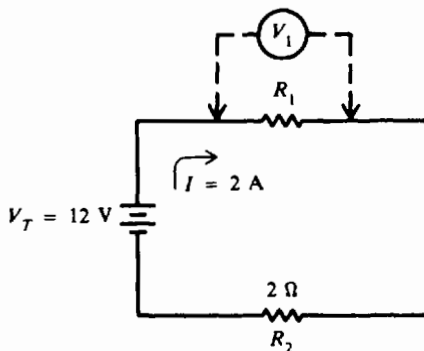


Fig. 4-13

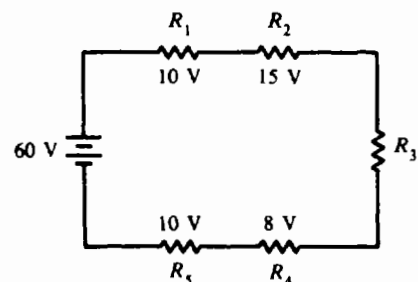


Fig. 4-14

4.4 For the circuit in Fig. 4-14, find the voltage drop of  $R_3$ .

$$\begin{aligned} \text{Sum of voltage drops} &= \text{applied voltage} \\ 10 + 15 + V_3 + 8 + 10 &= 60 \\ 43 + V_3 &= 60 \\ V_3 &= 60 - 43 = 17 \text{ V} \quad \text{Ans.} \end{aligned}$$

4.5 A series circuit (Fig. 4-15a) uses ground as a common connection and a reference point for voltage measurement. (The ground connection is at 0 V.) Mark the polarity of the voltage drops across the resistances  $R_1$ ,  $R_2$ , and find the voltage drops at points A and B with respect to ground.

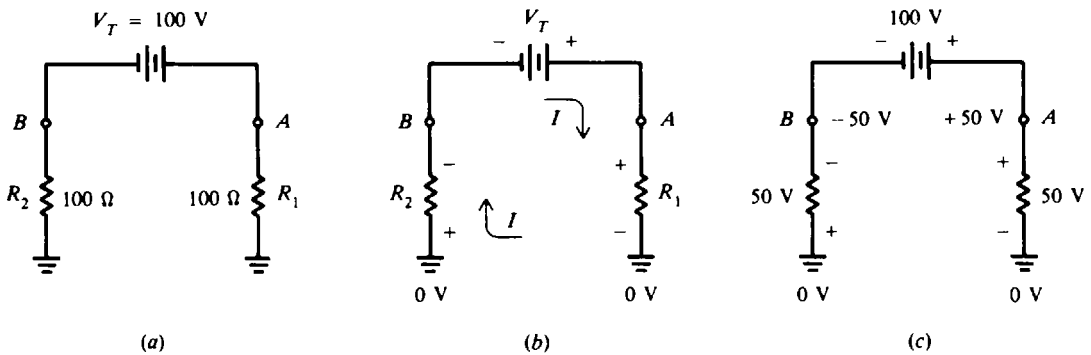


Fig. 4-15

**Step 1.** Mark the polarities. The current  $I$  flows from the positive terminal of the battery through  $R_1$ , through ground, up through  $R_2$ , and back to the negative terminal of the battery (Fig. 4-15b). Assign a + sign where the current enters the resistance and a - sign to the end where the current emerges (Fig. 4-15b). Mark the ground voltage 0 V as the reference to measure voltage drops.

**Step 2.** Find the total resistance, using Eq. (4-1)

$$R_T = R_1 + R_2 = 100 + 100 = 200 \Omega$$

**Step 3.** Find the current in the circuit.

$$I = \frac{V_T}{R_T} = \frac{100}{200} = 0.5 \text{ A}$$

**Step 4.** Find the voltage drops.

$$\begin{aligned} V_1 &= IR_1 = 0.5(100) = 50 \text{ V} \\ V_2 &= IR_2 = 0.5(100) = 50 \text{ V} \end{aligned}$$

**Step 5.** Find voltage polarity at points A and B. Point A is 50 V positive with respect to ground, while point B is 50 V negative with respect to ground (Fig. 4-15c). Point A is nearer to the positive terminal, while point B is nearer to the negative terminal.

**Step 6.** Verify the voltage drops.

$$\begin{aligned} \text{Sum of voltage drops} &= \text{applied voltage} \\ V_T &= V_1 + V_2 \\ 100 &= 50 + 50 \\ 100 \text{ V} &= 100 \text{ V} \quad \text{Check} \end{aligned}$$

4.6 The terminal voltage of the motor (Fig. 4-16) should be not less than 223 V at a rated current of 20 A. Utility voltage variations produce a minimum of 228 V at the panel. What size branch circuit conductors are needed?



Find the minimum allowable wire size for the voltage drop by calculating its resistance. The maximum voltage drop is  $228 - 223 = 5$  V. Then the maximum wire resistance is  $5/20 = 0.25 \Omega/500 \text{ ft} = 0.50 \Omega/1000 \text{ ft}$ . From Table 4-1, No. 6 wire is satisfactory since it has  $0.40 \Omega/1000 \text{ ft}$  (No. 7 wire has  $0.51 \Omega/1000 \text{ ft}$ ).

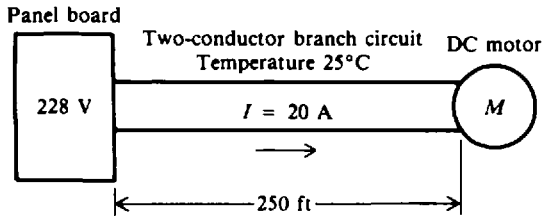


Fig. 4-16

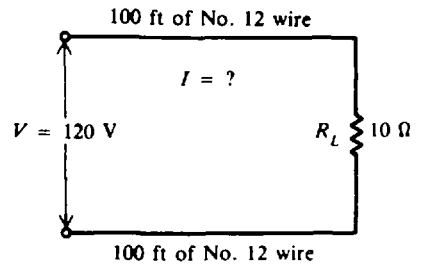


Fig. 4-17

- 4.7 How much current will flow in the circuit (Fig. 4-17) if No. 12 conductors are (a) copper, (b) tungsten, and (c) Nichrome? (Temperature is  $20^\circ\text{C}$ .)

(a) Copper conductor:

$$\rho = 10.4 \quad (\text{Table 4-2})$$

$$A = 6530 \text{ CM} \quad (\text{Table 4-1})$$

Copper conductor resistance:

$$\begin{aligned} R &= \rho \frac{l}{A} & (4-5) \\ &= \frac{10.4(200)}{6530} = 0.319 \Omega \end{aligned}$$

Total circuit resistance = conductor resistance + load resistance

$$R_T = R + R_L = 0.319 + 10 = 10.319 \Omega$$

$$I = \frac{V}{R_T} = \frac{120}{10.319} = 11.6 \text{ A} \quad \text{Ans.}$$

(b) Tungsten conductor:

$$\rho = 33.8 \quad (\text{Table 4-2})$$

$$A = 6530 \text{ CM} \quad (\text{equal diameter of copper conductor})$$

$$\begin{aligned} R &= \rho \frac{l}{A} & (4-5) \\ &= \frac{33.8(200)}{6530} = 1.035 \Omega \end{aligned}$$

$$R_T = R + R_L = 1.035 + 10 = 11.035 \Omega$$

$$I = \frac{V}{R_T} = \frac{120}{11.035} = 10.9 \text{ A} \quad \text{Ans.}$$

(c) Nichrome conductor:

$$\rho = 676 \quad (\text{Table 4-2})$$

$$A = 6530 \text{ CM} \quad (\text{equal diameter of copper conductor})$$

$$\begin{aligned} R &= \rho \frac{l}{A} & (4-5) \\ &= \frac{676(200)}{6530} = 20.7 \Omega \end{aligned}$$

$$R_T = R + R_L = 20.7 + 10 = 30.7 \Omega$$

$$I = \frac{V}{R_T} = \frac{120}{30.7} = 3.91 \text{ A} \quad \text{Ans.}$$

Notice that as the factor  $\rho$  increases, the circuit resistance increases and the circuit current decreases.

- 4.8** Five lamps are connected in series (Fig. 4-18). Each lamp requires 16 V and 0.1 A. Find the total power used.

The total voltage  $V_T$  equals the sum of the individual voltages across all parts in the series circuit.

$$\begin{aligned} V_T &= V_1 + V_2 + V_3 + V_4 + V_5 \\ &= 16 + 16 + 16 + 16 + 16 = 80 \text{ V} \end{aligned} \quad (4-2)$$

The current through each resistance (lamp) is the single current in the series circuit.

$$I = 0.1 \text{ A}$$

So the total power is 
$$P_T = IV_T = 0.1(80) = 8 \text{ W} \quad \text{Ans.} \quad (4-7)$$

Also total power is the sum of the individual powers.

For one lamp, 
$$P_1 = V_1 I = 16(0.1) = 1.6 \text{ W}$$

For five lamps, 
$$P_T = 5P_1 = 5(1.6) = 8 \text{ W} \quad \text{Ans.}$$

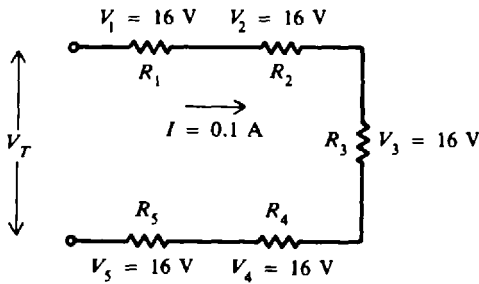


Fig. 4-18

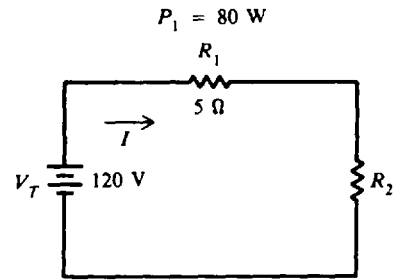


Fig. 4-19

- 4.9** Find  $I$ ,  $V_1$ ,  $V_2$ ,  $P_2$ , and  $R_2$  in the circuit shown (Fig. 4-19).

**Step 1.** Find  $I$ .

Use the power formula,  $P_1 = I_1^2 R_1$ . Then

$$I_1^2 = \frac{P_1}{R_1} = \frac{80}{5} = 16$$

Taking the square root,

$$I_1 = \sqrt{16} = 4 \text{ A}$$

Since this is a series circuit,

$$I = I_1 = 4 \text{ A} \quad \text{Ans.}$$

**Step 2.** Find  $V_1$ ,  $V_2$ .

$$V_1 = IR_1 = 4(5) = 20 \text{ V} \quad \text{Ans.}$$

$$V_2 = V_T - V_1 = 120 - 20 = 100 \text{ V} \quad \text{Ans.}$$

**Step 3.** Find  $P_2$ ,  $R_2$ .

$$P_2 = V_2 I = 100(4) = 400 \text{ W} \quad \text{Ans.}$$

$$R_2 = \frac{V_2}{I} = \frac{100}{4} = 25 \Omega \quad \text{Ans.}$$

- 4.10 Three  $20\text{-k}\Omega$  resistors  $R_1$ ,  $R_2$ , and  $R_3$  are in series across an applied voltage of  $120\text{ V}$ . What is the voltage drop across each resistor?

Since  $R_1$ ,  $R_2$ , and  $R_3$  are equal, each has exactly one-third the total resistance of the series circuit and one-third the total voltage drop. So

$$V = \frac{1}{3} 120 = 40\text{ V} \quad \text{Ans.}$$

- 4.11 Use the voltage-divider method to find voltage drop (Fig. 4-20) across each resistor.

$$V_1 = \frac{R_1}{R_T} V_T = \frac{3}{10} 10 = 3\text{ V} \quad \text{Ans.}$$

$$V_2 = \frac{R_2}{R_T} V_T = \frac{7}{10} 10 = 7\text{ V} \quad \text{Ans.}$$

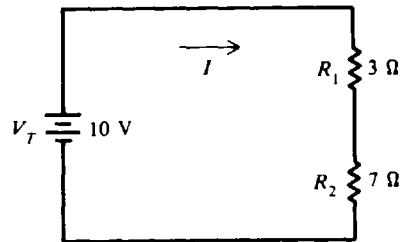


Fig. 4-20

An important advantage of using the voltage-divider formula is that we can find the voltage drops from  $V_T$  and the resistances without finding the current.

If we found the current first, then we could calculate the voltage drop by multiplying current and resistance. For example,

$$I = \frac{V_T}{R_T} = \frac{V_T}{R_1 + R_2} = \frac{10}{3 + 7} = \frac{10}{10} = 1\text{ A}$$

Then

$$V_1 = IR_1 = 1(3) = 3\text{ V} \quad \text{Check}$$

$$V_2 = IR_2 = 1(7) = 7\text{ V} \quad \text{Check}$$

- 4.12 Compare the effect on voltage drop of a  $1\text{-}\Omega$  resistor and a  $99\text{-}\Omega$  resistor in series.

Because series voltage drops are proportional to the resistances, a very small resistance ( $1\ \Omega$ ) has a very small effect in series with a much larger resistance ( $99\ \Omega$ ). For example, if the applied voltage were  $100\text{ V}$ , the voltage drop across the  $1\text{-}\Omega$  resistor would be  $1\text{ V}$  [ $(1/100)(100) = 1\text{ V}$ ], while across the  $99\text{-}\Omega$  resistor it would be  $99\text{ V}$  [ $(99/100)(100) = 99\text{ V}$ ].

- 4.13 A voltage of  $5\text{ V}$  is to be made available from a  $12\text{-V}$  source using a two-resistor voltage divider (Fig. 4-21). The current in the divider is to be  $100\text{ mA}$ . Find the values for resistors  $R_1$  and  $R_2$ .

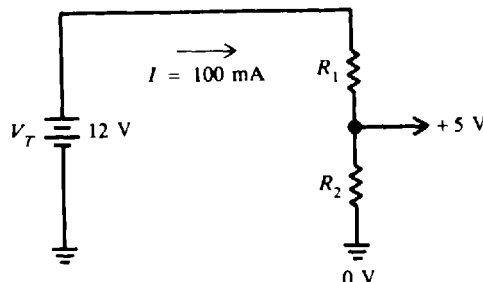


Fig. 4-21

**Step 1.** Find  $R_T$ .

$$R_T = \frac{V_T}{I} = \frac{12}{100 \times 10^{-3}} = 120 \Omega$$

**Step 2.** Find  $R_1$ . From Fig. 4-21, tracing the voltage across the resistors from ground at 0 V, we have 5 V across  $R_2$  ( $V_2 = 5$  V), so that there is 7 V across  $R_1$  ( $V_1 = 7$  V) for a total of 12 V ( $V_T = 12$  V). Use the voltage-divider formula.

$$V_1 = \frac{R_1}{R_T} V_T \quad (4-9)$$

Then 
$$\frac{R_1}{R_T} = \frac{V_1}{V_T} = \frac{7}{12}$$

The ratio of the two resistors is known because the ratio of the two voltages is 7/12. So

$$R_1 = \frac{7}{12} R_T = \frac{7}{12} 120 = 70 \Omega \quad \text{Ans.}$$

**Step 3.** Find  $R_2$ .


$$R_T = R_1 + R_2$$

Transpose and substitute.

$$R_2 = R_T - R_1 = 120 - 70 = 50 \Omega \quad \text{Ans.}$$

### Supplementary Problems

- 4.14** What is the total resistance of three 20- $\Omega$  resistors connected in series? *Ans.* 60  $\Omega$
- 4.15** A car has a 3-V, 1.5- $\Omega$  dash light and a 3-V, 1.5- $\Omega$  taillight connected in series to a battery delivering 2 A (Fig. 4-22). Find the battery voltage and total resistance of the circuit.  
*Ans.*  $V_T = 6$  V;  $R_T = 3.0 \Omega$

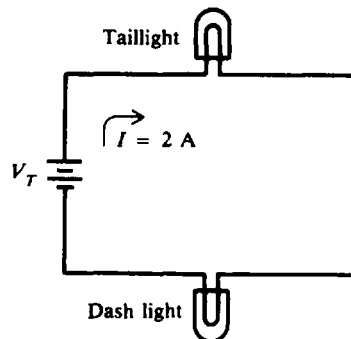

**Fig. 4-22**

- 4.16** A 3- $\Omega$ , a 5- $\Omega$  and a 4- $\Omega$  resistor are connected in series across a battery. The voltage drop across a 3- $\Omega$  resistor is 6 V. What is the battery voltage? *Ans.* 24 V
- 4.17** If three resistors are connected in series across a 12-V battery and the voltage drop across one resistor is 3 V and the voltage drop across the second resistor is 7 V, what is the voltage drop across the third resistor? *Ans.* 2 V
- 4.18** A lamp using 10 V, a 10- $\Omega$  resistor drawing 4 A, and a 24-V motor are connected in series. Find the total voltage and the total resistance. *Ans.*  $V_T = 74$  V;  $R_T = 18.5 \Omega$
- 4.19** Find all missing values of current, voltage, and resistance in a high-voltage regulator circuit in a color television receiver (Fig. 4-23). The voltage drop across each resistor is used to supply voltage in other parts of the receiver.  
*Ans.*  $V_1 = 700$  V,  $I_2 = 0.07$  mA;  $V_2 = 105$  V,  $I_3 = 0.07$  mA;  
 $R_3 = 500$  k $\Omega$ ,  $V_T = 840$  V;  $R_T = 12$  M $\Omega$ ,  $I = 0.07$  mA

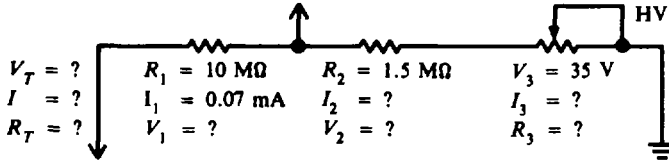


Fig. 4-23

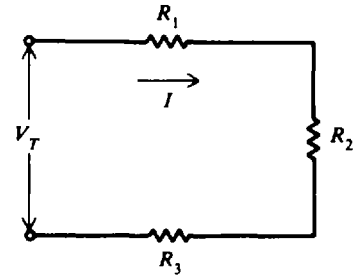


Fig. 4-24

- 4.20 Given  $I = 2 \text{ A}$ ,  $R_1 = 10 \Omega$ ,  $V_2 = 50 \text{ V}$ , and  $V_3 = 40 \text{ V}$ , find  $V_1$ ,  $V_T$ ,  $R_2$ ,  $R_3$ , and  $R_T$  (Fig. 4-24).  
 Ans.  $V_1 = 20 \text{ V}$ ;  $V_T = 110 \text{ V}$ ;  $R_2 = 25 \Omega$ ;  $R_3 = 20 \Omega$ ;  $R_T = 55 \Omega$
- 4.21 A current of  $3 \text{ mA}$  flows through a resistor that is connected to a  $1.5\text{-V}$  dry cell. If three additional  $1.5\text{-V}$  cells are connected in series to the first cell, find the current flowing through the resistor. Ans.  $I = 0.012 \text{ A} = 12 \text{ mA}$
- 4.22 A voltage divider consists of a  $3000\text{-}\Omega$ , a  $5000\text{-}\Omega$ , and a  $10\,000\text{-}\Omega$  resistor in series. The series current is  $15 \text{ mA}$ . Find (a) the voltage drop across each resistance, (b) the total voltage, and (c) the total resistance. Ans. (a)  $V_1 = 45 \text{ V}$ ,  $V_2 = 75 \text{ V}$ ,  $V_3 = 150 \text{ V}$ ; (b)  $V_T = 270 \text{ V}$ ; (c)  $R_T = 18\,000 \Omega$
- 4.23 A dc circuit to a specialized transistor circuit can be represented as shown in Fig. 4-25. Find the total resistance and voltage between points A and B. Ans.  $R_T = 50 \text{ k}\Omega$ ;  $V_{AB} = 30 \text{ V}$

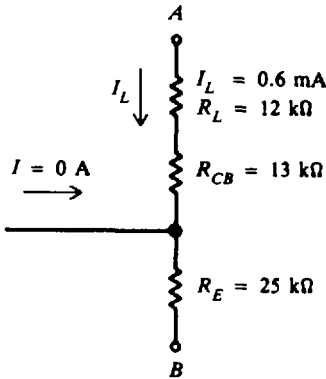


Fig. 4-25

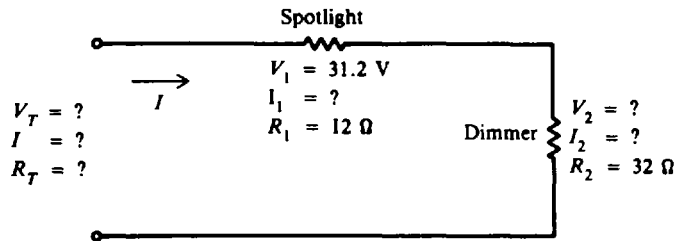


Fig. 4-26

- 4.24 A  $12\text{-}\Omega$  spotlight in a theater is connected in series with a dimming resistor of  $32 \Omega$  (Fig. 4-26). If the voltage drop across the light is  $31.2 \text{ V}$ , find the missing values indicated in Fig. 4-26.  
 Ans.  $I_1 = I_2 = I = 2.6 \text{ A}$ ;  $V_2 = 83.2 \text{ V}$ ;  $V_T = 114.4 \text{ V}$ ;  $R_T = 44 \Omega$

- 4.25 Find all missing values of current, voltage, and resistance in the circuit shown in Fig. 4-27.  
 Ans.  $V_3 = 30 \text{ V}$ ;  
 $I = I_1 = I_2 = I_3 = 0.667 \text{ A}$ ;  
 $R_1 = 30 \Omega$ ;  
 $R_2 = 90 \Omega$ ;  
 $R_3 = 45 \Omega$

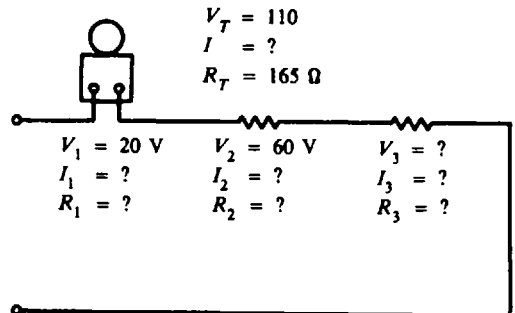


Fig. 4-27

- 4.26 Find voltage values at points A, B, C, and D shown in the circuit (Fig. 4-28) with respect to ground.  
 Ans.  $V_A = +60\text{ V}$ ;  $V_B = +50\text{ V}$ ;  $V_C = +30\text{ V}$ ;  $V_D = 0\text{ V}$

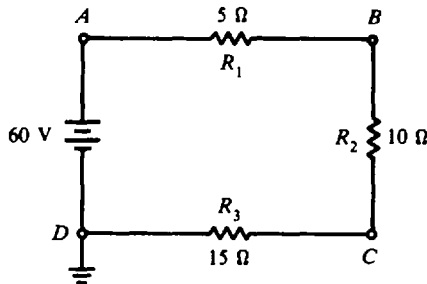


Fig. 4-28

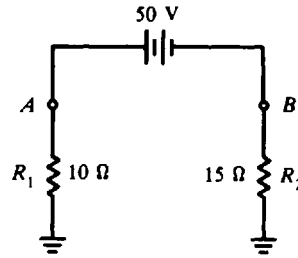


Fig. 4-29

- 4.27 Find the voltage at points A and B with respect to ground (Fig. 4-29).  
 Ans.  $V_A = +20\text{ V}$ ;  $V_B = -30\text{ V}$
- 4.28 A coil is wound with 4000 turns of No. 20 copper wire. If the average amount of wire in a turn is 3 in, how much is the total resistance of the coil? What will be its resistance if No. 25 wire is used instead? (The temperature is 25°C.)  
 Ans. 10.35 Ω, 33.0 Ω
- 4.29 Find the voltage drop across 1000 ft of No. 10 gauge copper wire connected to a 3-A load.  
 Ans. 3.05 V
- 4.30 If total line length is 200 ft, find the smallest size copper wire that will limit the line drop to 5 V with 115 V applied and a 6-A load.  
 Ans. No. 16 copper wire
- 4.31 A copper wire has a diameter of 0.031 96 in. Find (a) the circular-mil area, (b) its AWG size, and (c) the resistance of a 200-ft length.  
 Ans. (a) 1024 CM; (b) No. 20; (c) 2.07 Ω (for No. 20 wire)
- 4.32 What is the resistance of a 200-ft length of (a) No. 16 copper wire and (b) No. 20 aluminum wire? (Obtain diameter from Table 4-1.)  
 Ans. (a) 0.805 Ω; (b) 1.32 Ω
- 4.33 A copper conductor measures 0.8 Ω at 20°C. What is its resistance at 25°C?  
 Ans. 0.816 Ω
- 4.34 If a copper wire has a resistance of 4 Ω at 20°C, how much is its resistance at 75°C? If the wire is No. 10, what is its length in feet?  
 Ans. 4.88 Ω, 4800 ft
- 4.35 Calculate the load current  $I$  (Fig. 4-30) for the wire IR drop of 24.6 V with a supply of 115 V. Also find the value of  $R_L$ .  
 Ans.  $I = 30\text{ A}$ ;  $R_L = 3.01\text{ Ω}$

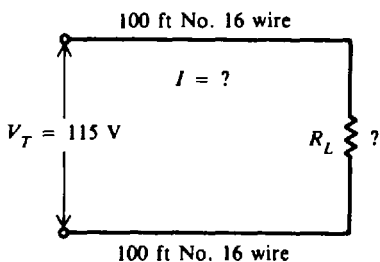


Fig. 4-30

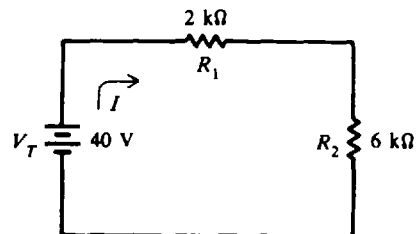


Fig. 4-31

- 4.36 Two resistors form the base-bias voltage divider for an audio amplifier. The voltage drops across them are 2.4 V and 6.6 V in the 1.5-mA circuit. Find the power used by each resistor and the total power used in milliwatts (mW).  
 Ans.  $P_1 = 3.6\text{ mW}$ ;  $P_2 = 9.9\text{ mW}$ ;  $P_T = 13.5\text{ mW}$

4.37 Find  $I$ ,  $V_1$ ,  $V_2$ ,  $P_1$ ,  $P_2$ , and  $P_T$  (Fig. 4-31).

Ans.  $I = 5 \text{ mA}$ ;  $V_1 = 10 \text{ V}$ ;  $V_2 = 30 \text{ V}$ ;  $P_1 = 50 \text{ mW}$ ;  $P_2 = 150 \text{ mW}$ ;  $P_T = 200 \text{ mW}$

4.38 Find  $V_1$ ,  $V_2$ ,  $V_3$ ,  $P_1$ ,  $P_2$ ,  $P_3$ ,  $P_T$ , and  $R_3$  (Fig. 4-32).

Ans.  $V_1 = 30 \text{ V}$ ;  $V_2 = 15 \text{ V}$ ;  $V_3 = 55 \text{ V}$ ;  $P_1 = 150 \text{ mW}$ ;  $P_2 = 75 \text{ mW}$ ;  $P_3 = 275 \text{ mW}$ ;  $P_T = 500 \text{ mW}$ ;  
 $R_3 = 11 \text{ k}\Omega$

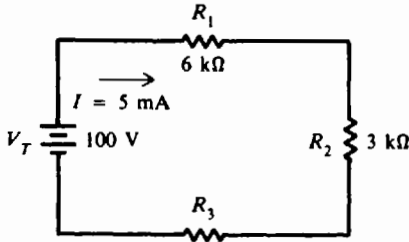


Fig. 4-32

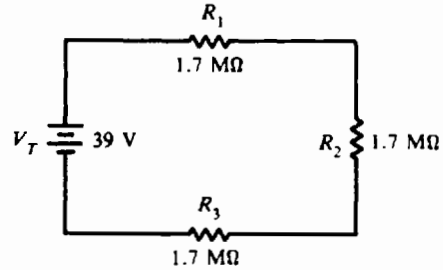


Fig. 4-33

4.39 Find  $P_T$ ,  $P_2$ , and  $V_3$  (Fig. 4-33). Ans.  $P_T = 298 \mu\text{W}$ ;  $P_2 = 99.5 \mu\text{W}$ ;  $V_3 = 13 \text{ V}$

4.40 A  $90\text{-}\Omega$  and a  $10\text{-}\Omega$  resistor are in series across a  $3\text{-V}$  source. Find the voltage drop across each resistor by the voltage-divider method. Ans.  $2.7 \text{ V}$ ,  $0.3 \text{ V}$

4.41 Eight  $10\text{-}\Omega$  resistances are in series across a  $120\text{-V}$  source. What is the voltage drop across each resistance? Ans.  $15 \text{ V}$

4.42 A potentiometer can be considered a simple two-resistor voltage divider (Fig. 4-34). To what resistance point would the control arm have to be set in a  $120\text{-}\Omega$  potentiometer to obtain  $2.5 \text{ V}$  between the arm (point A) of the potentiometer and ground (point B)? Ans.  $25\text{-}\Omega$  point from ground


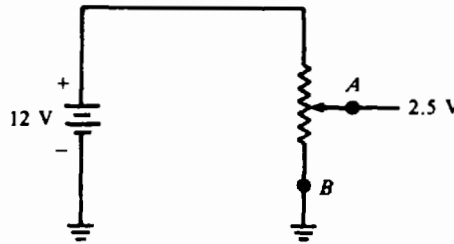


Fig. 4-34


4.43 Find the  $IR$  drop across each resistor in the following circuits by the voltage-divider method (Fig. 4-35).

Ans. (a)  $V_1 = 60 \text{ V}$ ;  $V_2 = 180 \text{ V}$  (b)  $V_1 = 25 \text{ V}$ ;  $V_2 = 50 \text{ V}$ ;  $V_3 = 35 \text{ V}$

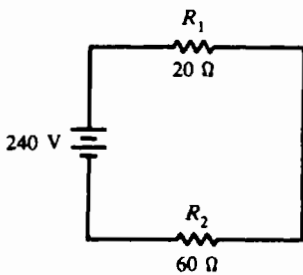
(c)  $V_1 = 11.5 \text{ V}$ ;  $V_2 = 23 \text{ V}$ ;  $V_3 = 34.5 \text{ V}$ ;  $V_4 = 46 \text{ V}$



(a)

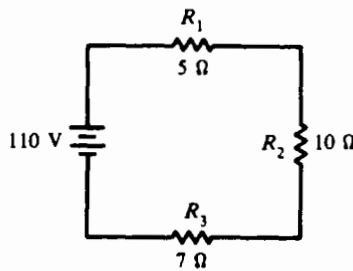

(b)

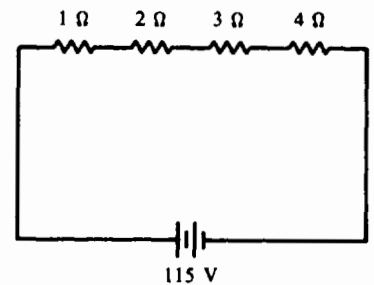

(c)

Fig. 4-35

# Chapter 5

## Direct-Current Parallel Circuits

### VOLTAGE AND CURRENT IN A PARALLEL CIRCUIT

A *parallel circuit* is a circuit in which two or more components are connected across the same voltage source (Fig. 5-1). The resistors  $R_1$ ,  $R_2$ , and  $R_3$  are in parallel with each other and with the battery. Each parallel path is then a branch with its own individual current. When the total current  $I_T$  leaves the voltage source  $V$ , part  $I_1$  of the current  $I_T$  will flow through  $R_1$ , part  $I_2$  will flow through  $R_2$ , and the remainder  $I_3$  through  $R_3$ . The branch currents  $I_1$ ,  $I_2$ , and  $I_3$  can be different. However, if a voltmeter (an instrument for measuring the voltage of a circuit) is connected across  $R_1$ ,  $R_2$ , and  $R_3$ , the respective voltages  $V_1$ ,  $V_2$ , and  $V_3$  will be equal. Therefore,

$$V = V_1 = V_2 = V_3 \quad (5-1)$$

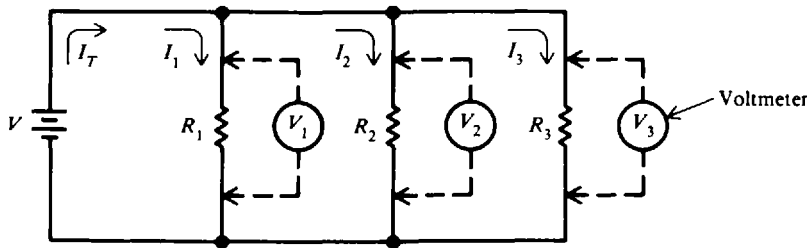


Fig. 5-1 A parallel circuit

The total current  $I_T$  is equal to the sum of all branch currents.

$$I_T = I_1 + I_2 + I_3 \quad (5-2)$$

This formula applies for any number of parallel branches whether the resistances are equal or unequal.

By Ohm's law, each branch current equals the applied voltage divided by the resistance between the two points where the voltage is applied. Hence (Fig. 5-1) for each branch we have the following equations:

$$\text{Branch 1:} \quad I_1 = \frac{V_1}{R_1} = \frac{V}{R_1}$$

$$\text{Branch 2:} \quad I_2 = \frac{V_2}{R_2} = \frac{V}{R_2} \quad (5-3)$$

$$\text{Branch 3:} \quad I_3 = \frac{V_3}{R_3} = \frac{V}{R_3}$$

With the same applied voltage, any branch that has less resistance allows more current through it than a branch with higher resistance.

**Example 5.1** Two lamps each drawing 2 A and a third lamp drawing 1 A are connected in parallel across a 110-V line (Fig. 5-2). What is the total current?

The formula for total current is

$$\begin{aligned} I_T &= I_1 + I_2 + I_3 \\ &= 2 + 2 + 1 = 5 \text{ A} \quad \text{Ans.} \end{aligned} \quad (5-2)$$

The total current is 5 A.



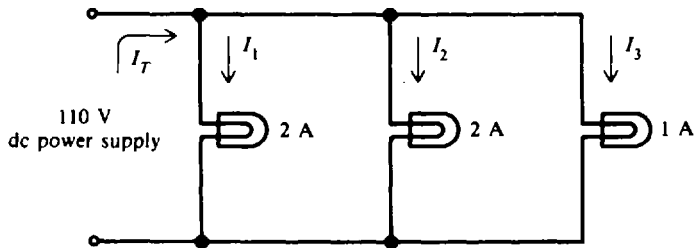


Fig. 5-2

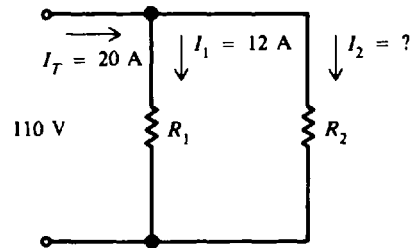


Fig. 5-3



**Example 5.2** Two branches  $R_1$  and  $R_2$  across a 110-V power line draw a total line current of 20 A (Fig. 5-3). Branch  $R_1$  takes 12 A. What is the current  $I_2$  in branch  $R_2$ ?

Starting with Eq. (5-2), transpose to find  $I_2$  and then substitute given values.

$$\begin{aligned} I_T &= I_1 + I_2 \\ I_2 &= I_T - I_1 \\ &= 20 - 12 = 8 \text{ A} \quad \text{Ans.} \end{aligned}$$

The current in branch  $R_2$  is 8 A.

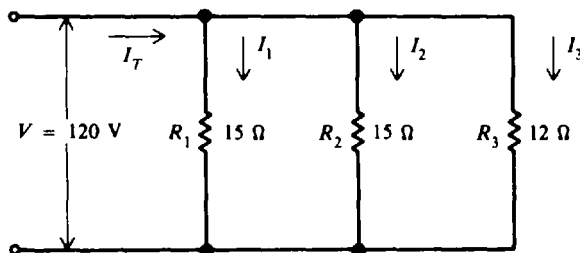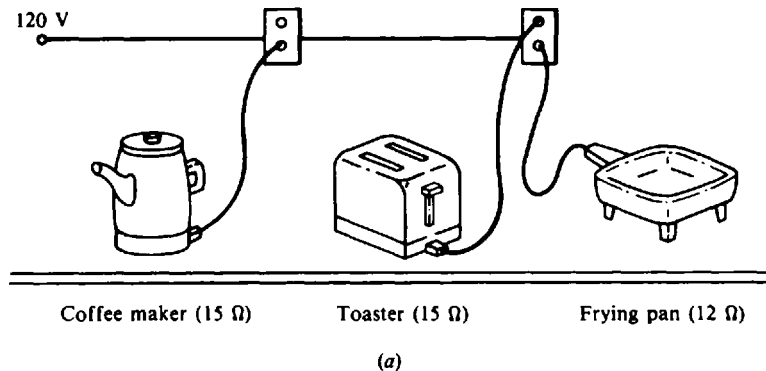**Example 5.3** A parallel circuit consists of a coffee maker, a toaster, and a frying pan plugged into a kitchen appliance circuit on a 120-V line (Fig. 5-4a). What currents will flow in each branch of the circuit and what is the total current drawn by all the appliances?



(b)

Fig. 5-4

First, draw the circuit diagram (Fig. 5-4b). Show the resistance for each appliance. There is a 120-V potential across each appliance. Then, using Eq. (5-3), apply Ohm's law to each appliance.

Coffee maker: 
$$I_1 = \frac{V}{R_1} = \frac{120}{15} = 8 \text{ A} \quad \text{Ans.}$$

Toaster: 
$$I_2 = \frac{V}{R_2} = \frac{120}{15} = 8 \text{ A} \quad \text{Ans.}$$

Frying pan: 
$$I_3 = \frac{V}{R_3} = \frac{120}{12} = 10 \text{ A} \quad \text{Ans.}$$

Now find total current, using Eq. (5-2).

$$\begin{aligned} I_T &= I_1 + I_2 + I_3 \\ &= 8 + 8 + 10 = 26 \text{ A} \quad \text{Ans.} \end{aligned}$$

With this load of 26 A, a 20-A circuit breaker or fuse will open the circuit. This example shows the desirability of having two 20-A kitchen appliance circuits.

**RESISTANCES IN PARALLEL**

**Total Resistance**

The total resistance in a parallel circuit is found by applying Ohm's law: Divide the common voltage across the parallel resistances by the total line current.

$$R_T = \frac{V}{I_T} \tag{5-4}$$

$R_T$  is the total resistance of all the parallel branches across the voltage source  $V$ , and  $I_T$  is the sum of all the branch currents.

**Example 5.4** What is the total resistance of the circuit shown in Fig. 5-4 (Example 5.3)?

In Example 5.3 the line voltage is 120 V and the total line current is 26 A. Therefore,

$$R_T = \frac{V}{I_T} = \frac{120}{26} = 4.62 \Omega \quad \text{Ans.}$$

The total load connected to the 120-V line is the same as the single equivalent resistance of 4.62  $\Omega$  connected across the line (Fig. 5-5). The words *total resistance* and *equivalent resistance* are used interchangeably.

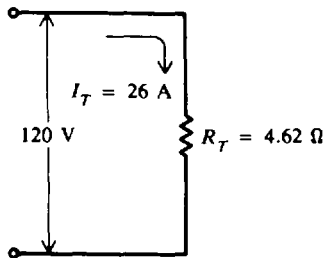


Fig. 5-5 Equivalent circuit to that of Fig. 5-4

**General Reciprocal Formula**

The total resistance in parallel is given by the formula

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_n} \tag{5-5}$$

where  $R_T$  is the total resistance in parallel and  $R_1$ ,  $R_2$ ,  $R_3$ , and  $R_n$  are the branch resistances.

**Example 5.5** Find the total resistance of a 2- $\Omega$ , a 4- $\Omega$ , and an 8- $\Omega$  resistor in parallel (Fig. 5-6).

Write the formula for three resistances in parallel.

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \tag{5-5}$$

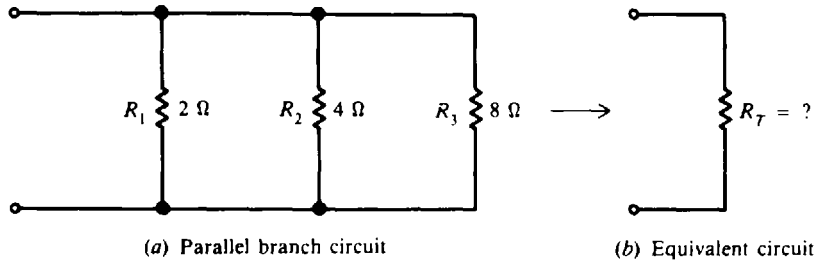


Fig. 5-6

Substitute the resistance values.

$$\frac{1}{R_T} = \frac{1}{2} + \frac{1}{4} + \frac{1}{8}$$

Add fractions.

$$\frac{1}{R_T} = \frac{4}{8} + \frac{2}{8} + \frac{1}{8} = \frac{7}{8}$$

Invert both sides of the equation to solve for  $R_T$ .

$$R_T = \frac{8}{7} = 1.14 \Omega \quad \text{Ans.}$$

Note that when resistances are connected in parallel, the total resistance is always less than the resistance of any single branch. In this case,  $R_T = 1.14 \Omega$  is less than  $R_1 = 2 \Omega$ ,  $R_2 = 4 \Omega$ , and  $R_3 = 8 \Omega$ .

**Example 5.6** Add a fourth resistor of  $2 \Omega$  in parallel to the circuit in Fig. 5-6. What is the new total resistance and what is the net effect of adding another resistance in parallel?

Write the formula for four resistances in parallel.

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \quad (5-5)$$

Substitute values.

$$\frac{1}{R_T} = \frac{1}{2} + \frac{1}{4} + \frac{1}{8} + \frac{1}{2}$$

Add fractions.

$$\frac{1}{R_T} = \frac{4}{8} + \frac{2}{8} + \frac{1}{8} + \frac{4}{8} = \frac{11}{8}$$

Invert.

$$R_T = \frac{8}{11} = 0.73 \Omega \quad \text{Ans.}$$

Thus we see that the net effect of adding another resistance in parallel is a *reduction* of the total resistance from  $1.14$  to  $0.73 \Omega$ .

### Simplified Formulas

The total resistance of *equal* resistors in parallel is equal to the resistance of one resistor divided by the number of resistors.

$$R_T = \frac{R}{N} \quad (5-6)$$

where  $R_T$  = total resistance of equal resistors in parallel,  $\Omega$   
 $R$  = resistance of one of the equal resistors,  $\Omega$   
 $N$  = number of equal resistors

**Example 5.7** Four lamps, each having a resistance of  $60\ \Omega$ , are connected in parallel. Find the total resistance.

Given are

$$R = R_1 = R_2 = R_3 = R_4 = 60\ \Omega$$

$$N = 4$$

Write Eq. (5-6) and substitute values.

$$R_T = \frac{R}{N} = \frac{60}{4} = 15\ \Omega \quad \text{Ans.}$$

When any two unequal resistors are in parallel, it is often easier to calculate the total resistance by multiplying the two resistances and then dividing the product by the sum of the resistances.

$$R_T = \frac{R_1 R_2}{R_1 + R_2} \quad (5-7)$$

where  $R_T$  is the total resistance in parallel and  $R_1$  and  $R_2$  are the two resistors in parallel.

**Example 5.8** Find the total resistance of a  $6\text{-}\Omega$  and an  $18\text{-}\Omega$  resistor in parallel.

Given are  $R_1 = 6\ \Omega$ ,  $R_2 = 18\ \Omega$ .

Write Eq. (5-7) and substitute values.

$$R_T = \frac{R_1 R_2}{R_1 + R_2} = \frac{6(18)}{6 + 18} = \frac{108}{24} = 4.5\ \Omega \quad \text{Ans.}$$

In some cases with two parallel resistors, it is useful to find what size  $R_x$  to connect in parallel with a known  $R$  in order to obtain a required value of  $R_T$ . To find the appropriate formula, we start with Eq. (5-7) and transpose the factors as follows:

$$R_T = \frac{RR_x}{R + R_x}$$

Cross-multiply.

$$R_T R + R_T R_x = RR_x$$

Transpose.

$$RR_x - R_T R_x = R_T R$$

Factor.

$$R_x(R - R_T) = R_T R$$

Solve for  $R_x$ .

$$R_x = \frac{RR_T}{R - R_T} \quad (5-8)$$

**Example 5.9** What value of resistance must be added in parallel with a  $4\text{-}\Omega$  resistor to provide a total resistance of  $3\ \Omega$  (Fig. 5-7)?

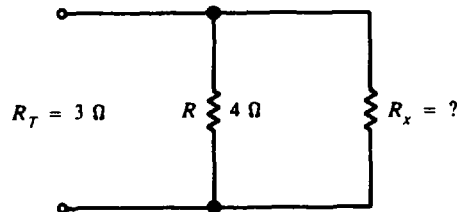


Fig. 5-7

Given are  $R = 4\ \Omega$  and  $R_T = 3\ \Omega$ . Write Eq. (5-8) and substitute values.

$$R_x = \frac{RR_T}{R - R_T} = \frac{4(3)}{4 - 3} = \frac{12}{1} = 12\ \Omega \quad \text{Ans.}$$

### OPEN AND SHORT CIRCUITS

An "open" in any part of a circuit is, in effect, an extremely high resistance that results in no current flow in the circuit. When there is an open in the main line (the "X" in Fig. 5-8a), current to all the parallel branches is stopped. When there is an open in one branch (branch 2 in Fig. 5-8b), only that branch will have no current. However, current in branches 1 and 3 will continue to flow so long as they are connected to the voltage source.

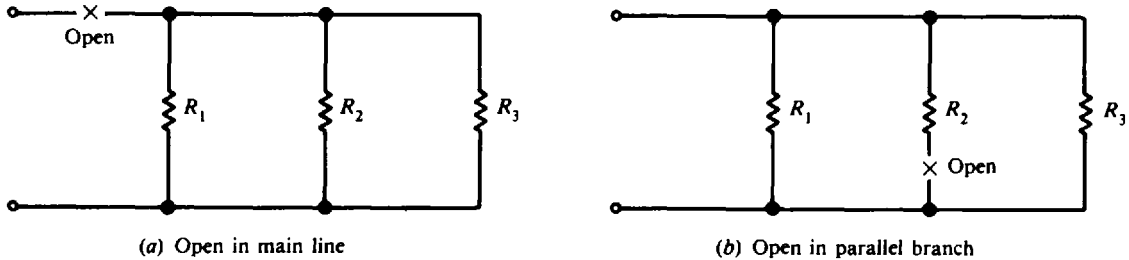


Fig. 5-8 Open parallel circuits

A "short" in any part of a circuit is, in effect, an extremely low resistance. The result is that very high current will flow through the short circuit. Assume that a conducting wire at point *a* in Fig. 5-9 should accidentally contact the wire at point *b*. Since the wire is an excellent conductor, the short circuit offers a parallel path with practically zero resistance from points *a* to *b*. Almost all the current will flow in this path. Since the resistance of the short circuit is practically zero, the voltage drop across *ab* will be almost zero (by Ohm's law). Thus resistors  $R_1$ ,  $R_2$ , and  $R_3$  will not draw their normal current.

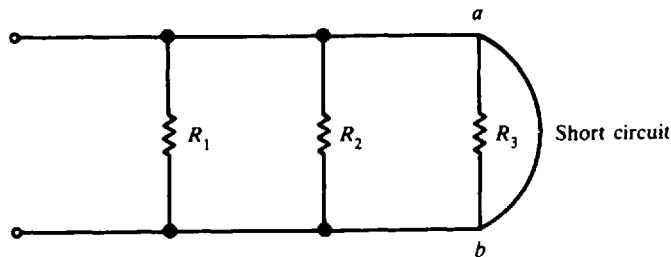


Fig. 5-9 Short in parallel circuit

**Example 5.10** Find the current in each parallel branch (Fig. 5-10a). If the resistor in the second branch burns out, causing an open circuit (Fig. 5-10b), find the new branch currents.

Use Eq. (5-3) and substitute values. With circuits normal (Fig. 5-10a),

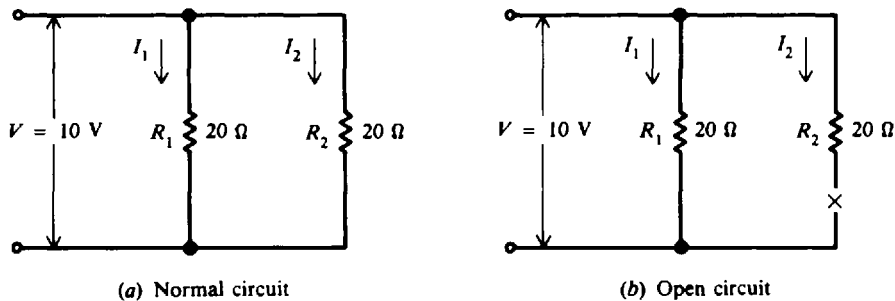


Fig. 5-10

$$I_1 = \frac{V}{R_1} = \frac{10}{20} = 0.5 \text{ A} \quad \text{Ans.}$$

$$I_2 = \frac{V}{R_2} = \frac{10}{20} = 0.5 \text{ A} \quad \text{Ans.}$$

With branch 2 open (Fig. 5-10b),

$$I_1 = \frac{V}{R_1} = \frac{10}{20} = 0.5 \text{ A} \quad \text{Ans.}$$

$$I_2 = 0 \text{ A} \quad \text{Ans.}$$

Branch 1 still operates normally at 0.5 A. This example shows the advantage of wiring components in parallel. An open circuit in one component merely opens the branch containing the component, while the other parallel branch keeps its normal voltage and current.

**DIVISION OF CURRENT IN TWO PARALLEL BRANCHES**

It is sometimes necessary to find the individual branch currents in a parallel circuit if the resistances and total current are known, but the voltage across the resistance bank is not known. When only two branches are involved, the current in one branch will be some fraction of the total current. This fraction is the quotient of the second resistance divided by the sum of the resistances.

$$I_1 = \frac{R_2}{R_1 + R_2} I_T \tag{5-9}$$

$$I_2 = \frac{R_1}{R_1 + R_2} I_T \tag{5-10}$$

where  $I_1$  and  $I_2$  are the currents in the respective branches. Notice that the equation for each branch current has the opposite  $R$  in the numerator. The reason is that each branch current is inversely proportional to the branch resistance. The denominator is the same in both equations, equal to the sum of the two branch resistances.

**Example 5.11** Find the branch currents  $I_1$  and  $I_2$  for the circuit shown in Fig. 5-11.

Given are  $I_T = 18 \text{ A}$ ,  $R_1 = 3 \Omega$ , and  $R_2 = 6 \Omega$ . Write the equations and substitute values.

$$I_1 = \frac{R_2}{R_1 + R_2} I_T \tag{5-9}$$

$$= \frac{6}{3 + 6} 18 = \frac{6}{9} 18 = 12 \text{ A} \quad \text{Ans.}$$

$$I_2 = \frac{R_1}{R_1 + R_2} I_T = \frac{3}{9} 18 = 6 \text{ A} \quad \text{Ans.} \tag{5-10}$$

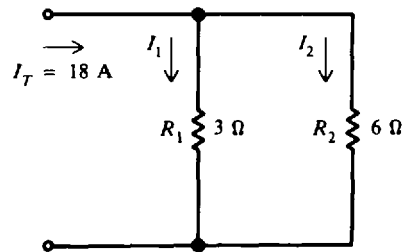


Fig. 5-11

Since  $I_T$  and  $I_1$  were known, we could have found  $I_2$  simply by subtracting:

$$I_T = I_1 + I_2$$

$$I_2 = I_T - I_1 = 18 - 12 = 6 \text{ A} \quad \text{Ans.}$$

**CONDUCTANCES IN PARALLEL**

*Conductance* is the opposite of resistance. The less the resistance, the higher the conductance. The symbol for conductance is  $G$  and its unit is siemens (S).  $G$  is the reciprocal of  $R$ , or

$$G = \frac{1}{R} \tag{5-11}$$

For example,  $6 \Omega$  resistance is equal to  $1/6 \text{ S}$  conductance.

Since conductance is equal to the reciprocal of resistance, the reciprocal resistance equation, Eq. (5-5), can be written for conductance as

$$G_T = G_1 + G_2 + G_3 + \cdots + G_n \quad (5-12)$$

where  $G_T$  is the total conductance in parallel and  $G_1$ ,  $G_2$ ,  $G_3$ , and  $G_n$  are the branch conductances.

**Example 5.12** Find the total conductance of the circuit in Fig. 5-12. Then find the total resistance  $R_T$  and check the value with that computed in Example 5.5.

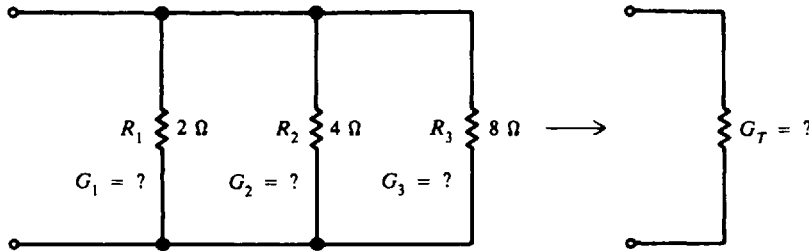


Fig. 5-12

This circuit is the same as that of Fig. 5-6 used in Example 5.5. Convert each branch resistance to conductance, using Eq. (5-11), and then add the values of conductance to obtain  $G_T$ .

$$G_1 = \frac{1}{R_1} = \frac{1}{2} = 0.5 \text{ S}$$

$$G_2 = \frac{1}{R_2} = \frac{1}{4} = 0.25 \text{ S}$$

$$G_3 = \frac{1}{R_3} = \frac{1}{8} = 0.125 \text{ S}$$

$$\begin{aligned} G_T &= G_1 + G_2 + G_3 \\ &= 0.5 + 0.25 + 0.125 = 0.875 \text{ S} \quad \text{Ans.} \end{aligned} \quad (5-12)$$

Finally

$$R_T = \frac{1}{G_T} = \frac{1}{0.875} = 1.14 \Omega \quad \text{Ans.}$$

which agrees with the  $R_T$  value found in Example 5.5.

Ohm's law can be written in terms of conductance. Recall that

$$R_T = \frac{V}{I_T} \quad (5-4)$$

$$I_T = \frac{V}{R_T}$$

But  $1/R_T = G_T$ , so

$$I_T = VG_T \quad (5-13)$$

**Example 5.13** If the source voltage across the parallel bank in Fig. 5-12 is 100 V, find the total current.

Given are  $V = 100 \text{ V}$  and  $G_T = 0.875 \text{ S}$ . Using Eq. (5-13),

$$I_T = VG_T = 100(0.875) = 87.5 \text{ A} \quad \text{Ans.}$$

**POWER IN PARALLEL CIRCUITS**

Since the power dissipated in the branch resistance must come from the voltage source, the total power equals the sum of the individual values of power in each branch.

$$P_T = P_1 + P_2 + P_3 + \dots + P_n \tag{5-14}$$

where  $P_T$  is the total power and  $P_1, P_2, P_3,$  and  $P_n$  are the branch powers.

Total power can also be calculated by the equation

$$P_T = VI_T \tag{5-15}$$

where  $P_T$  is the total power,  $V$  is the voltage source across all parallel branches, and  $I_T$  is the total current.

The power  $P$  dissipated in each branch is equal to  $VI$  and equal to  $V^2/R$ .

In both parallel and series arrangements the sum of the individual values of power dissipated in the circuit equals the total power generated by the source. The circuit arrangements cannot change the fact that all power in the circuit comes from the source.

**Example 5.14** Find the power dissipated in each branch and the total power of the circuit in Fig. 5-13.

First find the branch current and the power in each branch.

$$I_1 = \frac{V}{R_1} = \frac{20}{10} = 2 \text{ A}$$

$$I_2 = \frac{V}{R_2} = \frac{20}{5} = 4 \text{ A}$$

$$P_1 = VI_1 = 20(2) = 40 \text{ W} \quad \text{Ans.}$$

$$P_2 = VI_2 = 20(4) = 80 \text{ W} \quad \text{Ans.}$$

Then add these values for power in each branch to find  $P_T$ .

$$\begin{aligned} P_T &= P_1 + P_2 \\ &= 40 + 80 = 120 \text{ W} \quad \text{Ans.} \end{aligned} \tag{5-14}$$

Another way to find  $P_T$  is to solve for  $I_T$ .

$$I_T = I_1 + I_2 = 2 + 4 = 6 \text{ A}$$

Then

$$\begin{aligned} P_T &= VI_T \\ &= 20(6) = 120 \text{ W} \quad \text{Ans.} \end{aligned} \tag{5-15}$$

The 120 W of power supplied by the source is dissipated in the branch resistances.

There are still other ways to find power used in each branch and total power.

$$P_1 = \frac{V^2}{R_1} = \frac{(20)^2}{10} = 40 \text{ W}$$

$$P_2 = \frac{V^2}{R_2} = \frac{(20)^2}{5} = 80 \text{ W}$$

$$P_T = \frac{V^2}{R_T} = V^2 G_T = (20)^2(0.3) = 120 \text{ W}$$

where

$$G_T = \frac{1}{R_T} = \frac{R_1 + R_2}{R_1 R_2} = \frac{10 + 5}{10(5)} = 0.3 \text{ S}$$

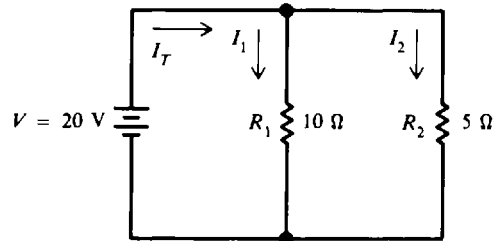


Fig. 5-13



## Solved Problems

5.1 Write the word or words which most correctly complete the following statements.

- (a) The equivalent resistance  $R_T$  of parallel branches is \_\_\_\_\_ than the smallest branch resistance since all the branches must take \_\_\_\_\_ current from the source than any one branch.
- (b) When two resistances are connected in parallel, the voltage across each is the \_\_\_\_\_.
- (c) An open in one branch results in \_\_\_\_\_ current through that branch, but the other branches can have their \_\_\_\_\_ current.
- (d) A short circuit has \_\_\_\_\_ resistance, resulting in \_\_\_\_\_ current.
- (e) If each of two resistances connected in parallel dissipates 5 W, the total power supplied by the voltage source equals \_\_\_\_\_ W.

Ans. (a) less, more; (b) same; (c) zero, normal; (d) zero, excessive; (e) 10

5.2 Branch circuits in a house wiring system are parallel circuits. A toaster, a coffee maker, and a frying pan are plugged into a kitchen appliance circuit across a 110-V line (Fig. 5-14). The current through the toaster is 8.3 A; through the coffee maker, 8.3 A; and through the frying pan, 9.6 A. Find (a) the total current from the main line, (b) the voltage across each appliance, and (c) the total resistance of the circuit.

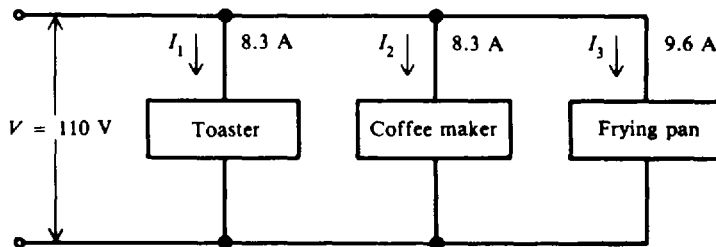


Fig. 5-14

(a) Find  $I_T$ .

$$\begin{aligned} I_T &= I_1 + I_2 + I_3 \\ &= 8.3 + 8.3 + 9.6 = 26.2 \text{ A} \quad \text{Ans.} \end{aligned} \quad (5-2)$$

(b) Find  $V_1$ ,  $V_2$ ,  $V_3$ , using Eq. (5-1).

$$V = V_1 = V_2 = V_3 = 110 \text{ V} \quad \text{Ans.}$$

(c) Find  $R_T$ .

$$\begin{aligned} R_T &= \frac{V}{I_T} \\ &= \frac{110}{26.2} = 4.198 = 4.20 \Omega \quad \text{Ans.} \end{aligned} \quad (5-4)$$

5.3 Four 60-W lamps, each having the same resistance, are connected in parallel across a household terminal of 120 V, producing a line current of 2 A (Fig. 5-15a). The schematic diagram shows resistances that represent the lamps (Fig. 5-15b). What is (a) the equivalent resistance of the circuit, (b) the resistance  $R$  of each lamp, and (c) the current that each lamp draws?

(a) 
$$R_T = \frac{V}{I_T} = \frac{120}{2} = 60 \Omega \quad \text{Ans.}$$

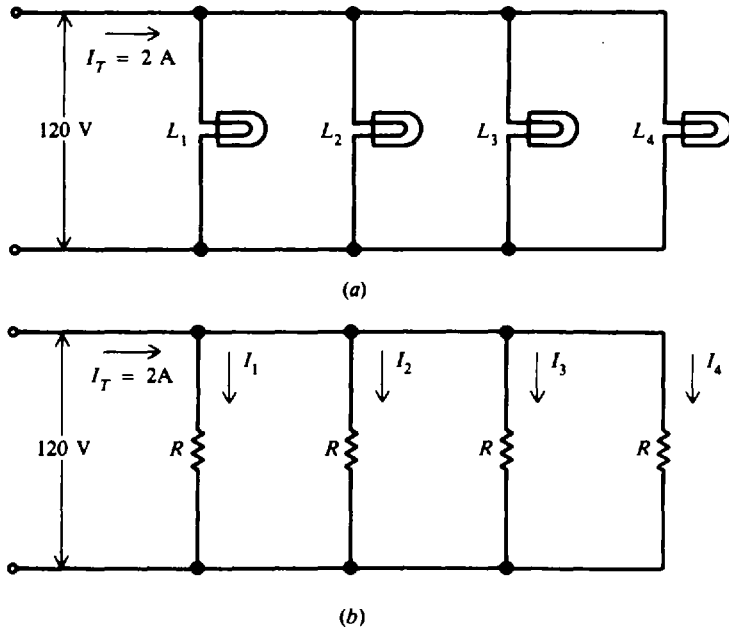


Fig. 5-15

(b) 
$$R_T = \frac{R}{N} \tag{5-6}$$

so that

$$R = R_T N = 60(4) = 240 \Omega \quad \text{Ans.}$$

(c) 
$$I_1 = I_2 = I_3 = I_4 = \frac{I_T}{N} = \frac{2}{4} = 0.5 \text{ A} \quad \text{Ans.}$$

With equal resistance in each branch, the current in each branch is equal and the power consumed by each branch is equal.

5.4 For the circuit in Fig. 5-16, find (a) the total resistance, (b) each branch current, and (c) the total current.

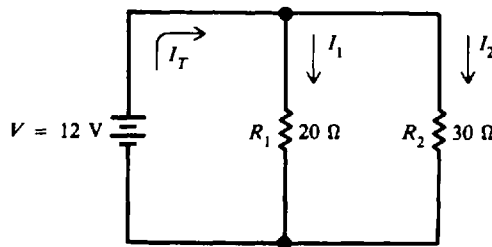


Fig. 5-16

(a) Since there are only two resistances in parallel, use the simplified formula, Eq. (5-7).

$$R_T = \frac{R_1 R_2}{R_1 + R_2} = \frac{20(30)}{20 + 30} = 12 \Omega \quad \text{Ans.}$$

(b) Use Eq. (5-3).

$$I_1 = \frac{V}{R_1} = \frac{12}{20} = 0.6 \text{ A} \quad \text{Ans.}$$

$$I_2 = \frac{V}{R_2} = \frac{12}{30} = 0.4 \text{ A} \quad \text{Ans.}$$

$$(c) \quad I_T = I_1 + I_2 = 0.6 + 0.4 = 1 \text{ A} \quad \text{Ans.}$$

Or, as a check,

$$I_T = \frac{V}{R_T} = \frac{12}{12} = 1 \text{ A} \quad \text{Ans.}$$

5.5 Find the total resistance  $R_T$  of each resistance arrangement in Fig. 5-17.

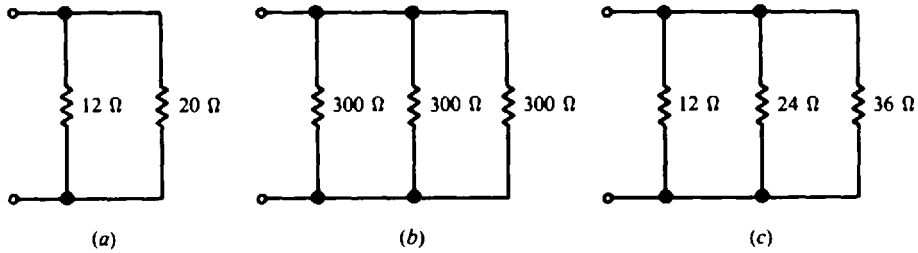


Fig. 5-17

(a) Use Eq. (5-7) for two parallel branches.

$$R_T = \frac{R_1 R_2}{R_1 + R_2} = \frac{12(20)}{12 + 20} = \frac{240}{32} = 7.5 \Omega \quad \text{Ans.}$$

(b) Since all the resistances are equal, use Eq. (5-6).

$$R_T = \frac{R}{N} = \frac{300}{3} = 100 \Omega \quad \text{Ans.}$$

(c) For three parallel branches with different resistances, use Eq. (5-5).

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} = \frac{1}{12} + \frac{1}{24} + \frac{1}{36} = \frac{11}{72}$$

$$R_T = \frac{72}{11} = 6.55 \Omega \quad \text{Ans.}$$

Note that the total resistance of a parallel circuit is always less than the smallest resistance of any individual resistor.

5.6 A spotlight of unknown resistance is placed in parallel with an automobile cigarette lighter of  $75 \Omega$  resistance (Fig. 5-18). If a current of  $0.8 \text{ A}$  flows when a voltage of  $12 \text{ V}$  is applied, find the resistance of the spotlight.

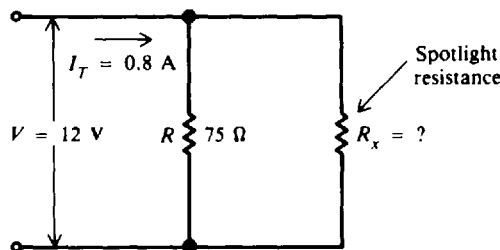


Fig. 5-18

Find  $R_T$ .

$$R_T = \frac{V}{I_T} \quad (5-4)$$

$$R_T = \frac{12}{0.8} = 15 \Omega$$

Then use Eq. (5-8) to find the unknown resistance.

$$R_x = \frac{RR_T}{R - R_T} = \frac{75(15)}{75 - 15} = \frac{1125}{60} = 18.8 \Omega \quad \text{Ans.}$$

Another way to find the answer is to use Ohm's law and the total current equation.

$$I_{\text{lighter}} = \frac{12}{75} = 0.16 \text{ A}$$

$$I_{\text{spot}} = 0.8 - 0.16 = 0.64 \text{ A}$$

$$R_{\text{spot}} = \frac{12}{0.64} = 18.75 = 18.8 \Omega \quad \text{Ans.}$$

5.7 (a) Derive Eq. (5-7)  $R_T = R_1R_2/(R_1 + R_2)$  from the reciprocal formula for two parallel resistances.

(b) Derive a formula for  $R_T$ , given three parallel resistances.

(a) 
$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} \quad (5-5)$$

Add fractions.

$$\frac{1}{R_T} = \frac{R_2}{R_1R_2} + \frac{R_1}{R_1R_2} = \frac{R_1 + R_2}{R_1R_2}$$

Invert.

$$R_T = \frac{R_1R_2}{R_1 + R_2} \quad \text{which is Eq. (5-7)}$$

(b) Use the formula

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \quad (5-5)$$

Find the common denominator and combine numerators.

$$\frac{1}{R_T} = \frac{R_2R_3 + R_1R_3 + R_1R_2}{R_1R_2R_3}$$

Invert.

$$R_T = \frac{R_1R_2R_3}{R_1R_2 + R_1R_3 + R_2R_3} \quad \text{Ans.}$$

5.8 Find the voltage required to send 2 A through a parallel combination of a 20-Ω, a 30-Ω, and a 40-Ω resistance (Fig. 5-19).

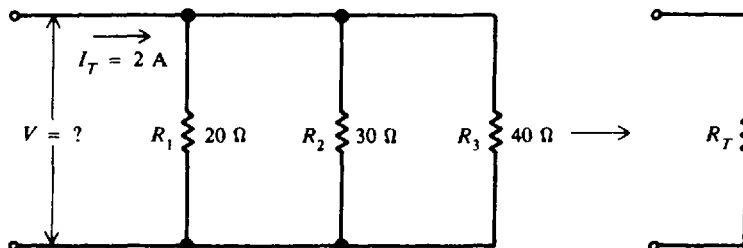


Fig. 5-19

Find  $R_T$ .

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \quad (5-5)$$

$$= \frac{1}{20} + \frac{1}{30} + \frac{1}{40} = \frac{13}{120}$$

$$R_T = \frac{120}{13} = 9.23 \Omega$$

Then  $V = I_T R_T = 2(9.23) = 18.5 \text{ V}$      *Ans.*

As a check,

$$I_1 = \frac{V}{R_1} = \frac{18.5}{20} = 0.925 \text{ A}$$

$$I_2 = \frac{V}{R_2} = \frac{18.5}{30} = 0.617 \text{ A}$$

$$I_3 = \frac{V}{R_3} = \frac{18.5}{40} = 0.463 \text{ A}$$

$$I_T = I_1 + I_2 + I_3 = 0.925 + 0.617 + 0.463 = 2.005 \approx 2 \text{ A}$$

which checks with the given value. (The sum of the currents is not exactly 2 A due to rounding off the individual branch currents.)

**5.9** Two resistances are arranged in parallel (Fig. 5-20). Find the current in each resistance.

Use formulas for the division of current.

$$I_1 = \frac{R_2}{R_1 + R_2} I_T \quad (5-9)$$

$$= \frac{18}{18 + 72} 30 = \frac{18}{90} 30 = 6 \text{ mA} \quad \textit{Ans.}$$

$$I_2 = \frac{R_1}{R_1 + R_2} I_T \quad (5-10)$$

$$= \frac{72}{18 + 72} 30 = \frac{72}{90} 30 = 24 \text{ mA} \quad \textit{Ans.}$$

Check:  $I_T = I_1 + I_2 = 6 + 24 = 30 \text{ mA}$ , which agrees with the given value.

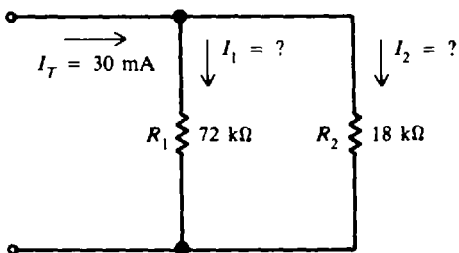


Fig. 5-20

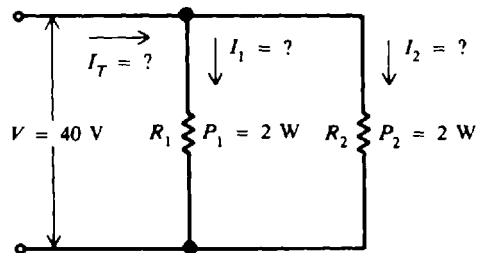


Fig. 5-21

**5.10** Two resistors, each dissipating 2 W, are connected in parallel across 40 V (Fig. 5-21). What is the current in each resistor? What is the total current drawn?

Find  $I_1$ ,  $I_2$ ,  $I_T$ .

$$I_1 = \frac{P_1}{V} = \frac{2}{40} = 0.05 \text{ A} \quad \textit{Ans.}$$

$$I_2 = \frac{P_2}{V} = \frac{2}{40} = 0.05 \text{ A} \quad \text{Ans.}$$

$$I_T = I_1 + I_2 = 0.05 + 0.05 = 0.1 \text{ A} \quad \text{Ans.}$$

Check:

$$P_T = P_1 + P_2 = 2 + 2 = 4 \text{ W}$$

$$I_T = \frac{P_T}{V} = \frac{4}{40} = 0.1 \text{ A}$$

which agrees with the previously calculated value.

5.11 The combined resistance of a coffee percolator and toaster in parallel is  $24 \Omega$ . Find the total power used if the line voltage is  $120 \text{ V}$ .

$$P_T = \frac{V^2}{R_T} = \frac{(120)^2}{24} = 600 \text{ W} \quad \text{Ans.}$$

5.12 Find  $I_3$  in the parallel current-divider circuit (Fig. 5-22).

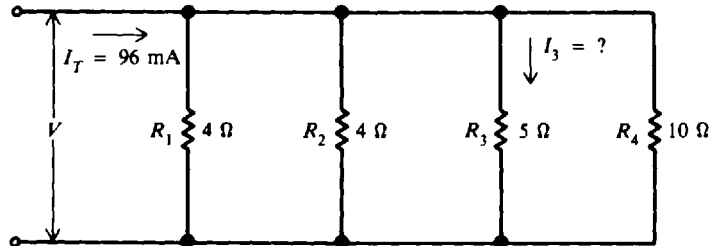


Fig. 5-22

Find  $R_T$ .

$$\begin{aligned} \frac{1}{R_T} &= \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \\ &= \frac{1}{4} + \frac{1}{4} + \frac{1}{5} + \frac{1}{10} = \frac{32}{40} \\ R_T &= \frac{40}{32} = 1.25 \Omega \end{aligned} \quad (5-5)$$

Find  $V$ .

$$V = I_T R_T = 96(1.25) = 120 \text{ mV}$$

Then find  $I_3$ .

$$I_3 = \frac{V}{R_3} = \frac{120}{5} = 24 \text{ mA} \quad \text{Ans.}$$

### Supplementary Problems

5.13 Write the word or words which most correctly complete the following statements.

- (a) There is only \_\_\_\_\_ voltage across all components in parallel.
- (b) If a parallel circuit is open in the main line, the current is \_\_\_\_\_ in all the branches.
- (c) For any number of conductances in parallel, their values are \_\_\_\_\_ to obtain  $G_T$ .

(d) When  $I_T$  divides into branch currents, each branch current is \_\_\_\_\_ proportional to the branch resistance.

(e) The sum of the \_\_\_\_\_ values of power dissipated in parallel resistances equals the \_\_\_\_\_ power produced by the source.

Ans. (a) one; (b) zero; (c) added; (d) inversely; (e) individual, total

5.14 A 100- $\Omega$  and a 150- $\Omega$  resistor are connected in parallel. What is the total resistance?

Ans.  $R_T = 60 \Omega$

5.15 When the voltage across  $R_4$  is 10 V, what is the source voltage in Fig. 5-23? Ans.  $V = 10 \text{ V}$

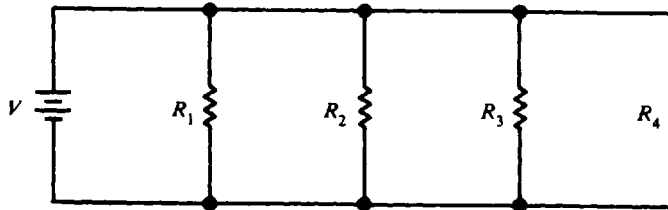


Fig. 5-23

5.16 Find the equivalent resistances in the circuits shown in Fig. 5-24.

Ans. (a)  $R_T = 1 \Omega$ ; (b)  $R_T = 2 \Omega$ ; (c)  $R_T = 4.8 \Omega$ ; (d)  $R_T = 3.6 \Omega$

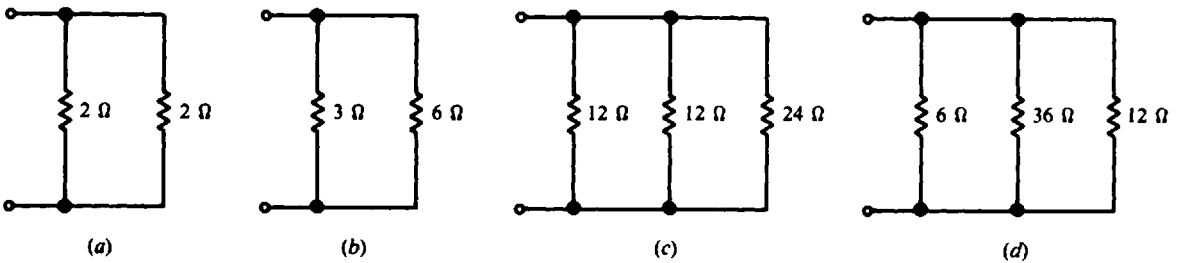


Fig. 5-24

5.17 Find the missing branch or total current as indicated in Fig. 5-25.

Ans. (a)  $I_T = 3 \text{ A}$ ; (b)  $I_3 = 2 \text{ A}$

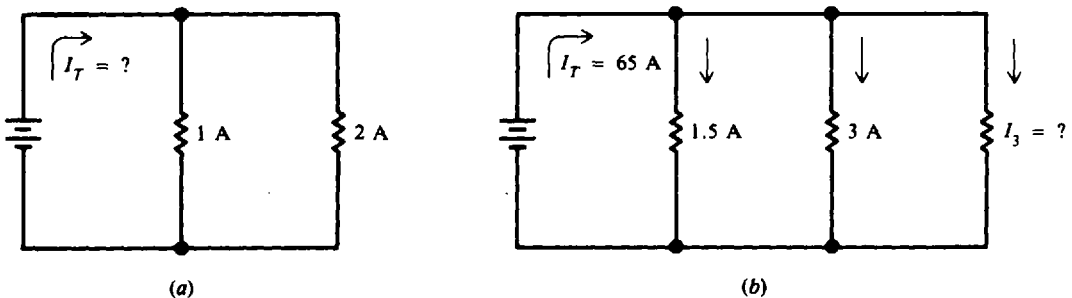


Fig. 5-25

5.18 Four equal resistances are connected in parallel across a 90-V source. If the resistances are  $36 \Omega$  for each branch, find the total resistance and the total current. Ans.  $R_T = 9 \Omega$ ;  $I_T = 10 \text{ A}$

5.19 Find the total resistance, each branch current, and total current (Fig. 5-26).

Ans.  $R_T = 2.67 \Omega$ ;  $I_1 = 2 \text{ A}$ ;  $I_2 = 1 \text{ A}$ ;  $I_T = 3 \text{ A}$

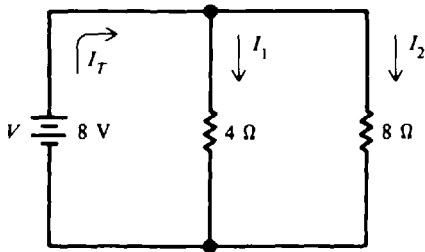


Fig. 5-26

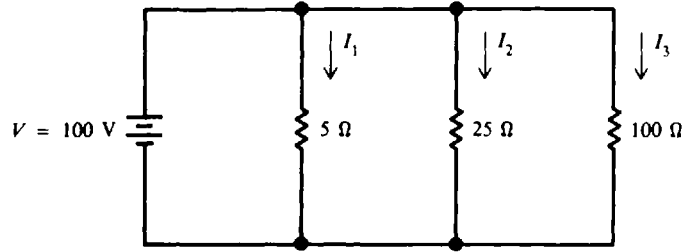


Fig. 5-27

- 5.20 In the circuit shown (Fig. 5-27), find the total resistance, each branch current, and total current.  
*Ans.*  $R_T = 4 \Omega$ ;  $I_1 = 20 \text{ A}$ ;  $I_2 = 4 \text{ A}$ ;  $I_3 = 1 \text{ A}$ ;  $I_T = 25 \text{ A}$
- 5.21 If the 25- $\Omega$  resistor is removed from the circuit in Fig. 5-27, what is the total current and total resistance? *Ans.*  $I_T = 21 \text{ A}$ ;  $R_T = 4.76 \Omega$
- 5.22 An ammeter (instrument that measures current) carries 0.05 A and is in parallel with a shunt resistor drawing 1.9 A (Fig. 5-28). If the voltage across the combination is 4.2 V, find (a) the total current, (b) resistance of the shunt, (c) resistance of the ammeter, and (d) total resistance.  
*Ans.* (a)  $I_T = 1.95 \text{ A}$ ; (b) Shunt  $R = 2.21 \Omega$ ; (c) Ammeter  $R = 84.0 \Omega$ ; (d)  $R_T = 2.15 \Omega$

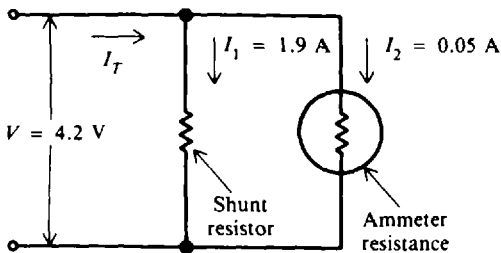


Fig. 5-28

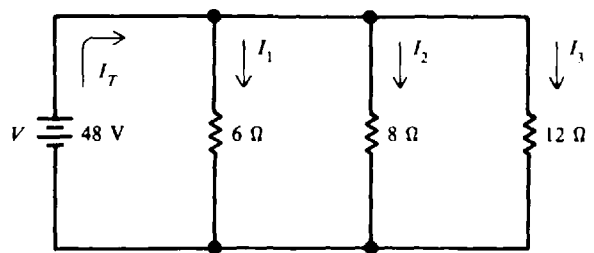


Fig. 5-29

- 5.23 Find the total resistance, each branch current, and total current (Fig. 5-29).  
*Ans.*  $R_T = 2.67 \Omega$ ;  $I_1 = 8 \text{ A}$ ;  $I_2 = 6 \text{ A}$ ;  $I_3 = 4 \text{ A}$ ;  $I_T = 18 \text{ A}$
- 5.24 A circuit consists of five identical resistances connected in parallel across a voltage source. If the total circuit current is 1 A, what is the current through each resistance? *Ans.*  $I = 0.2 \text{ A}$
- 5.25 In the circuit of Fig. 5-30, find  $V$  if  $I_3 = 0.2 \text{ A}$ . Then find  $I_T$ . *Ans.*  $V = 2 \text{ V}$ ;  $I_T = 0.4 \text{ A}$

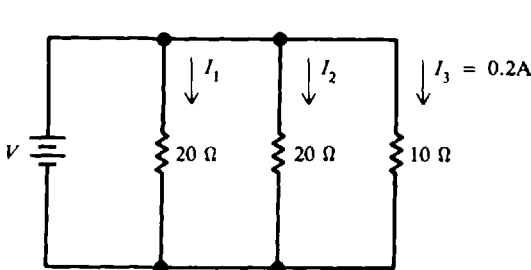


Fig. 5-30

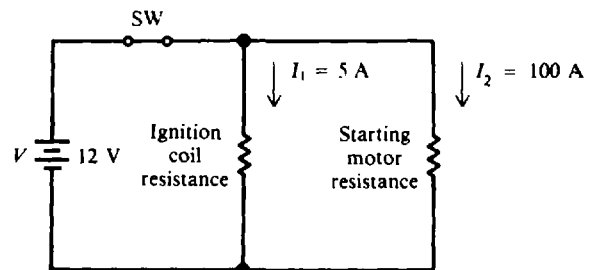


Fig. 5-31

- 5.26 The ignition coil and the starting motor of a car are connected in parallel across a 12-V battery through an ignition switch (Fig. 5-31). Find (a) the total current drawn from the battery, (b) the voltage across the coil and the motor, and (c) the total resistance of the circuit.  
*Ans.* (a)  $I = 105 \text{ A}$ ; (b)  $V_1 = V_2 = 12 \text{ V}$ ; (c)  $R_T = 0.114 \Omega$



- 5.27 Two headlight lamps, each drawing 4 A, and two taillight lamps, each drawing 1 A, are wired in parallel across a 12-V storage battery. What is the total current drawn and the total resistance of the circuit? *Ans.*  $I_T = 10$  A;  $R_T = 1.2$   $\Omega$
- 5.28 What is the value of a resistor that must be connected in parallel across a 100-k $\Omega$  resistance to reduce  $R_T$  to (a) 50 k $\Omega$ , (b) 25 k $\Omega$ , and (c) 10 k $\Omega$ ?  
*Ans.* (a)  $R_x = 100$  k $\Omega$ ; (b)  $R_x = 33.3$  k $\Omega$ ; (c)  $R_x = 11.1$  k $\Omega$
- 5.29 What resistance must be connected in parallel with a 20- $\Omega$  and a 60- $\Omega$  resistor in parallel in order to provide a total resistance of 10  $\Omega$ ? *Ans.* 30  $\Omega$
- 5.30 Two resistances are connected in parallel.  $R_1 = 24$   $\Omega$ ,  $R_2 = 24$   $\Omega$ , and  $I_T = 6$  A. Find the current in each branch. *Ans.*  $I_1 = I_2 = 3$  A
- 5.31 Find the current in each branch of a parallel circuit consisting of a 20- $\Omega$  percolator and a 30- $\Omega$  toaster if the total current is 10 A. *Ans.*  $I$  in percolator = 6 A;  $I$  in toaster = 4 A
- 5.32 Find the missing values in Fig. 5-32. *Ans.*  $V = 4.5$  V;  $I_1 = 1.50$  A;  $I_2 = 1.13$  A;  $I_3 = 0.38$  A

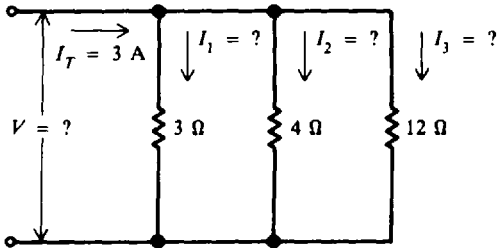


Fig. 5-32

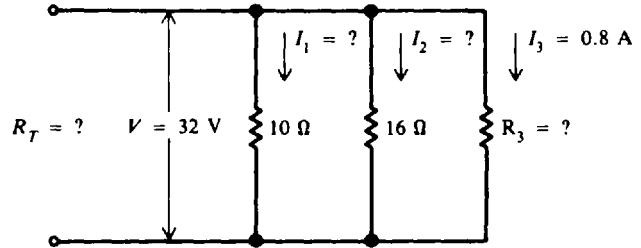


Fig. 5-33

- 5.33 Find the missing values in Fig. 5-33.  
*Ans.*  $R_3 = 40$   $\Omega$ ;  $R_T = 5.33$   $\Omega$ ;  $I_1 = 3.2$  A;  $I_2 = 2$  A;  $I_T = 6$  A
- 5.34 Find the total conductance in siemens for the following parallel branches:  $G_1 = 6000$   $\mu$ S,  $G_2 = 7000$   $\mu$ S, and  $G_3 = 20\,000$   $\mu$ S. *Ans.*  $G_T = 33\,000$   $\mu$ S
- 5.35  $I_T$  is 12 mA for two branch resistances.  $R_1$  is 10 k $\Omega$  and  $R_2$  is 36 k $\Omega$ . Find  $I_1$  and  $I_2$  in this parallel current-divider circuit. *Ans.*  $I_1 = 9.39$  mA;  $I_2 = 2.61$  mA
- 5.36 What is the total power used by a 4.5-A electric iron, a 0.9-A fan, and a 2.4-A refrigerator motor if they are all connected in parallel across a 120-V line? *Ans.*  $P_T = 936$  W
- 5.37 Find the power drawn from a 12-V battery by a parallel circuit of two headlights, each drawing 4.2 A, and two taillights, each drawing 0.9 A. *Ans.*  $P_T = 122.4$  W
- 5.38 Five 150-W light bulbs are connected in parallel across a 120-V power line. If one bulb opens, how many bulbs can light? *Ans.* Four
- 5.39 In Fig. 5-34 find (a) each branch current; (b)  $I_T$ ; (c)  $R_T$ ; and (d)  $P_1$ ,  $P_2$ ,  $P_3$ , and  $P_T$ .  
*Ans.* (a)  $I_1 = 30$  mA,  $I_2 = 14.6$  mA,  $I_3 = 60$  mA; (b)  $I_T = 104.6$  mA; (c)  $R_T = 1.15$  k $\Omega$ ; (d)  $P_1 = 3.60$  W,  $P_2 = 1.75$  W,  $P_3 = 7.20$  W,  $P_T = 12.6$  W
- 5.40 Find  $R_2$  in Fig. 5-35. *Ans.*  $R_2 = 1$  k $\Omega$

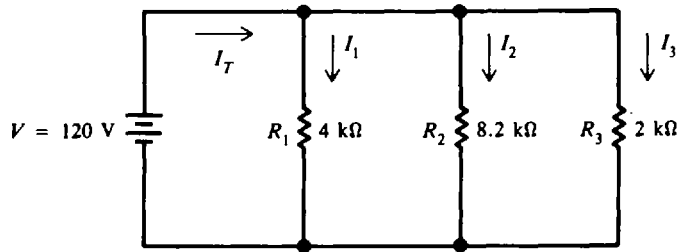


Fig. 5-34

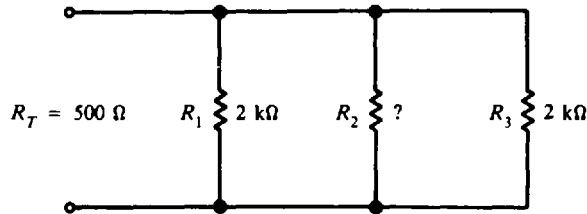


Fig. 5-35

5.41 Refer to Fig. 5-34 and assume that  $R_2$  opens. (a) What is the current through  $R_2$ ? (b) What is the current through  $R_1$ ? and through  $R_3$ ? (c) What is the line or total current? (d) What is the total resistance of the circuit? (e) How much power is generated by the battery?

Ans. (a)  $I_2 = 0 \text{ A}$ ; (b)  $I_1 = 30 \text{ mA}$ ,  $I_3 = 60 \text{ mA}$ ; (c)  $I_T = 90 \text{ mA}$ ; (d)  $R_T = 1.33 \text{ k}\Omega$ ; (e)  $P_T = 10.8 \text{ W}$

5.42 Find  $I_2$  and  $I_4$  in the parallel current-divider circuit (Fig. 5-36). Ans.  $I_2 = 2.5 \text{ A}$ ;  $I_4 = 1.67 \text{ A}$

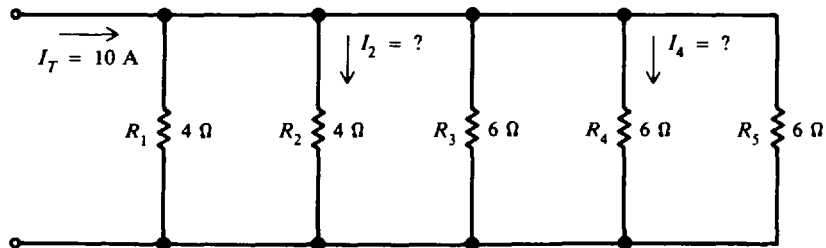


Fig. 5-36

## Batteries

### THE VOLTAIC CELL

A *voltaic chemical cell* is a combination of materials used to convert chemical energy into electric energy. The chemical cell consists of two electrodes made of different kinds of metals or metallic compounds, and an electrolyte, which is a solution capable of conducting an electric current (Fig. 6-1a). A battery is formed when two or more cells are connected.

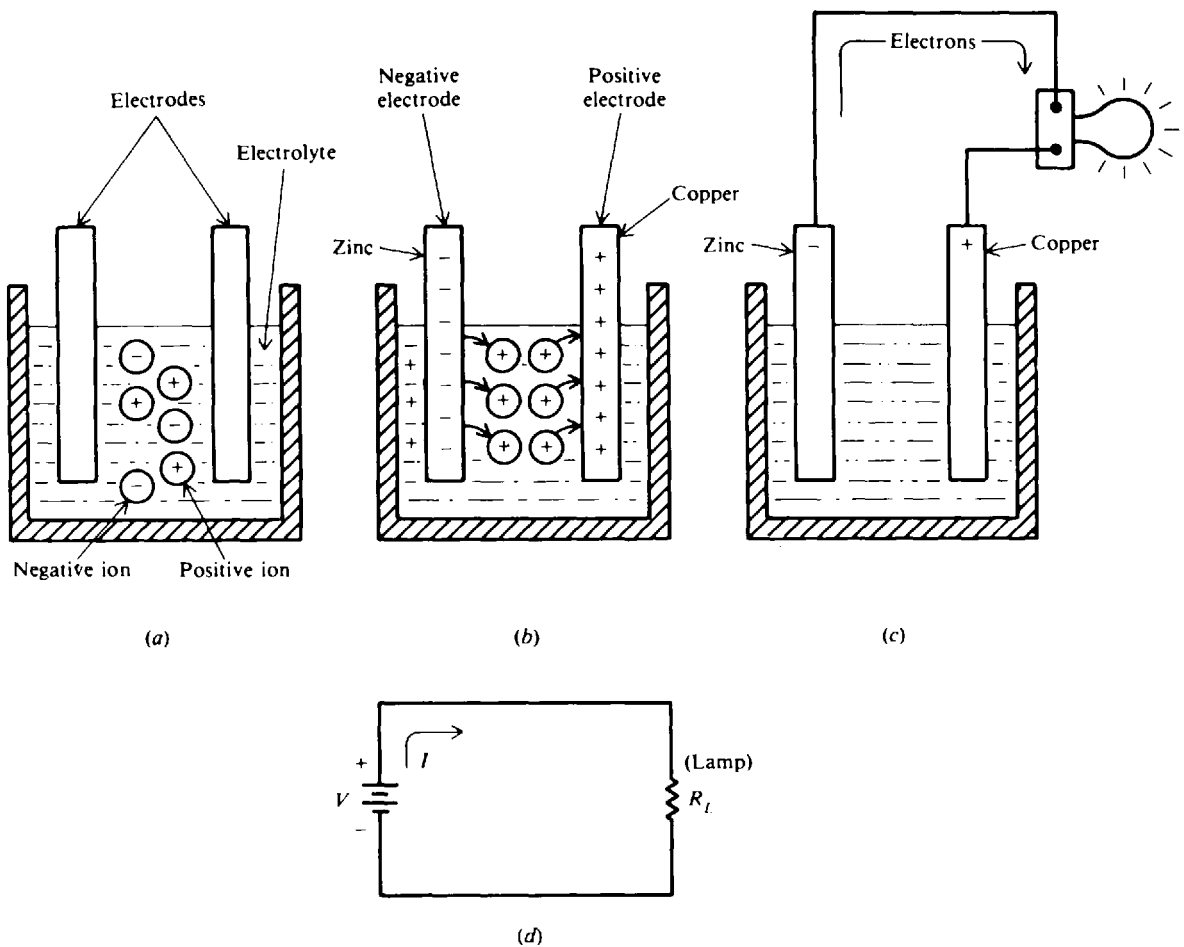


Fig. 6-1 Basic chemical action of a voltaic cell


An excellent example of a pair of electrodes is zinc and copper. Zinc contains an abundance of negatively charged atoms, while copper has an abundance of positively charged atoms. When plates of these metals are immersed in an electrolyte, chemical action between the two begins. The zinc electrode accumulates a much larger negative charge since it gradually dissolves into the electrolyte. The atoms which leave the zinc electrode are positively charged. They are attracted by the negatively charged ions (–) of the electrolyte, while they repel the positively charged ions (+) of the electrolyte toward the copper electrode (Fig. 6-1b). This causes electrons to be removed from the copper, leaving it with an excess of positive charge. If a load

such as a light bulb is connected across the terminals on the electrodes, the forces of attraction and repulsion will cause free electrons in the negative zinc electrode, connecting wires, and light bulb filament to move toward the positively charged copper electrode (Fig. 6-1c). The potential difference that results permits the cell to function as a source of applied voltage  $V$  (Fig. 6-1d).

The electrolyte of a cell may be liquid or a paste. If the electrolyte is a liquid, the cell is often called a *wet* cell. If the electrolyte is in a paste form, the cell is referred to as a *dry* cell.


**SERIES AND PARALLEL CELLS**

When cells are connected in series (Fig. 6-2), the total voltage across the battery of cells is equal to the sum of the voltage of each of the individual cells. In Fig. 6-2 the four 1.5-V cells in series provide a total battery voltage of 6 V. When cells are placed in series, the positive terminal of one cell is connected to the negative terminal of the other cell. The current flowing through such a battery of series cells is the same as for one cell because the same current flows through all the series cells.

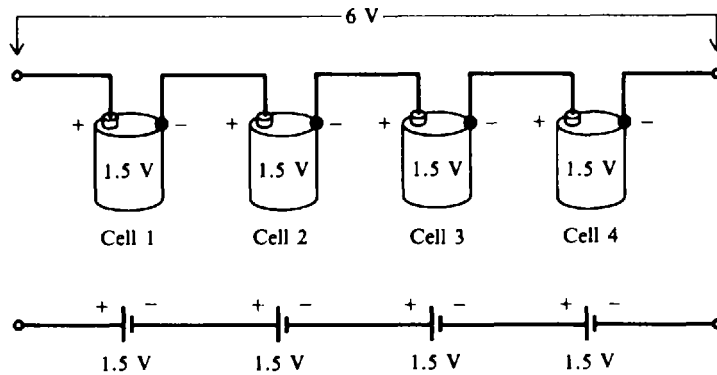

**Fig. 6-2** Cells in series

To obtain a greater current, the battery has cells in parallel (Fig. 6-3). When cells are placed in parallel, all the positive terminals are connected together and all the negative terminals are connected together. Any point on the positive side can serve as the positive terminal of the battery and any point on the negative side can be the negative terminal.

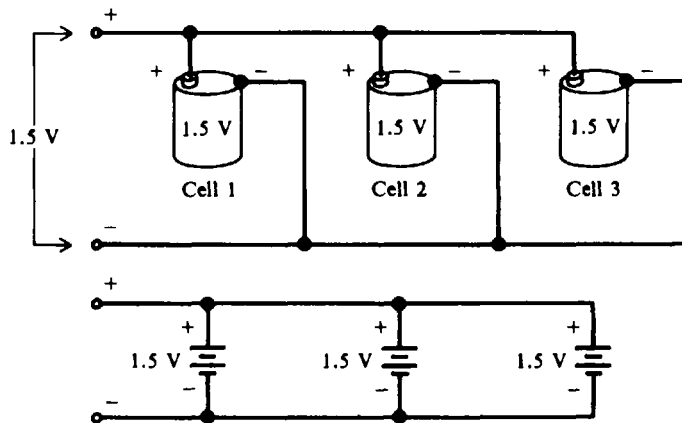

**Fig. 6-3** Cells in parallel

The total voltage output of a battery of three parallel cells is the same as that for a single cell (Fig. 6-3), but the available current is three times that of one cell. The parallel connection has the

same effect of increasing the size of the electrodes and electrolyte in a single cell, which increases the current capacity.

Identical cells in parallel all supply equal parts of the current to the load. For example, of three identical parallel cells producing a load current of 270 mA, each cell contributes 90 mA.

## PRIMARY AND SECONDARY CELLS

*Primary cells* are those which cannot be recharged or returned to good condition after their voltage output drops too low. Dry cells used in flashlights and transistor radios are examples of primary cells.

*Secondary cells* are those which are rechargeable. During recharging, the chemicals which provide electric energy are restored to their original condition. Recharging is done by passing direct current through a cell in a direction opposite to the direction of the current which the cell delivers to a circuit.

A cell is recharged by connecting it to a battery charger in "like-to-like" polarity (Fig. 6-4). Some battery chargers have a voltmeter and an ammeter which indicate the charging voltage and current.

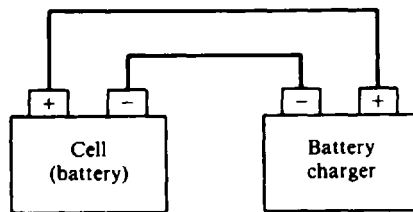


Fig. 6-4 Recharging a secondary cell with a battery charger


The most common example of a secondary cell is an automobile storage battery. Secondary cells or batteries are particularly useful for powering mobile equipment where a generator is available to keep them charged. Smaller, sealed secondary cells are used to power such portable equipment as shavers, electronic calculators, radios, and television receivers. These can be easily charged from ordinary house current by simple, low-cost chargers often built into the equipment or appliance itself.

## TYPES OF BATTERIES

### Lead-Acid Battery

The lead-acid battery consists of a number of lead-acid cells. Each cell has two groups of lead plates; one set is the positive terminal and the other is the negative terminal. All positive plates are connected together with a connecting strap (Fig. 6-5). All negative plates are similarly connected together. The positive and negative plates are *interlaced* so that alternately there is a positive plate and a negative plate. Between the plates are sheets of insulating material called *separators*, made either of porous wood, perforated wood, or fiberglass. The separators prevent the positive and negative plates from touching each other and producing a short circuit, which would destroy the cell. The positive plate is treated chemically to form lead peroxide (a combination of lead and oxygen), and the negative electrode consists of porous, spongy lead. The two sets of plates with the separators between them are placed in a container filled with a dilute solution of sulfuric acid and water. The term *lead-acid battery* refers to the lead plates and sulfuric acid that are the principal components of the battery.

The voltage in this type of cell is slightly more than 2 V. Batteries used in modern automobiles contain six cells connected in series so that the output voltage from the battery is slightly more than

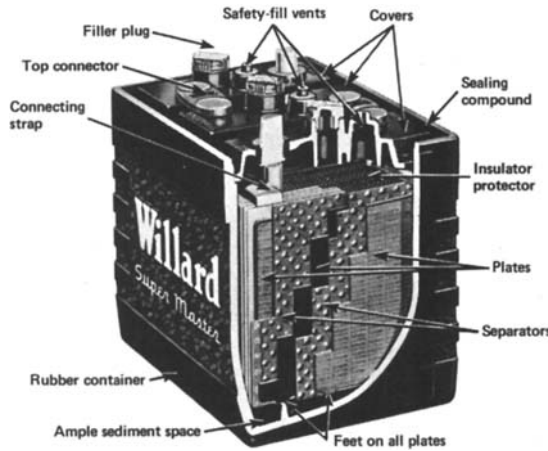


**Fig. 6-5** Cutaway view of a lead-acid battery. (From B. Grob, *Basic Electronics*, 4th ed., McGraw-Hill, New York, 1977, p. 247.)

12 V. Older automobiles made before the mid-1950s used batteries in which three cells were connected in series to give an output voltage of slightly more than 6 V.

The storage battery can supply current for a much longer time than the average dry cell. When the storage battery is discharged and is no longer able to supply the current required by the circuit, the battery can be removed from the circuit and recharged by passing current through it in the opposite direction. Once the battery has been recharged, it can again be connected to the circuit and will supply current to the circuit.

In an automobile, the battery is connected to a device called an *alternator*. As long as the car is running at a reasonable speed, the alternator is both charging the battery and supplying the current needed to operate the car. However, when the car is operated at a slow speed or when it is stopped, the alternator is not turning fast enough to provide the electricity needed by the car. The battery then supplies this energy, causing it to slowly discharge.

When the battery discharges, some of the acid of the electrolyte combines with the active material on the plates (Fig. 6-6a). This chemical action changes the material in both plates to lead sulfate. When the battery is being charged by the alternator, the reverse action takes place, and the acid which was absorbed by the plates is returned to the electrolyte (Fig. 6-6b). The result is that the active material on the plates is changed back into the original (charged condition) lead peroxide and sponge lead, and the electrolyte is restored to its original strength.

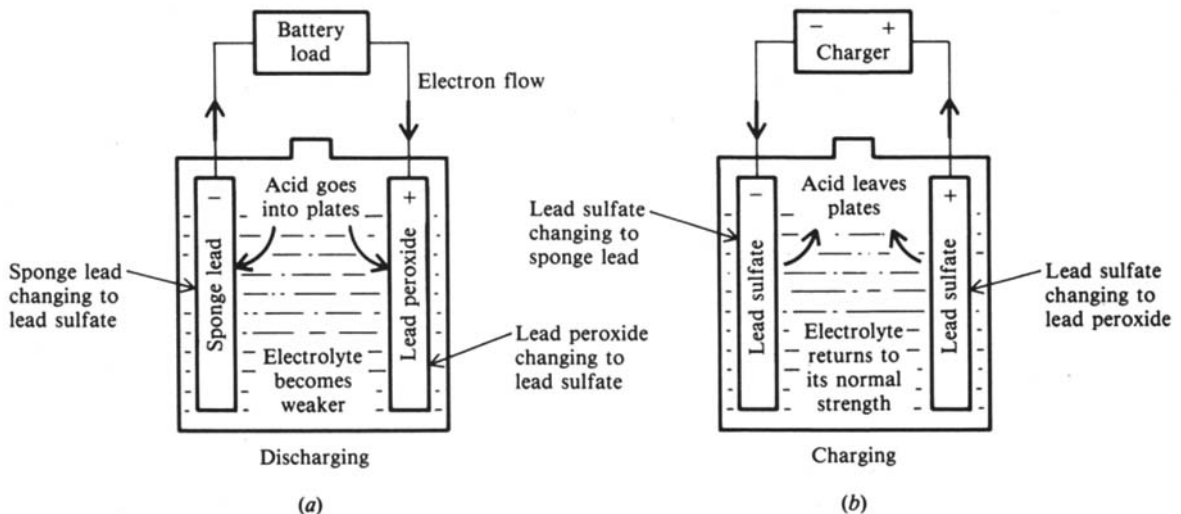


**Fig. 6-6** Chemical actions of a lead-acid cell

Whenever a battery is charging, the chemical action produces hydrogen gas on one plate surface and oxygen gas on the other. These gases bubble to the surface and escape through the vent hole in the cap on the cell. Thus water ( $H_2O$ ) is lost to the cell when the gases leave. The water that escapes must be replaced to maintain the proper electrolyte level. Only distilled water should be added to the cell. Otherwise, any impurity in the added water will combine chemically with the sulfuric acid on the plates and form a stable compound that will not enter into the charge or discharge action of the battery.

### Carbon-Zinc Cell

This is one of the oldest and most widely used commercial types of dry cell. The carbon, in the form of a rod that is placed in the center of the cell, is the positive terminal. The case of the cell is made of zinc, which is the negative electrode (Fig. 6-7). Between the carbon electrode and the zinc case is the electrolyte of a chemical pastelike mixture. The cell is sealed to prevent the liquid in the paste from evaporating. The voltage of a cell of this type is about 1.5 V.

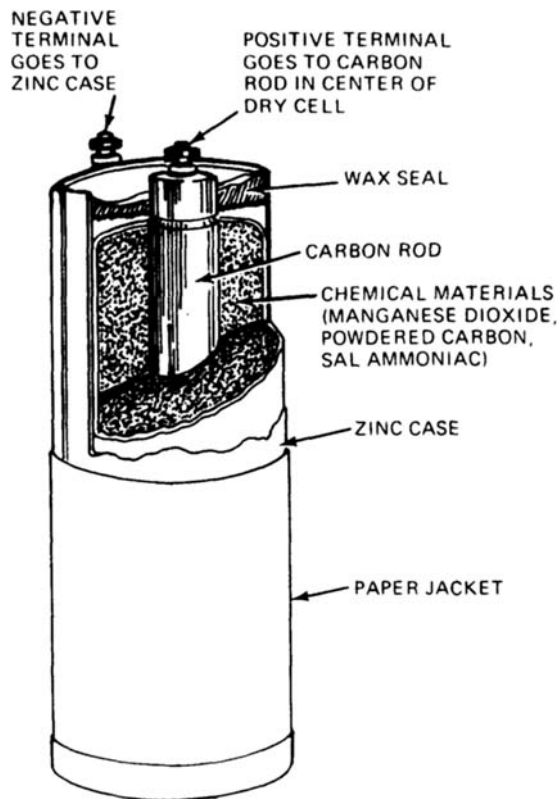


**Fig. 6-7** Construction of carbon-zinc cell, size No. 6. (Courtesy NRI Schools.)

### Alkaline Cell

The secondary alkaline cell is so called because it has an alkaline electrolyte of potassium hydroxide. One battery type that goes by the name *alkaline battery* has a negative electrode of zinc and a positive electrode of manganese dioxide. It generates 1.5 V.

The primary alkaline cell is similar in construction to the rechargeable type and has the same operating voltage (Fig. 6-8). This cell has extended life over a carbon-zinc cell of the same size.

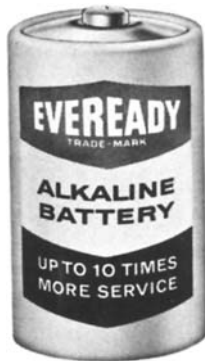

**Fig. 6-8** Manganese-alkaline battery. (From *Grob*, p. 251.)



**Fig. 6-9** Nickel-cadmium battery. (From *Grob*, p. 253.)

### Nickel-Cadmium Cell

In the secondary nickel-cadmium dry cell, the electrolyte is potassium hydroxide, the negative electrode is nickel hydroxide, and the positive electrode is cadmium oxide. The operating voltage is 1.25 V. These cells are manufactured in several sizes, including flat button shapes. The nickel-cadmium battery is the only dry battery that is a true storage battery with a reversible chemical reaction, allowing recharging many times (Fig. 6-9). It is a rugged device which gives dependable service under extreme conditions of shock, vibration, and temperature. Therefore, it is ideally suited for use in powering portable communication equipment such as a two-way radio.

### Edison Cell

A lighter, more rugged secondary cell than the lead-acid cell is the Edison, or nickel-iron-alkaline, cell. It operates at a no-load voltage of 1.4 V. When the voltage drops to 1.0 V, the cell should be recharged. When fully charged, it has a positive plate of nickel and nickel hydrate and a negative plate of iron. Like the lead-acid cell, the Edison cell also produces hydrogen and oxygen gases. As a result the electrolyte requires filling up with distilled water.

### Mercury Cell

There are two different types of mercury cells. One is a flat cell that is shaped like a button, while the other is a cylindrical cell that looks like a standard flashlight cell. The advantage of the button-type cell is that several of them can be stacked inside one container to form a battery. A typical battery is made up of three flat cells (Fig. 6-10). A cell produces 1.35 V.

Mercury cells and batteries have a good shelf life and are very rugged. Because they produce a constant output voltage under different load conditions, they are used in many different products, including electric watches, hearing aids, test instruments, and alarm systems.



**Fig. 6-10** A typical mercury battery. (Courtesy NRI Schools.)



**BATTERY CHARACTERISTICS**

**Internal Resistance**

A battery is a dc voltage generator. All generators have internal resistance,  $R_i$ . In a chemical cell, the resistance of the electrolyte between electrodes is responsible for most of the cell's internal resistance (Fig. 6-11). Since any current in the battery must flow through the internal resistance,  $R_i$  is in series with the generated voltage  $V_B$  (Fig. 6-12a). With no current, the voltage drop across  $R_i$  is zero so that the full generated voltage  $V_B$  develops across the output terminals (Fig. 6-12a). This is the open-circuit voltage, or no-load voltage. If a load resistance  $R_L$  is connected across the battery,  $R_L$  is in series with  $R_i$  (Fig. 6-12b). When current  $I_L$  flows in this circuit, the internal voltage drop,  $I_L R_i$ , decreases the terminal voltage  $V_L$  of the battery so that  $V_L = V_B - I_L R_i$ .

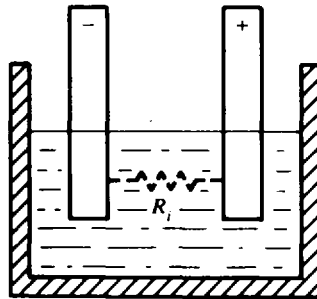


Fig. 6-11 Internal resistance in a cell

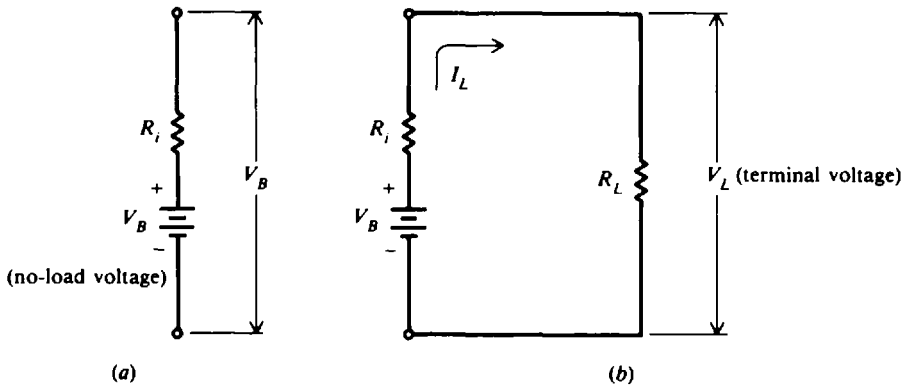


Fig. 6-12 Internal  $I_L R_i$  drop

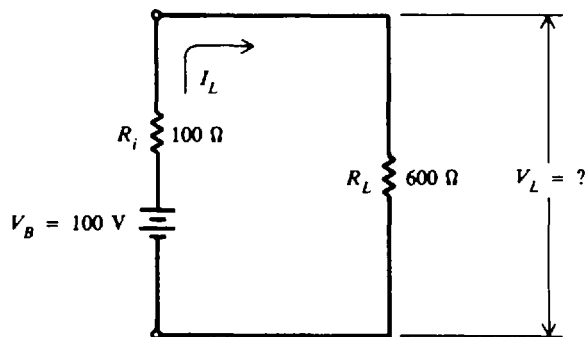


Fig. 6-13

**Example 6.1** A dry battery has an open-circuit, or no-load, voltage of 100 V (Fig. 6-13). If the internal resistance is  $100\ \Omega$  and the load resistance is  $600\ \Omega$ , find the voltage  $V_L$  across the output terminals.

The battery is marked 100 V because 100 V is its open-circuit voltage. With no load, the load current is zero. When load resistance  $R_L$  is added, there is a closed circuit, and the load current is calculated by Ohm's law.

$$I_L = \frac{V}{R_i + R_L} = \frac{100}{100 + 600} = \frac{100}{700} = 0.143\ \text{A}$$

The internal battery drop is

$$I_L R_i = 0.143(100) = 14.3\ \text{V}$$

so that the voltage at the battery's terminal is

$$V_L = V_B - I_L R_i = 100 - 14.3 = 85.7\ \text{V} \quad \text{Ans.}$$

### Specific Gravity

The *specific gravity* of any liquid is a ratio comparing its weight with the weight of an equal volume of water. Pure sulfuric acid has a specific gravity of 1.835 since it weighs 1.835 times as much as water per unit volume.

The specific gravity of the electrolyte solution in a lead-acid cell ranges from 1.210 to 1.300 for new, fully charged batteries. The higher the specific gravity, the less internal resistance of the cell and the higher the possible load current. As the cell discharges, the water formed dilutes the acid and the specific gravity gradually decreases to about 1.150, at which time the cell is considered to be fully discharged. Specific gravity is measured with a *hydrometer* of the syringe type, which has a compressible rubber bulb at the top, a glass barrel, and a rubber hose at the bottom of the barrel. In taking readings with a hydrometer, the decimal point is usually omitted. For example, a specific gravity of 1.270 is read simply as "twelve-seventy." A hydrometer reading of 1210 to 1300 indicates full charge; about 1250 is half-charge; and 1150 to 1200 is complete discharge.

### Capacity

The capacity of a battery is rated in ampere-hours (Ah). The capacity of a storage battery determines how long it will operate at a given discharge rate. For example, a 90-Ah battery must be recharged after 9 h of an average 10-A discharge.

A cell of a lead-acid automobile battery, when fully charged, has an initial voltage of about 2.1 V at no load, but discharges rapidly. The battery is "dead" after about 2 h of discharging under load condition. However, under normal use, this battery type is constantly recharged by the alternator in the automobile.

### Shelf Life

The *shelf life* of a cell is that period of time during which the cell can be stored without losing more than approximately 10 percent of its original capacity. The *capacity* of a cell is its ability to deliver a given amount of current to the circuit in which it is used. The loss of capacity of a stored cell is due primarily to the drying out of its electrolyte (wet cell) and to chemical actions which change the materials within the cell. Since heat stimulates both these actions, the shelf life of a cell can be extended by keeping it in a cool, dry place.

### Comparison of Types

Table 6-1 compares the types of cells described.

Table 6-1 Types of cells

Name	Voltage	Wet or Dry	Primary or Secondary Type	Examples and Characteristics
Lead-acid cell	2.2	Wet	Secondary	Very low $R_i$ and high current ratings; 6- and 12-V batteries
Carbon-zinc cell	1.5	Dry	Primary	AA, A, B, C, and D size cells; flashlight batteries; lowest price; short shelf life; low current capacity
Manganese-alkaline cell	1.5	Dry	Both types	Manganese dioxide and zinc in hydroxide; currents above 300 mA
Nickel-cadmium cell	1.25	Dry	Secondary	Hydroxide electrolyte; constant voltage; reversible chemical reaction; used in rechargeable flashlights, portable power tools
Edison cell	1.4	Wet	Secondary	Nickel and iron in hydroxide; industrial uses
Mercury cell	1.35	Dry	Both types	Mercuric oxide and zinc in hydroxide; constant voltage, long shelf life; B batteries; miniature button cells for hearing aids, cameras, watches, calculators

### Solved Problems

6.1 Write the word or words which most correctly complete the following statements.

- A \_\_\_\_\_ consists of \_\_\_\_\_ or more cells connected in series or parallel.
- A chemical cell consists basically of \_\_\_\_\_ electrodes of different kinds of metals or metallic compounds separated by an \_\_\_\_\_.
- Cells which cannot be effectively recharged are called \_\_\_\_\_ cells.

(d) A cell or a battery is recharged by passing current through it in a direction \_\_\_\_\_ to the direction of its discharge current.

(e) In order to obtain higher voltages, cells are connected in \_\_\_\_\_.

Ans. (a) battery, two; (b) two, electrolyte; (c) primary; (d) opposite; (e) series

6.2 Match the type of cell in column 1 to its characteristic in column 2 (use a letter once only)

Column 1	Column 2
1. Lead-acid	(a) Long shelf life
2. Carbon-zinc	(b) 1.4-V voltage
3. Nickel-cadmium	(c) Automobile battery
4. Edison cell	(d) Inexpensive flashlight cell
5. Mercury	(e) Potassium hydroxide electrolyte
	(f) 3-V voltage

Ans. 1. (c) 2. (d) 3. (e) 4. (b) 5. (a)

6.3 A 6-V battery is temporarily short-circuited. The short-circuit current  $I_{SC}$  is 30 A. What is the internal resistance?

The battery rating of 6 V in this case is the open-circuit, or no-load, voltage. So

$$R_i = \frac{V}{I_{SC}} = \frac{6}{30} = 0.2 \Omega \quad \text{Ans.}$$

Note that the presence of internal resistance prevents the current from becoming very high.

6.4 A battery has a 12-V output on an open circuit, which drops to 11.5 V with a load current of 1 A. Find the internal resistance.

$$\begin{aligned} \text{Open-circuit voltage} &= \text{internal resistance drop} + \text{terminal voltage} \\ V_B &= I_L R_i + V_L \end{aligned}$$

Solving for  $R_i$ ,

$$\begin{aligned} I_L R_i &= V_B - V_L \\ R_i &= \frac{V_B - V_L}{I_L} = \frac{12 - 11.5}{1} = \frac{0.5}{1} = 0.5 \Omega \quad \text{Ans.} \end{aligned}$$

We see that the internal resistance of any battery can be calculated by determining how much the output voltage drops for a specific amount of load current.

6.5 A discharged storage battery of three cells connected in series has an open-circuit voltage of 1.8 V per cell. Each cell has an internal resistance of 0.1  $\Omega$ . What is the minimum voltage of a charging battery to produce an initial charging rate of 10 A?

Charging battery voltage = battery voltage + internal resistance drop

$$\text{Battery voltage (cells in series)} = 3 \text{ cells} \times \frac{1.8 \text{ V}}{\text{cell}} = 5.4 \text{ V}$$

$$\text{Internal resistance drop} = IR_i = 10(3 \times 0.1) = 3 \text{ V}$$

Then,

$$\text{Charging battery voltage} = 5.4 + 3 = 8.4 \text{ V} \quad \text{Ans.}$$

- 6.6 A lead-acid battery is rated at 200 Ah. Based on an 8-h discharge, what average load current can this battery supply?

In units, Capacity = amperes  $\times$  hours

Then, Load current (in amperes) =  $\frac{\text{capacity}}{\text{hours}}$

and Load current =  $\frac{200}{8} = 25 \text{ A}$       *Ans.*

- 6.7 What is the no-load voltage across four carbon-zinc cells in series?

Voltage = 4  $\times$  no-load voltage of a single cell  
= 4(1.5) = 6 V      *Ans.*

- 6.8 What is the specific gravity of a solution with equal parts of sulfuric acid and water?

A solution with equal parts of sulfuric acid and water has a weight equally distributed between sulfuric acid and water (that is, each accounts for one-half the weight of the solution). If pure sulfuric acid has a specific gravity of 1.835, then

Specific gravity of solution =  $\frac{1}{2}(1.835) + \frac{1}{2}(1) = 0.918 + 0.500 = 1.418$       *Ans.*

### Supplementary Problems

- 6.9 Write the word or words which most correctly complete the following statements.

- (a) A cell which converts \_\_\_\_\_ energy into \_\_\_\_\_ energy is called a chemical cell.
- (b) A cell in which the electrolyte is a liquid is commonly referred to as a \_\_\_\_\_ cell, while a cell in which the electrolyte is in a paste form is called a \_\_\_\_\_ cell.
- (c) Cells which can be effectively recharged are called \_\_\_\_\_ cells.
- (d) When charging a cell or a battery, its positive terminal is connected to the \_\_\_\_\_ terminal of the battery charger, and its negative terminal is connected to the \_\_\_\_\_ terminal of the charger.
- (e) In order to obtain a greater current capacity, cells are connected in \_\_\_\_\_.

*Ans.* (a) chemical, electric; (b) wet, dry; (c) secondary; (d) positive, negative; (e) parallel

- 6.10 Match the type of cell in column 1 to its characteristic in column 2.

Column 1	Column 2
1. Lead-acid	(a) Nickel-iron-alkaline
2. Carbon-zinc	(b) 12-V battery
3. Nickel-cadmium	(c) Secondary dry battery
4. Edison cell	(d) 1.5-V primary cell
5. Mercury	(e) 5-V battery
	(f) Ideal for transistorized equipment

*Ans.* 1. (b) 2. (d) 3. (c) 4. (a) 5. (f)

6.11 Fill in the missing quantities (Fig. 6-14).

$V_B, V$	$R_i, \Omega$	$R_L, \Omega$	$I_L, A$	$I_L R_i, V$	$V_L, V$
100	?	?	2	?	80
6	0.2	1	?	?	?
12	?	5	?	?	2

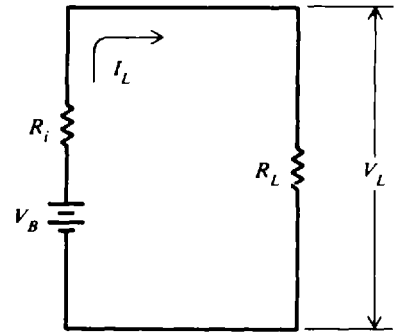


Fig. 6-14

Ans.

$V_B, V$	$R_i, \Omega$	$R_L, \Omega$	$I_L, A$	$I_L R_i, V$	$V_L, V$
....	10	40	....	20	....
....	....	....	5	1	5
....	25	....	0.4	10	....

6.12 The terminal voltage  $V_L$  drops as the load current  $I_L$  increases. For a 12-V battery with internal resistance of  $1 \Omega$ , we vary the load resistance from a very high value to zero in order to observe how the terminal voltage varies with changing load current. Fill in the missing values of the table.

$V_B, V$	$R_i, \Omega$	$R_L, \Omega$	$R_T = R_L + R_i, \Omega$	$I_L, A$	$I_L R_i, V$	$V_L = V_B - I_L R_i, V$
12	1	$\infty$	?	?	?	?
12	1	9	?	?	?	?
12	1	5	?	?	?	?
12	1	3	?	?	?	?
12	1	1	?	?	?	?
12	1	0	?	?	?	?

Ans.

$V_B, V$	$R_i, \Omega$	$R_L, \Omega$	$R_T = R_L + R_i, \Omega$	$I_L, A$	$I_L R_i, V$	$V_L = V_B - I_L R_i, V$
....	....	....	$\infty$	0	0	12
....	....	....	10	1.2	1.2	10.8
....	....	....	6	2	2	10
....	....	....	4	3	3	9
....	....	....	2	6	6	6
....	....	....	1	12	12	0

6.13 For Prob. 6.12 make a plot with terminal voltage  $V_L$  as the ordinate and load current  $I_L$  as the abscissa. Describe the plot.

Ans. See Fig. 6-15. The plot is a straight line, where  $V_L$  is a maximum when the circuit is open ( $I_L$  is zero) and a minimum when the circuit is shorted ( $I_L$  is a maximum).

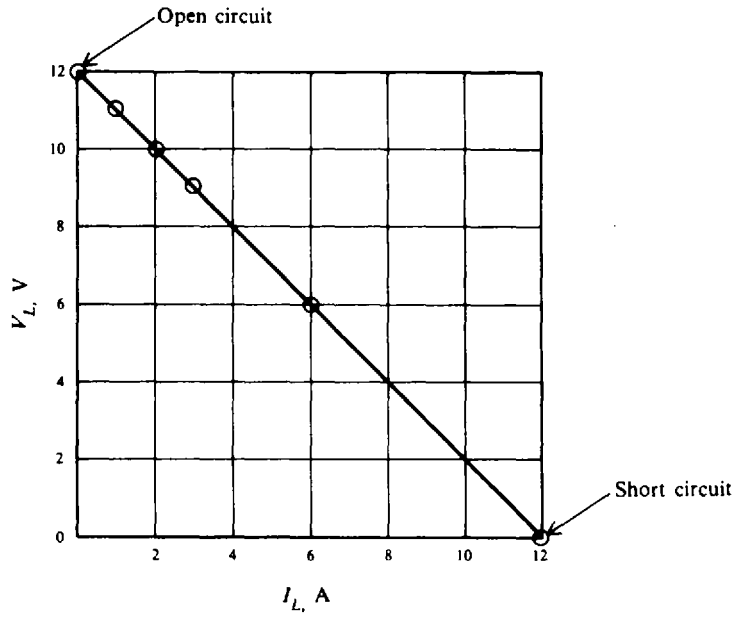


Fig. 6-15

- 6.14 A 6-V lead-acid battery has an internal resistance of  $0.02 \Omega$ . How much current will flow if the battery has a short circuit? *Ans.* 300 A
- 6.15 A new carbon-zinc cell has a voltage of 1.5 V. A battery made up of 30 cells connected in series ages so that its no-load voltage drops 15 percent. What is the no-load voltage of the cell and battery? *Ans.* 1.28 V, 38.2 V
- 6.16 What is the specific gravity of the electrolyte of a lead-acid battery with one-fourth part sulfuric acid and three-fourths part water? Would a hydrometer reading of that solution indicate full charge, half-charge, or discharge? *Ans.* 1.209, full charge
- 6.17 How many cells are necessary to produce a battery with double the voltage and current rating of a single cell? Draw a schematic diagram. *Ans.* Four cells; see Fig. 6-16.

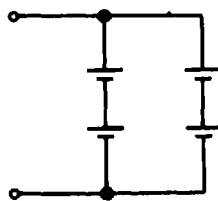


Fig. 6-16

- 6.18 Draw pictorial and schematic diagrams showing two 12-V lead-acid batteries being charged by a 15-V source. Show the direction of current during charge. *Ans.* See Fig. 6-17.

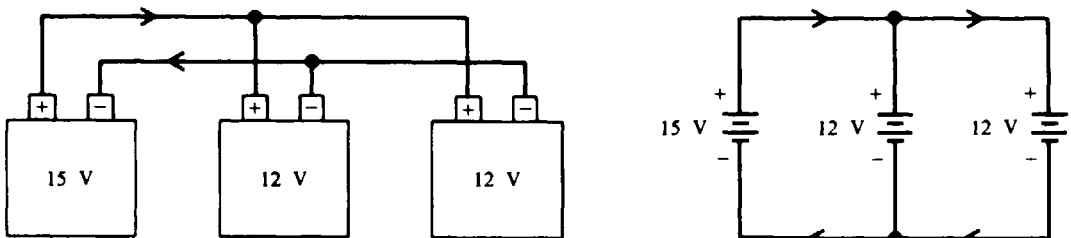


Fig. 6-17

## Kirchhoff's Laws

### KIRCHHOFF'S VOLTAGE LAW (KVL)

Kirchhoff's *voltage law* states that *the voltage applied to a closed circuit equals the sum of the voltage drops in that circuit*. This fact was used in the study of series circuits and was expressed as follows:

$$\begin{aligned} \text{Voltage applied} &= \text{sum of voltage drops} \\ V_A &= V_1 + V_2 + V_3 \end{aligned} \quad (7-1)$$

where  $V_A$  is the applied voltage and  $V_1$ ,  $V_2$ , and  $V_3$  are voltage drops.

Another way of stating KVL is that the algebraic sum of the voltage rises and voltage drops must be equal to zero. A voltage source or emf is considered a voltage rise; a voltage across a resistor is a voltage drop. Often for convenience in labeling, letter subscripts are shown for voltage sources and numerical subscripts for voltage drops. This form of the law can be written by transposing the right members of Eq. (7-1) to the left side.

$$\text{Voltage applied} - \text{sum of voltage drops} = 0$$

Substitute letters:

$$\begin{aligned} V_A - V_1 - V_2 - V_3 &= 0 \\ \text{or} \quad V_A - (V_1 + V_2 + V_3) &= 0 \end{aligned}$$

Using a new symbol,  $\Sigma$ , the Greek capital letter sigma, we have

$$\Sigma V = V_A - V_1 - V_2 - V_3 = 0 \quad (7-2)$$

in which  $\Sigma V$ , the algebraic sum of all the voltages around any closed circuit, equals zero.  $\Sigma$  means "sum of."

We assign a + sign to a voltage rise and a - sign to a voltage drop for the  $\Sigma V = 0$  formula (Fig. 7-1). In tracing voltage drops around a circuit, start at the negative terminal of the voltage source. The path from the negative terminal to the positive terminal through the source is a voltage rise. We continue to trace the circuit from the positive terminal through all resistors and back to the negative terminal of the source. In Fig. 7-1 if we start at point  $a$ , the negative terminal of the battery, and move around the circuit in the direction  $abcd$ , we go through  $V_A$  from - to + and  $V_A = +100$  V. If we start at point  $b$  and move in the opposite direction  $badcb$ , we go through  $V_A$  from + to - and  $V_A = -100$  V. The voltage drop across any resistance will be negative (-) if we trace it in the + to - direction. Thus in Fig. 7-1, if we trace the circuit in the direction  $abcd$ ,  $V_1 = -50$  V,  $V_2 = -30$  V, and  $V_3 = -20$  V. The voltage drop will be positive (+) if we

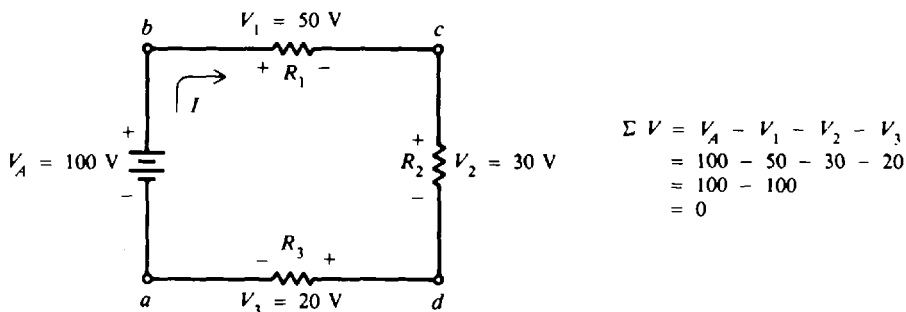


Fig. 7-1 Illustration of  $\Sigma V = 0$



go through the resistance in the - to + direction. So in tracing the circuit in the direction *abcd*, we have

$$\begin{aligned} \Sigma V &= 0 \\ V_A - V_1 - V_2 - V_3 &= 0 \\ 100 - 50 - 30 - 20 &= 0 \\ 0 &= 0 \end{aligned}$$

**Example 7.1** Determine the direction of voltage around the circuit *abcd* (Fig. 7-2), and then write the expression for voltages around the circuit.

Assume direction of current as shown. Mark the + and - polarities of each resistor.

- $V_A$  is a voltage source (+). (It is a voltage rise in the current direction assumed.)
- $V_1$  is a voltage drop (-). (It is a decrease in the direction assumed.)
- $V_2$  is a voltage drop (-). (It is a decrease in the direction assumed.)
- $V_B$  is a voltage source (-). (It is a decrease in voltage in the current direction assumed.)
- $V_3$  is a voltage drop (-). (It is a decrease in the direction assumed.)

$$\begin{aligned} \Sigma V &= 0 \\ +V_A - V_1 - V_2 - V_B - V_3 &= 0 \end{aligned}$$

Group the voltage rises and the voltage drops.

$$V_A - (V_1 + V_2 + V_3 + V_B)$$

Notice that the voltage drops include a voltage source  $V_B$ . Ordinarily a source would be positive. In this case the polarity of the source is acting against the assumed direction of current. Therefore, its effect is to decrease the voltage.

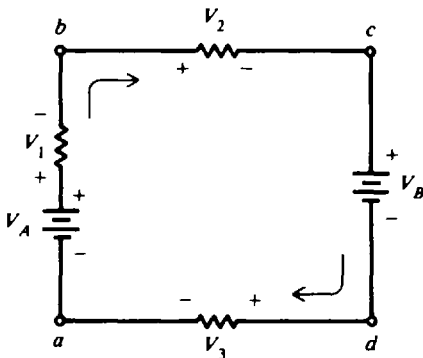


Fig. 7-2 KVL illustration with two sources

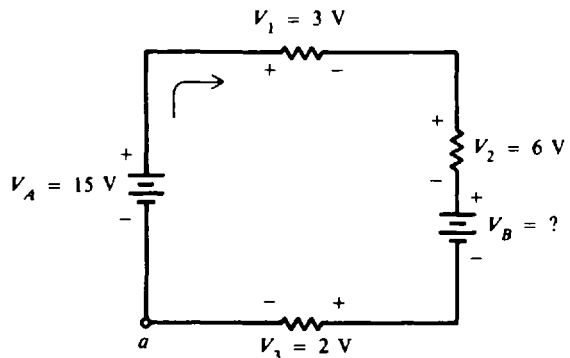


Fig. 7-3 Finding a source voltage

**Example 7.2** Determine the voltage  $V_B$  (Fig. 7-3).

The direction of current flow is shown by the arrow. Mark the polarity of the voltage drops across the resistors. Trace the circuit in the direction of current flow starting at point *a*. Write the voltage equation around the circuit.

$$\Sigma V = 0 \tag{7-2}$$

Use + and - rules for voltage rises and voltage drops.

$$V_A - V_1 - V_2 - V_B - V_3 = 0$$


Solve for  $V_B$ .

$$V_B = V_A - V_1 - V_2 - V_3 = 15 - 3 - 6 - 2 = 4 \text{ V} \quad \text{Ans.}$$

Since  $V_B$  was found to be positive, the assumed direction of current is in fact the actual direction of current.

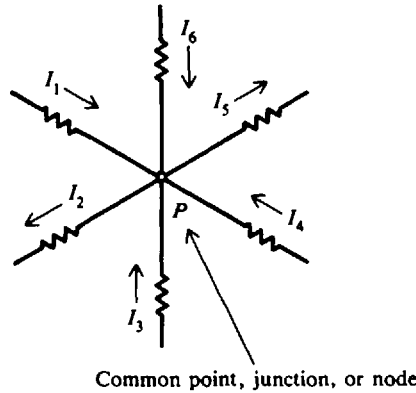**KIRCHHOFF'S CURRENT LAW (KCL)**

Kirchhoff's current law states that the sum of the currents entering a junction is equal to the sum of the currents leaving the junction. Suppose we have six currents leaving and entering a common junction or point, shown as P (Fig. 7-4). This common point is also called a node.



Common point, junction, or node  
**Fig. 7-4** Currents at a common point

Sum of all currents entering = sum of all currents leaving

Substitute letters:

$$I_1 + I_3 + I_4 + I_6 = I_2 + I_5$$

If we consider that the currents flowing toward a junction are positive (+) and those currents flowing away from the same junction are negative (-), then this law also states that the algebraic sum of all the currents meeting at a common junction is zero. Using the symbol  $\Sigma$ , we have


$$\Sigma I = 0 \tag{7-3}$$

where  $\Sigma I$ , the algebraic sum of all the currents at the common point, is zero.

$$I_1 - I_2 + I_3 + I_4 - I_5 + I_6 = 0$$

If the negative terms are transposed to the right side of the equal sign, we would have the same form as the original equation.

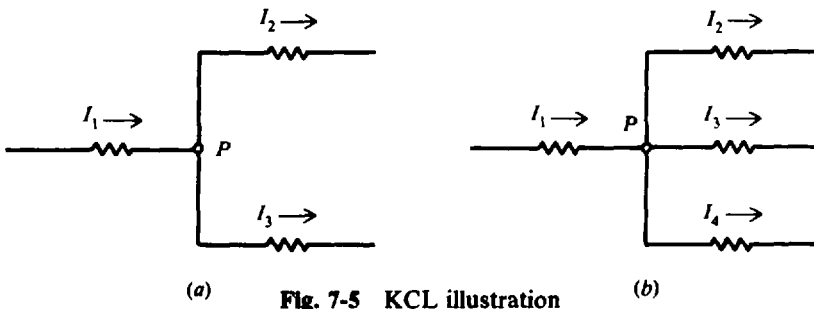**Example 7.3** Write the equation for current  $I_1$  for part a and part b of Fig. 7-5.



(a) **Fig. 7-5** KCL illustration (b)

The algebraic sum of all currents at the node is zero. Entering currents are +; leaving currents are -.


(a)  $+I_1 - I_2 - I_3 = 0$

$I_1 = I_2 + I_3$       *Ans.*

(b)  $+I_1 - I_2 - I_3 - I_4 = 0$

$I_1 = I_2 + I_3 + I_4$       *Ans.*

**Example 7.4** Find the unknown currents in part *a* and part *b* of Fig. 7-6.

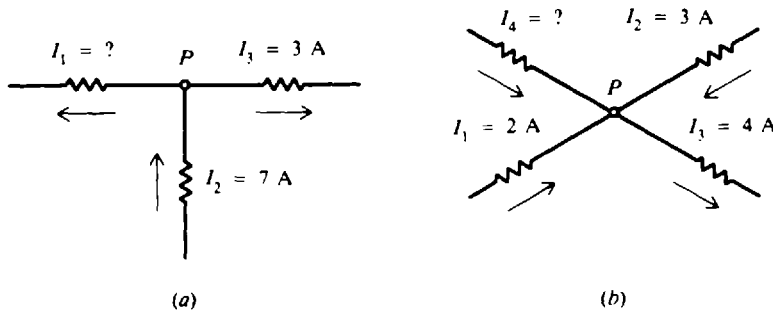

**Fig. 7-6** Finding current

The algebraic sum of all currents at the node is zero. Entering currents are +; leaving currents are -.

$$(a) \quad -I_1 + I_2 - I_3 = 0$$

$$I_1 = I_2 - I_3 = 7 - 3 = 4 \text{ A} \quad \text{Ans.}$$


$$(b) \quad +I_1 + I_2 - I_3 + I_4 = 0$$

$$I_4 = -I_1 - I_2 + I_3 = -2 - 3 + 4 = -1 \text{ A} \quad \text{Ans.}$$

The negative sign for  $I_4$  means that the assumed direction of  $I_4$  is incorrect and that  $I_4$  is actually flowing away from point  $P$ .

## MESH CURRENTS

A simplification of Kirchhoff's laws is a method that makes use of *mesh* or *loop currents*. A *mesh* is any closed path of a circuit. It does not matter whether the path contains a voltage source. In solving a circuit with mesh currents, we first must decide which paths will be the meshes. Then we assign a mesh current to each mesh. For convenience, mesh currents are usually assigned in a clockwise direction. This direction is arbitrary, but the clockwise direction is usually assumed. Kirchhoff's voltage law is then applied about the path of each mesh. The resulting equations determine the unknown mesh currents. From these currents, the current or voltage of any resistor can be found.

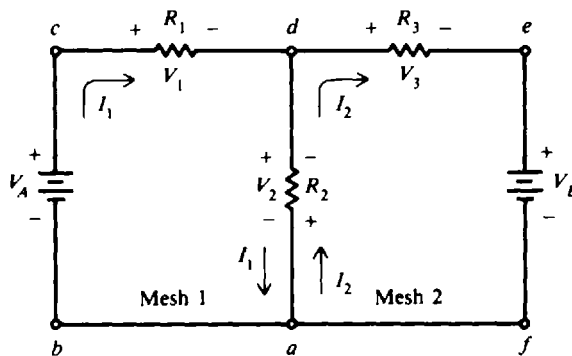

**Fig. 7-7** Two-mesh circuit

In Fig. 7-7, we have a two-mesh circuit marked mesh 1 and mesh 2. Mesh 1 is path  $abcda$  and mesh 2 is path  $adefa$ . All voltage sources and resistances are known. A procedure for finding mesh currents  $I_1$  and  $I_2$  is as follows:

**Step 1.** After the meshes are selected, show the direction of mesh currents  $I_1$  and  $I_2$  in a clockwise direction. Mark the voltage polarity across each resistor, consistent with the assumed

current. Remember that conventional current flow in a resistor produces positive polarity where the current enters.

**Step 2.** Apply Kirchhoff's voltage law,  $\Sigma V = 0$ , around each mesh. Trace each mesh in the direction of mesh current. Note that there are two different currents ( $I_1, I_2$ ) flowing in opposite directions through the same resistor,  $R_2$ , which is common to both meshes. For this reason two sets of polarities are shown by  $R_2$  (Fig. 7-7). Trace mesh 1 in direction *abcd*.

$$\begin{aligned} +V_A - I_1R_1 - I_1R_2 + I_2R_2 &= 0 \\ +V_A - I_1(R_1 + R_2) + I_2R_2 &= 0 \\ +I_1(R_1 + R_2) - I_2R_2 &= V_A \end{aligned} \tag{1}$$

Note that in the first expression  $I_2R_2$  is + since we go through a voltage drop from - to +. Trace mesh 2 in direction *adefa*.

$$\begin{aligned} -I_2R_2 + I_1R_2 - I_2R_3 - V_B &= 0 \\ +I_1R_2 - I_2(R_2 + R_3) &= V_B \end{aligned} \tag{2}$$

Note that  $I_1R_2$  is a + voltage drop since we go through a voltage drop from - to +.


**Step 3.** Find  $I_1$  and  $I_2$  by solving Eqs. (1) and (2) simultaneously.

**Step 4.** When mesh currents are known, find all resistor voltage drops by using Ohm's law.

**Step 5.** Check the solution of mesh currents by tracing mesh *abcdefa*.

$$V_A - I_1R_1 - I_2R_3 - V_B = 0$$

**Example 7.5** Given  $V_A = 58 \text{ V}$ ,  $V_B = 10 \text{ V}$ ,  $R_1 = 4 \Omega$ ,  $R_2 = 3 \Omega$ , and  $R_3 = 2 \Omega$  (Fig. 7-8a), find all mesh currents and voltage drops in the circuit.

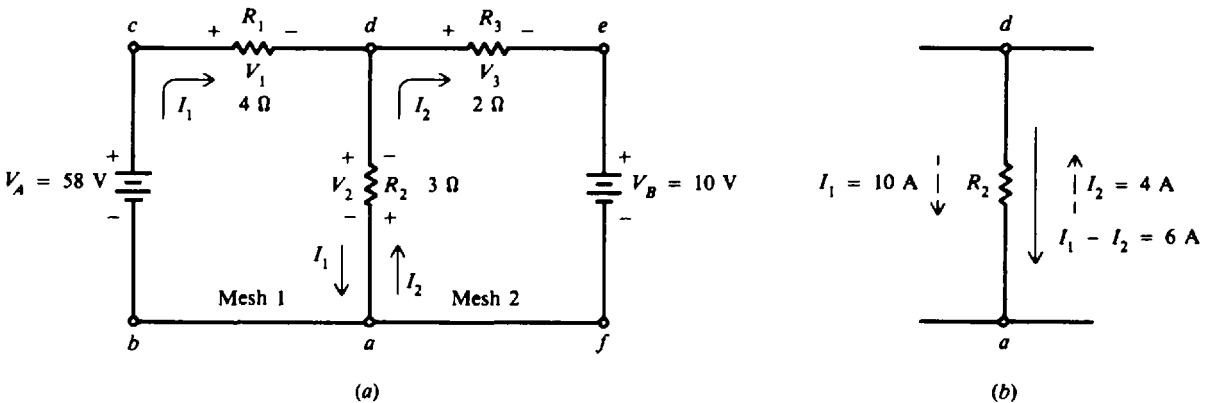

**Fig. 7-8** Finding mesh currents and voltage drops

**Step 1.** Choose the two loops or meshes shown. Show mesh current in the clockwise direction. Show polarity marks across each resistor.

**Step 2.** Apply  $\Sigma V = 0$  in mesh 1 and mesh 2 and trace the mesh in the direction of mesh current.

Mesh 1, *abcd*:

$$\begin{aligned} +58 - 4I_1 - 3I_1 + 3I_2 &= 0 \\ +7I_1 - 3I_2 &= 58 \end{aligned} \tag{1}$$

Mesh 2, *adefa*:

$$\begin{aligned} 3I_1 - 3I_2 - 2I_2 - 10 &= 0 \\ 3I_1 - 5I_2 &= 10 \end{aligned} \tag{2}$$

Note that mesh currents  $I_1$  and  $I_2$  flow through the common resistor  $R_2$ .

**Step 3.** Find  $I_1$  and  $I_2$  by solving Eqs. (1) and (2) simultaneously.

$$7I_1 - 3I_2 = 58 \quad (1)$$

$$3I_1 - 5I_2 = 10 \quad (2)$$

Multiply Eq. (1) by 5 and multiply Eq. (2) by 3, getting Eqs. (1a) and (2a) and then subtract Eq. (2a) from Eq. (1a).

$$35I_1 - 15I_2 = 290 \quad (1a)$$

$$9I_1 - 15I_2 = 30 \quad (2a)$$

$$\hline 26I_1 = 260$$

$$I_1 = 10 \text{ A} \quad \text{Ans.}$$

Substitute  $I_1 = 10 \text{ A}$  in Eq. (1) to find  $I_2$ .

$$7I_1 - 3I_2 = 58$$

$$7(10) - 3I_2 = 58$$

$$-3I_2 = 58 - 70$$

$$I_2 = \frac{70 - 58}{3} = \frac{12}{3} = 4 \text{ A} \quad \text{Ans.}$$

The current through branch  $da$  is

$$I_{da} = I_1 - I_2 = 10 - 4 = 6 \text{ A} \quad \text{Ans.}$$

In this case the assumed mesh current direction was correct because the current values are positive. If the current value were negative, the true direction would be opposite to the assumed direction of current. (See Fig. 7-8b.)

**Step 4.** Find all voltage drops.

$$V_1 = I_1 R_1 = 10(4) = 40 \text{ V} \quad \text{Ans.}$$

$$V_2 = (I_1 - I_2) R_2 = 6(3) = 18 \text{ V} \quad \text{Ans.}$$

$$V_3 = I_2 R_3 = 4(2) = 8 \text{ V} \quad \text{Ans.}$$

**Step 5.** Check mesh current solution by tracing loop  $abcdefa$  and applying KVL.

$$V_A - V_1 - V_3 - V_B = 0$$

$$58 - 40 - 8 - 10 = 0$$

$$58 - 58 = 0$$

$$0 = 0 \quad \text{Check}$$

## NODE VOLTAGES

Another method for solving a circuit with mesh currents uses the voltage drops to specify the currents at a node. Then node equations of currents are written to satisfy Kirchhoff's current law. By solving the node equations, we can calculate the unknown node voltages. A *node* is a common connection for two or more components. A *principal node* has three or more connections. To each node in a circuit a letter or number is assigned.  $A$ ,  $B$ ,  $G$ , and  $N$  are nodes, and  $G$  and  $N$  are principal nodes, or junctions (Fig. 7-9). A *node voltage* is the voltage of a given node with respect to one particular node called the *reference node*. Select node  $G$  connected to chassis ground as the reference node. Then  $V_{AG}$  is the voltage between nodes  $A$  and  $G$ ,  $V_{BG}$  is the voltage between nodes  $B$  and  $G$ , and  $V_{NG}$  is the voltage between nodes  $N$  and  $G$ . Since the node voltage is always determined with respect to a specified reference node, the notations  $V_A$  for  $V_{AG}$ ,  $V_B$  for  $V_{BG}$ , and  $V_N$  for  $V_{NG}$  are used.

With the exception of the reference node, equations using KCL can be written at each principal node. Thus the required number of equations is one less than the number of principal

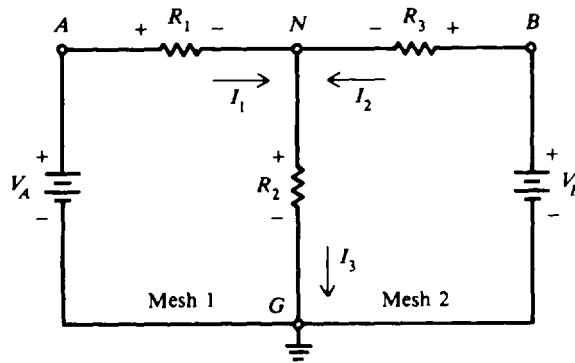


Fig. 7-9 Nodes in a two-mesh circuit

nodes. Since the circuit shown (Fig. 7-9) has two principal nodes ( $N$  and  $G$ ), only one equation need be written at node  $N$  to find all voltage drops and currents in the circuit.

Assume that branch currents  $I_1$  and  $I_2$  enter node  $N$ , and  $I_3$  leaves the node (Fig. 7-9). The selection of the direction of the currents is arbitrary. From KCL,

$$\begin{aligned} \Sigma I &= 0 \\ I_1 + I_2 - I_3 &= 0 \\ I_3 &= I_1 + I_2 \end{aligned} \tag{1}$$

By Ohm's law,

$$I_3 = \frac{V_N}{R_2} \tag{1a}$$

$$I_1 = \frac{V_A - V_N}{R_1} \tag{1b}$$

$$I_2 = \frac{V_B - V_N}{R_3} \tag{1c}$$

Substitute these expressions into Eq. (1).

$$\frac{V_N}{R_2} = \frac{V_A - V_N}{R_1} + \frac{V_B - V_N}{R_3} \tag{2}$$

If  $V_A$ ,  $V_B$ ,  $R_1$ ,  $R_2$ , and  $R_3$  are known,  $V_N$  can be calculated from Eq. (2). Then all voltage drops and currents in the circuit can be determined.

**Example 7.6** The circuit of Fig. 7-8 (Example 7.5) solved by the method of branch currents is redrawn in Fig. 7-10. Solve by node-voltage analysis.

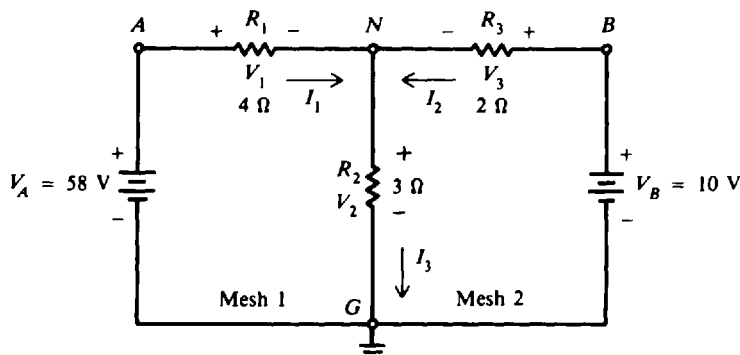


Fig. 7-10 Node-voltage analysis for same circuit as in Fig. 7-8

**Step 1.** Assume the direction of currents shown (Fig. 7-10). Mark nodes A, B, N, and G. Mark the voltage polarity across each resistor consistent with assumed direction of current.

**Step 2.** Apply KCL at principal node N and solve for  $V_N$ .

$$I_3 = I_1 + I_2$$

$$\frac{V_N}{R_2} = \frac{V_A - V_N}{R_1} + \frac{V_B - V_N}{R_3}$$

$$\frac{V_N}{3} = \frac{58 - V_N}{4} + \frac{10 - V_N}{2}$$

Clear fractions by multiplying each term by 12.

$$4V_N = 3(58 - V_N) + 6(10 - V_N)$$

$$4V_N = 174 - 3V_N + 60 - 6V_N$$

$$13V_N = 234$$

$$V_N = 18 \text{ V}$$

**Step 3.** Find all voltage drops and currents.

$$V_1 = V_A - V_N = 58 - 18 = 40 \text{ V} \quad \text{Ans.}$$

$$V_2 = V_N = 18 \text{ V} \quad \text{Ans.}$$

$$V_3 = V_B - V_N = 10 - 18 = -8 \text{ V} \quad \text{Ans.}$$

The negative value for  $V_3$  means  $I_2$  is flowing opposite to the assumed direction and the polarity of  $V_3$  is the reverse of the signs shown across  $R_3$  (Fig. 7-10).

$$I_1 = \frac{V_1}{R_1} = \frac{40}{4} = 10 \text{ A} \quad \text{Ans.}$$

$$I_2 = \frac{V_3}{R_3} = \frac{-8}{2} = -4 \text{ A} \quad \text{Ans.}$$


$$I_3 = I_1 + I_2 = 10 - 4 = 6 \text{ A} \quad \text{Ans.}$$

$$I_3 = \frac{V_2}{R_2} = \frac{18}{3} = 6 \text{ A} \quad \text{Check}$$

All calculated values agree with those of Example 7.5.

## Solved Problems

**7.1** Find the signs of the voltages when tracing the mesh *afedcba* and write the expression for KVL (Fig. 7-11).

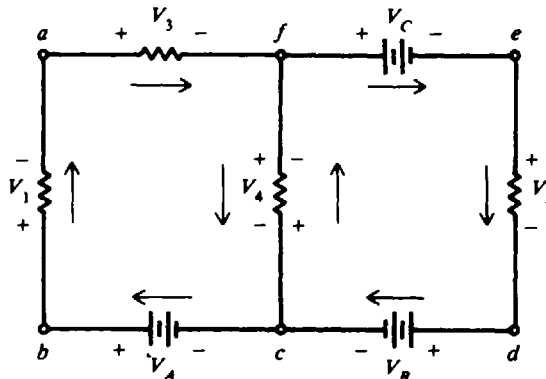

**Fig. 7-11** Tracing two meshes

Assume directions of current flow as indicated. Mark the polarities across each resistor.

- $V_3$  is - since we go through a voltage drop + to -.
- $V_C$  is - since we go through a voltage rise + to -.
- $V_2$  is - since we go through a voltage drop + to -.
- $V_B$  is - since we go through a voltage rise + to -.
- $V_A$  is + since we go through a voltage rise - to +.
- $V_1$  is - since we go through a voltage drop + to -.

$$\begin{aligned} \Sigma V &= 0 \\ -V_3 - V_C - V_2 - V_B + V_A - V_1 &= 0 \\ V_A - V_B - V_C - V_1 - V_2 - V_3 &= 0 \\ \underbrace{(V_A - V_B - V_C)}_{\text{Voltage rise}} - \underbrace{(V_1 + V_2 + V_3)}_{\text{Voltage drop}} &= 0 \end{aligned} \quad \text{Ans.}$$

7.2 Find  $I_3$  and  $I_4$  (Fig. 7-12).

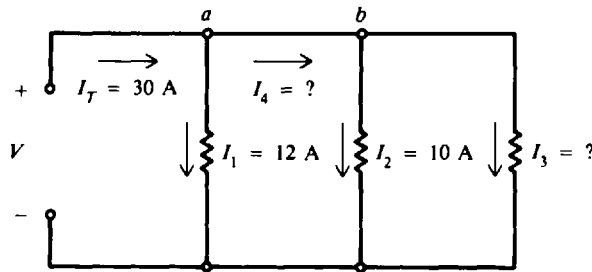


Fig. 7-12 Finding currents by KCL

Apply KCL,  $\Sigma I = 0$  at node  $a$ .

$$\begin{aligned} 30 - 12 - I_4 &= 0 \\ I_4 &= 30 - 12 = 18 \text{ A} \quad \text{Ans.} \end{aligned}$$

Apply KCL,  $\Sigma I = 0$  at node  $b$ .

$$\begin{aligned} 18 - 10 - I_3 &= 0 \\ I_3 &= 18 - 10 = 8 \text{ A} \quad \text{Ans.} \end{aligned}$$

Check solution.

$$\begin{aligned} I_T &= I_1 + I_2 + I_3 \\ 30 &= 12 + 10 + 8 \\ 30 &= 30 \quad \text{Check} \end{aligned}$$

7.3 Solve the two-mesh circuit for all mesh currents (Fig. 7-13).

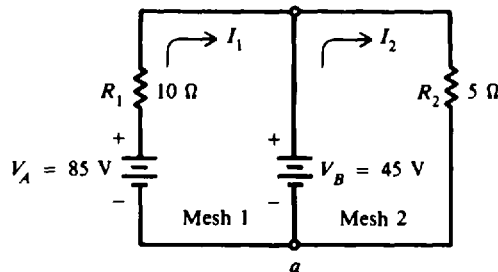


Fig. 7-13 Two meshes with voltage source in middle leg



**Step 1.** Show mesh currents in clockwise direction.

**Step 2.** Apply  $\Sigma V = 0$  for mesh 1 and mesh 2 and trace each mesh from *a* in the direction of mesh current.


$$\begin{aligned} \text{Mesh 1:} \quad & 85 - 10I_1 - 45 = 0 \\ & 10I_1 = 40 \\ & I_1 = 4 \text{ A} \quad \text{Ans.} \end{aligned}$$

$$\begin{aligned} \text{Mesh 2:} \quad & 45 - 5I_2 = 0 \\ & 5I_2 = 45 \\ & I_2 = 9 \text{ A} \quad \text{Ans.} \end{aligned}$$

**Step 3.** Check by tracing the loop of mesh 1 and 2 by using  $\Sigma V = 0$ .

$$\begin{aligned} V_A - I_1R_1 - I_2R_2 &= 0 \\ 85 - 4(10) - 9(5) &= 0 \\ 85 - 40 - 45 &= 0 \\ 85 - 85 &= 0 \quad \text{Check} \end{aligned}$$

**7.4** Find all mesh currents and voltage drops for the two-mesh circuit shown in Fig. 7-14.

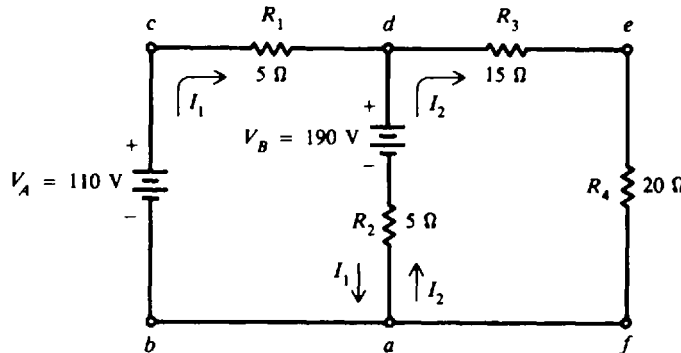

**Fig. 7-14** Two meshes with voltage source and resistor in middle leg

**Step 1.** Show the direction of mesh currents as indicated.

**Step 2.** Apply  $\Sigma V = 0$  for meshes 1 and 2, in the direction of mesh current.

$$\begin{aligned} \text{Mesh 1, } abcda: \quad & 110 - 5I_1 - 190 - 5I_1 + 5I_2 = 0 \\ & -10I_1 + 5I_2 - 80 = 0 \\ & -10I_1 + 5I_2 = 80 \end{aligned} \quad (1)$$

$$\begin{aligned} \text{Mesh 2, } adefa: \quad & 5I_1 - 5I_2 + 190 - 15I_2 - 20I_2 = 0 \\ & 5I_1 - 40I_2 = -190 \end{aligned} \quad (2)$$

**Step 3.** Find  $I_1$  and  $I_2$  by solving Eqs. (1) and (2) simultaneously.

$$-10I_1 + 5I_2 = 80 \quad (1)$$

$$5I_1 - 40I_2 = -190 \quad (2)$$

Multiply Eq. (2) by 2 to get Eq. (2a); then add.

$$-10I_1 + 5I_2 = 80 \quad (1)$$

$$\begin{aligned} & 10I_1 - 80I_2 = -380 \\ \hline & -75I_2 = -300 \end{aligned} \quad (2a)$$

$$I_2 = \frac{300}{75} = 4 \text{ A} \quad \text{Ans.}$$

Substitute  $I_2 = 4\text{ A}$  in Eq. (1) to find  $I_1$ .

$$\begin{aligned} -10I_1 + 5(4) &= 80 \\ -10I_1 &= 60 \\ I_1 &= -6\text{ A} \quad \text{Ans.} \end{aligned}$$

The negative sign means that the assumed direction for  $I_1$  was not correct.  $I_1$  is actually going in a counterclockwise direction. In branch  $ad$ ,  $I_1$  and  $I_2$  are going in the same direction. Therefore,

$$I_{ad} = I_1 + I_2 = 6 + 4 = 10\text{ A} \quad \text{Ans.}$$


**Step 4.** Find the voltage drops.

$$\begin{aligned} V_1 &= I_1 R_1 = 6(5) = 30\text{ V} \quad \text{Ans.} \\ V_2 &= (I_1 + I_2)R_2 = 10(5) = 50\text{ V} \quad \text{Ans.} \\ V_3 &= I_2 R_3 = 4(15) = 60\text{ V} \quad \text{Ans.} \\ V_4 &= I_2 R_4 = 4(20) = 80\text{ V} \quad \text{Ans.} \end{aligned}$$

**Step 5.** Check. Trace the loop  $abcdefa$  (use the original assumed direction for  $I_1$  and  $I_2$ ).

$$\begin{aligned} +V_A - I_1 R_1 - I_2 R_3 - I_2 R_4 &= 0 \\ 110 - (-6)(5) - 4(15) - 4(20) &= 0 \\ 110 + 30 - 60 - 80 &= 0 \\ 140 - 140 &= 0 \quad \text{Check} \end{aligned}$$

**7.5** Find the voltage  $V_2$  across  $R_2$  by the method of node-voltage analysis (Fig. 7-15a).

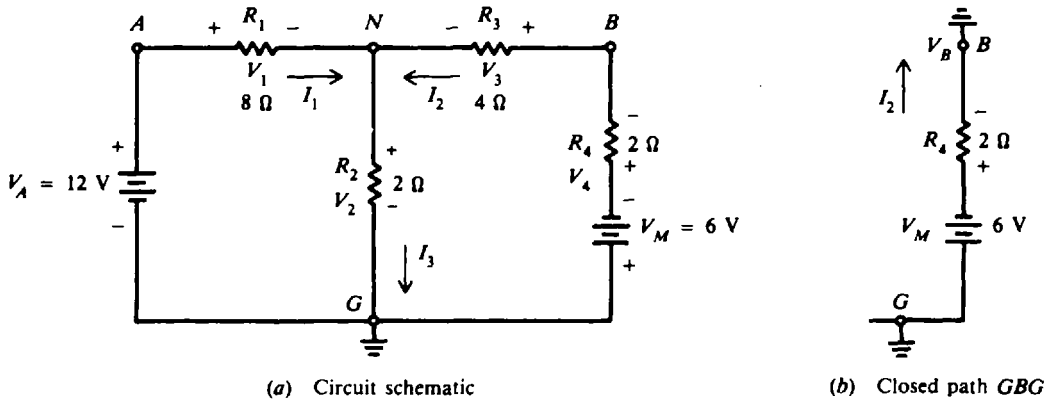

**Fig. 7-15** Finding  $V_2$  by the node-voltage method

**Step 1.** Assume direction of currents shown. Mark voltage polarities. Show nodes  $A, B, N, G$ .

**Step 2.** Apply  $\sum I = 0$  at principal node  $N$ .

$$I_3 = I_1 + I_2 \tag{1}$$

$$I_3 = \frac{V_2}{R_2} = \frac{V_N}{2} \tag{1a}$$

$$I_1 = \frac{V_1}{R_1} = \frac{V_A - V_N}{R_1} = \frac{12 - V_N}{8} \tag{1b}$$

$$I_2 = \frac{V_3}{R_3} = \frac{V_B - V_N}{R_3} = \frac{V_B - V_N}{4} \tag{1c}$$

We are unable to determine  $V_B$  by inspection in Eq. (1c) because voltage drop  $V_4$  is not given (Fig. 7-15a). So we use KVL to find  $V_B$  by tracing the complete circuit from  $G$  to  $B$  in the direction of  $I_2$  (Fig. 7-15b).  $GBG$  is a complete path because  $V_B$  is the voltage at  $B$  with respect to ground.

$$\begin{aligned} -6 - 2I_2 - V_B &= 0 \\ V_B &= -6 - 2I_2 \end{aligned}$$

Substitute expression for  $V_B$  into Eq. (1c),

$$I_2 = \frac{-6 - 2I_2 - V_N}{4}$$

from which we obtain

$$I_2 = \frac{-6 - V_N}{6}$$

Substitute the three expressions for current into Eq. (1).

$$\frac{V_N}{2} = \frac{12 - V_N}{8} + \frac{-6 - V_N}{6} \quad (2)$$

Now Eq. (2) has one unknown,  $V_N$ .

**Step 3.** Find  $V_2$  ( $V_2 = V_N$ ). Multiply each member of Eq. (2) by 24.

$$\begin{aligned} 12V_N &= (36 - 3V_N) + (-24 - 4V_N) \\ 19V_N &= 12 \\ V_N &= \frac{12}{19} = 0.632 \text{ V} \\ V_2 = V_N &= 0.632 \text{ V} \quad \text{Ans.} \end{aligned}$$

**7.6** Write the mesh equations for the three-mesh circuit (Fig. 7-16). Do not solve.

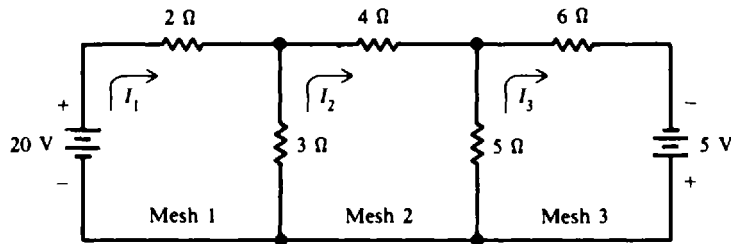


Fig. 7-16 A three-mesh circuit

Show mesh currents in clockwise direction. Trace loops in assumed direction of current, using KVL,  $\sum V = 0$ .

$$\text{Mesh 1:} \quad 20 - 2I_1 - 3I_1 + 3I_2 = 0 \quad (1)$$

$$\text{Mesh 2:} \quad -4I_2 - 5I_2 + 5I_3 - 3I_2 + 3I_1 = 0 \quad (2)$$

$$\text{Mesh 3:} \quad -6I_3 + 5 - 5I_3 + 5I_2 = 0 \quad (3)$$

Combine and rearrange terms in each equation.

$$\text{Mesh 1:} \quad 20 = 5I_1 - 3I_2 \quad \text{Ans.} \quad (1a)$$


$$\text{Mesh 2:} \quad 0 = -3I_1 + 12I_2 - 5I_3 \quad \text{Ans.} \quad (2a)$$

$$\text{Mesh 3:} \quad 5 = -5I_2 + 11I_3 \quad \text{Ans.} \quad (3a)$$


A set with any number of simultaneous equations, for any number of meshes, can be solved by using determinants. This procedure is shown in mathematics textbooks.

### Supplementary Problems

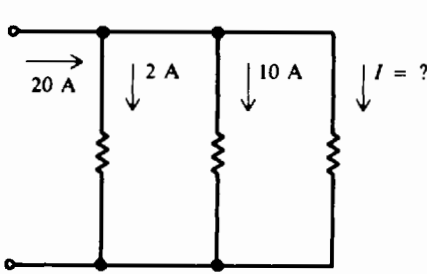7.7 Find the unknown quantities indicated in Fig. 7-17a and b. *Ans.* (a)  $I = 8\text{ A}$ ; (b)  $V_B = 10\text{ V}$



(a)

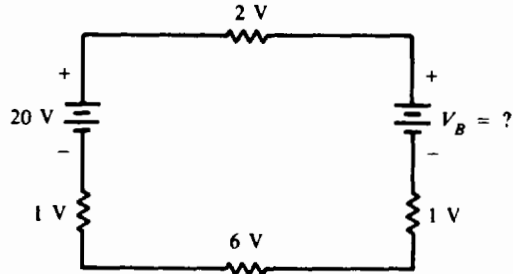

(b)

Fig. 7-17

7.8 Find the series current and voltage drops across  $R_1$  and  $R_2$  (Fig. 7-18).

*Ans.*  $I = 1\text{ A}$ ;  $V_1 = 10\text{ V}$ ;  $V_2 = 20\text{ V}$

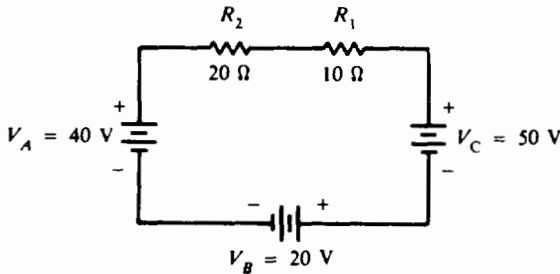


Fig. 7-18

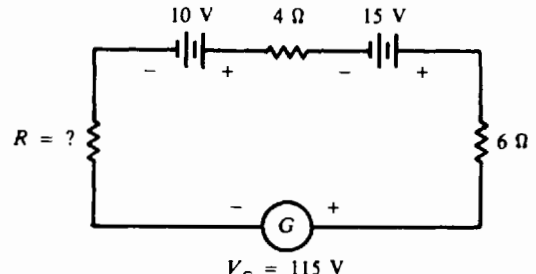


Fig. 7-19

7.9 A current of 6 A flows in the circuit (Fig. 7-19). Find the value of  $R$ . *Ans.*  $R = 5\text{ Ohms}$

7.10 Find  $I_2$ ,  $I_3$ , and  $V_A$  (Fig. 7-20). *Ans.*  $I_2 = 6\text{ A}$ ;  $I_3 = 2\text{ A}$ ;  $V_A = 152\text{ V}$

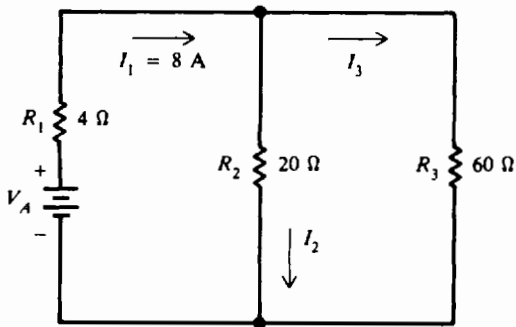


Fig. 7-20

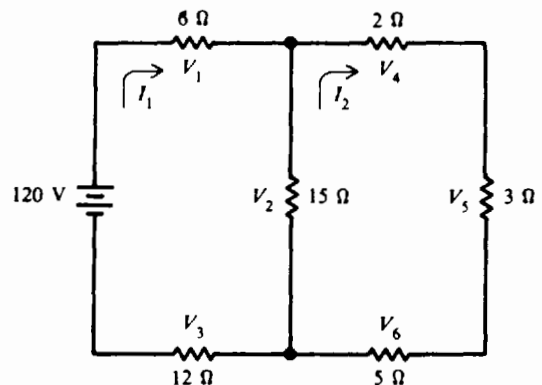


Fig. 7-21

7.11 Find mesh currents  $I_1$  and  $I_2$  and all voltage drops by the mesh-current method (Fig. 7-21).

*Ans.*  $I_1 = 5\text{ A}$ ;  $I_2 = 3\text{ A}$ ;  $V_1 = 30\text{ V}$ ;  $V_2 = 30\text{ V}$ ;  $V_3 = 60\text{ V}$ ;  $V_4 = 6\text{ V}$ ;  $V_5 = 9\text{ V}$ ;  $V_6 = 15\text{ V}$

7.12 Find all currents through the resistances by the mesh-current method (Fig. 7-22).

*Ans.*  $I_1 = 3\text{ A}$ ;  $I_2 = 1\text{ A}$ ;  $I_1 - I_2 = 2\text{ A}$  (flowing from a to b)

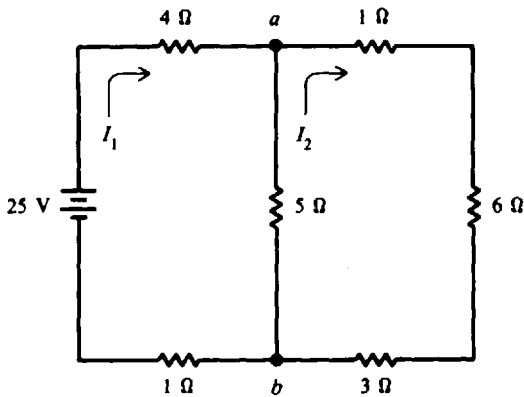


Fig. 7-22

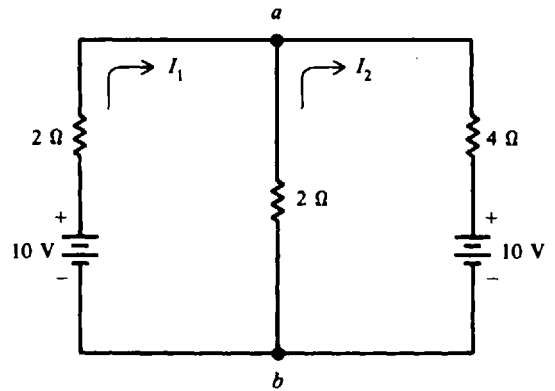


Fig. 7-23

- 7.13 Find the current in each resistor, using the mesh-current method (Fig. 7-23).  
 Ans.  $I_1 = 2 \text{ A}$ ;  $I_2 = -1 \text{ A}$  (current direction was assumed incorrectly), or  $I_2 = 1 \text{ A}$  in counter-clockwise direction;  $I_1 + I_2 = 3 \text{ A}$  (flowing from a to b)
- 7.14 Find currents  $I_1$  and  $I_2$  and the current through the 20-V battery using the mesh-current method (Fig. 7-24).  
 Ans.  $I_1 = 2 \text{ A}$ ;  $I_2 = 5 \text{ A}$ ;  $I_2 - I_1 = 3 \text{ A}$  (flowing from b to a)

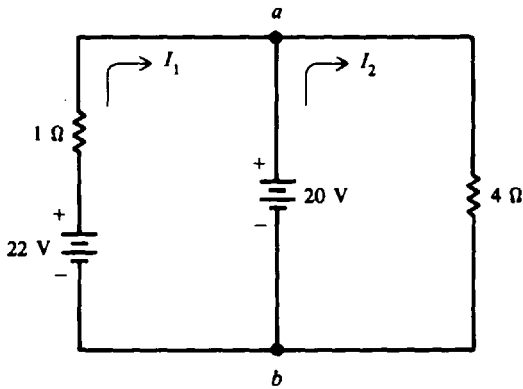


Fig. 7-24

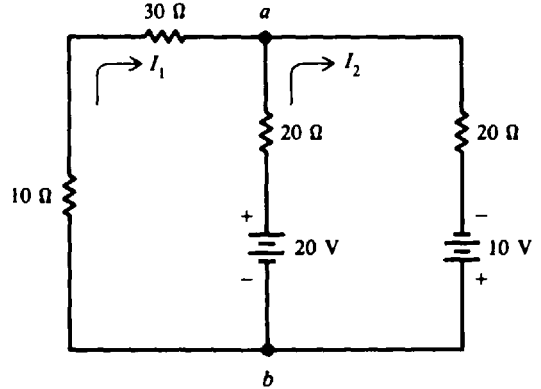


Fig. 7-25

- 7.15 Find currents  $I_1$  and  $I_2$  and the current through the resistor in series with the 20-V battery (Fig. 7-25). Use the mesh-current method.  
 Ans.  $I_1 = -0.1 \text{ A}$  (direction assumed incorrectly.  $I_1$  is actually going in the counterclockwise direction);  $I_2 = 0.7 \text{ A}$ ;  $I_1 + I_2 = 0.8 \text{ A}$  (flowing from b to a)
- 7.16 Find currents  $I_1$  and  $I_2$  and current through the 20-Ω resistor common to meshes 1 and 2 (Fig. 7-26). Use the mesh-current method.  
 Ans.  $I_1 = 0.6 \text{ A}$ ;  $I_2 = 0.4 \text{ A}$ ;  $I_1 - I_2 = 0.2 \text{ A}$  (flowing from a to b)

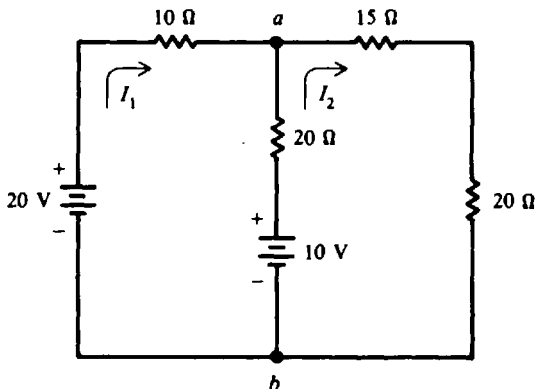


Fig. 7-26

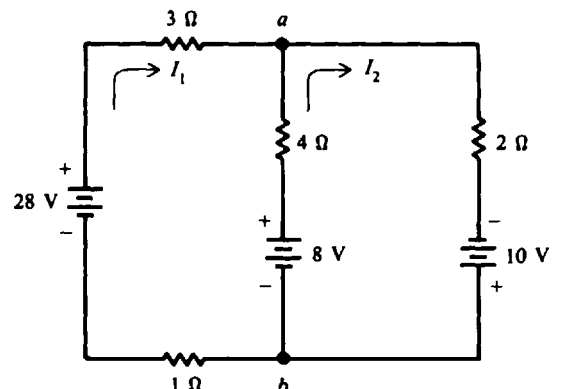


Fig. 7-27

7.17 Find all the currents in the circuit shown by the mesh-current method (Fig. 7-27).

Ans.  $I_1 = 6 \text{ A}$ ;  $I_2 = 7 \text{ A}$ ;  $I_2 - I_1 = 1 \text{ A}$  (flowing from  $b$  to  $a$ )

7.18 Find all the currents and voltage drops by the method of node-voltage analysis (Fig. 7-28).

Ans.  $I_1 = 5 \text{ A}$ ;  $I_2 = -1 \text{ A}$  (opposite to direction shown);  $I_3 = 4 \text{ A}$ ;  $V_1 = 60 \text{ V}$ ;  $V_2 = 24 \text{ V}$ ;  $V_3 = 3 \text{ V}$

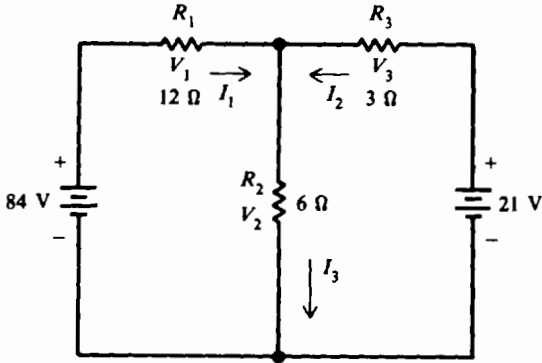


Fig. 7-28

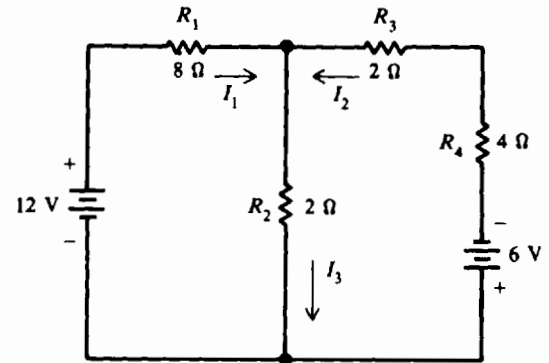


Fig. 7-29

7.19 Find by the node-voltage method all currents and voltage drops (Fig. 7-29).

Ans.  $I_1 = 1.42 \text{ A}$ ;  $I_2 = -1.10 \text{ A}$  (opposite to direction shown);  $I_3 = 0.32 \text{ A}$ ;  $V_1 = 11.4 \text{ V}$ ;  $V_2 = 0.64 \text{ V}$ ;  $V_3 = 2.2 \text{ V}$ ;  $V_4 = 4.4 \text{ V}$

7.20 Write the mesh equations for the circuit (Fig. 7-30). Do not solve.

Ans.  $6I_1 - 2I_2 = 10$ ;  $-2I_1 + 8I_2 - 2I_3 = 0$ ;  $-2I_2 + 6I_3 = -4$

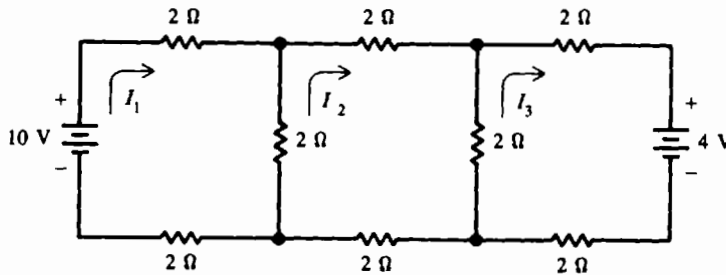



Fig. 7-30

7.21 Verify values of currents in circuit shown in Fig. 7-23 (Prob. 7.13) by the node-voltage method.

7.22 Verify values of currents in circuit of Fig. 7-25 (Prob. 7.15) by the node-voltage method.

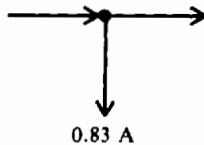7.23 Find the magnitude of all currents and show their directions at node  $N$  (Fig. 7-31). (Hint:  $V_N = 1.67 \text{ V}$ .)

Ans.  $0.94 \text{ A}$   $N$   $0.11 \text{ A}$



7.24 If the  $20\text{-}\Omega$  resistor (Fig. 7-31) is replaced by a  $30\text{-}\Omega$  resistor, what is the nodal voltage  $V_N$ !

Ans.  $V_N = 3.75 \text{ V}$

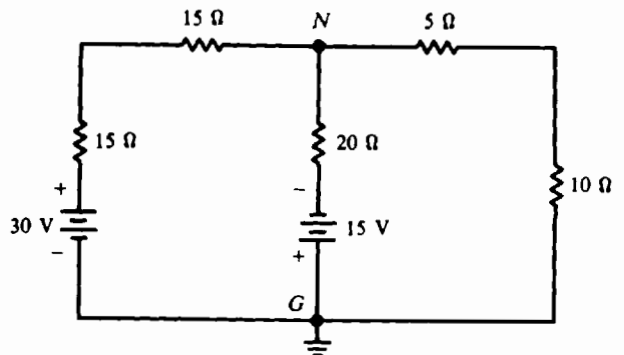


Fig. 7-31

## Network Calculations

### Y AND DELTA NETWORKS

The network in Fig. 8-1 is called a T ("tee") or Y ("wye") network because of its shape. T and Y are different names for the same network, except that in the Y network the  $R_a$  and  $R_b$  arms form the upper part of a Y.

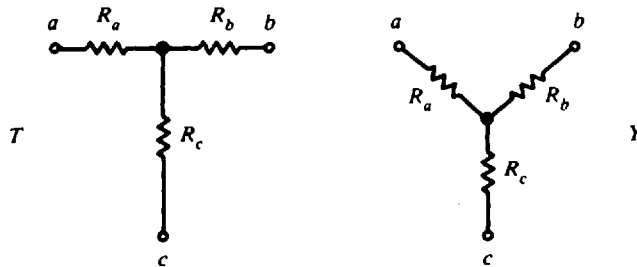


Fig. 8-1 Form of a T or Y network

The network in Fig. 8-2 is called a  $\Pi$  (pi) or  $\Delta$  (delta) network because its shape resembles these Greek letters;  $\Pi$  and  $\Delta$  are different names for the same network.

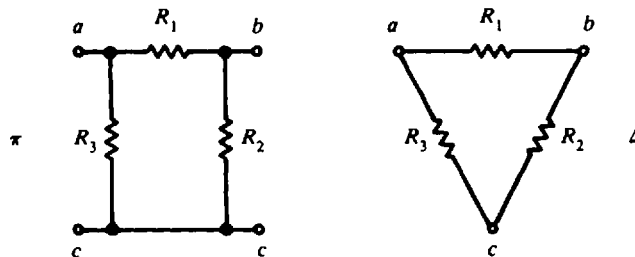


Fig. 8-2 Form of a  $\pi$  or  $\Delta$  network

In analyzing networks it is helpful to convert Y to  $\Delta$  or  $\Delta$  to Y to simplify the solution. The formulas for these conversions are derived from Kirchhoff's laws. Note that resistances in Y have subscript letters,  $R_a$ ,  $R_b$ , and  $R_c$ , while the resistances in  $\Delta$  are numbered  $R_1$ ,  $R_2$ , and  $R_3$ .

Resistances are shown in a three-terminal network with three terminals  $a$ ,  $b$ , and  $c$ . After the conversion formulas are used, one network is equivalent to the other because they have equivalent resistances across any one pair of terminals.

### $\Delta$ to Y Conversion, or $\Pi$ to T

See Fig. 8-3.

$$R_a = \frac{R_1 R_3}{R_1 + R_2 + R_3} \quad (8-1)$$

$$R_b = \frac{R_1 R_2}{R_1 + R_2 + R_3} \quad (8-2)$$

$$R_c = \frac{R_2 R_3}{R_1 + R_2 + R_3} \quad (8-3)$$

**Rule 1:** The rule for  $\Delta$  to Y conversion can be stated as follows: The resistance of any branch of the Y network is equal to the product of the two adjacent sides of the  $\Delta$  network divided by the sum of the three  $\Delta$  resistances.

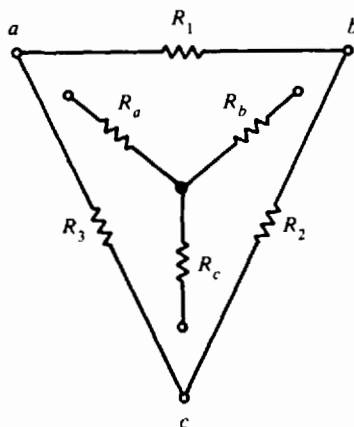


Fig. 8-3 Conversion between Y and  $\Delta$  networks

### Y to $\Delta$ Conversion, or T to $\Pi$

See Fig. 8-3.

$$R_1 = \frac{R_a R_b + R_b R_c + R_c R_a}{R_c} \quad (8-4)$$

$$R_2 = \frac{R_a R_b + R_b R_c + R_c R_a}{R_a} \quad (8-5)$$

$$R_3 = \frac{R_a R_b + R_b R_c + R_c R_a}{R_b} \quad (8-6)$$

**Rule 2:** The rule for Y to  $\Delta$  conversion can be stated as follows: The resistance of any side of the  $\Delta$  network is equal to the sum of the Y network resistances multiplied two at a time, divided by the resistance of the opposite branch of the Y network.

As an aid in using Eqs. (8-1) to (8-6), the following scheme is useful. Place the Y inside the  $\Delta$  (Fig. 8-3). Note that the  $\Delta$  has three closed sides, while the Y has three open arms. Also note how each resistor in the open has two adjacent resistors in the closed sides. For  $R_a$ , adjacent resistors are  $R_1$  and  $R_3$ ; for  $R_b$ , adjacent resistors are  $R_1$  and  $R_2$ ; and for  $R_c$ , adjacent resistors are  $R_2$  and  $R_3$ . Furthermore, each resistor can be considered opposite each other in the two networks. For example, open arm  $R_c$  is opposite closed side  $R_1$ ;  $R_b$  is opposite  $R_3$ ; and  $R_a$  is opposite  $R_2$ .

**Example 8.1** A  $\Delta$  network is shown in Fig. 8-4a. Find the resistances of an equivalent Y network (Fig. 8-4b) and draw the network.


Place Y network within  $\Delta$  network and find resistances by using  $\Delta$  to Y conversion rule (see Fig. 8-4c).

$$\begin{aligned} R_a &= \frac{R_1 R_3}{R_1 + R_2 + R_3} & (8-1) \\ &= \frac{4(6)}{10 + 6 + 4} = \frac{24}{20} = 1.2 \Omega & \text{Ans.} \end{aligned}$$


$$\begin{aligned} R_b &= \frac{R_1 R_2}{R_1 + R_2 + R_3} & (8-2) \\ &= \frac{4(10)}{20} = \frac{40}{20} = 2 \Omega & \text{Ans.} \end{aligned}$$
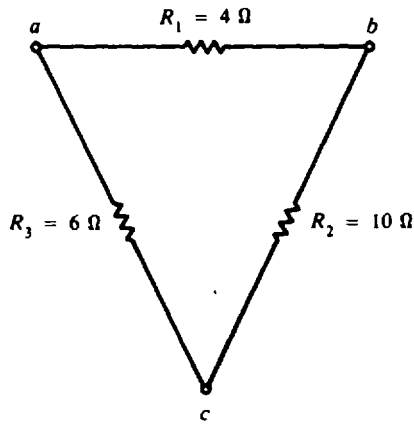
$$\begin{aligned} R_c &= \frac{R_2 R_3}{R_1 + R_2 + R_3} & (8-3) \\ &= \frac{10(6)}{20} = \frac{60}{20} = 3 \Omega & \text{Ans.} \end{aligned}$$







(a)  $\Delta$  Known

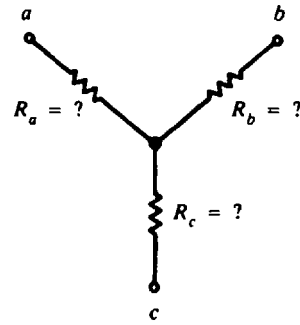

(b) Y Unknown

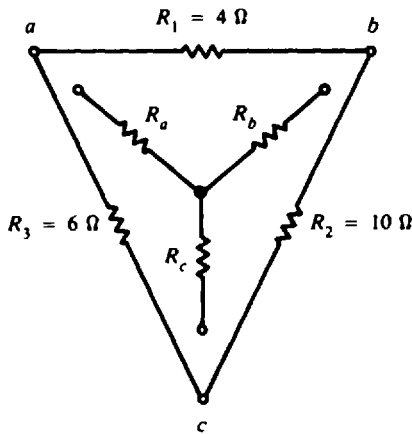


(c)

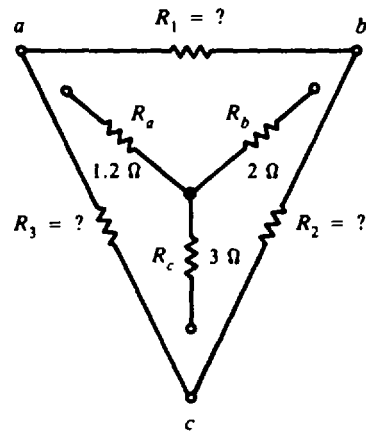

(d)

Fig. 8-4  $\Delta$  to Y conversion

The equivalent Y network is

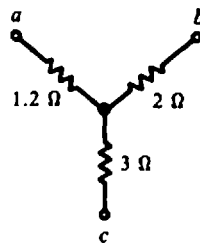

Ans.

**Example 8.2** Given the calculated resistances of the Y network in Example 8.1,  $R_a = 1.2 \Omega$ ,  $R_b = 2 \Omega$ , and  $R_c = 3 \Omega$ , confirm the values of equivalent resistances in the  $\Delta$  network of  $R_1 = 4 \Omega$ ,  $R_2 = 10 \Omega$ , and  $R_3 = 6 \Omega$ .

Place Y network within  $\Delta$  network as in previous example and find  $\Delta$  resistance by using Y to  $\Delta$  rule. (See Fig. 8-4d.)

$$R_1 = \frac{R_a R_b + R_b R_c + R_c R_a}{R_c} \tag{8-4}$$

$$= \frac{1.2(2) + 2(3) + 3(1.2)}{3} = \frac{2.4 + 6 + 3.6}{3} = \frac{12}{3} = 4 \Omega \quad \text{Ans.}$$

$$R_2 = \frac{R_a R_b + R_b R_c + R_c R_a}{R_a} \tag{8-5}$$

$$= \frac{12}{1.2} = 10 \Omega \quad \text{Ans.}$$

$$R_3 = \frac{R_a R_b + R_b R_c + R_c R_a}{R_b} \tag{8-6}$$

$$= \frac{12}{2} = 6 \Omega \quad \text{Ans.}$$

The results show that the  $\Delta$  and Y networks (Fig. 8-4) are equivalent to each other when they have three resistance values obtained with the conversion formulas.

**Example 8.3** Use network conversion to find the equivalent or total resistance  $R_T$  between  $a$  and  $d$  in a bridge circuit consisting of two deltas (Fig. 8-5a).

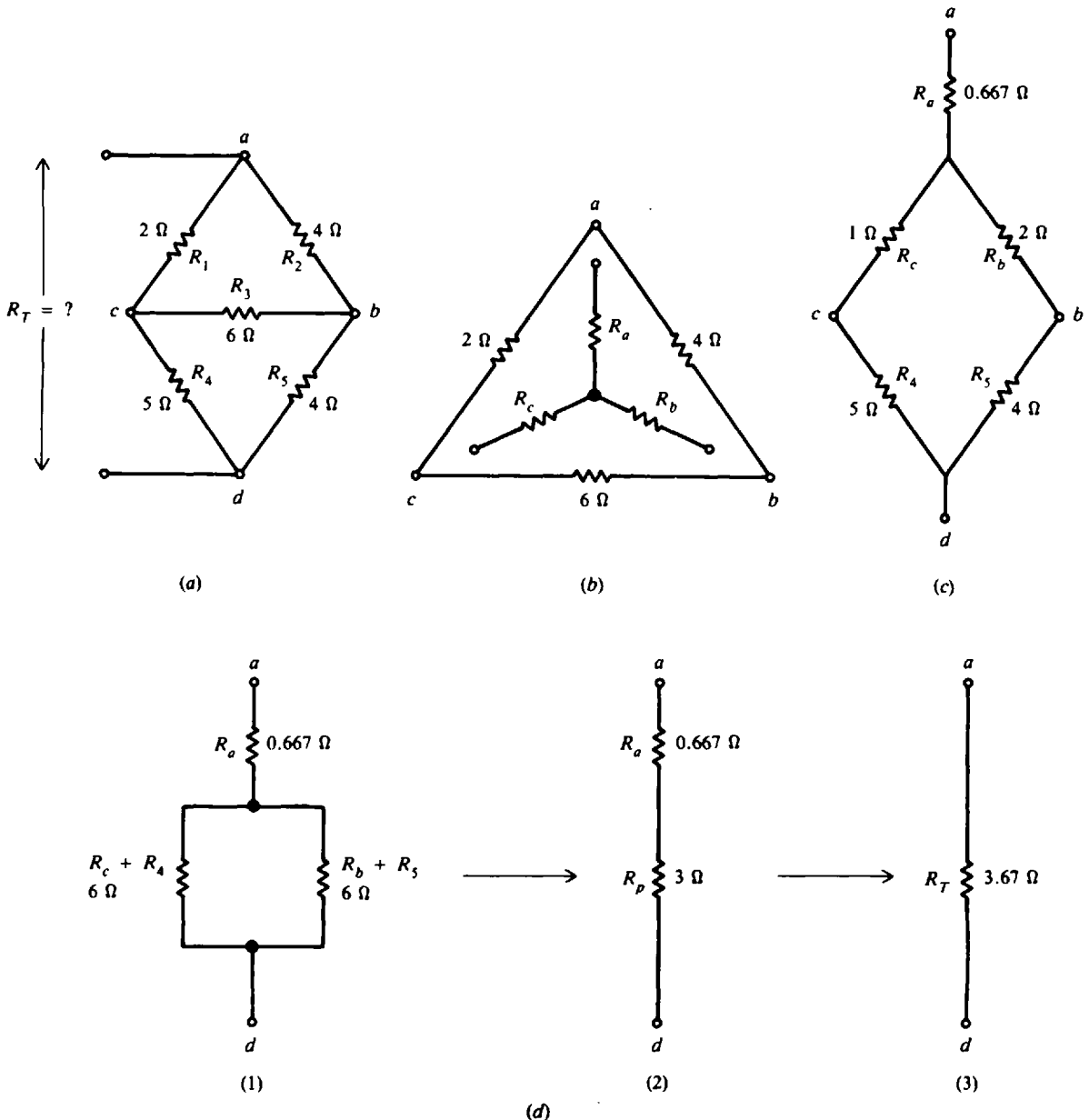


Fig. 8-5 Reducing a bridge circuit by  $\Delta$  to Y conversion

**Step 1.** Transform  $\Delta$  network  $abc$  into its equivalent  $Y$ . Use the rule for  $\Delta$  to  $Y$  conversion (Fig. 8-5b).

$$R_a = \frac{2(4)}{2 + 4 + 6} = \frac{8}{12} = 0.667 \Omega$$

$$R_b = \frac{4(6)}{12} = \frac{24}{12} = 2 \Omega$$

$$R_c = \frac{2(6)}{12} = \frac{12}{12} = 1 \Omega$$

**Step 2.** Replace the  $\Delta$  with its  $Y$  equivalent (Fig. 8-5c) in the original bridge circuit.

**Step 3.** Simplify the series-parallel circuit. First, combine series resistances. Resistances  $R_c$  and  $R_4$  are in series, and  $R_b$  and  $R_5$  are in series [Fig. 8-5d(1)].

$$R_c + R_4 = 1 + 5 = 6 \Omega$$

$$R_b + R_5 = 2 + 4 = 6 \Omega$$

Next combine the parallel branches,  $R_c + R_4$  and  $R_b + R_5$ . Since the resistances are equal [Fig. 8-5d(2)],

$$R_p = \frac{6}{2} = 3 \Omega$$

Finally, combine series resistances  $R_a$  and  $R_p$  [Fig. 8-5d(3)].

$$R_T = R_a + R_p = 0.667 + 3 = 3.67 \Omega \quad \text{Ans.}$$

## SUPERPOSITION

The superposition theorem states that in a network with two or more sources the current or voltage for any component is the algebraic sum of the effects produced by each source acting independently. In order to use one source at a time, all other sources are removed from the circuit. A voltage source is removed by replacing it with a short circuit. A current source is removed by replacing it with an open circuit.

In order to superimpose currents and voltages, all the components must be linear and bilateral. *Linear* means that the current is proportional to the applied voltage; that is, the current and voltage obey Ohm's law,  $I = V/R$ . Then the currents calculated for different source voltages can be superimposed, that is, added algebraically. *Bilateral* means that the current is the same amount for opposite polarities of the source voltage. Then the values for opposite directions of current can be added algebraically.

**Example 8.4** Find branch currents  $I_1$ ,  $I_2$ , and  $I_3$  by the superposition theorem (Fig. 8-6a).

**Step 1.** Find the currents produced by voltage source  $V_1$  only.

(a) Replace voltage source  $V_2$  with a short circuit (Fig. 8-6b). Use the subscript  $V_1$  after a comma to indicate that only source  $V_1$  is supplying the circuit. For example,  $I_{1, v_1}$  is current  $I_1$  due only to source  $V_1$  and  $I_{2, v_1}$  is current  $I_2$  due only to source  $V_1$ .

(b) Combine series and parallel resistances to reduce the circuit to a single source and a single resistance (Fig. 8-6c). Solve for currents produced by  $V_1$ .

$$R_4 = R_1 + \frac{R_2 R_3}{R_2 + R_3} = 1 + \frac{1(1)}{1 + 1} = 1 + 0.5 = 1.5 \Omega$$

$$I_{1, v_1} = \frac{V_1}{R_4} = \frac{3}{1.5} = 2 \text{ A}$$

$I_{1, v_1}$  will divide symmetrically at point  $a$  because of equal resistances  $R_2$  and  $R_3$  (Fig. 8-6b) so that

$$I_{2, v_1} = -\frac{1}{2} I_{1, v_1} = -\frac{1}{2} 2 = -1 \text{ A}$$

$$I_{3, v_1} = \frac{1}{2} I_{1, v_1} = \frac{1}{2} 2 = 1 \text{ A}$$

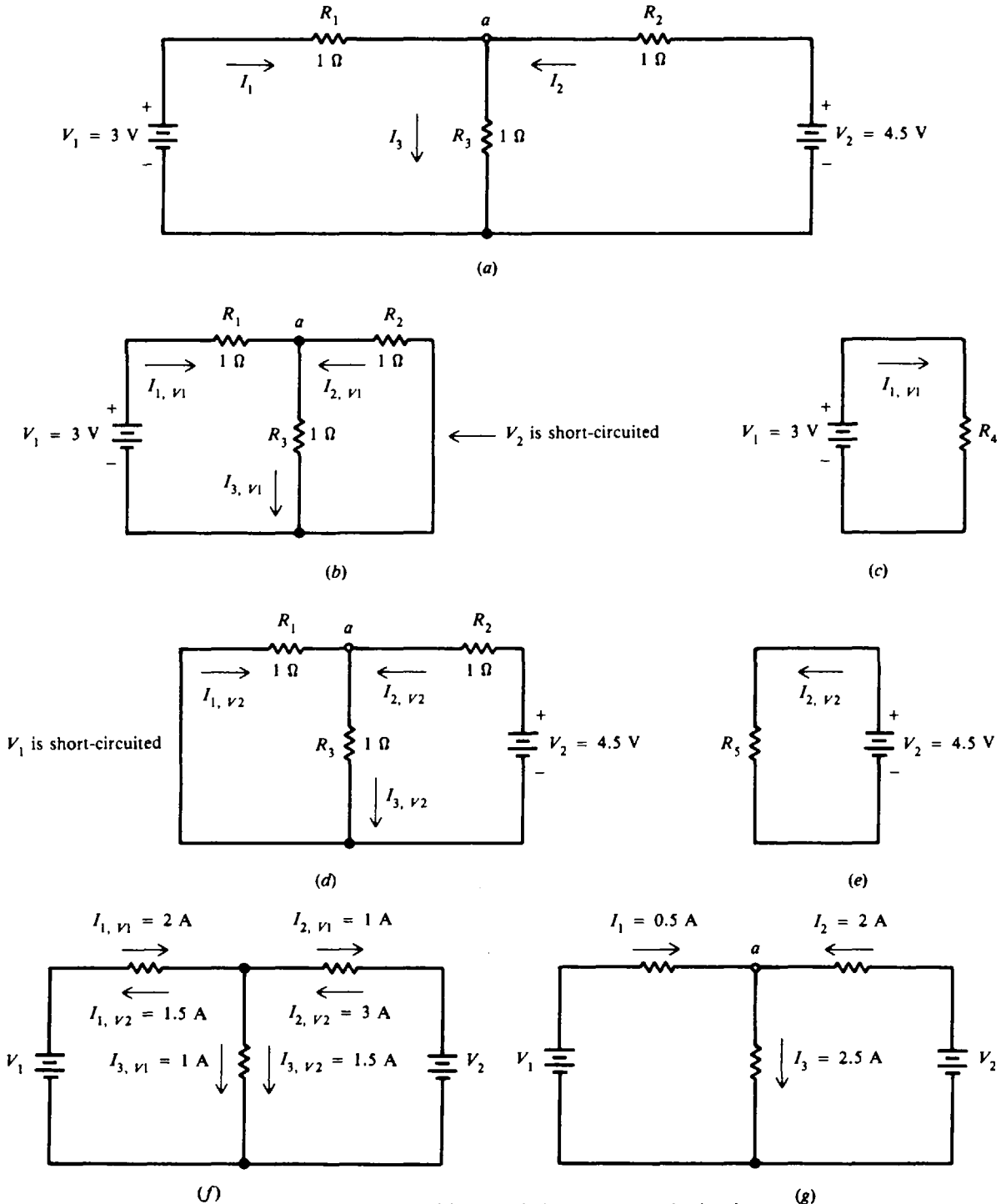


Fig. 8-6 Superposition applied to a two-mesh circuit

The negative sign is used to show that  $I_{2, v1}$  actually leaves point  $a$  rather than enters point  $a$  as assumed.

**Step 2.** Find the currents produced by voltage source  $V_2$  only.

- (a) Replace voltage source  $V_1$  with a short circuit (Fig. 8-6d). Use a subscript  $V_2$  after a comma to indicate that only source  $V_2$  is supplying the circuit. For example,  $I_1, V_2$  is current  $I_1$  due only to source  $V_2$ .

- (b) Reduce the circuit to a single source and a single resistance (Fig. 8-6e). Solve for currents produced by  $V_2$ .

$$R_5 = R_2 + \frac{R_1 R_3}{R_1 + R_3} = 1 + \frac{1(1)}{1+1} = 1 + 0.5 = 1.5 \Omega$$

$$I_{2, v_2} = \frac{V_2}{R_5} = \frac{4.5}{1.5} = 3 \text{ A}$$

$I_{2, v_2}$  will divide symmetrically at point  $a$  (Fig. 8-6d) so that

$$I_{3, v_2} = \frac{1}{2} I_{2, v_2} = \frac{1}{2} 3 = 1.5 \text{ A}$$

$$I_{1, v_2} = -\frac{1}{2} I_{2, v_2} = -\frac{1}{2} 3 = -1.5 \text{ A}$$

The negative sign shows that  $I_{1, v_2}$  actually leaves point  $a$  and does not enter point  $a$  as assumed.

- Step 3.** Add algebraically the individual currents to find the currents produced by both  $V_1$  and  $V_2$  (Figs. 8-6f and g).


$$I_1 = I_{1, v_1} + I_{1, v_2} = 2 - 1.5 = 0.5 \text{ A} \quad \text{Ans.}$$

$$I_2 = I_{2, v_1} + I_{2, v_2} = -1 + 3 = 2 \text{ A} \quad \text{Ans.}$$

$$I_3 = I_{3, v_1} + I_{3, v_2} = 1 + 1.5 = 2.5 \text{ A} \quad \text{Ans.}$$

## THEVENIN'S THEOREM

Thevenin's theorem is a method used to change a complex circuit into a simple equivalent circuit. Thevenin's theorem states that any linear network of voltage sources and resistances, if viewed from any two points in the network, can be replaced by an equivalent resistance  $R_{Th}$  in series with an equivalent source  $V_{Th}$ . Figure 8-7a shows the original linear network with terminals  $a$  and  $b$ ; Fig. 8-7b shows its connection to an external network or load; and Fig. 8-7c shows the Thevenin equivalent  $V_{Th}$  and  $R_{Th}$  that can be substituted for the linear network at the terminals  $a$  and  $b$ . The polarity of  $V_{Th}$  is such that it will produce current from  $a$  to  $b$  in the same direction as in the original network.  $R_{Th}$  is the Thevenin resistance across the network terminals  $a$  and  $b$  with each internal voltage source short-circuited.  $V_{Th}$  is the Thevenin voltage that would appear across the terminals  $a$  and  $b$  with the voltage sources in place and no load connected across  $a$  and  $b$ . For this reason,  $V_{Th}$  is also called the open-circuit voltage.

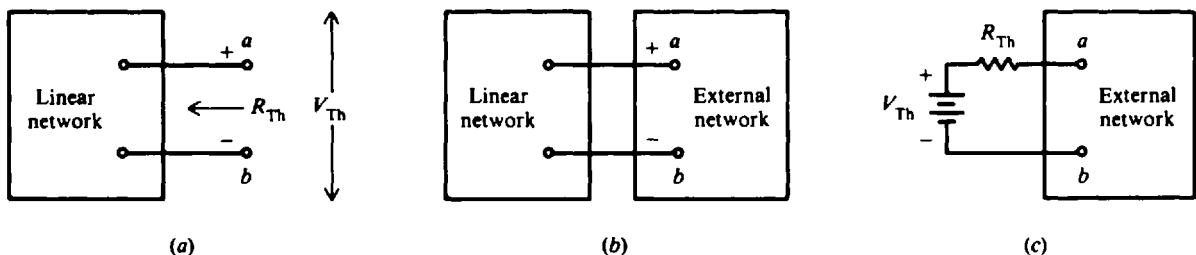


**Fig. 8-7** Thevenin equivalent,  $V_{Th}$ , and series  $R_{Th}$

**Example 8.5** Find the Thevenin equivalent to the circuit at terminals  $a$  and  $b$  (Fig. 8-8a).

- Step 1.** Find  $R_{Th}$ . Short-circuit the voltage source  $V = 10 \text{ V}$  (Fig. 8-8b).  $R_1$  and  $R_2$  are in parallel.

$$R_{Th} = \frac{R_1 R_2}{R_1 + R_2} = \frac{4(6)}{4+6} = \frac{20}{10} = 2.4 \Omega \quad \text{Ans.}$$

- Step 2.** Find  $V_{Th}$ .  $V_{Th}$  is the voltage across terminals  $a$  and  $b$ , which is the same as the voltage drop across resistance  $R_2$ .

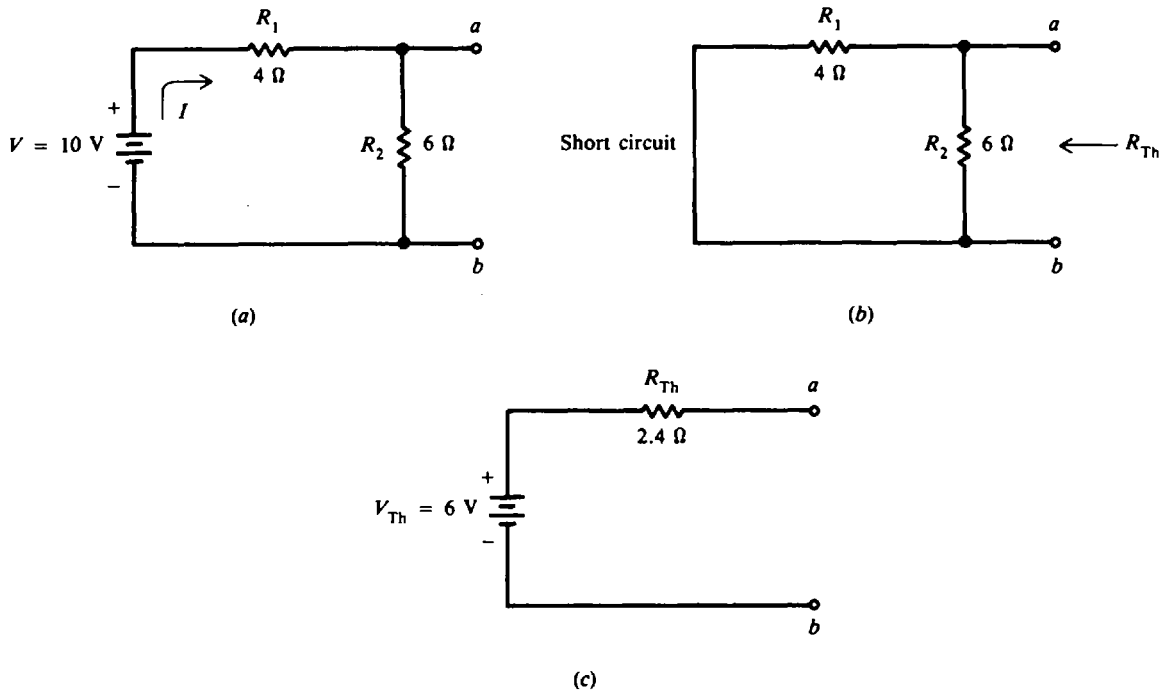

**Fig. 8-8** Thevenin equivalent without load

$$I = \frac{V}{R_1 + R_2} = \frac{10}{4 + 6} = \frac{10}{10} = 1 \text{ A}$$

$$V_{Th} = V_2 = IR_2$$

Then  $V_{Th} = 1(6) = 6 \text{ V}$       **Ans.**

The Thevenin equivalent is then as in Fig. 8-8c.


**Example 8.6** To the circuit in Fig. 8-8a, add a resistor load  $R_L$  of  $3.6 \Omega$  and find the current  $I_L$  through the load and voltage  $V_L$  across the load.

The new circuit is as shown in Fig. 8-9a and with the Thevenin equivalent is as shown in Fig. 8-9b.

$$I_L = \frac{V_{Th}}{R_{Th} + R_L} = \frac{6}{2.4 + 3.6} = \frac{6}{6} = 1 \text{ A} \quad \text{Ans.}$$

$$V_L = I_L R_L = 1(3.6) = 3.6 \text{ V} \quad \text{Ans.}$$

Note how the Thevenin equivalent has simplified the solution of the given two-mesh network. Further, if the load  $R_L$  were changed, we would not have to recalculate the entire network.

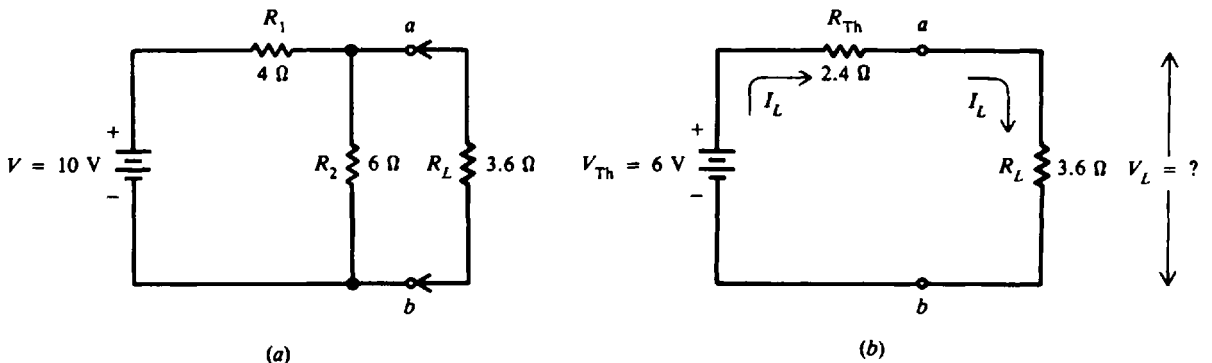

**Fig. 8-9** Thevenin equivalent with load

**NORTON'S THEOREM**

Norton's theorem is used to simplify a network in terms of currents instead of voltages. For current analysis, this theorem can be used to reduce a network to a simple parallel circuit with a current source, which supplies a total line current that can be divided among parallel branches.

If the current  $I$  (Fig. 8-10) is a 4-A source, it supplies 4 A no matter what is connected across the output terminals  $a$  and  $b$ . With nothing connected across  $a$  and  $b$ , all the 4 A flows through shunt  $R$ . When a load resistance  $R_L$  is connected across  $a$  and  $b$ , then the 4-A current divides according to the current-division rule for parallel branches.


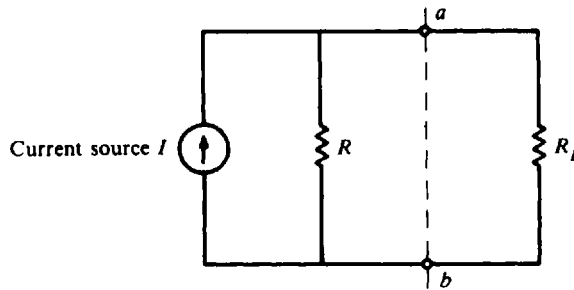



Fig. 8-10  $I$  source with parallel  $R$

The symbol for a current source is a circle with an arrow inside (Fig. 8-10) to show the direction of current. This direction must be the same as the current produced by the polarity of the corresponding voltage source. Remember that a source produces current flow out from the positive terminal.

Norton's theorem states that any network connected to terminals  $a$  and  $b$  [Fig. 8-11a(1)] can be replaced by a single current source  $I_N$  in parallel with a single resistance  $R_N$  [Fig. 8-11a(2)].  $I_N$  is equal to the short-circuit current through the  $ab$  terminals (the current that the network would produce through  $a$  and  $b$  with a short circuit across these two terminals).  $R_N$  is the resistance at terminals  $a$  and  $b$ , looking back from the open  $ab$  terminals. The value of the single resistor is the same for both the Norton and Thevenin equivalent circuits.

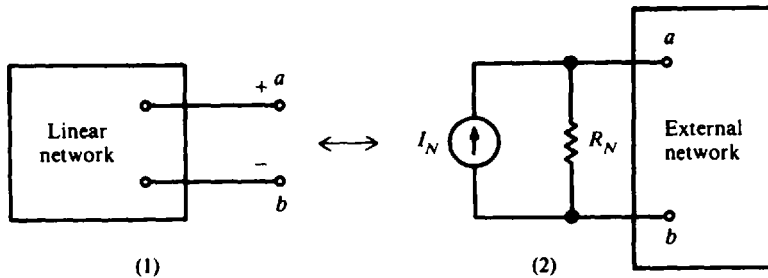

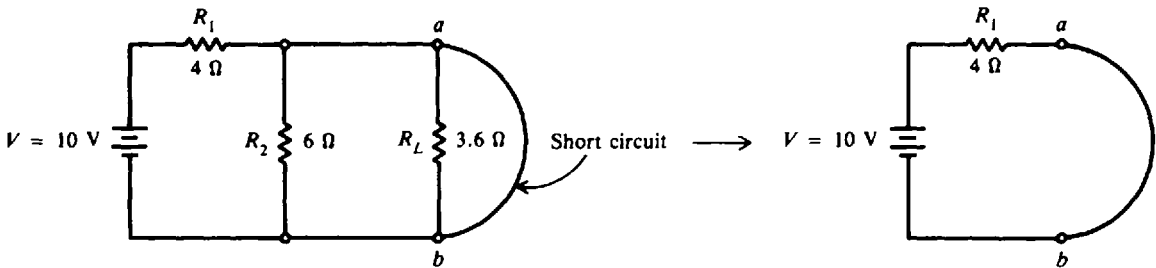(a) Norton equivalent,  $I_N$  and parallel  $R_N$



(b)

Fig. 8-11a, b

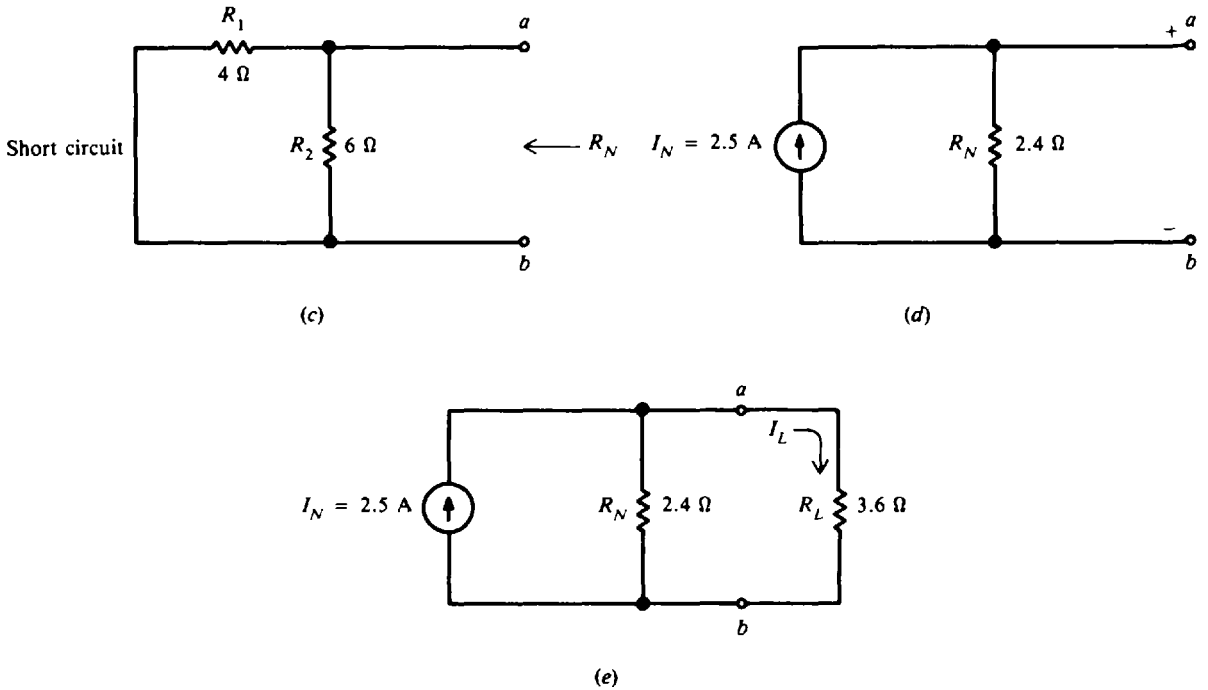


Fig. 8-11c, d, e

**Example 8.7** Calculate the current  $I_L$  (see Fig. 8-9a) by Norton's theorem. (This was solved in Example 8.6 by Thevenin's theorem.)

**Step 1.** Find  $I_N$ . Short-circuit across  $ab$  terminals (Fig. 8-11b). A short circuit across  $ab$  short-circuits  $R_L$  and the parallel  $R_2$ . Then the only resistance in the circuit is  $R_1$  in series with source  $V$ .

$$I_N = \frac{V}{R_1} = \frac{10}{4} = 2.5\ \text{A}$$

**Step 2.** Find  $R_N$ . Open terminals  $ab$  and short-circuit  $V$  (Fig. 8-11c).  $R_1$  and  $R_2$  are in parallel, so

$$R_N = \frac{4(6)}{4 + 6} = \frac{24}{10} = 2.4\ \Omega$$

Note that  $R_N$  is the same as  $R_{Th}$ .

The Norton equivalent is then as in Fig. 8-11d. The arrow on the current source shows the direction of conventional current from terminal  $a$  to terminal  $b$ , as in the original circuit.

**Step 3.** Find  $I_L$ . Reconnect  $R_L$  to  $ab$  terminals (Fig. 8-11e). The current source still delivers 2.5 A, but now the current divides between the two branches  $R_N$  and  $R_L$ .

$$I_L = \frac{R_N}{R_N + R_L} I_N = \frac{2.4}{2.4 + 3.6} 2.5 = \frac{2.4}{6} 2.5 = 1\ \text{A} \quad \text{Ans.}$$

This value is the same load current calculated in Example 8.6. Also,  $V_L$  can be calculated as  $I_L R_L$ , or  $(1\ \text{A})(3.6\ \Omega) = 3.6\ \text{V}$ .

We therefore see that the Thevenin equivalent circuit (Fig. 8-12a) corresponds to the Norton equivalent circuit (Fig. 8-12b). So a general voltage source with a series resistance (Fig. 8-12a) can be converted to an equivalent current source with the same resistance in parallel (Fig. 8-12b). Divide the general source  $V$  by its series resistance  $R$  to find the value of  $I$  for the equivalent current source shunted by the same resistance  $R$ ; that is,  $I_N = V_{Th}/R_{Th}$ .



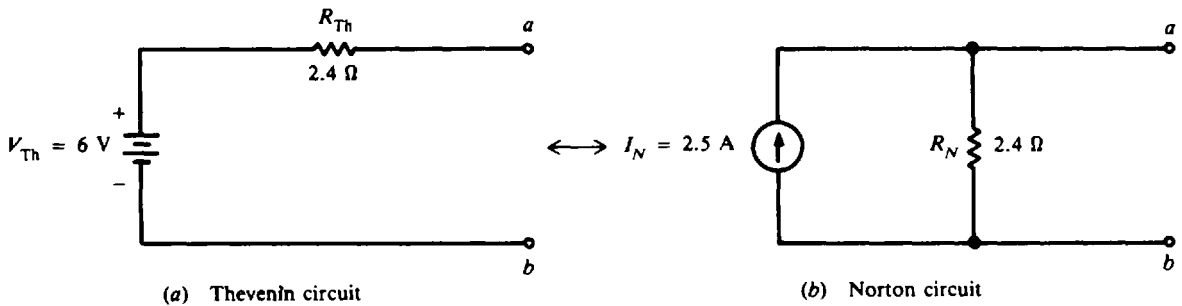


Fig. 8-12 Equivalent circuits

**SERIES-PARALLEL CIRCUITS**

Many circuits consist of a combination of series and parallel circuits. These combination circuits are called *series-parallel circuits*. An example of a series-parallel circuit is shown in Fig. 8-13, where two parallel resistors  $R_2$  and  $R_3$  are connected in series with the resistor  $R_1$  and the voltage source  $V$ . In a circuit of this type, the current  $I_T$  divides after it flows through  $R_1$ , and part flows through  $R_2$  and part flows through  $R_3$ . Then the current joins at the junction of the two resistors and flows back to the negative terminal of the voltage source and through the voltage source to the positive terminal.

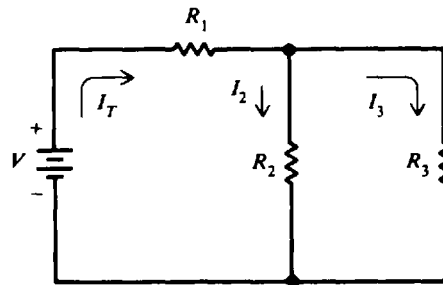


Fig. 8-13 A series-parallel circuit

In solving for values of current, voltage, and resistance in a series-parallel circuit, follow the rules that apply to a series circuit for the series part of the circuit, and follow the rules that apply to a parallel circuit for the parallel part of the circuit. Solving series-parallel circuits is simplified if all parallel and series groups are first reduced to single equivalent resistances and the circuits redrawn in simplified form. The redrawn circuit is called an *equivalent circuit*.

There are no general formulas for the solution of series-parallel circuits because there are so many different forms of these circuits.

**Example 8.6** Find the total resistance, total circuit current, and branch currents of the circuit shown in Fig. 8-14a.

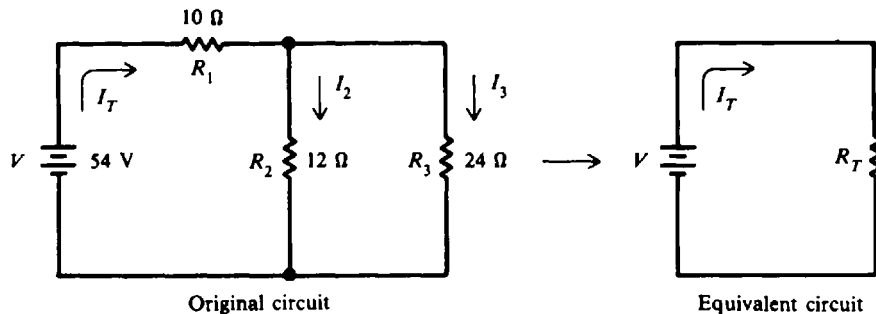


Fig. 8-14a

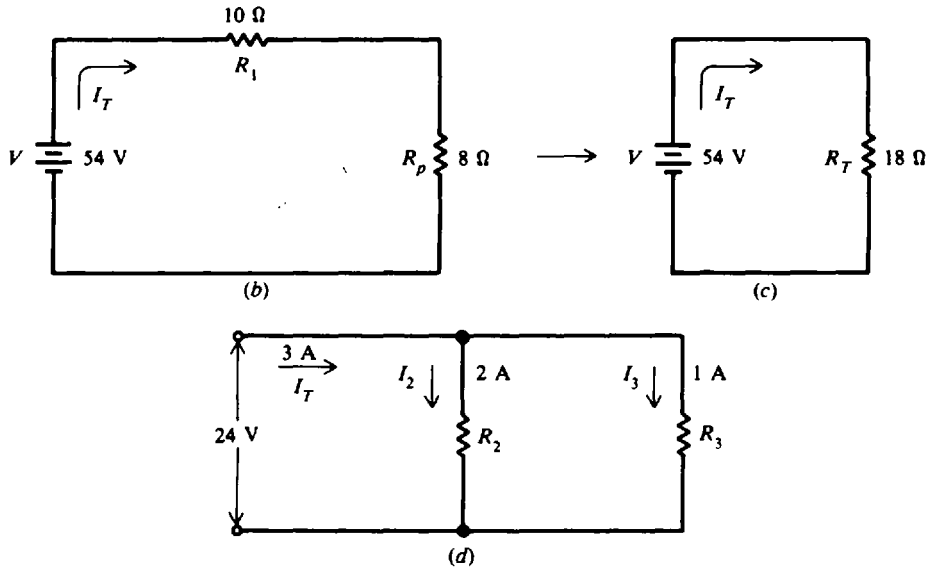


Fig. 8-14b, c, d

It is best to solve combination circuits in steps:

**Step 1.** Find the equivalent resistance of the parallel branch.

$$R_p = \frac{R_2 R_3}{R_2 + R_3} = \frac{12(24)}{12 + 24} = \frac{288}{36} = 8 \Omega$$

The equivalent circuit reduces to a series circuit (Fig. 8-14b).

**Step 2.** Find the resistance of the equivalent series circuit.

$$R_T = R_1 + R_p = 10 + 8 = 18 \Omega \quad \text{Ans.}$$

The equivalent circuit reduces to a single voltage source and a single resistance (Fig. 8-14c).

**Step 3.** Find  $I_T$ . ( $I_T$  is the actual current being supplied in the original series-parallel circuit.)

$$I_T = \frac{V}{R_T} = \frac{54}{18} = 3 \text{ A} \quad \text{Ans.}$$

**Step 4.** Find  $I_2$  and  $I_3$ . The voltage across  $R_2$  and  $R_3$  is equal to the applied voltage  $V$  less the voltage drop across  $R_1$ . See Fig. 8-14d.

$$V_2 = V_3 = V - I_T R_1 = 54 - (3 \times 10) = 24 \text{ V}$$

Then

$$I_2 = \frac{V_2}{R_2} = \frac{24}{12} = 2 \text{ A} \quad \text{Ans.}$$

$$I_3 = \frac{V_3}{R_3} = \frac{24}{24} = 1 \text{ A} \quad \text{Ans.}$$

or, by KCL,

$$I_T = I_1 = I_2 + I_3$$

$$I_3 = I_T - I_2 = 3 - 2 = 1 \text{ A}$$

**Example 8.9** Find the total resistance  $R_T$  (Fig. 8-15a).

**Step 1.** Add series resistances in each branch (Fig. 8-15b).

Branch *ab*:  $R_1 + R_2 = 5 + 10 = 15 \Omega$

Branch *cd*:  $R_3 + R_4 = 6 + 9 = 15 \Omega$

Branch *ef*:  $R_5 + R_6 + R_7 = 8 + 5 + 2 = 15 \Omega$

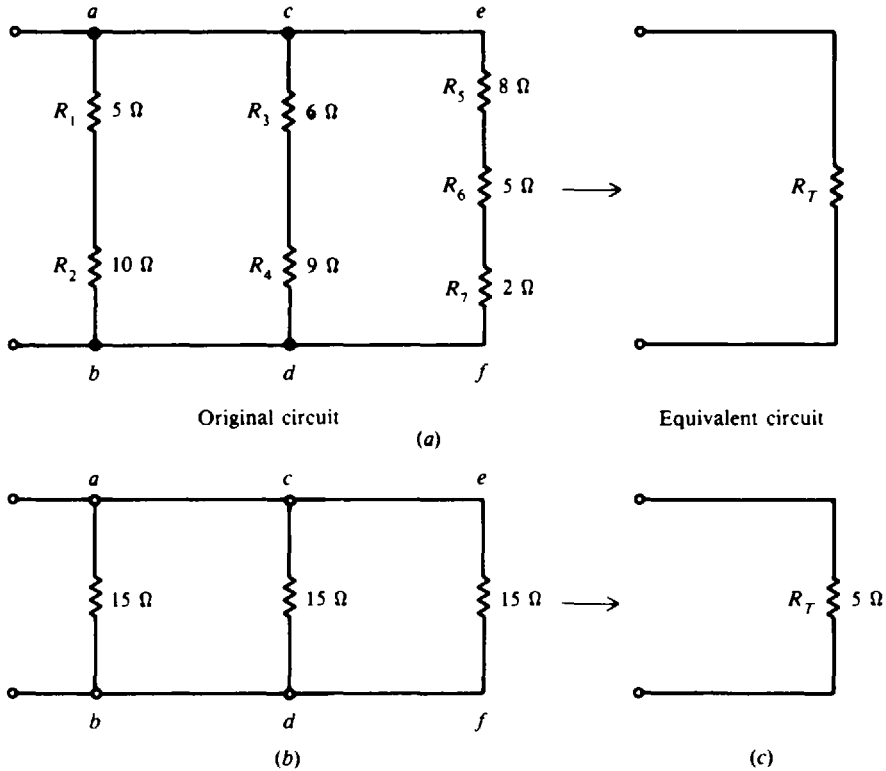


Fig. 8-15

**Step 2.** Find  $R_T$ . Each of three parallel resistors is  $15\ \Omega$ . See Fig. 8-15c.

$$R_T = \frac{R}{N} = \frac{15}{3} = 5\ \Omega \quad \text{Ans.}$$

**WHEATSTONE BRIDGE CIRCUIT**

The Wheatstone bridge (Fig. 8-16) can be used to measure an unknown resistance  $R_x$ . Switch  $S_2$  applies battery voltage to the four resistors in the bridge. To balance the bridge, the value of  $R_3$  is varied. Balance is indicated by zero current in galvanometer  $G$  when switch  $S_1$  is closed.

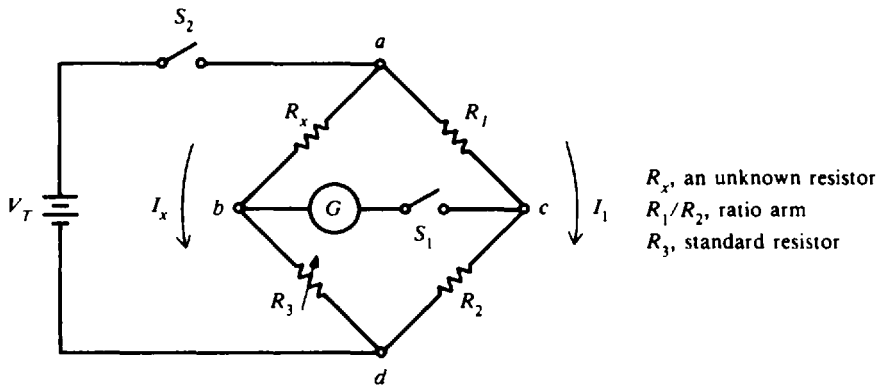


Fig. 8-16 Wheatstone bridge

When the bridge is balanced, points  $b$  and  $c$  must be at the same potential. Therefore

$$I_x R_x = I_1 R_1 \tag{1}$$

$$I_x R_3 = I_1 R_2 \tag{2}$$

Divide Eqs. (1) and (2). Note that  $I_x$  and  $I_1$  cancel.

$$\frac{I_x R_x}{I_x R_3} = \frac{I_1 R_1}{I_1 R_2}$$

$$\frac{R_x}{R_3} = \frac{R_1}{R_2}$$

Solve for  $R_x$ .

$$R_x = \frac{R_1}{R_2} R_3 \tag{8-7}$$

The ratio arm of the bridge is  $R_1/R_2$ . A rotary switching arrangement is used often in commercial bridges to adjust the ratio arm over a wide range of ratios. The bridge is balanced by varying  $R_3$  for zero current in the meter. A decade box, where resistance can be varied in small ohmic steps up to as high as 10 K $\Omega$ , is commonly used as  $R_3$ . The value of  $R_x$  can be read directly from the calibrated scale of the rheostat when  $R_3$  is adjusted for balance.

When current flows through the meter path  $bc$ , the bridge circuit is unbalanced and must be analyzed by Kirchhoff's laws or network theorems.

**Example 8.10** An unknown resistance is to be measured by the Wheatstone bridge. If the ratio of  $R_1/R_2$  is 1/100 and  $R_3$  is 352  $\Omega$  when the bridge is balanced, find the value of the unknown resistance.

Substitute known values into Eq. (8-7).

$$R_x = \frac{R_1}{R_2} R_3 = \frac{1}{100} 352 = 3.52 \Omega \quad \text{Ans.}$$

**MAXIMUM POWER TRANSFER**

The maximum power is supplied by the voltage source and received by the load resistor if the value of the load resistor equals the value of the internal resistance of the voltage source (Fig. 8-17). For maximum power transfer, then

$$R_L = R_i$$

and power received at the load is

$$P_L = I^2 R_L \quad \text{where} \quad I = \frac{V}{R_i + R_L}$$

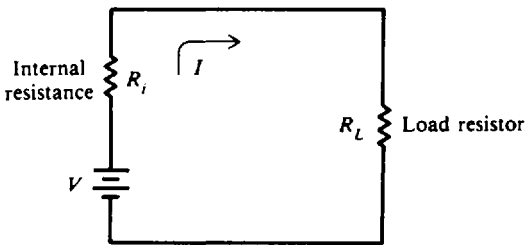


Fig. 8-17

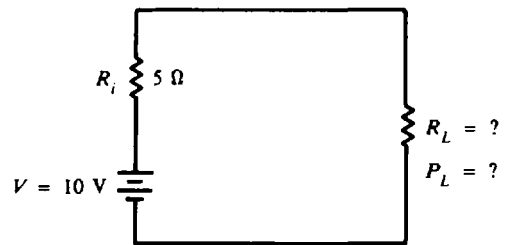


Fig. 8-18

**Example 8.11** If a 10-V battery has an internal resistance of  $R_i = 5 \Omega$ , what is the maximum power that can be delivered to the load resistor (Fig. 8-18)?

For maximum power transfer,

$$R_L = R_i = 5 \Omega$$

$$I = \frac{V}{R_i + R_L} = \frac{10}{5 + 5} = \frac{10}{10} = 1 \text{ A}$$

$$P_L = I^2 R_L = 1^2(5) = 5 \text{ W} \quad \text{Ans.}$$

**Example 8.12** For Example 8.11 prepare a table of values of power delivered to the load when the load resistance  $R_L$  is 1  $\Omega$ , 3  $\Omega$ , 4  $\Omega$ , 5  $\Omega$ , 6  $\Omega$ , 7  $\Omega$ , and 10  $\Omega$ .

Power Delivered to  $R_L$

$R_L, \Omega$	$R_i, \Omega$	$I = \frac{V}{R_i + R_L}, \text{ A}$	$P_L = I^2 R_L, \text{ W}$
1	5	1.67	2.79
3	5	1.25	4.69
4	5	1.11	4.93
5	5	1.00	5.00 (max. power)
6	5	0.91	4.97
7	5	0.83	4.82
10	5	0.67	4.49

Notice that when  $R_L = R_i = 5 \Omega$ , the maximum power of 5 W is transferred to the load.

### LINE-DROP CALCULATIONS

The connecting wires are generally very short in electric circuits. Because the resistance of these short lengths is low, it was neglected in previous calculations. However, in home and factory electrical installations, where long lines of wires or feeders are used, the resistance of these long lengths must be included in all calculations.

The voltage drop across the resistance of the line wires is called the *line drop*. For example, if a generator delivers 120 V but the voltage available at a motor some distance away is only 117 V, then there has been a line drop in voltage of 3 V.

We must be careful about specifying the kind and size of wires used in any installation. If the wires are incorrectly chosen, then the line drop may be too large so that the voltage available to an electrical apparatus will be too low for proper operation (refer to the section on wire measurement in Chap. 4).

**Example 8.13** A lamp bank consisting of three lamps, each drawing 1.5 A, is connected to a 120-V source (Fig. 8-19). Each line wire has a resistance of 0.25  $\Omega$ . Find the line drop, line power loss, and voltage available at the load.

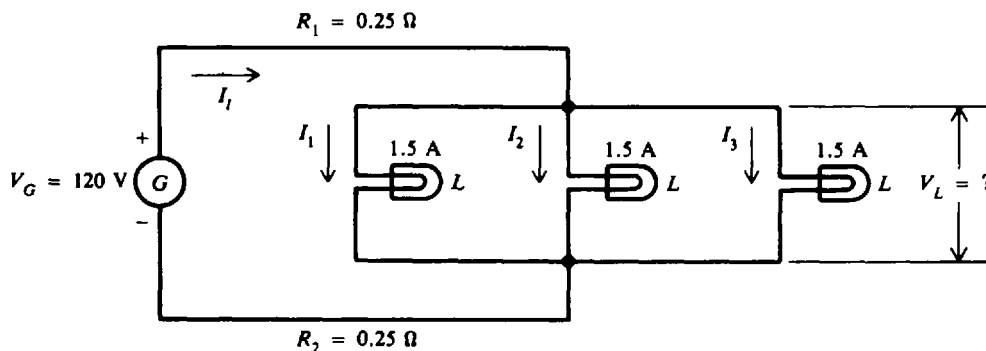


Fig. 8-19

**Step 1.** Find the line current  $I_1$ .

$$I_1 = I_1 + I_2 + I_3 = 1.5 + 1.5 + 1.5 + = 4.5 \text{ A}$$

**Step 2.** Find the resistance of the line wires  $R_l$ . Since the line wires are in series,

$$R_l = R_1 + R_2 = 0.25 + 0.25 = 0.5 \Omega$$

**Step 3.** Find the line drop by Ohm's law.

$$V_l = I_l R_l = 4.5(0.5) = 2.25 \text{ V} \quad \text{Ans.}$$

**Step 4.** Find the line power loss.

$$P_l = I_l^2 R_l = (4.5)^2(0.5) = 10.1 \text{ W} \quad \text{Ans.}$$

**Step 5.** Find voltage available at load.

$$V_L = V_G - V_l = 120 - 2.25 = 117.75 = 117.8 \text{ V} \quad \text{Ans.}$$

**Example 8.14** A bank of lathes is operated by individual motors in a machine shop (Fig. 8-20). The motors draw a total of 60 A at 110 V from the distributing panel box. What is the smallest size copper wire required for the two-wire line between the panel box and the switchboard, located 100 ft away, if the switchboard voltage is 115 V?

**Step 1.** Find the line drop between the switchboard and the panel box.

$$V_l = V_G - V_L = 115 - 110 = 5 \text{ V}$$

**Step 2.** Find the line resistance  $R_l$  for this drop.

$$V_l = I_l R_l$$

$$R_l = \frac{V_l}{I_l} = \frac{5}{60} = 0.0833 \Omega$$

**Step 3.** Find the circular-mil area of the wire that has this resistance. Since there are two wires,  $l = 2L = 2(100) = 200$  ft. Use resistivity formula to solve for area  $A$  of wire.

$$R_l = \rho \frac{l}{A} \tag{4-5}$$

$$A = \frac{\rho l}{R_l}$$

$$\rho = 10.4 \quad (\text{from Table 4-2}) \quad l = 200 \text{ ft} \quad R_l = 0.0833 \Omega$$

$$A = \frac{10.4(200)}{0.0833} = 25\,000 \text{ CM}$$

**Step 4.** Find the gauge number of the wire whose circular-mil area is larger than 25 000 CM. Refer to Table 4-1. Read down column 3, circular-mil area, until you get to a number just larger than 25 000 CM. The number is 26 250 CM. Read left to column 1 to find gauge No. 6. *Ans.*

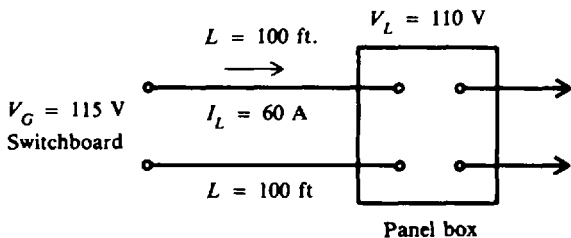


Fig. 8-20

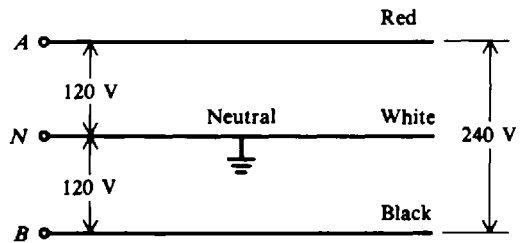


Fig. 8-21 Three-wire distribution system

**THREE-WIRE DISTRIBUTION SYSTEMS**

The basic circuit described so far has been a two-wire circuit to a lamp, motor, or other load device. The basic two-wire circuit uses 120 V to supply the many household and factory load devices designed for that voltage. The three-wire circuit was developed to reduce the problems of

voltage drop and power loss in the lines while still providing 120-V supply. The three wires of Fig. 8-21, including the grounded neutral, can be used for either 240 or 120 V. From either red or black high side to neutral, 120 V is available for separate branch circuits to the lights and outlets. Across the red and black wires, 240 V is available for high-power appliances such as a freezer or automatic clothes dryer. This 120/240-V three-wire distribution with a grounded neutral is called the *Edison system*.

### The Edison System with Two Voltage Sources

This system (Fig. 8-22) has two direct-current generators,  $G_A$  and  $G_B$ , with load voltages  $V_{L1}$  and  $V_{L2}$ .  $R_1$ ,  $R_2$ , and  $R_3$  are the resistances of the line wires between the generators and the load.  $R_{L1}$  and  $R_{L2}$  are the load resistances.  $I_1$ ,  $I_2$ , and  $I_3$  are the currents in the line wires.

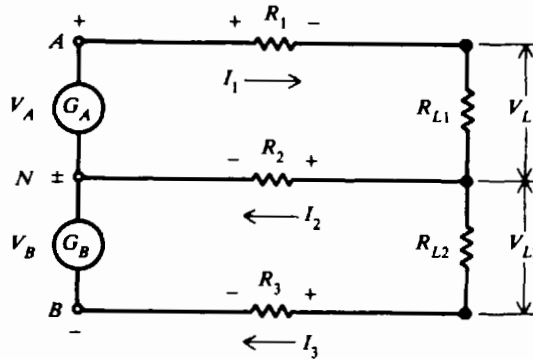


Fig. 8-22 Three-wire system with two voltage sources

$I_1$  and  $I_3$  will always flow in the direction indicated.  $I_2$  may flow in either direction. The actual direction of flow will be determined by the sign of  $I_2$ . A + sign for  $I_2$  means that it actually flows in the direction indicated, while a - sign means  $I_2$  flows in the reverse direction.

By KCL and KVL, we can write

$$I_3 = I_1 - I_2 \quad (1)$$

$$V_A - I_1 R_1 - I_1 R_{L1} - I_2 R_2 = 0 \quad (2)$$

$$V_B + I_2 R_2 - I_3 R_{L2} - I_3 R_3 = 0 \quad (3)$$

If the three wires are equal in size, as they usually are, their resistances are equal. So  $R = R_1 = R_2 = R_3$ .

Equations (1), (2), and (3) can be solved to find the line currents.

$$I_1 = \frac{R V_B + V_A (2R + R_{L2})}{(R + R_{L1})(2R + R_{L2}) + R(R_{L2} + R)} \quad (8-8)$$

$$I_2 = \frac{I_1 (R_{L2} + R) - V_B}{2R + R_{L2}} \quad (8-9)$$

$$I_3 = I_1 - I_2 \quad (8-10)$$

**Example 8.15** A three-wire 240/120-V circuit has line resistances of  $0.5 \Omega$  per line and load resistors  $R_{L1} = 10 \Omega$  and  $R_{L2} = 5 \Omega$  (Fig. 8-23).  $V_A$  and  $V_B$  are 120 V each. Find the currents and voltages at the loads.

**Step 1.** Solve for  $I_1$ ,  $I_2$ , and  $I_3$ . Substitute known values into the line current equations.

$$I_1 = \frac{R V_B + V_A (2R + R_{L2})}{(R + R_{L1})(2R + R_{L2}) + R(R_{L2} + R)} \quad (8-8)$$

$$= \frac{0.5(120) + 120(1.0 + 5)}{(0.5 + 10)(1.0 + 5) + 0.5(5 + 0.5)} = \frac{60 + 720}{63 + 2.75} = \frac{780}{65.75} = 11.9 \text{ A} \quad \text{Ans.}$$

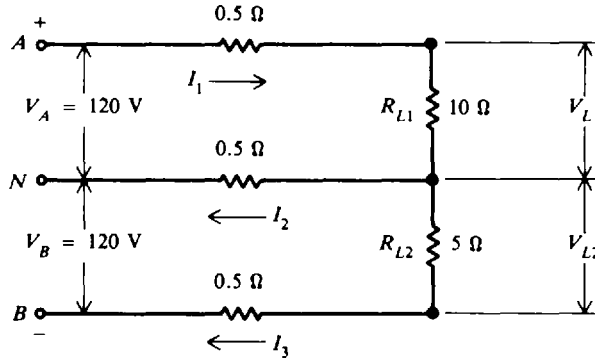


Fig. 8-23

$$I_2 = \frac{I_1(R_{L2} + R) - V_B}{2R + R_{L2}} \tag{8-9}$$

$$= \frac{11.9(5 + 0.5) - 120}{1.0 + 5} = \frac{-54.55}{6} = -9.1 \text{ A} \quad \text{Ans.}$$

$I_2$  is thus flowing in opposite direction to that shown (Fig. 8-23).

$$I_3 = I_1 - I_2 \tag{8-10}$$

$$I_3 = 11.9 - (-9.1) = 11.9 + 9.1 = 21 \text{ A} \quad \text{Ans.}$$

Note that because  $I_3$  has the higher current, the heavier load is connected between the negative (lower) line and the neutral, and the neutral carries current away from the generator. If the 120-V loads were balanced on each side of the neutral ( $R_{L1} = R_{L2}$ ), the neutral would carry no current ( $I_2 = 0$ ).

**Step 2.** Find voltages across the loads by Ohm's law.

$$V_{L1} = I_1 R_{L1} = 11.9(10) = 119 \text{ V} \quad \text{Ans.}$$

$$V_{L2} = I_3 R_{L2} = 21(5) = 105 \text{ V} \quad \text{Ans.}$$

**Example 8.16** Assume that the fuse in the neutral line is blown, opening the neutral line in Fig. 8-23. What now are the voltages across the two loads?

The connection is now reduced to a two-wire circuit (Fig. 8-24). By Ohm's law,

$$I = \frac{240}{0.5 + 10 + 5 + 0.5} = \frac{240}{16} = 15 \text{ A}$$

$$V_{L1} = IR_{L1} = 15(10) = 150 \text{ V} \quad \text{Ans.}$$

$$V_{L2} = IR_{L2} = 15(5) = 75 \text{ V} \quad \text{Ans.}$$

The high voltage of 150 V across the 10 Ω load resistor could destroy the equipment connected at that point in the circuit. If the load were lights, the light bulbs would burn out fairly quickly with a 31-V overage ( $150 - 119 = 31$ ). For this reason, the neutral wire must not contain a fuse for protection of the circuit. Generally, electrical codes forbid fuses in the neutral line.

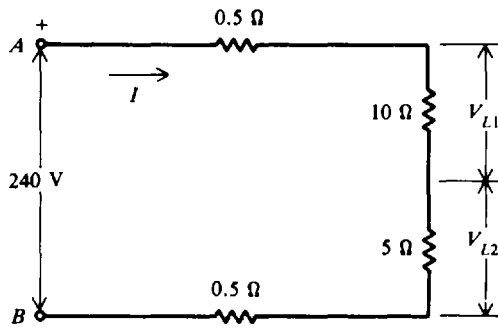


Fig. 8-24



### Solved Problems

- 8.1** Reduce the bridge circuit (Fig. 8-25a) to a single equivalent input resistance at terminals *a* and *d*.

**Step 1.** Convert Y network *bcd* to its equivalent  $\Delta$  network. Use Rule 2 and visual aid. (See Fig. 8-25b.)

$$R_1 = \frac{10(10) + 10(10) + 10(10)}{10} = \frac{300}{10} = 30 \Omega$$

$$R_2 = \frac{300}{10} = 30 \Omega$$

$$R_3 = \frac{300}{10} = 30 \Omega$$

**Step 2.** Redraw Y as its  $\Delta$  equivalent and connect it to the rest of the original circuit. (See Fig. 8-25c.)

**Step 3.** Reduce the circuit. The two 10- and 30- $\Omega$  branches are in parallel. (See Fig. 8-25d.)

$$R_p = \frac{10(30)}{10 + 30} = \frac{300}{40} = 7.5 \Omega$$

$$R_q = \frac{10(30)}{10 + 30} = \frac{300}{40} = 7.5 \Omega$$

$$R_r = \frac{30(15)}{30 + 15} = \frac{450}{45} = 10 \Omega$$

$$R_T = 10 + 10 = 20 \Omega \quad \text{Ans.}$$

- 8.2** Find the equivalent resistance  $R_T$  and output voltage  $V_o$  of a network with a bridged T form (Fig. 8-26a).

**Step 1.** Transform the T (or Y) network into its equivalent  $\Delta$ . Use the rule for Y to  $\Delta$  conversion (Fig. 8-26b).

$$R_1 = \frac{2(2) + 2(2) + 2(2)}{2} = \frac{12}{2} = 6 \Omega$$

$$R_2 = \frac{12}{2} = 6 \Omega$$

$$R_3 = \frac{12}{2} = 6 \Omega$$





**Step 2.** Redraw T as its  $\Delta$  equivalent and connect it to the remainder of the original circuit (Fig. 8-26c).

**Step 3.** Redraw the circuit to show more clearly the two parallel branches, each containing two 6- $\Omega$  resistances. Then reduce the circuit until you get a single equivalent resistance  $R_T$  (Fig. 8-26d and e). Two 6- $\Omega$  resistances in parallel are equal to  $6/2 = 3 \Omega$ .







$$R_T = \frac{6}{2} = 3 \Omega \quad \text{Ans.}$$

**Step 4.** Solve for  $V$  by voltage distribution of 10 V. Look at circuit (3) in Fig. 8-26d. By the voltage-division rule,
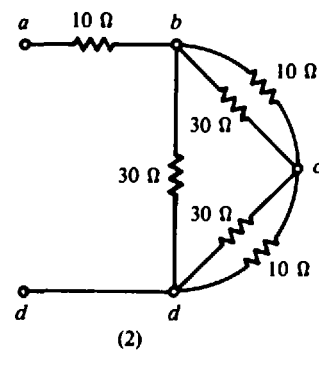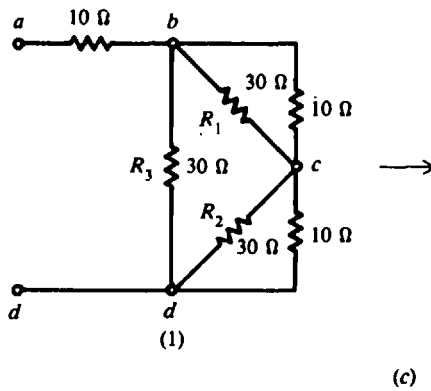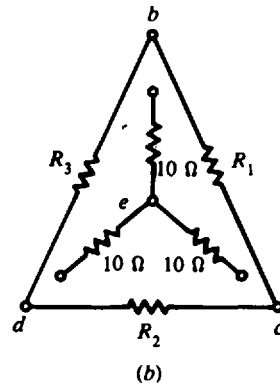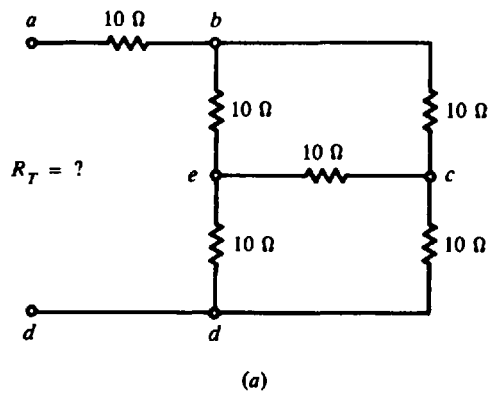
$$V_o = (\text{resistance ratio})(V_{ad}) = \left(\frac{3 \Omega}{3 \Omega + 3 \Omega}\right)(10 \text{ V}) = \frac{3}{6} 10 = 5 \text{ V} \quad \text{Ans.}$$



(c)

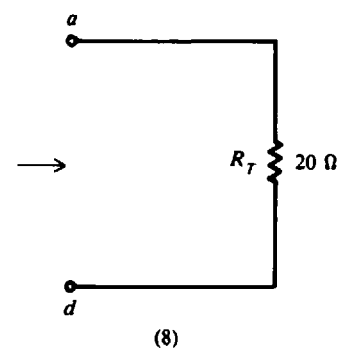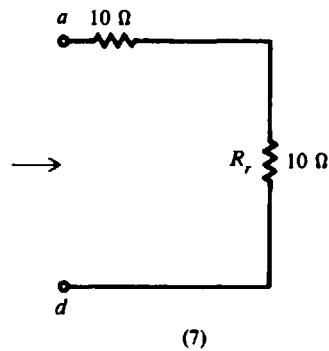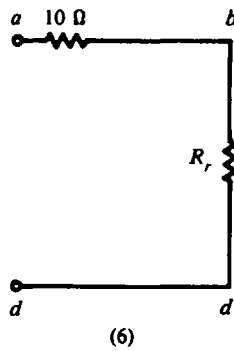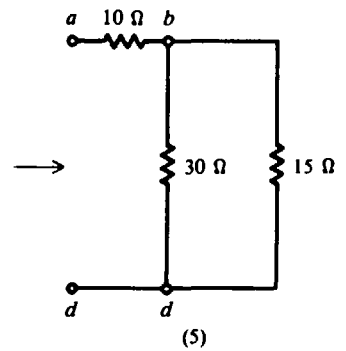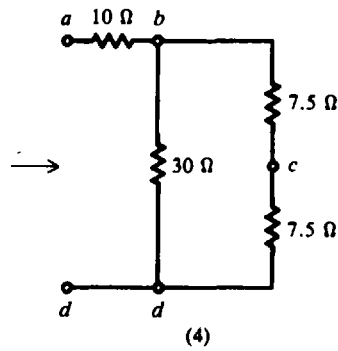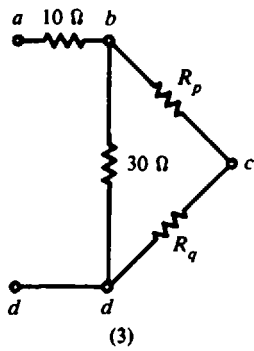

(d)

Fig. 8-25


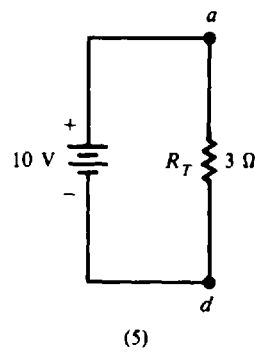
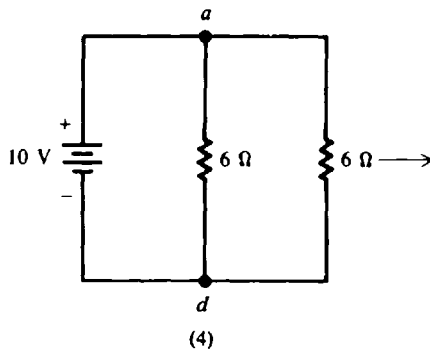
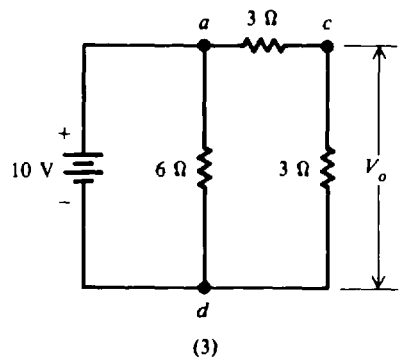
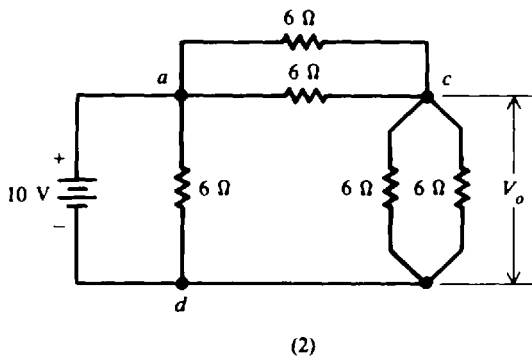
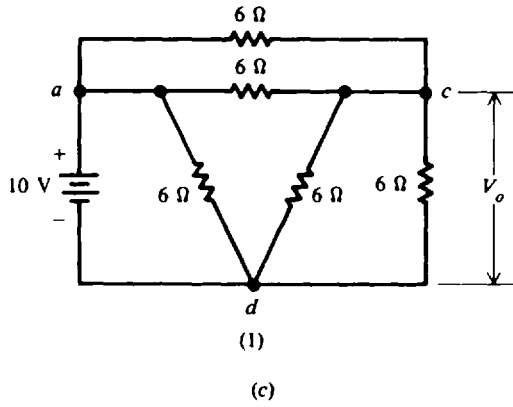
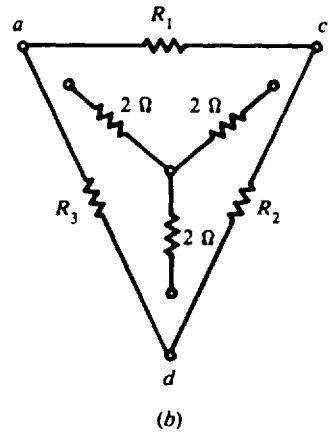
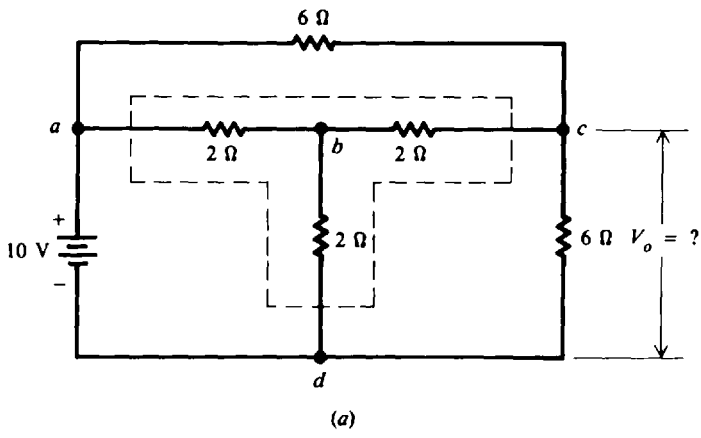
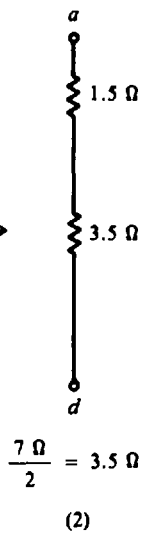
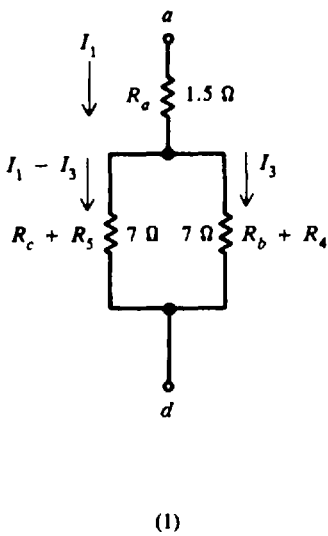
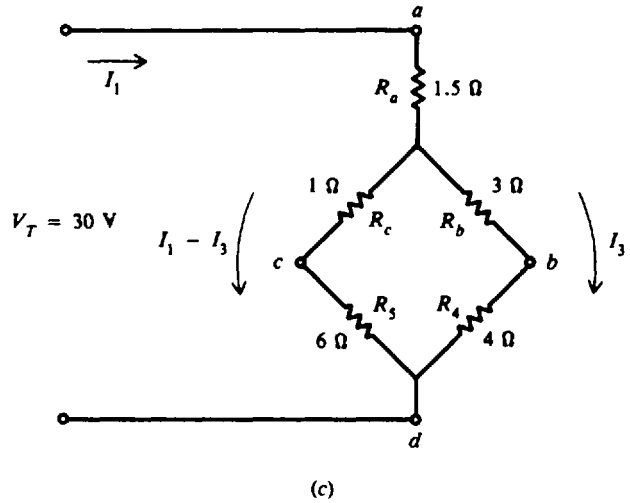
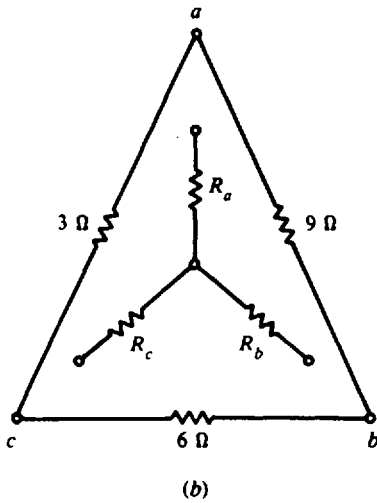


Fig. 8-26

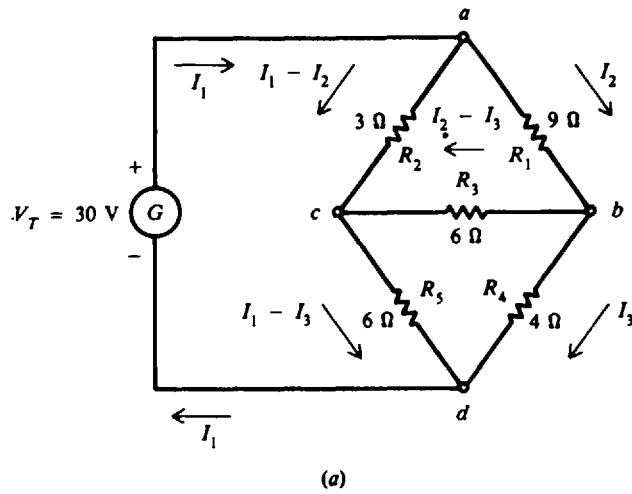
8.3 For a two-delta bridge circuit (Fig. 8-27a), find the values of current through all the resistors.



$$\frac{7 \Omega}{2} = 3.5 \Omega$$

(2)

(d)

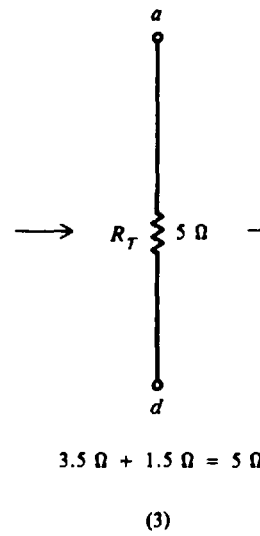

$$3.5 \Omega + 1.5 \Omega = 5 \Omega$$

(3)

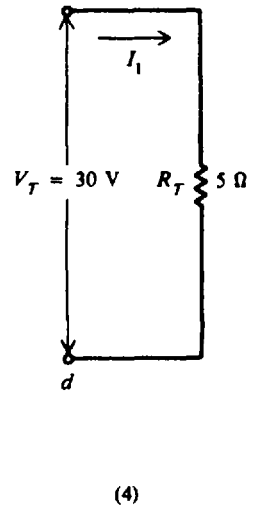


Fig. 8-27

**Step 1.** Find the equivalent resistance between terminals *a* and *d*.

(a) Transform  $\Delta abc$  to its equivalent Y (Fig. 8-27b).

$$R_a = \frac{3(9)}{3+6+9} = \frac{27}{18} = 1.5 \Omega \quad R_b = \frac{9(6)}{18} = \frac{54}{18} = 3 \Omega \quad R_c = \frac{3(6)}{18} = \frac{18}{18} = 1 \Omega$$

(b) Connect the Y equivalent circuit to the original circuit (Fig. 8-27c).

(c) Reduce the series-parallel circuit to its equivalent (Fig. 8-27d).

**Step 2.** Find  $I_1$  and  $I_3$ .

$$I_1 = \frac{V_T}{R_T} = \frac{30}{5} = 6 \text{ A}$$

$I_1$  divides equally into the two 7- $\Omega$  parallel branches so that

$$I_3 = \frac{7}{14} 6 = \frac{6}{2} = 3 \text{ A}$$

**Step 3.** Solve for  $I_2$  by KVL,  $\Sigma V = 0$ . Trace circuit *abca* in the clockwise direction (Fig. 8-27a).

$$-I_2 R_1 - (I_2 - I_3) R_3 + (I_1 - I_2) R_2 = 0$$

Substitute  $R_1 = 9 \Omega$ ,  $R_2 = 3 \Omega$ ,  $R_3 = 6 \Omega$ ,  $I_1 = 6 \text{ A}$ , and  $I_3 = 3 \text{ A}$ .

$$-9I_2 - (I_2 - 3)(6) + (6 - I_2)(3) = 0$$

$$-9I_2 - 6I_2 + 18 + 18 - 3I_2 = 0$$

$$-18I_2 + 36 = 0$$

$$-18I_2 = -36$$

$$I_2 = 2 \text{ A}$$

**Step 4.** Show currents through individual resistors (Fig. 8-27a).

$$I_1 - I_2 = 6 - 2 = 4 \text{ A} \quad \text{Ans.}$$

$$I_2 = 2 \text{ A} \quad \text{Ans.}$$

$$I_1 - I_3 = 6 - 3 = 3 \text{ A} \quad \text{Ans.}$$

$$I_2 - I_3 = 2 - 3 = -1 \text{ A} \quad \text{Ans.}$$

$$I_3 = 3 \text{ A} \quad \text{Ans.}$$

The negative sign for  $I_2 - I_3$  indicates that the current actually flows in the direction of *c* to *b*.

**8.4** The superposition principle can be applied to a voltage-divider circuit with two sources (Fig. 8-28a). Find  $V_p$ .

The method is to calculate  $V_p$  contributed by each source separately and then add (superimpose) these voltages algebraically.

**Step 1.** Short-circuit  $G_2$  and find  $V_{p,G_1}$  due only to source  $G_1$  (Fig. 8-28b).


$R_1$  and  $R_2$  form a series voltage divider for the  $V_1$  source.  $V_{p,G_1}$  is the same as the voltage across  $R_2$ . To find  $V_{p,G_1}$  use the voltage-divider formula:

$$V_{p,G_1} = \frac{R_2}{R_1 + R_2} V_1 = \frac{40}{20 + 40} 240 = \frac{40}{60} 240 = 160 \text{ V}$$


$V_{p,G_1}$  is positive because  $V_1$  is positive.

**Step 2.** Short-circuit  $G_1$  and find  $V_{p,G_2}$  due only to source  $G_2$  (Fig. 8-28c).

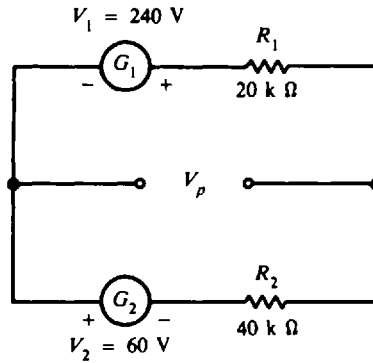
$R_1$  and  $R_2$  form a series voltage divider again, but here  $V_{p,G_2}$  is the same as the voltage across  $R_1$ . To find  $V_{p,G_2}$  we use the voltage-divider formula, but this time we have a negative voltage source  $G_2$ .



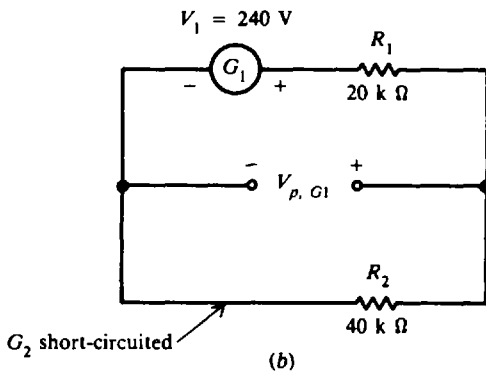(a) Voltage divider circuit with two voltage sources



(b)

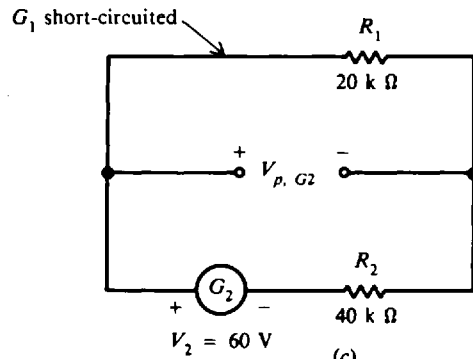

(c)

Fig. 8-28

$$V_{p, G2} = \frac{R_1}{R_1 + R_2} V_2 = \frac{20}{20 + 40} (-60 \text{ V}) = \frac{20}{60} (-60 \text{ V}) = -20 \text{ V}$$

Step 3. To find  $V_p$  add the voltages calculated.

$$V_p = V_{p, G1} + V_{p, G2} = 160 - 20 = 140 \text{ V} \quad \text{Ans.}$$

8.5 Find the current through the load resistor  $R_L$  in the two-generator source circuit (Fig. 8-29a) by superposition.  $R_1$  and  $R_2$  are the internal resistances of the generators.

Step 1. Find the current in  $R_L$  due to  $G_1$  alone, designated  $I_{L, G1}$ .

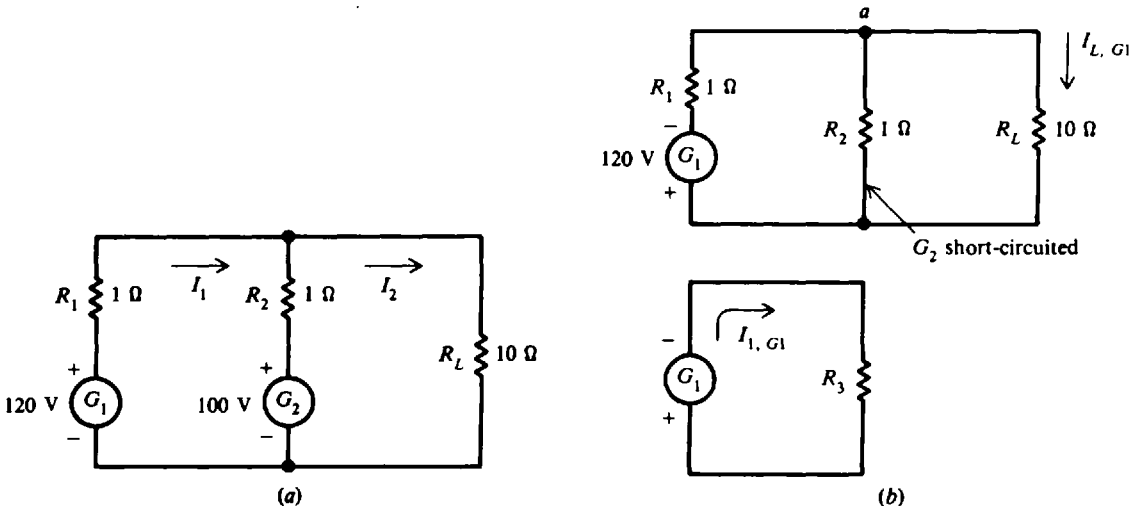


Fig. 8-29a, b

(a) Short-circuit  $G_2$  and reduce the circuit (Fig. 8-29b).

$$R_3 = R_1 + \frac{R_2 R_L}{R_2 + R_L} = 1 + \frac{1(10)}{1 + 10} = 1 + \frac{10}{11} = 1.91 \Omega$$

$$I_{1, G_1} = \frac{V_1}{R_3} = \frac{120}{1.91} = 62.8 \text{ A}$$

(b) Use current-divider formula to find  $I_{L, G_1}$  at point  $a$ .

$$I_{L, G_1} = \frac{R_2}{R_2 + R_L} I_{1, G_1} = \frac{1}{11} 62.8 = 5.71 \text{ A}$$

**Step 2.** Find the current in  $R_L$  due to  $G_2$  alone, namely  $I_{L, G_2}$ . Short-circuit  $G_1$  and reduce the circuit (Fig. 8-29c).

$$R_4 = R_2 + \frac{R_1 R_L}{R_1 + R_L} = 1 + \frac{1(10)}{1 + 10} = 1.91 \Omega$$

$$I_{2, G_2} = \frac{V_2}{R_4} = \frac{100}{1.91} = 52.4 \text{ A}$$

$$I_{L, G_2} = \frac{R_1}{R_1 + R_L} I_{2, G_2} = \frac{1}{11} 52.4 = 4.76 \text{ A}$$

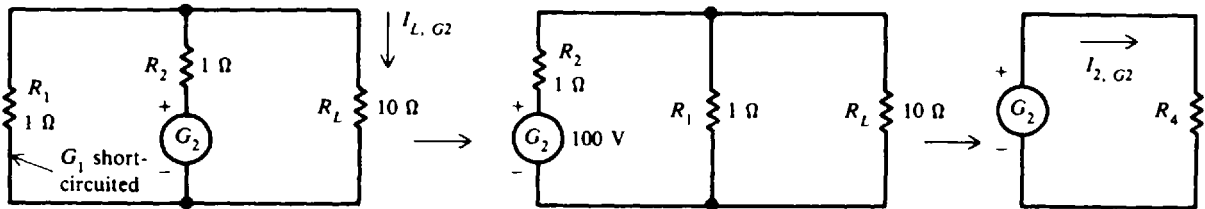


Fig. 8-29c

**Step 3.** Add the individual currents algebraically.

$$I_L = I_{L, G_1} + I_{L, G_2} = 5.71 + 4.76 = 10.5 \text{ A} \quad \text{Ans.}$$

**8.6** Find the load current  $I_L$  and the load voltage  $V_L$  in the circuit (Fig. 8-30a) by use of Thevenin's theorem.

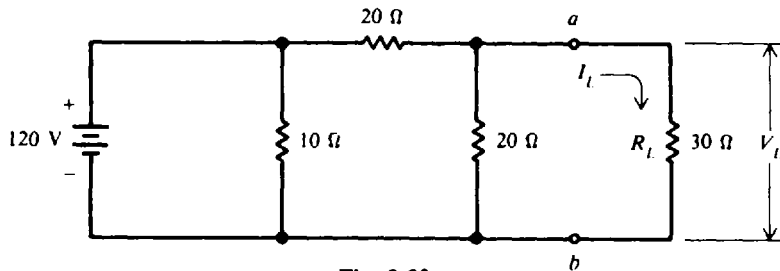


Fig. 8-30a

**Step 1.** Find  $R_{Th}$ . Remove the load  $R_L$ . Short-circuit the voltage source of 120 V (Fig. 8-30b). Short-circuiting the battery also short-circuits the 10- $\Omega$  resistor, leaving two 20- $\Omega$  resistors in parallel.

$$R_{Th} = \frac{20}{2} = 10 \Omega$$

**Step 2.** Find  $V_{Th}$ . The two 20- $\Omega$  resistors are in series across the 120-V line (Fig. 8-30a). Since the voltage is the same across equal resistances and  $V_{Th}$  is the open-circuit voltage at  $a$  and  $b$  across the 20- $\Omega$  resistor,

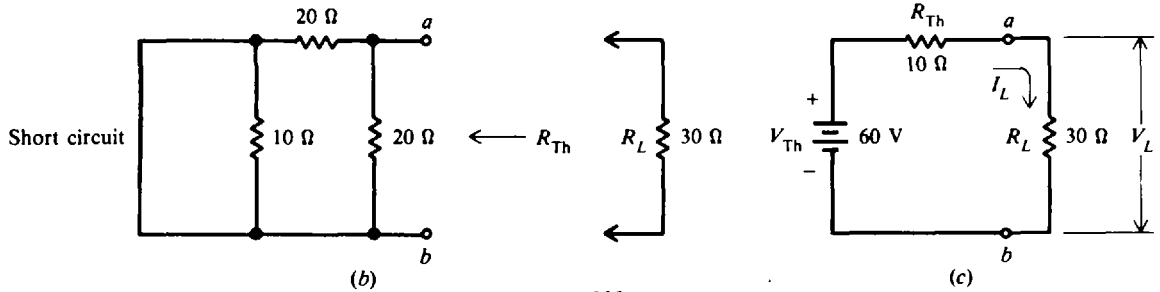


Fig. 8-30b, c

$$V_{Th} = \frac{120}{2} = 60 \text{ V}$$

Step 3. Draw the equivalent circuit with  $R_L$  and find  $I_L$  and  $V_L$  (Fig. 8-30c).

$$I_L = \frac{V_{Th}}{R_L + R_{Th}} = \frac{60}{30 + 10} = \frac{60}{40} = 1.5 \text{ A} \quad \text{Ans.}$$

$$V_L = I_L R_L = 1.5(30) = 45 \text{ V} \quad \text{Ans.}$$

8.7 Find the Thevenin equivalent across  $R_L$  of the Wheatstone bridge network (Fig. 8-31a).

Step 1. For greater clarity, move the voltage source inside the bridge and show the load outside the bridge (Fig. 8-31b).

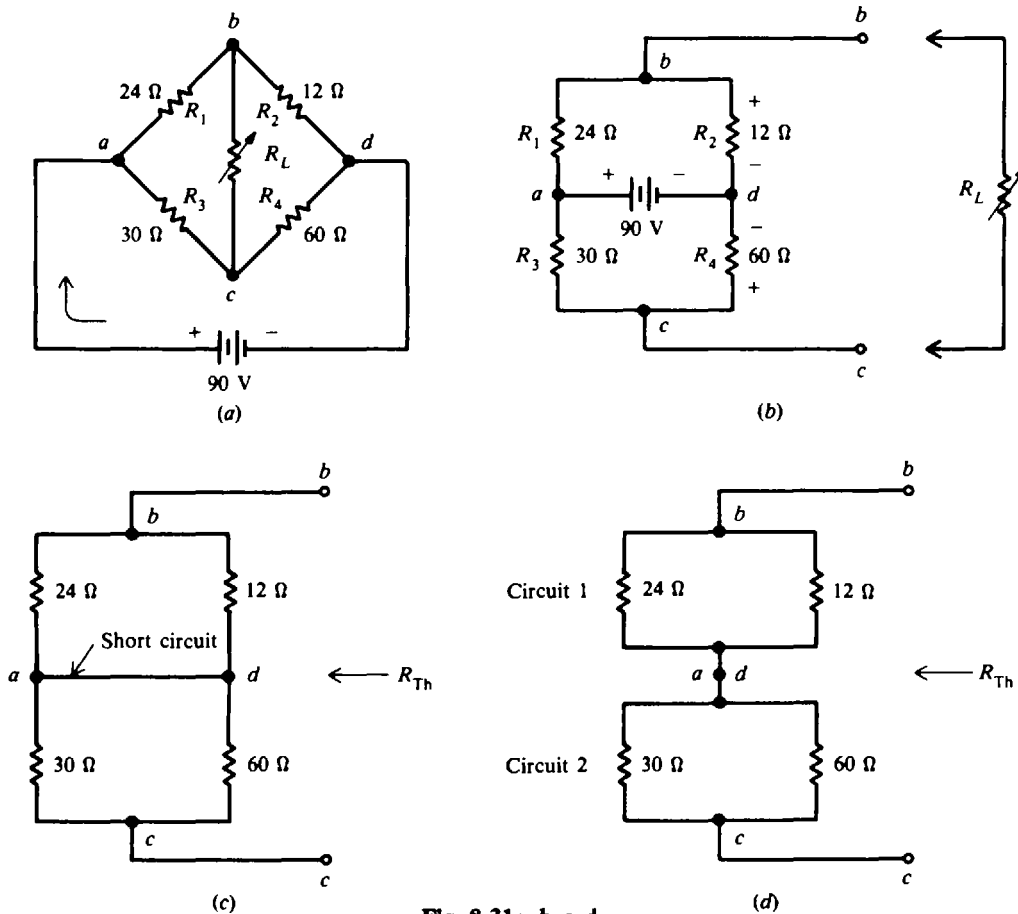


Fig. 8-31a, b, c, d



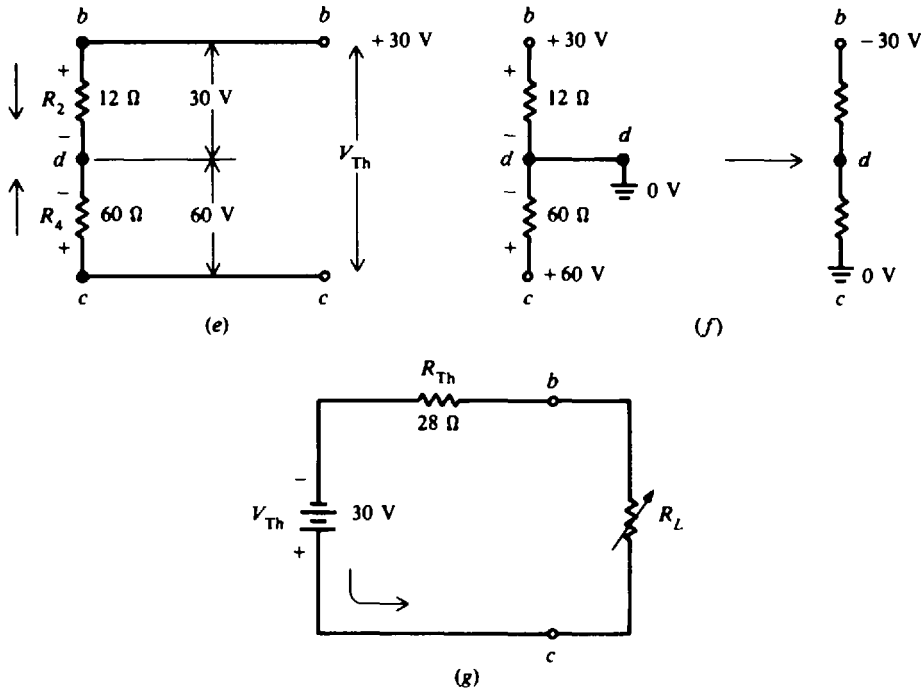


Fig. 8-31e, f, g

**Step 2.** Find  $R_{Th}$ . Short-circuit the 90-V source (Fig. 8-31c).

Redraw the circuit for simplicity (Fig. 8-31d). Find  $R_{eq1}$  for circuit 1,  $R_{eq2}$  for circuit 2, and then combine  $R_{eq1}$  and  $R_{eq2}$  in series to find  $R_{Th}$ .

$$R_{eq1} = \frac{24(12)}{24 + 12} = 8 \Omega$$

$$R_{eq2} = \frac{30(60)}{30 + 60} = 20 \Omega$$

$$R_{Th} = R_{eq1} + R_{eq2} = 8 + 20 = 28 \Omega \quad \text{Ans.}$$

**Step 3.** Find  $V_{Th}$ .  $V_{Th}$  is the open-circuit voltage across terminals  $b$  and  $c$  and is equal to the algebraic sum of voltages across  $R_2$  and  $R_4$  (see Fig. 8-31e). By the voltage-division rule,

$$V_2 = \frac{12}{12 + 24} 90 = \frac{1}{3} 90 = 30 \text{ V}$$

$$V_4 = \frac{60}{60 + 30} 90 = \frac{2}{3} 90 = 60 \text{ V}$$

$$V_{Th} = V_4 - V_2 = 60 - 30 = 30 \text{ V} \quad \text{Ans.}$$

To show the polarity of  $V_{Th}$ , ground  $d$  and note that the voltage at  $b$  is  $+30 \text{ V}$  and the voltage at  $c$  is  $+60 \text{ V}$  with respect to ground. So the voltage at  $b$  is  $-30 \text{ V}$  with respect to  $c$ . This can be seen if we ground point  $c$ . (See Fig. 8-31f.)

**Step 4.** Draw the equivalent circuit with  $R_L$ . Note the polarity of the source. (See Fig. 8-31g.)

**8.8** Convert the voltage source circuit (Fig. 8-32a) to its equivalent current source circuit. Prove that the two circuits are equivalent by calculating the voltage drop and current through a  $10\text{-}\Omega$  load resistor.

**Step 1.** Find the current source equivalent.

$$I = \frac{V}{R} = \frac{15}{5} = 3 \text{ A}$$

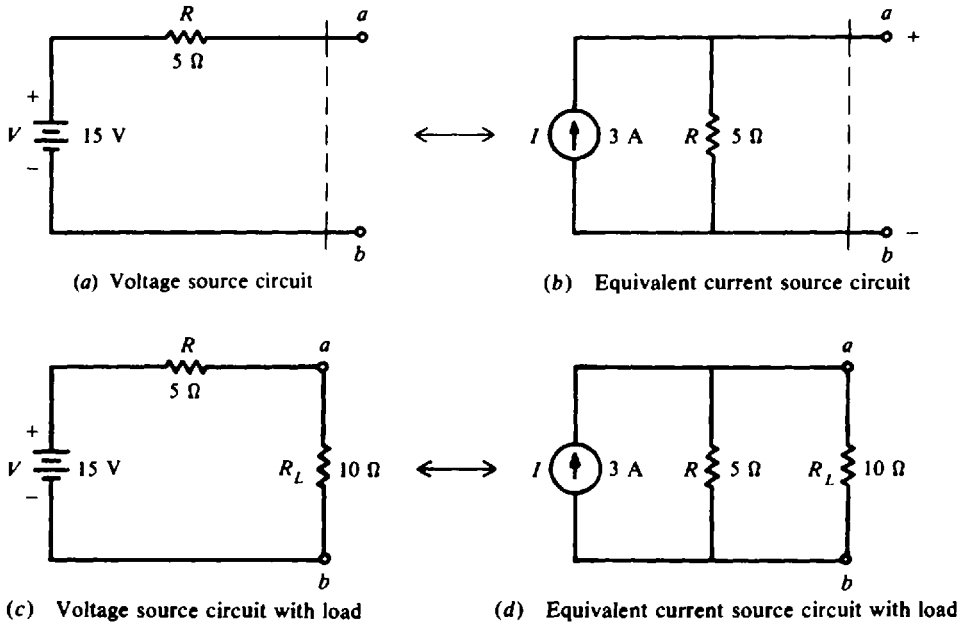


Fig. 8-32

Shunt  $R$  is equal to the series  $R$  of  $5\ \Omega$ . Therefore, the equivalent current source circuit is as shown in Fig. 8-32b.

**Step 2.** Add  $R_L$  at terminals  $a$  and  $b$ . Find  $I_L$  and  $V_L$  in each equivalent circuit and compare their values. From Fig. 8-32c:

$$I_L = \frac{V}{R + R_L} = \frac{15}{5 + 10} = 1\ \text{A}$$

$$V_L = I_L R_L = 1(10) = 10\ \text{V}$$

From Fig. 8-32d:

$$I_L = \frac{R}{R + R_L} I = \frac{5}{5 + 10} 3 = \frac{1}{3} 3 = 1\ \text{A}$$

$$V_L = I_L R_L = 1(10) = 10\ \text{V}$$

The values of load current and load voltage are the same for each circuit.

**8.9** Conversion of voltage and current sources can often simplify circuits when there are two or more sources. Voltage sources are easier for series connections because we can add voltages, whereas current sources are easier for parallel connections because we can add currents. Find the current  $I_L$  through the middle load resistor  $R_L$  (Fig. 8-33a).

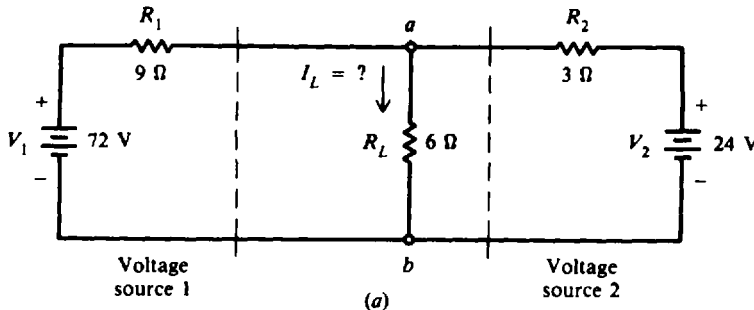


Fig. 8-33a

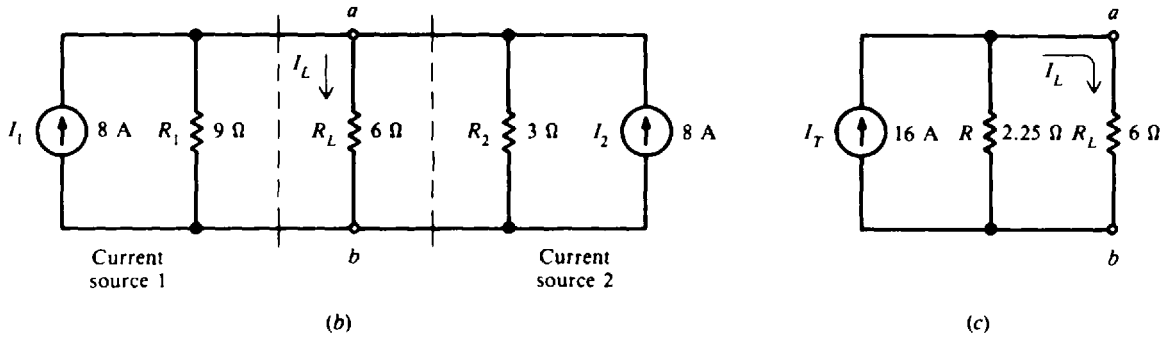


Fig. 8-33b, c

**Step 1.** Convert voltage sources  $V_1$  and  $V_2$  into current sources.

$$I_1 = \frac{V_1}{R_1} = \frac{72}{9} = 8 \text{ A} \quad \text{Shunt } R_1 = \text{series } R_1 = 9 \Omega$$

$$I_2 = \frac{V_2}{R_2} = \frac{24}{3} = 8 \text{ A} \quad \text{Shunt } R_2 = \text{series } R_2 = 3 \Omega$$

**Step 2.** Draw the equivalent current source circuit (see Fig. 8-33b).  $I_1$  and  $I_2$  can be combined for one equivalent current source  $I_T$ . Since they produce current in the same direction through  $R_L$ , they are added.

$$I_T = I_1 + I_2 = 8 + 8 = 16 \text{ A}$$

The shunt  $R$  for the 16-A combined current source is the combined resistance of the  $9\text{-}\Omega$   $R_1$  and the  $3\text{-}\Omega$   $R_2$  in parallel. So

$$\text{Shunt } R = \frac{R_1 R_2}{R_1 + R_2} = \frac{9(3)}{9 + 3} = \frac{27}{12} = 2.25 \Omega$$

The circuit of Fig. 8-33b can be redrawn as shown in Fig. 8-33c.

**Step 3.** Find  $I_L$ . Use the current-divider formula for the  $6\text{-}\Omega$  and  $2.25\text{-}\Omega$  branches.

$$I_L = \frac{2.25}{2.25 + 6} 16 = \frac{2.25}{8.25} 16 = 4.36 \text{ A} \quad \text{Ans.}$$

**8.10** Find the current  $I_L$  by converting the series current sources  $I_1$  and  $I_2$  into series voltage sources (Fig. 8-34a).


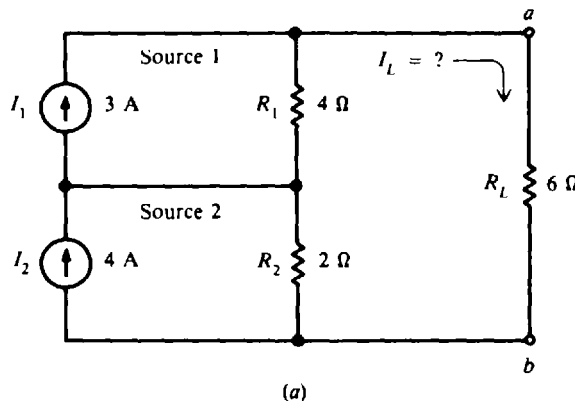


Fig. 8-34a

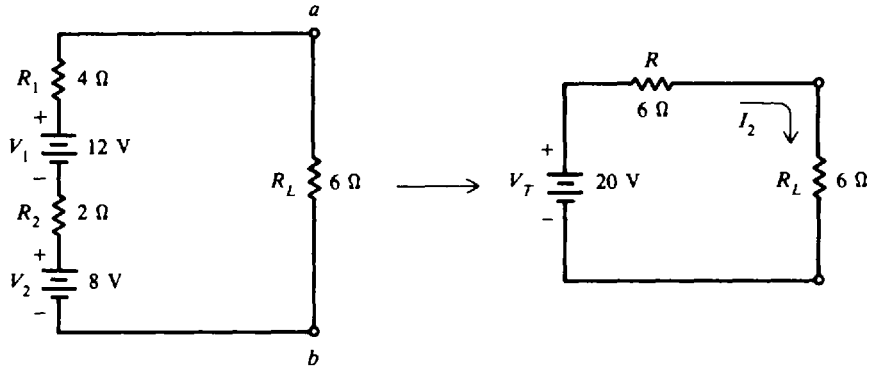

(b)  
Fig. 8-34b

Step 1. Convert  $I_1$  and  $I_2$  into voltage sources.

$$V_1 = I_1 R_1 = 3(4) = 12 \text{ V} \quad \text{Shunt } R_1 = \text{series } R_1 = 4 \Omega$$

$$V_2 = I_2 R_2 = 4(2) = 8 \text{ V} \quad \text{Shunt } R_2 = \text{series } R_2 = 2 \Omega$$

Step 2. Draw the equivalent voltage source circuit (see Fig. 8-34b). The series voltages are added because they are series-aiding.

$$V_T = V_1 + V_2 = 12 + 8 = 20 \text{ V}$$


The series resistances are added.

$$R = R_1 + R_2 = 4 + 2 = 6 \Omega$$

Then by Ohm's law,

$$I_L = \frac{V_T}{R + R_L} = \frac{20}{6 + 6} = \frac{20}{12} = 1.67 \text{ A} \quad \text{Ans.}$$

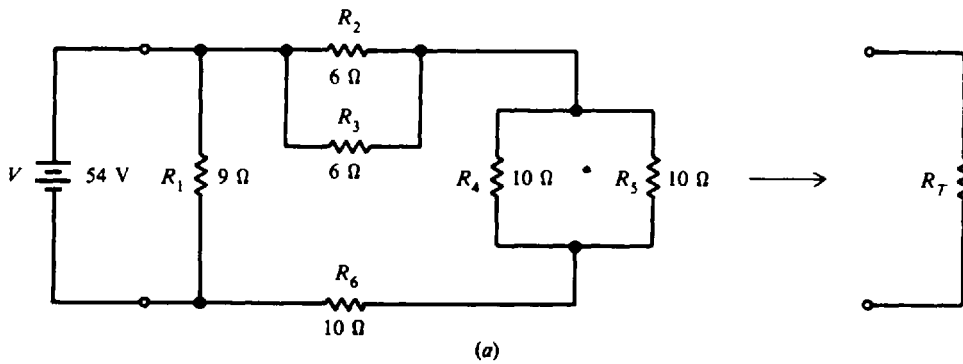8.11 Find the total resistance  $R_T$  of the circuit shown in Fig. 8-35a.



(a)  
Fig. 8-35a

Step 1. Reduce the parallel resistances  $R_2$ ,  $R_3$  and  $R_4$ ,  $R_5$  to a single resistance. Use formula for  $R/N$ . (See Fig. 8-35b.)

$$\frac{R_2}{2} = \frac{6}{2} = 3 \Omega$$

$$\frac{R_4}{2} = \frac{10}{2} = 5 \Omega$$

**Step 2.** Add series resistances. (See Fig. 8-35c.)

$$R_p = 10 + 5 + 3 = 18 \Omega$$

**Step 3.** Find  $R_T$ . (See Fig. 8-35d.)

$$R_T = \frac{R_1 R_p}{R_1 + R_p} = \frac{9(18)}{9 + 18} = 6 \Omega \quad \text{Ans.}$$

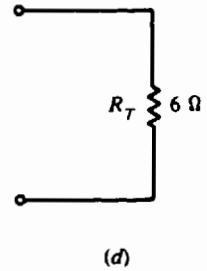
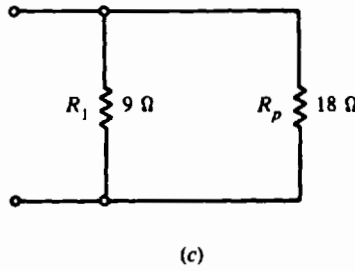
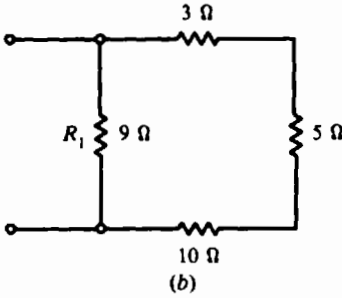


Fig. 8-35b, c, d

**8.12** For the circuit in Fig. 8-35a, determine the current values through all the resistors when the applied voltage is 54 V. Having found the equivalent resistances by steps in Prob. 8.11, we shall work backward, starting with  $R_T$  and proceeding toward the original circuit.

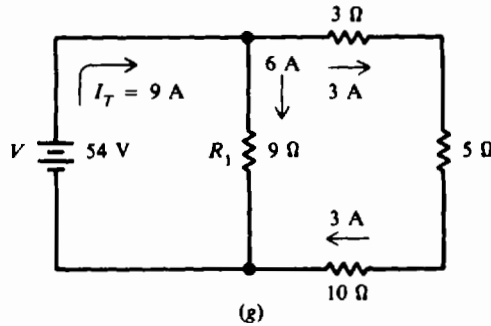
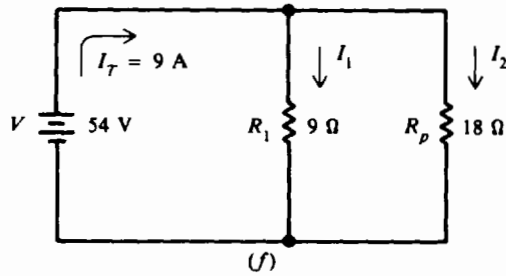
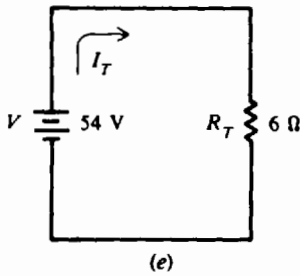


Fig. 8-35e, f, g

**Step 1.** Find  $I_T$  (Fig. 8-35e).

$$I_T = \frac{54}{6} = 9 \text{ A}$$


**Step 2.** Find  $I_1$  and  $I_2$  (Fig. 8-35f). By Ohm's law,

$$I_1 = \frac{V}{R_1} = \frac{54}{9} = 6 \text{ A}$$

$$I_2 = \frac{V}{R_p} = \frac{54}{18} = 3 \text{ A}$$

**Step 3.** Show the circuit equivalent. (See Fig. 8-35g.)

**Step 4.** Show the original circuit. (See Fig. 8-35h.)

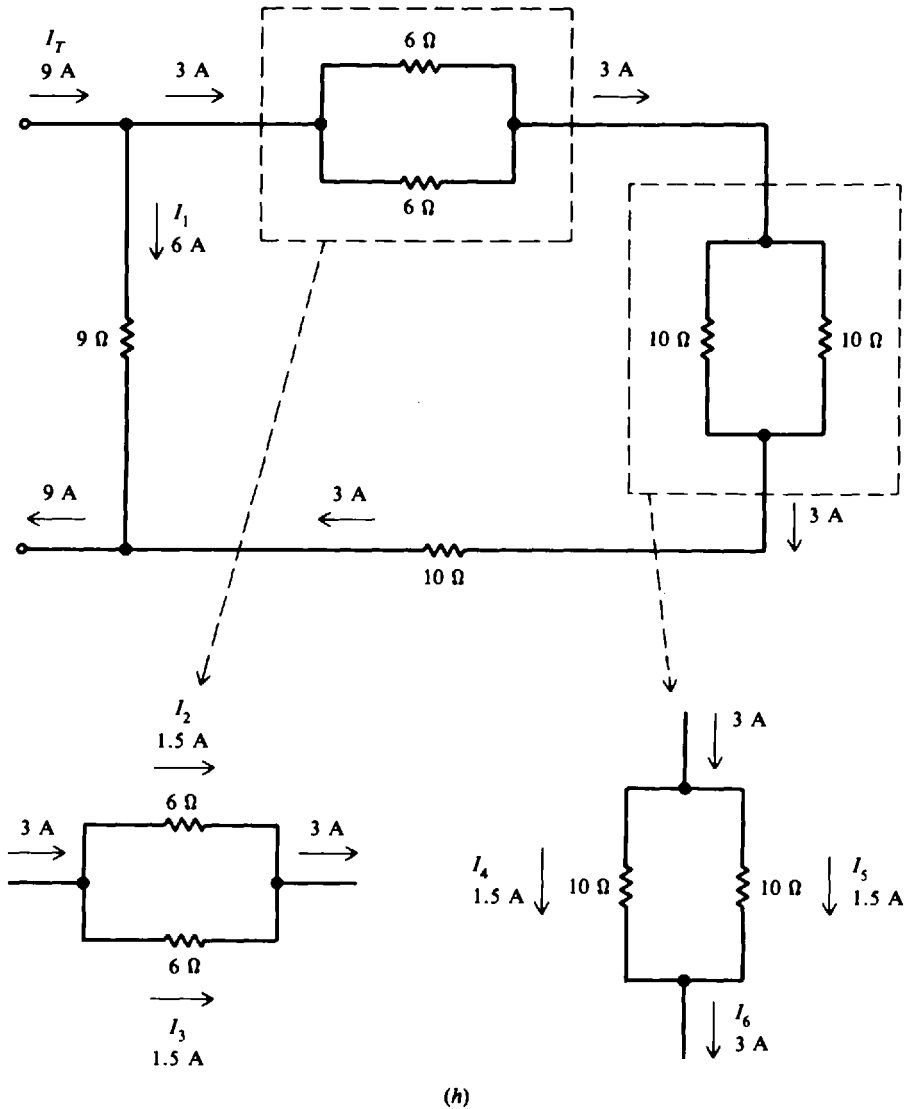

**Fig. 8-35h**

Because the parallel resistances are equal, the current of 3 A divides equally into 1.5 A and 1.5 A.

$$\begin{array}{ll}
 I_1 = 6 \text{ A} & I_4 = 1.5 \text{ A} \\
 I_2 = 1.5 \text{ A} & I_5 = 1.5 \text{ A} \quad \text{Ans.} \\
 I_3 = 1.5 \text{ A} & I_6 = 3 \text{ A}
 \end{array}$$

**8.13** Find the total resistance of the circuit (Fig. 8-36a).

**Step 1.** Reduce the circuit progressively from right to left. Add series resistances. (See Fig. 8-36b.)

$$R_A = R_6 + R_3 + R_7 = 30 + 40 + 50 = 120 \Omega$$

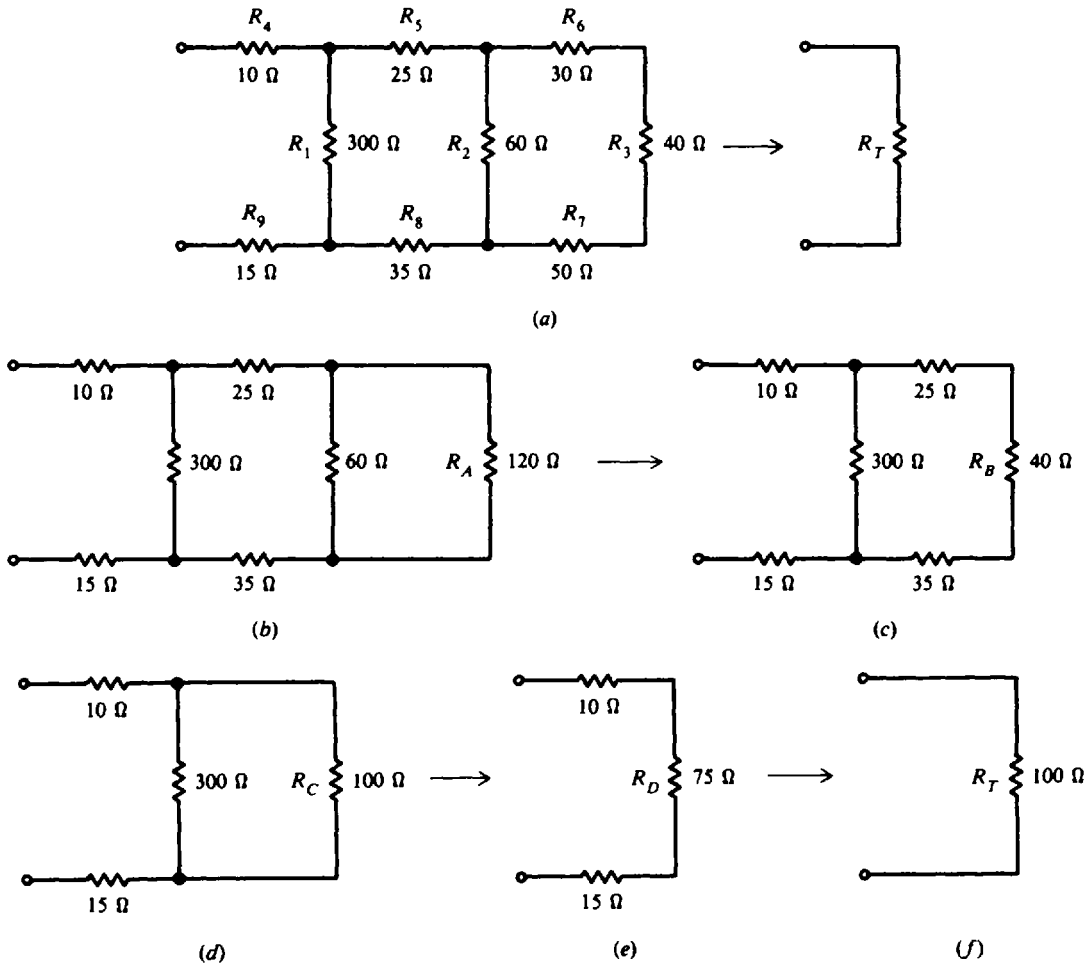


Fig. 8-36

**Step 2.** Combine parallel branches (Fig. 8-36c).

$$R_B = \frac{60(120)}{60 + 120} = 40 \Omega$$

**Step 3.** Add series resistances (Fig. 8-36d).

$$R_C = 35 + 40 + 25 = 100 \Omega$$

**Step 4.** Combine parallel branches (Fig. 8-36e).

$$R_D = \frac{300(100)}{300 + 100} = 75 \Omega$$

**Step 5.** Find  $R_T$  by combining series resistances (Fig. 8-36f).

$$R_T = 10 + 75 + 15 = 100 \Omega \quad \text{Ans.}$$

**8.14** In the Wheatstone bridge circuit (Fig. 8-37), the bridge is balanced. Calculate  $R_x$ ,  $I_x$ ,  $I_1$ , and each voltage.

**Step 1.** Calculate  $R_x$  by Eq. (8-7).

$$R_x = \frac{R_1}{R_2} R_3 = \frac{1000}{10\,000} 42 = 4.2 \Omega \quad \text{Ans.}$$

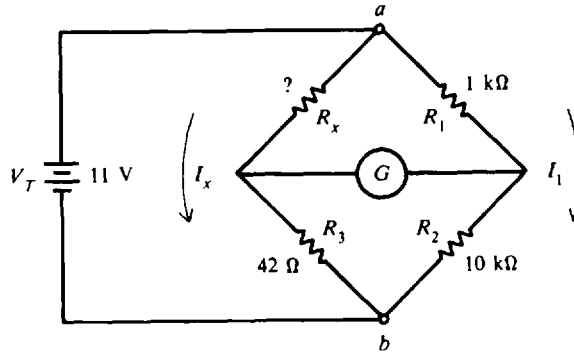


Fig. 8-37

**Step 2.** Calculate currents  $I_x$  and  $I_1$ . Express the voltage drop across terminals  $a$  and  $b$ .

$$I_x R_x + I_x R_3 = V_T$$

$$I_x (R_x + R_3) = V_T$$

$$I_x = \frac{V_T}{R_x + R_3} = \frac{11}{4.2 + 42} = \frac{11}{46.2} = 0.238 \text{ A} \quad \text{Ans.}$$

Similarly,  $I_1 R_1 + I_1 R_2 = V_T$

$$I_1 (R_1 + R_2) = V_T$$

$$I_1 = \frac{V_T}{R_1 + R_2} = \frac{11}{1000 + 10\,000} = \frac{11}{11\,000} = 0.001 \text{ A} \quad \text{Ans.}$$

**Step 3.** Find each voltage. By Ohm's law,

$$V_x = I_x R_x = 0.237(4.2) = 1 \text{ V} \quad \text{Ans.}$$

$$V_1 = I_1 R_1 = 0.001(1000) = 1 \text{ V} \quad \text{Ans.}$$

$$V_2 = I_1 R_2 = 0.001(10\,000) = 10 \text{ V} \quad \text{Ans.}$$

$$V_3 = I_x R_3 = 0.237(42) = 10 \text{ V} \quad \text{Ans.}$$

When the bridge is balanced, no current flows through the galvanometer, so that

$$V_x = V_1$$

$$1 \text{ V} = 1 \text{ V} \quad \text{Check}$$

and

$$V_3 = V_2$$

$$10 \text{ V} = 10 \text{ V} \quad \text{Check}$$

An alternative method to find each voltage is by the voltage-divider rule. With this method we need not solve for the currents.

$$V_1 = \frac{R_1}{R_1 + R_2} V_T = \frac{1}{1 + 10} 11 = \frac{1}{11} 11 = 1 \text{ V}$$

Then

$$V_2 = V_T - V_1 = 11 - 1 = 10 \text{ V}$$

Similarly,

$$V_x = \frac{R_x}{R_x + R_3} V_T = \frac{4.2}{4.2 + 42} 11 = \frac{4.2}{46.2} 11 = 1 \text{ V}$$

and

$$V_3 = V_T - V_x = 11 - 1 = 10 \text{ V}$$

**8.15** Find the value of load resistance  $R_L$  that will provide the maximum power delivered to the load (Fig. 8-38a). Also calculate maximum power  $P_L$ .

**Step 1.** Show the Thevenin equivalent circuit (Fig. 8-36b).  $R_1$  and  $R_2$  are in parallel.

$$R_{th} = \frac{R_1 R_2}{R_1 + R_2} = \frac{5(20)}{5 + 20} = 4 \Omega$$



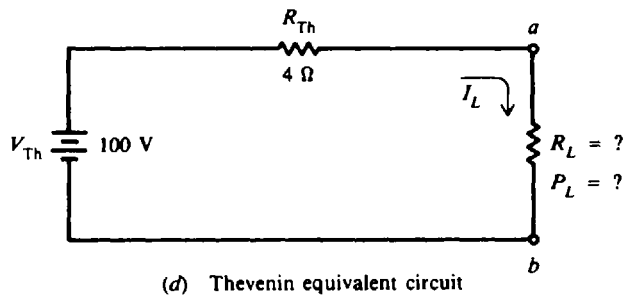
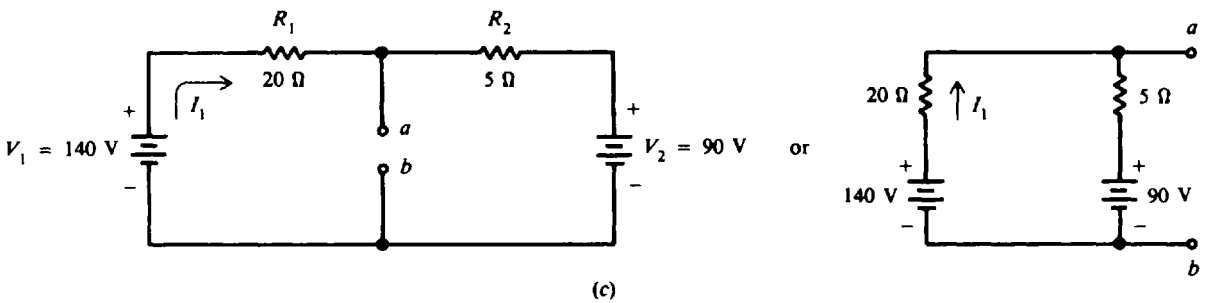
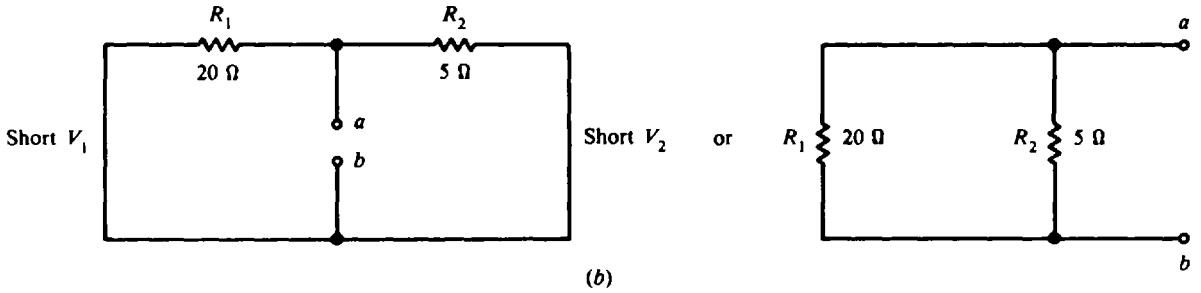
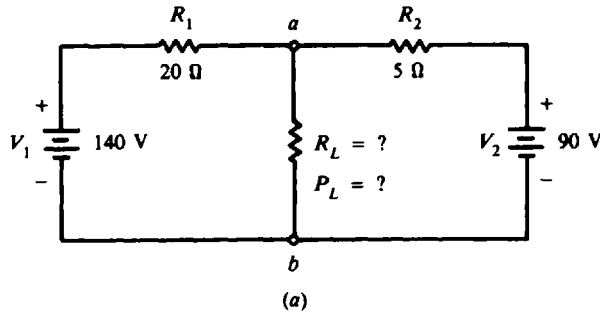


Fig. 8-38

By Ohm's law (see Fig. 8-38c).

$$I_1 = \frac{V_1 - V_2}{R_1 + R_2} = \frac{140 - 90}{20 + 5} = \frac{50}{25} = 2 \text{ A}$$

$$V_{Th} = V_{ab} = V_1 - I_1 R_1 = 140 - 2(20) = 140 - 40 = 100 \text{ V}$$

The Thevenin equivalent circuit is shown in Fig. 8-38d.

Step 2. Find  $R_L$  and  $P_L$ . For maximum power to be delivered to the load,  $R_L = R_{Th}$ . Therefore,

$$R_L = 4 \Omega \quad \text{Ans.}$$

$$P_L = I_L^2 R_L = \left( \frac{V_{Th}}{R_{Th} + R_L} \right)^2 (R_L) = \left( \frac{100}{4 + 4} \right)^2 (4) = 625 \text{ W} \quad \text{Ans.}$$

Or, more simply, since source voltage divides in half between  $R_{Th}$  and  $R_L$ ,

$$V_L = 50 \text{ V} \quad \text{and} \quad P_L = \frac{V_L^2}{R_L} = \frac{50^2}{4} = 625 \text{ W}$$

Note that maximum power is received by the load if the load resistance  $R_L$  is equal to a fixed value of series resistance, which may include the internal resistance of the voltage source. In this problem the series resistance is equivalent to the Thevenin resistance  $R_{Th}$ .

**8.16** A motor drawing 8333 W is operating from a 232-V source 100 ft away (Fig. 8-39). For power installations, the National Electrical Code permits a 5 percent drop. What is the line power loss? What is the minimum size copper wire that may be used for the line supplying the motor to avoid exceeding the 5 percent voltage drop?

**Step 1.** Find the minimum voltage at the motor load,  $V_L$ .


$$\begin{aligned} V_{\text{source}} &= 232 \text{ V} \\ V_{\text{line drop}} &= 0.05(232) = 11.6 \text{ V} \\ V_L &= V_{\text{source}} - V_{\text{line drop}} = 232 - 11.6 = 220.4 \text{ V} \end{aligned}$$

**Step 2.** Find current drawn by motor,  $I_L$ .

$$\begin{aligned} P_L &= I_L V_L \\ I_L &= \frac{P_L}{V_L} = \frac{8333}{220.4} = 37.8 \text{ A} \end{aligned}$$

**Step 3.** Find line power loss  $P_l$ .

$$\begin{aligned} \text{Line drop } V_l &= 0.05(232) = 11.6 \text{ V} \\ I_L &= 37.8 \text{ A} \\ P_l &= V_l I_L \\ &= 11.6(37.8) = 438 \text{ W} \quad \text{Ans.} \end{aligned}$$

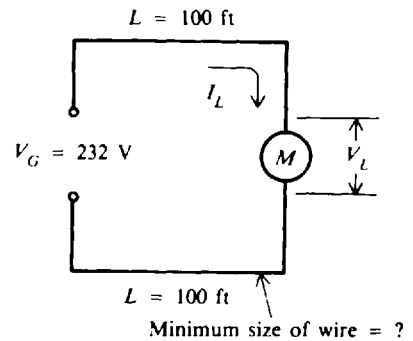

**Fig. 8-39**

**Step 4.** Find the resistance of the line wires,  $R_l$ .

$$\begin{aligned} V_l &= I_L R_l \\ R_l &= \frac{V_l}{I_L} = \frac{11.6}{37.8} = 0.307 \Omega \end{aligned}$$

**Step 5.** Find the circular-mil area of the wire that has this resistance.

$$\begin{aligned} R_l &= \rho \frac{l}{A} & (4-5) \\ A &= \rho \frac{l}{R_l} \\ \rho &= 10.4 \quad (\text{Table 4-2}) \quad l = 2L = 200 \text{ ft} \quad R_l = 0.307 \Omega \\ A &= \frac{10.4(200)}{0.307} = 6780 \text{ CM} \end{aligned}$$

**Step 6.** Find the gauge number of the wire whose circular-mil area is larger than 6780 CM. Refer to Table 4-1; No. 11 wire is the minimum wire size that can be used to limit voltage drop to 5 percent. *Ans.*

**8.17** Find the voltage across the motor and across the lamp bank of the circuit (Fig. 8-40). The motor draws 4 A and the lamp bank 5 A. Resistances of the feeder line are indicated.

**Step 1.** Find the current distribution.

$$I_G = I_M + I_L = 4 + 5 = 9 \text{ A}$$

In section 1 the current is 9 A, and in section 2 the current is 5 A.

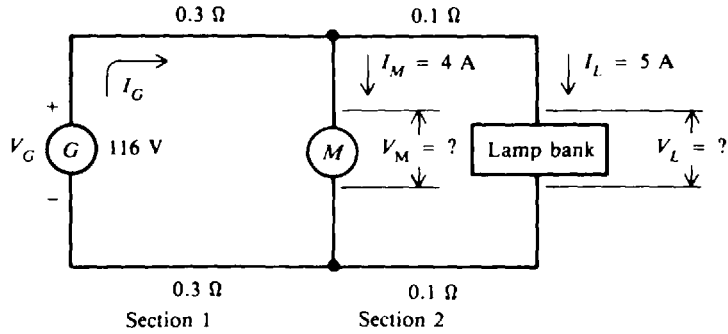


Fig. 8-40

**Step 2.** Find the line drop in each section.


Section 1:  $R_{l1} = 0.3 + 0.3 = 0.6 \Omega$   
 $V_{l1} = I_G R_{l1} = 9(0.6) = 5.4 \text{ V}$

Section 2:  $R_{l2} = 0.1 + 0.1 = 0.2 \Omega$   
 $V_{l2} = I_L R_{l2} = 5(0.2) = 1 \text{ V}$


**Step 3.** Find the load voltages.

$V_M = V_G - V_{l1} = 116 - 5.4 = 110.6 \text{ V}$      *Ans.*  
 $V_L = V_M - V_{l2} = 110.6 - 1 = 109.6 \text{ V}$      *Ans.*

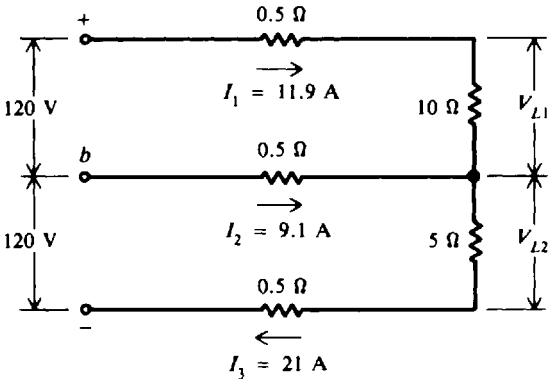**8.18** Compare the line drop and load voltage of a three-wire system and a two-wire system. Use the circuit of Fig. 8-23 with the 10-Ω load for your calculations (see Fig. 8-41).



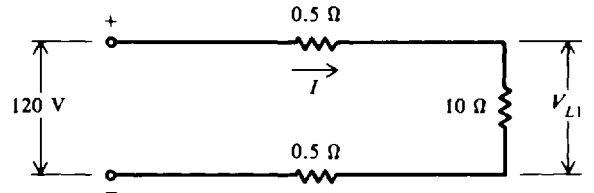(a) Original three-wire system (Fig. 8-23)



(b) Two-wire system

Fig. 8-41

For three-wire system with respect to 10-Ω load (Fig. 8-41a):

$V_{l1} = 11.9(0.5) = 5.95 \text{ V}$

$V_{l2} = 9.1(0.5) = 4.55 \text{ V}$

Total line drop =  $V_{l1} + V_{l2} = 5.95 + 4.55 = 10.5 \text{ V}$

$V_{L1} = 11.9(10) = 119 \text{ V}$

For two-wire system (Fig. 8-41b):

$I = \frac{120}{0.5 + 10 + 0.5} = \frac{120}{11} = 10.9 \text{ A}$

Total line drop =  $10.9(1) = 10.9 \text{ V}$

$V_{L1} = 10.9(10) = 109 \text{ V}$

Then,

Difference in line drop =  $10.9 - 10.5 = 0.4 \text{ V}$      *Ans.*

Difference in load voltage =  $119 - 109 = 10 \text{ V}$      *Ans.*

So we see that in this case a three-wire system has a line drop of 0.4 V less than that of a two-wire system and a higher load voltage by 10 V.

### Supplementary Problems

**8.19** Transform the  $\Delta$  networks of Fig. 8-42a into Y networks. (Hint: Draw visual aid.)  
 Ans. See Fig. 8-42b.

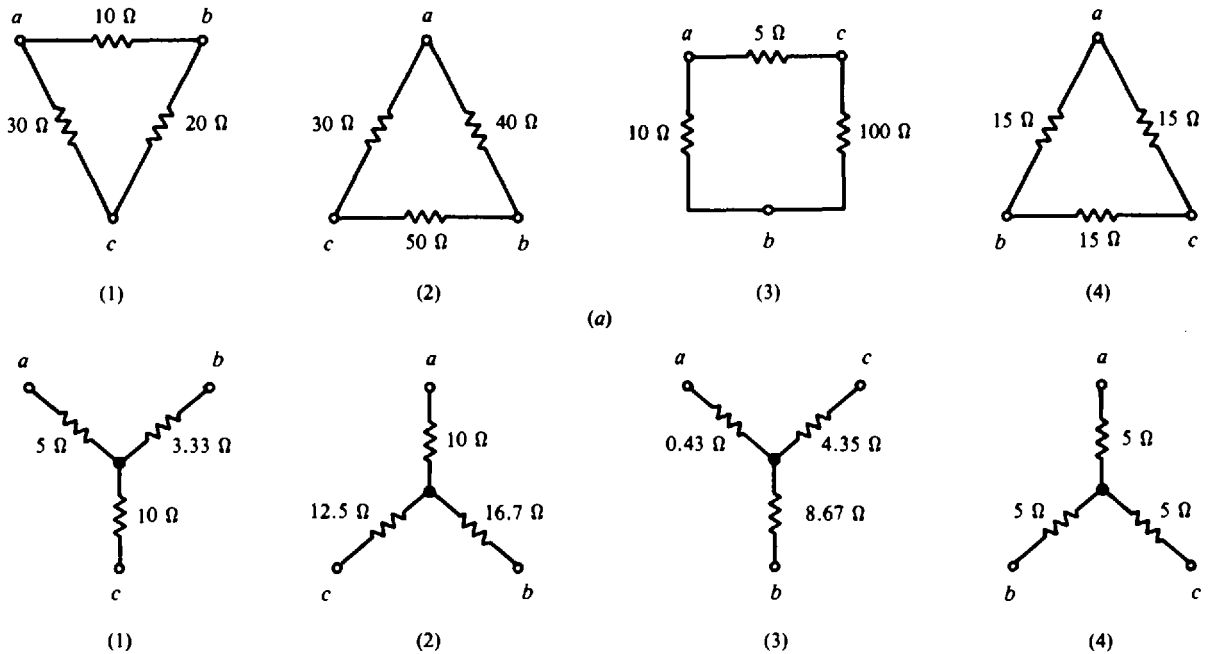


Fig. 8-42

**8.20** Transform the Y networks of Fig. 8-43a into  $\Delta$  networks. (Hint: Draw visual aid.)  
 Ans. See Fig. 8-43b.

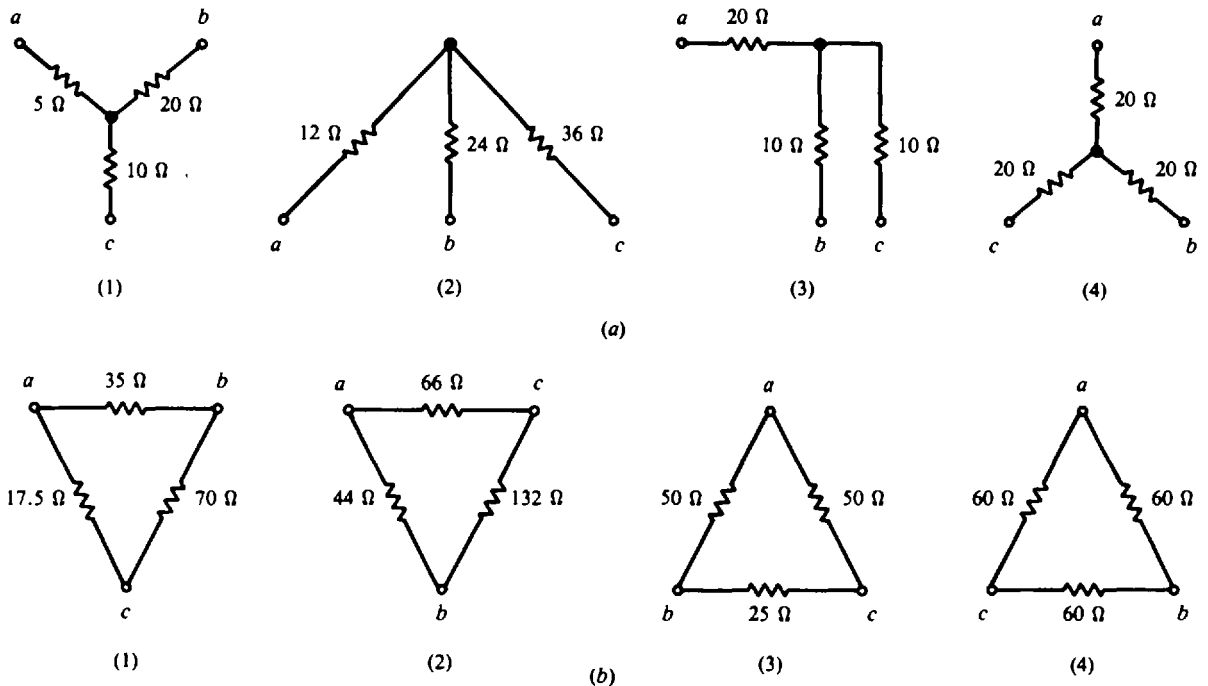


Fig. 8-43

8.21 Find the equivalent input resistance between terminals  $a$  and  $d$  for the bridge networks (Fig. 8-44).  
 Ans. (a)  $R_T = 10 \Omega$ ; (b)  $R_T = 11.0 \Omega$ ; (c)  $R_T = 5 \Omega$

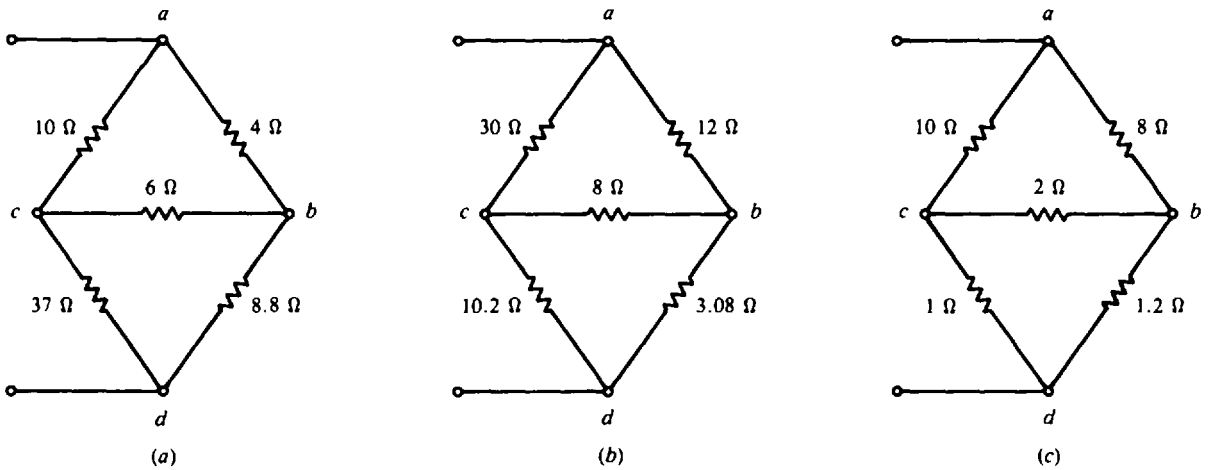


Fig. 8-44

8.22 If 50 V were applied between terminals  $a$  and  $d$  to the circuit shown in Fig. 8-44c, find the current in each resistor.  
 Ans.  $I_{10\Omega} = 4.5 \text{ A}$ ;  $I_{8\Omega} = 5.5 \text{ A}$ ;  $I_{2\Omega} = 0.5 \text{ A}$ ;  $I_{1\Omega} = 5 \text{ A}$ ;  $I_{1.2\Omega} = 5 \text{ A}$

8.23 Find the equivalent resistance and output voltage  $V_o$  of a bridged T network (Fig. 8-45).  
 Ans.  $R_T = 25 \Omega$ ;  $V_o = 7.5 \text{ V}$

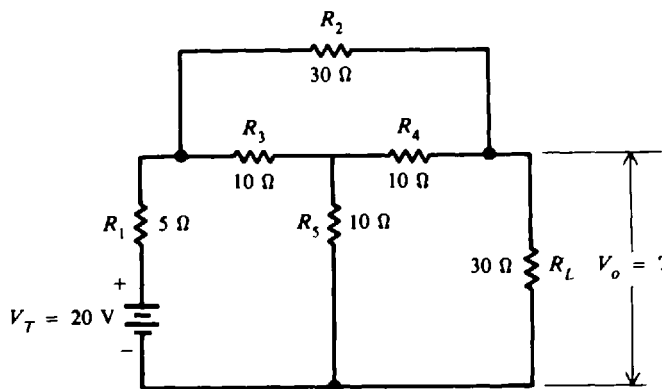


Fig. 8-45

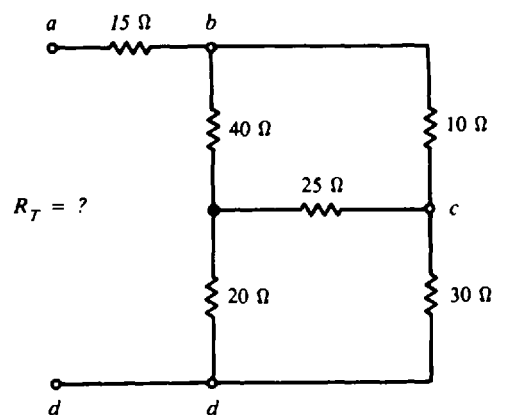


Fig. 8-46

8.24 Find the equivalent input resistance between terminals  $a$  and  $d$  (Fig. 8-46).  
 Ans.  $R_T = 37 \Omega$

8.25 Determine the voltage  $V_p$  by superposition (Fig. 8-47).  
 Ans.  $V_p = 30 \text{ V}$

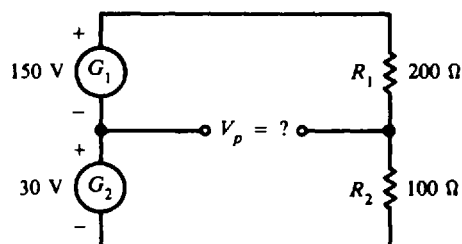


Fig. 8-47

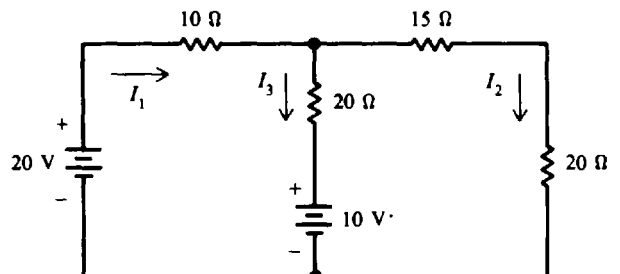


Fig. 8-48

8.26 Solve for the indicated currents by using superposition (Fig. 8-48).  
 Ans.  $I_1 = 0.6 \text{ A}$ ;  $I_2 = 0.4 \text{ A}$ ;  $I_3 = 0.2 \text{ A}$

8.27 Find the current in the load  $R_L$  by superposition (Fig. 8-49).  
 Ans.  $I_L = 14.8 \text{ A}$  (rounded from 14.84 A)

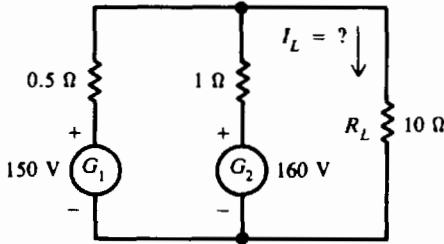


Fig. 8-49

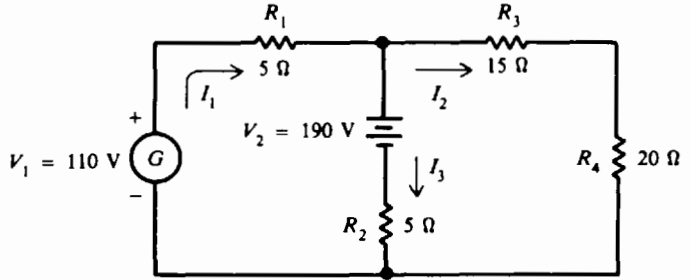



Fig. 8-50

8.28 Find currents  $I_1$ ,  $I_2$ , and  $I_3$  in a two-mesh circuit by superposition (Fig. 8-50).


Ans.  $I_1 = -6 \text{ A}$  (actual direction of current is opposite to the assumed direction);  $I_2 = 4 \text{ A}$ ;  $I_3 = -10 \text{ A}$  (actual direction is opposite to assumed direction)

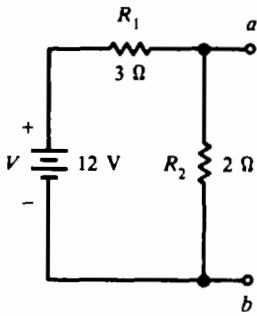8.29 Find the Thevenin equivalents to the circuits of Fig. 8-51.


Ans. (a)  $R_{Th} = 1.2 \Omega$ ;  $V_{Th} = 4.8 \text{ V}$ ; (b)  $R_{Th} = 1.6 \Omega$ ;  $V_{Th} = 2.4 \text{ V}$ ;  
 (c)  $R_{Th} = 0.89 \Omega$ ;  $V_{Th} = 1.33 \text{ V}$



(a)

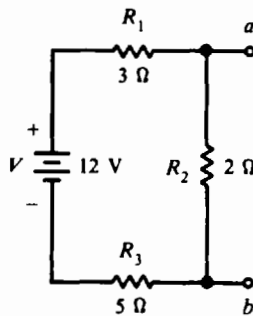

(b)

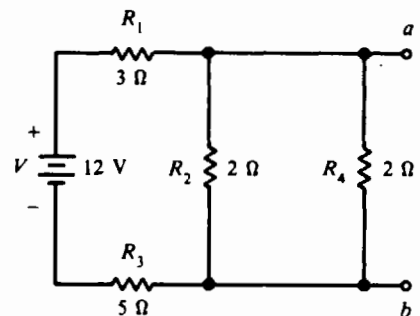

(c)

Fig. 8-51

8.30 Add a resistor load  $R_L$  of  $5 \Omega$  between terminals  $a$  and  $b$  to each circuit of Prob. 8.29, and find the load current  $I_L$  and load voltage  $V_L$ .

Ans. (a)  $I_L = 0.77 \text{ A}$ ;  $V_L = 3.87 \text{ V}$ ; (b)  $I_L = 0.36 \text{ A}$ ;  $V_L = 1.82 \text{ V}$ ; (c)  $I_L = 0.23 \text{ A}$ ;  $V_L = 1.13 \text{ V}$

8.31 Find  $I_L$  and  $V_L$  by the Thevenin equivalent for the circuit of Fig. 8-52. Ans.  $I_L = 2 \text{ A}$ ;  $V_L = 20 \text{ V}$

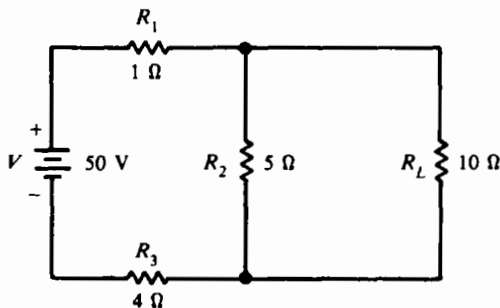


Fig. 8-52

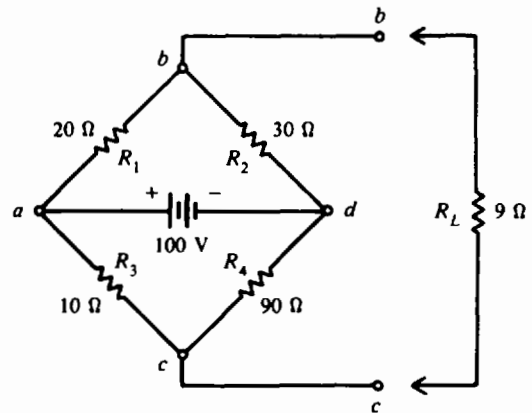


Fig. 8-53

8.32 In the Wheatstone bridge network (Fig. 8-53), find the Thevenin equivalents  $R_{Th}$  and  $V_{Th}$ , and then find  $I_L$  and  $V_L$ . *Ans.*  $R_{Th} = 21 \Omega$ ;  $V_{Th} = 30 \text{ V}$ ;  $I_L = 1 \text{ A}$ ;  $V_L = 9 \text{ V}$

8.33 Find  $I_L$  and  $V_L$  (Fig. 8-54) by the Thevenin theorem. *Ans.*  $I_L = 3 \text{ A}$ ;  $V_L = 18 \text{ V}$ ; ( $R_{Th} = 1.71 \Omega$ ;  $V_{Th} = 23.1 \text{ V}$ )

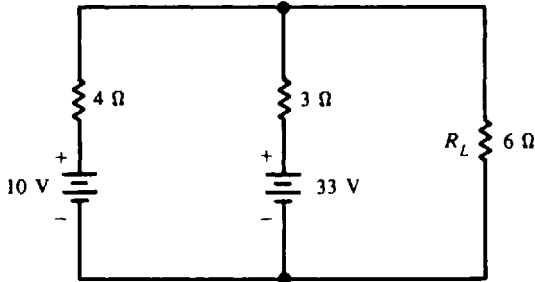


Fig. 8-54


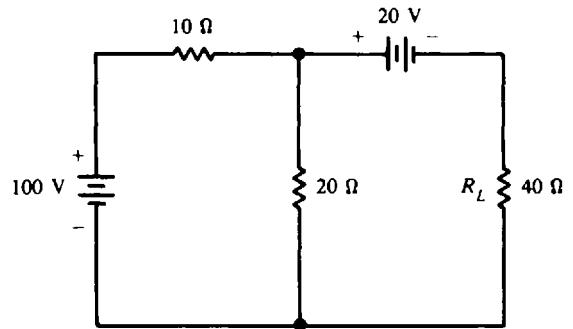



Fig. 8-55

8.34 Find  $I_L$  and  $V_L$  (Fig. 8-55). *Ans.*  $I_L = 1 \text{ A}$ ;  $V_L = 40 \text{ V}$ ; ( $R_{Th} = 6.67 \Omega$ ;  $V_{Th} = 46.7 \text{ V}$ )

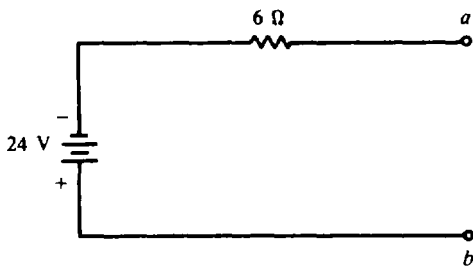8.35 A voltage source has 24 V in series with 6 Ω (Fig. 8-56a). Draw the equivalent current source circuit. *Ans.* See Fig. 8-56b.




(a)

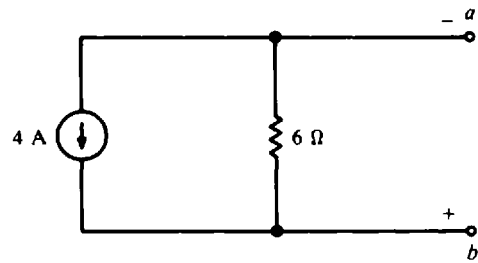


(b)

Fig. 8-56

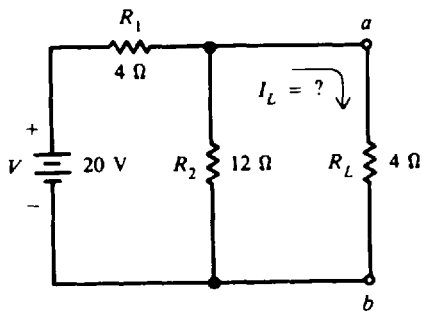8.36 Show the Norton equivalent circuit (Fig. 8-57a) and find  $I_L$ . *Ans.* See Fig. 8-57b.  $I_L = 2.14 \text{ A}$ .



(a)

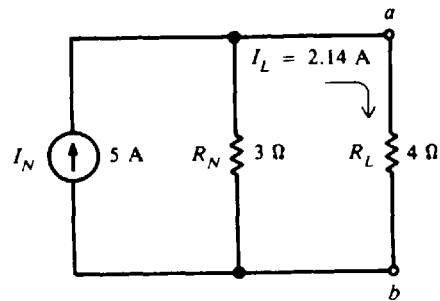

(b)

Fig. 8-57

8.37 Find the Norton equivalent to the circuits of Fig. 8-58a, b, and c. (These are the same circuits for which you found the Thevenin equivalents in Prob. 8.29.)

*Ans.* (a)  $I_N = 4 \text{ A}$ ;  $R_N = 1.2 \Omega$ ; (b)  $I_N = 1.5 \text{ A}$ ;  $R_N = 1.6 \Omega$ ; (c)  $I_N = 1.5 \text{ A}$ ;  $R_N = 0.89 \Omega$

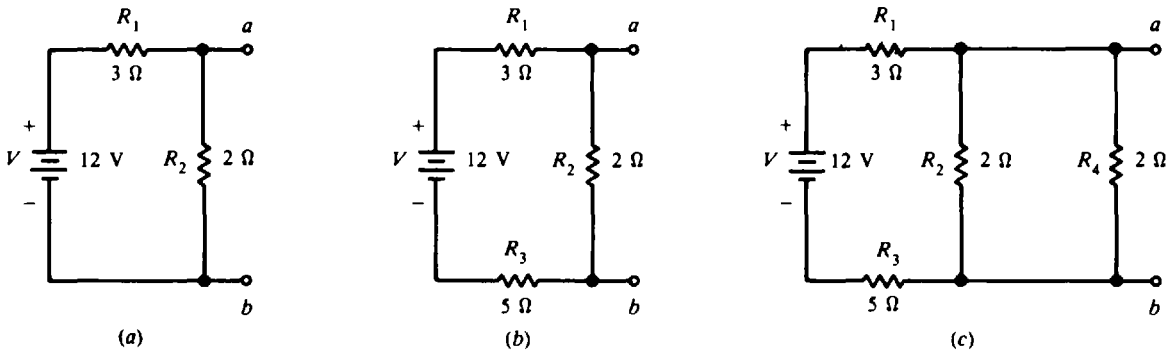


Fig. 8-58

**8.38** Add a resistor load  $R_L$  of  $5\ \Omega$  between terminals  $a$  and  $b$  to each circuit of Prob. 8.37. Calculate the load current  $I_L$  and load voltage  $V_L$ . Check your answers with those for Prob. 8.30.  
 Ans. (a)  $I_L = 0.77\ \text{A}$ ;  $V_L = 3.87\ \text{V}$ ; (b)  $I_L = 0.36\ \text{A}$ ;  $V_L = 1.82\ \text{V}$ ; (c)  $I_L = 0.23\ \text{A}$ ;  $V_L = 1.13\ \text{V}$

**8.39** Show the Thevenin equivalent (Fig. 8-59) and calculate  $V_L$ .  
 Ans.  $R_{Th} = 3\ \Omega$ ;  $V_{Th} = 22.5\ \text{V}$ ;  $V_L = 18\ \text{V}$

**8.40** In Fig. 8-59, solve for  $V_L$  by superposition.  
 Ans.  $V_L = 18\ \text{V}$  ( $I_{L, v_1} = 1\ \text{A}$ ,  $I_{L, v_2} = 0.5\ \text{A}$ ,  $I_L = 1.5\ \text{A}$ )

**8.41** In Fig. 8-59, solve for  $V_L$  by the Norton equivalent theorem.  
 Ans.  $V_L = 18\ \text{V}$  ( $I_N = 7.5\ \text{A}$ ,  $R_N = 3\ \Omega$ )

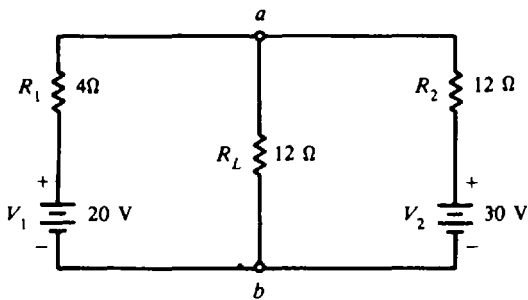


Fig. 8-59


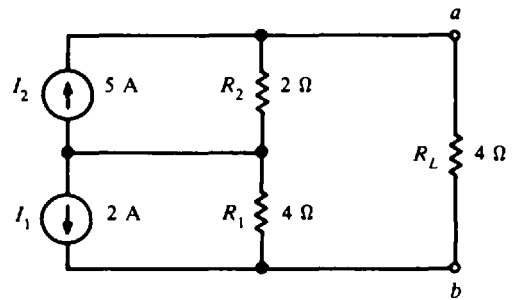



Fig. 8-60

**8.42** Find the current through the load resistor  $R_L$  (Fig. 8-60).  
 Ans.  $I_L = 0.2\ \text{A}$

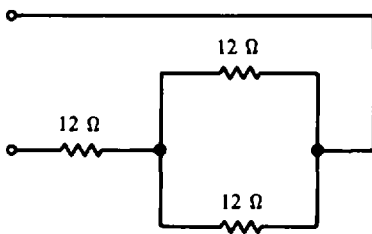**8.43** Find the total resistance of each circuit in Fig. 8-61a, b, c, and d.  
 Ans. (a)  $R_T = 18\ \Omega$ ; (b)  $R_T = 10.6\ \Omega$ ; (c)  $R_T = 3.21\ \Omega$ ; (d)  $R_T = 2.86\ \Omega$



(a)

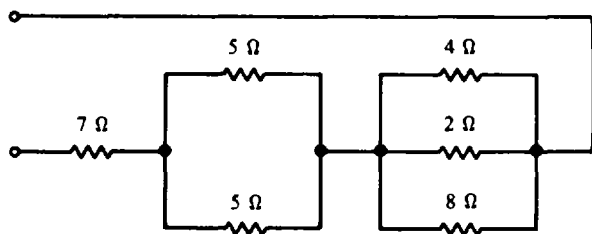

(b)

Fig. 8-61a, b





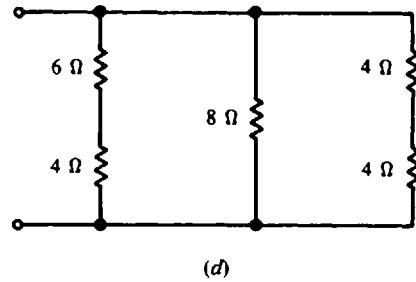
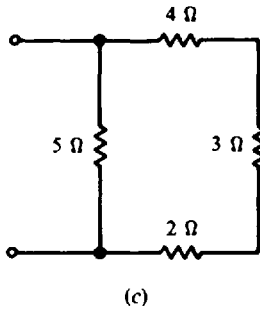


Fig. 8-61c, d

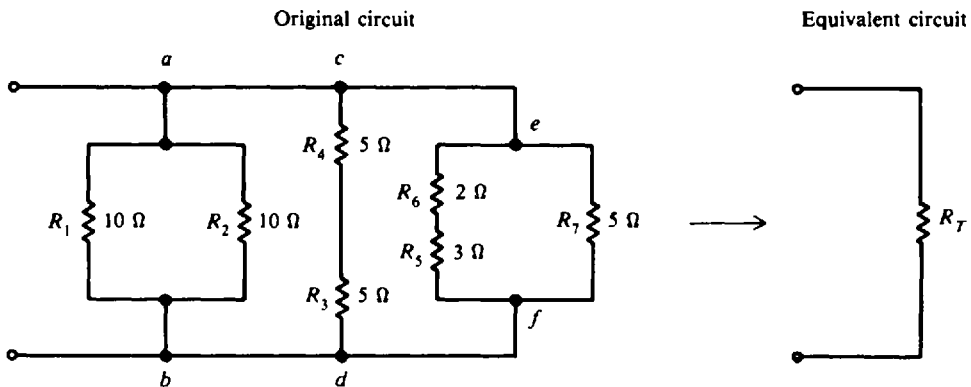8.44 Find the total resistance  $R_T$  (Fig. 8-62). *Ans.*  $R_T = 1.43 \Omega$



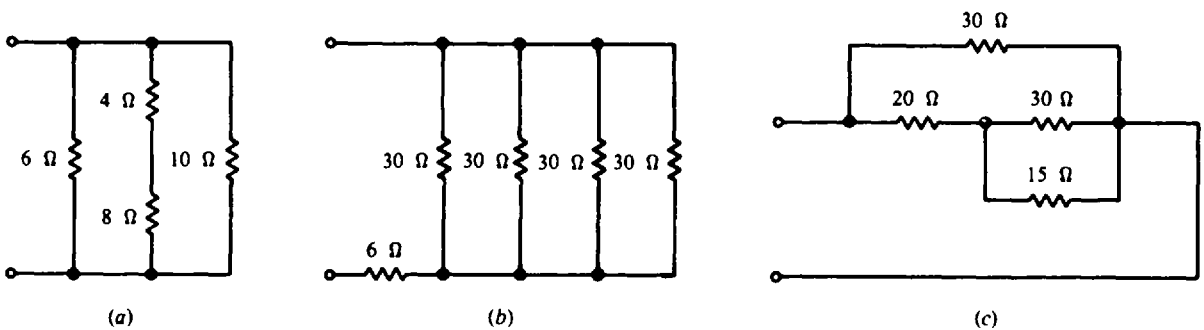8.45 Find the equivalent resistance of each resistance configuration (Fig. 8-63a, b, and c).  
*Ans.* (a)  $R_T = 2.86 \Omega$ ; (b)  $R_T = 13.5 \Omega$ ; (c)  $R_T = 15 \Omega$



8.46 For the circuit (Fig. 8-64), find  $R_T$ ,  $I_1$ ,  $I_2$ , and  $I_3$ .  
*Ans.*  $R_T = 10 \Omega$ ;  $I_1 = 15 \text{ A}$ ;  $I_2 = 10 \text{ A}$ ;  $I_3 = 5 \text{ A}$

8.47 Find the total resistance of the circuit (Fig. 8-65). *Ans.*  $R_T = 30 \Omega$

8.48 Find the total resistance of the circuit in Fig. 8-65 if the  $60\text{-}\Omega$  resistor were to burn out and open.  
*Ans.*  $R_T = 60 \Omega$

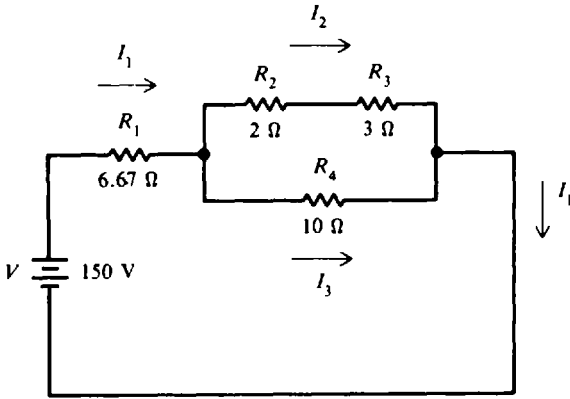


Fig. 8-64

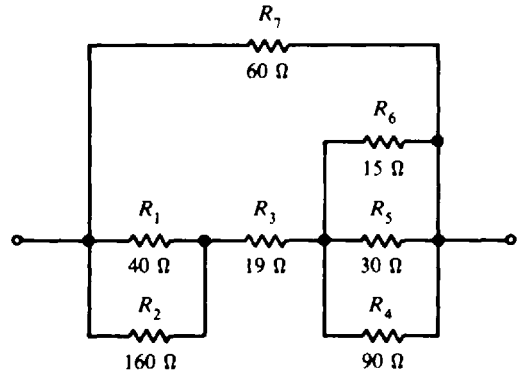


Fig. 8-65

- 8.49 An unknown resistance is to be checked by the Wheatstone bridge circuit (Fig. 8-66). When  $R_3$  is adjusted for  $54 \Omega$ , there is zero deflection on the galvanometer. Find  $R_x$  and each voltage.  
 Ans.  $R_x = 1080 \Omega$ ;  $V_x = V_1 = 20 \text{ V}$ ;  $V_2 = V_3 = 1 \text{ V}$

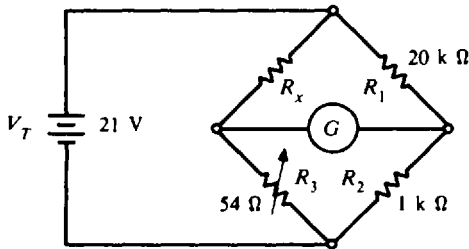


Fig. 8-66

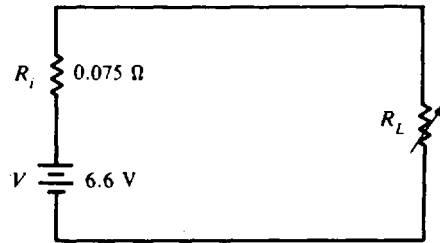


Fig. 8-67

- 8.50 What load resistance  $R_L$  will produce maximum power at the load (Fig. 8-67) and what is the value of that power? Ans.  $R_L = 0.075 \Omega$ ;  $P_L = 145 \text{ W}$
- 8.51 Determine the size of the load resistor needed for maximum transfer of power (Fig. 8-68). How much power then will be dissipated by the load? Ans.  $R_L = 2.4 \Omega$ ;  $P_L = 3.75 \text{ W}$

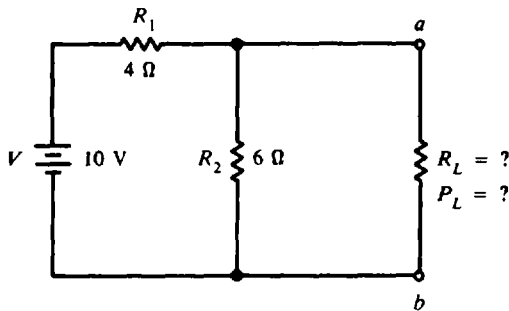


Fig. 8-68

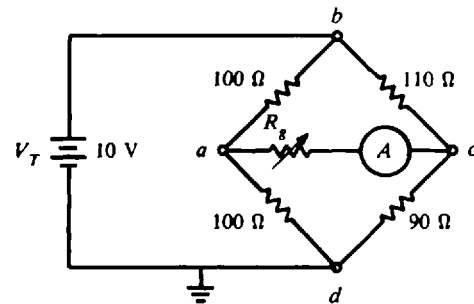


Fig. 8-69

- 8.52 The unbalanced Wheatstone bridge circuit has a resistance  $R_g$  in series with an ammeter (Fig. 8-69). Find the value of  $R_g$  so that it dissipates maximum power. (Hint: Reduce the given bridge circuit to its Thevenin equivalent.) Ans.  $R_g = 99.5 \Omega$  ( $R_g = R_{Th}$ )

8.53 Calculate the value of maximum power for the circuit in Fig. 8-69. What is the reading of the ammeter? *Ans.*  $P_L = 0.628 \text{ mW}$ ;  $I_L = 2.51 \text{ mA}$  ( $V_{Th} = 0.5 \text{ V}$ ,  $R_{Th} = 99.5 \Omega$ )

8.54 A motor is connected to a generator by two wires, each having a resistance of  $0.15 \Omega$ . The motor takes  $30 \text{ A}$  at  $211 \text{ V}$ . What is the line drop, line power loss, and generator voltage? *Ans.*  $V_l = 9 \text{ V}$ ;  $P_l = 270 \text{ W}$ ;  $V_G = 220 \text{ V}$

8.55 Fixture wiring is often done with No. 16 wire, which has a resistance of  $0.409 \Omega$  for a 100-ft length. What is the loss in voltage from the house meter to an electric broiler using  $10 \text{ A}$  and located 100 ft from the meter? What is the power loss? *Ans.*  $V_l = 8.18 \text{ V}$ ;  $P_l = 81.8 \text{ W}$

8.56 A generator is feeding current to a motor and lamp bank connected in parallel (Fig. 8-70). The feeder lines have the resistance shown. Find the voltage across the motor and lamp bank. *Ans.*  $V_M = 113.8 \text{ V}$ ;  $V_L = 112 \text{ V}$

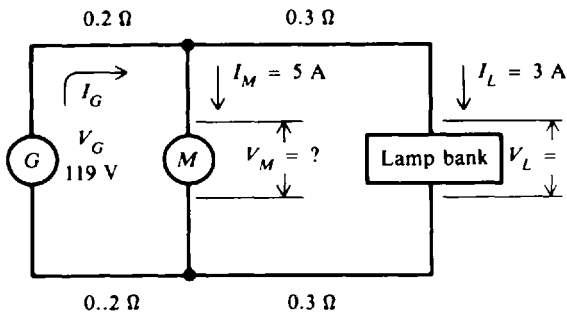


Fig. 8-70

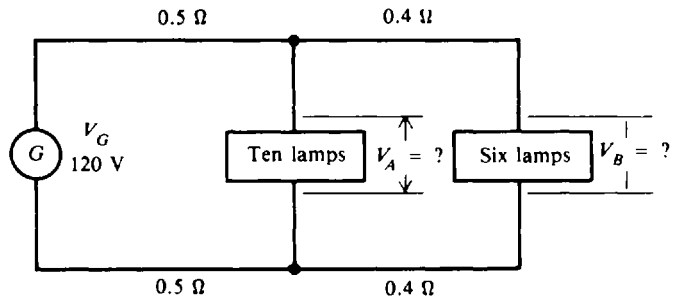


Fig. 8-71

8.57 Each lamp takes  $0.5 \text{ A}$  (Fig. 8-71). Find  $V_A$  and  $V_B$ . *Ans.*  $V_A = 112 \text{ V}$ ;  $V_B = 109.6 \text{ V}$

8.58 A 20-kW motor load is 100 ft from a 230-V source. If the allowable drop is 5 percent, what is the smallest size copper wire that can be used? *Ans.* No. 8 wire (circular-mil area = 16 500)

8.59 A load 400 ft from a generator requires  $80 \text{ A}$ . The generator voltage is  $115.6 \text{ V}$ , and the load requires  $110 \text{ V}$ . What is the smallest size wire that may be used so that no less than  $110 \text{ V}$  will be across the load? (*Note:* Not only must voltage drop be considered, but the amperage capacity of the wire must not be exceeded.) *Ans.* No. 2 wire (circular-mil area = 59 400)

8.60 Find the currents in the three lines of the Edison system with two voltage sources (Fig. 8-72). *Ans.*  $I_1 = 6.64 \text{ A}$ ;  $I_2 = 1.65 \text{ A}$ ;  $I_3 = 4.99 \text{ A}$

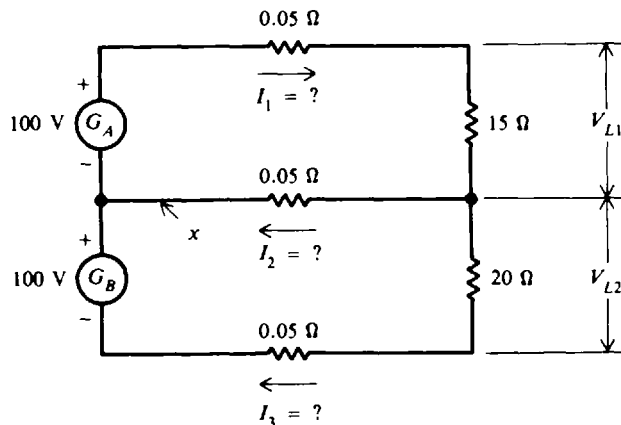


Fig. 8-72

- 8.61 If the neutral leg (Fig. 8-72) is broken at point X, possibly by a blown fuse, what is the current through the loads and the voltages across the loads? *Ans.*  $I = 5.70 \text{ A}$ ;  $V_{L1} = 85.5 \text{ V}$ ;  $V_{L2} = 114 \text{ V}$
- 8.62 If the  $15\text{-}\Omega$  resistor (Fig. 8-72) is now replaced by a  $20\text{-}\Omega$  resistor, find the new values for the current in the three feeder lines (with equal source voltages, line resistances, and load resistances, the three-wire system is balanced).  
*Ans.*  $I_1 = 4.99 \text{ A}$ ;  $I_2 = 0 \text{ A}$  (current in neutral wire is zero for a balanced three-wire system);  $I_3 = 4.99 \text{ A}$
- 8.63 If each lamp (Fig. 8-73) requires a current of  $1 \text{ A}$ , find (a) the current in each of the three lines, (b) the  $IR$  drop in each line, and (c) the voltages  $V_1$  and  $V_2$ . (d) Which line carries the heavier load?  
*Ans.* (a)  $I_1 = 4 \text{ A}$ ;  $I_2 = 2 \text{ A}$ ;  $I_3 = 2 \text{ A}$ ; (b) Positive line,  $3.2 \text{ V}$ ; neutral,  $1.6 \text{ V}$ ; negative,  $1.6 \text{ V}$ ; (c)  $V_1 = 115.2 \text{ V}$ ;  $V_2 = 120 \text{ V}$ ; (d) Positive line

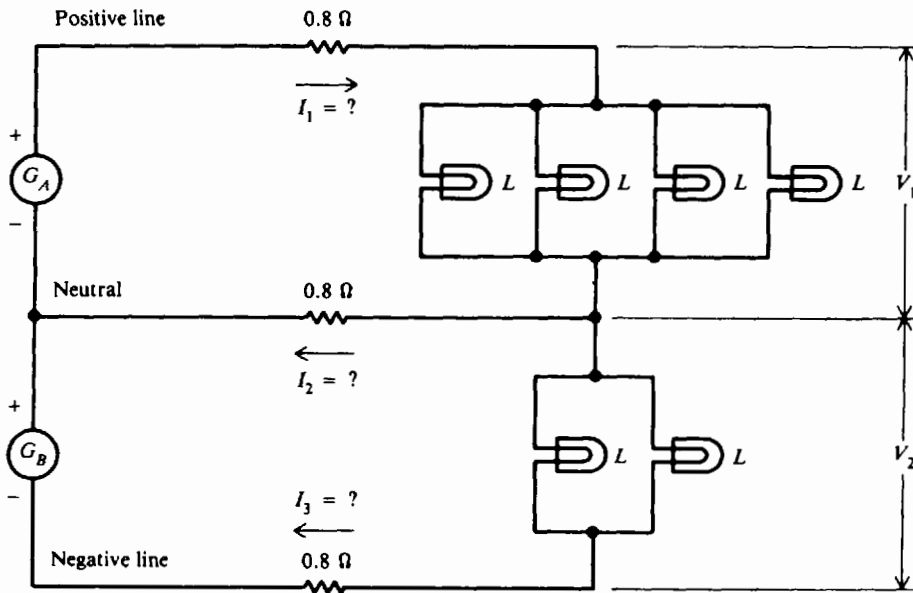


Fig. 8-73

- 8.64 In the three-wire dc distribution system (Fig. 8-74), each lamp bank consists of 50 lamps. Each lamp takes a power of  $60 \text{ W}$  when the voltage is  $115 \text{ V}$ . All three conductors are of the same size. Specify the size of copper wire to be used in order that the voltage at each bank be  $115 \text{ V}$  with all lamps turned on. *Ans.* No. 5 AWG

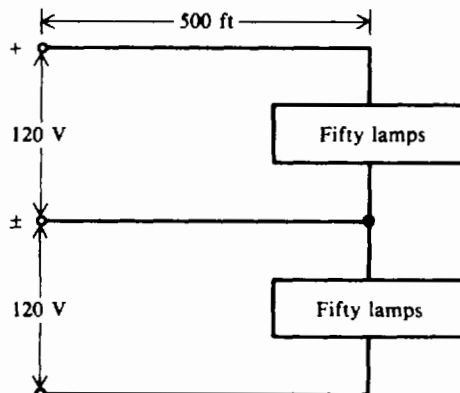


Fig. 8-74

## Magnetism and Electromagnetism

### THE NATURE OF MAGNETISM

Most electrical equipment depends directly or indirectly upon magnetism. Without magnetism the electrical world we perceive today would not exist. There are few electrical devices used today that do not make use of magnetism.

#### Natural Magnets

The phenomenon of magnetism was discovered by the Chinese about 2637 B.C. The magnets used in their primitive compasses were called *lodestones* or *leading stones*. It is now known that lodestones were crude pieces of iron ore known as *magnetite*. Since magnetite has magnetic properties in its natural state, lodestones are classified as *natural magnets*. The only other natural magnet is the earth itself. All other magnets are human-made and are known as *artificial magnets*.

#### Magnetic Fields

Every magnet has two points opposite each other which most readily attract pieces of iron. These points are called the *poles* of the magnet: the north pole and the south pole. Just as like electric charges repel each other and opposite charges attract each other, like magnetic poles repel each other and unlike poles attract each other.

A magnet clearly attracts a bit of iron because of some force that exists around the magnet. This force is called the *magnetic field*. Although it is invisible to the naked eye, its force can be shown to exist by sprinkling small iron filings on a sheet of glass or paper over a bar magnet (Fig. 9-1a). If the sheet is tapped gently, the filings will move into a definite pattern which describes the field of force around the magnet. The field seems to be made up of *lines of force* that appear to leave the magnet at the north pole, travel through the air around the magnet, and continue through the magnet to the south pole to form a *closed loop* of force. The stronger the magnet, the greater the number of lines of force and the larger the area covered by the field.

In order to visualize the magnetic field without iron filings, the field is shown as lines of force in Fig. 9-1b. The direction of the lines outside the magnet shows the path a north pole would follow in the field, repelled away from the north pole of the magnet and attracted to its south pole.

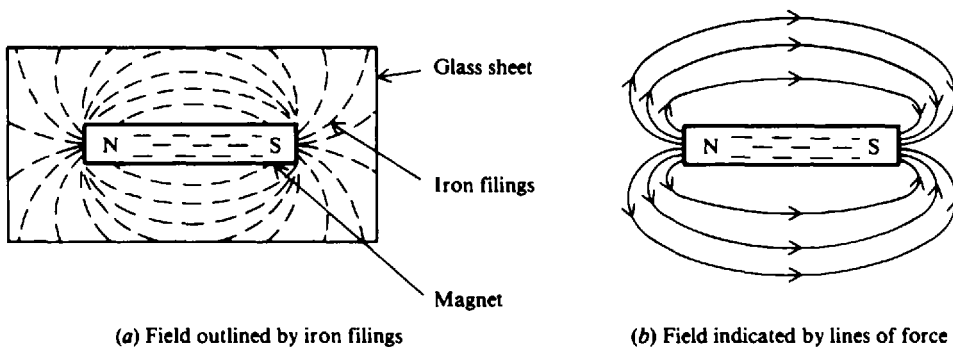


Fig. 9-1 Magnetic field of force around a bar magnet

#### Magnetic Flux $\phi$

The entire group of magnetic field lines, which flow outward from the north pole of a magnet, is called the *magnetic flux*. The symbol for magnetic flux is the Greek lowercase letter  $\phi$  (phi).

The SI unit of magnetic flux is the weber (Wb). One weber equals  $1 \times 10^8$  magnetic field lines. Since the weber is a large unit for typical fields, the microweber ( $\mu\text{Wb}$ ) is used ( $1 \mu\text{Wb} = 10^{-6} \text{Wb}$ ).

**Example 9.1** If a magnetic flux  $\phi$  has 3000 lines, find the number of microwebers.

Convert number of lines to microwebers.

$$\phi = \frac{3000 \text{ lines}}{1 \times 10^8 \text{ lines/Wb}} = \frac{3 \times 10^3}{10^8} = 30 \times 10^{-6} \text{ Wb} = 30 \mu\text{Wb} \quad \text{Ans.}$$

### Magnetic Flux Density $B$

The *magnetic flux density* is the magnetic flux per unit area of a section perpendicular to the direction of flux. The equation for magnetic flux density is

$$B = \frac{\phi}{A} \quad (9-1)$$

where  $B$  = magnetic flux density in teslas (T)

$\phi$  = magnetic flux, Wb

$A$  = area in square meters ( $\text{m}^2$ )

We see that the SI unit for  $B$  is webers per square meter ( $\text{Wb}/\text{m}^2$ ). One weber per square meter is called a *tesla*.

**Example 9.2** What is the flux density in teslas when there exists a flux of  $600 \mu\text{Wb}$  through an area of  $0.0003 \text{m}^2$ ?

Given

$$\phi = 600 \mu\text{Wb} = 6 \times 10^{-4} \text{ Wb}$$

$$A = 0.0003 \text{ m}^2 = 3 \times 10^{-4} \text{ m}^2$$

Substitute values of  $\phi$  and  $A$  in Eq. (9-1).

$$B = \frac{\phi}{A} = \frac{6 \times 10^{-4} \text{ Wb}}{3 \times 10^{-4} \text{ m}^2} = 2 \text{ T} \quad \text{Ans.}$$

## MAGNETIC MATERIALS

Magnetic materials are those materials which are attracted or repelled by a magnet and which can be magnetized themselves. Iron and steel are the most common magnetic materials. Permanent magnets are those of hard magnetic materials, such as cobalt steel, that retain their magnetism when the magnetizing field is removed. A temporary magnet is one that has *no* ability to retain a magnetized state when the magnetizing field is removed.

*Permeability* refers to the ability of a magnetic material to concentrate magnetic flux. Any material that is easily magnetized has high permeability. A measure of permeability for different materials in comparison with air or vacuum is called *relative permeability*. The symbol for relative permeability is  $\mu_r$  (mu), where the subscript  $r$  stands for *relative*.  $\mu_r$  is not expressed in units because it is a ratio of two flux densities, so the units cancel.

Classifying magnetic materials as either *magnetic* or *nonmagnetic* is based on the strong magnetic properties of iron. However, since weak magnetic materials can be important in some applications, classification includes three groups:

1. *Ferromagnetic materials*. These include iron, steel, nickel, cobalt, and commercial alloys such as alnico and Permalloy. The *ferrites* are nonmagnetic materials that have ferromagnetic properties of iron. A ferrite is a ceramic material. The permeability of ferrites is in the range of 50 to 3000. A common application is a ferrite core in the coils for RF (radio-frequency) transformers.

2. *Paramagnetic materials.* These include aluminum, platinum, manganese, and chromium. Relative permeability is slightly more than 1.
3. *Diamagnetic materials.* These include bismuth, antimony, copper, zinc, mercury, gold, and silver. Relative permeability is less than 1.

## ELECTROMAGNETISM

In 1819 a Danish scientist named Oersted discovered a relation between magnetism and electric current. He found that an electric current flowing through a conductor produced a magnetic field around that conductor. In Fig. 9-2a filings in a definite pattern of concentric rings around the conductor show the magnetic field of the current in the wire. Every section of the wire has this field of force around it in a plane perpendicular to the wire (Fig. 9-2b). The strength of the magnetic field around a conductor carrying current depends on the current. A high current will produce many lines of force extending far from the wire, while a low current will produce only a few lines close to the wire (Fig. 9-3).

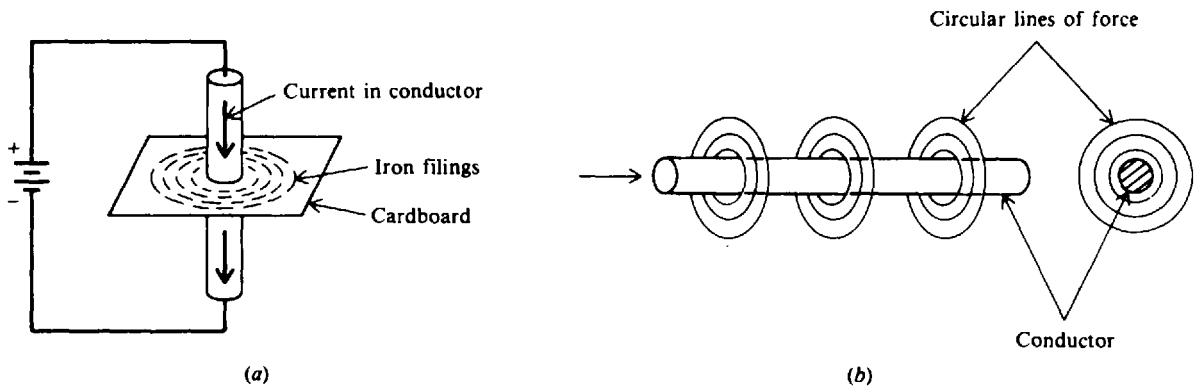


Fig. 9-2 Circular pattern of magnetic lines around current in a conductor

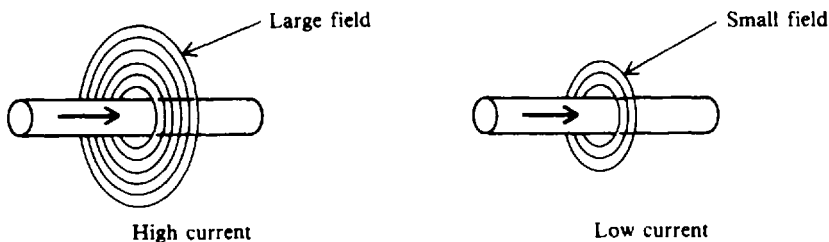


Fig. 9-3 Strength of the magnetic field depends on the amount of current

### Polarity of a Single Conductor

The *right-hand rule* is a convenient way to determine the relationship between the flow of current in a conductor (wire) and the direction of the magnetic lines of force around the conductor. Grasp the current-carrying wire in the right hand, wrapping the four fingers around the wire and extending the thumb along the wire. If the thumb points along the wire in the direction of current flow, the fingers will be pointing in the direction of the lines of force around the conductor (Fig. 9-4).

### Magnetic Fields Aiding or Canceling

In Fig. 9-5 the magnetic fields are shown for two parallel conductors with opposite directions of current. The cross in the middle of the field of the conductor in Fig. 9-5a symbolizes the back of


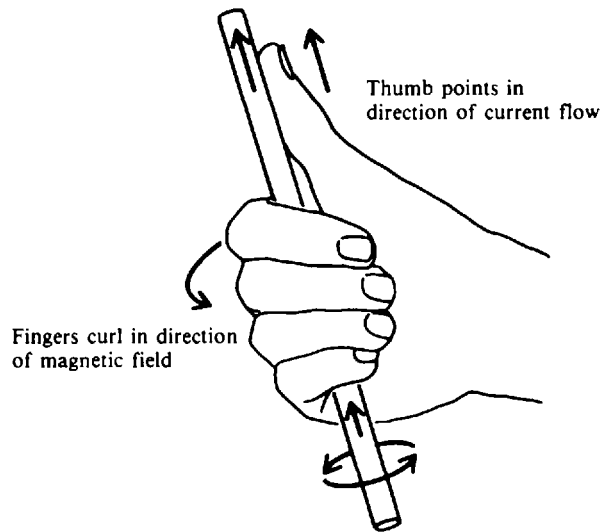


Fig. 9-4 Right-hand rule

an arrow to indicate current into the paper. (Think of it as the feathers at the end of an arrow moving away from you.) The dot (Fig. 9-5*b*) symbolizes current moving out of the paper. (In this case, it's a point of the arrow facing toward you.) By applying the right-hand rule, you determine the clockwise direction of the field of the conductor in Fig. 9-5*a* and the counterclockwise field direction of the conductor in Fig. 9-5*b*. Because the magnetic lines between the conductors are in the *same* direction, the fields *aid* to make a stronger total field. On either side of the conductors, the two fields are opposite in direction and tend to cancel each other.

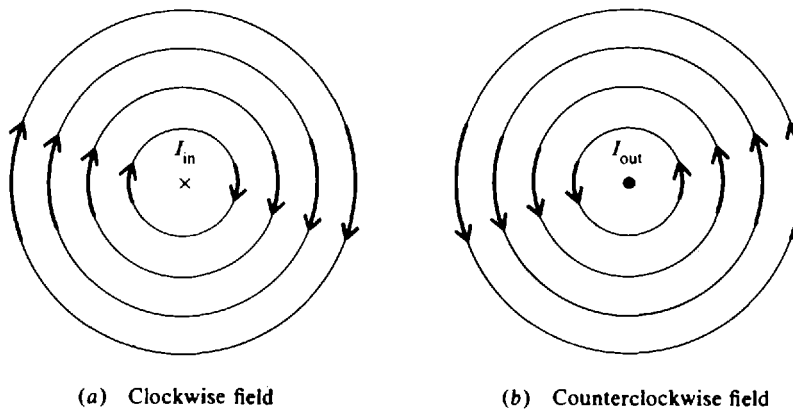

(a) Clockwise field

(b) Counterclockwise field

Fig. 9-5 Fields aiding with opposite directions of current

### Magnetic Field and Polarity of a Coil

Bending a straight conductor into the form of a single loop has two results. First, the magnetic field lines are more dense inside the loop, although the total number of lines is the same as for the straight conductor. Second, all the lines inside the loop are aiding in the same direction.

A coil of wire conductor is formed when there is more than one loop or turn. To determine the magnetic polarity of a coil, use the right-hand rule (Fig. 9-6). If the coil is grasped with the fingers of the right hand curled in the direction of current flow through the coil, the thumb points to the north pole of the coil.

Adding an iron core inside the coil increases the flux density. The polarity of the core is the same as that of the coil. The polarity depends on the direction of current flow and the direction of



winding. Current flow is from the positive side of the voltage source, through the coil, and back to the negative terminal (Fig. 9-7). The north pole is found by using the right-hand rule.

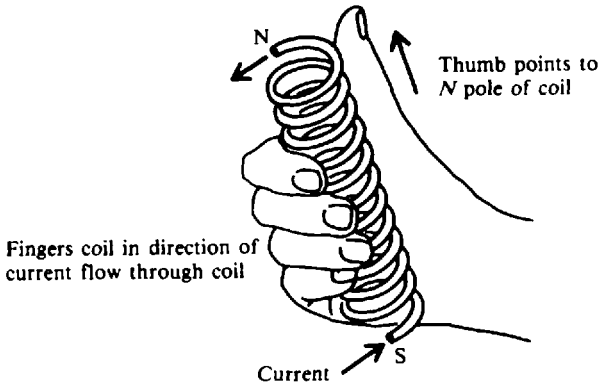


Fig. 9-6 Right-hand rule for coil of wire with several turns (solenoid)

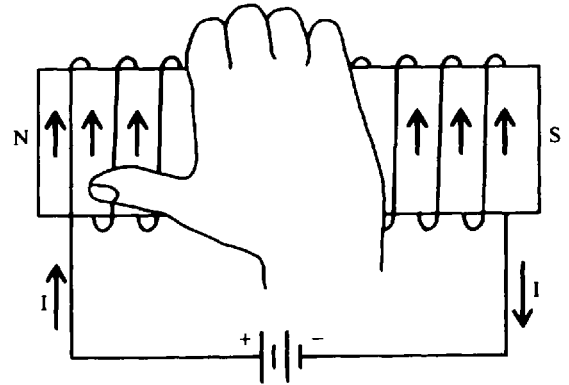


Fig. 9-7 Right-hand rule to find north pole of an electromagnet

**Example 9.3** Determine the magnetic polarity of the pictured electromagnets (Fig. 9-8) by the right-hand rule.

The correct polarities are circled. Notice that *A* has the same direction of winding and current as in Fig. 9-7. In *B*, the battery polarity is opposite from *A* to reverse the direction of current. In *C*, the direction of winding is reversed from *A*; and in *D*, it is reversed from *B*.

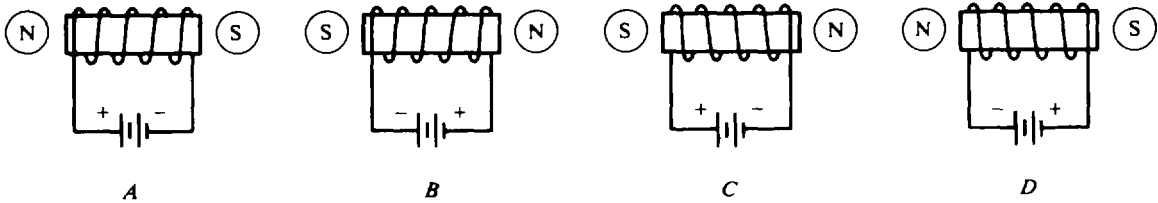


Fig. 9-8 Finding the polarity of a coil

**Electromagnet Applications**

If a bar of iron or soft steel is placed in the magnetic field of a coil (Fig. 9-9), the bar will become magnetized. If the magnetic field is strong enough, the bar will be drawn into the coil until it is approximately centered within the magnetic field.

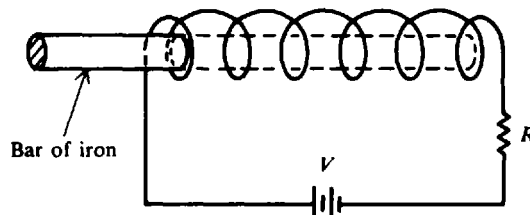


Fig. 9-9 A current-carrying coil magnetizes and attracts an iron bar placed in its field

Electromagnets are widely used in electrical devices. One of the simplest and most common applications is in a relay. When the switch *S* is closed in a relay circuit (Fig. 9-10), current flows in the coil, causing a strong magnetic field around the coil. The soft iron bar in the lamp circuit is attracted toward the right end of the electromagnet and makes contact with the conductor at *A*. A path is thus completed for current in the lamp circuit. When the switch is opened, the current flow through the electromagnet ceases and the magnetic field collapses and disappears. Since the

attraction for the soft iron bar by the electromagnet no longer exists, the iron bar is pulled away from the contact by the piece of spring steel to which it is attached. This opens the contacts at *A* and breaks the circuit for the lamp.

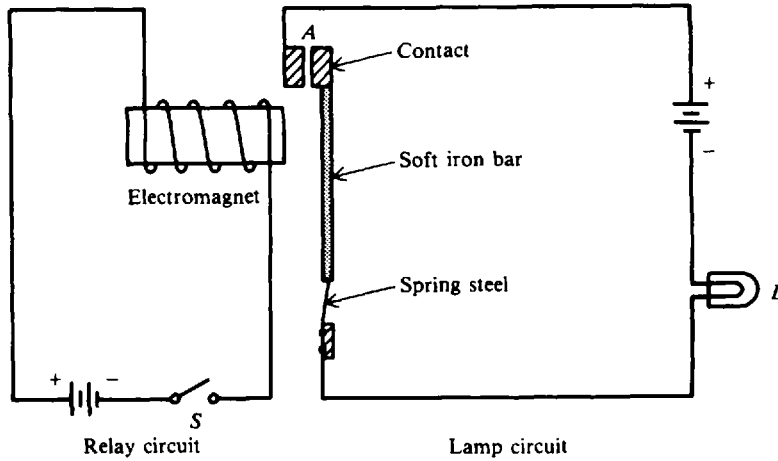


Fig. 9-10 A simple relay circuit

**MAGNETIC UNITS**

**Ampere-Turns *NI***

The strength of a magnetic field in a coil of wire depends on how much current flows in the turns of the coil. The more current, the stronger the magnetic field. Also, the more turns, the more concentrated are the lines of force. The product of the current times the number of turns of the coil, which is expressed in units called *ampere-turns* (At), is known as the *magnetomotive force* (mmf). As a formula,

$$F = \text{ampere-turns} = NI \tag{9-2}$$

where *F* = magnetomotive force, At  
*N* = number of turns  
*I* = current, A

**Example 9.4** Calculate the ampere-turns for a coil with 1500 turns and a 4-mA current.

Use Eq. (9-2) and substitute *N* = 1500 turns and *I* = 4 × 10<sup>-3</sup> A.

$$NI = 1500(4 \times 10^{-3}) = 6 \text{ At} \quad \text{Ans.}$$

**Field Intensity *H***


If a coil with a certain number of ampere-turns is stretched out to twice its original length, the intensity of the magnetic field, that is, the concentration of lines of force, will be half as great. The field intensity thus depends on how long the coil is. Expressed as an equation,

$$H = \frac{NI}{l} \tag{9-3}$$

where *H* = magnetic field intensity, ampere-turns per meter (At/m)  
*NI* = ampere-turns, At  
*l* = length between poles of the coil, m

Equation (9-3) is for a solenoid. *H* is the intensity at the center of an air core. With an iron core, *H* is the intensity through the entire core and *l* is the length or distance between poles of the iron core.

**Example 9.5** (a) Find the field intensity of a 40-turn, 10-cm-long coil, with 3 A flowing in it (Fig. 9-11a). (b) If the same coil is stretched to 20 cm, with the wire length and current remaining the same, what is the new value of field intensity (Fig. 9-11b)? (c) The 10-cm coil in part (a) with the same 3 A flowing is now wound around an iron core that is 20 cm long (Fig. 9-11c). What is the field intensity?

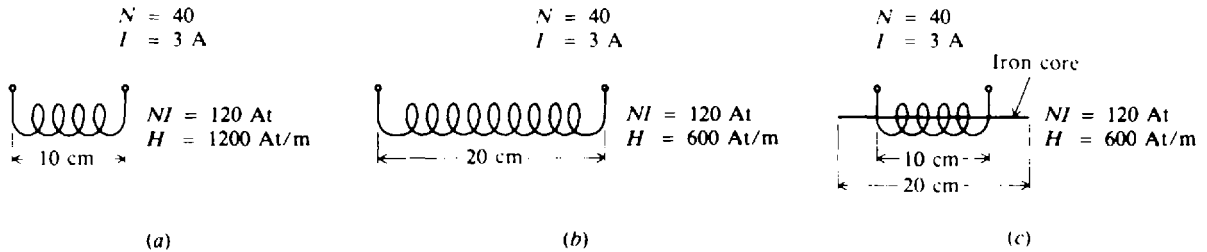

**Fig. 9-11** Relation between mmf and field intensity with same value of mmf

(a) Apply Eq. (9-3), where  $N = 40$  turns,  $l = 10 \text{ cm} = 0.1 \text{ m}$ , and  $I = 3 \text{ A}$ .

$$H = \frac{NI}{l} = \frac{40(3)}{0.1} = 1200 \text{ At/m} \quad \text{Ans.}$$

(b) The length  $l$  in Eq. (9-3) is between poles. The coil is stretched from 10 to 20 cm. Though the wire length is the same, the length between poles is  $20 \text{ cm} = 0.2 \text{ m}$ . So

$$H = \frac{40(3)}{0.2} = 600 \text{ At/m} \quad \text{Ans.}$$

Stretching out the coil to twice its original distance reduces the mmf by one-half.

(c) The length  $l$  in Eq. (9-3) is 20 cm between the poles at the ends of the iron core although the winding is 10 cm long.

$$H = \frac{40(3)}{0.2} = 600 \text{ At/m} \quad \text{Ans.}$$

Note that cases (b) and (c) have the same  $H$  value.

## BH MAGNETIZATION CURVE

The  $BH$  curve (Fig. 9-12) is used to show how much flux density  $B$  results from increasing the amount of field intensity  $H$ . This curve is for two types of soft iron plotted for typical values. It shows that soft iron number 1 increases rapidly in  $B$  with an increase in  $H$  before it develops a "knee" and becomes saturated at  $H = 2000 \text{ At/m}$ ,  $B = 0.2 \text{ T}$ . Past the knee an increase in  $H$  has little effect on the  $B$  value. Soft iron number 2 needs much more  $H$  to reach its saturation level at  $H = 5000 \text{ At/m}$ ,  $B = 0.3 \text{ T}$ . Similar curves are obtained for all magnetic materials. Air, being nonmagnetic, has a very low  $BH$  profile (Fig. 9-12).

The permeability  $\mu$  of a magnetic material is the ratio of  $B$  to  $H$ .

$$\mu = \frac{B}{H} \quad (9-4)$$

Its average value is measured at the point where the knee is first established. Figure 9-12 illustrates that the normal or average permeability is as follows:

$$\mu \text{ for soft iron number 1} = \frac{B}{H} = \frac{0.2}{2000} = 1 \times 10^{-4} (\text{T} \cdot \text{m})/\text{At}$$

$$\mu \text{ for soft iron number 2} = \frac{B}{H} = \frac{0.3}{5000} = 6 \times 10^{-5} (\text{T} \cdot \text{m})/\text{At}$$

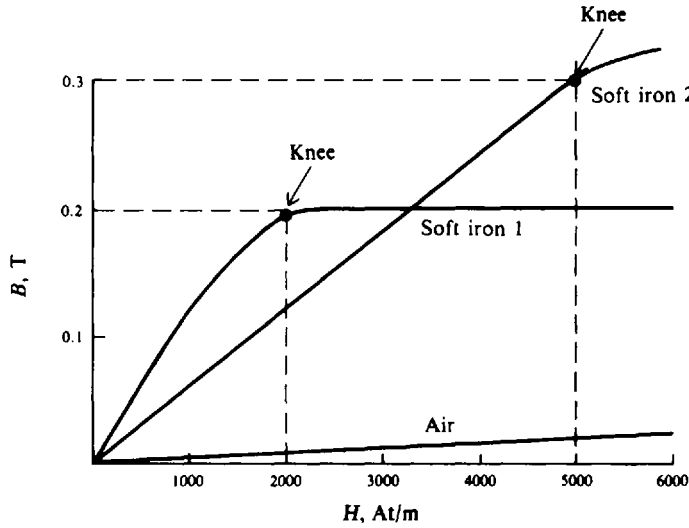


Fig. 9-12 Typical BH curve for two types of soft iron

In SI units, the permeability of air is  $\mu_0 = 4\pi \times 10^{-7}$  or  $1.26 \times 10^{-6}$ . To calculate  $\mu$ , the value of relative permeability  $\mu_r$  must be multiplied by  $\mu_0$ .

$$\mu = \mu_r \times \mu_0 \tag{9-5}$$

**Example 9.6** If a magnetic material has a relative permeability  $\mu_r$  of 100, find its permeability  $\mu$ . Use Eq. (9-5) and substitute known values.

$$\begin{aligned} \mu &= \mu_r \mu_0 = 100(1.26 \times 10^{-6}) \\ &= 126 \times 10^{-6} \text{ (T} \cdot \text{m)/At} \quad \text{Ans.} \end{aligned}$$

**Hysteresis**

When the current in a coil of wire reverses thousands of times per second, the hysteresis can cause a considerable loss of energy. *Hysteresis* means “a lagging behind”; that is, the magnetic flux in an iron core lags behind the increases or decreases of the magnetizing force.

The hysteresis loop is a series of curves that show the characteristics of a magnetic material (Fig. 9-13). Opposite directions of current result in the opposite directions of  $+H$  and  $-H$  for field intensity. Similarly, opposite polarities are shown for flux density as  $+B$  or  $-B$ . The current starts at the center 0 (zero) when the material is unmagnetized. The dotted line is recognized as the magnetization curve illustrated in Fig. 9-12. Positive  $H$  values increase  $B$  to saturation at  $+B_{max}$ . Next  $H$  decreases to zero, but  $B$  drops to the value of  $B_r$  because of hysteresis. The current that produced the original magnetization now is reversed so that  $H$  becomes negative.  $B$  drops to zero and continues to  $-B_{max}$ . Then as the  $-H$  values decrease,  $B$  is reduced to  $-B_r$  when  $H$  is zero. Now with a positive swing of current,  $H$  becomes positive, producing saturation at  $+B_{max}$  again. The hysteresis loop is now completed. The curve doesn't return to zero at the center because of hysteresis.

The value of  $+B_r$  or  $-B_r$ , which is the flux density remaining after the magnetizing force is zero ( $H = 0$ ), is called the *retentivity* of a magnetic material. The value of  $-H_c$ , which is the magnetizing force that must be applied in the reverse direction to reduce the flux density to zero ( $B = 0$ ), is called the *coercive force* of the material.

The larger the area enclosed by the hysteresis loop, the greater the hysteresis loss.

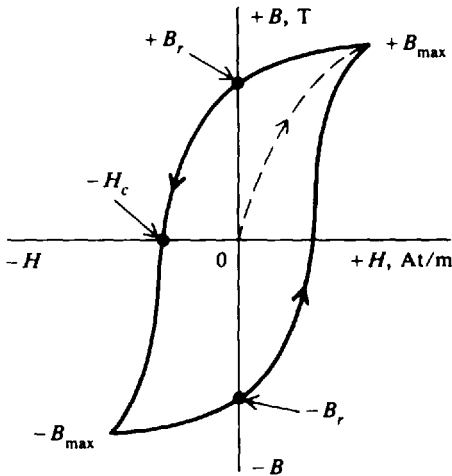


Fig. 9-13 Hysteresis loop for magnetic materials

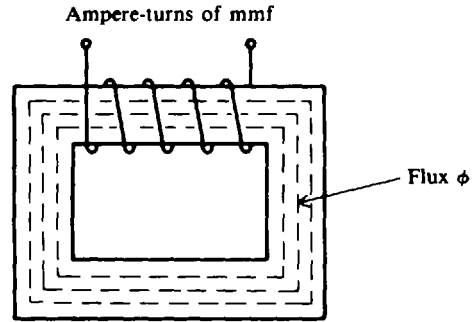


Fig. 9-14 Magnetic circuit with closed iron path

**MAGNETIC CIRCUITS**

A magnetic circuit can be compared with an electric current in which an emf produces a current flow. Consider a simple magnetic circuit (Fig. 9-14). The ampere-turns  $NI$  of the magnetomotive force produce the magnetic flux  $\phi$ . Therefore, the mmf compares to emf or voltage and the flux  $\phi$  compares to current. Opposition to the production of flux in a material is called its *reluctance*, which corresponds to resistance.

**Reluctance  $\mathcal{R}$**

The symbol for reluctance is  $\mathcal{R}$ . Reluctance is inversely proportional to permeability. Iron has high permeability and therefore low reluctance. Air has low permeability and hence high reluctance.

Different forms of electromagnets generally have different values of reluctance (Fig. 9-15). The air gap is the air space between the poles of a magnet. Since air has high reluctance, the size of the air gap affects the value of reluctance. The magnetic circuit in Fig. 9-15a has widely spaced poles in air so it has a high reluctance. In Fig. 9-15b the reluctance has been decreased by bringing the two poles closer together. The field between N and S is more intense, assuming the same number of ampere-turns in the coils. In Fig. 9-15c the air gap is smaller than that in Fig. 9-15b so the reluctance is lower. In Fig. 9-15d there is no air gap in the toroid-shaped core so its reluctance is very low.

The shorter the air gap, the stronger the field in the gap. Since air is not magnetic and thus is unable to concentrate magnetic lines, a larger air gap only provides more space for the magnetic lines to spread out.

**Ohm's Law for Magnetic Circuits**

Ohm's law for magnetic circuits, corresponding to  $I = V/R$ , is

$$\phi = \frac{\text{mmf}}{\mathcal{R}} \tag{9-6}$$

where  $\phi$  = magnetic flux, Wb  
 mmf = magnetomotive force, At  
 $\mathcal{R}$  = reluctance, At/Wb

Reluctance can be expressed as an equation as follows:

$$\mathcal{R} = \frac{l}{\mu A} \tag{9-7}$$

where  $\mathcal{R}$  = reluctance, At/Wb  
 $l$  = length of coil, m  
 $\mu$  = permeability of magnetic material, (T · m)/At  
 $A$  = cross-sectional area of coil, m<sup>2</sup>

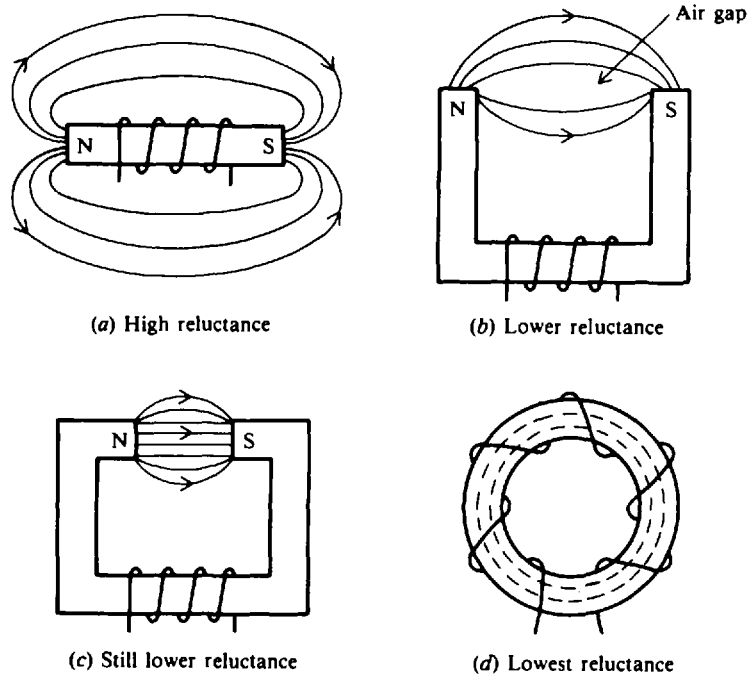


Fig. 9-15 Different physical forms of electromagnets

**Example 9.7** A coil has an mmf of 500 At and a reluctance of  $2 \times 10^6$  At/Wb. Compute the total flux  $\phi$ . Write Ohm's law for magnetic circuits and substitute given values.

$$\begin{aligned} \phi &= \frac{\text{mmf}}{\mathcal{R}} && (9-6) \\ &= \frac{500 \text{ At}}{2 \times 10^6 \text{ At/Wb}} = 250 \times 10^{-6} \text{ Wb} = 250 \mu\text{Wb} && \text{Ans.} \end{aligned}$$

**Example 9.8** Starting with Eq. (9-6), show that  $\mathcal{R} = l/\mu A$ , which is Eq. (9-7).

$$\phi = \frac{\text{mmf}}{\mathcal{R}} \tag{9-6}$$

Also

$$\phi = BA \tag{9-1}$$

Substitute  $B = \mu H$  [Eq. (9-4)] and  $H = NI/l$  [Eq. (9-3)] to obtain

$$\phi = BA = \mu HA = \frac{\mu NIA}{l} = NI \frac{\mu A}{l} = \frac{NI}{l/\mu A}$$

But Eq. (9-6) tells us that

$$\phi = \frac{\text{mmf}}{\mathcal{R}} = \frac{NI}{\mathcal{R}}$$

By comparing denominators of the two expressions for  $\phi$  with the same numerator, we see that

$$\mathcal{R} = \frac{l}{\mu A}$$

which is Eq. (9-7).

## ELECTROMAGNETIC INDUCTION

In 1831 Michael Faraday discovered the principle of electromagnetic induction. It states that if a conductor "cuts across" lines of magnetic force, or if lines of force cut across a conductor, an emf, or voltage, is induced across the ends of the conductor. Consider a magnet with its lines of force extending from the north to the south pole (Fig. 9-16). A conductor *C*, which can be moved between the poles, is connected to a galvanometer *G* used to indicate the presence of an emf. When the conductor is *not* moving, the galvanometer shows zero emf. If the wire conductor is moving *outside* the magnetic field at position 1, the galvanometer will still show zero. When the conductor is moved to the left to position 2, it cuts across the lines of magnetic force and the galvanometer pointer will deflect to *A*. This indicates that an emf was induced in the conductor because lines of force were cut. In position 3, the galvanometer pointer swings back to zero because no lines of force are being cut. Now reverse the direction of the conductor by moving it right through the lines of force back to position 1. During this movement, the pointer will deflect to *B*, showing that an emf has again been induced in the wire, but in the *opposite* direction. If the wire is held stationary in the middle of the field of force at position 2, the galvanometer reads zero. If the conductor is moved up or down *parallel* to the lines of force so that none is cut, no emf will be induced.

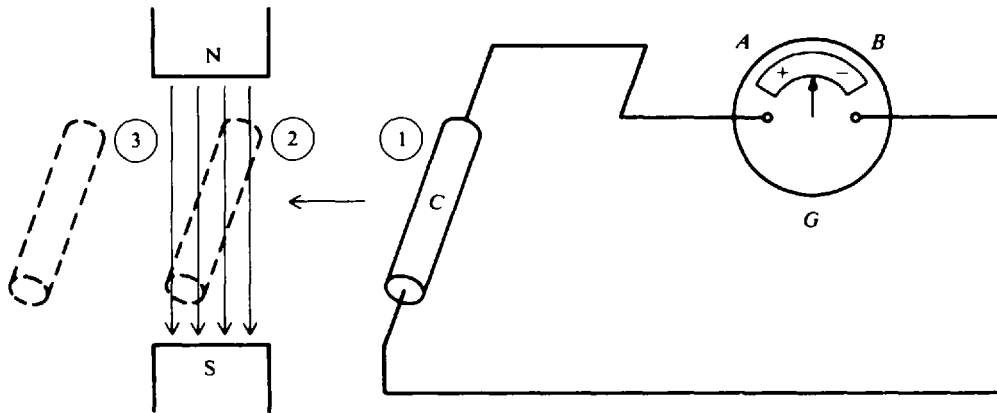


Fig. 9-16 When a conductor cuts lines of force, an emf is induced in the conductor

In summary,

1. When lines of force are cut by a conductor or lines of force cut a conductor, an emf, or voltage, is induced in the conductor.
2. There must be relative motion between the conductor and the lines of force in order to induce an emf.
3. Changing the direction of cutting will change the direction of the induced emf.

The most important application of relative motion between conductor and magnetic field is made in electric generators. In a dc generator, fixed electromagnets are arranged in a cylindrical housing. Many conductors in the form of a coil are rotated on a core within the magnetic field so that these conductors are continually cutting the lines of force. As a result, voltage is induced in each of the conductors. Since the conductors are in series in the coil, the induced voltages add together to produce the output voltage of the generator.

### Faraday's Law of Induced Voltage

The value of the induced voltage depends upon the number of turns of a coil and how fast the conductor cuts across the lines of force or flux. Either the conductor or the flux can move. The

equation to calculate the value of the induced voltage is

$$v_{\text{ind}} = N \frac{\Delta\phi}{\Delta t} \quad (9-8)$$

where  $v_{\text{ind}}$  = induced voltage, V  
 $N$  = number of turns in a coil  
 $\Delta\phi/\Delta t$  = rate at which the flux cuts across the conductor, Wb/s

From Eq. (9-8) we see that  $v_{\text{ind}}$  is determined by three factors:

1. *Amount of flux.* The more lines of force that cut across the conductor, the higher the value of induced voltage.
2. *Number of turns.* The more turns in a coil, the higher the induced voltage.
3. *Time rate of cutting.* The faster the flux cuts a conductor or the conductor cuts the flux, the higher the induced voltage because more lines of force cut the conductor within a given period of time.

**Example 9.9** The flux of an electromagnet is 6 Wb. The flux increases uniformly to 12 Wb in a period of 2 s. Calculate the voltage induced in a coil that has 10 turns if the coil is stationary in the magnetic field. Write down known values.

$$\Delta\phi = \text{change in flux} = 12 \text{ Wb} - 6 \text{ Wb} = 6 \text{ Wb}$$

$$\Delta t = \text{change in time corresponding to the increase in flux} = 2 \text{ s}$$

Then 
$$\frac{\Delta\phi}{\Delta t} = \frac{6}{2} = 3 \text{ Wb/s}$$

We are given that  $N = 10$  turns. Substitute values into Eq. (9-8) and solve for  $v_{\text{ind}}$ .

$$v_{\text{ind}} = N \frac{\Delta\phi}{\Delta t} = 10(3) = 30 \text{ V} \quad \text{Ans.}$$

**Example 9.10** In Example 9.9 what is the value of induced voltage if the flux remains at 6 Wb after 2 s? Since there is no change in flux,  $\Delta\phi = 0$ . Using Eq. (9-8),

$$v_{\text{ind}} = N \frac{\Delta\phi}{\Delta t} = N \frac{0}{\Delta t} = N0 = 0 \text{ V} \quad \text{Ans.}$$

That no voltage is induced in Example 9.10 confirms the principle that there must be relative motion between the conductor and the flux in order to induce a voltage. A magnetic field whose flux is increasing or decreasing in strength is, in effect, moving relative to any conductors in the field.

### Lenz's Law

The polarity of the induced voltage is determined by Lenz's law. The induced voltage has the polarity that *opposes* the change causing the induction. When a current flows as a result of an induced voltage, this current sets up a magnetic field about the conductor such that this conductor magnetic field reacts with the external magnetic field, producing the induced voltage to oppose the change in the external magnetic field. If the external field increases, the conductor magnetic field of the induced current will be in the opposite direction. If the external field decreases, the conductor magnetic field will be in the same direction, thus sustaining the external field.

**Example 9.11** A permanent magnet is moved into a coil and causes an induced current to flow in the coil circuit (Fig. 9-17a). Determine the polarity of the coil and the direction of the induced current.

By use of Lenz's law, the left end of the coil must be the N pole to oppose the motion of the magnet. Then the direction of the induced current can be determined by the right-hand rule. If the right thumb points to the left for the N pole, the fingers coil around the direction of current (Fig. 9-17b).



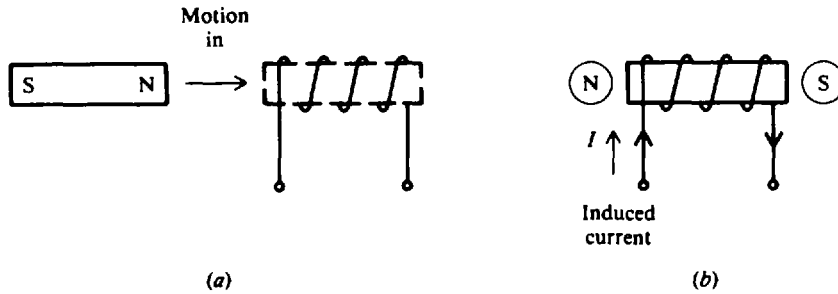


Fig. 9-17 Illustration of Lenz's law

**INTERNATIONAL SYSTEM OF UNITS**

Table 9-1 lists the SI units for magnetism.

**Table 9-1 International System of Units for Magnetism**

Term	Symbol	Unit (Abbreviation)
Flux	$\phi$	Weber (Wb)
Flux density	$B$	Weber per square meter ( $\text{Wb}/\text{m}^2$ ) = tesla (T)
Potential	mmf	Ampere-turn (At)
Field intensity	$H$	Ampere-turn per meter ( $\text{At}/\text{m}$ )
Reluctance	$\mathcal{R}$	Ampere-turn per weber ( $\text{At}/\text{Wb}$ )
Relative permeability	$\mu_r$	None, pure number
Permeability	$\mu = \mu_r \times 1.26 \times 10^{-6}$	$B/H$ = tesla per ampere-turn per meter [ $(\text{T} \cdot \text{m})/\text{At}$ ]

**Solved Problems**

9.1 Match the term in column 1 with its closest meaning in column 2.

- | Column 1                 | Column 2                                     |
|--------------------------|--|
| 1. One weber             | (a) $B/\dot{H}$                              |
| 2. Lenz's law            | (b) Ceramic material                         |
| 3. Two north poles       | (c) Force of repulsion                       |
| 4. $v_{\text{ind}}$      | (d) Inversely proportional to permeability   |
| 5. Field intensity       | (e) $H/B$                                    |
| 6. Electric generator    | (f) $1 \times 10^8$ lines of force           |
| 7. Relative permeability | (g) Application of electromagnetic induction |
| 8. High permeability     | (h) $N \frac{\Delta\phi}{\Delta t}$          |
| 9. Ferrite               | (i) Respect to air                           |
| 10. Reluctance           | (j) Polarity of induced voltage              |
|                          | (k) $NI$                                     |
|                          | (l) Force of attraction                      |
|                          | (m) $\text{At}/\text{m}$                     |
|                          | (n) Easily magnetized                        |

Ans. 1. (f) 2. (j) 3. (c) 4. (h) 5. (m) 6. (g) 7. (i) 8. (n) 9. (b) 10. (d)

9.2 Describe the action that takes place when two like poles and when two unlike poles are placed near each other.

See Fig. 9-18. If the N poles of two magnets are placed near each other (Fig. 9-18a), the lines of force emanating from the N poles have the same direction and thus repel each other. This force of repulsion tends to move the two magnets apart. On the other hand, if the N and the S poles of two magnets are placed near each other (Fig. 9-18b), the adjacent lines of force are opposite in direction and they link together to form long loops. These long, continuous lines tend to contract and this force of attraction pulls the two magnets together. So fields from like poles repel, tending to push the magnets apart, while fields from unlike poles attract, tending to pull the magnets together.

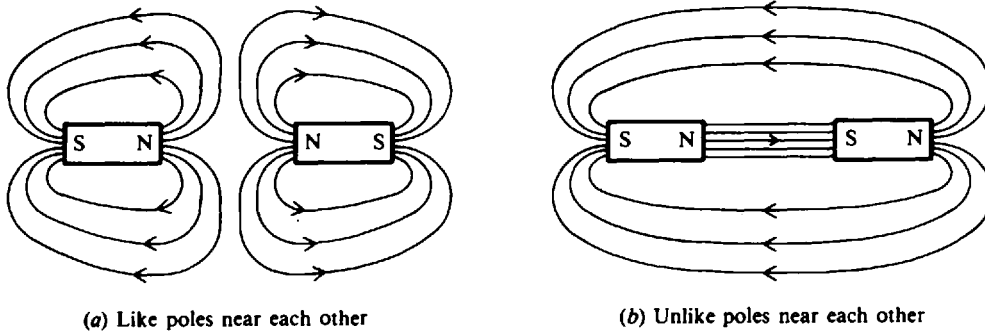


Fig. 9-18 Interaction of magnetic poles

9.3 An example of magnetic attraction is the navigator's compass and the earth's magnetic field. The earth itself is a huge natural magnet. The earth has its magnetic south (S) pole near the geographic north (N) pole, and its magnetic north (N) pole near the geographic south (S) pole. The compass needle is a long, thin permanent magnet that is free to move on its central bearing point. The compass needle always lines up its magnetic field with the magnetic field of the earth, with its north end pointing toward the earth's magnetic south pole. The geographic N pole is located near the magnetic S pole. Show how a magnetic compass is used to indicate direction.

See Fig. 9-19.

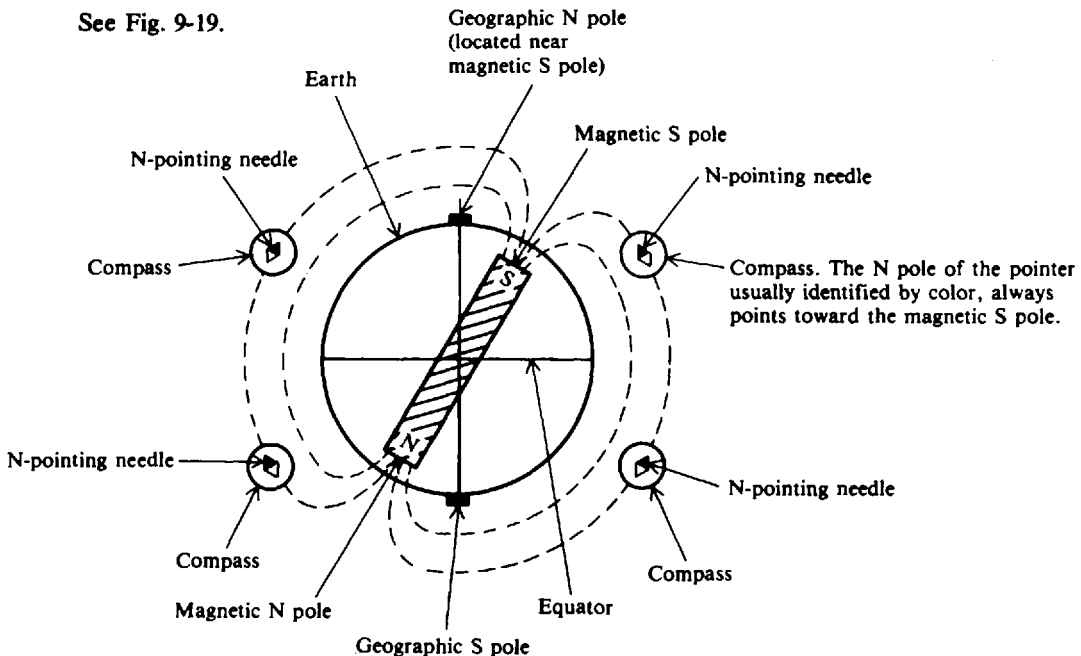


Fig. 9-19 The earth as a magnet

9.4 Would 1 A flowing through a 2-m length of wire made into a single loop produce more, the same, or less mmf if it were wound into a coil 2 cm in diameter and 4 cm long?

Basically flux is produced by current flowing in a wire. The mmf produced is the product of the current times the number of turns of the coil. Since 1 A is flowing through a coil of 1 turn in both cases, though the physical configuration of the coils is different, the mmf is the same at 1 At.

- 9.5 (a) Consider a coil with an air core (Fig. 9-20a). The coil is 5 cm long and has 8 turns. When the switch is closed, a current of 5 A flows in it. Find the mmf and  $H$ .  
 (b) If an iron core were slipped into the coil (Fig. 9-20b), what is now the mmf and  $H$ ? What qualitative changes take place?  
 (c) The coil length remains the same, but the iron core is lengthened to 10 cm (Fig. 9-20c). What are the values of the mmf and  $H$ ?

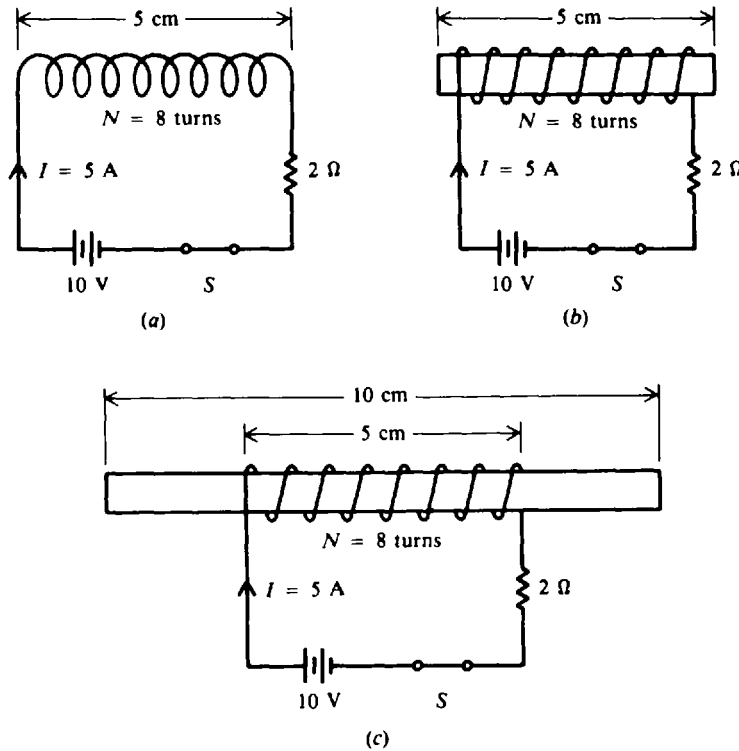


Fig. 9-20 Relation between mmf and  $H$

(a)  $F = \text{mmf} = NI$  (9-2)

$= (8 \text{ turns})(5 \text{ A}) = 400 \text{ At}$  Ans.

$H = \frac{NI}{l}$  (9-3)

$= \frac{400 \text{ At}}{5 \times 10^{-2} \text{ m}} = 8000 \text{ At/m}$  Ans.

(b) Since the quantities  $N$ ,  $I$ , and  $l$  haven't changed, the values of mmf and  $H$  remain the same as in part (a). So

$\text{mmf} = 400 \text{ At}$  Ans.

$H = 8000 \text{ At/m}$  Ans.

What changes is a large increase in flux density  $B$ . Suppose the iron core in air produced 50 lines of force. With the core placed into an energized coil, the number of lines in the core area might

be 250,000. In this case, iron would have a permeability 5000 times that of air. Therefore, the use of an iron core instead of an air core increases the effectiveness of the magnet several thousand times. For this reason most electromagnets are made with iron cores.

- (c) The lengthening of the iron core doesn't change the ampere-turns of the coil, so

$$\text{mmf} = 400 \text{ At} \quad \text{Ans.}$$

However, with a longer iron core that is twice the initial length (10 cm = 2 × 5 cm), the field intensity is reduced by half.

$$H = \frac{1}{2} \times 8000 \text{ At/m} = 4000 \text{ At/m} \quad \text{or} \quad H = \frac{NI}{l} = \frac{400}{0.1} = 4000 \text{ At/m} \quad \text{Ans.}$$

- 9.6 An iron ring has a mean circumferential length of 40 cm and a cross-sectional area of 1 cm<sup>2</sup>. It is wound uniformly with 500 turns of wire. Measurements made with a search coil around the ring show that the current in the windings is 0.06 A and the flux in the ring is 6 × 10<sup>-6</sup> Wb. Find the flux density *B*, field intensity *H*, permeability  $\mu$ , and relative permeability  $\mu_r$ .

*B* is found by using Eq. (9-1).

$$B = \frac{\phi}{A} = \frac{6 \times 10^{-6} \text{ Wb}}{10^{-4} \text{ m}^2} = 6 \times 10^{-2} \text{ T} \quad \text{Ans.}$$

*H* is found by using Eq. (9-3)

$$H = \frac{NI}{l} = \frac{500 \times 0.06}{0.4} = 75 \text{ At/m} \quad \text{Ans.}$$

$\mu$  is found from Eq. (9-4).

$$\mu = \frac{B}{H} = \frac{6 \times 10^{-2}}{75} = 8 \times 10^{-4} (\text{T} \cdot \text{m})/\text{At} \quad \text{Ans.}$$

$\mu_r$  is found by Eq. (9-5).

$$\begin{aligned} \mu &= \mu_r \mu_0 \\ \mu_r &= \mu / \mu_0 = \frac{8 \times 10^{-4}}{1.26 \times 10^{-6}} = 635 \quad \text{Ans.} \end{aligned}$$

The relative permeability is a pure number that has no unit of measurement.

- 9.7 Hysteresis loops of three different magnetic materials are shown in Fig. 9-21. Rank them in order from least to most hysteresis loss.

The smaller the area enclosed by the hysteresis loop, the lower the hysteresis loss. Hysteresis loss is likened to magnetic friction that must be overcome in magnetizing a material. Curve *B*, having the smallest area, has the least hysteresis loss. Loop *B* is characteristic of a temporary-magnet material. The coercive force is very small and hysteresis loss would be negligible. Next in area size is loop *A*, which is typical of a relatively permanent magnet material. And loop *C* with the largest area has the highest loss. This rectangular-shaped curve typifies permanent-magnet material, such as alnico.

- 9.8 A core of annealed steel with a *B* of 0.72 T has a permeability  $\mu$  of 8 × 10<sup>-3</sup> (T · m)/At. If the length of the coil is 20 cm and the area of the core is 3 cm<sup>2</sup>, find the reluctance of the path.

Given are  $l = 20 \text{ cm} = 0.2 \text{ m}$ ,  $A = 3 \text{ cm}^2 = 3 \times 10^{-4} \text{ m}^2$ ,  $\mu = 8 \times 10^{-3} (\text{T} \cdot \text{m})/\text{At}$ . Substitute these values in the formula for reluctance.

$$\begin{aligned} \mathcal{R} &= \frac{l}{\mu A} && (9-7) \\ &= \frac{0.2}{(8 \times 10^{-3})(3 \times 10^{-4})} = 83\,300 \text{ At/Wb} \quad \text{Ans.} \end{aligned}$$

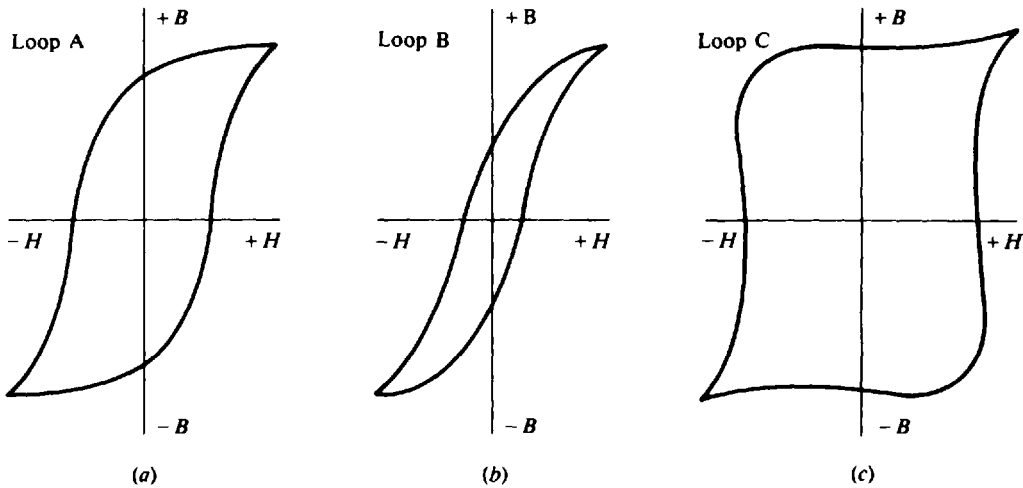


Fig. 9-21 Hysteresis loops

- 9.9 If the magnetic circuit of Prob. 9.8 has an air gap of 0.2 cm in addition to the 20 cm of annealed steel path, what is the reluctance of the air gap and how many ampere-turns would be needed to maintain a  $B$  of 0.72 T? Assume that the area of the air gap is the same as the area of the steel core.

The total reluctance of the magnetic circuit,  $\mathcal{R}_T$ , is the reluctance of the steel path plus the reluctance of the air gap. The  $\mu_0$  of air is  $1.26 \times 10^{-6}$  (T·m)/At. The reluctance  $\mathcal{R}$  of the steel, as determined in Prob. 9.8, is 83 300 At/Wb. The reluctance of the air gap is

$$\begin{aligned} \mathcal{R}_A &= \frac{l}{\mu_0 A} & (9-7) \\ &= \frac{2 \times 10^{-3}}{(1.26 \times 10^{-6})(3 \times 10^{-4})} = 5\,290\,000 \text{ At/Wb} & \text{Ans.} \end{aligned}$$

The total reluctance  $\mathcal{R}_T$  is the sum of  $\mathcal{R}$  and  $\mathcal{R}_A$ .

$$\mathcal{R}_T = \mathcal{R} + \mathcal{R}_A = 83\,300 + 5\,290\,000 = 5\,373\,300 = 5.37 \times 10^6 \text{ At/Wb}$$

To maintain a  $B$  of 0.72 T requires a total flux of

$$\phi = BA = 0.72(3 \times 10^{-4}) = 216 \times 10^{-6} \text{ Wb}$$

The mmf in ampere-turns is found by use of Eq. (9-6).

$$\phi = \frac{\text{mmf}}{\mathcal{R}_T}$$

from which

$$\text{mmf} = \mathcal{R}_T \phi = (5.37 \times 10^6)(216 \times 10^{-6}) = 1160 \text{ At} \quad \text{Ans.}$$

- 9.10 Explain the terms of the induced voltage formula.

The equation is

$$v_{\text{ind}} = N \frac{\Delta\phi}{\Delta t} \quad (9-8)$$

$N$ , the number of turns, is a constant. More turns will provide more induced voltage, while fewer turns mean less voltage. Two factors are included in  $\Delta\phi/\Delta t$ . Its value can be increased by a higher value of  $\Delta\phi$  or a smaller value of  $\Delta t$ . As an example, the value of 4 Wb/s for  $\Delta\phi/\Delta t$  can be doubled by either increasing  $\Delta\phi$  to 8 Wb or reducing  $\Delta t$  to  $\frac{1}{2}$ s. Then  $\Delta\phi/\Delta t$  is 8/1 or 4/(1/2), which equals 8 Wb/s in either case. For the opposite case,  $\Delta\phi/\Delta t$  can be reduced by a smaller value of  $\Delta\phi$  or a higher value of  $\Delta t$ .

9.11 The hysteresis loop for a magnetic material is shown by plotting a curve of flux density  $B$  for a periodically reversing magnetizing force  $H$  (Fig. 9-22). For this material what are its (a) permeability, (b) retentivity, and (c) coercive force?

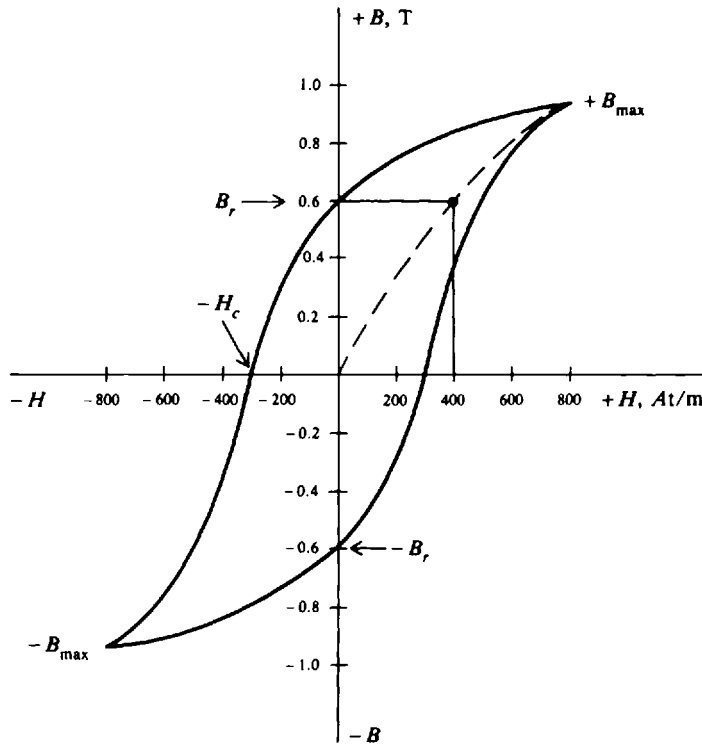


Fig. 9-22 Hysteresis loop,  $BH$  curve

(a)  $\mu = B/H$ , which is the slope of the curve from zero at the center (current is zero when the material is unmagnetized) to  $+B_{max}$ . Since this curve is normally not a straight line, we approximate its slope from Fig. 9-22. Approximately,

$$\mu = \frac{B}{H} \approx \frac{0.6}{400} = 1.5 \times 10^{-3} \text{ (T} \cdot \text{m)/At} \quad \text{Ans.}$$

(b)  $+B_r$ , or  $-B_r$ , is the flux density remaining after the magnetizing force  $H$  has been reduced to zero. This residual induction of a magnetic material is called its *retentivity*. From Fig. 9-22,

$$B_r = 0.6 \text{ T} \quad \text{Ans.}$$

(c) The coercive force of the material is  $-H_c$ , which equals the magnetizing force that must be applied to reduce flux density to zero. From Fig. 9-22,

$$H_c = 300 \text{ At/m} \quad \text{Ans.}$$

### Supplementary Problems

9.12 Match the term in column 1 with its closest meaning in column 2.

Column 1	Column 2
1. North and south pole	(a) natural magnet
2. Ohm's law	(b) $NI$
3. Magnetite	(c) Iron
4. North pole	(d) Value of $B$ when $H = 0$
5. Relative permeability	(e) Force of attraction
6. Induced voltage	(f) $\mu_r$ less than 1
7. Ferromagnetic	(g) $\text{mmf}/\mathcal{R}$
8. Retentivity	(h) $H$ value when $B = 0$
9. Diamagnetic	(i) Lines of force cutting a conductor
10. mmf	(j) $B/H$
	(k) $\mu_0/\mu$
	(l) Lines of force flowing from
	(m) Force of repulsion
	(n) Aluminum

Ans. 1. (e) 2. (g) 3. (a) 4. (l) 5. (k) 6. (i) 7. (c) 8. (d) 9. (f) 10. (b)

9.13 What is the flux density of a core having 20 000 lines and a cross-sectional area of  $5 \text{ cm}^2$ ?

Ans.  $B = 0.4 \text{ T}$

9.14 Fill in the indicated values. All answers should be in SI units.

	$\phi$	$B$	$A$
(a)	$35 \mu\text{Wb}$	?	$0.001 \text{ m}^2$
(b)	?	$0.8 \text{ T}$	$0.005 \text{ m}^2$
(c)	10 000 lines	?	$2 \text{ cm}^2$
(d)	$90 \mu\text{Wb}$	?	$0.003 \text{ m}^2$

Ans.

	$\phi$	$B$	$A$
(a)	....	$0.035 \text{ T}$	....
(b)	$400 \mu\text{Wb}$	....	....
(c)	....	$0.5 \text{ T}$	....
(d)	....	$0.03 \text{ T}$	....

9.15 Draw the lines of force between the south poles of two bar magnets and indicate strong and weak fields. Ans. See Fig. 9-23.

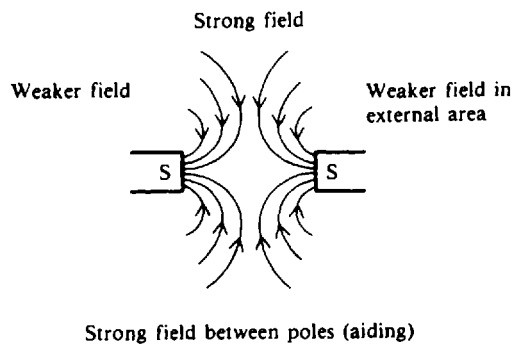


Fig. 9-23

9.16 Draw the lines of force for two parallel conductors having the same direction of current and indicate the strong and weak fields. Ans. See Fig. 9-24.

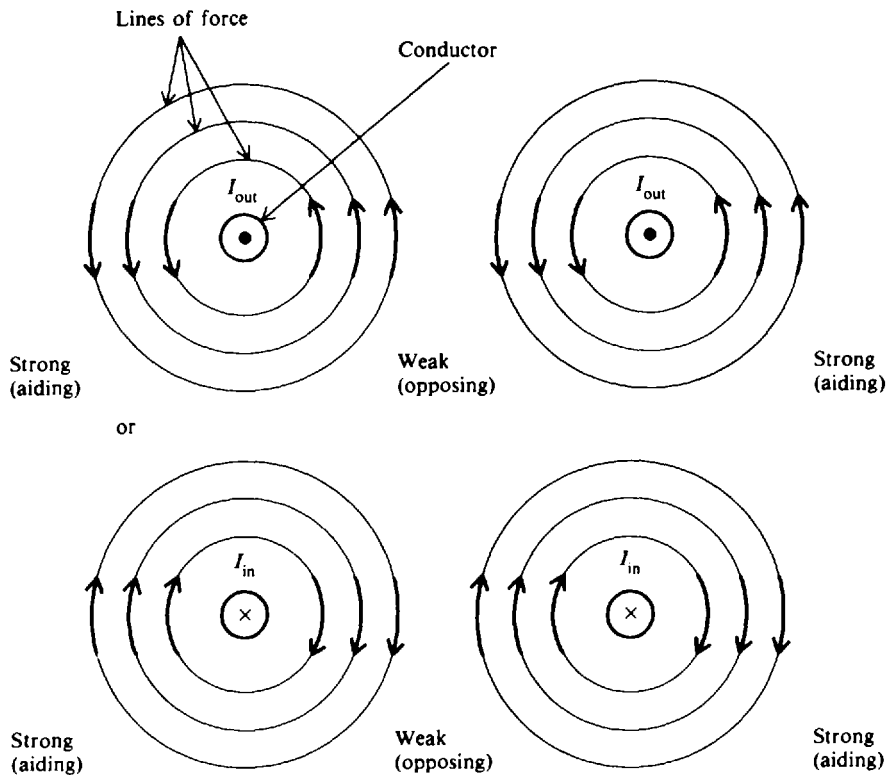


Fig. 9-24

- 9.17 Compute the ampere-turns rating of an electromagnet wound with 600 turns of wire when it is energized with 3 A of current. *Ans.*  $NI = 1800 \text{ At}$
- 9.18 A core of annealed sheet steel is wound with 1500 turns of wire through which a current of 12 mA is flowing. If the length of the coil is 20 cm, find the magnetomotive force and field intensity. *Ans.*  $NI = 18 \text{ At}$ ,  $H = 90 \text{ At/m}$
- 9.19 A coil has a field intensity of 300 At. Its length is doubled from 20 to 40 cm for the same  $NI$ . What is the new magnetic field intensity? *Ans.*  $H = 750 \text{ At/m}$
- 9.20 An iron core has 250 times more flux density than air for the same field intensity. What is the value of  $\mu_r$ ? *Ans.*  $\mu_r = 250$
- 9.21 Fill in the indicated values. All answers are in SI units.

	$B, \text{ T}$	$H, \text{ At/m}$	$\mu, (\text{T} \cdot \text{m})/\text{At}$	$\mu_r$
(a)	?	1200	$650 \times 10^{-6}$	?
(b)	?	1000	?	200
(c)	0.8	?	?	500
(d)	0.1	150	?	?

<i>Ans.</i>	$B, \text{ T}$	$H, \text{ At/m}$	$\mu, (\text{T} \cdot \text{m})/\text{At}$	$\mu_r$
(a)	0.78	....	....	516
(b)	0.25	....	$252 \times 10^{-6}$	....
(c)	....	1270	$630 \times 10^{-6}$	....
(d)	....	....	$667 \times 10^{-6}$	529

- 9.22 A  $BH$  curve for soft iron is shown (Fig. 9-25). Find the value of permeability, retentivity, and coercive force. *Ans.*  $\mu = B/H \approx 0.4/200 = 2000 \times 10^{-6} (\text{T} \cdot \text{m})/\text{At}$ ;  $B_r = 0.4 \text{ T}$ ;  $H_c = 200 \text{ At/m}$



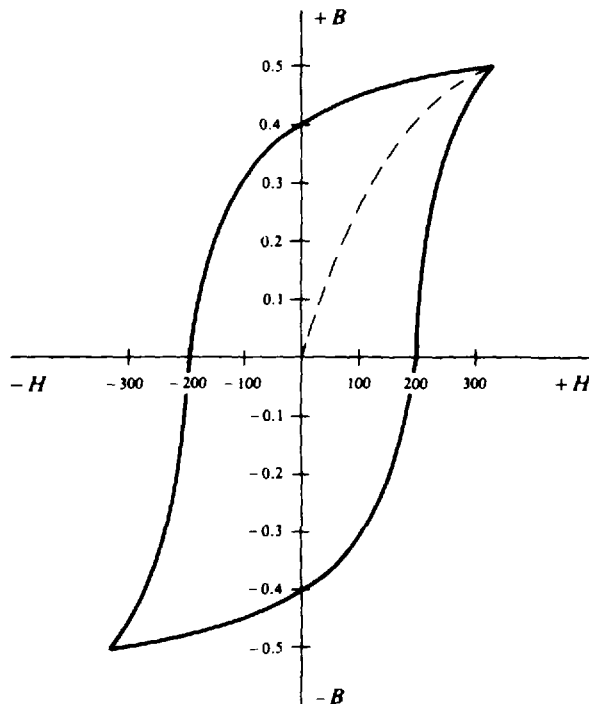


Fig. 9-25

- 9.23 When it has an annealed iron core, a coil has a flux density of 1.44 T at a field intensity of 500 At/m. Find  $\mu$  and  $\mu_r$ . *Ans.*  $\mu = 2880 \times 10^{-6} (\text{T} \cdot \text{m})/\text{At}$ ;  $\mu_r = 2290$
- 9.24 The  $\mu$  of an annealed iron core is  $5600 \times 10^{-6} (\text{T} \cdot \text{m})/\text{At}$  when the current is 80 mA. The coil consists of 200 turns on core 20 cm in length. Find  $H$ ,  $B$ , and  $\mu_r$ .  
*Ans.*  $H = 80 \text{ At/m}$ ;  $B = 0.45 \text{ T}$ ;  $\mu_r = 4440$
- 9.25 A coil of 100 turns is 8 cm in length. The current in the coil is 0.2 A. If the core is cast iron with a  $B$  of 0.13 T, find  $H$ ,  $\mu$ , and  $\mu_r$ .  
*Ans.*  $H = 250 \text{ At/m}$ ;  $\mu = 520 \times 10^{-6} (\text{T} \cdot \text{m})/\text{At}$ ;  $\mu_r = 413$
- 9.26 If the core in Prob. 9.25 has a cross-sectional area of  $2 \text{ cm}^2$ , find the reluctance and the mmf of this magnetic circuit. *Ans.*  $\mathcal{R} = 769\,000 \text{ At/Wb}$ ;  $\text{mmf} = 20 \text{ At}$
- 9.27 A coil has 200 At (Fig. 9-26a) with a flux of  $25 \mu\text{Wb}$  in the iron core. Calculate the reluctance. If the reluctance of the path with an air gap were  $800 \times 10^6 \text{ At/Wb}$  (Fig. 9-26b), how much mmf would be needed for the same flux of  $25 \mu\text{Wb}$ ? *Ans.*  $\mathcal{R} = 8 \times 10^6 \text{ At/Wb}$ ;  $\text{mmf} = 20\,000 \text{ At}$
- 9.28 A magnetic flux of 1000 lines cuts across a coil of 800 turns in  $2 \mu\text{s}$ . What is the voltage induced in the coil? *Ans.*  $v_{\text{ind}} = 4 \text{ kV}$
- 9.29 In a stationary field coil of 500 turns calculate the induced voltage produced by the following flux changes: (a) 4 Wb increasing to 6 Wb in 1 s; (b) Wb decreasing to 4 Wb in 1 s; (c) 4000 lines of flux increasing to 5000 lines in  $5 \mu\text{s}$ ; (d) 4 Wb remaining the same over 1 s.  
*Ans.* (a)  $v_{\text{ind}} = 1 \text{ kV}$ ; (b)  $v_{\text{ind}} = 1 \text{ kV}$ ; (c)  $v_{\text{ind}} = 1 \text{ kV}$ ; (d)  $v_{\text{ind}} = 0 \text{ V}$
- 9.30 A magnetic circuit has a 10-V battery connected to a  $50\text{-}\Omega$  coil of 500 turns with an iron core of 20 cm in length (Fig. 9-27). Find (a) mmf; (b) field intensity  $H$ ; (c) flux density  $B$  in a core with  $\mu_r$  of 600; and (d) the total flux  $\phi$  at each pole with an area of  $4 \text{ cm}^2$ .  
*Ans.* (a)  $\text{mmf} = 100 \text{ At}$ ; (b)  $H = 500 \text{ At/m}$ ; (c)  $B = 0.378 \text{ T}$ ; (d)  $\phi = 1.51 \times 10^{-4} \text{ Wb}$

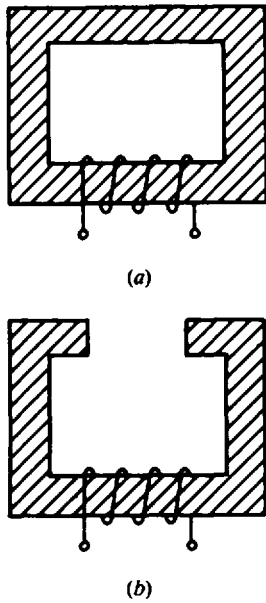


Fig. 9-26

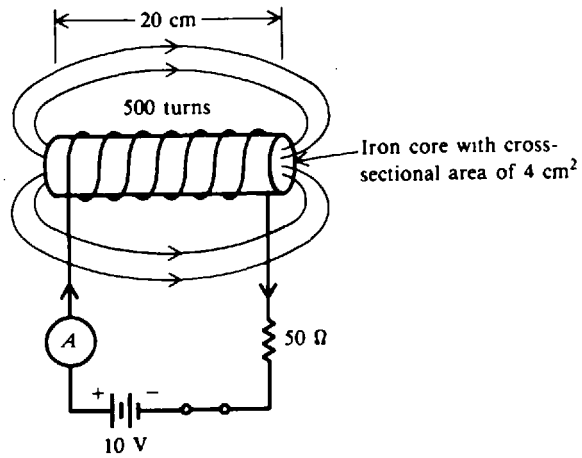


Fig. 9-27

9.31 If a conductor cuts 3.5 Wb in 0.25 s, what is the voltage induced in the conductor?

Ans.  $v_{ind} = 14 \text{ V}$

9.32 If the iron core is removed from the coil in Prob. 9.30, (a) What will the flux be in the air-core coil? (b) What value of induced voltage would be produced by this change in flux while the core is being moved out in  $\frac{1}{2}$  s? (c) What is the induced voltage after the core is removed and the flux remains constant?

Ans. (a)  $\phi = 2.52 \times 10^{-7} \text{ Wb}$ ; (b)  $v_{ind} = 0.151 \text{ V}$ ; (c)  $v_{ind} = 0 \text{ V}$

9.33 The N pole of a permanent magnet is moved away from the coil (Fig. 9-28a). What is the polarity of the coil and the direction of induced current? Ans. See Fig. 9-28b.

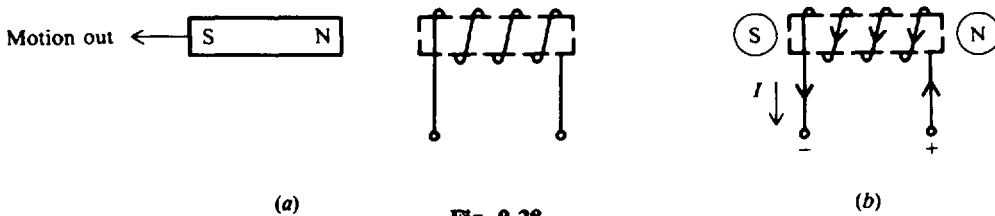


Fig. 9-28

9.34 A BH magnetization curve for soft iron has the following values:

B, T	H, At/m
0.126	1000
0.252	2000
0.378	3000
0.428	4000
0.441	5000

(a) What is the value of  $\mu$ ? (b) Find  $\mu_r$ . (c) At what value of H does the BH curve begin to saturate?

Ans. (a)  $\mu \approx 1.25 \times 10^{-4} (\text{T} \cdot \text{m})/\text{At}$ ; (b)  $\mu_r = 100$ ; (c)  $H = 4000 \text{ At/m}$


## Direct-Current Generators and Motors

### MOTORS AND GENERATORS

A *motor* is a machine that converts electric energy into rotary mechanical energy. Motors turn washing machines, dryers, fans, furnace blowers, and much of the machinery found in industry. A *generator*, on the other hand, is a machine that converts rotary mechanical energy into electric energy. The mechanical energy might be supplied by a waterfall, steam, wind, gasoline or diesel engine, or an electric motor.

### Components

The main parts of direct-current motors and generators are basically the same (Fig. 10-1).

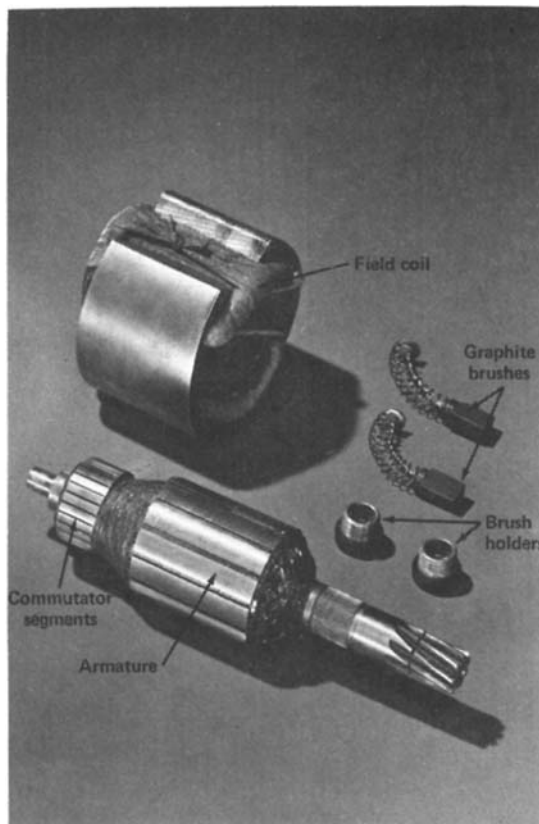

**Fig. 10-1** Main parts of a dc motor. (From B. Grob, *Basic Electronics*, McGraw-Hill, New York, 1977, 4th, ed., p. 338)

### Armature

In a motor, the armature receives current from an external electrical source. This causes the armature to turn. In a generator, the armature is rotated by an external mechanical force. The voltage generated in the armature is then connected to an external circuit. In brief, the motor armature receives current from an external circuit (the power supply), and the generator armature delivers current to an external circuit (the load). Since the armature rotates, it is also called a *rotor*.

**Commutator**

A dc machine has a commutator to convert the alternating current flowing in its armature into the direct current at its terminals (in the case of the generator). The commutator (Fig. 10-1) consists of copper segments with one pair of segments for each armature coil. Each commutator segment is insulated from the others by mica. The segments are mounted around the armature shaft and are insulated from the shaft and armature iron. Two stationary brushes are mounted on the frame of the machine so that they contact opposite segments of the commutator.

**Brushes**


These graphite connectors are stationary and spring-mounted to slide or “brush” against the commutator on the armature shaft. Thus, brushes provide a connection between the armature coils and the external load.

**Field Winding**

This electromagnet produces the flux cut by the armature. In a motor, current for the field is provided by the same source that supplies the armature. In a generator, the field-current source may come from a separate source called an *exciter* or from its own armature output.

**SIMPLE DC GENERATOR**

A simple dc generator consists of an armature coil with a single turn of wire. This armature coil cuts across the magnetic field to produce voltage. If a complete path is present, current will move through the circuit in the direction shown by the arrows (Fig. 10-2a). In this position of the coil, commutator segment 1 is in contact with brush 1, while commutator segment 2 is in contact with brush 2. As the armature rotates a half turn in a clockwise direction, the contacts between the commutator segments and the brushes are reversed (Fig. 10-2b). Now, segment 1 is in contact with brush 2 and segment 2 is in contact with brush 1. Because of this commutator action, that side of the armature coil which is in contact with either of the brushes is always cutting across the magnetic field in the same direction. Therefore, brushes 1 and 2 have constant polarity, and a pulsating direct current is delivered to the external load circuit.

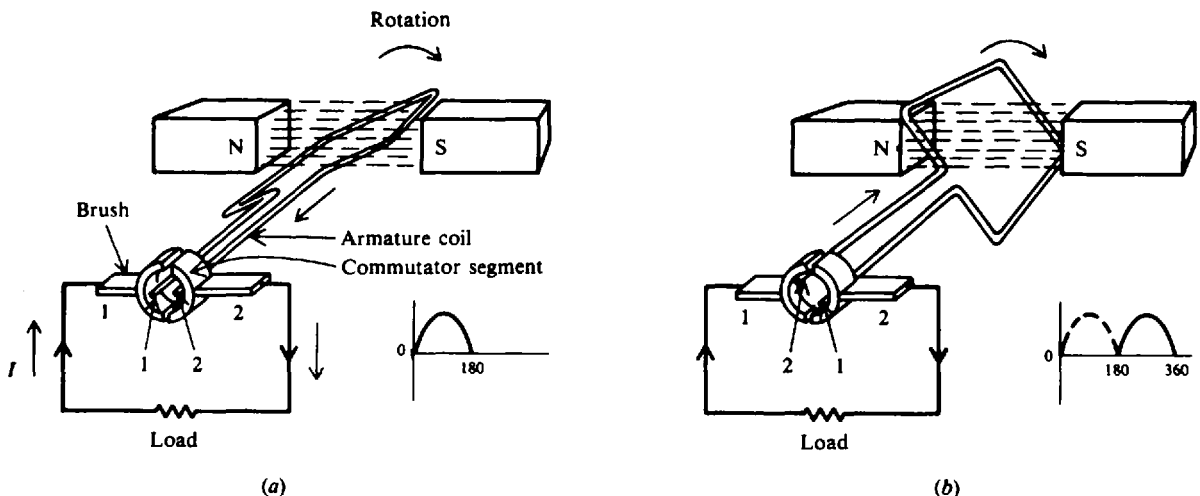

**Fig. 10-2** Basic operation of a dc generator

**Example 10.1** A dc generator with a single coil produces a pulsating dc output. By using more coils and combining their output, a smoother waveform can be obtained. Draw a voltage output waveform that results when a second coil is added to the armature and placed perpendicular to the first coil.

See Fig. 10-3. Notice that a voltage is induced at all times. Although the current still pulsates, the output is smoother. In practical generators, many coils are wound around the armature to produce a still smoother dc output.

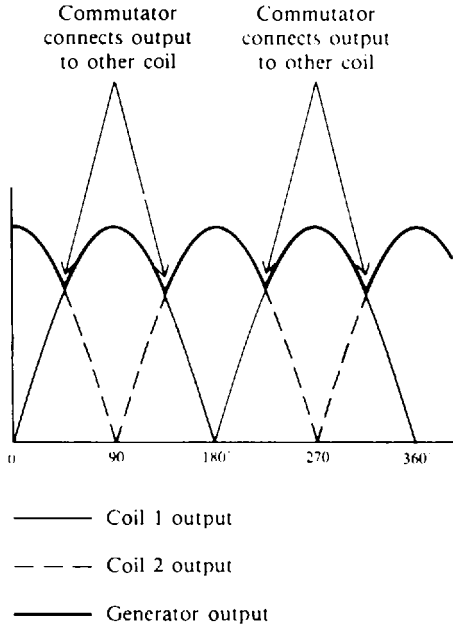


Fig. 10-3 Output of a two-coil dc generator

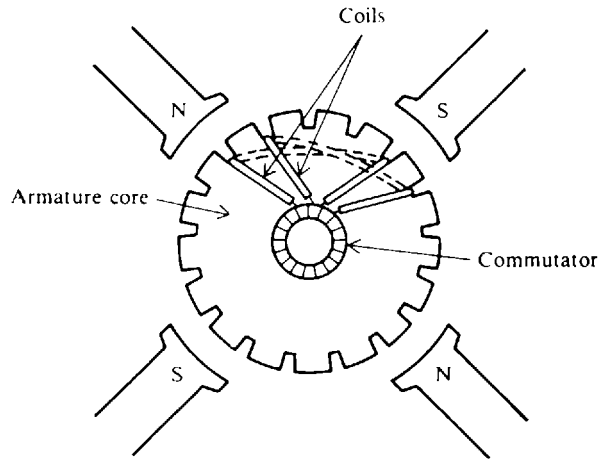


Fig. 10-4 Simplex lap winding

**ARMATURE WINDINGS**

The armature coils used in large dc machines are usually wound in their final shape before being put on the armature. The sides of the preformed coil are placed in the slots of the laminated armature core. There are two ways the coils can be connected, *lap winding* and *wave winding*.

In a *simplex lap winding*, the ends of each coil are connected to adjacent commutator segments (Fig. 10-4). In this way all the coils are connected in series. In a *duplex lap winding* there are in effect two separate sets of coils, each set connected in series (Fig. 10-5). The two sets of coils are connected

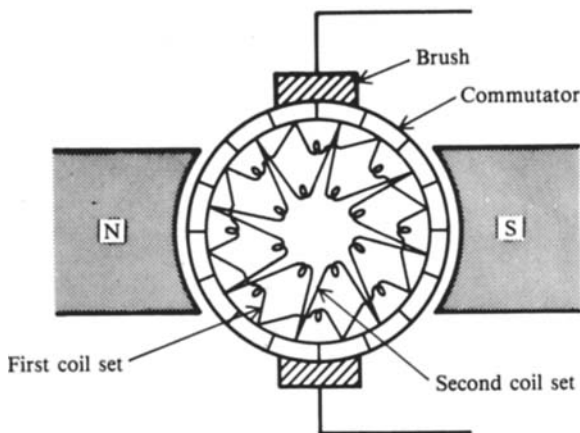


Fig. 10-5 Duplex lap winding

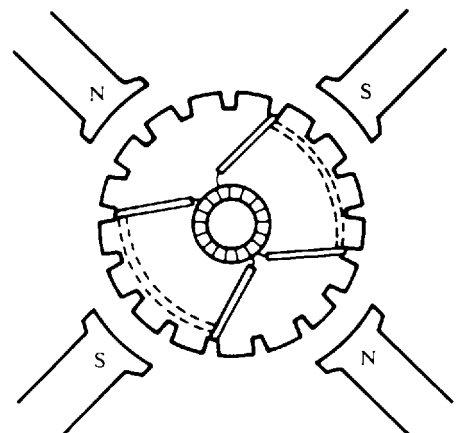


Fig. 10-6 Wave winding for a four-pole dc machine


to each other only by the brushes. Similarly, a *triplex lap winding* is in effect three separate sets of series-connected coils. In a simplex lap winding, a single brush short-circuits the two ends of a single coil.

In a *wave winding*, the ends of each coil are connected to commutator segments two pole spans apart (Fig. 10-6). Instead of short-circuiting a single coil, a brush will short-circuit a small group of coils in series.


The area in a generator where no voltage can be induced in an armature coil is called the *commutating* or *neutral plane*. This plane is midway between adjacent north and south field poles. The brushes are always set so that they short-circuit the armature coils passing through the neutral plane while, at the same time, the output is taken from the other coils.

**Example 10.2** Explain the commutating action in a simplex lap-wound armature that has 22 coils.

See Fig. 10-7. An armature with 22 coils is connected to 22 commutator segments. There are two brushes. The + brush is short-circuiting armature coil 11, while the - brush is short-circuiting armature coil 22. There is no voltage induced in either of these coils. The two coil groups, 1 to 10 and 12 to 21, are connected in parallel by the brushes because the voltages in both coil groups have the same polarity. The brushes also connect the generated voltage to the external load circuit. While the brush is short-circuiting one armature coil, it is receiving the voltage and current induced in the other armature coils because one end of two different coils is connected to the same commutator segment (e.g., coil 21 and coil 22).

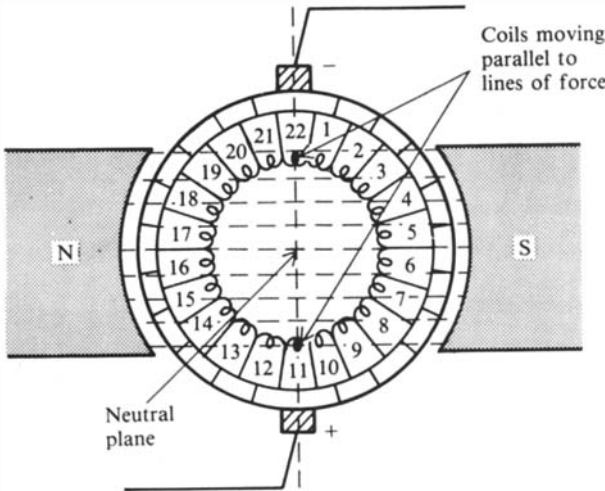

**Fig. 10-7** Brush-commutator action in a simplex lap-wound armature

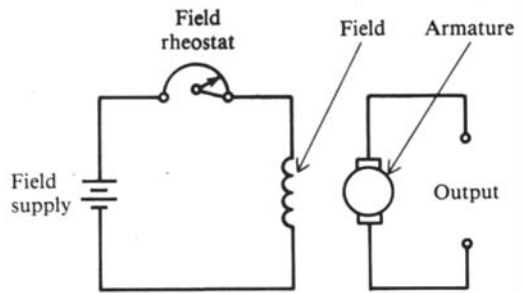

**Fig. 10-8** Circuit diagram of separately excited generator

**FIELD EXCITATION**

Dc generators take their names from the type of field excitation used. When the generator's field is supplied or "excited" from a separate dc source, such as a battery, it is called a *separately excited* generator (Fig. 10-8). When a generator supplies its own excitation, it is called a *self-excited* generator. If its field is connected in parallel with the armature circuit, it is called a *shunt* generator (Fig. 10-9a). When the field is in series with the armature, the generator is called a *series* generator (Fig. 10-9b). If both shunt and series fields are used, the generator is called a *compound* generator. Compound generators may be connected *short-shunt* (Fig. 10-9c), with the shunt field in parallel only with the armature, or *long-shunt* (Fig. 10-9d), with the shunt field in parallel with both the armature and series field. When the series field is so connected that its ampere-turns act in the same direction as those of the shunt field, the generator is said to be a *cumulative-compound* generator. Field rheostats are adjustable resistances placed in the field circuits to vary the field flux and therefore the emf generated by the generator.

The compound generator is used more extensively than other types of generators because it can be designed so that it has a wide variety of characteristics.

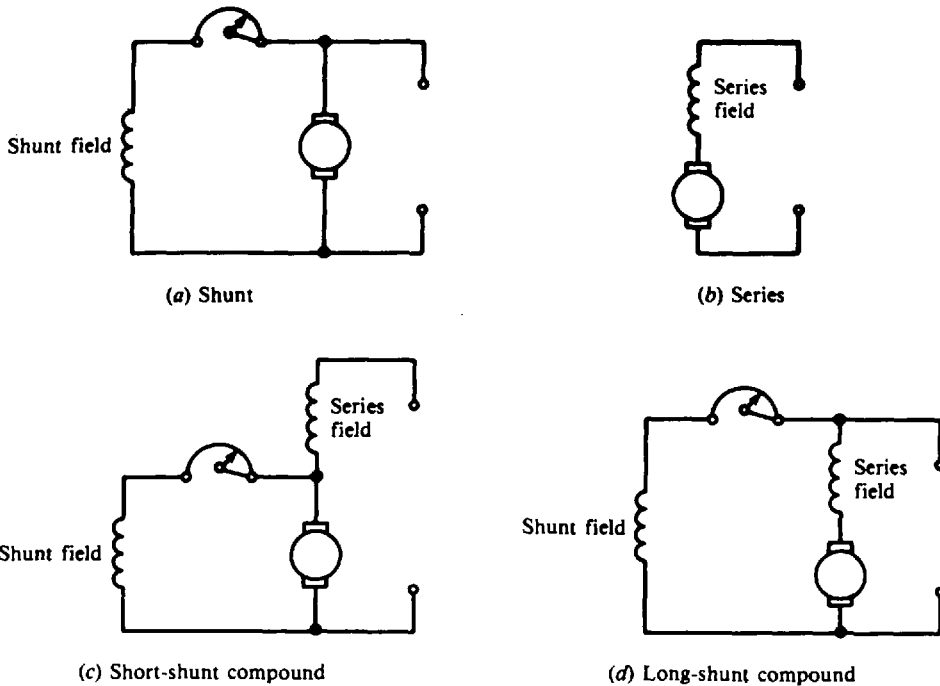


Fig. 10-9 Circuit diagrams of dc generators

**DC GENERATOR EQUIVALENT CIRCUIT**

Voltage and current relationships of a dc generator equivalent circuit (Fig. 10-10) are, according to Ohm's law,

$$V_{ta} = V_g - I_a r_a \tag{10-1}$$

$$V_t = V_g - I_a (r_a + r_s) \tag{10-2}$$

$$I_L = I_a - I_f \tag{10-3}$$

- where
- $V_{ta}$  = armature terminal voltage, V
  - $V_g$  = armature generated voltage, V
  - $I_a$  = armature current, A
  - $V_t$  = generator terminal voltage, V
  - $r_a$  = armature-circuit resistance,  $\Omega$
  - $r_s$  = series-field resistance,  $\Omega$
  - $r_f$  = shunt-field resistance,  $\Omega$
  - $I_L$  = line current, A
  - $I_f$  = shunt-field current, A

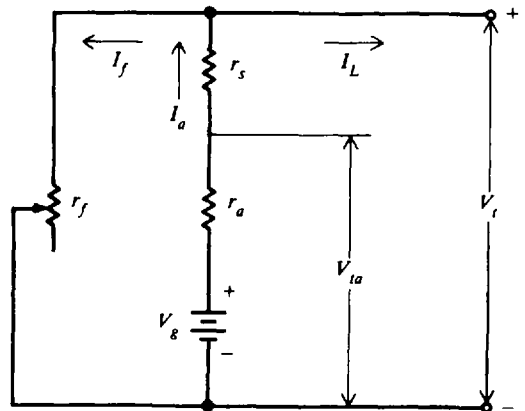


Fig. 10-10 DC generator equivalent circuit

**Example 10.3** A dc generator has a 100-kW, 250-V rating. What do these ratings mean?

The generator can continuously deliver 100 kW of power to an external load. The terminal voltage  $V_t$  of the generator is 250 V when it is delivering its rated current.

**Example 10.4** A 100-kW, 250-V dc generator has an armature current of 400 A, armature resistance (including brushes) of 0.025  $\Omega$ , and series-field resistance of 0.005  $\Omega$ . It is driven at 1200 revolutions per minute (rpm) by a constant-speed motor. Compute the armature generated voltage. From Eq. (10-2),

$$\begin{aligned} V_g &= V_t + I_a (r_a + r_s) \\ &= 250 + 400(0.025 + 0.005) = 250 + 12 = 262 \text{ V} \quad \text{Ans.} \end{aligned}$$

**GENERATOR VOLTAGE EQUATIONS AND VOLTAGE REGULATION**

The average generated voltage  $V_g$  of a generator may be calculated from the formula

$$V_g = \frac{pZ\phi n}{60b \times 10^8} \quad (10-4)$$

where  $V_g$  = average generated voltage of a dc generator, V  
 $p$  = number of poles  
 $Z$  = total number of conductors on armature (also called inductors)  
 $\phi$  = flux per pole  
 $n$  = speed of the armature, rpm  
 $b$  = number of parallel paths through armature, depending on type of armature winding

For any generator, all factors in Eq. (10-4) are fixed values except  $\phi$  and  $n$ . Hence Eq. (10-4) may be simplified to

$$V_g = k\phi n \quad (10-5)$$

where  $k = \frac{pZ}{60b \times 10^8}$

Equation (10-5) indicates that the value of an induced emf in any circuit is proportional to the rate at which the flux is being cut. Thus, if  $\phi$  is doubled while the  $n$  remains constant,  $V_g$  is doubled. Similarly, if  $n$  is doubled,  $\phi$  remaining constant,  $V_g$  will be doubled.

**Example 10.5** When a generator is being driven at 1200 rpm, the generated voltage is 120 V. What will be the generated voltage (a) if the field flux is decreased by 10 percent with the speed remaining fixed and (b) if the speed is reduced to 1000 rpm, the field flux staying unchanged?

$$(a) \quad V_{g1} = k\phi_1 n_1 \quad \text{or} \quad k = \frac{V_{g1}}{\phi_1 n_1} \quad (10-5)$$

$$V_{g2} = k\phi_2 n_1 = \frac{V_{g1}}{\phi_1 n_1} \phi_2 n_1 = V_{g1} \frac{\phi_2}{\phi_1} = 120 \frac{1.00}{1.00 - 0.10} = 120(0.90) = 108 \text{ V} \quad \text{Ans.}$$

$$(b) \quad V_{g2} = k\phi_1 n_2 = \frac{V_{g1}}{\phi_1 n_1} \phi_1 n_2 = V_{g1} \frac{n_2}{n_1} = 120 \frac{1000}{1200} = 100 \text{ V} \quad \text{Ans.}$$

*Voltage regulation* is the difference between the no-load (NL) and full-load (FL) terminal voltage of a generator and is expressed as a percentage of the full-load value.

$$\text{Voltage regulation} = \frac{\text{NL voltage} - \text{FL voltage}}{\text{FL voltage}} \quad (10-6)$$

Low-percentage regulation, characteristic of lighting circuits, means that the generator's terminal voltage is nearly the same at full load as it is at no load.

**Example 10.6** A shunt generator has a full-load terminal voltage of 120 V. When the load is removed, the voltage increases to 150 V. What is the percentage voltage regulation?

$$\text{Voltage regulation} = \frac{\text{NL voltage} - \text{FL voltage}}{\text{FL voltage}} = \frac{150 - 120}{120} = \frac{30}{120} = 0.25 = 25\% \quad \text{Ans.}$$

**LOSSES AND EFFICIENCY OF A DC MACHINE**

The losses of generators and motors consist of copper losses in the electric circuits and mechanical losses due to the rotation of the machine. Losses include:



1. Copper losses
  - (a) Armature  $I^2R$  losses
  - (b) Field losses
    - (1) Shunt field  $I^2R$
    - (2) Series field  $I^2R$
2. Mechanical or rotational losses
  - (a) Iron losses
    - (1) Eddy-current loss
    - (2) Hysteresis loss
  - (b) Friction losses
    - (1) Bearing friction
    - (2) Brush friction
    - (3) Windage or air friction loss

Copper losses are present because power is used when a current is made to flow through a resistance. As the armature rotates in a magnetic field, the emf induced in the iron parts causes eddy currents to flow which heat the iron and thus represent wasted energy. Hysteresis loss also results when a magnetic material is first magnetized in one direction and then in an opposite direction. Other rotational losses are caused by bearing friction, the friction of the brushes riding on the commutator, and air friction or windage.

*Efficiency* is the ratio of the useful power output to total power input.

$$\text{Efficiency} = \frac{\text{output}}{\text{input}} \quad (10-7)$$

Also

$$\text{Efficiency} = \frac{\text{input} - \text{losses}}{\text{input}} = \frac{\text{output}}{\text{output} + \text{losses}} \quad (10-8)$$

Efficiency is usually expressed as a percentage.

$$\text{Efficiency (\%)} = \frac{\text{output}}{\text{input}} \times 100$$

**Example 10.7** A shunt generator has an armature-circuit resistance of  $0.4 \Omega$ , a field-circuit resistance of  $60 \Omega$ , and a terminal voltage of  $120 \text{ V}$  when it is supplying a load current of  $30 \text{ A}$  (Fig. 10-11). Find the (a) field current, (b) armature current, (c) copper losses at the above load. (d) If the rotational losses are  $350 \text{ W}$ , what is the efficiency at the above load?

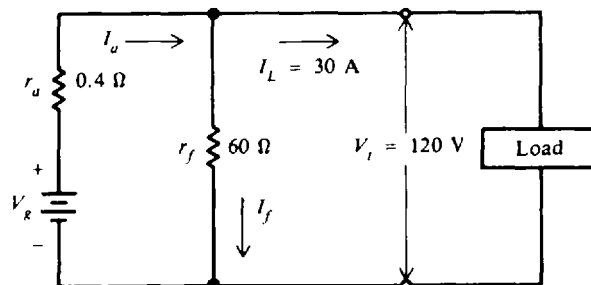


Fig. 10-11 DC shunt generator

(a)  $I_f = \frac{V_t}{r_f} = \frac{120}{60} = 2 \text{ A}$       *Ans.*

(b)  $I_a = I_L + I_f = 30 + 2 = 32 \text{ A}$       *Ans.*

(c) Armature loss =  $I_a^2 r_a = 32^2(0.4) = 410 \text{ W}$   
 Shunt-field loss =  $I_f^2 r_f = 2^2(60) = 240 \text{ W}$

Copper loss = armature loss + shunt-field loss =  $410 + 240 = 650 \text{ W}$       *Ans.*

$$(d) \quad \text{Efficiency} = \frac{\text{output}}{\text{output} + \text{losses}} \quad (10-8)$$

$$\text{Output} = P = V_i I_L = 120(30) = 3600 \text{ W}$$

$$\text{Total losses} = \text{copper losses} + \text{rotational losses} = 650 + 350 = 1000 \text{ W}$$

$$\text{Efficiency (\%)} = \frac{3600}{3600 + 1000} 100 = \frac{3600}{4600} 100 = 0.783(100) = 78.3\% \quad \text{Ans.}$$

## DIRECT-CURRENT MOTOR

### Motor Principle

Although the mechanical construction of dc motors and generators is very similar, their functions are different. The function of a generator is to generate a voltage when conductors are moved through a field, while that of a motor is to develop a turning effort, or *torque*, to produce mechanical rotation.

### Direction of Armature Rotation

The *left-hand rule* is used to determine the direction of rotation of the armature conductors. The left-hand rule for motors is as follows: With the forefinger, middle finger, and thumb of the left hand mutually perpendicular, point the forefinger in the direction of the field and the middle finger in the direction of the current in the conductor; the thumb will point in the direction in which the conductor tends to move (Fig. 10-12a). In a single-turn rectangular coil parallel to a magnetic field (Fig. 10-12b), the direction of current in the left-hand conductor is out of the paper, while in the right-hand conductor it is into the paper. Therefore, the left-hand conductor tends to move upward with a force  $F_1$ , and the right-hand conductor tends to move downward with an equal force  $F_2$ . Both forces act to develop a torque which turns the coil in a clockwise direction. A single-coil motor (Fig. 10-12b) is impractical because it has dead centers and the torque developed is pulsating. Good results are obtained when a large number of coils is used as in a four-pole motor (Fig. 10-13). As the armature rotates and the conductors move away from under a pole into the neutral plane, the current is reversed in them by the action of the commutator. Thus, the conductors under a given pole carry current in the same direction at all times.

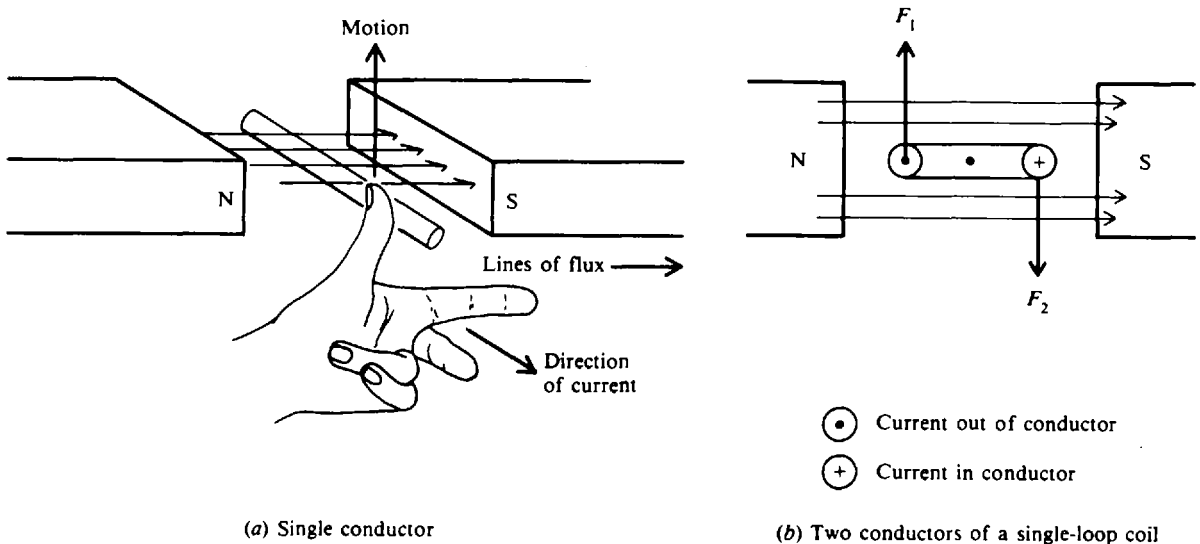



Fig. 10-12 Applications of left-hand rule for motors

**Torque**


The torque  $T$  developed by a motor is proportional to the strength of the magnetic field and to the armature current.

$$T = k_t \phi I_a \tag{10-9}$$

- where  $T$  = torque, ft-lb
- $k_t$  = constant depending on physical dimensions of motor
- $\phi$  = total number of lines of flux entering the armature from one N pole
- $I_a$  = armature current, A

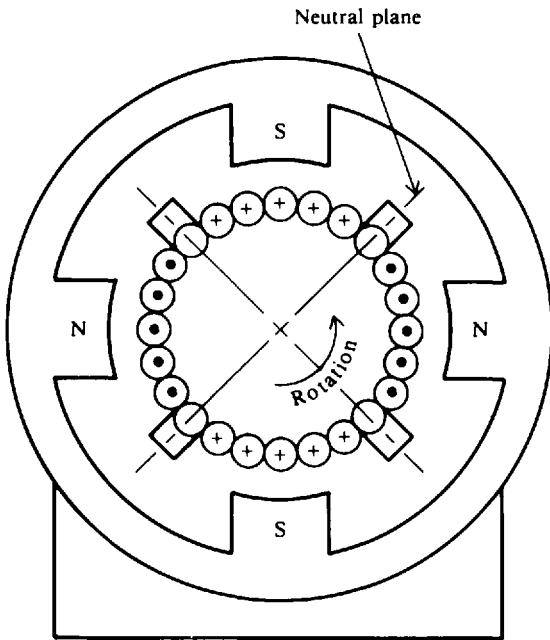

**Fig. 10-13** Armature-current directions in a four-pole motor for counterclockwise rotation

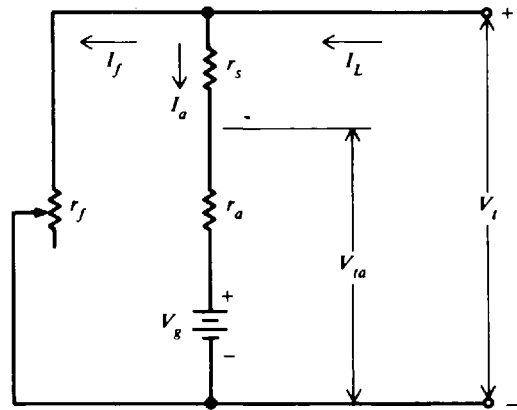

**Fig. 10-14** DC motor equivalent circuit

**DC MOTOR EQUIVALENT CIRCUIT**

Voltage and current relationships of a dc motor equivalent circuit (Fig. 10-14) are as follows:

$$V_{ta} = V_g + I_a r_a \tag{10-10}$$

$$V_t = V_g + I_a (r_a + r_s) \tag{10-11}$$

$$I_L = I_a + I_f \tag{10-12}$$

- where  $V_{ta}$  = armature terminal voltage, V
- $V_g$  = counter emf, V
- $I_a$  = armature current, A
- $V_t$  = motor terminal voltage, V

and  $r_a$ ,  $r_s$ ,  $r_f$ ,  $I_L$ , and  $I_f$  are as defined for the dc generator equivalent circuit (Fig. 10-10). A comparison of a generator equivalent circuit (Fig. 10-10) with a motor equivalent circuit (Fig. 10-14) shows that the only difference is the direction of line and armature current.

The counter emf of a motor,  $V_g$ , is generated by the action of the armature conductors cutting lines of force. If in a shunt motor, Eq. (10-11) is multiplied by  $I_a$  ( $r_s = 0$ ),

$$V_t I_a = V_g I_a + I_a^2 r_a \tag{10-13}$$

$V_t I_a$  is the power supplied to the armature of the motor;  $I_a^2 r_a$  is the power lost as heat in the armature current; and  $V_g I_a$  is the power developed by the armature. But this armature power is not the useful output since some of it must be used to overcome the mechanical or rotational losses of the motor. The rated output of the motor is equal to the input ( $V_t I_L$ ) less the heat losses ( $I^2 R$ ) and rotational losses. The common unit for motor output is *horsepower* (hp), where

$$\text{Horsepower} = \frac{\text{watts}}{746} \tag{10-14}$$

**Example 10.8** (a) Find the counter emf of a motor when the terminal voltage is 240 V and the armature current is 50 A. The armature resistance is 0.08 Ω. The field current is negligible. (b) What is the power developed by the motor armature? (c) What is the power delivered to the motor in kilowatts?

- (a)  $V_t = V_g + I_a r_a \quad r_s = 0$   
 $V_g = V_t - I_a r_a = 240 - 50(0.08) = 240 - 4 = 236 \text{ V} \quad \text{Ans.}$
- (b) Power developed =  $V_g I_a = 236(50) = 11\,800 \text{ W}$   
 Horsepower =  $\frac{\text{watts}}{746} = \frac{11\,800}{746} = 15.8 \text{ hp} \quad \text{Ans.}$
- (c) Power delivered =  $V_t I_L = 240(50) = 12\,000 \text{ W} = 12 \text{ kW} \quad \text{Ans.}$

**SPEED OF A MOTOR**

Speed is designated by the number of revolutions of the shaft with respect to time and is expressed in units of revolutions per minute (rpm). A reduction of the field flux of a motor causes the motor speed to increase. Conversely, an increase in the field flux causes the motor speed to decrease. Because the speed of a motor varies with field excitation, a convenient means for controlling the speed is to vary the field flux by adjusting the resistance in the field circuit.

If a motor is able to maintain a nearly constant speed for varying loads, the motor is said to have a good speed regulation. Speed regulation is usually expressed as a percentage as follows:

$$\text{Speed regulation} = \frac{\text{no-load speed} - \text{full-load speed}}{\text{full-load speed}} \tag{10-15}$$

**Example 10.9** A 220-V shunt motor has an armature resistance of 0.2 Ω. For a given load on the motor, the armature current is 25 A. What is the immediate effect on the torque developed by the motor if the field flux is reduced by 2 percent?

The torque developed when  $I_a = 25 \text{ A}$  is

$$T_1 = k_t \phi I_a = 25 k_t \phi$$

and the counter emf is

$$V_{g1} = V_t - I_a r_a = 220 - 25(0.2) = 215 \text{ V}$$

If  $\phi$  is reduced by 2 percent, the value of  $V_g$  is also reduced by 2 percent since  $V_g = k \phi n$  and the speed  $n$  cannot change instantly. Hence, the new counter emf is

$$V_{g2} = 0.98(215) = 210.7 \text{ V}$$

The new armature current is

$$I_{a2} = \frac{V_t - V_{g2}}{r_a} = \frac{220 - 210.7}{0.2} = 46.5 \text{ A}$$

and the new torque developed is

$$T_2 = k_t(0.98)\phi(46.5) = 45.6 k_t \phi$$

The torque increase is

$$\frac{T_2}{T_1} = \frac{45.6 k_t \phi}{25 k_t \phi} = 1.82 \text{ times} \quad \text{Ans.}$$

Thus a decrease in flux by 2 percent increases the torque of a motor 1.82 times. This increased torque causes the armature speed to increase to a higher value, at which the increased counter emf ( $V_g \propto n$ ) limits the armature current to a value just high enough to carry the load at the higher speed.


**Example 10.10** The no-load speed of a dc shunt motor is 1200 rpm. When the motor carries its rated load, the speed drops to 1140. What is the speed regulation?

$$\begin{aligned} \text{Speed regulation} &= \frac{\text{NL speed} - \text{FL speed}}{\text{FL speed}} && (10-15) \\ &= \frac{1200 - 1140}{1140} = 0.053 = 5.3\% && \text{Ans.} \end{aligned}$$


## MOTOR TYPES
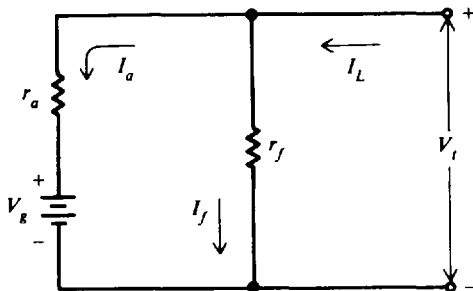
### Shunt Motor

This is the most common type of dc motor. It is connected in the same way as the shunt generator (Fig. 10-15a). Its characteristic speed-load and torque-load curves (Fig. 10-15b) show that the torque increases linearly with an increase in armature current, while the speed drops slightly as the armature current is increased. The basic speed is the full-load speed. Speed adjustment is made by inserting resistance in the field circuit with a field rheostat. At one setting of the rheostat, the motor speed remains practically constant for all loads. Starters used with dc motors limit the armature starting current to 125 to 200 percent of full-load current. Care must be taken never to open the field circuit of a shunt motor that is running unloaded because the motor speed will increase without limit until the motor destroys itself.



(a) Schematic diagram

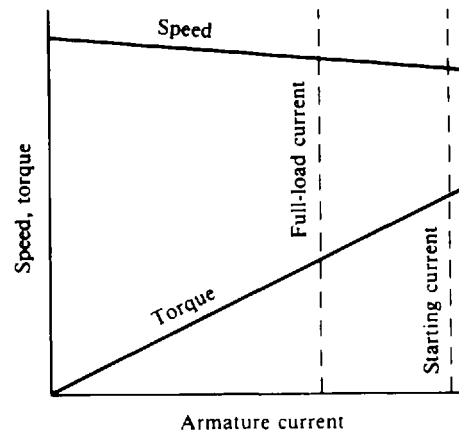

(b) Speed-load and torque-load curves

**Fig. 10-15** Characteristics of a typical shunt motor

### Series Motor

The field of this type of motor is connected in series with the armature (Fig. 10-16a). The speed varies from a very high speed at light load to a lower speed at full load (Fig. 10-16b). The series motor is suitable for starting with heavy, connected loads (driving cranes and winches) because at high armature currents, it develops a high torque and operates at low speed (Fig. 10-16b). At no load the speed of a series motor will increase without limit until the motor destroys itself (Fig. 10-16b). Large series motors are therefore generally connected directly to their load rather than by belts and pulleys.

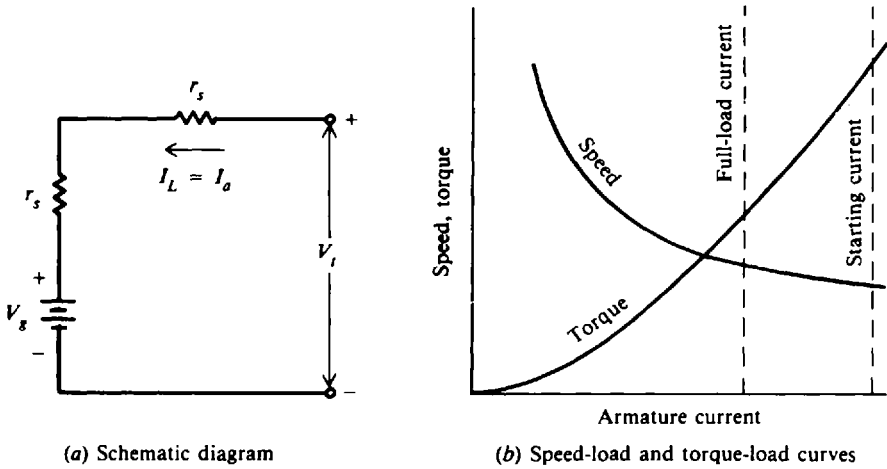


Fig. 10-16 Characteristics of a typical series motor

**Compound Motor**

It combines the operating characteristics of the shunt and series motors (Fig. 10-17a and b). The compound motor may be operated safely at no load. As load is added, its speed decreases, and torque is greater compared with that of a shunt motor (Fig. 10-18).

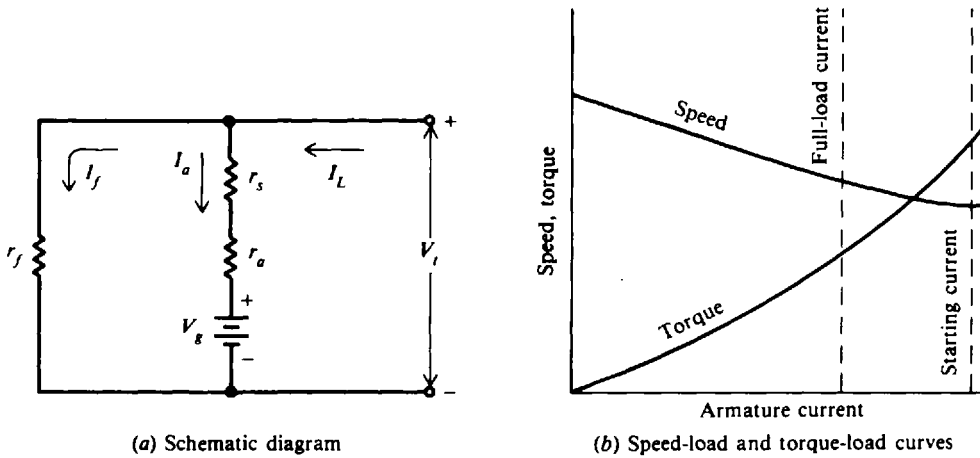


Fig. 10-17 Characteristics of a typical compound motor

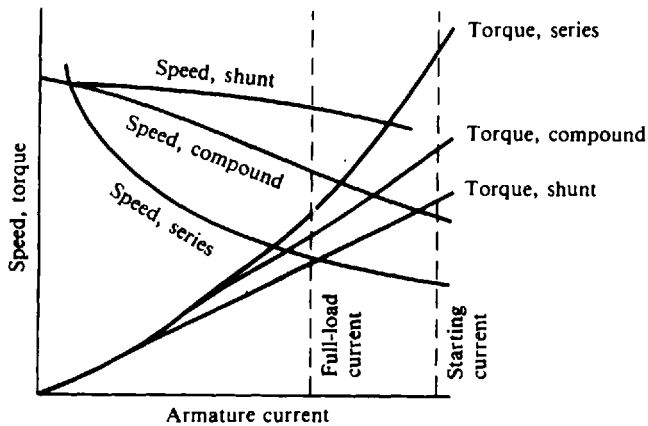


Fig. 10-18 Comparative characteristics for shunt, series, and compound dc motors

**STARTING REQUIREMENTS FOR MOTORS**

There are two starting requirements for motors:

1. Both motor and supply lines are protected from flow of excessive current during the starting period by placing external resistance in series with the armature circuit.
2. Motor-starting torque should be made as large as possible to bring the motor up to full speed in minimum time.

The amount of starting resistance needed to limit the armature starting current to the desired value is

$$R_s = \frac{V_t}{I_s} - r_a \tag{10-16}$$

where  $R_s$  = starting resistance,  $\Omega$   
 $V_t$  = motor voltage, V  
 $I_s$  = desired armature starting current, A  
 $r_a$  = armature resistance,  $\Omega$

**Example 10.11** A shunt motor on a 240-V line has an armature current of 75 A. If the field-circuit resistance is 100  $\Omega$ , find the field current, line current, and power input to the motor (Fig. 10-19).

$$I_f = \frac{V_t}{r_f} = \frac{240}{100} = 2.4 \text{ A} \quad \text{Ans.}$$

$$I_L = I_f + I_a = 2.4 + 75 = 77.4 \text{ A} \quad \text{Ans.}$$

$$P_{IN} = V_t I_L = 240(77.4) = 18\,576 \text{ W} = 18.6 \text{ kW} \quad \text{Ans.}$$

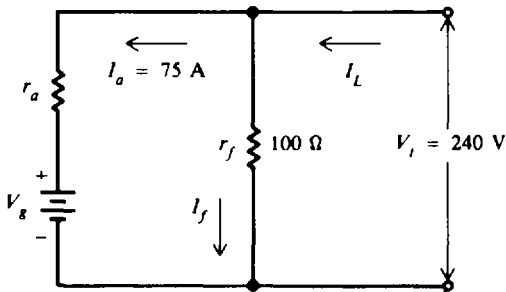


Fig. 10-19 Shunt motor

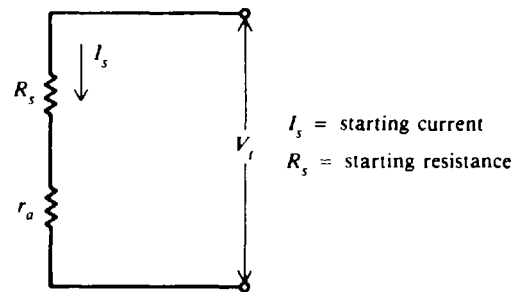


Fig. 10-20 Equivalent dc motor circuit at start-up

$I_s$  = starting current  
 $R_s$  = starting resistance

**Example 10.12** A 10-hp shunt motor with an armature resistance of 0.5  $\Omega$  is connected directly to a 220-V supply line. What is the resulting current if the armature is held stationary? Neglect the field current. If the full-load armature current is 40 A and it is desired to limit the starting current to 150 percent of this value, find the starting resistance that must be added in series with the armature.

At start-up, when a motor armature is stationary, no counter emf is being generated. The only factor limiting the current being drawn from the supply, therefore, is the armature-circuit resistance (Fig. 10-20). At motor start-up, with  $R_s = 0$ ,  $V_g = 0$ , and negligible shunt current,

$$I = \frac{V_t}{r_a} = \frac{220}{0.5} = 440 \text{ A} \quad \text{Ans.}$$

which is far above the normal full-load armature current for a motor of this size. The result will be probable damage to brushes, commutator, and windings. With  $R_s$  added in series in the armature circuit,

$$R_s = \frac{V_t}{I_s} - r_a \tag{10-16}$$

$$= \frac{220}{40(1.5)} - 0.5 = 3.67 - 0.5 = 3.17 \Omega \quad \text{Ans.}$$

### Solved Problems

- 10.1** A generator has an emf of 520 V, has 2000 armature conductors or inductors, a flux per pole of 1 300 000 lines, a speed of 1200 rpm, and the armature has four paths. Find the number of poles.

From Eq. (10-4),

$$p = \frac{V_g(60b \times 10^8)}{Z\phi n} = \frac{520[60(4) \times 10^8]}{(2 \times 10^3)(1.3 \times 10^6)(1.2 \times 10^3)} = 4 \text{ poles} \quad \text{Ans.}$$

- 10.2** A shunt-field winding of a 240-V generator has a resistance of 50 Ω (Fig. 10-21). How much field-rheostat resistance must be added to limit the field current to 3 A when the generator is operating at rated voltage?

Solve Ohm's law for  $r$ :  $I_f = \frac{V_t}{r_f + r}$

$$r = \frac{V_t - I_f r_f}{I_f} = \frac{240 - 3(50)}{3} = 30 \Omega \quad \text{Ans.}$$

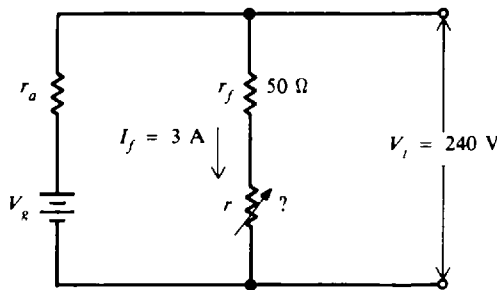


Fig. 10-21 Adding resistance to limit  $I_f$

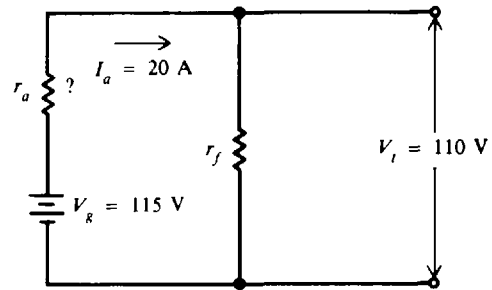


Fig. 10-22

- 10.3** The terminal voltage of a shunt generator is 110 V when the generated voltage is 115 V and the armature current is 20 A (Fig. 10-22). What is the armature resistance?

The generated voltage minus the voltage drop across the armature equals the terminal voltage.

$$V_g - I_a r_a = V_t \quad (10-2)$$

Solve for  $r_a$ :  $r_a = \frac{V_g - V_t}{I_a} = \frac{115 - 110}{20} = 0.25 \Omega \quad \text{Ans.}$

- 10.4** The terminal voltage of a 75-kW shunt generator is 600 V at rated load. The resistance of the shunt field is 120 Ω and the armature resistance is 0.2 Ω (Fig. 10-23). Find the generated emf.

The rated current is

$$I_L = \frac{P}{V_t} = \frac{75\,000}{600} = 125 \text{ A}$$

$$I_f = \frac{V_t}{r_f} = \frac{600}{120} = 5 \text{ A}$$

$$I_a = I_f + I_L = 5 + 125 = 130 \text{ A}$$

$$V_g = V_t + I_a r_a = 600 + 130(0.2) = 626 \text{ V} \quad \text{Ans.}$$



- 10.5 A shunt generator requires 50-hp input from its prime mover when it delivers 150 A at 240 V. Find the efficiency of the generator.

$$\text{Output} = 240(150) = 36\,000 \text{ W}$$

$$\text{Input} = 50(746) = 37\,300 \text{ W}$$

$$\begin{aligned} \text{Efficiency (\%)} &= \frac{\text{output}}{\text{input}} \times 100 && (10-7) \\ &= \frac{36\,000}{37\,300} 100 = 0.965(100) = 96.5\% && \text{Ans.} \end{aligned}$$

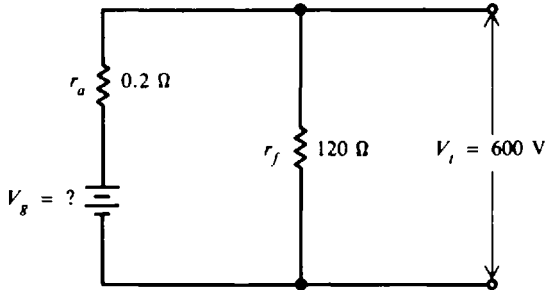


Fig. 10-23

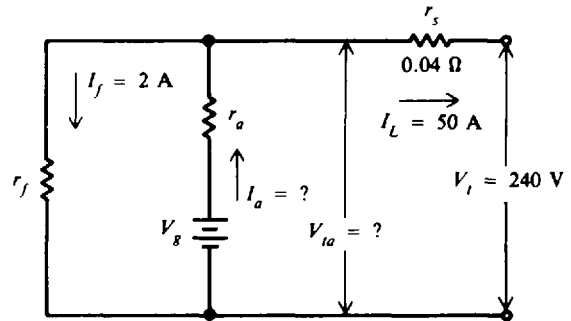


Fig. 10-24 Short-shunt compound generator

- 10.6 A short-shunt compound generator has a terminal voltage of 240 V when the line current is 50 A (Fig. 10-24). The series-field resistance is 0.04 Ω. (a) Find the voltage drop across the series field. (b) Find the voltage drop across the armature. (c) Find the armature current if the shunt-field current is 2 A. (d) If the losses are 2000 W, what is the efficiency?

(a)  $I_L r_s = 50(0.04) = 2 \text{ V}$       *Ans.*

(b)  $V_{ia} = V_t + I_L r_s = 240 + 2 = 242 \text{ V}$       *Ans.*

(c)  $I_a = I_f + I_L = 2 + 50 = 52 \text{ A}$       *Ans.*

(d)  $\text{Output} = V_t I_L = 240(50) = 12\,000 \text{ W}$

$$\begin{aligned} \text{Efficiency (\%)} &= \frac{\text{output}}{\text{output} + \text{losses}} \times 100 && (10-8) \\ &= \frac{12\,000}{12\,000 + 2000} 100 = \frac{12\,000}{14\,000} 100 = 0.857(100) = 85.7\% && \text{Ans.} \end{aligned}$$

- 10.7 From the following data on a shunt generator (Fig. 10-25), find the efficiency at full load:

Rated power output = 10 kW

Rated voltage = 230 V

Armature resistance = 0.6 Ω

Field resistance = 182 Ω

Rotational losses at full load = 700 W

First find the generator currents and then the copper losses.

$$I_L = \frac{\text{power out}}{V_t} = \frac{10\,000}{230} = 43.48 \text{ A}$$

$$I_f = \frac{V_t}{r_f} = \frac{230}{182} = 1.26 \text{ A}$$

$$I_a = I_f + I_L = 1.26 + 43.48 = 44.74 \text{ A}$$

Copper losses:

$$\begin{aligned} \text{Armature: } I_a^2 r_a &= (44.74)^2(0.6) = 1201 \text{ W} \\ \text{Field: } I_f^2 r_f &= (1.26)^2(182) = 289 \text{ W} \\ \text{Total copper losses} &= 1490 \text{ W} \end{aligned}$$

Total losses:

$$\begin{aligned} \text{Copper: } & 1490 \text{ W} \\ \text{Rotational: } & 700 \text{ W} \\ \text{Total} &= 2190 \text{ W} \end{aligned}$$

$$\text{Efficiency (\%)} = \frac{\text{output}}{\text{output} + \text{losses}} \times 100 \tag{10-8}$$

$$= \frac{10\,000}{10\,000 + 2190} 100 = \frac{10\,000}{12\,190} 100 = 0.820(100) = 82.0\% \quad \text{Ans.}$$

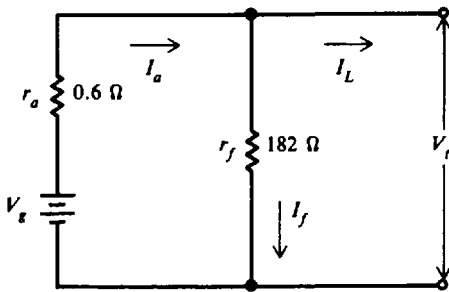


Fig. 10-25

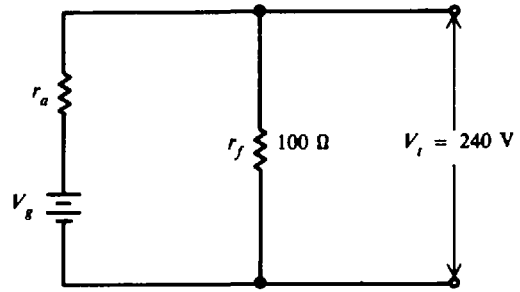


Fig. 10-26

10.8 A shunt motor draws 6 kW from a 240-V line (Fig. 10-26). If the field resistance is 100 Ω, find  $I_L$ ,  $I_f$ , and  $I_a$ .

$$\begin{aligned} P_{IN} &= V_t I_L \\ I_L &= \frac{P_{IN}}{V_t} = \frac{6000}{240} = 25 \text{ A} \quad \text{Ans.} \\ I_f &= \frac{V_t}{r_f} = \frac{240}{100} = 2.4 \text{ A} \quad \text{Ans.} \\ I_a &= I_L - I_f = 25 - 2.4 = 22.6 \text{ A} \quad \text{Ans.} \end{aligned}$$

10.9 A shunt motor connected to a 120-V line runs at a speed of 1200 rpm when the armature current is 20 A (Fig. 10-27). The armature resistance is 0.05 Ω. Assuming constant field flux, what is the speed when the armature current is 60 A?

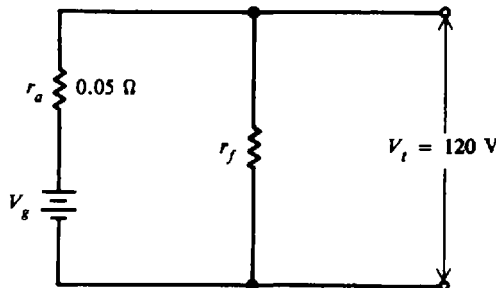


Fig. 10-27

Speed is directly proportional to counter emf.

$$V_{R1} = V_t - I_{a1}r_a = 120 - 20(0.05) = 119 \text{ V}$$

$$V_{R2} = V_t - I_{a2}r_a = 120 - 60(0.5) = 117 \text{ V}$$

$$\frac{V_{g1}}{V_{R2}} = \frac{n_1}{n_2}$$

$$n_2 = \frac{V_{g2}}{V_{R1}} n_1 = \frac{117}{119} 1200 = 1180 \text{ rpm} \quad \text{Ans.}$$

- 10.10** The counter emf of a shunt motor is 218 V, the field resistance is 150  $\Omega$ , and the field current is 1.5 A. The line current is 36.5 A (Fig. 10-28). (a) Find the armature resistance. (b) If the line current during start-up must be limited to 55 A, how much starter resistance must be added in series with the armature? (c) What is the horsepower developed by the motor? If the mechanical and iron losses total 550 W, what is the horsepower output?

(a)  $V_t = I_f r_f = 1.5(150) = 225 \text{ V}$

$$I_a = I_L - I_f = 36.5 - 1.5 = 35 \text{ A}$$

$$I_a r_a + V_g = V_t$$

$$r_a = \frac{V_t - V_g}{I_a} = \frac{225 - 218}{35} = \frac{7}{35} = 0.2 \text{ } \Omega \quad \text{Ans.}$$

(b) Neglecting the field current,

$$\begin{aligned} R_s &= \frac{V_t}{I_s} - r_a = \frac{225}{55} - 0.2 \\ &= 4.09 - 0.20 = 3.89 \text{ } \Omega \quad \text{Ans.} \end{aligned}$$

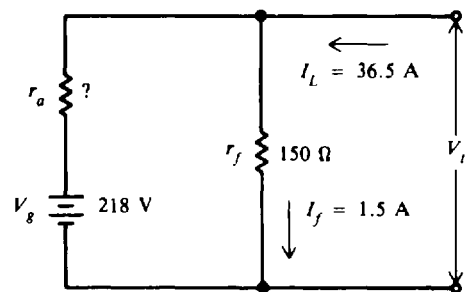


Fig. 10-28

(c) The horsepower of the motor is the horsepower developed by the armature. The power output is the horsepower available at the motor shaft.

$$V_g I_a = 218(35) = 7630 \text{ W}$$

$$1 \text{ hp} = 746 \text{ W}$$

So 
$$\text{hp} = \frac{7630}{746} = 10.2 \quad \text{Ans.}$$

The horsepower output is the horsepower developed by the armature less the power needed to overcome the mechanical or rotational losses of the motor.

$$\text{hp output} = \frac{7630 - 550}{746} = \frac{7080}{746} = 9.5 \quad \text{Ans.}$$

- 10.11** The efficiency at rated load of a 100-hp 600-V shunt motor is 85 percent (0.85) (Fig. 10-29). The field resistance is 190  $\Omega$  and the armature resistance is 0.22  $\Omega$ . The full-load speed is 1200 rpm. Find (a) the rated line current, (b) the field current, (c) the armature current at full load, and (d) the counter emf at full load.

(a) Efficiency =  $\frac{\text{output}}{\text{input}}$

$$\text{Input} = \frac{\text{output}}{\text{efficiency}} = \frac{100(746)}{0.85} = 87\,765 \text{ W}$$

$$V_t I_L = \text{input} = 87\,765 \text{ W}$$

$$I_L = \frac{87\,765}{600} = \frac{87\,865}{600} = 146.3 \text{ A} \quad \text{Ans.}$$

(b)  $I_f = \frac{V_t}{r_f} = \frac{600}{190} = 3.16 \text{ A} \quad \text{Ans.}$

(c)  $I_a = I_L - I_f = 146.3 - 3.2 = 143.1 \text{ A} \quad \text{Ans.}$

(d)  $V_g = V_t - I_a r_a = 600 - 143.1(0.22) = 600 - 31.5 = 568.5 \text{ V} \quad \text{Ans.}$

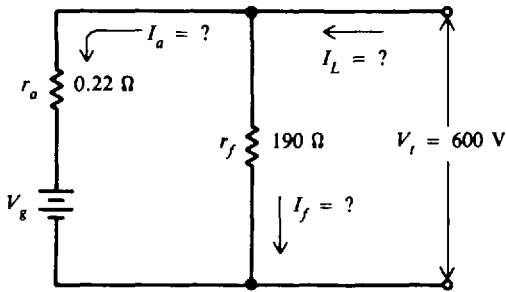


Fig. 10-29

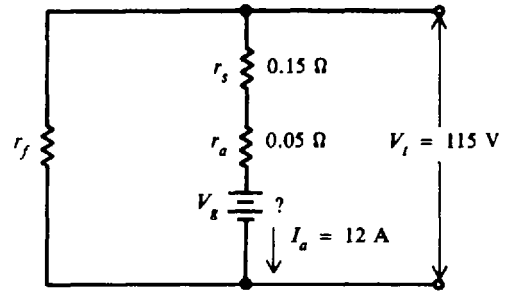


Fig. 10-30

10.12 A long-shunt compound motor has an armature current of 12 A, armature resistance of 0.05 Ω, and a series-field resistance of 0.15 Ω (Fig. 10-30). The motor is connected to a 115-V supply. Find (a) the counter emf and (b) the horsepower developed in the armature.

(a)  $V_t = V_g + I_a(r_a + r_s)$   
 $V_g = V_t - I_a(r_a + r_s) = 115 - 12(0.05 + 0.15) = 115 - 12(0.2) = 115 - 2.4 = 112.6 \text{ V}$      *Ans.*

(b) Developed hp =  $\frac{V_g I_a}{746} = \frac{112.6(12)}{746} = 1.8 \text{ hp}$      *Ans.*

10.13 At full load a 15-hp motor draws 55 A from a 240-V line. (a) What is the motor efficiency? (b) What is the motor efficiency at no load?

(a) Motor input =  $I_L V_t = 55(240) = 13\,200 \text{ W}$   
 Motor output =  $15 \text{ hp} = 15(746) = 11\,190 \text{ W}$   
 Motor efficiency (%) =  $\frac{\text{output}}{\text{input}} \times 100 = \frac{11\,190}{13\,200} \times 100 = 0.848(100) = 84.8\%$      *Ans.*

(b) The output of a motor is considered the power delivered to a load. At no load, motor output is zero. Therefore,

Motor efficiency = 0%     *Ans.*

10.14 At rated load the rotational (iron losses plus mechanical losses) of a 240-V shunt motor are 900 W (Fig. 10-31). The field resistance is 94 Ω and the armature-circuit resistance is 0.15 Ω. The rated motor current is 145 A. Find (a) the field copper loss, (b) the armature copper loss, (c) the rated horsepower output, and (d) the efficiency.

(a)  $I_f = \frac{V_t}{r_f} = \frac{240}{94} = 2.55 \text{ A}$   
 Field copper loss =  $I_f^2 r_f = (2.55)^2(94) = 611 \text{ W}$      *Ans.*

(b)  $I_a = I_L - I_f = 145 - 2.55 = 142.5 \text{ A}$      *Ans.*  
 Armature copper loss =  $I_a^2 r_a = (142.5)^2(0.15) = 3046 \text{ W}$      *Ans.*

(c) Total copper losses =  $611 + 3046 = 3657 \text{ W}$   
 Rotational losses =  $900 \text{ W}$   
 Total losses =  $4557 \text{ W}$   
 Output = input - total losses  
 =  $V_t I_L - \text{total losses} = 240(145) - 4557 = 34\,800 - 4557 = 30\,243 \text{ W}$   
 Rated hp output =  $\frac{30\,243}{746} = 40.5$      *Ans.*

$$\begin{aligned}
 (d) \text{ Efficiency } (\%) &= \frac{\text{output}}{\text{input}} \times 100 \\
 &= \frac{30\,243}{34\,800} 100 = 0.869(100) = 86.9\% \quad \text{Ans.}
 \end{aligned}$$

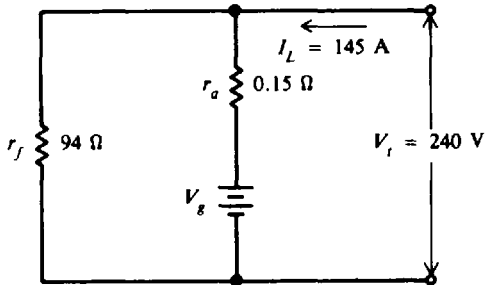


Fig. 10-31

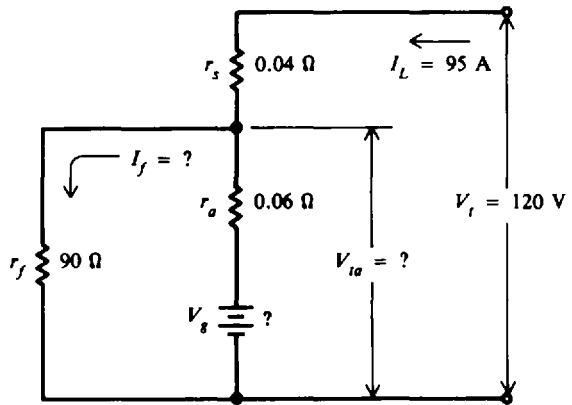


Fig. 10-32

**10.15** A 10-hp short-shunt compound motor is supplied by a 120-V source (Fig. 10-32). The full load current is 95 A. The shunt-field resistance is 90 Ω, the armature resistance is 0.06 Ω and the series-field resistance is 0.04. Find (a) the shunt-field current, (b) the armature current, (c) the counter emf, (d) the efficiency at full load, (e) the full-load copper losses, and (f) the rotational losses.

- (a)  $V_{ta} = V_t - I_L r_s = 120 - 95(0.04) = 116.2 \text{ V}$   
 $I_f = \frac{V_{ta}}{r_f} = \frac{116.2}{90} = 1.29 \text{ A} \quad \text{Ans.}$
- (b)  $I_a = I_L - I_f = 95 - 1.29 = 93.7 \text{ A} \quad \text{Ans.}$
- (c)  $V_g = V_{ta} - I_a r_a = 116.2 - 93.7(0.06) = 110.6 \text{ V} \quad \text{Ans.}$
- (d)  $\text{Efficiency} = \frac{\text{output}}{\text{input}} = \frac{10 \text{ hp}}{V_t I_L} = \frac{10(746)}{120(95)} = \frac{7460}{11\,400} = 0.654$   
 $\text{Efficiency } (\%) = 0.654(100) = 65.4\% \quad \text{Ans.}$
- (e) Shunt-field copper loss =  $I_f^2 r_f = (1.29)^2(90) = 150 \text{ W}$   
 Series-field copper loss =  $I_L^2 r_s = (95)^2(0.04) = 361 \text{ W}$   
 Armature copper loss =  $I_a^2 r_a = (93.7)^2(0.06) = 527 \text{ W}$   
 Total copper loss = 1038 W Ans.
- (f) Total losses = input - output = 11 400 - 7460 = 3940 W  
 Total losses = total copper losses + rotational losses = 3940  
 Rotational losses = 3940 - 1038 = 2902 W Ans.

### Supplementary Problems

- 10.16** How many amperes will a 60-kW 240-V dc generator deliver at full load? Ans. 250 A
- 10.17** What is the full-load kilowatt output of a dc generator if the full-load line current is 30 A and the terminal voltage is 115 V? Ans. 3.45 kW

- 10.18 A shunt generator generates 100 V when its speed is 800 rpm. What emf does it generate if the speed is increased to 1200 rpm, the field flux remaining constant? *Ans.* 150 V
- 10.19 If the generated voltage of a generator is 120 V and the  $IR$  drop in the armature circuit is 5 V, what is the terminal voltage? *Ans.* 115 V
- 10.20 A 240-V shunt generator has a field resistance of 100  $\Omega$ . What is the field current when the generator operates at rated voltage? *Ans.* 2.4 A
- 10.21 A shunt generator is rated at 200 kW at 240 V. (a) What is the full-load current? (b) If the field resistance is 120  $\Omega$ , what is the field current? (c) What is the full-load armature current?  
*Ans.* (a) 833.3 A; (b) 2 A; (c) 835.3 A
- 10.22 In a 50-kW 250-V shunt generator, 260 V is generated in the armature when the generator delivers rated current at rated voltage. The shunt-field current is 4 A. What is the resistance in the armature circuit? *Ans.*  $r_a = 0.049 \Omega$
- 10.23 A shunt generator has a field resistance of 50  $\Omega$  in series with a rheostat. When the terminal voltage of the generator is 110 V, the field current is 2 A. How much resistance is cut in on the shunt-field rheostat? *Ans.* 5  $\Omega$
- 10.24 Find the efficiency at full load of a 50-kW generator when the input is 80 hp. *Ans.* 83.8%
- 10.25 The losses of a 20-kW generator at full load are 5000 W. What is its efficiency? *Ans.* 80%
- 10.26 The full-load losses of a 20-kW 230-V shunt generator are as follows:
- Field  $I^2R$  loss = 200 W  
 Armature  $I^2R$  loss = 1200 W  
 Windage and friction losses = 400 W  
 Iron loss = 350 W
- Find the efficiency at full load. *Ans.* 90.3%
- 10.27 A short-shunt compound generator delivers 210 A to a load at 250 V. Its shunt-field resistance is 24.6  $\Omega$ , its shunt-field rheostat resistance is 6.4  $\Omega$ , its series-field resistance is 0.038  $\Omega$ , and its armature resistance is 0.094  $\Omega$ . Find the copper losses in (a) the shunt-field winding, (b) the shunt-field rheostat, (c) the series field, and (d) the armature winding. (e) If the rotational losses at full load are 800 W, find the efficiency.  
*Ans.* (a) 1704 W; (b) 443 W; (c) 1676 W; (d) 4480 W; (e) 85.2%
- 10.28 The voltage of a 110-V generator rises to 120 V when the load is removed. What is the percent of regulation of the generator? *Ans.* 9.1%
- 10.29 Indicate direction of rotation of the motor armature in Fig. 10-33a and b.  
*Ans.* (a) Clockwise; (b) counterclockwise

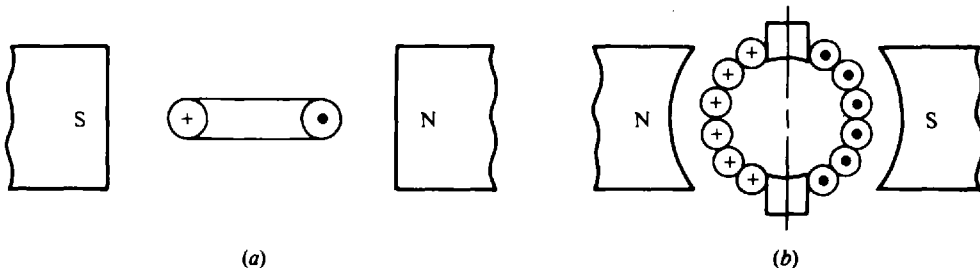


Fig. 10-33

- 10.30** Find the armature current of a shunt motor when the terminal voltage is 110 V, the counter emf is 108 V, and the armature-circuit resistance is  $0.2 \Omega$ . *Ans.* 10 A
- 10.31** A certain shunt motor is connected to a 240-V line. The armature-circuit resistance is  $0.1 \Omega$ . When the armature current is 50 A, what is the counter emf? *Ans.* 235 V
- 10.32** A shunt motor draws a current of 38 A from a 120-V source. The field-circuit resistance is  $50 \Omega$  and the armature-circuit resistance is  $0.25 \Omega$ . Find (a) the field current, (b) the armature current, (c) the counter emf, and (d) the counter emf at start-up.  
*Ans.* (a) 2.4 A; (b) 35.6 A; (c) 111.1 V; (d) 0 V
- 10.33** A 10-hp motor has a shunt-field resistance of  $110 \Omega$  and a field current of 2 A. What is the applied voltage? *Ans.* 220 V
- 10.34** What horsepower is developed by a motor when the armature current is 18 A, the applied voltage is 130 V, and the counter emf is 124 V? *Ans.* 3 hp
- 10.35** A motor has a no-load speed of 900 rpm and a full-load speed of 855 rpm. What is the speed regulation? *Ans.* 5.3%
- 10.36** The armature resistance of a shunt motor is  $0.05 \Omega$ . When the motor is connected across 120 V, it develops a counter emf of 111 V. Find (a) the  $IR$  drop in the armature circuit, (b) the armature current, (c) the armature current if the armature were stationary, and (d) the counter emf when the armature current is 155 A. *Ans.* (a) 9 V; (b)  $I_a = 180$  A; (c)  $I_a = 2400$  A; (d)  $V_r = 112.2$  V
- 10.37** The power input to a shunt motor is 5810 W for a given load on the motor. The terminal voltage is 220 V, the  $I_a R_a$  drop is 5.4 V, and the armature resistance is  $0.25 \Omega$ . Find (a) the counter emf, (b) the power taken by the field, and (c) the field current.  
*Ans.* (a)  $V_r = 214.6$  V; (b) 1056 W; (c)  $I_f = 4.8$  A
- 10.38** A 10-hp short-shunt compound motor is supplied by a 120-V source. The full-load current is 86 A. The shunt-field resistance is  $90 \Omega$ , the armature resistance is  $0.07 \Omega$ , and the series-field resistance is  $0.06 \Omega$ . Find (a) the shunt-field current, (b) the armature current, (c) the counter emf, (d) the efficiency at full load, (e) the full-load copper losses, and (f) the rotational losses.  
*Ans.* (a)  $I_f = 1.28$  A; (b)  $I_a = 84.7$  A; (c)  $V_r = 108.9$  V; (d) 72.3%; (e) 1093 W; (f) 1767 W
- 10.39** If the 10-hp motor of Prob. 10.38 is now connected by *long-shunt* and the parameters given remain the same, find the same quantities.  
*Ans.* (a)  $I_f = 1.33$  A; (b)  $I_a = 84.7$  A; (c)  $V_r = 109.0$  V; (d) 72.3%; (e) 1091 W; (f) 1769 W

## Principles of Alternating Current

### GENERATING AN ALTERNATING VOLTAGE

An ac voltage is one that continually changes in magnitude and periodically reverses in polarity (Fig. 11-1). The zero axis is a horizontal line across the center. The vertical variations on the voltage wave show the changes in magnitude. The voltages above the horizontal axis have positive (+) polarity, while voltages below the horizontal axis have negative (-) polarity.

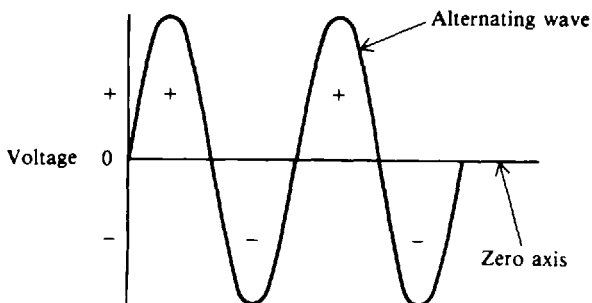


Fig. 11-1 An ac voltage waveform

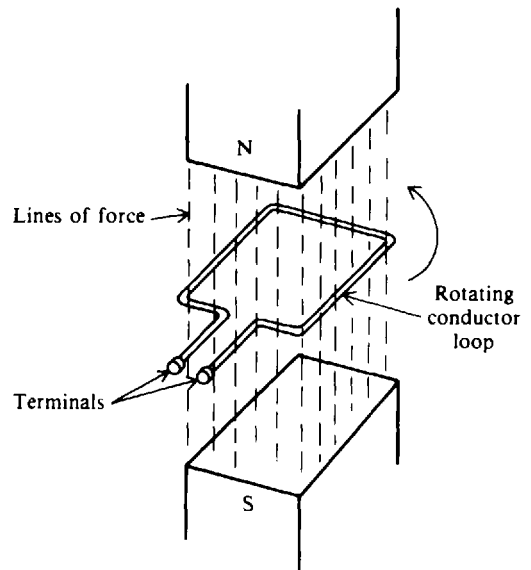


Fig. 11-2 Loop rotating in magnetic field produces an ac voltage

An ac voltage can be produced by a generator, called an *alternator* (Fig. 11-2). In the simplified generator shown, the conductor loop rotates through the magnetic field and cuts lines of force to generate an induced ac voltage across its terminals. One complete revolution of the loop around the circle is a *cycle*. Consider the position of the loop at each quarter turn during a cycle (Fig. 11-3). At position *A*, the loop is traveling parallel to the magnetic flux and therefore cuts no lines of force. The induced voltage is zero. At top position *B*, the loop cuts across the field at  $90^\circ$  to produce maximum voltage. When it reaches *C*, the conductor is again moving parallel to the field and cannot cut across the flux. The ac wave from *A* to *C* is  $\frac{1}{2}$  cycle of revolution, called an *alternation*. In *D*, the loop cuts across the flux again for maximum voltage, but here the flux is cut in the opposite direction (left to right) from *B* (right to left). Thus the polarity at *D* is negative. The loop completes the last quarter turn in the cycle where it returns to position *A*, the point where it started. The cycle of voltage values is repeated in positions *A'B'C'D'A''* as the loop continues to rotate (Fig. 11-3). A cycle includes the variations between two successive points having the same value and varying in the same direction. For example, 1 cycle can be shown also between *B* and *B'* (Fig. 11-3).

### ANGULAR MEASUREMENT

Because the cycles of voltage correspond to rotation of the loop around a circle, parts of the circle are expressed in angles. The complete circle is  $360^\circ$ . One half cycle, or one alternation, is



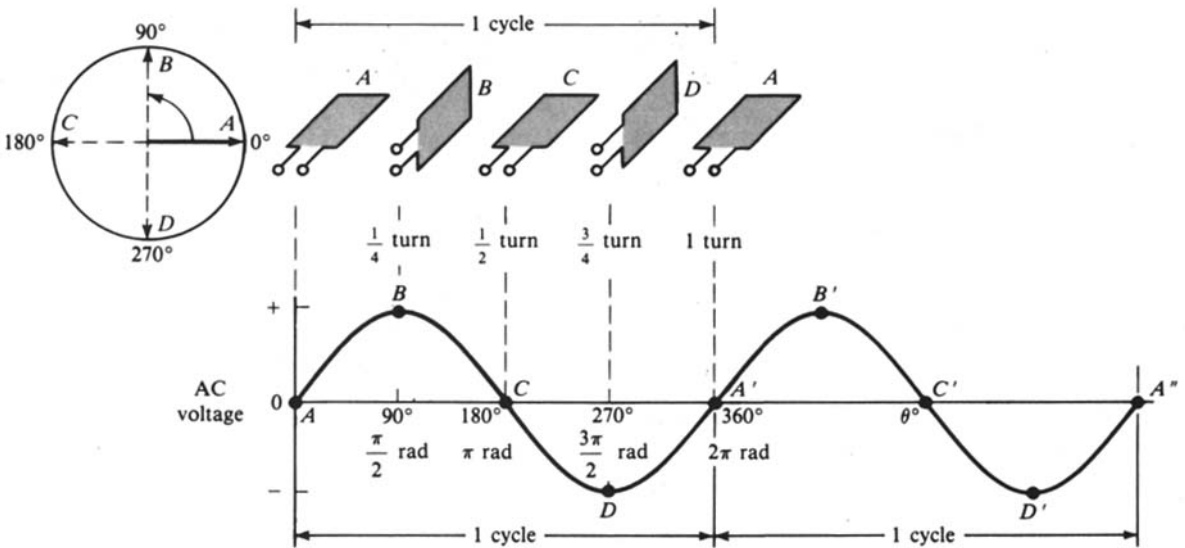


Fig. 11-3 Two cycles of alternating voltage generated by rotating loop. (From B. Grob, *Basic Electronics*, 4th. ed., McGraw-Hill, New York, 1977, p. 313)

180°. A quarter turn is 90°. Degrees are also expressed in *radians* (rad). One radian is equal to 57.3°. A complete circle has  $2\pi$  rad; therefore

$$360^\circ = 2\pi \text{ rad}$$

Then 
$$1^\circ = \frac{\pi}{180} \text{ rad} \tag{11-1}$$

or 
$$1 \text{ rad} = \frac{180^\circ}{\pi} \tag{11-2}$$

In a two-pole generator (Fig. 11-2), the rotation of the armature coil through 360 geometric degrees (1 revolution) will always generate 1 cycle (360°) of ac voltage. But in a four-pole generator, an armature rotation through only 180 geometric degrees will generate 1 ac cycle or 180 electrical degrees. Therefore, the degree markings along the horizontal axis of ac voltage or current refer to *electrical degrees* rather than *geometric degrees*.

**Example 11.1** How many radians are there in 30°?  
Use Eq. (11-1) to convert from degrees into radians.

$$30^\circ = 30^\circ \times \frac{\text{equivalent rad}}{1^\circ} = 30^\circ \times \frac{\pi/180 \text{ rad}}{1^\circ} = \frac{\pi}{6} \text{ rad} \quad \text{Ans.}$$

**Example 11.2** How many degrees are there in  $\pi/3$  rad?  
Use Eq. (11-2) to convert from radians into degrees.

$$\frac{\pi}{3} \text{ rad} = \frac{\pi}{3} \text{ rad} \times \frac{\text{equivalent}^\circ}{1 \text{ rad}} = \frac{\pi}{3} \text{ rad} \times \frac{180^\circ/\pi}{1 \text{ rad}} = 60^\circ \quad \text{Ans.}$$

In most handheld calculators, there is a selector switch to designate angles either in degrees or radians (DEG or RAD), so it normally won't be necessary to convert the angles. However, it is useful to know how the angle conversions can be done.

**SINE WAVE**

The voltage waveform (Fig. 11-3) is called a *sine wave*. The instantaneous value of voltage at any point on the sine wave is expressed by the equation

$$v = V_M \sin \theta \tag{11-3}$$

where  $v$  = instantaneous value of voltage, V  
 $V_M$  = maximum value of voltage, V  
 $\theta$  = angle of rotation, degrees ( $\theta$  is the Greek lowercase letter theta)

**Example 11.3** A sine wave voltage varies from zero to a maximum of 10 V. What is the value of voltage at the instant that the cycle is at 30°? 45°? 60°? 90°? 180°? 270°?  
 Substitute 10 for  $V_M$  in Eq. (11-3):

	$v = 10 \sin \theta$	
At 30°:	$v = 10 \sin 30^\circ = 10(0.5) = 5 \text{ V}$	Ans.
At 45°:	$v = 10 \sin 45^\circ = 10(0.707) = 7.07 \text{ V}$	Ans.
At 60°:	$v = 10 \sin 60^\circ = 10(0.866) = 8.66 \text{ V}$	Ans.
At 90°:	$v = 10 \sin 90^\circ = 10(1) = 10 \text{ V}$	Ans.
At 180°:	$v = 10 \sin 180^\circ = 10(0) = 0 \text{ V}$	Ans.
At 270°:	$v = 10 \sin 270^\circ = 10(-1) = -10 \text{ V}$	Ans.

**ALTERNATING CURRENT**

When a sine wave of alternating voltage is connected across a load resistance, the current that flows in the circuit is also a sine wave (Fig. 11-4).

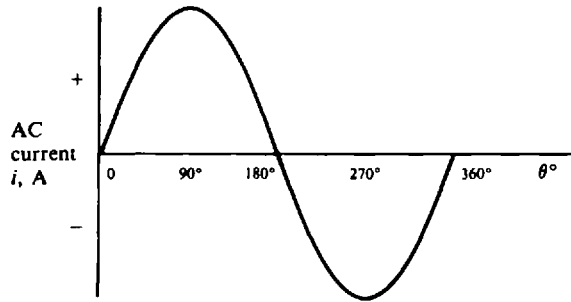


Fig. 11-4 One cycle of alternating current

**Example 11.4** The ac sine wave voltage (Fig. 11-5a) is applied across a load resistance of 10 Ω (Fig. 11-5b). Show the resulting sine wave of alternating current.

The instantaneous value of current is  $i = v/R$ . In a pure resistance circuit, the current waveform follows the polarity of the voltage waveform. The maximum value of current is

$$I_M = \frac{V_M}{R} = \frac{10}{10} = 1 \text{ A}$$

In the form of an equation  $i = I_M \sin \theta$ . (See Fig. 11-6.)

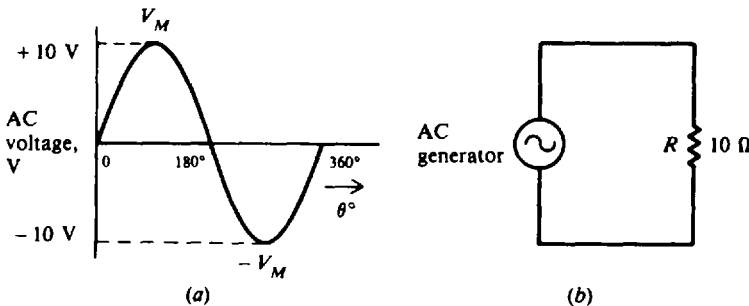


Fig. 11-5 An ac voltage source is applied to a simple resistance circuit


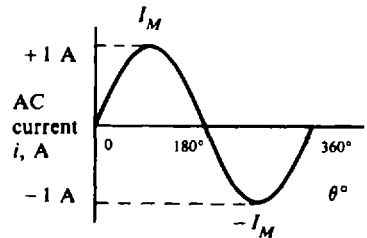


Fig. 11-6

**FREQUENCY AND PERIOD**

The number of cycles per second is called *frequency*. It is indicated by the symbol  $f$  and is expressed in hertz (Hz). One cycle per second equals one hertz. Thus 60 cycles per second (sometimes abbreviated cps) equals 60 Hz. A frequency of 2 Hz (Fig. 11-7b) is twice the frequency of 1 Hz (Fig. 11-7a).

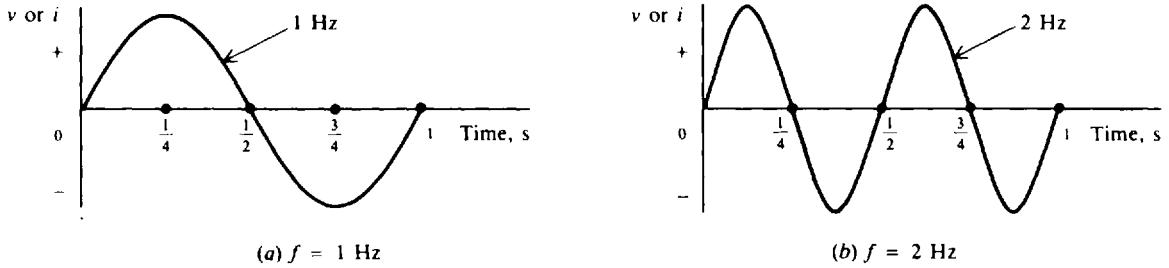

**Fig. 11-7** Comparison of frequencies


The amount of time for the completion of 1 cycle is the *period*. It is indicated by the symbol  $T$  for time and is expressed in seconds (s). Frequency and period are reciprocals of each other.

$$f = \frac{1}{T} \tag{11-4}$$


$$T = \frac{1}{f} \tag{11-5}$$

The higher the frequency, the shorter the period.

The angle of  $360^\circ$  represents the time for 1 cycle, or the period  $T$ . So we can show the horizontal axis of the sine wave in units of either electrical degrees or seconds (Fig. 11-8).

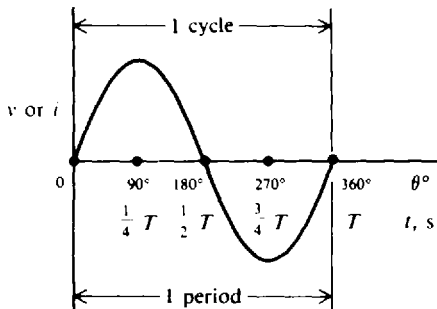

**Fig. 11-8** Relationship between electrical degrees and time

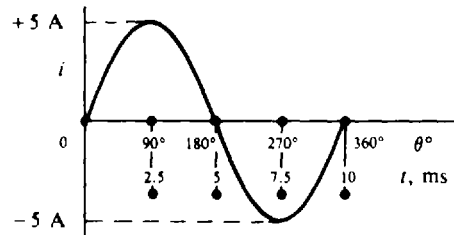

**Fig. 11-9**

**Example 11.5** An ac current varies through one complete cycle in  $1/100$  s. What are the period and frequency? If the current has a maximum value of 5 A, show the current waveform in units of degrees and milliseconds.

$$T = \frac{1}{100} \text{ s} \quad \text{or} \quad 0.01 \text{ s} \quad \text{or} \quad 10 \text{ ms} \quad \text{Ans.}$$

$$f = \frac{1}{T} \tag{11-4}$$

$$= \frac{1}{1/100} = 100 \text{ Hz} \quad \text{Ans.}$$

See Fig. 11-9 for the waveform.

The *wavelength*  $\lambda$  (Greek lowercase lambda) is the length of one complete wave or cycle. It depends upon the frequency of the periodic variation and its velocity of transmission. Expressed as a formula,

$$\lambda = \frac{\text{velocity}}{\text{frequency}} \tag{11-6}$$

For electromagnetic radio waves, the velocity in air or a vacuum is 186 000 mi/s, or  $3 \times 10^8$  m/s, which is the speed of light. Equation (11-6) is written in the familiar form

$$\lambda = \frac{c}{f} \tag{11-7}$$

where  $\lambda$  = wavelength, m  
 $c$  = speed of light,  $3 \times 10^8$  m/s, a constant  
 $f$  = radio frequency, Hz

**Example 11.6** TV Channel 2 has a frequency of 60 MHz. What is its wavelength?  
 Convert  $f = 60$  MHz to  $f = 60 \times 10^6$  Hz and substitute into Eq. (11-7).

$$\lambda = \frac{c}{f} = \frac{3 \times 10^8}{60 \times 10^6} = 5 \text{ m} \quad \text{Ans.}$$

**PHASE RELATIONSHIPS**

The *phase angle* between two waveforms of the same frequency is the angular difference at a given instant of time. As an example, the phase angle between waves *B* and *A* (Fig. 11-10a) is  $90^\circ$ . Take the instant of time at  $90^\circ$ . The horizontal axis is shown in angular units of time. Wave *B* starts at maximum value and reduces to zero value at  $90^\circ$ , while wave *A* starts at zero and increases to maximum value at  $90^\circ$ . Wave *B* reaches its maximum value  $90^\circ$  ahead of wave *A*, so wave *B* leads wave *A* by  $90^\circ$ . This  $90^\circ$  phase angle between waves *B* and *A* is maintained throughout the complete cycle and all successive cycles. At any instant of time, wave *B* has the value that wave *A* will have  $90^\circ$  later. Wave *B* is a cosine wave because it is displaced  $90^\circ$  from wave *A*, which is a sine wave. Both waveforms are called *sinusoids*.

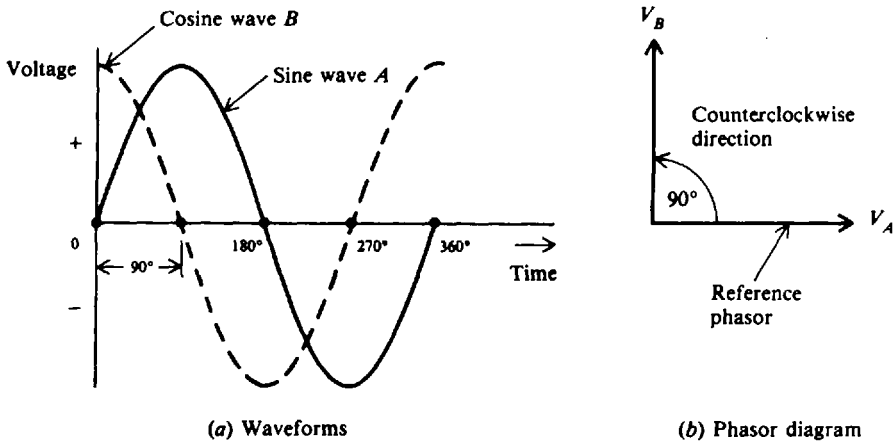


Fig. 11-10 Wave *B* leads wave *A* by a phase angle of  $90^\circ$

**PHASORS**

To compare phase angles or phases of alternating voltages and currents, it is more convenient to use phasor diagrams corresponding to the voltage and current waveforms. A *phasor* is a quantity that has magnitude and direction. The terms *phasor* and *vector* are used for quantities

that have direction. However, a phasor quantity varies with time, while a vector quantity has direction in space. The length of the arrow in a phasor diagram indicates the magnitude of the alternating voltage. The angle of the arrow with respect to the horizontal axis indicates the phase angle. One waveform is chosen as the reference. Then the second waveform can be compared with the reference by means of the angle between the phasor arrows. For example, the phasor  $V_A$  represents the voltage wave  $A$  with a phase angle of  $0^\circ$  (Fig. 11-10b). The phasor  $V_B$  is vertical (Fig. 11-10b) to show the phase angle of  $90^\circ$  with respect to phasor  $V_A$ , which is the reference. Since lead angles are shown in the counterclockwise direction from the reference phasor,  $V_B$  leads  $V_A$  by  $90^\circ$  (Fig. 11-10b).

Generally, the reference phasor is horizontal, corresponding to  $0^\circ$ . If  $V_B$  were shown as the reference (Fig. 11-11b),  $V_A$  would have to be  $90^\circ$  clockwise in order to have the same phase angle. In this case  $V_A$  lags  $V_B$  by  $90^\circ$ . There is no fundamental difference between  $V_B$  leading  $V_A$  by  $90^\circ$  (Fig. 11-11a) or  $V_A$  lagging  $V_B$  by  $90^\circ$  (Fig. 11-11b).

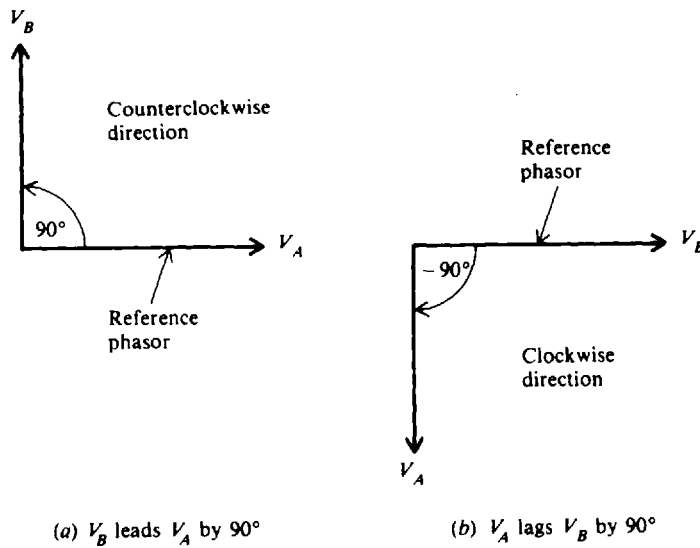


Fig. 11-11 Leading and lagging phase angles

When two waves are in phase (Fig. 11-12a), the phase angle is zero. Then the amplitudes add (Fig. 11-12b). When two waves are exactly out of phase (Fig. 11-13a), the phase angle is  $180^\circ$ . Their amplitudes are opposing (Fig. 11-13b). Equal values of opposite phase cancel each other.

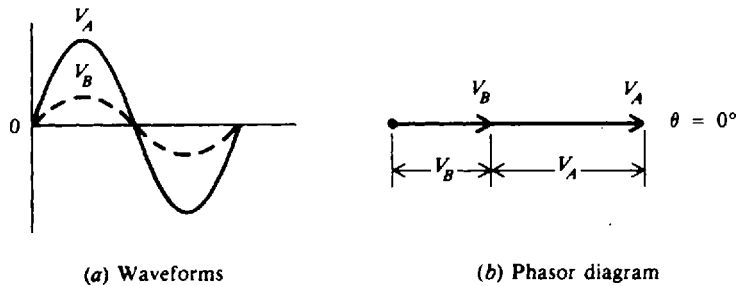


Fig. 11-12 Two waves in phase with angle of  $0^\circ$

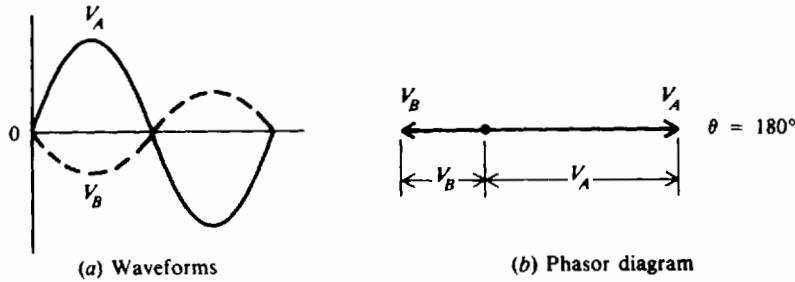


Fig. 11-13 Two waves in opposite phase with angle of 180°

**Example 11.7** What is the phase angle between waves A and B (Fig. 11-14)? Draw the phasor diagram first with wave A as reference and then with wave B as reference.


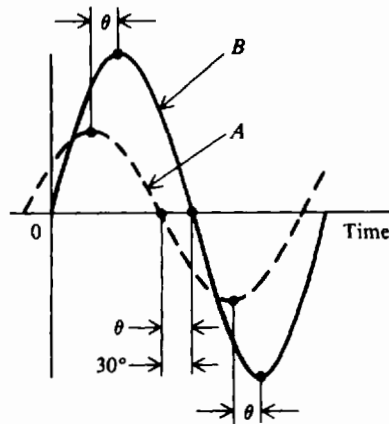



Fig. 11-14 Finding the phase angle between wave A and wave B

The phase angle is the angular distance between corresponding points on waves A and B. Convenient corresponding points are the maximum, minimum, and zero crossing of each wave. At the zero crossings on the horizontal axis (Fig. 11-14), the phase angle  $\theta = 30^\circ$ . Since wave A reaches its zero crossing before wave B does, A leads B.

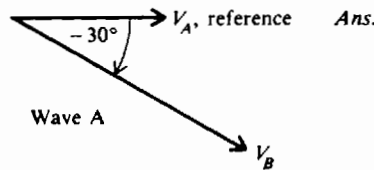Wave A as reference:  $V_B$  lags  $V_A$  by  $30^\circ$ .



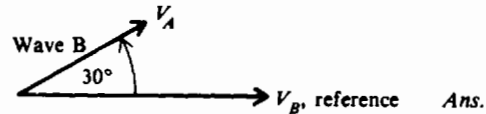Wave B as reference:  $V_A$  leads  $V_B$  by  $30^\circ$ .



Though the phasors are not drawn to scale,  $V_A$  is drawn smaller than  $V_B$  because the maximum value of wave A is less than that of wave B.

**CHARACTERISTIC VALUES OF VOLTAGE AND CURRENT**

Since an ac sine wave voltage or current has many instantaneous values throughout the cycle, it is convenient to specify magnitudes for comparing one wave with another. The peak, average, or root-mean-square (rms) value can be specified (Fig. 11-15). These values apply to current or voltage.

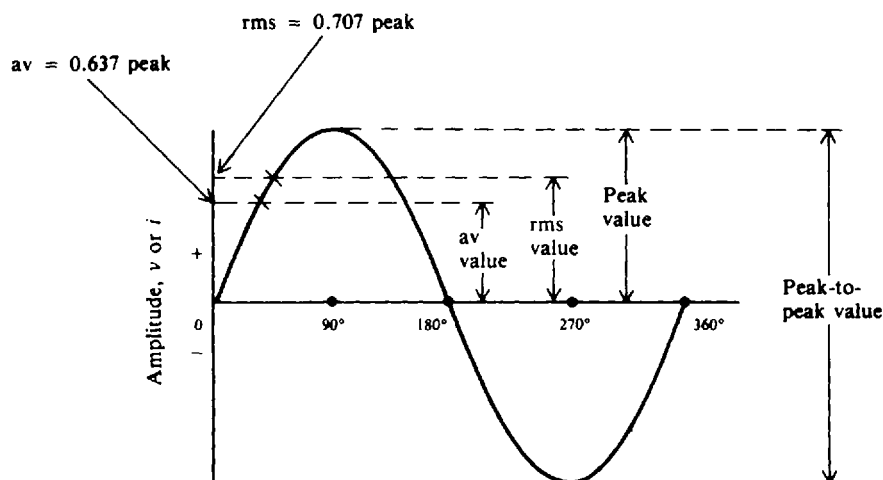


Fig. 11-15 Amplitude values for ac sine wave

The *peak value* is the maximum value  $V_M$  or  $I_M$ . It applies to either the positive or negative peak. The *peak-to-peak (p-p) value* may be specified and is double the peak value when the positive and negative peaks are symmetrical.

The *average value* is the arithmetic average of all values in a sine wave for 1 half-cycle. The half-cycle is used for the average because over a full cycle the average value is zero.

$$\text{Average value} = 0.637 \times \text{peak value} \quad (11-8)$$

or

$$V_{av} = 0.637 V_m$$

$$I_{av} = 0.637 I_M$$

The *root-mean-square value* or *effective value* is 0.707 times the peak value.

$$\text{RMS value} = 0.707 \times \text{peak value} \quad (11-9)$$

or

$$V_{rms} = 0.707 V_M$$

$$I_{rms} = 0.707 I_M$$

The rms value of an alternating sine wave corresponds to the same amount of direct current or voltage in heating power. An alternating voltage with an rms value of 115 V, for example, is just as effective in heating the filament of a light bulb as 115 V from a steady dc voltage source. For this reason, the rms value is also called the effective value.

Unless indicated otherwise, all sine wave ac measurements are given in rms values. The letters  $V$  and  $I$  are used to denote rms voltage and current. For instance,  $V = 220 \text{ V}$  (an ac power-line voltage) is understood to mean 220 V rms.

Use Table 11-1 as a convenient way to convert from one characteristic value to another.

Table 11-1 Conversion Table for AC Sine Wave Voltage and Current

Multiply the Value	By	To Get the Value
Peak	2	Peak-to-peak
Peak-to-peak	0.5	Peak
Peak	0.637	Average
Average	1.570	Peak
Peak	0.707	RMS (effective)
RMS (effective)	1.414	Peak
Average	1.110	RMS (effective)
RMS (effective)	0.901	Average

**Example 11.8** If the peak voltage for an ac wave is 60 V, what are its average and rms values?

$$\begin{aligned} \text{Average value} &= 0.637 \times \text{peak value} && (11-8) \\ &= 0.637(60) = 38.2 \text{ V} && \text{Ans.} \end{aligned}$$

$$\begin{aligned} \text{RMS value} &= 0.707 \times \text{peak value} && (11-9) \\ &= 0.707(60) = 42.4 \text{ V} && \text{Ans.} \end{aligned}$$

**Example 11.9** It is often necessary to convert from rms to peak value. Develop the formula. Start with

$$\text{RMS value} = 0.707 \times \text{peak value} \quad (11-9)$$

Then invert:

$$\text{Peak value} = \frac{1}{0.707} \times \text{rms value} = 1.414 \times \text{rms value}$$

or

$$\begin{aligned} V_M &= 1.414 V_{rms} \\ I_M &= 1.414 I_{rms} \end{aligned}$$

Verify this relationship by referring to Table 11-1.

**Example 11.10** A commercial ac power-line voltage is 240 V. What are the peak and peak-to-peak voltages?


AC measurements are given in rms values unless noted otherwise. From Table 11-1,

$$V_M = 1.414 V_{rms} = 1.414(240) = 339.4 \text{ V} \quad \text{Ans.}$$


$$V_{p-p} = 2V_M = 2(339.4) = 678.8 \text{ V} \quad \text{Ans.}$$

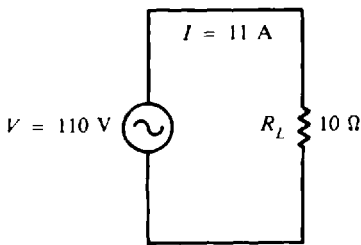**RESISTANCE IN AC CIRCUITS**


In an ac circuit with only resistance, the current variations are in phase with the applied voltage (Fig. 11-16). This in-phase relationship between  $V$  and  $I$  means that such an ac circuit can be analyzed by the same methods used for dc circuits. Therefore, Ohm's laws for dc circuits are applicable also to ac circuits with resistance only. The calculations in ac circuits are generally in rms values, unless otherwise specified. For the series circuit (Fig. 11-16a),  $I = V/R = 110/10 = 11 \text{ A}$ . The rms power dissipation is  $P = I^2R = 11^2(10) = 1210 \text{ W}$ .



(a) Schematic diagram

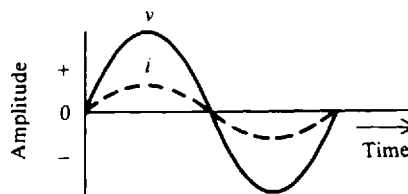

(b) Waveforms of  $i$  and  $v$

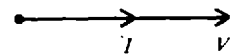

(c) Phasor diagram.  $I$  in phase with  $V$

**Fig. 11-16** AC circuit with only resistance

**Example 11.11** A 110-V ac voltage is applied across 5- and 15- $\Omega$  resistances in series (Fig. 11-17a). Find the current and voltage drop across each resistance. Draw the phasor diagram.

Use Ohm's law.

$$R_T = R_1 + R_2 = 5 + 15 = 20 \Omega$$

$$I = \frac{V}{R_T} = \frac{110}{20} = 5.5 \text{ A} \quad \text{Ans.}$$



$$V_1 = IR_1 = 5.5(5) = 27.5 \text{ V} \quad \text{Ans.}$$

$$V_2 = IR_2 = 5.5(15) = 82.5 \text{ V} \quad \text{Ans.}$$

Since the ac voltages  $V_1$  and  $V_2$  are in phase, phasors  $V_1$  and  $V_2$  are added to obtain phasor  $V$ . See Fig. 11-17b. The length of each phasor is proportional to its magnitude.  $I$  is in phase with  $V$ .

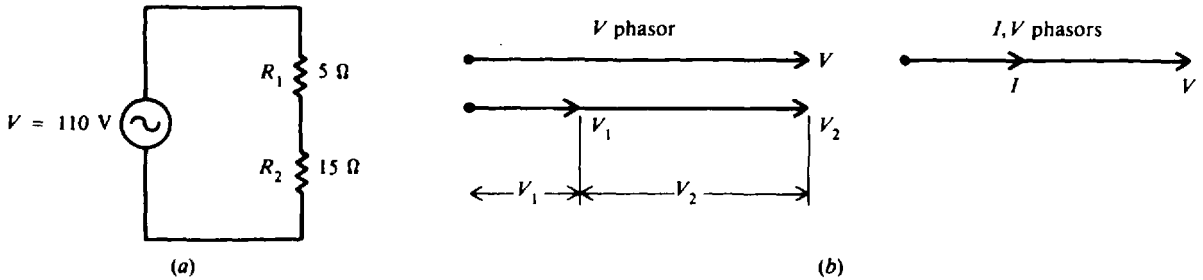


Fig. 11-17

### Solved Problems

11.1 Find the instantaneous current when  $\theta = 30^\circ$  and  $225^\circ$  for the ac current wave (Fig. 11-18), and locate these points on the waveform.

It is seen that  $I_M = 100 \text{ mA}$ . The current wave is then

$$i = I_M \sin \theta = 100 \sin \theta$$

At  $\theta = 30^\circ$ :  $i = 100 \sin 30^\circ = 100(0.5) = 50 \text{ mA}$  **Ans.**

At  $\theta = 225^\circ$ :  $i = 100 \sin 225^\circ = 100(-0.707) = -70.7 \text{ mA}$  **Ans.**

See Fig. 11-19.

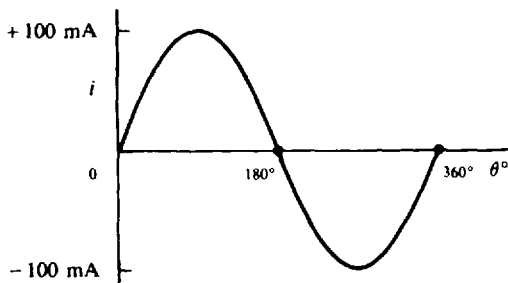


Fig. 11-18 Alternating-current waveform

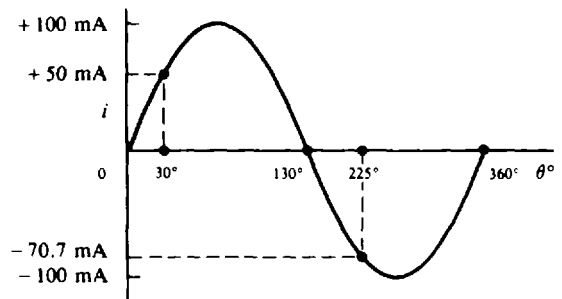


Fig. 11-19

11.2 Many ac waves (e.g., sine wave, square wave) can be produced by a device called a *signal generator*. This unit usually can generate an ac voltage with a frequency as low as 20 Hz or as high as 200 MHz. Three basic control knobs are function, frequency, and amplitude. The operator selects the controls to produce a sine wave (function) at 100 kHz (frequency) with 5 V amplitude (maximum value). Draw 2 cycles of the ac voltage generated. Show both degrees and time units on the horizontal axis.

To obtain time units, solve for the period  $T$ , using Eq. (11-5).

$$T = \frac{1}{f} = \frac{1}{100 \times 10^3} = 10 \times 10^{-6} \text{ s} = 10 \mu\text{s}$$

Now draw the sine wave of voltage (Fig. 11-20).

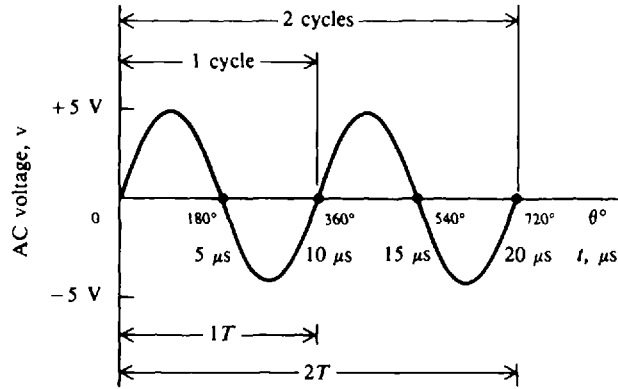


Fig. 11-20 AC voltage wave

11.3 Calculate the time delay for a phase angle of 45° at a frequency of 500 Hz.

Find the period that corresponds to the time for 1 cycle of 360°, and then find the proportional part of the period that corresponds to 45°.

$$T = \frac{1}{f} \tag{11-5}$$

$$= \frac{1}{500} = 2 \times 10^{-3} = 2 \text{ ms}$$

At  $\theta = 45^\circ$ :  $t = \frac{45^\circ}{360^\circ}(2 \text{ ms}) = 0.25 \text{ ms}$       *Ans.*

11.4 The sine wave of an alternating current shows a maximum value of 80 A. What value of dc current will produce the same heating effect?

If an ac wave produces as much heat as 1 A of direct current, we say that the ac wave is as effective as 1 A of direct current. So

$$I_{dc} = I_{rms} = 0.707 I_M \tag{11-9}$$

$$= 0.707(80) = 56.6 \text{ A} \quad \textit{Ans.}$$

11.5 If an ac voltage has a peak value of 155.6 V, what is the phase angle at which the instantaneous voltage is 110 V?

Write  $v = V_M \sin \theta$  (11-3)

Solve for  $\theta$ :  $\sin \theta = \frac{v}{V_M}$

$$\theta = \arcsin \frac{v}{V_M} = \arcsin \frac{110}{155.6} = 0.707 = 45^\circ \quad \textit{Ans.}$$

11.6 The frequency of the audio range extends from 20 Hz to 20 kHz. Find the range of period and wavelength over the range of audio frequencies.

Range of  $T$ :  $T = \frac{1}{f}$  (11-5)

At 20 Hz:  $T = \frac{1}{20} = 0.05 \text{ s} = 50 \text{ ms}$

At 20 kHz:  $T = \frac{1}{20 \times 10^3} = 0.05 \text{ ms}$

So  $T$  is from 0.05 to 50 ms      *Ans.*

Range of  $\lambda$ : 
$$\lambda = \frac{c}{f} \tag{11-7}$$

where  $c = \text{speed of light at } 3 \times 10^8 \text{ m/s}$

At 20 Hz: 
$$\lambda = \frac{3 \times 10^8}{20} = 15 \times 10^6 \text{ m}$$

At 20 kHz: 
$$\lambda = \frac{3 \times 10^8}{20 \times 10^3} = 15 \times 10^3 \text{ m}$$

So  $\lambda$  is from  $15 \times 10^3$  to  $15 \times 10^6 \text{ m}$  *Ans.*

11.7 Find the phase angle for the following ac waves (Fig. 11-21) and draw their phasor diagrams.


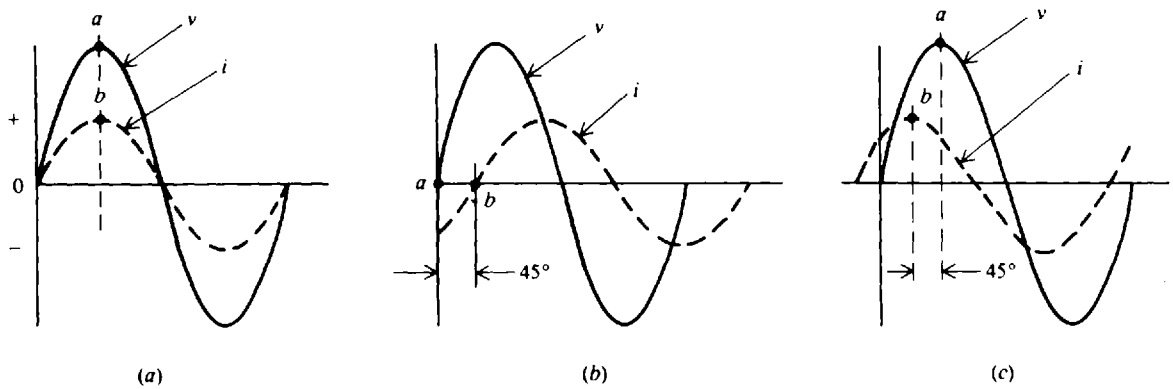



Fig. 11-21 Finding the phase angle between voltage and current waveforms

To determine the phase angle, select a corresponding point on each wave. The maximum and zero crossing corresponding points are convenient. The angular difference of the two points is the phase angle. Then compare the two points to decide if one wave is in phase with, leading, or lagging the other wave.

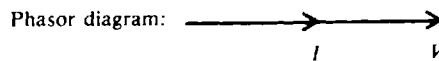
In Fig. 11-21a, curves  $v$  and  $i$  reach their maximum values at the same instant, so they are in phase (the phasor diagram is as shown).



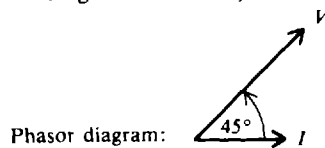In Fig. 11-21b curve  $v$  reaches its zero value at  $a$ ,  $45^\circ$  before curve  $i$  is zero at the corresponding point  $b$ , so  $v$  leads  $i$  by  $45^\circ$  (phasor diagram as shown).



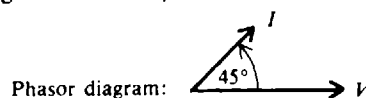In Fig. 11-21c, curve  $i$  reaches its maximum at  $b$  before curve  $v$  reaches its maximum at  $a$  so  $i$  leads  $v$  by  $45^\circ$  (phasor diagram as shown).



11.8 A, B, and C are three sine ac voltage waveforms of the same frequency. Sine wave A leads sine wave B by a phase angle of  $60^\circ$  and lags sine wave C by  $130^\circ$ . What is the phase angle between wave B and wave C? Which wave is leading?

Draw the sine waves with phase angles described. A convenient way to draw or measure the phase angle between two sine waves is to compare their zero crossings. Wave A is drawn as the reference beginning at 0° (Fig. 11-22). Wave B is drawn beginning at 60° to indicate that wave A leads wave B by 60°. Wave C is shown beginning at -130° to show that A lags C by that angle. Compare the zero crossings on the horizontal axis of waves B and C as they move toward the positive cycle. B crosses the axis upward at 60°, while C does so at 230°. The phase angle is the phase difference between 230° and 60°, or 170°. Since B crosses the axis before wave C, B leads C.

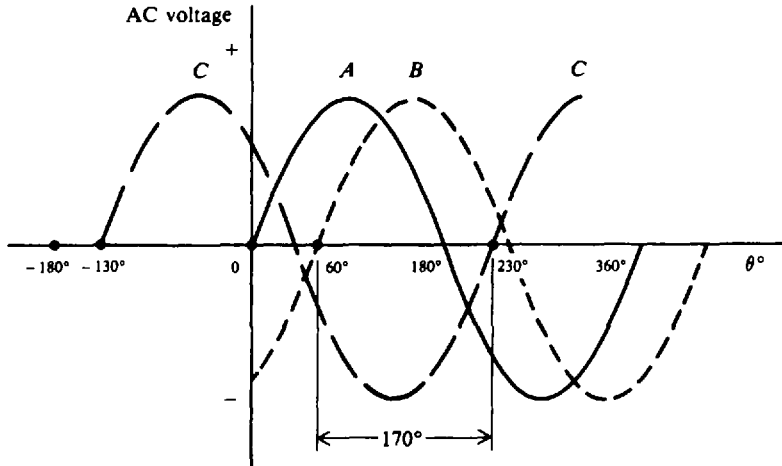


Fig. 11-22 Measuring phase angle between sine waves

**11.9** Alternating-current and voltage meters are always calibrated to read effective values. An ac voltmeter indicates that the voltage across a resistive load is 40 V. What is the peak voltage across this load?

From Table 11-1,

$$V_M = 1.414 V \quad (\text{effective or rms value is understood for } V)$$

$$= 1.414(40) = 56.6 V \quad \text{Ans.}$$

**11.10** The current through an incandescent lamp is measured with an ac ammeter and found to be 0.95 A. What is the average value of this current?

From Table 11-1,

$$I_{av} = 0.901 I \quad (\text{effective or rms value is understood for } I)$$

$$= 0.901(0.95) = 0.86 A \quad \text{Ans.}$$

**11.11** Find  $V$ , period  $T$ , frequency  $f$ , and peak-to-peak voltage  $V_{p-p}$  of the voltage waveform shown (Fig. 11-23).

Use Eq. (11-9).

$$V = 0.707 V_M = 0.707(48 \mu V) = 33.9 \mu V \quad \text{Ans.}$$

The time for 1 cycle is  $5 \mu s$ . Therefore,

$$T = 5 \mu s = 5 \times 10^{-6} s \quad \text{Ans.}$$

$$f = \frac{1}{T} \tag{11-4}$$

$$= \frac{1}{5 \times 10^{-6}} = 200 \times 10^3 \text{ Hz} = 200 \text{ kHz} \quad \text{Ans.}$$

The ac wave is symmetric with respect to the horizontal axis. So

$$V_{p-p} = 2V_M = 2(48) = 96 \mu V \quad \text{Ans.}$$

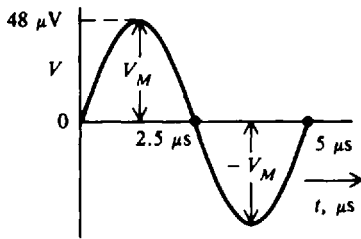


Fig. 11-23 Finding characteristics of a sine wave

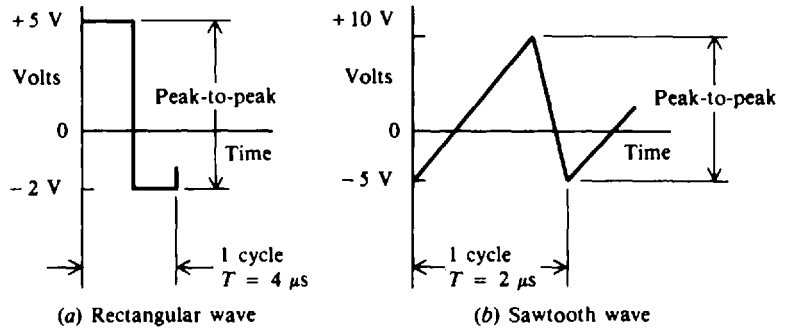


Fig. 11-24 Nonsinusoidal waveforms

11.12 Any waveform that is not a sine or cosine wave is a *nonsinusoidal* waveform. Common examples are the rectangular and sawtooth waves (Fig. 11-24). What are the peak-to-peak voltages for these particular waves?

Peak-to-peak amplitudes, measured between the maximum and minimum peak values, are generally used for measuring nonsinusoidal wave shapes since they often have nonsymmetrical peaks. By inspection of Fig. 11-24.

Rectangular wave:  $V_{p-p} = 5 + 2 = 7 \text{ V}$       *Ans.*

Sawtooth wave:  $V_{p-p} = 10 + 5 = 15 \text{ V}$       *Ans.*

11.13 Calculate the frequency of the nonsinusoidal waveforms shown in Fig. 11-24.

The period  $T$  for a complete cycle is  $4 \mu\text{s}$  (Fig. 11-24a) and  $2 \mu\text{s}$  (Fig. 11-24b).

$$f = \frac{1}{T} \quad \text{also for periodic nonsinusoids}$$

Rectangular wave:  $f = \frac{1}{4 \mu\text{s}} = 0.25 \text{ MHz}$       *Ans.*

Sawtooth wave:  $f = \frac{1}{2 \mu\text{s}} = 0.5 \text{ MHz}$       *Ans.*

11.14 A 120-V ac voltage is applied across a  $20\text{-}\Omega$  resistive load (Fig. 11-25). Find values of  $I$ ,  $V_M$ ,  $V_{p-p}$ ,  $V_{av}$ ,  $I_M$ ,  $I_{p-p}$ ,  $I_{av}$ , and  $P$ .

By Ohm's law,

$$I = \frac{V}{R_L} = \frac{120}{20} = 6 \text{ A} \quad \text{Ans.}$$

Use Table 11-1 to calculate voltage and current values.

$$V_M = 1.414 V = 1.414(120) = 169.7 \text{ V} \quad \text{Ans.}$$

$$V_{p-p} = 2V_M = 2(169.7) = 339.4 \text{ V} \quad \text{Ans.}$$

$$V_{av} = 0.637 V_M = 0.637(169.7) = 108.3 \text{ V} \quad \text{Ans.}$$


$$I_M = 1.414 I = 1.414(6) = 8.5 \text{ A} \quad \text{Ans.}$$

$$I_{p-p} = 2I_M = 2(8.5) = 17.0 \text{ A} \quad \text{Ans.}$$


$$I_{av} = 0.637 I_M = 0.637(8.5) = 5.4 \text{ A} \quad \text{Ans.}$$

$$P = I^2 R_L = 6^2(20) = 720 \text{ W} \quad \text{Ans.}$$

or  $P = \frac{V^2}{R_L} = \frac{120^2}{20} = 720 \text{ W}$       or  $P = VI = 120(6) = 720 \text{ W}$       *Ans.*

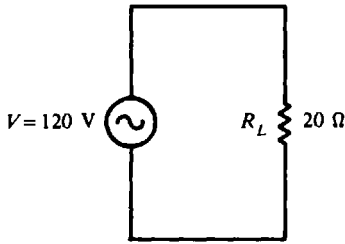

**Fig. 11-25** AC source with single resistance load

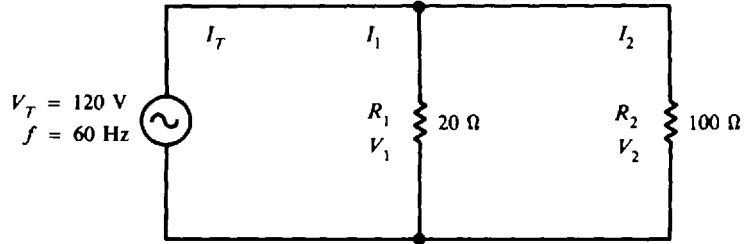

**Fig. 11-26** AC source in parallel circuit

**11.15** A 20-Ω electric iron and a 100-Ω lamp are connected in parallel across a 120-V 60-Hz ac line (Fig. 11-26). Find the total current, the total resistance, and the total power drawn by the circuit, and draw the phasor diagram.

For a parallel circuit,  $V_T = V_1 = V_2 = 120 \text{ V}$ .

$$I_1 = \frac{V_1}{R_1} = \frac{120}{20} = 6 \text{ A} \quad I_2 = \frac{V_2}{R_2} = \frac{120}{100} = 1.2 \text{ A}$$

Then


$$I_T = I_1 + I_2 = 6 + 1.2 = 7.2 \text{ A} \quad \text{Ans.}$$

$$R_T = \frac{V_T}{I_T} = \frac{120}{7.2} = 16.7 \text{ Ω} \quad \text{Ans.}$$

In a purely resistive set of branch currents, the total current  $I_T$  is in phase with the total voltage  $V_T$ . The phase angle is therefore equal to  $0^\circ$ .


$$P = V_T I_T \cos \theta = 120(7.2)(\cos 0^\circ) = 120(7.2)(1) = 864 \text{ W} \quad \text{Ans.}$$

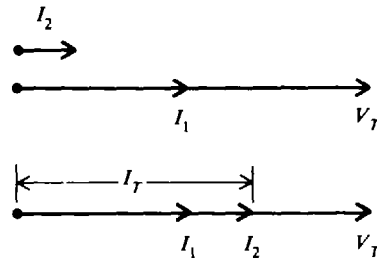Since the voltage in a parallel circuit is constant, the voltage is used as the reference phasor. The currents  $I_1$  and  $I_2$  are drawn in the same direction as the voltage because the current through pure resistances is in phase with the voltage. The  $I_1$  phasor is shown longer than  $I_2$  because its current value is higher (see the phasor diagram).



Phasor diagram

**11.16** A series-parallel ac circuit has two branches across the 60-Hz 120-V power line (Fig. 11-27). Find  $I_1, I_2, I_3, V_1, V_2,$  and  $V_3$ . (Double-ended arrows are sometimes used to indicate direction for ac current.)

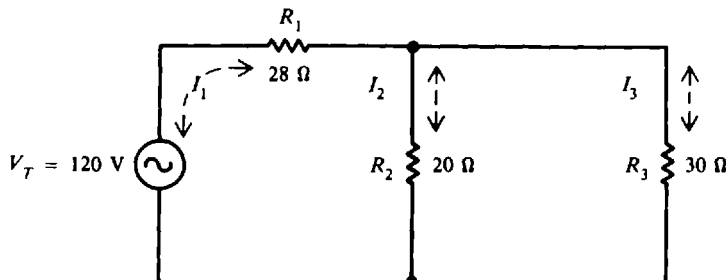

**Fig. 11-27** AC source in series-parallel circuit

Proceed to solve the ac circuit with resistance only in the same manner as a dc circuit.

**Step 1:** Simplify the circuit to a single resistance  $R_T$ .



$$R_a = \frac{R_2 R_3}{R_2 + R_3} = \frac{20(30)}{20 + 30} = \frac{600}{50} = 12 \Omega$$

$$R_T = R_1 + R_a = 12 + 28 = 40 \Omega$$

**Step 2:** Solve for the total current  $I_T$ .

$$I_T = \frac{V_T}{R_T} = I_1 = \frac{120}{40} = 3 \text{ A} \quad \text{Ans.}$$

**Step 3:** Solve for the branch currents  $I_2$  and  $I_3$ .

$$I_2 = \frac{R_3}{R_2 + R_3} I_T = \frac{30}{50} 3 = 1.8 \text{ A} \quad \text{Ans.}$$

$$I_3 = I_T - I_2 = 3 - 1.8 = 1.2 \text{ A} \quad \text{Ans.}$$

**Step 4:** Solve for the branch voltages  $V_2$  and  $V_3$ .

$$V_1 = I_1 R_1 = 3(28) = 84 \text{ V} \quad \text{Ans.}$$

$$V_2 = V_3 = I_3 R_2 = 1.2(20) = 36 \text{ V} \quad \text{Ans.}$$

**Step 5:** Verify answer on voltage division.

$$V_T = V_1 + V_2$$

$$120 = 84 + 36$$

$$120 \text{ V} = 120 \text{ V} \quad \text{Check}$$

### Supplementary Problems

11.17 The peak voltage of an ac sine wave is 100 V. Find the instantaneous voltage at 0, 30, 60, 90, 135, and 245°. Plot these points and draw the sine wave voltage. *Ans.* See Fig. 11-28.

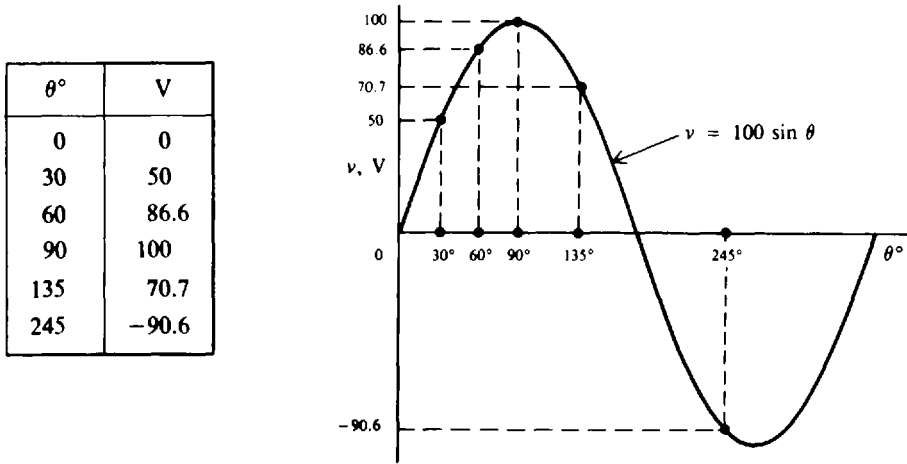


Fig. 11-28

11.18 If an ac voltage wave has an instantaneous value of 90 V at 30°, find the peak value.  
*Ans.*  $V_M = 180$  V

11.19 An ac wave has an effective value of 50 mA. Find the maximum value and the instantaneous value at 60°. *Ans.*  $I_M = 70.7$  mA;  $i = 61.2$  mA

11.20 An electric stove draws 7.5 A from a 120-V dc source. What is the maximum value of an alternating current which will produce heat at the same rate? Find the power drawn from the ac line.  
*Ans.*  $I_M = 10.6$  A;  $P = 900$  W

11.21 Calculate  $V$ ,  $V_{p-p}$ ,  $T$ , and  $f$  for the sine wave voltage in Fig. 11-29.  
*Ans.*  $V = 38.2 \mu\text{V}$ ;  $V_{p-p} = 108 \mu\text{V}$ ;  $T = 2 \mu\text{s}$ ;  $f = 0.5$  MHz

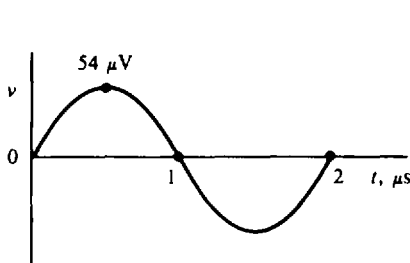


Fig. 11-29

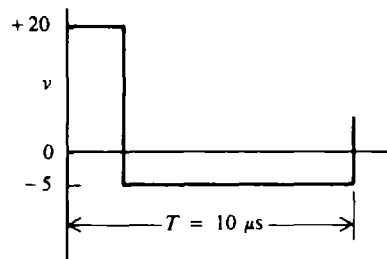


Fig. 11-30


11.22 What is the peak-to-peak voltage and frequency of the nonsymmetrical rectangular waveform in Fig. 11-30? *Ans.*  $V_{p-p} = 25$  V;  $f = 0.1$  MHz

11.23 Find the instantaneous voltage at 45° in a wave whose peak value is 175 V. *Ans.*  $V = 123.7$  V

11.24 Find the peak value of an ac wave if the instantaneous current is 35 A at 30°. *Ans.*  $I_M = 70$  A



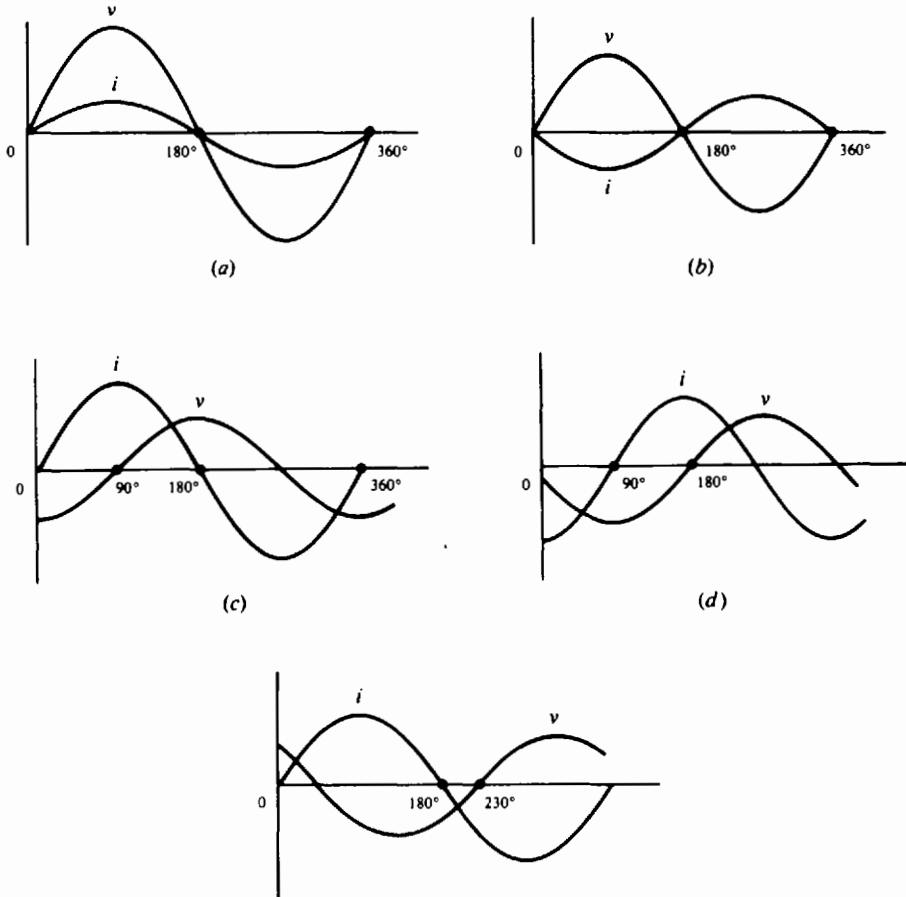
- 11.25 Find the phase angle at which an instantaneous voltage of 36.5 V appears in a wave whose peak value is 125 V. *Ans.*  $\theta = 17^\circ$
- 11.26 What is the period of an ac voltage that has a frequency of (a) 50 Hz, (b) 95 kHz, and (c) 106 kHz? *Ans.* (a)  $T = 0.02$  s; (b)  $T = 0.0105$  ms; (c)  $T = 0.00943$  ms or  $9.43 \mu\text{s}$
- 11.27 Find the frequency of an ac current when its period is (a) 0.01 s, (b) 0.03 ms, and (c) 0.006 ms. *Ans.* (a)  $f = 100$  Hz; (b)  $f = 33.3$  kHz; (c)  $f = 166.7$  kHz
- 11.28 What is the wavelength of radio station WMAL which broadcasts FM (frequency modulation) at a frequency of 107.3 kHz? *Ans.*  $\lambda = 2796$  m
- 11.29 What is the wavelength of an ac wave whose frequency is (a) 60 Hz, (b) 1 kHz, (c) 30 kHz, and (d) 800 kHz? *Ans.* (a)  $\lambda = 5 \times 10^6$  m; (b)  $\lambda = 3 \times 10^5$  m; (c)  $\lambda = 10\,000$  m; (d)  $\lambda = 375$  m
- 11.30 Find the frequency of a radio wave whose wavelength is (a) 600 m, (b) 2000 m, (c) 3000 m, and (d) 6000 m. *Ans.* (a)  $f = 500$  kHz; (b)  $f = 150$  kHz; (c)  $f = 100$  kHz; (d)  $f = 50$  kHz
- 11.31 Determine the phase angle for each ac wave shown (Fig. 11-31) and draw its phasor. One cycle is shown for each wave. Show  $I$  as the reference phasor.



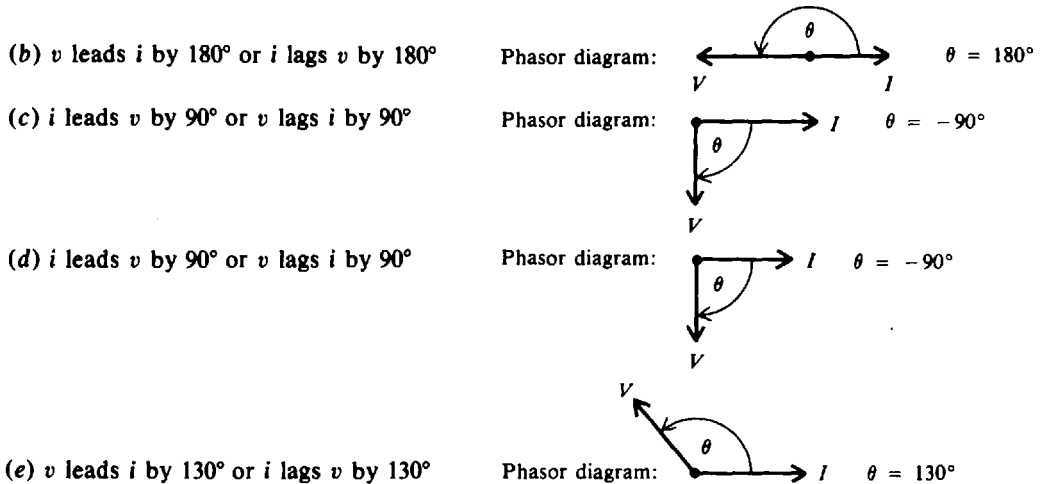(e)  
Fig. 11-31

*Ans.* (a)  $v$  and  $i$  are in phase

Phasor diagram:  $\bullet \xrightarrow{\quad} \xrightarrow{\quad} \bullet \quad \theta = 0^\circ$   
 $I \qquad V$



11.32 The ac power line delivers 120 V to your home. This is the voltage as measured by an ac voltmeter. What is the peak value of this voltage?      Ans.  $V_M = 169.7$  V

11.33 An industrial oven draws 8.5 A from a 120-V dc source. What is the maximum value of an ac current which will heat at the same rate?      Ans.  $I_M = 12.0$  A

11.34 Find the values indicated.

	Peak Value	RMS Value	Average Value	Phase Angle	Instantaneous Value
(a)	45 A	?	?	$45^\circ$	?
(b)	?	220 V	?	$60^\circ$	?
(c)	?	?	10 A	$30^\circ$	?
(d)	200 V	?	?	$60^\circ$	?
(e)	?	110 V	?	$75^\circ$	?
(f)	?	?	?	$15^\circ$	75.1 V
(g)	100 V	?	?	?	86.6 V
(h)	?	?	20 A	?	15.7 A
(i)	?	30 A	?	?	30 A
(j)	?	?	100.1 V	?	136.1 V


Ans.

	Peak Value	RMS Value	Average Value	Phase Angle	Instantaneous Value
(a)	....	31.8 A	28.7 A	....	31.8 A
(b)	311.1 V	....	198.2 V	....	269.4 V
(c)	15.7 A	11.1 A	....	....	7.85 A
(d)	....	141.4 V	127.4 V	....	173.2 V
(e)	155.6 V	....	99.1 V	....	150.3 V
(f)	290.2 V	205.2 V	184.9 V	....	....
(g)	....	141.4 V	63.7 V	$60^\circ$	....
(h)	31.4 V	22.2 A	....	$30^\circ$	....
(i)	42.4 A	....	27.0 A	$45^\circ$	....
(j)	157.1 V	111.1 V	....	$60^\circ$	....


11.35 An ac ammeter reads 22 A rms current through a resistive load, and a voltmeter reads 385 V rms drop across the load. What are the peak values and the average values of the alternating current and voltage? *Ans.*  $I_M = 31.1 \text{ A}$ ;  $V_M = 545 \text{ V}$ ;  $I_{av} = 19.8 \text{ A}$ ;  $V_{av} = 347 \text{ V}$

11.36 An ac power line delivers 240 V to a sidewalk heating cable that has a total resistance of 5  $\Omega$ . Find  $I$ ,  $V_M$ ,  $V_{p-p}$ ,  $V_{av}$ ,  $I_M$ ,  $I_{p-p}$ ,  $I_{av}$ , and  $P$ .  
*Ans.*  $I = 48 \text{ A}$ ;  $V_M = 339 \text{ V}$ ;  $V_{p-p} = 678 \text{ V}$ ;  $V_{av} = 216 \text{ V}$ ;  
 $I_M = 67.9 \text{ A}$ ;  $I_{p-p} = 135.8 \text{ A}$ ;  $I_{av} = 43.3 \text{ A}$ ;  $P = 11\,520 \text{ W}$

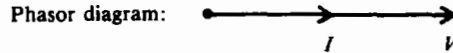11.37 An electric soldering iron draws 0.8 A from a 120-V 60-Hz power line. What is its resistance? How much power will it consume? Draw the phasor diagram. *Ans.*  $R = 150 \Omega$ ;  $P = 96 \text{ W}$



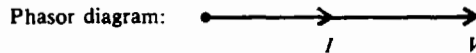11.38 Find the current and power drawn from a 110-V 60-Hz line by a tungsten lamp whose resistance is 275  $\Omega$ . Draw the phasor diagram. *Ans.*  $I = 0.4 \text{ A}$ ;  $P = 44 \text{ W}$



11.39 A circuit has a 5-M $\Omega$  resistor  $R_1$  in series with a 15-M $\Omega$  resistor  $R_2$  across a 200-V ac source. Calculate  $I$ ,  $V_1$ ,  $V_2$ ,  $P_1$ , and  $P_2$ .  
*Ans.*  $I = 10 \mu\text{A}$ ;  $V_1 = 50 \text{ V}$ ;  $V_2 = 150 \text{ V}$ ;  $P_1 = 0.5 \text{ mW}$ ;  $P_2 = 1.5 \text{ mW}$

11.40 For the ac series-parallel circuit (Fig. 11-32), find the total current, the current through each resistance, and the voltage across each resistance.  
*Ans.*  $I_T = I_1 = 24 \text{ A}$ ;  $I_2 = 12 \text{ A}$ ;  $I_3 = 12 \text{ A}$ ;  $V_1 = 96 \text{ V}$ ;  $V_2 = V_3 = 24 \text{ V}$

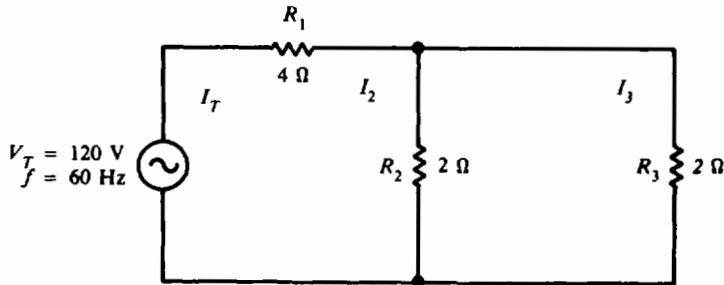


Fig. 11-32

11.41 A series-parallel ac circuit has two branches across the 60-Hz 120-V power line. One branch has a 20- $\Omega$   $R_1$  in series with a 10- $\Omega$   $R_2$ . The other branch has a 30-M $\Omega$   $R_3$  in series with a 10-M $\Omega$   $R_4$ . Calculate  $V_1$ ,  $V_2$ ,  $V_3$ , and  $V_4$ . *Ans.*  $V_1 = 80 \text{ V}$ ;  $V_2 = 40 \text{ V}$ ;  $V_3 = 90 \text{ V}$ ;  $V_4 = 30 \text{ V}$

11.42 An ac circuit has a 5-M $\Omega$  resistor  $R_1$  in parallel with a 10-M $\Omega$  resistor  $R_2$  across a 200-V source. Find  $I_1$ ,  $I_2$ ,  $V_1$ ,  $V_2$ ,  $P_1$ , and  $P_2$ .  
*Ans.*  $I_1 = 40 \mu\text{A}$ ;  $I_2 = 20 \mu\text{A}$ ;  $V_1 = V_2 = 200 \text{ V}$ ;  $P_1 = 8 \text{ mW}$ ;  $P_2 = 4 \text{ mW}$


## Inductance, Inductive Reactance, and Inductive Circuits

### INDUCTION

The ability of a conductor to induce voltage in itself when the current changes is its *self-inductance*, or simply *inductance*. The symbol for inductance is  $L$ , and its unit is the *henry* (H). One henry is the amount of inductance that permits one volt to be induced when the current changes at the rate of one ampere per second (Fig. 12-1). The formula for inductance is

$$L = \frac{v_L}{\Delta i / \Delta t} \quad (12-1)$$

where  $L$  = inductance, H  
 $v_L$  = induced voltage across the coil, V  
 $\Delta i / \Delta t$  = rate of change of current, A/s

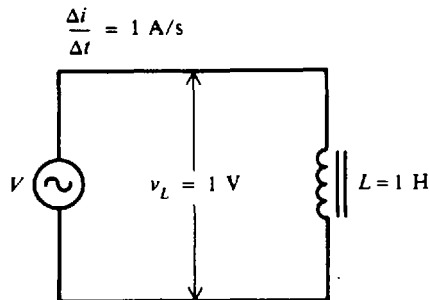

**Fig. 12-1** The inductance of a coil is 1 H when a change of 1 A/s induces 1 V across the coil

The self-induced voltage  $v_L$  from Eq. (12-1) is

$$v_L = L \frac{\Delta i}{\Delta t} \quad (12-2)$$

**Example 12.1** What is the value of inductance of a coil that induces 20 V when the current through the coil changes from 12 to 20 A in 2 s?

We are given that

$$v_L = 20 \text{ V} \quad \Delta i = 20 - 12 = 8 \text{ A} \quad \Delta t = 2 \text{ s}$$

So

$$\frac{\Delta i}{\Delta t} = \frac{8}{2} = 4 \text{ A/s}$$

$$\begin{aligned} L &= \frac{v_L}{\Delta i / \Delta t} && (12-1) \\ &= \frac{20}{4} = 5 \text{ H} && \text{Ans.} \end{aligned}$$

**Example 12.2** A coil has an inductance of  $50 \mu\text{H}$ . What voltage is induced across the coil when the rate of change of the current is  $10\,000 \text{ A/s}$ ?

$$\begin{aligned} v_L &= L \frac{\Delta i}{\Delta t} && (12-2) \\ &= (50 \times 10^{-6})(10^4) = 0.5 \text{ V} && \text{Ans.} \end{aligned}$$

When the current in a conductor or coil changes, the varying flux can cut across any other conductor or coil located nearby, thus inducing voltages in both. A varying current in  $L_1$ , therefore, induces voltage across  $L_1$  and across  $L_2$  (Fig. 12-2). When the induced voltage  $v_{L2}$  produces current in  $L_2$ , its varying magnetic field induces voltage in  $L_1$ . Hence, the two coils  $L_1$  and  $L_2$  have *mutual inductance* because current change in one coil can induce voltage in the other. The unit of mutual inductance is the henry, and the symbol is  $L_M$ . Two coils have  $L_M$  of 1 H when a current change of 1 A/s in one coil induces 1 V in the other coil.

The schematic symbol for two coils with mutual inductance is shown in Fig. 12-3.

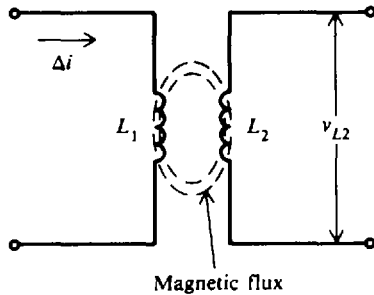


Fig. 12-2 Mutual inductance between  $L_1$  and  $L_2$

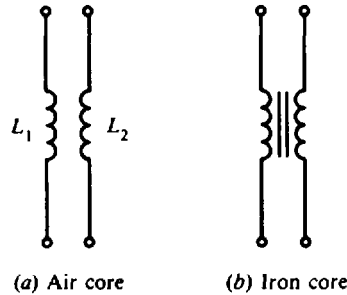


Fig. 12-3 Schematic symbols for two coils with mutual inductance

## CHARACTERISTICS OF COILS

### Physical Characteristics

A coil's inductance depends on how it is wound, the core material on which it is wound, and the number of turns of wire with which it is wound.

1. Inductance  $L$  increases as the number of turns of wire  $N$  around the core increases. Inductance increases as the square of the turns increases. For example, if the number of turns is doubled ( $2\times$ ), inductance increases  $2^2$  or  $4\times$ , assuming the area and length of the coil remain constant.
2. Inductance increases as the relative permeability  $\mu_r$  of the core material increases.
3. As the area  $A$  enclosed by each turn increases, the inductance increases. Since the area is a function of the square of the diameter of the coil, inductance increases as the square of the diameter.
4. Inductance decreases as the length of the coil increases (assuming the number of turns remains constant).

**Example 12.3** An approximate formula in SI units for the inductance of a coil where the length is at least 10 times the diameter is

$$L = \mu_r \frac{N^2 A}{l} (1.26 \times 10^{-6}), \text{ H}$$

Note that this formula follows the proportional relationships described. Find  $L$  when  $\mu_r = 200$ ,  $N = 200$  turns,  $A = 1 \times 10^{-4} \text{ m}^2$ , and  $l = 0.1 \text{ m}$ .

$$L = 200 \frac{200^2 (1 \times 10^{-4})}{0.1} (1.26 \times 10^{-6}) = 10 \times 10^{-3} \text{ H} = 10 \text{ mH} \quad \text{Ans.}$$

### Core Losses

Losses in the magnetic core are due to *eddy-current* losses and *hysteresis* losses. Eddy currents flow in a circular path within the core material itself and dissipate as heat in the core. The loss is equal to  $I^2 R$ , where  $R$  is the resistance of the path through the core. The higher the frequency of alternating current in the inductance, the higher the eddy currents and the greater the eddy-current loss.

Hysteresis losses arise from the additional power needed to reverse the magnetic field in magnetic materials with an alternating current. Hysteresis losses generally are less than eddy-current losses.

To reduce eddy-current losses while sustaining flux density, the iron core can be made of laminated sheets insulated from each other, insulated powdered-iron granules pressed into one solid, or ferrite material. Air-core coils have practically no losses from eddy currents or hysteresis.

**INDUCTIVE REACTANCE**

*Inductive reactance*  $X_L$  is the opposition to ac current due to the inductance in the circuit. The unit of inductive reactance is the ohm. The formula for inductive reactance is

$$X_L = 2\pi fL \tag{12-3}$$

Since  $2\pi = 2(3.14) = 6.28$ , Eq. (12-3) becomes

$$X_L = 6.28 fL$$

where  $X_L$  = inductive reactance,  $\Omega$   
 $f$  = frequency, Hz  
 $L$  = inductance, H

If any two quantities are known in Eq. (12-3), the third can be found.

$$L = \frac{X_L}{6.28 f} \tag{12-4}$$

$$f = \frac{X_L}{6.28 L} \tag{12-5}$$

In a circuit containing only inductance (Fig. 12-4), Ohm's law can be used to find current and voltage by substituting  $X_L$  for R.

$$I_L = \frac{V_L}{X_L} \tag{12-6}$$

$$X_L = \frac{V_L}{I_L} \tag{12-7}$$

$$V_L = I_L X_L \tag{12-8}$$

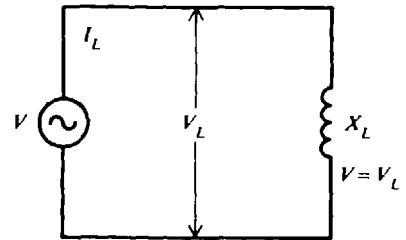


Fig. 12-4 Circuit with only  $X_L$ .

where  $I_L$  = current through the inductance, A  
 $V_L$  = voltage across the inductance, V  
 $X_L$  = inductive reactance,  $\Omega$

**Example 12.4** A resonant tank circuit consists of a 20-mH coil operating at a frequency of 950 kHz. What is the inductive reactance of the coil?

$$X_L = 6.28 fL \tag{12-3}$$

$$= 6.28(950 \times 10^3)(20 \times 10^{-3}) = 11.93 \times 10^4 = 119\,300 \Omega \quad \text{Ans.}$$

**Example 12.5** What must the inductance of a coil be in order that it have a reactance of 942  $\Omega$  at a frequency of 60 kHz?

$$L = \frac{X_L}{6.28 f} \tag{12-4}$$

$$= \frac{942}{6.28(60 \times 10^3)} = 2.5 \times 10^{-3} = 2.5 \text{ mH} \quad \text{Ans.}$$

**Example 12.6** A tuning coil in a radio transmitter has an inductance of  $300 \mu\text{H}$ . At what frequency will it have an inductive reactance of  $3768 \Omega$ ?

$$f = \frac{X_L}{6.28 L} \quad (12-5)$$

$$= \frac{3768}{6.28(300 \times 10^{-6})} = 2 \times 10^6 = 2 \text{ MHz} \quad \text{Ans.}$$

**Example 12.7** A choke coil of negligible resistance is to limit the current through it to  $50 \text{ mA}$  when  $25 \text{ V}$  is applied across it at  $400 \text{ kHz}$ . Find its inductance.

Find  $X_L$  by Ohm's law and then find  $L$ .

$$X_L = \frac{V_L}{I_L} \quad (12-7)$$

$$= \frac{25}{50 \times 10^{-3}} = 500 \Omega \quad \text{Ans.}$$

$$L = \frac{X_L}{6.28 f} \quad (12-4)$$

$$= \frac{500}{6.28(400 \times 10^3)} = 0.199 \times 10^{-3} = 0.20 \text{ mH} \quad \text{Ans.}$$

**Example 12.8** The primary coil of a power transformer has an inductance of  $30 \text{ mH}$  with negligible resistance (Fig. 12-5). Find its inductive reactance at a frequency of  $60 \text{ Hz}$  and the current it will draw from a  $120\text{-V}$  line.

Find  $X_L$  by using Eq. (12-4) and then  $I_L$  by using Ohm's law [Eq. (12-6)].

$$X_L = 6.28 fL = 6.28(60)(30 \times 10^{-3}) = 11.3 \Omega \quad \text{Ans.}$$

$$I_L = \frac{V_L}{X_L} = \frac{120}{11.3} = 10.6 \text{ A} \quad \text{Ans.}$$

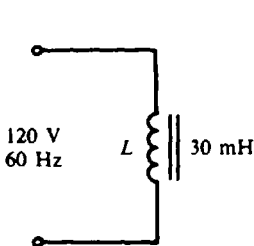


Fig. 12-5  $X_L$  circuit

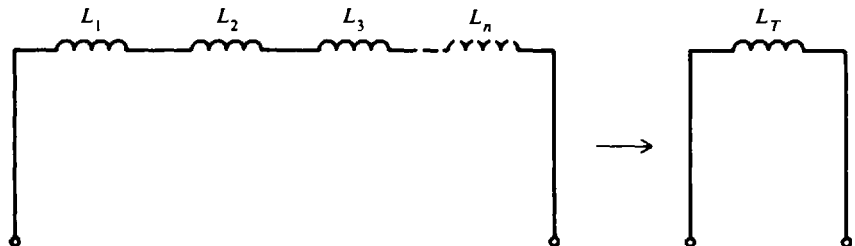


Fig. 12-6 Inductances in series without mutual coupling

## INDUCTORS IN SERIES OR PARALLEL

If inductors are spaced sufficiently far apart so that they do not interact electromagnetically with each other, their values can be combined just like resistors when connected together. If a number of inductors are connected in series (Fig. 12-6), the total inductance  $L_T$  is the sum of the individual inductances, or

Series: 
$$L_T = L_1 + L_2 + L_3 + \cdots + L_n \quad (12-9)$$

If two series-connected coils are spaced close together so that their magnetic field lines interlink, their mutual inductance will have an effect on the circuit. In that case the total inductance is

$$L_T = L_1 + L_2 \pm 2L_M \quad (12-10)$$

where  $L_M$  is the mutual inductance between the coils. The plus (+) sign in Eq. (12-10) is used if the coils are arranged in *series-aiding* form, while the minus (-) sign is used if the coils are connected in *series-opposing* form. Series aiding means that the common current produces the same direction of magnetic field for the two coils. The series-opposing connection results in opposite fields.

Three different arrangements for coils  $L_1$  and  $L_2$  are shown both pictorially and schematically in Fig. 12-7. In Fig. 12-7a, the coils are spaced too far apart to interact electromagnetically. There is no mutual inductance, so  $L_M$  is zero. The total inductance is  $L_T = L_1 + L_2$ . In Fig. 12-7b, the coils are spaced close together and have windings in the same direction, as indicated by the dots. The coils are series-aiding, so  $L_T = L_1 + L_2 + 2L_M$ . In Fig. 12-7c, the coil windings are in the opposite direction, so the coils are series-opposing, and  $L_T = L_1 + L_2 - 2L_M$ .

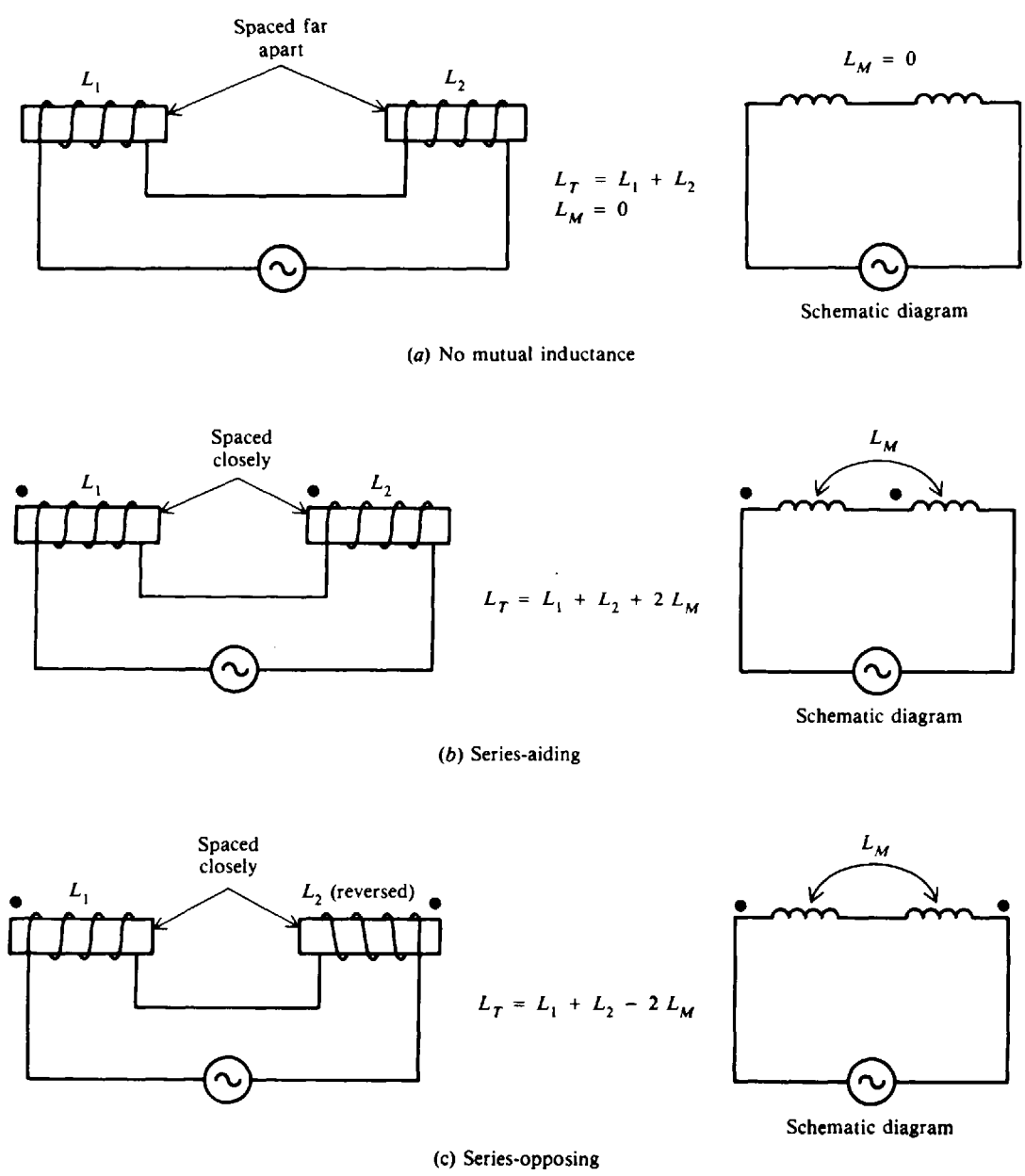


Fig. 12-7  $L_1$  and  $L_2$  in series with mutual coupling  $L_M$



The large dots above the coil (Fig. 12-7*b* and *c*) are used to indicate the polarity of the windings without having to show the actual physical construction. Coils with dots at the same end (Fig. 12-7*b*) have the same polarity or same direction of winding. When current enters the dotted ends for  $L_1$  and  $L_2$ , their fields are aiding and  $L_M$  has the same sense as  $L$ .

If inductors are spaced sufficiently far apart so that their mutual inductance is negligible ( $L_M = 0$ ), the rules for combining inductors in parallel are the same as for resistors. If a number of inductors are connected in parallel (Fig. 12-8), their total inductance  $L_T$  is

Parallel: 
$$\frac{1}{L_T} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} + \cdots + \frac{1}{L_n} \quad (12-11)$$

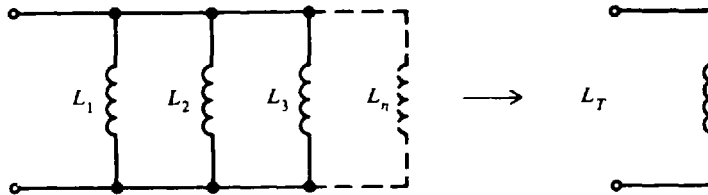


Fig. 12-8 Inductances in parallel without mutual coupling

The total inductance of two coils connected in parallel is

Parallel: 
$$L_T = \frac{L_1 L_2}{L_1 + L_2} \quad (12-12)$$

All inductances must be given in the same units. The shortcuts for calculating parallel  $R$  can be used with parallel  $L$ . For example, if two 8-mH inductors are in parallel, the total inductance is  $L_T = L/n = 8/2 = 4$  mH.

**Example 12.9** A 10- and a 12-H choke used to limit current in a circuit are connected in series. Initially they are spaced far apart. What is the total inductance?

$$\begin{aligned} L_T &= L_1 + L_2 & (12-9) \\ &= 10 + 12 = 22 \text{ H} & \text{Ans.} \end{aligned}$$

**Example 12.10** The two chokes of Example 12.9 are moved close together so that they are coupled by a mutual inductance of 7 H. What are the total inductances if (a) the coils are wound in the same direction and (b) the coils are wound in opposing directions?

(a) Series-aiding:

$$\begin{aligned} L_T &= L_1 + L_2 + 2L_M & (12-10) \\ &= 10 + 12 + 2(7) = 22 + 14 = 36 \text{ H} & \text{Ans.} \end{aligned}$$

(b) Series-opposing:

$$\begin{aligned} L_T &= L_1 + L_2 - 2L_M & (12-10) \\ &= 10 + 12 - 2(7) = 22 - 14 = 8 \text{ H} & \text{Ans.} \end{aligned}$$

**Example 12.11** What is the total inductance of two parallel inductors with values of 8 and 12 H?

$$\begin{aligned} L_T &= \frac{L_1 L_2}{L_1 + L_2} & (12-12) \\ &= \frac{8(12)}{8 + 12} = \frac{96}{20} = 4.8 \text{ H} & \text{Ans.} \end{aligned}$$

**Example 12.12** A 6-H inductor and a 22-H inductor are connected in series and plugged into a 120-V ac 60-Hz outlet. Assume that their resistance is negligible and that they have no mutual inductance. What is their inductive reactance and what current will they draw?

$$L_T = L_1 + L_2 = 6 + 22 = 28 \text{ H}$$

$$X_L = 6.28 fL_T \tag{12-3}$$

$$= 6.28(60)(28) = 10\,550 \ \Omega \quad \text{Ans.}$$

$$I_L = \frac{V}{X_L} = \frac{120}{10\,550} = 0.0114 \text{ A} \quad \text{or} \quad 11.4 \text{ mA} \quad \text{Ans.} \tag{12-6}$$

**INDUCTIVE CIRCUITS**

**Inductance Only**

If an ac voltage  $v$  is applied across a circuit having *only* inductance (Fig. 12-9a), the resulting ac current through the inductance,  $i_L$ , will lag the voltage across the inductance,  $v_L$ , by  $90^\circ$  (Fig. 12-9b and c). Voltages  $v$  and  $v_L$  are the same because the total applied voltage is dropped only across the inductance. Both  $i_L$  and  $v_L$  are sine waves with the same frequency. Lowercase letters such as  $i$  and  $v$  indicate instantaneous values; capital letters such as  $I$  and  $V$  show dc or ac rms values.

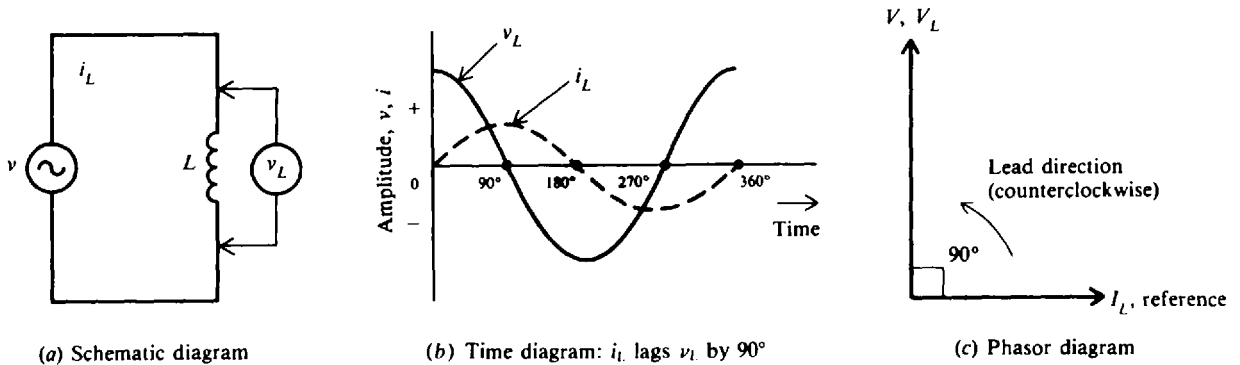


Fig. 12-9 Circuit with  $L$  only

**RL in Series**

When a coil has series resistance (Fig. 12-10a), the rms current  $I$  is limited by both  $X_L$  and  $R$ .  $I$  is the same in  $X_L$  and  $R$  since they are in series. The voltage drop across  $R$  is  $V_R = IR$ , and the voltage drop across  $X_L$  is  $V_L = IX_L$ . The current  $I$  through  $X_L$  must lag  $V_L$  by  $90^\circ$  because this is the phase angle between current through an inductance and its self-induced voltage (Fig. 12-10b). The current  $I$  through  $R$  and its  $IR$  voltage drop are in phase so the phase angle is  $0^\circ$  (Fig. 12-10b).

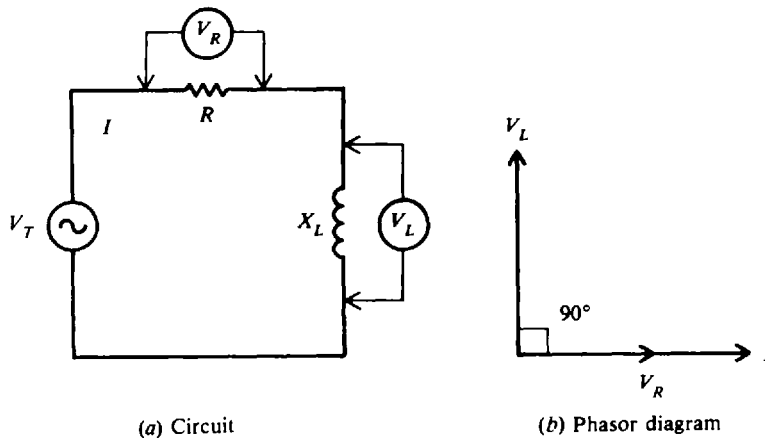


Fig. 12-10  $R$  and  $X_L$  in series

To combine two waveforms out of phase, we add their equivalent phasors. The method is to add the tail of one phasor to the arrowhead of the other, using the angle to show their relative phase. The sum of the phasors is a resultant phasor from the start of one phasor to the end of the other phasor. Since the  $V_R$  and  $V_L$  phasors form a right angle, the resultant phasor is the hypotenuse of a right triangle (Fig. 12-11). From the geometry of a right triangle, the pythagorean theorem states that the hypotenuse is equal to the square root of the sum of the squares of the sides. Therefore, the resultant is

$$V_T = \sqrt{V_R^2 + V_L^2} \quad (12-13)$$

where the total voltage  $V_T$  is the phasor sum of the two voltages  $V_R$  and  $V_L$  that are  $90^\circ$  out of phase. All the voltages must be in the same units—rms values, peak values, or instantaneous values. For example, when  $V_T$  is an rms value,  $V_R$  and  $V_L$  also are rms values. Most of the ac calculations will be made in rms units.

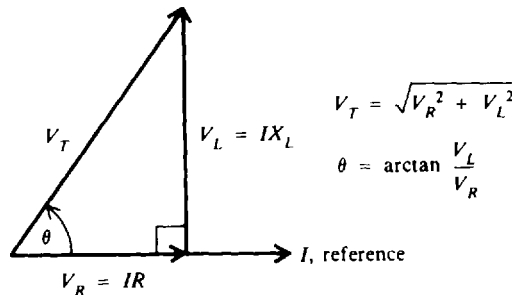


Fig. 12-11 Phasor-voltage triangle

The phase angle  $\theta$  between  $V_T$  and  $V_R$  (Fig. 12-11) is

$$\begin{aligned} \tan \theta &= \frac{V_L}{V_R} \\ \theta &= \arctan \frac{V_L}{V_R} \end{aligned} \quad (12-14)$$

Since  $V_R$  is in phase with  $I$ ,  $\theta$  is also the phase angle between  $V_T$  and  $I$  where  $I$  lags  $V_T$ .

**Example 12.13** A  $RL$  series ac circuit has a current of 1 A peak with  $R = 50 \Omega$  and  $X_L = 50 \Omega$  (Fig. 12-12a). Calculate  $V_R$ ,  $V_L$ ,  $V_T$ , and  $\theta$ . Draw the phasor diagram of  $V_T$  and  $I$ . Draw also the time diagram of  $i$ ,  $v_R$ ,  $v_L$ , and  $v_T$ .


$$V_R = IR = 1(50) = 50 \text{ V peak} \quad \text{Ans.}$$

$$V_L = IX_L = 1(50) = 50 \text{ V peak} \quad \text{Ans.}$$


$$\begin{aligned} \text{Then (see Fig. 12-12b)} \quad V_T &= \sqrt{V_R^2 + V_L^2} \\ &= \sqrt{50^2 + 50^2} = \sqrt{2500 + 2500} = \sqrt{5000} = 70.7 \text{ V peak} \end{aligned} \quad (12-13) \quad \text{Ans.}$$

$$\theta = \arctan \frac{V_L}{V_R} = \arctan \frac{50}{50} = \arctan 1 = 45^\circ \quad \text{Ans.}$$

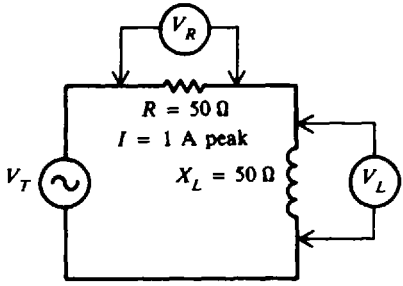
In a series circuit, since  $I$  is the same in  $R$  and  $X_L$ , it is convenient to show  $I$  as the reference phasor at  $0^\circ$ . The phasor diagram is shown as Fig. 12-12c and the time diagram as Fig. 12-12d.




(a) *RL* series circuit

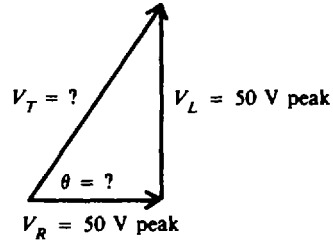

(b)

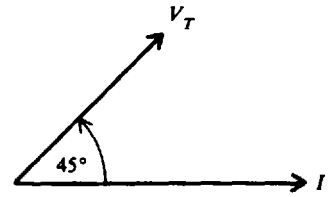

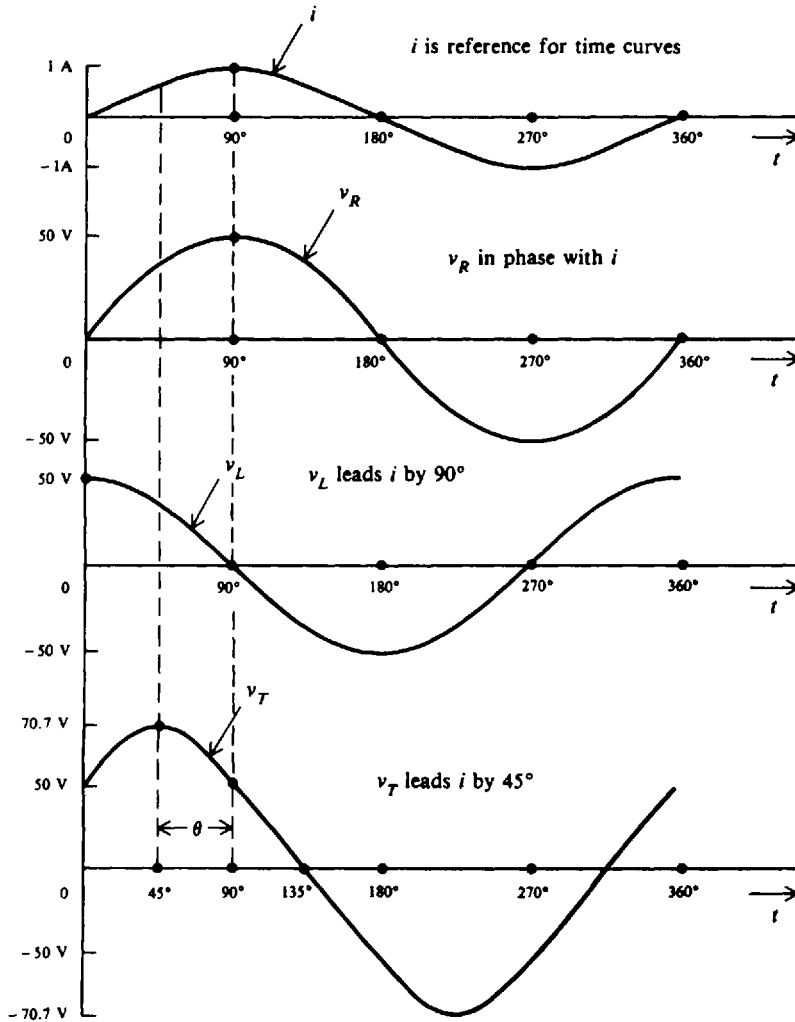(c) Phasor diagram ( $I$  lags  $V_T$  by  $45^\circ$ )



(d) Time diagram


Fig. 12-12

**Impedance in Series RL**

The resultant of the phasor addition of  $R$  and  $X_L$  is called *impedance*. The symbol for impedance is  $Z$ . Impedance is the total opposition to the flow of current, expressed in ohms. The impedance triangle (Fig. 12-13) corresponds to the voltage triangle (Fig. 12-11), but the common factor  $I$  cancels. The equations for impedance and phase angle are derived as follows:


$$\begin{aligned}
 V_T^2 &= V_R^2 + V_L^2 \\
 (IZ)^2 &= (IR)^2 + (IX_L)^2 \\
 Z^2 &= R^2 + X_L^2 \\
 Z &= \sqrt{R^2 + X_L^2}
 \end{aligned}
 \tag{12-15}$$

$$\begin{aligned}
 \tan \theta &= \frac{X_L}{R} \\
 \theta &= \arctan \frac{X_L}{R}
 \end{aligned}
 \tag{12-16}$$

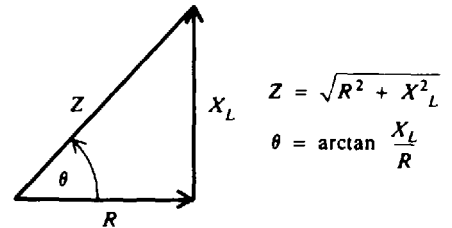

**Fig. 12-13** Phasor addition of  $R$  and  $X_L$  to find  $Z$

**Example 12.14** If a  $50\text{-}\Omega$   $R$  and a  $70\text{-}\Omega$   $X_L$  are in series with  $120\text{ V}$  applied (Fig. 12-14a), find the following:  $Z$ ,  $\theta$ ,  $I$ ,  $V_R$ , and  $V_L$ . What is the phase angle of  $V_L$ ,  $V_R$ , and  $V_T$  with respect to  $I$ ? Prove that the sum of the series voltage drops equals the applied voltage  $V_T$ .

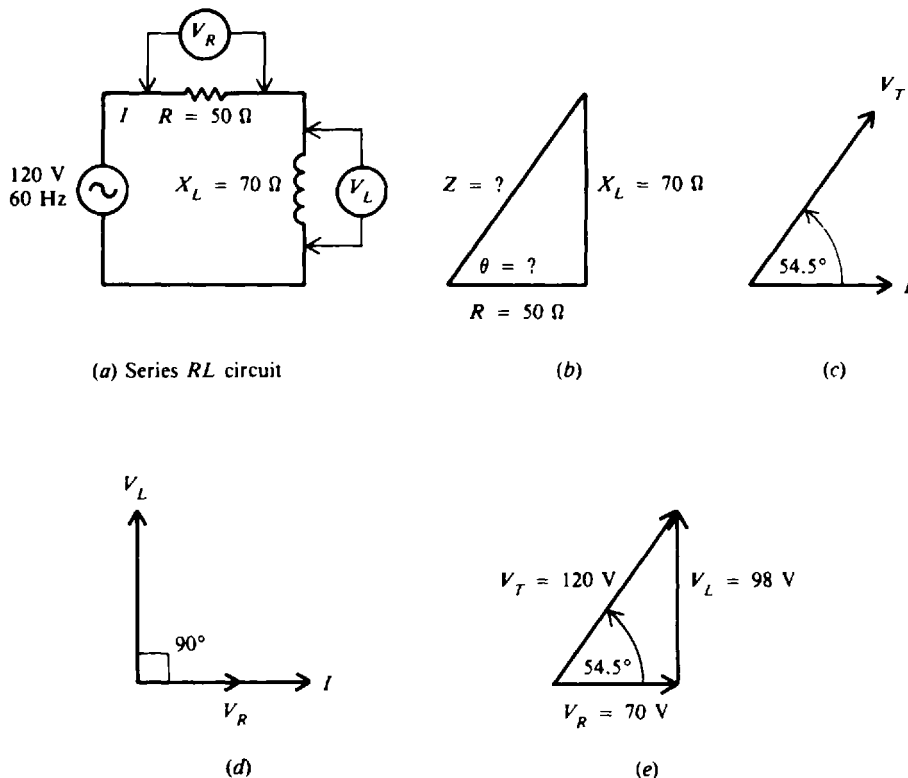

**Fig. 12-14**

**Step 1.** Find  $Z$  and  $\theta$  (see Fig. 12-14b).

$$\begin{aligned}
 Z &= \sqrt{R^2 + X_L^2} \\
 &= \sqrt{50^2 + 70^2} = \sqrt{2500 + 4900} = \sqrt{7400} = 86 \Omega
 \end{aligned}
 \tag{12-15}$$

*Ans.*

$$\begin{aligned} \theta &= \arctan \frac{X_L}{R} && (12-16) \\ &= \arctan \frac{70}{50} = \arctan 1.40 = 54.5^\circ && \text{Ans.} \end{aligned}$$

$V_T$  leads  $I$  by  $54.5^\circ$  (see Fig. 12-14c).

**Step 2.** Find  $I$ ,  $V_R$ ,  $V_L$ .

$$I = \frac{V_T}{Z} = \frac{120}{86} = 1.40 \text{ A} \quad \text{Ans.}$$

$$V_R = IR = 1.40(50) = 70.0 \text{ V} \quad \text{Ans.}$$

$$V_L = IX_L = 1.40(70) = 98.0 \text{ V} \quad \text{Ans.}$$

$I$  and  $V_R$  are in phase.  $V_L$  leads  $I$  by  $90^\circ$  (see Fig. 12-14d).

**Step 3.** Show that  $V_T$  is the phasor sum of  $V_R$  and  $V_L$  (see Fig. 12-14e).

$$\begin{aligned} V_T &= \sqrt{V_R^2 + V_L^2} && (12-13) \\ &= \sqrt{(70.0)^2 + (98.0)^2} = \sqrt{14\,504} \approx 120 \text{ V} && \text{Ans.} \end{aligned}$$

(The answer is not exactly 120 V because of rounding off  $I$ .) Therefore, the sum of the voltage drops equals the applied voltage.


**RL in Parallel**

For parallel circuits with  $R$  and  $X_L$  (Fig. 12-15a), the same applied voltage  $V_T$  is across  $R$  and  $X_L$  since both are in parallel with  $V_T$ . There is no phase difference between these voltages. Therefore,  $V_T$  will be used as the reference phasor. The resistive branch current  $I_R = V_T/R$  is in phase with  $V_T$ . The inductive branch current  $I_L = V_T/X_L$  lags  $V_T$  by  $90^\circ$  (Fig. 12-15b) because the current in an inductance lags the voltage across it by  $90^\circ$ . The phasor sum of  $I_R$  and  $I_L$  equals the total line current  $I_T$  (Fig. 12-15c), or


$$I_T = \sqrt{I_R^2 + I_L^2} \quad (12-17)$$

$$\tan \theta = -\frac{I_L}{I_R}$$

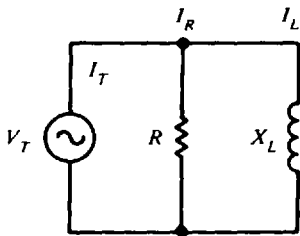
$$\theta = \arctan \left( -\frac{I_L}{I_R} \right) \quad (12-18)$$



(a) Circuit

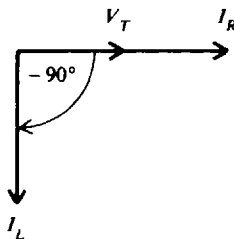

(b) Phasor diagram

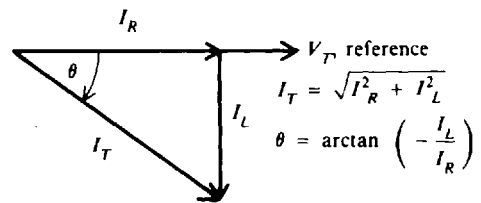

(c) Current-phasor triangle

**Fig. 12-15**  $R$  and  $X_L$  in parallel

**Example 12.15** A  $RL$  parallel ac circuit has 100-V peak applied across  $R = 20 \Omega$  and  $X_L = 20 \Omega$  (Fig. 12-16a). Find  $I_R$ ,  $I_L$ ,  $I_T$ , and  $\theta$ . (See Fig. 12-16b.) Draw the phasor and time diagrams of  $v_T$ ,  $i_R$ ,  $i_L$ , and  $i_T$ .

$$I_R = \frac{V_T}{R} = \frac{100}{20} = 5 \text{ A peak} \quad \text{Ans.}$$



$$I_L = \frac{V_T}{X_L} = \frac{100}{20} = 5 \text{ A peak} \quad \text{Ans.}$$

$$\begin{aligned} I_T &= \sqrt{I_R^2 + I_L^2} && (12-17) \\ &= \sqrt{5^2 + 5^2} = \sqrt{50} = 7.07 \text{ A peak} && \text{Ans.} \end{aligned}$$

$$\theta = \arctan \left( -\frac{I_L}{I_R} \right) \tag{12-18}$$

$$= \arctan \left( -\frac{5}{5} \right) = \arctan (-1) = -45^\circ \quad \text{Ans.}$$

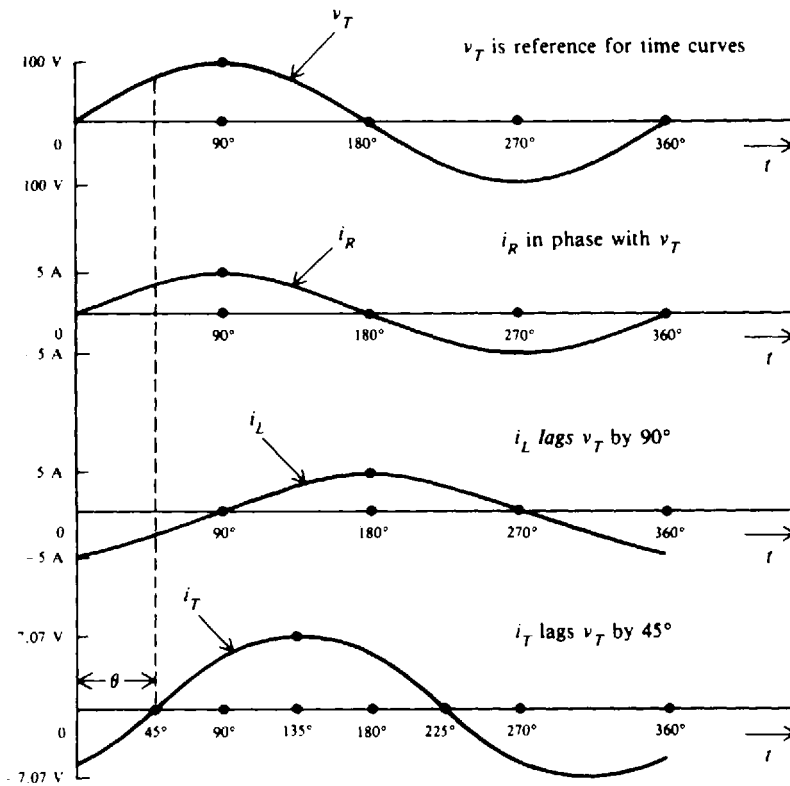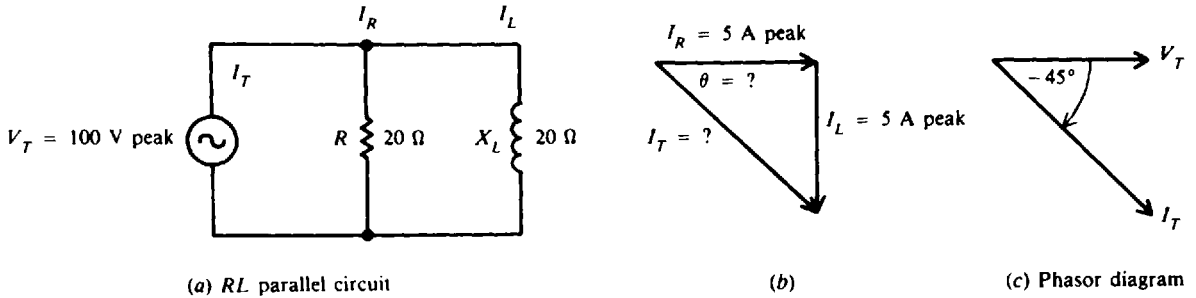Since  $V_T$  is the same throughout the parallel circuit,  $V_T$  is shown as the reference phasor at  $0^\circ$ .  $I_T$  lags  $V_T$  by  $45^\circ$ . (See Fig. 12-16c.) For the time diagram, see Fig. 12-16d.



(d) Time diagram

Fig. 12-16

**Impedance in Parallel *RL***

For the general case of calculating the total impedance  $Z_T$  of  $R$  and  $X_L$  in parallel, assume any number for the applied voltage  $V_T$  because in the calculation of  $Z_T$  in terms of the branch currents the value of  $V_T$  cancels. A convenient value to assume for  $V_T$  is the value of either  $R$  or  $X_L$ , whichever is the higher number. This is only one method among others for calculating  $Z_T$ .

**Example 12.16** What is the impedance  $Z_T$  of a 200- $\Omega$   $R$  in parallel with a 400- $\Omega$   $X_L$ ? Assume 400 V for the applied voltage  $V_T$ .

$$I_R = \frac{V_T}{R} = \frac{400}{200} = 2 \text{ A}$$

$$I_L = \frac{V_T}{X_L} = \frac{400}{400} = 1 \text{ A}$$

$$I_T = \sqrt{I_R^2 + I_L^2} = \sqrt{4 + 1} = \sqrt{5} = 2.24 \text{ A}$$

$$Z_T = \frac{V_T}{I_T} = \frac{400}{2.24} = 178.6 \Omega \quad \text{Ans.}$$

The combined impedance of a 200- $\Omega$   $R$  in parallel with a 400- $\Omega$   $X_L$  is equal to 178.6  $\Omega$  regardless of the value of the applied voltage. The combined impedance must be less than the lowest number of ohms in the parallel branches. The total impedance of a parallel  $RL$  circuit does not equal that of a series  $RL$  circuit; that is  $Z_T \neq \sqrt{R^2 + X_L^2}$ , because the resistance and inductive reactance combine to present a different load condition to the voltage source.

**Q OF A COIL**


The quality or merit  $Q$  of a coil is indicated by the equation

$$Q = \frac{X_L}{R_i} = \frac{6.28 fL}{R_i} \tag{12-19}$$


where  $R_i$  is the internal resistance of the coil equal to the resistance of the wire in the coil (Fig. 12-17).  $Q$  is a numerical value without any units since the ohms cancel in the ratio of reactance to resistance. If the  $Q$  of a coil is 200, it means that the  $X_L$  of the coil is 200 times more than its  $R_i$ .

The  $Q$  of a coil may range in value from less than 10 for a low- $Q$  coil up to 1000 for a very high  $Q$  coil. Radio frequency (RF) coils have a  $Q$  of about 30 to 300.

As an example, a coil with an  $X_L$  of 300  $\Omega$  and a  $R_i$  of 3  $\Omega$  has a  $Q$  of  $300/3 = 100$ .

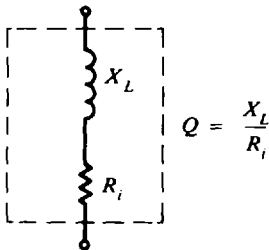

**Fig. 12-17** Schematic diagram of  $Q$  of a coil.  $X_L$  and  $R_i$  are distributed uniformly over the length of the coil

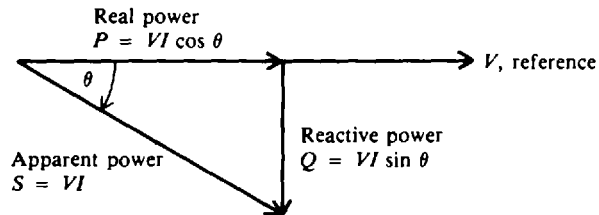

**Fig. 12-18** Power triangle for  $RL$  circuit

**POWER IN RL CIRCUITS**

In an ac circuit with inductive reactance, the line current  $I$  lags the applied voltage  $V$ . The real power  $P$  is equal to the voltage multiplied by only that portion of the line current which is in phase with the voltage. Therefore,

$$\text{Real power } P = V(I \cos \theta) = VI \cos \theta \tag{12-20}$$

where  $\theta$  is the phase angle between  $V$  and  $I$ , and  $\cos \theta$  is the power factor (PF) of the circuit. Also,

$$\text{Real power } P = I^2R \tag{12-21}$$

where  $R$  is the total resistive component of the circuit.

Reactive power  $Q$  in voltamperes reactive (VAR), is expressed as follows:

$$\text{Reactive power } Q = VI \sin \theta \tag{12-22}$$



Apparent power  $S$  is the product of  $V \times I$ . The unit is voltamperes (VA). In formula form,

$$\text{Apparent power } S = VI \quad (12-23)$$

In all the power formulas, the  $V$  and  $I$  are in rms values. The relationships of real, reactive, and apparent power can be illustrated by the phasor diagram of power (Fig. 12-18).

**Example 12.17** The ac circuit (Fig. 12-19a) has 2 A through a 173- $\Omega$   $R$  in series with an  $X_L$  of 100  $\Omega$ . Find the power factor, the applied voltage  $V$ , real power  $P$ , reactive power  $Q$ , and apparent power  $S$ .

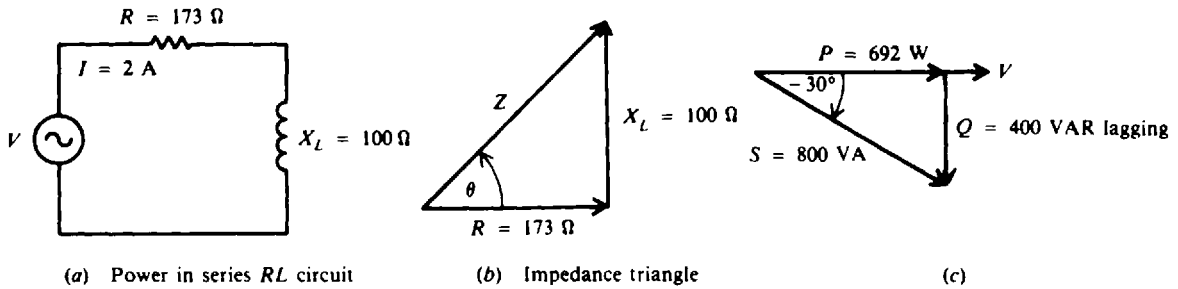


Fig. 12-19

**Step 1.** Find the phase angle  $\theta$ ,  $\cos \theta$ , and impedance  $Z$  by the impedance triangle (Fig. 12-19b).

$$\theta = \arctan \frac{X_L}{R} = \arctan \frac{100}{173} = \arctan 0.578 = 30^\circ \quad \text{Ans.}$$

$$\text{PF} = \cos \theta = \cos 30^\circ = 0.866 \quad \text{Ans.}$$

$$Z = \frac{R}{\cos \theta} = \frac{173}{\cos 30^\circ} = 200 \Omega \quad \text{Ans.}$$

An alternative method to find  $Z$  is by using  $Z = \sqrt{R^2 + X_L^2}$ .

**Step 2.** Find  $V$ .

$$V = IZ = 2(200) = 400 \text{ V} \quad \text{Ans.}$$

**Step 3.** Find  $P$ .

$$P = I^2 R \quad (12-21)$$

$$= 2^2(173) = 692 \text{ W} \quad \text{Ans.}$$

or

$$P = VI \cos \theta \quad (12-20)$$

$$= 400(2)(\cos 30^\circ) = 692 \text{ W}$$

In both  $P$  calculations, the real power is the same because this is the amount of power supplied by the voltage source and dissipated in the resistance. The inductive reactance merely transforms power back to the circuit. Either formula for  $P$  can be used, depending on which is more convenient.

**Step 4.** Find  $Q$  and  $S$ .

$$Q = VI \sin \theta \quad (12-22)$$

$$= 400(2)(\sin 30^\circ) = 400 \text{ VAR lagging} \quad \text{Ans.}$$

In an inductive circuit, reactive power is lagging because  $I$  lags  $V$ .

$$S = VI \quad (12-23)$$

$$= 400(2) = 800 \text{ VA} \quad \text{Ans.}$$

See Fig. 12-19c.

Summary Table for Series and Parallel RL Circuits

$X_L$ and $R$ in Series	$X_L$ and $R$ in Parallel
$I$ the same in $X_L$ and $R$	$V_T$ the same across $X_L$ and $R$
$V_T = \sqrt{V_R^2 + V_L^2}$	$I_T = \sqrt{I_R^2 + I_L^2}$
$Z = \sqrt{R^2 + X_L^2} = \frac{V_T}{I}$	$Z_T = \frac{V_T}{I_T}$
$V_R$ lags $V_L$ by $90^\circ$	$I_L$ lags $I_R$ by $90^\circ$
$\theta = \arctan \frac{X_L}{R}$	$\theta = \arctan \left( -\frac{I_L}{I_R} \right)$

### Solved Problems

- 12.1 A steady current of 20 mA is passed through a coil with an inductance of 100 mH. What is the voltage induced by the coil?

If the circuit is dc, the rate of change of current  $\Delta i/\Delta t = 0$ . So

$$v_L = L \frac{\Delta i}{\Delta t} \tag{12-2}$$

$$= L(0) = 0 \text{ V} \quad \text{Ans.}$$

A voltage can be induced only when a coil is carrying a *changing* current.

- 12.2 Current through a coil increases to 20 A in 1/1000 s. If its inductance is 100  $\mu$ H, what is the induced voltage at that instant?

$$v_L = L \frac{\Delta i}{\Delta t} \tag{12-2}$$

$$= (100 \times 10^{-6}) \left( \frac{20}{1/1000} \right) = (10^{-4})(2 \times 10^4) = 2 \text{ V} \quad \text{Ans.}$$

- 12.3 A 120-Hz 20-mA ac current is present in a 10-H inductor. What is the reactance of the inductor and the voltage drop across the inductor?

$$X_L = 6.28 fL \tag{12-3}$$

$$= 6.28(120)(10) = 7536 \Omega \quad \text{Ans.}$$

$$V_L = I_L X_L$$

$$= (20 \times 10^{-3})(7536) = 150.7 \text{ V} \quad \text{Ans.}$$

- 12.4 In Prob. 12.3, what are the maximum and average values of the voltage developed across the inductor?

In a reactive ac circuit the same relations exist for the various values of voltage such as rms, peak, average, and instantaneous. The rms value is implied when no statement is made otherwise.

$$V_M = 1.414 V$$

$$V_{L,M} = 1.414 V_L = 1.414(150.7) = 213.1 \text{ V} \quad \text{Ans.}$$

$$V_{av} = 0.91 V$$

$$V_{L,av} = 0.91 V_L = 0.91(150.7) = 137.1 \text{ V} \quad \text{Ans.}$$

12.5 A 255- $\mu$ H choke coil of negligible resistance is to limit the current through it to 25 mA when 40 V are impressed across it. What is the frequency of the current?

$$X_L = \frac{V_L}{I_L} \tag{12-7}$$

$$= \frac{40}{25 \times 10^{-3}} = 1600 \Omega$$

$$f = \frac{X_L}{6.28 L} \tag{12-5}$$

$$= \frac{1600}{6.28(255 \times 10^{-6})} = 10^6 = 1 \text{ MHz or } 1000 \text{ kHz} \quad \text{Ans.}$$

12.6 A simple high-pass filter (Fig. 12-20) is one in which high-frequency waves pass through the capacitor  $C$  to the output and low-frequency waves pass through the inductor  $L$ . What is the reactance of the 15-mH coil to (a) a 2000-Hz (low-frequency) current and (b) a 400-kHz (high-frequency) current?

(a)  $X_L = 6.28 fL$  (12-3)  
 $= 6.28(2 \times 10^3)(15 \times 10^{-3}) = 188.4 \Omega$  Ans.

(b)  $X_L = 6.28(400 \times 10^3)(15 \times 10^{-3}) = 37\,680 \Omega$  Ans.

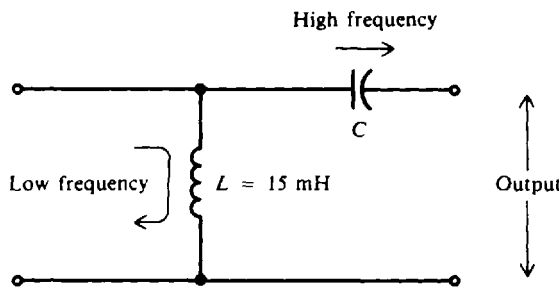


Fig. 12-20

12.7 What is the total inductance of the circuit shown in Fig. 12-21a?

Step 1. Reduce the parallel inductors to their equivalents.

$$L_4 = \frac{L_2 L_3}{L_2 + L_3} = \frac{3(6)}{3 + 6} = \frac{18}{9} = 2 \text{ mH}$$

See Fig. 12-21b.

Step 2. Add the series inductors.

$$L_T = L_1 + L_4 = 10 + 2 = 12 \text{ mH} \quad \text{Ans.}$$

See Fig. 12-21c.

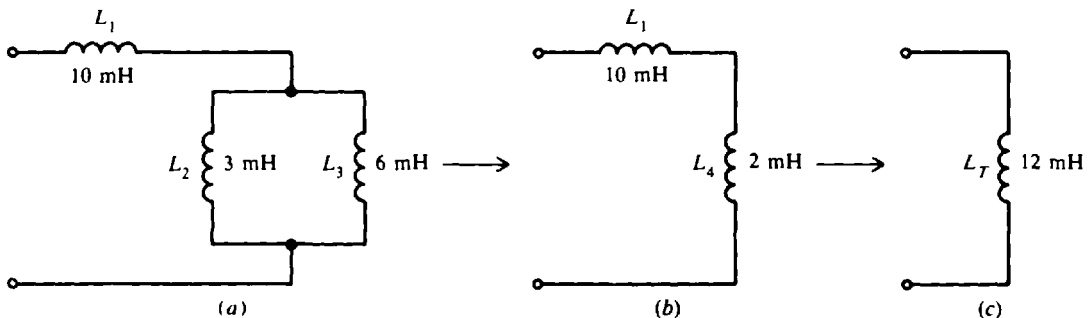


Fig. 12-21

- 12.8 If a frequency of 2 MHz is applied to the circuit of Fig. 12-21, what is the reactance of the circuit?

$$X_L = 6.28fL_T = 6.28(2 \times 10^6)(12 \times 10^{-3}) = 150.72 \times 10^3 = 150\,720 \, \Omega \quad \text{Ans.}$$

- 12.9 With two coils  $L_1$  and  $L_2$  as wound (Fig. 12-22), find the total inductance.

Since the windings are wound in the same direction relative to the dots,  $L_1$  and  $L_2$  are series-aiding. Then, using Eq. (12-10),

$$L_T = L_1 + L_2 + 2L_M = 9 + 13 + 6 = 28 \, \text{H} \quad \text{Ans.}$$

- 12.10 The windings of  $L_2$  (Fig. 12-22) are now wound in reverse (Fig. 12-23). What is the total inductance now?

Because the windings are wound in opposite directions relative to the dots,  $L_1$  and  $L_2$  are series-opposing. Then

$$L_T = L_1 + L_2 - 2L_M = 9 + 13 - 6 = 16 \, \text{H} \quad \text{Ans.}$$

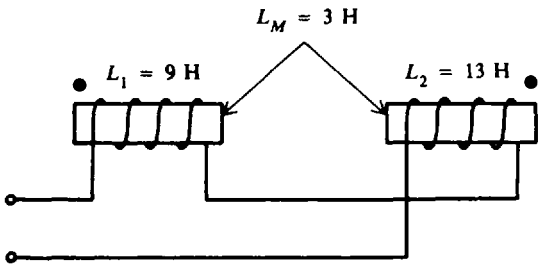


Fig. 12-22

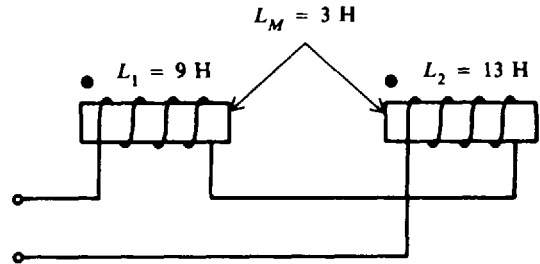


Fig. 12-23

- 12.11 A 20-H coil is connected across a 110-V 60-Hz power line. If the coil has zero resistance, find the current and power drawn. Draw the phasor diagram.

$$X_L = 6.28fL \tag{12-3}$$

$$= 6.28(60)(20) = 7536 \, \Omega$$


$$I_L = \frac{V_L}{X_L} \tag{12-6}$$

$$= \frac{110}{7536} = 14.6 \, \text{mA} \quad \text{Ans.}$$

$$P = VI \cos \theta \tag{12-20}$$

$$= 110(14.6 \times 10^{-3})(\cos 90^\circ) = 110(14.6 \times 10^{-3})(0) = 0 \, \text{W} \quad \text{Ans.}$$

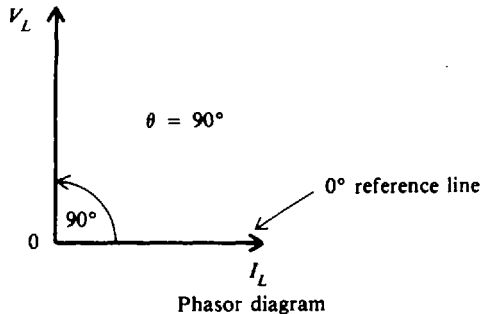In a purely reactive circuit ( $R = 0$ ), real power is zero because no energy is dissipated. Also  $P = I^2R = I^2(0) = 0$ . In the phasor diagram,  $I_L$  lags  $V_L$  by  $90^\circ$ .



**12.12** A tuning coil has an inductance of  $39.8 \mu\text{H}$  and an internal resistance of  $20 \Omega$ . Find its impedance to a frequency of  $100 \text{ kHz}$  and the current through the coil if the voltage drop is  $80 \text{ V}$  across the entire coil. Also find the resistive drop and the inductive drop of the coil, and draw the phasor diagram.

A coil with  $R_i$  and  $X_L$  is treated as a series  $RL$  circuit.

**Step 1.** Find  $X_L$  and then  $Z$ ,  $\theta$ .

$$\begin{aligned} X_L &= 6.28 fL \\ &= 6.28(10^5)(39.8 \times 10^{-6}) = 25 \Omega \end{aligned} \quad (12-3)$$

$$\begin{aligned} Z &= \sqrt{R_i^2 + X_L^2} \\ &= \sqrt{20^2 + 25^2} = 32 \Omega \quad \text{Ans.} \end{aligned} \quad (12-15)$$

$$\begin{aligned} \theta &= \arctan \frac{X_L}{R_i} \\ &= \arctan \frac{25}{20} = \arctan 1.25 = 51.3^\circ \end{aligned} \quad (12-16)$$

**Step 2.** Find  $I$ .

$$I = \frac{V}{Z} = \frac{80}{32} = 2.5 \text{ A} \quad \text{Ans.}$$

**Step 3.** Find  $V_R$ ,  $V_L$ , and check  $\theta$ .


$$V_R = IR_i = 2.5(20) = 50 \text{ V} \quad \text{Ans.}$$

$$V_L = IX_L = 2.5(25) = 62.5 \text{ V} \quad \text{Ans.}$$

$$\begin{aligned} \text{Also} \quad \theta &= \arctan \frac{V_L}{V_R} \\ &= \arctan \frac{62.5}{50} = 1.25 = 51.3^\circ \quad \text{Check} \end{aligned} \quad (12-14)$$

**Step 4.** Draw phasor diagram.

Ans.

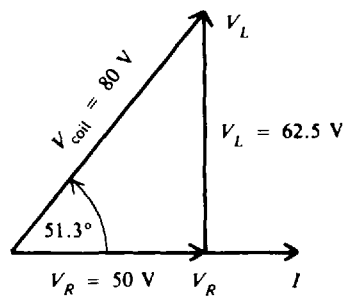

Phasor diagram

**12.13** A choke is an inductance coil with a very low resistance. The ac voltage drop across  $R$  is therefore very low. That is, practically all the ac voltage drop is across  $L$ . For this to occur,  $X_L$  is taken as 10 or more times the series  $R$ . Find the minimum inductance required for a choke with a resistance of  $100 \Omega$  when the frequency of the circuit is (a)  $5 \text{ kHz}$ , (b)  $5 \text{ MHz}$ , and (c)  $50 \text{ MHz}$ . If the applied voltage  $V_T$  is  $200 \text{ V}$ , (d) what is the voltage across the choke and the resistance?

$$X_L = 10R = 10(100) = 1000 \Omega$$

$$(a) \quad L = \frac{X_L}{6.28f} \tag{12-5}$$

$$= \frac{1000}{6.28(5 \times 10^3)} = 32 \text{ mH} \quad \text{Ans.}$$

$$(b) \quad L = \frac{1000}{6.28(5 \times 10^6)} = 32 \mu\text{H} \quad \text{Ans.}$$

$$(c) \quad L = \frac{1000}{6.28(5 \times 10^7)} = 3.2 \mu\text{H} \quad \text{Ans.}$$

$$(d) \quad Z = \sqrt{R^2 + X_L^2} \tag{12-15}$$

$$= \sqrt{100^2 + 1000^2} = 1005 \Omega$$

$$I = \frac{V_T}{Z} = \frac{200}{1005} = 0.199 \text{ A}$$

$$V_R = IR = 0.199(100) = 19.9 \text{ V} \quad \text{Ans.}$$

$$V_L = IX_L = 0.199(1000) = 199 \text{ V} \quad \text{Ans.}$$

Note that  $V_L$  is practically all the applied voltage and  $V_R$  is small by comparison.

**12.14** The purpose of a high-pass filter circuit (Fig. 12-24) is to permit high frequencies to pass on to the load but to prevent the passing of low frequencies. Find the branch currents, the total current, and the percentage of the total current passing through the resistor for (a) a 1.5-kHz (low) audio-frequency signal and (b) a 1-MHz (high) radio-frequency signal.

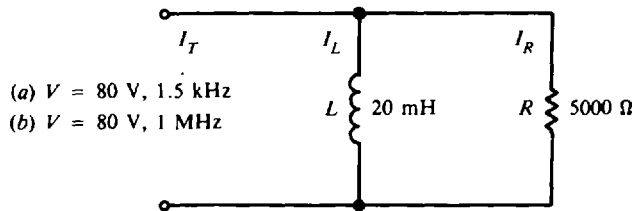


Fig. 12-24

(a) **Step 1.** Find  $X_L$  at  $f = 1.5 \text{ kHz}$ .

$$X_L = 6.28fL = 6.28(1.5 \times 10^3)(20 \times 10^{-3}) = 188.4 \Omega$$

**Step 2.** Find branch currents  $I_L$  and  $I_R$ .

$$I_L = \frac{V}{X_L} = \frac{80}{188.4} = 0.425 \text{ A} \quad \text{Ans.}$$

$$I_R = \frac{V}{R} = \frac{80}{5000} = 0.016 \text{ A} \quad \text{Ans.}$$

**Step 3.** Find total current  $I_T$ .

$$I_T = \sqrt{I_R^2 + I_L^2} \tag{12-17}$$

$$= \sqrt{(0.016)^2 + (0.425)^2} = \sqrt{0.1809} = 0.425 \text{ A} \quad \text{Ans.}$$

Since  $X_L \ll R$ , the current is mostly inductive.

**Step 4.** Find  $I_R$  as a percentage of  $I_T$ .

$$\frac{I_R}{I_T} \times 100 = \frac{0.016}{0.425} 100 = 0.038(100) = 3.8\% \quad \text{Ans.}$$

Therefore, only 3.8 percent of the 1.5-kHz audio signal passes through the resistor.

(b) **Step 1.** Find  $X_L$  now at  $f = 1$  MHz.

$$X_L = 6.28fL = 6.28(1 \times 10^6)(20 \times 10^{-3}) = 125.6 \text{ k}\Omega$$

**Step 2.** Find  $I_L$  and  $I_R$ .

$$I_L = \frac{V}{X_L} = \frac{80}{125.6 \times 10^3} = 0.637 \text{ mA} \quad \text{Ans.}$$

$$I_R = 16 \text{ mA} \quad \text{Ans.}$$

$I_R$  remains the same as in part (a).

**Step 3.** Find  $I_T$ .

$$I_T = \sqrt{I_R^2 + I_L^2} = \sqrt{16^2 + (0.637)^2} = \sqrt{256.41} = 16.01 \text{ mA} \quad \text{Ans.}$$

Since  $R \ll X_L$ , the current is mostly resistive.

**Step 4.** Find  $I_R$  as a percentage of  $I_T$ .

$$\frac{I_R}{I_T} \times 100 = \frac{16}{16.01} 100 = 0.999(100) = 99.9\% \quad \text{Ans.}$$

Thus, theoretically 100 percent of the 1-MHz radio signal passes through the resistor.

It is clear that the circuit is an excellent high-pass filter by passing almost 100 percent of the high radio frequency to the load and only 3.8 percent of the low audio frequency to the load.

**12.15** If the  $Q$  of a coil is greater than 5, its internal resistance  $R_i$  may be disregarded so that  $Z = X_L$ . If the  $Q$  is smaller than 5, then the resistance must be added to the reactance to obtain the impedance by the formula  $Z = \sqrt{R_i^2 + X_L^2}$ . A coil has  $R_i = 5 \Omega$  and  $X_L = 30 \Omega$  at a certain frequency. Find the  $Q$  and  $Z$  of the coil.

$$\begin{aligned} Q &= \frac{X_L}{R_i} && (12-19) \\ &= \frac{30}{5} = 6 && \text{Ans.} \end{aligned}$$

Since  $Q > 5$ , the resistance may be disregarded, so the impedance is equal to the inductive reactance.

$$Z = X_L = 30 \Omega \quad \text{Ans.}$$

We can determine the percent error by finding  $Z$  with  $R$  included and comparing values.

$$Z = \sqrt{R_i^2 + X_L^2} = \sqrt{5^2 + 30^2} = 30.4 \Omega$$

With  $R$  not included,  $Z = 30 \Omega$ , as found above. The error is  $30.4 - 30 = 0.4 \Omega$ . Therefore, the percent error is

$$\frac{0.4}{30.4} 100 = 1.3\%$$

The error is well within the range of human error in taking measurements and therefore is negligible.

**12.16** What is the inductance of a coil whose resistance is  $100 \Omega$  if it draws  $0.55$  A from a  $110$ -V,  $60$ -Hz power line?

**Step 1.** Find  $Z$ .

$$Z = \frac{V}{I} = \frac{110}{0.55} = 200 \Omega$$

**Step 2.** Find  $X_L$ .

$$\begin{aligned} Z &= \sqrt{R_i^2 + X_L^2} \\ Z^2 &= R_i^2 + X_L^2 \\ X_L &= \sqrt{Z^2 - R_i^2} = \sqrt{200^2 - 100^2} = \sqrt{3 \times 10^4} = 173 \Omega \end{aligned}$$

Step 3. Find  $L$ .

$$L = \frac{X_L}{6.28f} = \frac{173}{6.28 \times 60} = 0.459 H \quad \text{Ans.}$$

12.17 A  $500\text{-}\Omega$   $R$  is in parallel with  $300\text{-}\Omega$   $X_L$  (Fig. 12-25). Find  $I_T$ ,  $\theta$ , and  $Z_T$ .

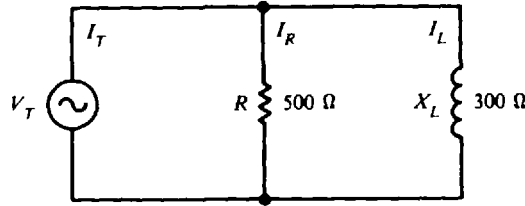


Fig. 12-25

Assume  $V_T = 500$  V. Then

$$I_R = \frac{V_T}{R} = \frac{500}{500} = 1 \text{ A}$$

$$I_L = \frac{V_T}{X_L} = \frac{500}{300} = 1.67 \text{ A}$$

$$I_T = \sqrt{I_R^2 + I_L^2} = \sqrt{1^2 + (1.67)^2} = 1.95 \text{ A} \quad \text{Ans.}$$

$$\theta = \arctan\left(-\frac{I_L}{I_R}\right) = \arctan(-1.67) = -59.1^\circ \quad \text{Ans.}$$

$$Z_T = \frac{V_T}{I_T} = \frac{500}{1.95} = 256.4 \text{ }\Omega \quad \text{Ans.}$$

12.18 The frequency in Prob. 12.17 is increased by a factor of 2. Now find  $I_T$ ,  $\theta$ , and  $Z_T$ .

Since  $X_L$  is directly proportional to  $f$ ,

$$X_L = 300(2) = 600 \text{ }\Omega$$

Assume  $V_T = 600$  V. Then

$$I_R = \frac{V_T}{R} = \frac{600}{500} = 1.2 \text{ A}$$

$$I_L = \frac{V_T}{X_L} = \frac{600}{600} = 1 \text{ A}$$

$$I_T = \sqrt{I_R^2 + I_L^2} = \sqrt{(1.2)^2 + 1^2} = 1.56 \text{ A} \quad \text{Ans.}$$

$$\theta = \arctan\left(-\frac{I_L}{I_R}\right) = \arctan\left(-\frac{1}{1.2}\right) = \arctan(-0.83) = -39.8^\circ \quad \text{Ans.}$$

$$Z_T = \frac{V_T}{I_T} = \frac{600}{1.56} = 384.6 \text{ }\Omega \quad \text{Ans.}$$

Increasing the frequency in a  $RL$  parallel circuit decreases  $\theta$ , since more  $X_L$  means less  $I_L$ .

12.19 Show that the real power  $P = (V_M I_M / 2) \cos \theta$ .

$$P = VI \cos \theta \tag{12-20}$$

The effective or rms value of voltage (or current) is its maximum value divided by  $\sqrt{2}$ . So substitute

$$V = \frac{V_M}{\sqrt{2}} \quad \text{and} \quad I = \frac{I_M}{\sqrt{2}}$$



into Eq. (12-20) to obtain

$$P = \left( \frac{V_M I_M}{\sqrt{2} \sqrt{2}} \right) \cos \theta = \frac{V_M I_M}{2} \cos \theta \quad \text{Ans.}$$

- 12.20** An induction motor operating at a power factor of 0.8 draws 1056 W from a 110-V ac line. What is the current?

Given  $\text{PF} = \cos \theta = 0.80$ ,  $V = 110 \text{ V}$ , and  $P = 1056 \text{ W}$ .

$$P = VI \cos \theta \quad (12-20)$$

from which

$$I = \frac{P}{V \cos \theta} = \frac{1056}{110(0.8)} = 12 \text{ A} \quad \text{Ans.}$$

### Supplementary Problems

- 12.21** If the rate of change of current in a coil is large, the voltage induced is high. Compare the induced voltages of a coil with an inductance of 10 mH when the rate of change of current is 2000 A/s and when the rate is 5 times faster at 10 000 A/s.  
*Ans.* When  $\Delta i/\Delta t = 2000 \text{ A/s}$ ,  $v_L = 20 \text{ V}$ . When  $\Delta i/\Delta t = 10\,000 \text{ A/s}$ ,  $v_L = 100 \text{ V}$ .
- 12.22** How fast must current change in a 100- $\mu\text{H}$  coil so that a voltage of 3 V is induced? *Ans.*  $\Delta i/\Delta t = 30\,000 \text{ A/s}$
- 12.23** At a particular instant the current changes at 1000 A/s. If 1.5 V is induced, what is the inductance of the coil? *Ans.*  $L = 1.5 \text{ mH}$
- 12.24** Find the inductive reactance of a 0.5-H choke coil at (a) 200 Hz, (b) 2000 Hz, (c) 20 kHz, and (d) 2 MHz. *Ans.* (a)  $X_L = 628 \Omega$ ; (b)  $X_L = 6280 \Omega$ ; (c)  $X_L = 62\,800 \Omega$ ; (d)  $X_L = 6280 \text{ k}\Omega$
- 12.25** A choke coil in a FM receiver has an inductance of 20  $\mu\text{H}$ . What is its reactance at 10 MHz? *Ans.*  $X_L = 1256 \Omega$
- 12.26** A 2-mH coil in a tuning circuit is resonant at 460 kHz. What is its inductive reactance at this frequency? *Ans.*  $X_L = 5778 \Omega$
- 12.27** A transmitter tuning coil must have a reactance of 95.6  $\Omega$  at 3.9 MHz. Find the inductance of the coil. *Ans.*  $L = 3.9 \mu\text{H}$
- 12.28** A 25-H choke coil in a filter circuit of a power supply operates at 60 Hz. Find (a) its inductive reactance, (b) the coil current flowing if the voltage across the coil is 105 V, and (c) the rms, peak, and average values of this current.  
*Ans.* (a)  $X_L = 9420 \Omega$ ; (b)  $I_L = 11.1 \text{ mA}$ ; (c)  $I_L = 11.1 \text{ mA}$ ;  $I_{L,M} = 15.7 \text{ mA}$ ;  $I_{L,av} = 10.1 \text{ mA}$
- 12.29** A choke coil with no resistance acts as a current limiter to 25 mA when 40 V is applied across it at a frequency of 500 kHz. What is its inductance? *Ans.*  $L = 0.51 \text{ mH}$
- 12.30** Two 2-H coils are connected in series so that the mutual inductance between them is 0.2 H. Find the total inductance when they are connected to be (a) series-aiding and (b) series-opposing.  
*Ans.* (a)  $L_T = 4.4 \text{ H}$ ; (b)  $L_T = 3.6 \text{ H}$

**12.31** A number of coils are connected together to form an inductance network. Group A is made up of three 12-H chokes in parallel; group B of a 3- and a 5-H choke in parallel; and group C of a 4- and 6-H choke in parallel. Groups A, B, and C are then connected in series. Find the equivalent inductance of (a) group A, (b) group B, and (c) group C; and (d) find the total inductance of the network.  
 Ans. (a) 4 H; (b) 1.88 H; (c) 2.4 H; (d) 8.3 H

**12.32** Find the total inductance of the circuits (Fig. 12-26). The coils are spaced far apart so that mutual inductance is negligible.  
 Ans. (a)  $L_T = 15$  mH; (b)  $L_T = 4$  mH; (c)  $L_T = 1.48$  H; (d)  $L_T = 5.1$  H

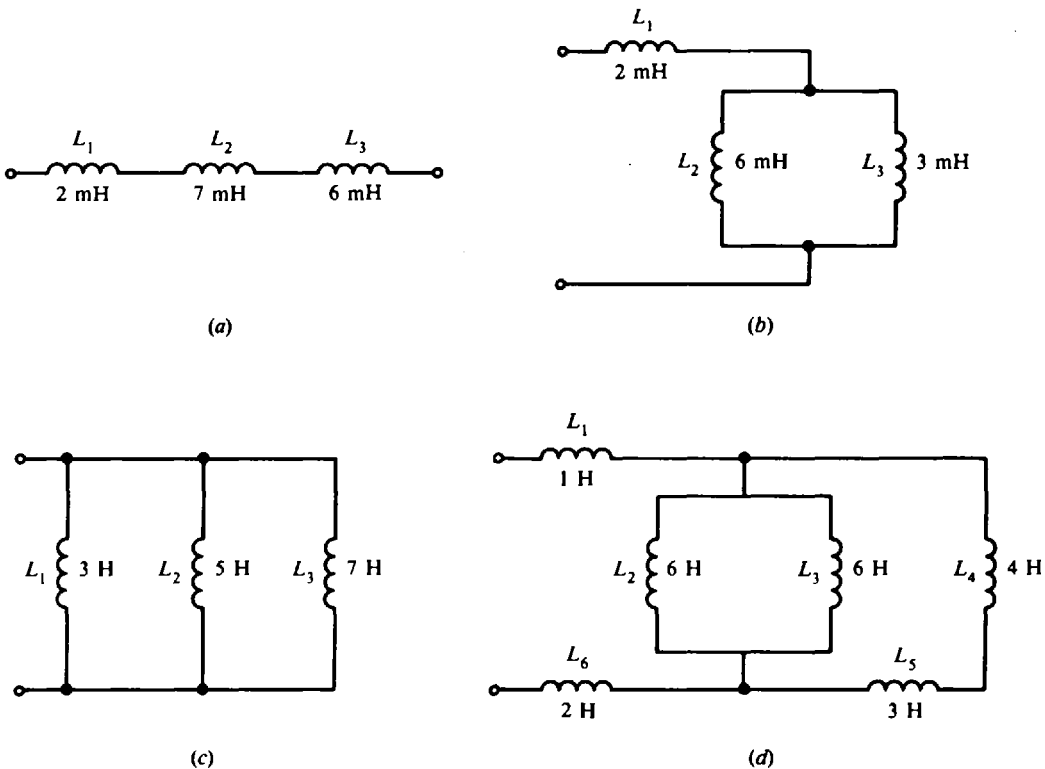


Fig. 12-26

**12.33** Find the total inductance of the circuits (Fig. 12-27). The coils are spaced sufficiently close so that mutual inductance is present.

Ans. (a)  $L_T = 11$  H; (b)  $L_T = 8$  H; (c)  $L_T = 14$  H; (d)  $L_T = 8$  H

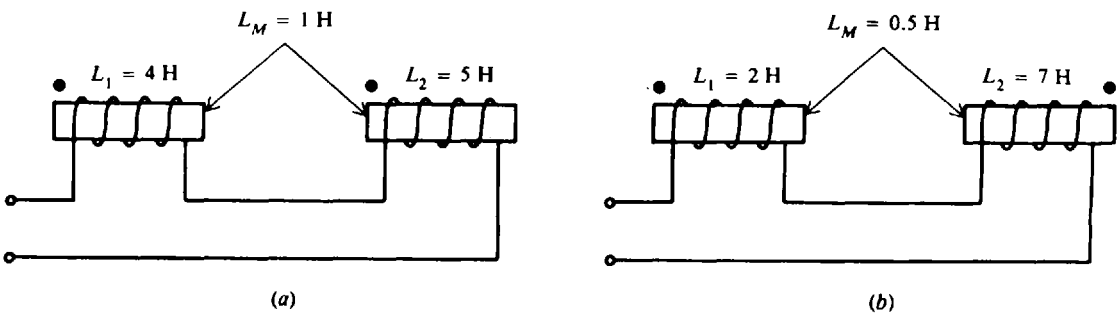


Fig. 12-27a, b

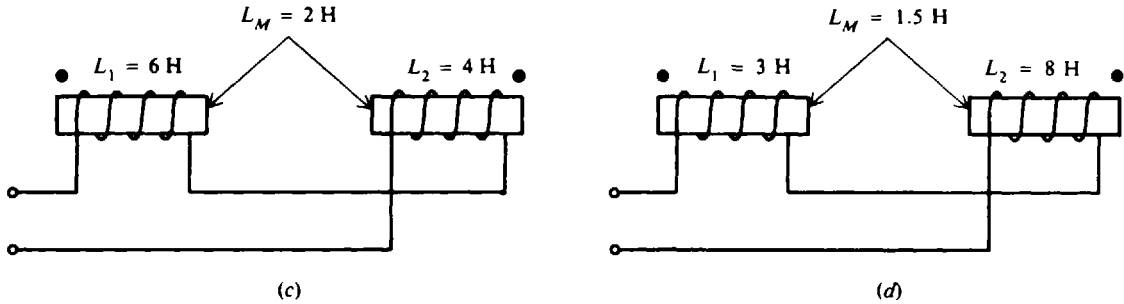


Fig. 12-27c, d

- 12.34** A resistance of  $12\ \Omega$  is connected in series with a coil whose inductive reactance is  $5\ \Omega$ . If the impressed ac voltage is  $104\ \text{V}$ , find the impedance, the line current, the voltage drop across the resistor and coil, the phase angle, and the power. Draw the voltage-phasor diagram.  
*Ans.*  $Z = 13\ \Omega$ ;  $I = 8\ \text{A}$ ;  $V_R = 96\ \text{V}$ ;  $V_L = 40\ \text{V}$ ;  $\theta = 22.6^\circ$ ,  $I$  lags  $V_T$ ;  $P = 768\ \text{W}$ ; phasor diagram: see Fig. 12-28.
- 12.35** A lightning protector circuit contains a  $55.7\text{-mH}$  coil in series with a  $6\text{-}\Omega$  resistor. What current will flow when it is tested with a  $110\text{-V}$   $60\text{-Hz}$  voltage? How much power will the lightning protector consume? *Ans.*  $I = 5.05\ \text{A}$  ( $Z = 21.8\ \Omega$ );  $P = 153\ \text{W}$

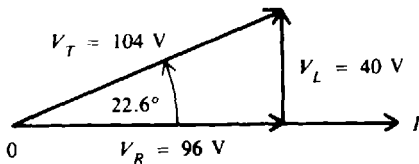


Fig. 12-28 Phasor diagram

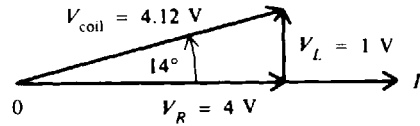


Fig. 12-29 Phasor diagram

- 12.36** The coil of a telephone relay has a resistance of  $400\ \Omega$  and an inductance of  $16\ \text{mH}$ . If the relay is operated at a frequency of  $1\ \text{kHz}$ , find the impedance of the coil and the voltage that must be impressed across the coil in order to operate the relay at its rated current of  $10\ \text{mA}$ . Draw the voltage-phasor diagram. *Ans.*  $Z = 412.4\ \Omega$ ;  $V_{\text{coil}} = 4.12\ \text{V}$ ; phasor diagram: see Fig. 12-29.
- 12.37** A  $60\text{-V}$  source at  $1.5\ \text{kHz}$  is impressed across a loudspeaker of  $5000\ \Omega$  and  $2.12\ \text{H}$  inductance. Find the current and power drawn. *Ans.*  $I = 2.9\ \text{mA}$  ( $Z = 20\ 600\ \Omega$ );  $P = 42.1\ \text{mW}$
- 12.38** What is the inductive reactance of a single-phase motor if the line voltage is  $220\ \text{V}$ , the line current is  $15\ \text{A}$ , and the resistance of the motor coils is  $10\ \Omega$ ? Also what is the angle of lag, the power factor, and the power consumed by the motor? (Treat this problem as a simple  $RL$  series circuit.)  
*Ans.*  $X_L = 10.7\ \Omega$ ;  $\theta = 47^\circ$ ;  $\text{PF} = 0.682$ ;  $P = 2250\ \text{W}$
- 12.39** What is the minimum inductance for a RF choke in series with a resistance of  $50\ \Omega$  at a radio frequency of  $1000\ \text{kHz}$ , if the resistive drop is to be considered negligible? If the applied voltage is  $100\ \text{V}$ , what is the voltage across the resistance? (See Prob. 12.13.) *Ans.*  $L = 0.08\ \text{mH}$ ;  $V_R = 9.95\ \text{V}$
- 12.40** A  $20\text{-}\Omega$  resistor and a  $15\text{-}\Omega$  inductive reactance are placed in parallel across a  $120\text{-V}$  ac line. Find the branch currents, the total current, the impedance, and the power drawn; and draw the phasor diagram. *Ans.*  $I_R = 6\ \text{A}$ ;  $I_L = 8\ \text{A}$ ;  $I_T = 10\ \text{A}$ ;  $Z_T = 12\ \Omega$ ;  $P = 720\ \text{W}$ ; phasor diagram: see Fig. 12-30.
- 12.41** A  $100\text{-}\Omega$   $R$  is in parallel with a  $100\text{-}\Omega$   $X_L$ . If  $V_T = 100\ \text{V}$ , calculate  $I_T$ ,  $\theta$ , and  $Z_T$ .  
*Ans.*  $I_T = 1.41\ \text{A}$ ;  $\theta = -45^\circ$ ;  $Z_T = 70.7\ \Omega$

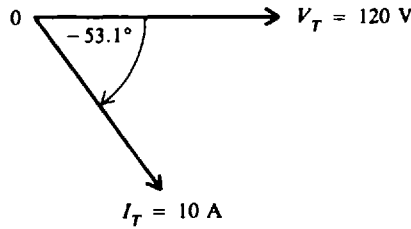


Fig. 12-30 Phasor diagram

- 12.42 The frequency is halved in Prob. 12.41. Find  $I_T$ ,  $\theta$ , and  $Z_T$ . Compare the difference in values.  
 Ans.  $I_T = 2.24$  A;  $\theta = -63.4^\circ$ ;  $Z_T = 44.6 \Omega$ . Reducing the frequency in a  $RL$  parallel circuit increases  $\theta$  because less  $X_L$  means more  $I_L$ . With less  $X_L$ ,  $Z_T$  is less.
- 12.43 A  $50\text{-}\Omega$   $R$  and a  $120\text{-}\Omega$   $X_L$  are connected in parallel across a  $120\text{-V}$  ac line. Find the (a) branch currents, (b) total current, (c) impedance, and (d) power drawn; and (e) draw the phasor diagram.  
 Ans. (a)  $I_R = 2.4$  A;  $I_L = 1$  A; (b)  $I_T = 2.6$  A; (c)  $Z_T = 46.2 \Omega$ ; (d)  $P = 288$  W; (e) phasor diagram: see Fig. 12-31.

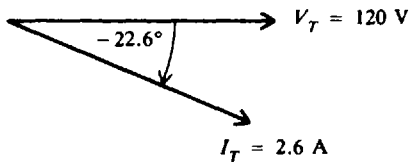


Fig. 12-31

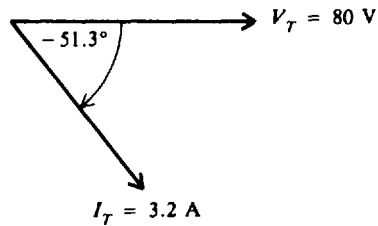


Fig. 12-32

- 12.44 A  $40\text{-}\Omega$  resistor and a  $10\text{-mH}$  coil are in parallel across an  $80\text{-V}$   $500\text{-Hz}$  ac line. Find the (a) branch currents, (b) total current, (c) impedance, and (d) power drawn; and (e) draw the phasor diagram.  
 Ans. (a)  $I_R = 2$  A;  $I_L = 2.5$  A; (b)  $I_T = 3.2$  A; (c)  $Z_T = 25 \Omega$ ; (d)  $P = 160$  W; (e) phasor diagram: see Fig. 12-32.
- 12.45 For the high-pass filter circuit (Fig. 12-33), find the (a) branch currents, (b) total current, and (c) percentage of total current that passes through the resistor for the case of audio frequency (AF) at  $1$  kHz and for the case of radio frequency (RF) at  $2$  MHz. (Calculate current values to three significant figures.)  
 Ans. AF case: (a)  $I_L = 0.797$  A;  $I_R = 0.0333$  A; (b)  $I_T = 0.798$  A; (c)  $4.2\%$ . RF case: (a)  $I_L = 0.398$  mA;  $I_R = 33.3$  mA; (b)  $I_T = 33.3$  mA; (c)  $100\%$

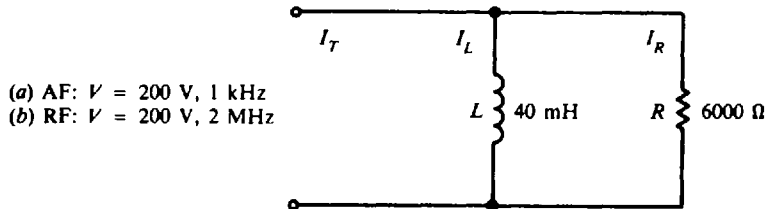


Fig. 12-33

- 12.46 A  $120\text{-V}$   $60\text{-Hz}$  power line is connected across a  $12\text{-H}$  choke coil whose resistance is  $500 \Omega$ . Find (a) the inductive reactance, (b) the  $Q$  of the coil, (c) the impedance, and (d) the current.  
 Ans. (a)  $X_L = 4522 \Omega$ ; (b)  $Q = 9.0$ ; (c)  $Z = 4522 \Omega$ ; (d)  $I_L = 27$  mA
- 12.47 The primary of an audio-frequency transformer has a resistance of  $100 \Omega$  and an inductance of  $25$  mH. What are the inductive reactance and the impedance at  $2$  kHz?  
 Ans.  $X_L = 314 \Omega$ ;  $Z = 330 \Omega$

- 12.48 Find the inductance of a coil whose resistance is  $500\ \Omega$  if it draws 10 mA from a 110-V 60-Hz source. *Ans.*  $L = 29.2\ \text{H}$  ( $X_L = 11\ 000\ \Omega$ )
- 12.49 A coil having a  $Q$  of 25 draws 20 mA when connected to a 12-V, 1-kHz power supply. What is its inductance? *Ans.*  $L = 95.5\ \text{mH}$  ( $X_L = 600\ \Omega$ )
- 12.50 For the circuit (Fig. 12-34), find (a) the inductive reactance, (b) the impedance, (c) the rms current, and (d) the peak current.  
*Ans.* (a)  $X_L = 37.7\ \Omega$ ; (b)  $Z = 41.0\ \Omega$  (circuit  $R = 16\ \Omega$ ); (c)  $I = 5.85\ \text{A}$ ; (d)  $I_M = 8.27\ \text{A}$
- 12.51 An inductive load operating at a phase angle of  $53^\circ$  draws 1400 W from a 120-V line. Find the current drawn. *Ans.*  $I = 19.4\ \text{A}$
- 12.52 An inductance of  $5\ \Omega$  resistance and  $12\ \Omega$  reactance is connected across a 117-V 60-Hz ac line. Find the real, apparent, and reactive power. *Ans.*  $P = 405\ \text{W}$ ;  $S = 1053\ \text{VA}$ ;  $Q = 972\ \text{VAR}$  lagging

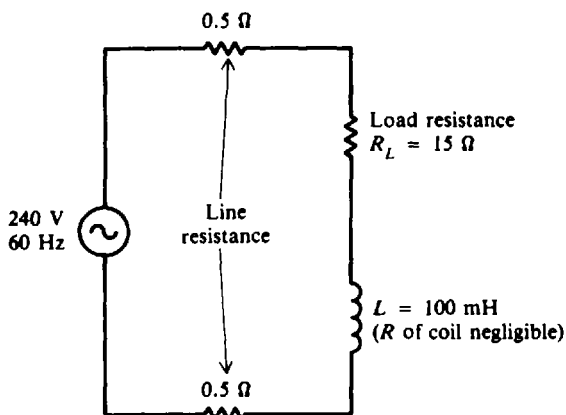


Fig. 12-34

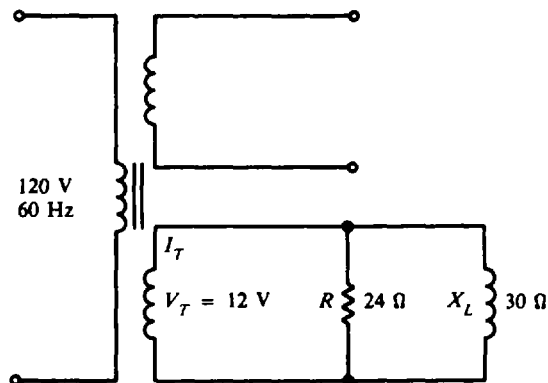


Fig. 12-35

- 12.53 A toy electric train semaphore has a  $24\text{-}\Omega$  lamp in parallel with a solenoid coil of  $30\text{-}\Omega$  inductive reactance (Fig. 12-35). If it operates from the 12-V winding of a 60-Hz power transformer, find (a) the total current, (b) the impedance, (c) the phase angle, (d) the power drawn, and (e) the reactive power.  
*Ans.* (a)  $I_T = 0.64\ \text{A}$ ; (b)  $Z_T = 18.8\ \Omega$ ; (c)  $\theta = -38.7^\circ$ ; (d)  $P = 6\ \text{W}$ ; (e)  $Q = 4.8\ \text{VAR}$  lagging

## Capacitance, Capacitive Reactance, and Capacitive Circuits

### CAPACITOR

A *capacitor* is an electrical device which consists of two conducting plates of metal separated by an insulating material called a *dielectric* (Fig. 13-1a). Schematic symbols shown (Fig. 13-1b and c) apply to all capacitors.

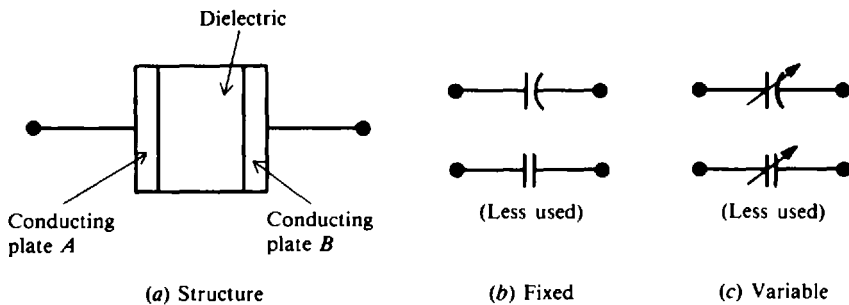


Fig. 13-1 Capacitor and schematic symbols

A capacitor stores electric charge in the dielectric. The two plates of the capacitor shown in Fig. 13-2a are electrically neutral since there are as many protons (positive charge) as electrons (negative charge) on each plate. Thus the capacitor has *no charge*. Now a battery is connected across the plates (Fig. 13-2b). When the switch is closed (Fig. 13-2c), the negative charge on plate A is attracted to the positive terminal of the battery, while the positive charge on plate B is attracted to the negative terminal of the battery. This movement of charges will continue until the difference in charge between plates A and B is equal to the electromotive force (voltage) of the battery. The capacitor is now *charged*. Since almost none of the charge can cross the space between plates, the capacitor will remain in this condition even if the battery is removed (Fig. 13-3a). However, if a conductor is placed across the plates (Fig. 13-3b), the electrons find a path back to plate A and the charges on each plate are again neutralized. The capacitor is now *discharged*.

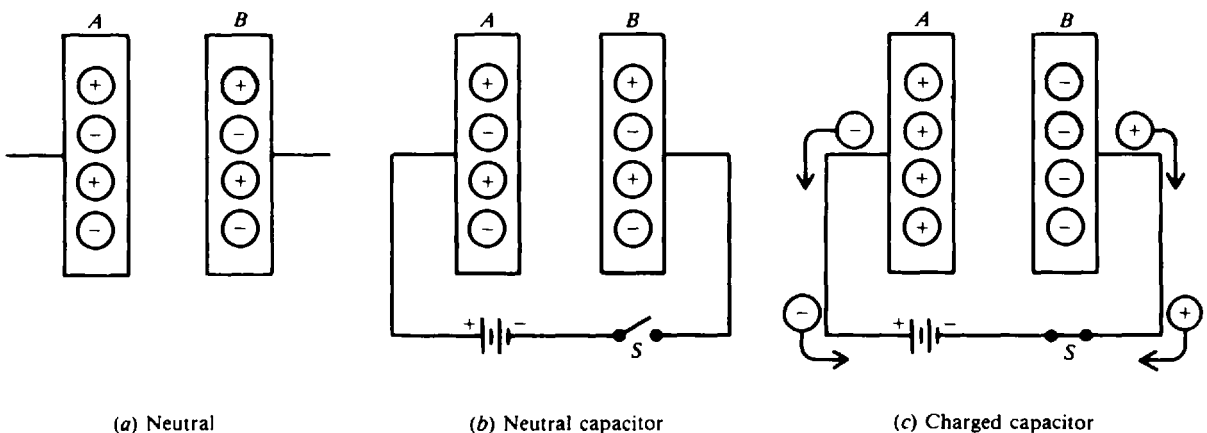


Fig. 13-2 Charging a capacitor

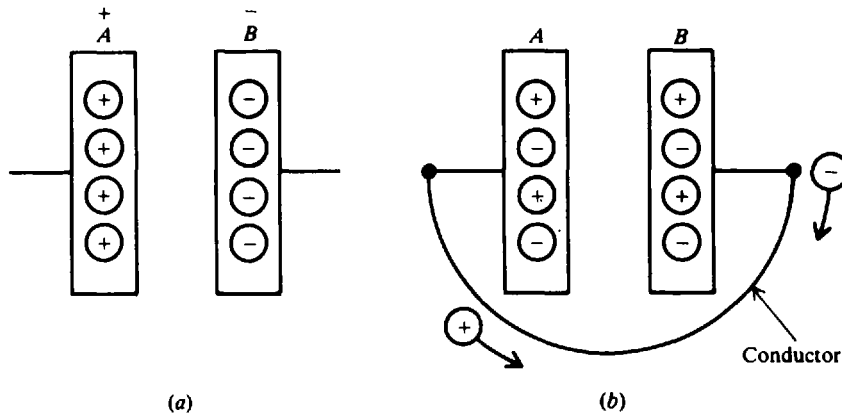


Fig. 13-3 Discharging a capacitor

**Example 13.1** Explain the charging and discharging action of a simple capacitor circuit when switch 1 is closed with switch 2 open (Fig. 13-4a), and when switch 1 is open with switch 2 closed (Fig. 13-4b).

When switch  $S_1$  is closed and switch  $S_2$  is open (Fig. 13-4a), the battery voltage is applied across the two plates  $A$  and  $B$ . The capacitor charges to a voltage equal to that of the battery. Plate  $A$  is charged positively and plate  $B$  is charged negatively. When  $S_1$  is open and  $S_2$  is closed, the excess electrons on plate  $B$  will move through  $S_2$  to plate  $A$  (Fig. 13-4b). Now the capacitor acts as a voltage source with plate  $A$  the positive terminal and plate  $B$  the negative terminal. The motion of electrons off plate  $B$  reduces its negative charge, and their arrival at plate  $A$  reduces its positive charge. This motion of electrons continues until there is no charge on plate  $A$  or plate  $B$  and the voltage between the two plates is zero.

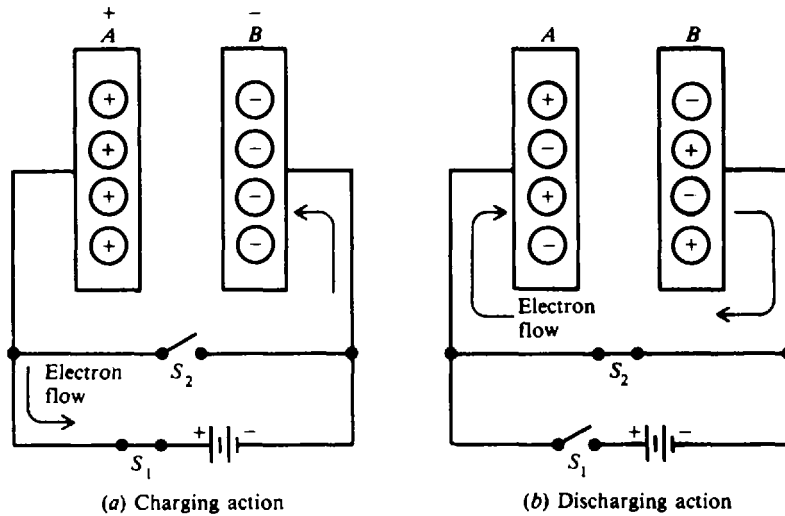


Fig. 13-4 Simple capacitor circuit

**CAPACITANCE**

Electrically, *capacitance* is the ability to store an electric charge. Capacitance is equal to the amount of charge that can be stored in a capacitor divided by the voltage applied across the plates

$$C = \frac{Q}{V} \tag{13-1}$$

where  $C$  = capacitance, F  
 $Q$  = amount of charge, C  
 $V$  = voltage, V

Equation (13-1) can be rewritten as follows:

$$Q = CV \quad (13-2)$$

$$V = \frac{Q}{C} \quad (13-3)$$

The unit of capacitance is the farad (F). The farad is that capacitance that will store one coulomb of charge in the dielectric when the voltage applied across the capacitor terminals is one volt.

The characteristic of a dielectric that describes its ability to store electric energy is called the *dielectric constant*. Air is used as a reference and is given a dielectric constant of 1. Some other dielectric materials are Teflon, paper, mica, Bakelite, or ceramic. Paper, for example, has an average dielectric constant of 4, meaning it can provide an electric flux density four times as great as that for air for the same applied voltage and equal physical size.

The capacitance of a capacitor depends on the area of the conductor plates, the separation between the plates, and the dielectric constant of the insulating material. For a capacitor with two parallel plates, the formula to find its capacitance is

$$C = k \frac{A}{d} (8.85 \times 10^{-12}) \quad (13-4)$$

where  $C$  = capacitance, F  
 $k$  = dielectric constant of the insulating material  
 $A$  = area of the plate,  $m^2$   
 $d$  = distance between the plates, m

The farad is too high a unit for most capacitors. Therefore, we conveniently use the microfarad ( $\mu F$ ), which equals one-millionth farad ( $10^{-6}$  F), the nanofarad (nF), which equals one-billionth farad ( $10^{-9}$  F), and the picofarad (pF), which equals one-millionth microfarad ( $10^{-6}$   $\mu F$ ). Thus,  $1 F = 10^6 \mu F = 10^9 nF = 10^{12} pF$ .

**Example 13.2** What is the capacitance of a capacitor that stores 4 C of charge at 2 V?

$$\begin{aligned} C &= \frac{Q}{V} & (13-1) \\ &= \frac{4}{2} = 2 F & \text{Ans.} \end{aligned}$$

**Example 13.3** What is the charge taken on by a 10-F capacitor at 3 V?

$$\begin{aligned} Q &= CV & (13-2) \\ &= 10(3) = 30 C & \text{Ans.} \end{aligned}$$

**Example 13.4** What is the voltage across a 0.001-F capacitor that stores 2 C?

$$\begin{aligned} V &= \frac{Q}{C} & (13-3) \\ &= \frac{2}{0.001} = 2000 V & \text{Ans.} \end{aligned}$$

**Example 13.5** The area of one plate of a two-plate mica capacitor is  $0.0025 m^2$  and the separation between plates is 0.02 m. If the dielectric constant of mica is 7, find the capacitance of the capacitor.

$$\begin{aligned} C &= k \frac{A}{d} (8.85 \times 10^{-12}) & (13-4) \\ &= 7 \frac{0.0025}{0.02} (8.85 \times 10^{-12}) = 7.74 \times 10^{-12} F = 7.74 pF & \text{Ans.} \end{aligned}$$



**Example 13.6** If the number of plates in Example 13.5 is increased to form a multiple capacitor with five dielectric spaces, and neither the dielectric nor the spacing is changed for the capacitor, what is the new capacitance? Since capacitance is proportional to area, five parallel plates will give a capacitance five times greater so that

$$C = 5(7.74) = 38.7 \text{ pF} \quad \text{Ans.}$$

**TYPES OF CAPACITORS**

Commercial capacitors are named according to their dielectric. Most common are air, mica, paper, and ceramic capacitors, plus the electrolytic type. These types are compared in Table 13-1. Most types of capacitors can be connected to an electric circuit without regard to polarity. But electrolytic capacitors and certain ceramic capacitors are marked to show which side must be connected to the more positive side of a circuit.

**Table 13-1 Types of Capacitors**

Dielectric	Construction	Capacitance Range
Air	Meshed plates	10–400 pF
Mica	Stacked sheets	10–5000 pF
Paper	Rolled foil	0.001–1 μF
Ceramic	Tubular	0.5–1600 pF
	Disk	0.002–0.1 μF
Electrolytic	Aluminum	5–1000 μF
	Tantalum	0.01–300 μF

**CAPACITORS IN SERIES AND PARALLEL**


When capacitors are connected in series (Fig. 13-5), the total capacitance  $C_T$  is

Series: 
$$\frac{1}{C_T} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots + \frac{1}{C_n} \quad (13-5)$$

The total capacitance of two capacitors in series is

Series: 
$$C_T = \frac{C_1 C_2}{C_1 + C_2} \quad (13-6)$$

When  $n$  number of series capacitors have the same capacitance,  $C_T = C/n$ .

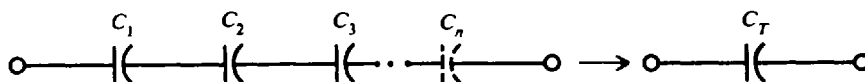

**Fig. 13-5 Capacitors in series**

When capacitors are connected in parallel (Fig. 13-6), the total capacitance  $C_T$  is the sum of the individual capacitances.

Parallel:  $C_T = C_1 + C_2 + C_3 + \dots + C_n$  (13-7)

There is a limit to the voltage that may be applied across any capacitor. If too high a voltage is applied, a current will be forced through the dielectric, sometimes burning a hole in it. The capacitor then will short-circuit and must be discarded. The maximum voltage that may be applied to a capacitor is called the *working voltage* and should not be exceeded.

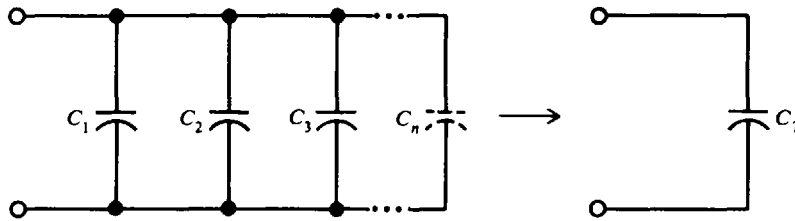


Fig. 13-6 Capacitances in parallel

**Example 13.7** Find the total capacitance of a 3- $\mu$ F, a 5- $\mu$ F, and a 10- $\mu$ F capacitor connected in series (Fig. 13-7).

Write Eq. (13-5) for three capacitors in series.

$$\frac{1}{C_T} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} = \frac{1}{3} + \frac{1}{5} + \frac{1}{10} = \frac{19}{30}$$

$$C_T = \frac{30}{19} = 1.6 \mu\text{F} \quad \text{Ans.}$$

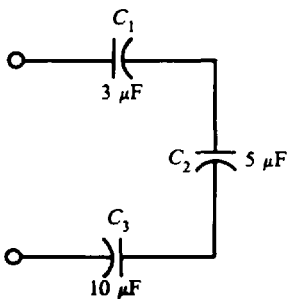


Fig. 13-7

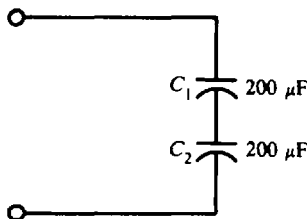


Fig. 13-8

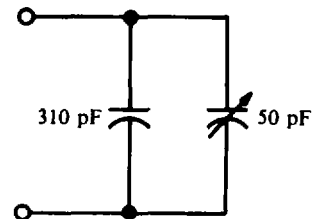


Fig. 13-9

**Example 13.8** What is the total capacitance and working voltage of a capacitor series combination if \$C\_1\$ and \$C\_2\$ are both 200- $\mu$ F 150-V capacitors (Fig. 13-8)?

$$C_T = \frac{C}{n} = \frac{200}{2} = 100 \mu\text{F} \quad \text{Ans.}$$

The total voltage that may be applied across a group of capacitors in series is equal to the sum of the working voltages of the individual capacitors. Therefore,

$$\text{Working voltage} = 150 + 150 = 300 \text{ V} \quad \text{Ans.}$$

**Example 13.9** A capacitor in a radio receiver tuning circuit has a capacitance of 310 pF (Fig. 13-9). When the stage is aligned, a variable capacitor (called a *trimmer*) in parallel with it is adjusted to a capacitance of 50 pF. What is the total capacitance of the combination?

Write Eq. (13-7) for two capacitors in parallel.

$$C_T = C_1 + C_2 = 310 + 50 = 360 \text{ pF} \quad \text{Ans.}$$

### CAPACITIVE REACTANCE

Capacitive reactance  $X_C$  is the opposition to the flow of ac current due to the capacitance in the circuit. The unit of capacitive reactance is the ohm. Capacitive reactance can be found by using the equation

$$X_C = \frac{1}{2\pi fC} = \frac{0.159}{fC} \quad (13-8)$$

where  $X_C$  = capacitive reactance,  $\Omega$   
 $f$  = frequency, Hz  
 $C$  = capacitance, F

If any two quantities in Eq. (13-8) are known, the third can be found.

$$C = \frac{0.159}{fX_C} \quad (13-9)$$

$$f = \frac{0.159}{CX_C} \quad (13-10)$$

Voltage and current in a circuit containing only capacitive reactance can be found using Ohm's law. However, in the case of a capacitive circuit,  $R$  is replaced by  $X_C$ .

$$V_C = I_C X_C \quad (13-11)$$

$$I_C = \frac{V_C}{X_C} \quad (13-12)$$

$$X_C = \frac{V_C}{I_C} \quad (13-13)$$

where  $I_C$  = current through the capacitor, A  
 $V_C$  = voltage across the capacitor, V  
 $X_C$  = capacitive reactance,  $\Omega$

**Example 13.10** What is the capacitive reactance of a 0.001-F capacitor at 60 Hz (Fig. 13-10)?

$$\begin{aligned} X_C &= \frac{0.159}{fC} \\ &= \frac{0.159}{60(0.001)} = 2.65 \Omega \quad \text{Ans.} \end{aligned} \quad (13-8)$$

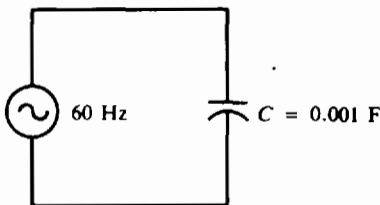


Fig. 13-10

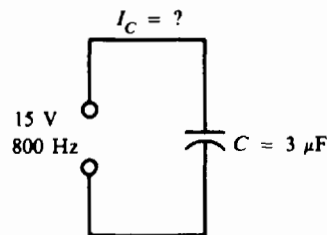


Fig. 13-11

**Example 13.11** A capacitor in a telephone circuit has a capacitance of  $3 \mu\text{F}$  (Fig. 13-11). What current flows through it when 15 V at 800 Hz is impressed across it?

Find  $X_C$  and then  $I_C$  by Ohm's law.

$$\begin{aligned} X_C &= \frac{0.159}{fC} \\ &= \frac{0.159}{800(3 \times 10^{-6})} = 66.25 \Omega \end{aligned} \quad (13-8)$$

$$I_C = \frac{V_C}{X_C} \tag{13-12}$$

$$= \frac{15}{66.25} = 0.226 = 226 \text{ mA} \quad \text{Ans.}$$

**Example 13.12** A 120-Hz 25-mA ac current flows in a circuit containing a 10 μF capacitor (Fig. 13-12). What is the voltage drop across the capacitor?

Find  $X_C$  and then  $V_C$  by Ohm's law.

$$X_C = \frac{0.159}{fC} \tag{13-8}$$

$$= \frac{0.159}{120(10 \times 10^{-6})} = 132.5 \Omega$$

$$V_C = I_C X_C \tag{13-11}$$

$$= (25 \times 10^{-3})(132.5) = 3.31 \text{ V} \quad \text{Ans.}$$

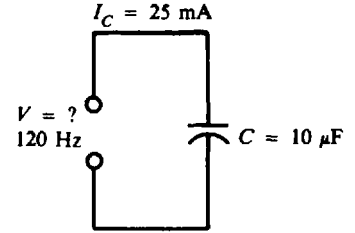


Fig. 13-12

**CAPACITIVE CIRCUITS**

**Capacitance Only**

If an ac voltage  $v$  is applied across a circuit having *only* capacitance (Fig. 13-13a), the resulting ac current through the capacitance,  $i_c$ , will lead the voltage across the capacitance,  $v_c$ , by 90° (Fig. 13-13b and c). (Quantities expressed as lowercase letters,  $i_c$  and  $v_c$ , indicate instantaneous values.) Voltages  $v$  and  $v_c$  are the same because they are parallel. Both  $i_c$  and  $v_c$  are sine waves with the same frequency. In series circuits, the current  $I_C$  is the horizontal phasor for reference (Fig. 13-13d) so the voltage  $V_C$  can be considered to lag  $I_C$  by 90°.

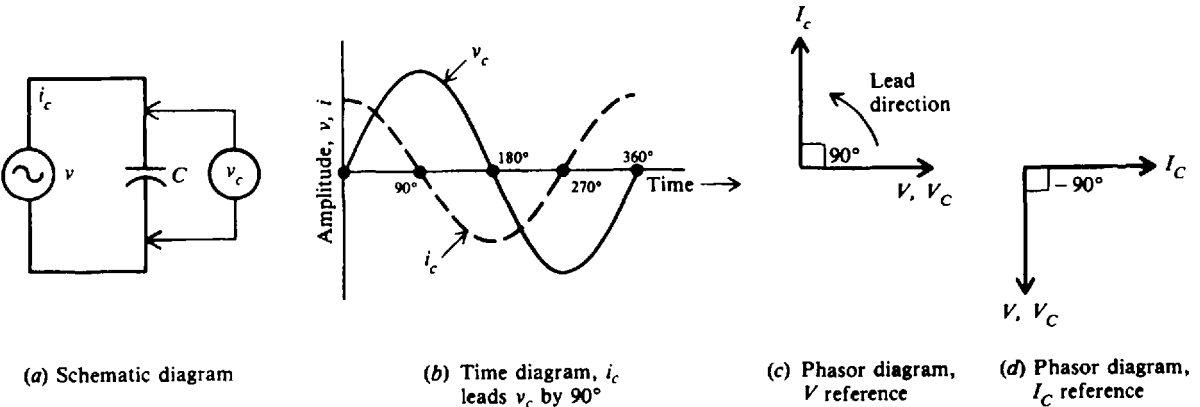


Fig. 13-13 Circuit with C only

**RC in Series**

As with inductive circuits, the combination of resistance and capacitive reactance (Fig. 13-14a) is called *impedance*. In a series circuit containing  $R$  and  $X_C$ , the same current  $I$  flows in  $X_C$  and  $R$ . The voltage drop across  $R$  is  $V_R = IR$ , and the voltage drop across  $X_C$  is  $V_C = IX_C$ . The voltage across  $X_C$  lags the current through  $X_C$  by 90° (Fig. 13-14b). The voltage across  $R$  is in phase with  $I$  since resistance does not produce a phase shift (Fig. 13-14b).

To find the total voltage  $V_T$ , we add phasors  $V_R$  and  $V_C$ . Since they form a right triangle (Fig. 13-15),

$$V_T = \sqrt{V_R^2 + V_C^2} \tag{13-14}$$

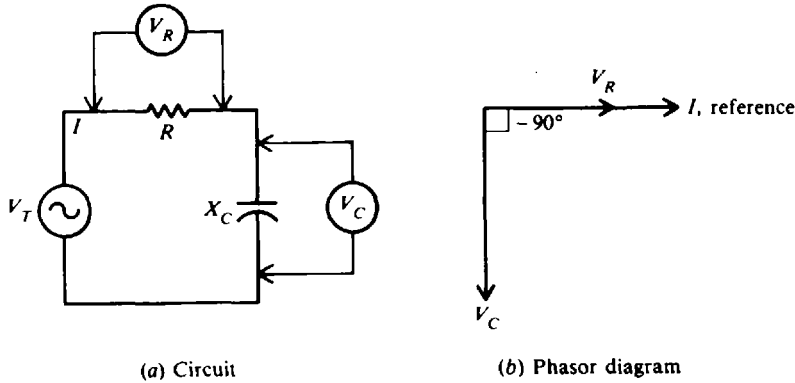


Fig. 13-14 R and  $X_C$  in series

Note that the  $IX_C$  phasor is downward, exactly opposite from an  $IX_L$  phasor (see Fig. 12-11), because of the opposite phase angle.

The phase angle  $\theta$  between  $V_T$  and  $V_R$  (Fig. 13-15) is expressed according to the following equation:

$$\tan \theta = -\frac{V_C}{V_R}$$

$$\theta = \arctan\left(-\frac{V_C}{V_R}\right) \tag{13-15}$$

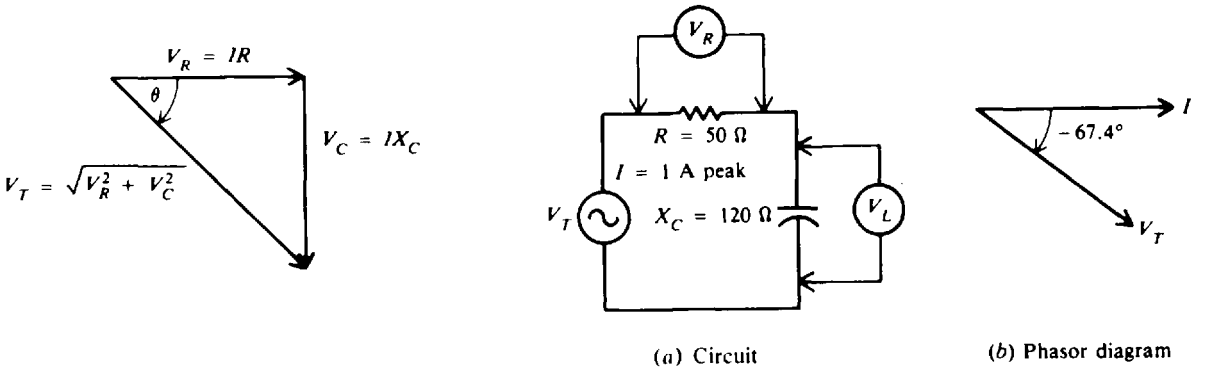


Fig. 13-15 Voltage-triangle phasor

Fig. 13-16a, b

**Example 13.13** A RC series ac circuit has a current of 1 A peak with  $R = 50 \Omega$  and  $X_C = 120 \Omega$  (Fig. 13-16a). Calculate  $V_R$ ,  $V_C$ ,  $V_T$ , and  $\theta$ . Draw the phasor diagram of  $V_C$  and  $I$ . Also draw the time diagram of  $i$ ,  $v_R$ ,  $v_C$ , and  $v_T$ .

Then

$$V_R = IR = 1(50) = 50 \text{ V peak} \quad \text{Ans.}$$

$$V_C = IX_C = 1(120) = 120 \text{ V peak} \quad \text{Ans.}$$

$$V_T = \sqrt{V_R^2 + V_C^2} \tag{13-14}$$


$$= \sqrt{50^2 + 120^2}$$

$$= \sqrt{2500 + 14400} = \sqrt{16900} = 130 \text{ V peak} \quad \text{Ans.}$$

$$\theta = \arctan\left(-\frac{V_C}{V_R}\right) \tag{13-15}$$

$$= \arctan\left(-\frac{120}{50}\right) = \arctan(-2.4) = -67.4^\circ \quad \text{Ans.}$$

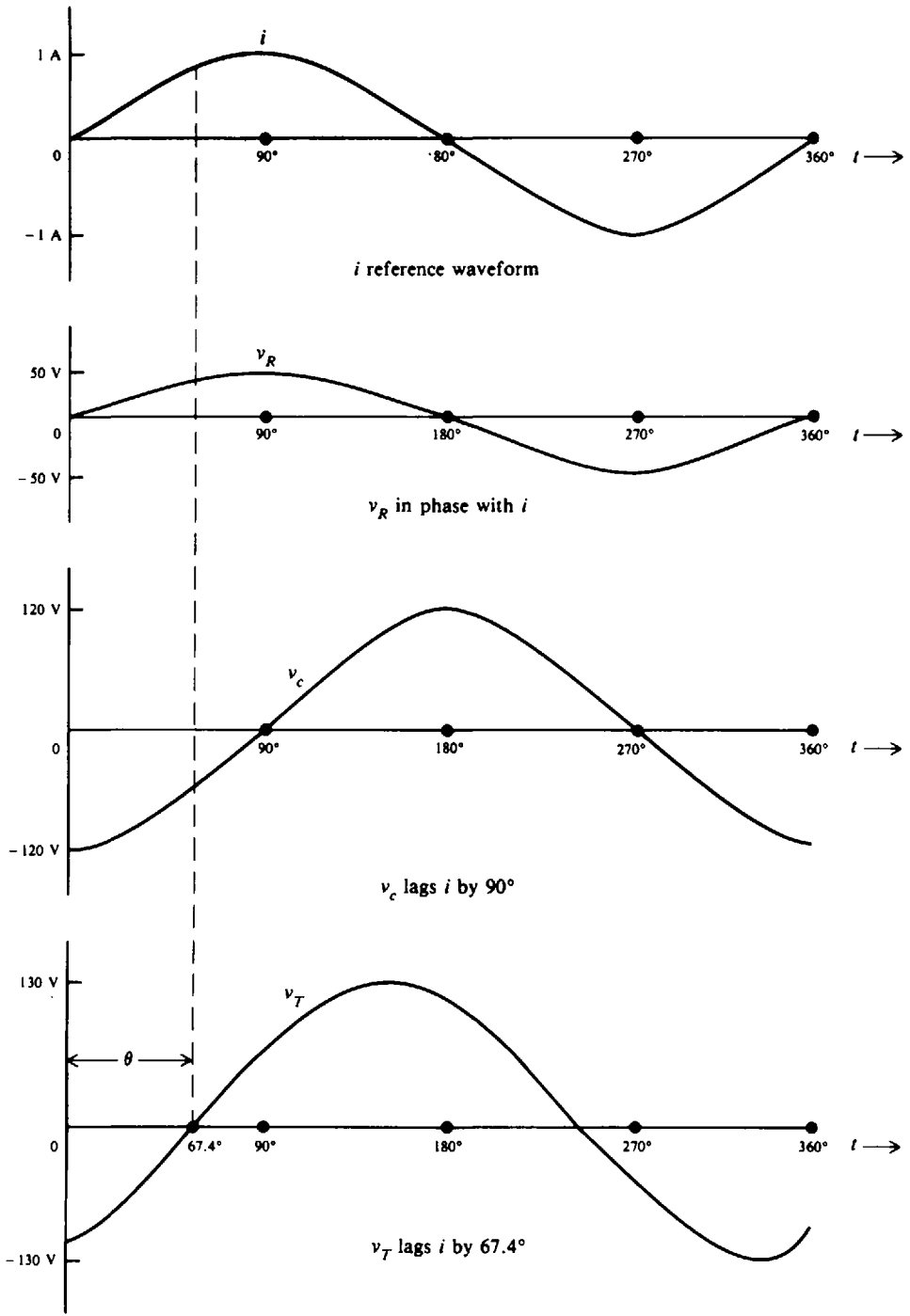In a series circuit since  $I$  is the same in  $R$  and  $X_C$ ,  $I$  is shown as the reference phasor at  $0^\circ$  (Fig. 13-16b).  $I$  leads  $V_T$  by  $67.4^\circ$  or, equivalently,  $V_T$  lags  $I$  by  $67.4^\circ$ . For the time diagram, see Fig. 13-16c.



(c) Time diagram

**Fig. 13-16c** Time diagram


**Impedance in Series RC**

The voltage triangle (Fig. 13-15) corresponds to the impedance triangle (Fig. 13-17) because the common factor  $I$  in  $V_C$  and  $V_R$  cancels.

$$V_C = IX_C$$

$$V_R = IR$$

$$\tan \theta = -\frac{IX_C}{IR} = -\frac{X_C}{R}$$

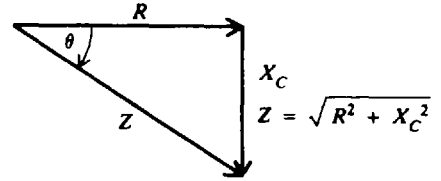

**Fig. 13-17** Series RC impedance triangle

Impedance  $Z$  is equal to the phasor sum of  $R$  and  $X_C$ .

$$Z = \sqrt{R^2 + X_C^2} \tag{13-16}$$

The phase angle  $\theta$  is

$$\theta = \arctan\left(-\frac{X_C}{R}\right) \tag{13-17}$$

**Example 13.14** A  $40\text{-}\Omega$   $X_C$  and a  $30\text{-}\Omega$   $R$  are in series across a  $120\text{-V}$  source (Fig. 13-18a). Calculate  $Z$ ,  $I$ , and  $\theta$ . Draw the phasor diagram.

$$Z = \sqrt{R^2 + X_C^2}$$

$$= \sqrt{30^2 + 40^2} = \sqrt{2500} = 50 \Omega \quad \text{Ans.} \tag{13-16}$$


By Ohm's law,

$$I = \frac{V_T}{Z} = \frac{120}{50} = 2.4 \text{ A} \quad \text{Ans.}$$

$$\theta = \arctan\left(-\frac{X_C}{R}\right) \tag{13-17}$$

$$= \arctan\left(-\frac{40}{30}\right) = \arctan(-1.33) = -53.1^\circ \quad \text{Ans.}$$

For the phasor diagram, see Fig. 13-18b.

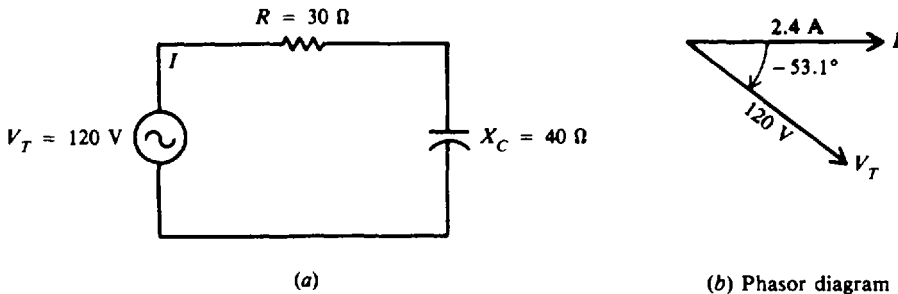

**Fig. 13-18**

**RC in Parallel**

In the RC parallel circuit (Fig. 13-19a), the voltage is the same across the source,  $R$ , and  $X_C$  since they are all in parallel. Each branch has its individual current. The resistive branch current  $I_R = V_T/R$  is in phase with  $V_T$ . The capacitive branch current  $I_C = V_T/X_C$  leads  $V_T$  by  $90^\circ$  (Fig. 13-19b). The phasor diagram has the source voltage  $V_T$  as the reference phasor because it is the same throughout the circuit. The total line current  $I_T$  equals the phasor sum of  $I_R$  and  $I_C$  (Fig. 13-19c).

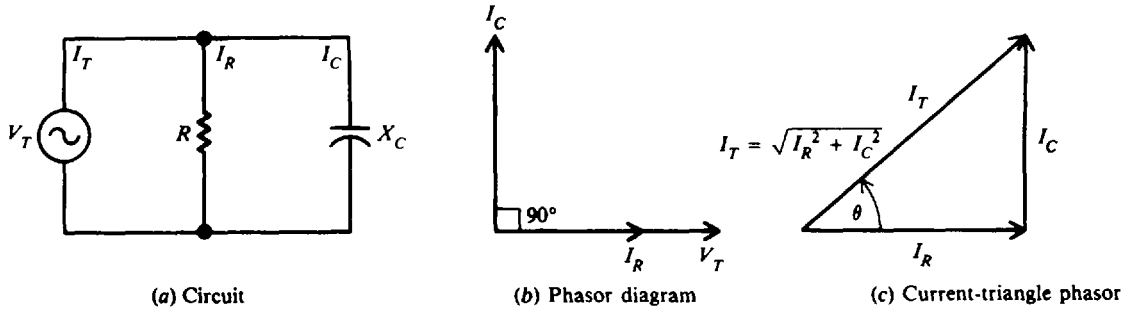


Fig. 13-19  $X_C$  and  $R$  in parallel

$$I_T = \sqrt{I_R^2 + I_C^2} \tag{13-18}$$

$$\tan \theta = \frac{I_C}{I_R}$$

$$\theta = \arctan \frac{I_C}{I_R} \tag{13-19}$$

**Impedance in Parallel RC**

The impedance of a parallel circuit equals the total voltage  $V_T$  divided by the total current  $I_T$ .

$$Z_T = \frac{V_T}{I_T} \tag{13-20}$$

**Example 13.15** A  $15\text{-}\Omega$  resistor and a capacitor of  $20\ \Omega$  capacitive reactance are placed in parallel across a  $120\text{-V}$  ac line (Fig. 13-20a). Calculate  $I_R$ ,  $I_C$ ,  $I_T$ ,  $\theta$ , and  $Z$ . Draw the phasor diagram.

$$I_R = \frac{V_T}{R} = \frac{120}{15} = 8\ \text{A} \quad \text{Ans.}$$

$$I_C = \frac{V_T}{X_C} = \frac{120}{20} = 6\ \text{A} \quad \text{Ans.}$$

$$I_T = \sqrt{I_R^2 + I_C^2} = \sqrt{8^2 + 6^2} = \sqrt{100} = 10\ \text{A} \quad \text{Ans.} \tag{13-18}$$

$$\theta = \arctan \frac{I_C}{I_R} \tag{13-19}$$

$$= \arctan \frac{6}{8} = \arctan 0.75 = 36.9^\circ \quad \text{Ans.}$$

$$Z_T = \frac{V_T}{I_T} \tag{13-20}$$

$$= \frac{120}{10} = 12\ \Omega \quad \text{Ans.}$$

For the phasor diagram, see Fig. 13-20b.

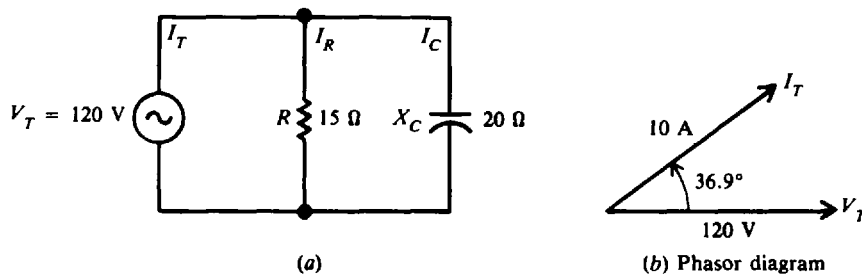


Fig. 13-20



### POWER IN RC CIRCUITS

The power formulas given previously for  $RL$  circuits are equally applicable to  $RC$  circuits.

$$\text{Real power } P = VI \cos \theta, \text{ W} \quad (13-21)$$

or 
$$P = I^2 R = \frac{V^2}{R}, \text{ W} \quad (13-22)$$

$$\text{Reactive power } Q = VI \sin \theta, \text{ VAR} \quad (13-23)$$

$$\text{Apparent power } S = VI, \text{ VA} \quad (13-24)$$

Capacitance, like inductance, consumes no power. The only part of the circuit consuming power is the resistance.

Summary Table for Series and Parallel  $RC$  Circuits

$X_C$ and $R$ in Series	$X_C$ and $R$ in Parallel
$I$ the same in $X_C$ and $R$	$V_T$ the same across $X_C$ and $R$
$V_T = \sqrt{V_R^2 + V_C^2}$	$I_T = \sqrt{I_R^2 + I_C^2}$
$Z = \sqrt{R^2 + X_C^2} = \frac{V_T}{I}$	$Z_T = \frac{V_T}{I_T}$
$V_C$ lags $V_R$ by $90^\circ$	$I_C$ leads $I_R$ by $90^\circ$
$\theta = \arctan\left(-\frac{X_C}{R}\right)$	$\theta = \arctan\frac{I_C}{I_R}$

### Solved Problems

- 13.1 What is the total capacitance of three capacitors connected in parallel if their values are  $0.15 \mu\text{F}$ ,  $50 \text{ V}$ ;  $0.015 \mu\text{F}$ ,  $100 \text{ V}$ ; and  $0.003 \mu\text{F}$ ,  $150 \text{ V}$  (Fig. 13-21)? What would be the working voltage of this combination?

Write Eq. (13-5) for three capacitors in parallel.

$$C_T = C_1 + C_2 + C_3 = 0.15 + 0.015 + 0.003 = 0.168 \mu\text{F} \quad \text{Ans.}$$

The working voltage of a group of parallel capacitors is only as high as the lowest working voltage. Therefore, the working voltage of this combination is only  $50 \text{ V}$ .

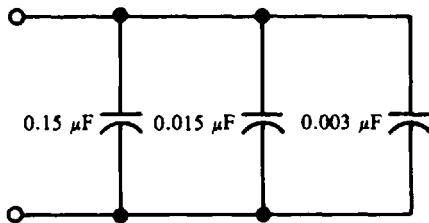


Fig. 13-21

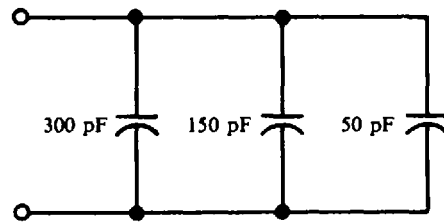


Fig. 13-22

- 13.2 A technician has the following capacitors available:  $300 \text{ pF}$ ,  $75 \text{ V}$ ;  $250 \text{ pF}$ ,  $50 \text{ V}$ ;  $200 \text{ pF}$ ,  $50 \text{ V}$ ;  $150 \text{ pF}$ ,  $75 \text{ V}$ ; and  $50 \text{ pF}$ ,  $75 \text{ V}$ . Which of these should be connected in parallel to form a combination with a capacitance of  $500 \text{ pF}$  and  $75 \text{ V}$  working voltage?

Capacitors with voltage ratings less than  $75 \text{ V}$  must not be used because of possible short-circuit damage. The remaining capacitors with  $75\text{-V}$  ratings are  $300$ ,  $150$ , and  $50 \text{ pF}$ , the sum of which is  $500 \text{ pF}$ . Therefore, the safe parallel combination is as shown in Fig. 13-22, where  $C_T = 300 + 150 + 50 = 500 \text{ pF}$ .

13.3 What is the range of total capacitances available in an oscillator circuit that uses a variable tuning capacitor of 35- to 300-pF range in series with a fixed capacitor of 250 pF (Fig. 13-23)?

At the low point in the range of total capacitance, we have 35 pF in series with 250 pF.

$$C_{T1} = \frac{C_1 C_2}{C_1 + C_2} = \frac{35(250)}{35 + 250} = \frac{8750}{285} = 30.7 \text{ pF} \quad \text{Ans.}$$

At the high point in the range, we have 300 pF in series with 250 pF.

$$C_{T2} = \frac{300(250)}{300 + 250} = \frac{75\,000}{550} = 136.4 \text{ pF} \quad \text{Ans.}$$

Therefore, the range is from 30.7 to 136.4 pF.

13.4 What capacitance must be added in parallel with a 550-pF capacitor in order to get a total capacitance of 750 pF (Fig. 13-24)?

Write Eq. (13-7) for two capacitors in parallel.

$$\begin{aligned} C_T &= C_1 + C_2 \\ 750 &= 550 + C_2 \\ C_2 &= 750 - 550 = 200 \text{ pF} \quad \text{Ans.} \end{aligned}$$

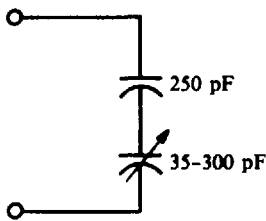


Fig. 13-23

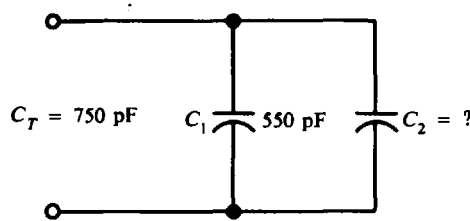


Fig. 13-24

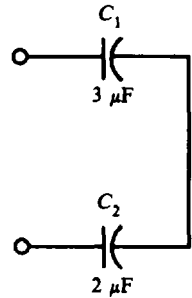


Fig. 13-25

13.5 Find the total capacitance of the capacitive networks shown in Figs. 13-25, 13-26a, and 13-27a.

(a) See Fig. 13-25. Simple series combination:

$$C_T = \frac{C_1 C_2}{C_1 + C_2} = \frac{3(2)}{3 + 2} = \frac{6}{5} = 1.2 \mu\text{F} \quad \text{Ans.}$$

(b) See Fig. 13-26a, b, and c. Series-parallel combination:

Parallel:  $C_a = C_2 + C_3 = 0.1 + 0.2 = 0.3 \mu\text{F}$

Series:  $C_T = \frac{C_1 C_a}{C_1 + C_a} = \frac{0.3(0.3)}{0.3 + 0.3} = \frac{0.09}{0.6} = 0.15 \mu\text{F} \quad \text{Ans.}$

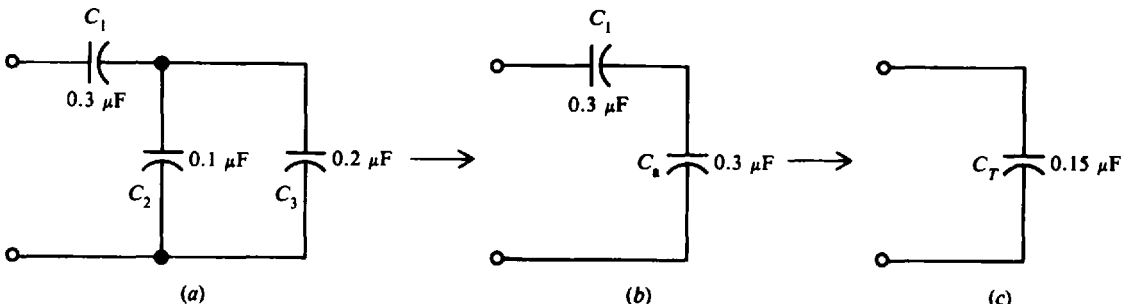


Fig. 13-26

(c) See Fig. 13-27*a*, *b*, and *c*. Parallel-series combination:

$$\text{Series: } C_a = \frac{C_3 C_4}{C_3 + C_4} = \frac{4(5)}{4 + 5} = \frac{20}{9} = 2.22 \text{ pF}$$

$$\text{Parallel: } C_T = C_1 + C_2 + C_a = 2 + 3 + 2.22 = 7.22 \text{ pF} \quad \text{Ans.}$$

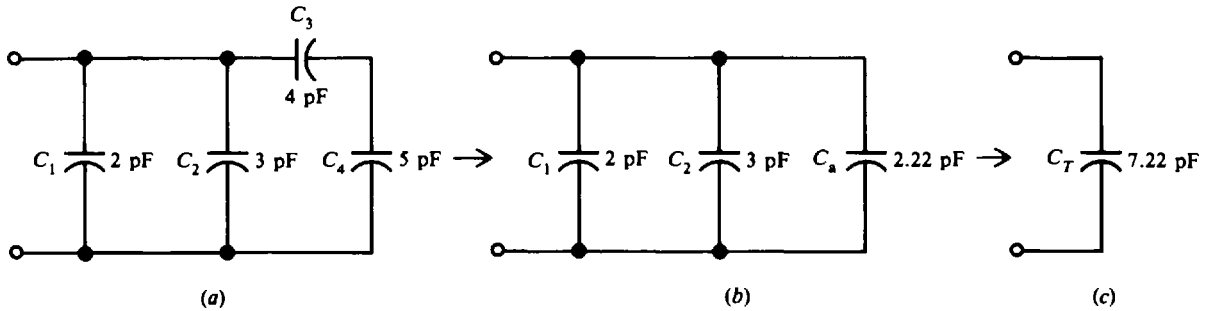


Fig. 13-27

13.6 Find the total capacitance of the series circuit and the capacitive reactance of the group of capacitors when used in a 60-Hz circuit (Fig. 13-28).

$$\frac{1}{C_T} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \quad (13-5)$$

$$= \frac{1}{0.1} + \frac{1}{0.5} + \frac{1}{0.25} = 0.5$$

$$C_T = \frac{0.5}{8} = 0.0625 \mu\text{F} \quad \text{Ans.}$$

$$X_C = \frac{0.159}{fC_T} \quad (13-8)$$

$$= \frac{0.159}{60(0.0625 \times 10^{-6})} = 42\,400 \Omega \quad \text{Ans.}$$

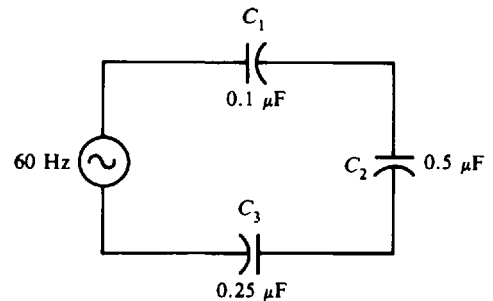


Fig. 13-28

13.7 A capacitor draws 6 mA when connected across a 110-V 60-Hz line. What will be the current drawn if both the frequency and capacitance are doubled?

We look at two relationships. First, because  $I_C = V_C/X_C$ , we can say  $I_C$  is inversely proportional to  $X_C$ , or

$$I_C \propto \frac{1}{X_C}$$

Second, because  $X_C = 0.159/fC$ , we can say  $X_C$  is inversely proportional to the product of  $f$  and  $C$ , or

$$X_C \propto \frac{1}{fC}$$

So if  $f$  and  $C$  are doubled,  $X_C$  is decreased by 1/4.

$$X_C \propto \frac{1}{(2f)(2C)} = \frac{1}{4fC}$$

And when  $X_C$  is decreased by 1/4,  $I_C$  is increased four times. Therefore

$$I_C = 4(6) = 24 \text{ mA} \quad \text{Ans.}$$

13.8 A 20- $\mu\text{F}$  capacitor in an audio amplifier circuit produces a voltage drop of 5 V at 1 kHz. Find the current passed by the capacitor.

Find  $X_C$  and then  $I_C$ .

$$X_C = \frac{0.159}{fC} \quad (13-8)$$

$$= \frac{0.159}{(1 \times 10^3)(20 \times 10^{-6})} = 7.95 \Omega$$

$$I_C = \frac{V_C}{X_C} \quad (13-12)$$

$$= \frac{5}{7.95} = 0.629 \text{ A} \quad \text{Ans.}$$

- 13.9 Calculate the value of the bypass capacitor in an audio circuit if it is to have a reactance of  $800 \Omega$  at 10 kHz.

$$C = \frac{0.159}{fX_C} \quad (13-9)$$

$$= \frac{0.159}{(10 \times 10^3)(800)} = 0.02 \mu\text{F} \quad \text{Ans.}$$

- 13.10 A capacitor is inserted in a circuit to obtain a leading current of 5 A. If the voltage is 110 V, 60 Hz, what is the capacitance?

Find  $X_C$  and then  $C$ .

$$X_C = \frac{V_C}{I_C} \quad (13-13)$$

$$= \frac{110}{5} = 22 \Omega$$

$$C = \frac{0.159}{fX_C} \quad (13-9)$$

$$= \frac{0.159}{60(22)} = 121 \times 10^{-6} = 121 \mu\text{F} \quad \text{Ans.}$$

- 13.11 A capacitance of 20 pF draws 10 mA when connected across a 95-V source. Find the frequency of the ac voltage.

Find  $X_C$  and then  $f$ .

$$X_C = \frac{V_C}{I_C} \quad (13-13)$$

$$= \frac{95}{10 \times 10^{-3}} = 9500 \Omega$$

$$f = \frac{0.159}{CX_C} \quad (13-10)$$

$$= \frac{0.159}{(20 \times 10^{-12})(9500)} = 838 \text{ kHz} \quad \text{Ans.}$$

- 13.12 Find the impedance of a  $RC$  combination when the coupling capacitor is  $0.01 \mu\text{F}$ , the audio frequency is 1 kHz, and the resistance of the circuit is  $3 \text{ k}\Omega$  (Fig. 13-29). A coupling capacitor, because it provides more reactance at lower frequencies, results in less ac voltage across  $R$  and more across  $C$ .

Find  $X_C$  and then  $Z$ .

$$X_C = \frac{0.159}{fC} \tag{13-9}$$

$$= \frac{0.159}{(1 \times 10^3)(0.01 \times 10^{-6})} = 15\,900 \, \Omega$$

$$Z = \sqrt{R^2 + X_C^2} \tag{13-16}$$

$$= \sqrt{3000^2 + 15\,900^2} = 16\,180 \, \Omega \quad \text{Ans.}$$

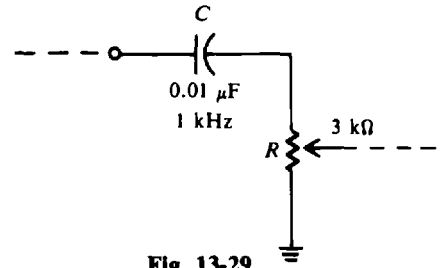


Fig. 13-29

**13.13** In a series  $RC$  circuit, the *higher* the  $X_C$  compared with  $R$ , the more capacitive is the circuit. With higher  $X_C$  there is more voltage drop across the capacitive reactance, and the phase angle increases toward  $-90^\circ$ . To illustrate, find the indicated quantity.

Case	$R, \Omega$	$X_C, \Omega$	$Z, \Omega$	$\theta$	Nature of Circuit
(a) $X_C = R$	10	10	?	?	?
(b) $X_C < R$	10	1	?	?	?
(c) $X_C > R$	1	10	?	?	?

$$(a) \quad Z = \sqrt{R^2 + X_C^2} \tag{13-16}$$

$$= \sqrt{10^2 + 10^2} = 14.1 \, \Omega \quad \text{Ans.}$$

$$\theta = \arctan\left(-\frac{X_C}{R}\right) \tag{13-17}$$

$$= \arctan\left(-\frac{10}{10}\right) = \arctan(-1) = -45^\circ \quad \text{Ans.}$$

The circuit is capacitive.

$$(b) \quad Z = \sqrt{10^2 + 1^2} = 10.0 \, \Omega \quad \text{Ans.}$$

$$\theta = \arctan(-0.1) = -5.7^\circ \quad \text{Ans.}$$

The circuit is only slightly capacitive.

$$(c) \quad Z = \sqrt{1^2 + 10^2} = 10.0 \, \Omega \quad \text{Ans.}$$

$$\theta = \arctan(-10) = -84.3^\circ \quad \text{Ans.}$$

The circuit is almost entirely capacitive. Recall that if  $R = 0$  (pure capacitive circuit),  $Z = X_C = 10 \, \Omega$  at  $\theta = -90^\circ$ . The complete table is as follows:

Case	$R, \Omega$	$X_C, \Omega$	$Z, \Omega$	$\theta$	Nature of Circuit
(a) $X_C = R$	10	10	14.1	$-45^\circ$	Capacitive
(b) $X_C < R$	10	1	10.0	$-5.7^\circ$	Slightly capacitive
(c) $X_C > R$	1	10	10.0	$-84.3^\circ$	Very capacitive

**13.14** In a parallel  $RC$  circuit, as  $X_C$  becomes *smaller* compared with  $R$ , practically all the line current is the  $I_C$  component. Thus the parallel circuit is capacitive. The phase angle approaches  $90^\circ$  because the line current is mostly capacitive. To illustrate, find the indicated quantity. Assume  $V_T = 10 \, \text{V}$ .

	Case	$R, \Omega$	$X_C, \Omega$	$I_R, A$	$I_C, A$	$I_T, A$	$\theta$	Nature of Circuit
(a)	$X_C = R$	10	10	?	?	?	?	?
(b)	$X_C > R$	1	10	?	?	?	?	?
(c)	$X_C < R$	10	1	?	?	?	?	?

(a)

$$I_R = \frac{V_T}{R} = \frac{10}{10} = 1 \text{ A} \quad \text{Ans.}$$

$$I_C = \frac{V_T}{X_C} = \frac{10}{10} = 1 \text{ A} \quad \text{Ans.}$$

$$I_T = \sqrt{I_R^2 + I_C^2} \quad (13-18)$$

$$= \sqrt{1^2 + 1^2} = 1.41 \text{ A} \quad \text{Ans.}$$

$$\theta = \arctan \frac{I_C}{I_R} \quad (13-19)$$

$$= \arctan 1 = 45^\circ \quad \text{Ans.}$$

The circuit is capacitive.

(b)

$$I_R = \frac{10}{1} = 10 \text{ A} \quad \text{Ans.}$$

$$I_C = \frac{10}{10} = 1 \text{ A} \quad \text{Ans.}$$

$$I_T = \sqrt{10^2 + 1^2} = 10.0 \text{ A} \quad \text{Ans.}$$

$$\theta = \arctan \frac{1}{10} = 5.7^\circ \quad \text{Ans.}$$

The circuit is only slightly capacitive.

(c)

$$I_R = \frac{10}{10} = 1 \text{ A} \quad \text{Ans.}$$

$$I_C = \frac{10}{1} = 10 \text{ A} \quad \text{Ans.}$$

$$I_T = \sqrt{1^2 + 10^2} = 10.0 \text{ A} \quad \text{Ans.}$$

$$\theta = \arctan 10 = 84.3^\circ \quad \text{Ans.}$$

The circuit is almost entirely capacitive.

Recall that if  $R = 0$  (pure capacitive circuit),  $I_T = I_C = 10 \text{ A}$  at  $\theta = 90^\circ$ . The complete table is as follows:

	Case	$R, \Omega$	$X_C, \Omega$	$I_R, A$	$I_C, A$	$I_T, A$	$\theta$	Nature of Circuit
(a)	$X_C = R$	10	10	1	1	1.4	$45^\circ$	Capacitive
(b)	$X_C > R$	1	10	10	1	10.0	$5.7^\circ$	Slightly capacitive
(c)	$X_C < R$	10	1	1	10	10.0	$84.3^\circ$	Very capacitive

**13.15** A voltage of 10 V at a frequency of 20 kHz is applied across a 1- $\mu\text{F}$  capacitor. Find the current and the real power used. Draw the phasor diagram.

Find  $X_C$  and then  $I_C$ .

$$X_C = \frac{0.159}{fC}$$

$$= \frac{0.159}{(20 \times 10^3)(1 \times 10^{-6})} = 7.95 \Omega$$

$$I_C = \frac{V_C}{X_C}$$

$$= \frac{10}{7.95} = 1.26 \text{ A} \quad \text{Ans.}$$

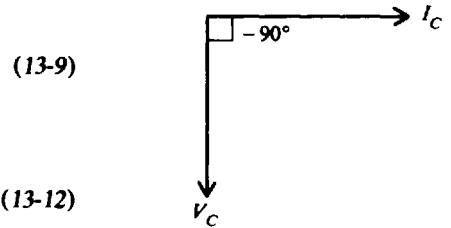


Fig. 13-30 Phasor diagram

Now find  $P$ .

$$P = VI \cos \theta \tag{13-21}$$

$$V = V_C \quad \text{and} \quad I = I_C \quad \text{so}$$

$$P = 10(1.26)(\cos 90^\circ) = 10(1.26)(0) = 0 \text{ W} \quad \text{Ans.}$$

No net power is consumed in the circuit when there is no resistance. For the phasor diagram, see Fig. 13-30.  $I_C$  leads  $V_C$  by  $90^\circ$ .

**13.16** A capacitance of  $3.53 \mu\text{F}$  and a resistance of  $40 \Omega$  are connected in series across a 110-V 1.5-kHz ac source (Fig. 13-31). Find  $X_C$ ,  $Z$ ,  $\theta$ ,  $I$ ,  $V_R$ ,  $V_C$ , and  $P$ . Draw the phasor diagram.

**Step 1.** Find  $X_C$ .

$$X_C = \frac{0.159}{fC} = \frac{0.159}{(1.5 \times 10^3)(3.53 \times 10^{-6})} = 30 \Omega \quad \text{Ans.}$$

**Step 2.** Find  $Z$  and  $\theta$ .

$$Z = \sqrt{R^2 + X_C^2} = \sqrt{40^2 + 30^2} = 50 \Omega \quad \text{Ans.}$$

$$\theta = \arctan\left(-\frac{X_C}{R}\right) = \arctan\left(-\frac{30}{40}\right) = \arctan(-0.75) = -36.9^\circ \quad \text{Ans.}$$

**Step 3.** Find  $I$ .

$$I = \frac{V_T}{Z} = \frac{110}{50} = 2.2 \text{ A} \quad \text{Ans.}$$

**Step 4.** Find  $V_R$  and  $V_C$ . By Ohm's law,


$$V_R = IR = 2.2(40) = 88 \text{ V} \quad \text{Ans.}$$

$$V_C = IX_C = 2.2(30) = 66 \text{ V} \quad \text{Ans.}$$


**Step 5.** Find  $P$ .

$$P = I^2R = (2.2)^2(40) = 193.6 \text{ W} \quad \text{Ans.}$$

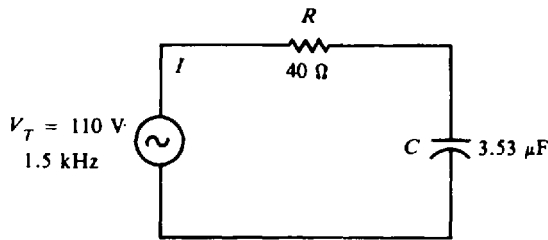**Step 6.** Draw the phasor diagram (see Fig. 13-31b).  $I$  leads  $V_T$  by  $36.9^\circ$ .




(a)

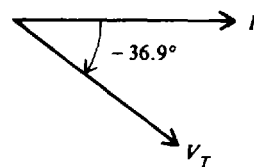

(b) Phasor diagram

Fig. 13-31

**13.17** The purpose of a low-pass filter circuit (Fig. 13-32) is to permit low frequencies to pass on to the load but to prevent the passing of high frequencies. Find the branch currents, total current, phase angle, and the percentage of the total current passing through the resistor for (a) a 1.5-kHz (low) audio-frequency signal and (b) a 1-MHz (high) radio-frequency signal.

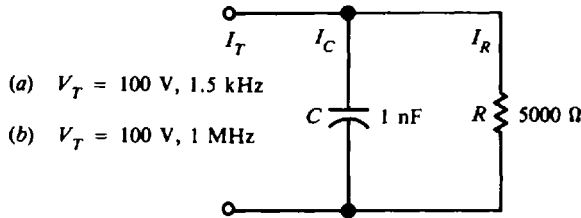

**Fig. 13-32**

(a) **Step 1.** Find  $X_C$  at  $f = 1.5$  kHz.

$$X_C = \frac{0.159}{fC} = \frac{0.159}{(1.5 \times 10^3)(1 \times 10^{-9})} = 106 \text{ k}\Omega$$

**Step 2.** Find branch currents  $I_C$  and  $I_R$ .

$$I_C = \frac{V_T}{X_C} = \frac{100}{106 \times 10^3} = 0.94 \text{ mA} \quad \text{Ans.}$$

$$I_R = \frac{V_T}{R} = \frac{100}{5 \times 10^3} = 20 \text{ mA} \quad \text{Ans.}$$

**Step 3.** Find  $I_T$  and  $\theta$ .

$$I_T = \sqrt{I_R^2 + I_C^2} = \sqrt{20^2 + (0.94)^2} = \sqrt{400 + 0.88} = \sqrt{400.88} = 20.02 \text{ mA} \quad \text{Ans.}$$

$$\theta = \arctan \frac{I_C}{I_R} = \arctan \frac{0.94}{20} = \arctan 0.047 = 2.7^\circ \quad \text{Ans.}$$

**Step 4.** Find  $I_R$  as a percentage of  $I_T$ .

$$\frac{I_R}{I_T} \times 100 = \frac{20}{20.02} \times 100 = 0.999(100) = 99.9\% \quad \text{Ans.}$$

Thus, practically all the 1.5-kHz audio-signal current passes through the resistor.

(b) **Step 1.** Find  $X_C$  now at  $f = 1$  MHz.

$$X_C = \frac{0.159}{fC} = \frac{0.159}{(1 \times 10^6)(1 \times 10^{-9})} = 159 \Omega$$

**Step 2.** Find  $I_C$  and  $I_R$ .

$$I_C = \frac{V_T}{X_C} = \frac{100}{159} = 0.629 = 629 \text{ mA} \quad \text{Ans.}$$

$$I_R = 20 \text{ mA} \quad \text{Ans.}$$

$I_R$  is the same as in part (a).

**Step 3.** Find  $I_T$  and  $\theta$ .

$$I_T = \sqrt{I_R^2 + I_C^2} = \sqrt{20^2 + 629^2} = \sqrt{400 + 395\,641} = \sqrt{396\,041} = 629.3 \text{ mA} \quad \text{Ans.}$$

$$\theta = \arctan \frac{I_C}{I_R} = \arctan \frac{629}{20} = \arctan 31.45 = 88.2^\circ \quad \text{Ans.}$$

**Step 4.** Find  $I_R$  as a percentage of  $I_T$ .

$$\frac{I_R}{I_T} \times 100 = \frac{20}{629.3} \times 100 = 0.032(100) = 3.2\% \quad \text{Ans.}$$



Thus, only 3.2 percent of the 1-MHz radio signal current passes through the resistor.

It is clear that the circuit is an excellent low-pass filter by passing practically all the low-frequency (1.5-kHz) current through the resistor, but very little of the high-frequency (1-MHz) current through it.

### Supplementary Problems

- 13.18 What is the capacitance of a capacitor that stores 10.35 C at 3 V?    *Ans.*  $C = 3.45 \text{ F}$
- 13.19 What charge is taken on by a 0.5-F capacitor connected across a 50-V source?    *Ans.*  $Q = 25 \text{ C}$
- 13.20 Find the capacitance of a capacitor that has one plate area of  $0.5 \text{ m}^2$ , a distance between plates of 0.01 m, and a dielectric of paper with a dielectric constant of 3.5.    *Ans.*  $C = 1549 \text{ pF}$
- 13.21 What is the reactance of a 500-pF capacitor at (a) 40 kHz, (b) 100 kHz, and (c) 1200 kHz?  
*Ans.* (a)  $X_C = 7950 \Omega$ ; (b)  $X_C = 3180 \Omega$ ; (c)  $X_C = 265 \Omega$
- 13.22 Two capacitors in parallel are connected across a 120-V line. The first capacitor has a charge of 0.00006 C and the second capacitor has a charge of 0.000048 C. What is the capacitance of each capacitor and what is the total capacitance?    *Ans.*  $C_1 = 0.5 \mu\text{F}$ ;  $C_2 = 0.4 \mu\text{F}$ ;  $C_T = 0.9 \mu\text{F}$
- 13.23 Find the indicated quantity.

	C, F	Q, C	V, V
(a)	?	11	110
(b)	0.3	?	220
(c)	0.2	50	?

*Ans.*

	C, F	Q, C	V, V
(a)	0.1	....	....
(b)	....	66	....
(c)	....	....	250

- 13.24 The capacitance of a known parallel-plate capacitor with air as a dielectric is  $0.248 \mu\text{F}$ . What is the capacitance if (a) Teflon with a dielectric constant of 2.1 replaces air; (b) the area of one plate is reduced by one-half; (c) the separation distance is increased by a factor of  $1\frac{1}{2}$ ; and (d) rubber with a dielectric constant of 3 replaces air, the area of a plate is increased by  $1\frac{1}{4}$ , and the separation distance is reduced to three-fourths its original value?  
*Ans.* (a)  $C = 0.521 \mu\text{F}$ ; (b)  $C = 0.124 \mu\text{F}$ ; (c)  $C = 0.165 \mu\text{F}$ ; (d)  $C = 1.24 \mu\text{F}$
- 13.25 What is the reactance of an oscillator capacitor of 400 pF to a frequency of 630 kHz?  
*Ans.*  $X_C = 631 \Omega$
- 13.26 Find the total capacitance of the capacitive networks shown (Fig. 13-33).  
*Ans.* (a)  $C_T = 0.40 \mu\text{F}$ ; (b)  $C_T = 0.065 \mu\text{F}$ ; (c)  $C_T = 0.04 \mu\text{F}$ ; (d)  $C_T = 0.05 \mu\text{F}$ ;  
(e)  $C_T = 0.84 \mu\text{F}$
- 13.27 A 10-V 1-MHz signal appears across a 1200-pF capacitor. Find the current passed by the capacitor.  
*Ans.*  $I_C = 75.2 \text{ mA}$ ; ( $X_C = 133 \Omega$ )
- 13.28 A filter circuit consists of an inductor and two capacitors (Fig. 13-34). Its purpose is to smooth the power-supply voltages so that a pure direct current is delivered to the load. If the reactance of  $C_1$  is  $175 \Omega$  at a frequency of 60 Hz, what is its capacitance?    *Ans.*  $C_1 = 15.1 \mu\text{F}$

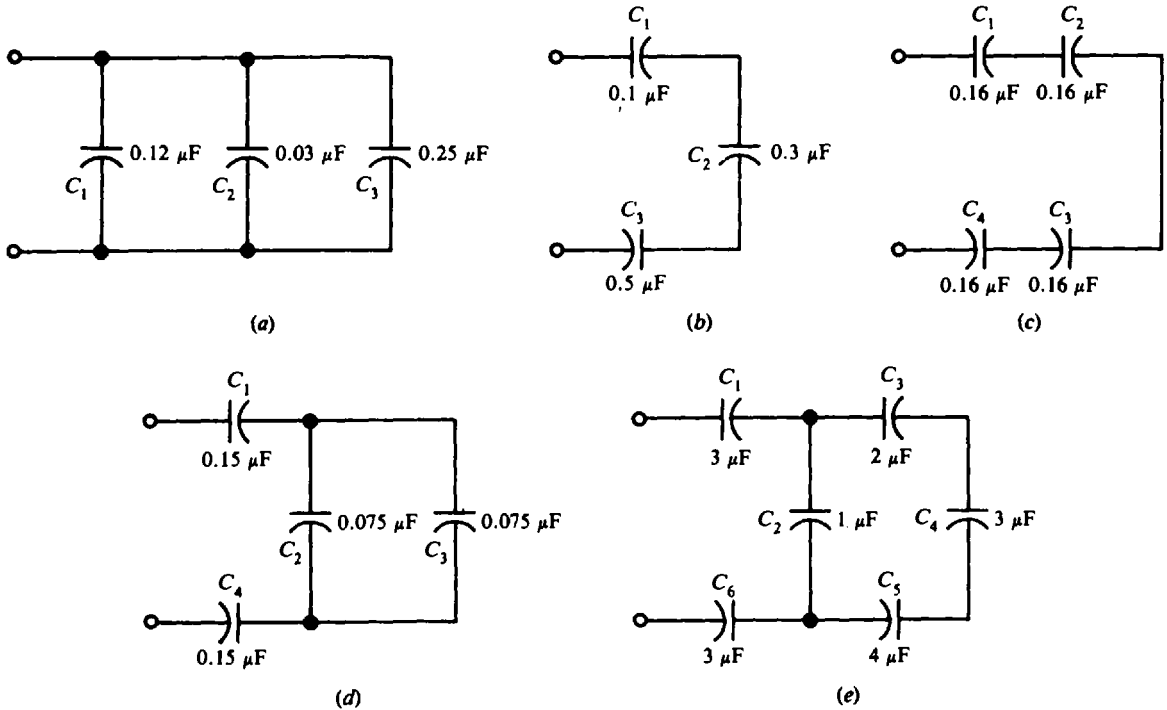


Fig. 13-33

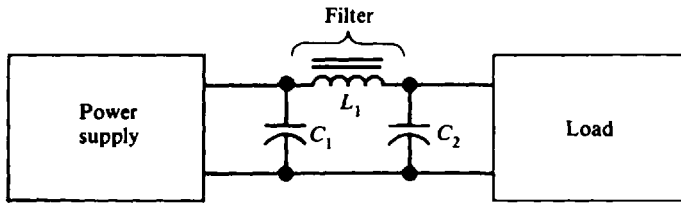


Fig. 13-34

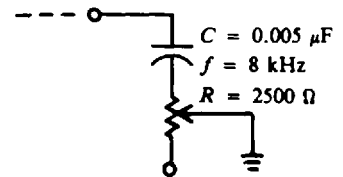


Fig. 13-35

- 13.29** Find the impedance of the output of the tone control circuit (Fig. 13-35).  
*Ans.*  $Z = 4700 \Omega$  ( $X_C = 3980 \Omega$ )
- 13.30** What is the total capacitance of each of the following three capacitors connected in parallel: 300-pF 100-V, 0.001- $\mu$ F 150-V, and 0.003- $\mu$ F 50-V? What is the working voltage of the parallel combination?  
*Ans.*  $C_T = 4300 \text{ pF}$  or  $0.0043 \mu\text{F}$ , 50 V
- 13.31** What capacitance must be added in parallel to a 200-pF capacitor in order to obtain a total capacitance of 1100 pF? *Ans.* 900 pF
- 13.32** Two capacitors are placed in series across the secondary line of a transformer to reduce voltage peaks. What is the total capacitance and what is the working voltage of the pair of 0.008- $\mu$ F 650-V capacitors? *Ans.*  $C_T = 0.004 \mu\text{F}$ , 1300 V
- 13.33** A Colpitts oscillator has two capacitors in series,  $C_1 = 300 \text{ pF}$  and  $C_2 = 300 \text{ pF}$ , and oscillates at a frequency of 100 kHz. What is the total capacitance and what is the reactance?  
*Ans.*  $C_T = 150 \text{ pF}$ ;  $X_C = 10\,600 \Omega$
- 13.34** What is the capacitive reactance between two transmission wires if the stray capacitance between them is 10 pF and one wire carries a radio frequency of 1200 kHz?  
*Ans.*  $X_C = 13\,250 \Omega$  or  $13.25 \text{ k}\Omega$

13.35 Find the indicated quantity.

	$X_C, \Omega$	$f$	$C$	$I_C$	$V_C, V$
(a)	?	120 Hz	$10 \mu F$	25 mA	?
(b)	?	4.2 MHz	?	160 mA	400
(c)	200	600 kHz	?	?	10
(d)	?	800 Hz	$2 \mu F$	?	20
(e)	1000	500 Hz	?	22 mA	?
(f)	?	?	30 pF	20 mA	106
(g)	?	?	$0.01 \mu F$	4 A	3

Ans.

	$X_C, \Omega$	$f$	$C$	$I_C$	$V_C, V$
(a)	133	....	....	....	3.32
(b)	2500	....	15.2 pF	....	....
(c)	....	....	1325 pF	50 mA	....
(d)	99.4	....	....	0.2 A	....
(e)	....	....	$0.318 \mu F$	....	22
(f)	5300	1 MHz	....	....	....
(g)	0.75	21.25 MHz	....	....	....

13.36 Find the impedance of a capacitor if its reactance is  $40 \Omega$  and its resistance is  $20 \Omega$ .

Ans.  $Z = 44.7 \Omega$

13.37 Find the impedance of a capacitive circuit to a 1.5-kHz audio signal if the resistance is  $2000 \Omega$  and the capacitance is  $0.02 \mu F$ . Ans.  $Z = 5670 \Omega$

13.38 What is the impedance of a capacitive circuit to a 20-kHz frequency if its resistance is  $400 \Omega$  and its capacitance is  $0.032 \mu F$ ? Ans.  $Z = 471 \Omega$

13.39 A 120-V 60-Hz ac voltage is impressed across a series circuit of a  $10\text{-}\Omega$  resistor and a capacitor whose reactance is  $15 \Omega$ . Find the impedance, phase angle, line current, voltage drop across the resistor and the capacitor, and power. Draw the phasor diagram.

Ans.  $Z = 18 \Omega$ ;  $\theta = 56.3^\circ$ ,  $I$  leading  $V_T$ ;  $I = 6.67 \text{ A}$ ;  $V_R = 66.7 \text{ V}$ ;  $V_C = 100 \text{ V}$ ;  $P = 444 \text{ W}$ . For the phasor diagram, see Fig. 13-36.

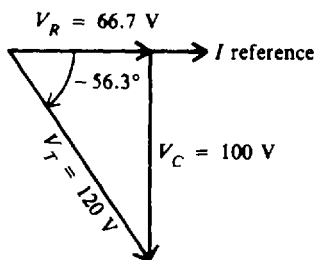


Fig. 13-36

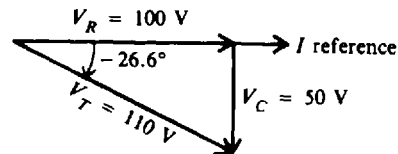


Fig. 13-37

13.40 A 110-V 200-Hz ac voltage is applied across a series circuit of a  $100\text{-}\Omega$  resistor and a  $15.9\text{-}\mu F$  capacitor. Find  $Z$ ,  $\theta$ ,  $I$ ,  $V_R$ ,  $V_C$ , and  $P$ . Draw the phasor diagram.

Ans.  $Z = 122 \Omega$ ;  $\theta = 26.6^\circ$ ,  $I$  leading  $V_T$ ;  $I = 0.982 \text{ A}$ ;  $V_R = 100 \text{ V}$ ;  $V_C = 50 \text{ V}$ ;  $P = 100 \text{ W}$ . For the phasor diagram, see Fig. 13-37.

13.41 A 5-k $\Omega$  resistor and an unknown capacitor are placed in series across a 60-Hz line. If the voltage across the resistor is 30 V and the voltage across the capacitor is 60 V, find the impressed voltage, the current in the resistor, the capacitive reactance, and the capacitance of the capacitor.  
 Ans.  $V_T = 67.1 \text{ V}$ ;  $I = I_R = 6 \text{ mA}$ ;  $X_C = 10 \text{ k}\Omega$ ;  $C = 0.265 \mu\text{F}$

13.42 A circuit consisting of a 30- $\mu\text{F}$  capacitance in series with a rheostat is connected across a 120-V 60-Hz line. What must the value of the resistance be in order to permit a current of 1 A to flow? (Hint: Solve the impedance triangle in Fig. 13-38 for  $R$ .) Ans.  $R = 81.2 \Omega$

13.43 In a resistance-coupled stage (Fig. 13-39), the voltage drop across points A and B is 14.14 V. If the frequency of the current is 1 kHz, find the voltage across the resistor. Draw the phasor diagram.  
 Ans.  $V_R = 10 \text{ V}$ ; for the phasor diagram, see Fig. 13-40.

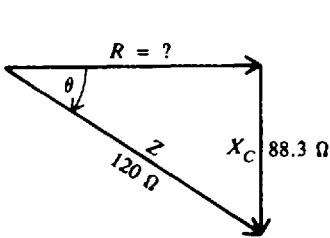


Fig. 13-38

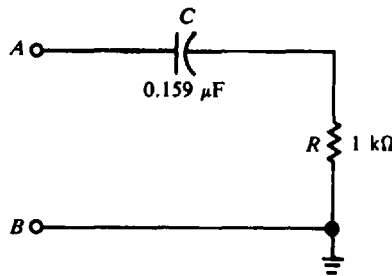


Fig. 13-39

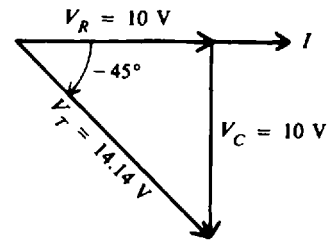


Fig. 13-40

13.44 A 15- $\Omega$  resistor and an 8- $\Omega$  capacitive reactance are placed in parallel across a 120-V ac line. Find the phasor branch currents, total current and phase angle, impedance, and power drawn; and draw the phasor diagram.  
 Ans.  $I_R = 8 \text{ A}$ ;  $I_C = 15 \text{ A}$ ;  $I_T = 17 \text{ A}$ ,  $\theta = 61.9^\circ$ ,  $I_T$  leads  $V_T$ ;  $Z_T = 7.1 \Omega$ ;  $P = 960 \text{ W}$ ; for the phasor diagram, see Fig. 13-41.

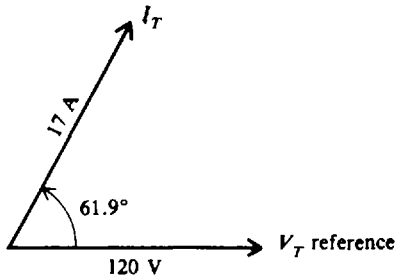


Fig. 13-41

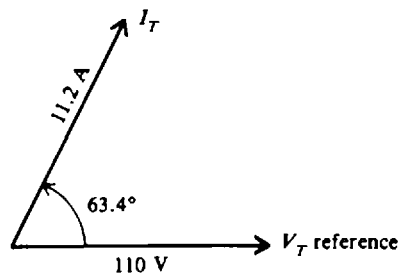


Fig. 13-42

13.45 A 20- $\Omega$  resistor and a 7.95- $\mu\text{F}$  capacitor are connected in parallel across a 100-V 2-kHz source. Find the branch currents, total current and phase angle, impedance, and power drawn; and draw the phasor diagram.  
 Ans.  $I_R = 5 \text{ A}$ ;  $I_C = 10 \text{ A}$ ;  $I_T = 11.2 \text{ A}$ ,  $\theta = 63.4^\circ$ ,  $I_T$  leads  $V_T$ ;  $Z_T = 8.9 \Omega$ ;  $P = 500 \text{ W}$ ; for the phasor diagram, see Fig. 13-42.

13.46 For the low-pass filter circuit (Fig. 13-43), find  $I_C$ ,  $I_R$ ,  $I_T$ , and the percentage of  $I_T$  that passes through the resistor for an audio frequency at 1 kHz and for a radio frequency at 2 MHz.  
 Ans. AF case:  $I_C = 0.5 \text{ mA}$ ;  $I_R = 19.9 \text{ mA}$ ;  $I_T = 19.9 \text{ mA}$ ; 100 percent; RF case:  $I_C = 1 \text{ A}$ ;  $I_R = 19.9 \text{ mA}$ ;  $I_T = 1.002 \text{ A}$ ; 2 percent

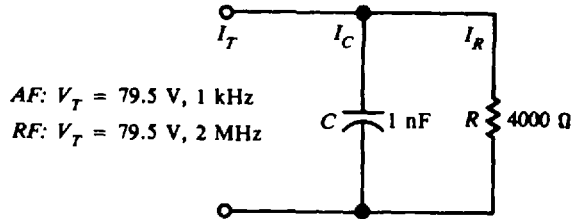


Fig. 13-43

13.47 Find the indicated values for an RC parallel circuit.

	$V_T, \text{V}$	$R$	$X_C$	$I_R$	$I_C$	$I_T$	$Z_T$	$\theta^\circ$	$P, \text{W}$
(a)	120	120 $\Omega$	60 $\Omega$	?	?	?	?	?	?
(b)	8	4 k $\Omega$	8 k $\Omega$	?	?	?	?	?	?
(c)	20	40 $\Omega$	40 $\Omega$	?	?	?	?	?	?

Ans.

	$V_T, \text{V}$	$R$	$X_C$	$I_R$	$I_C$	$I_T$	$Z_T$	$\theta^\circ$	$P, \text{W}$
(a)	....	....	....	1 A	2 A	2.24 A	54.5 $\Omega$	63.4	120
(b)	....	....	....	2 mA	1 mA	2.24 mA	3.57 k $\Omega$	26.6	0.016
(c)	....	....	....	0.5 A	0.5 A	0.707 A	28.2 $\Omega$	45	10

## Single-Phase Circuits

### THE GENERAL RLC CIRCUIT

The preceding two chapters have explained how a combination of inductance and resistance and then capacitance and resistance behave in a series circuit and in a parallel circuit. We saw how the  $RL$  and  $RC$  combination affect the current, voltages, power, power factor, and phase angle of a circuit. In this chapter all three fundamental circuit parameters—inductance, capacitance, and resistance—are combined and their effect on circuit values studied.

### RLC IN SERIES

Current in a series circuit containing resistance, inductive reactance, and capacitive reactance (Fig. 14-1a) is determined by the total impedance of the combination. The current  $I$  is the same in  $R$ ,  $X_L$ , and  $X_C$  since they are in series. The voltage drop across each element is found by Ohm's law:

$$V_R = IR \quad V_L = IX_L \quad V_C = IX_C$$

where  $V_R$  = voltage drop across the resistance, V  
 $V_L$  = voltage drop across the inductance, V  
 $V_C$  = voltage drop across the capacitance, V

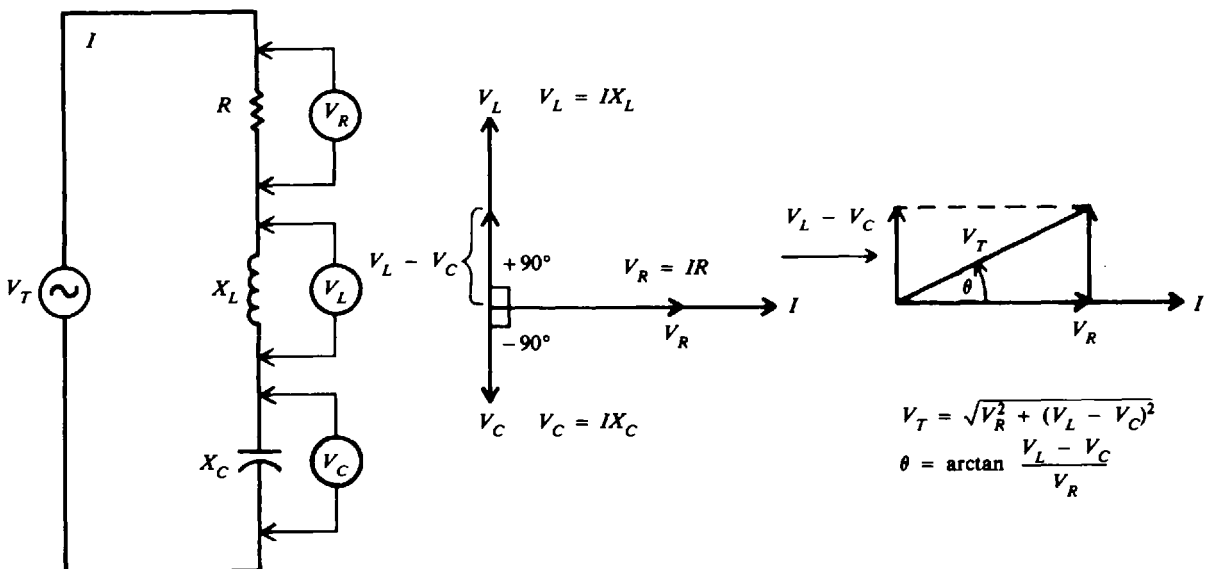
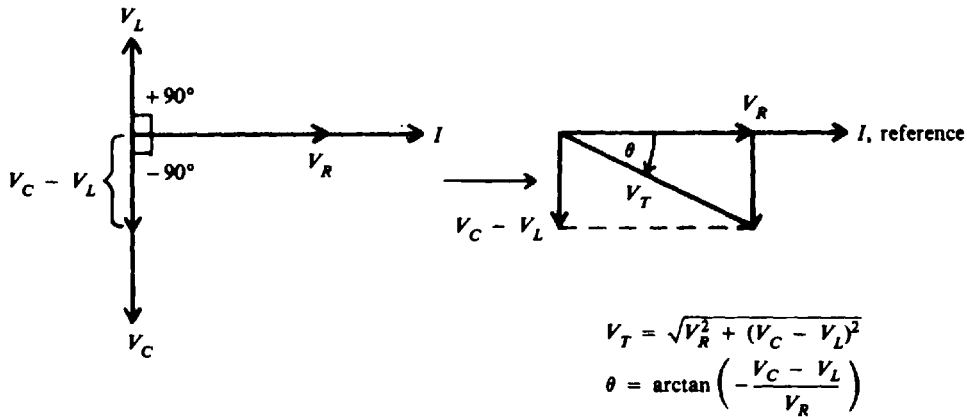


Fig. 14-1  $R$ ,  $X_L$ , and  $X_C$  in series;  $X_L > X_C$  for inductive circuit

The voltage drop across the resistance is in phase with the current through the resistance (Fig. 14-1b). The voltage across the inductance leads the current through the inductance by  $90^\circ$ . The voltage across the capacitance lags the current through the capacitance by  $90^\circ$  (Fig. 14-1b). Since  $V_L$  and  $V_C$  are exactly  $180^\circ$  out of phase and acting in exactly opposite directions, they are added algebraically. When  $X_L$  is greater than  $X_C$ , the circuit is inductive,  $V_L$  is greater than  $V_C$ , and  $I$  lags  $V_T$  (Fig. 14-1c).

When  $X_C$  is greater than  $X_L$ , the circuit is capacitive. Now  $V_C$  is greater than  $V_L$  so that  $I$  leads  $V_T$  (Fig. 14-2).

(a) Phasor diagram,  $V_C > V_L$ (b) Voltage-phasor triangle,  $V_C > V_L$ **Fig. 14-2**  $R$ ,  $X_L$ , and  $X_C$  in series;  $X_C > X_L$  for capacitive circuit

When  $X_L > X_C$ , the voltage-phasor diagram (Fig. 14-1c) shows that the total voltage  $V_T$  and phase angle are as follows:

$$V_T = \sqrt{V_R^2 + (V_L - V_C)^2} \quad (14-1)$$

$$\theta = \arctan \frac{V_L - V_C}{V_R} \quad (14-2)$$

When  $X_C > X_L$  (Fig. 14-2b),

$$V_T = \sqrt{V_R^2 + (V_C - V_L)^2} \quad (14-3)$$

$$\theta = \arctan \left( -\frac{V_C - V_L}{V_R} \right) \quad (14-4)$$

where  $V_T$  = applied voltage, V  
 $V_R$  = voltage drop across the resistance, V  
 $V_L$  = voltage drop across the inductance, V  
 $V_C$  = voltage drop across the capacitance, V  
 $\theta$  = phase angle between  $V_T$  and  $I$ , degrees

**Example 14.1** In a  $RLC$  series ac circuit (Fig. 14-3a), find the applied voltage and phase angle. Draw the voltage-phasor diagram.

By Ohm's law,

$$V_R = IR = 2(4) = 8 \text{ V} \quad V_L = IX_L = 2(19.5) = 39 \text{ V} \quad V_C = IX_C = 2(12) = 24 \text{ V}$$

With  $V_L > V_C$ ,

$$V_T = \sqrt{V_R^2 + (V_L - V_C)^2} = \sqrt{8^2 + (39 - 24)^2} = \sqrt{8^2 + 15^2} = 17 \text{ V} \quad \text{Ans.} \quad (14-1)$$

$$\theta = \arctan \frac{V_L - V_C}{V_R} \quad (14-2)$$

$$= \arctan \frac{39 - 24}{8} = \arctan \frac{15}{8} = \arctan 1.88 = 61.9^\circ \quad I \text{ lags } V_T \quad \text{Ans.}$$

For the phasor diagram, see Fig. 14-3b.

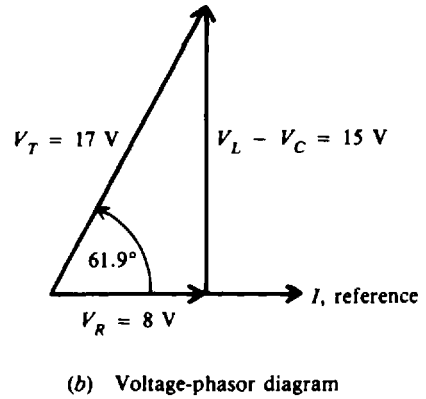
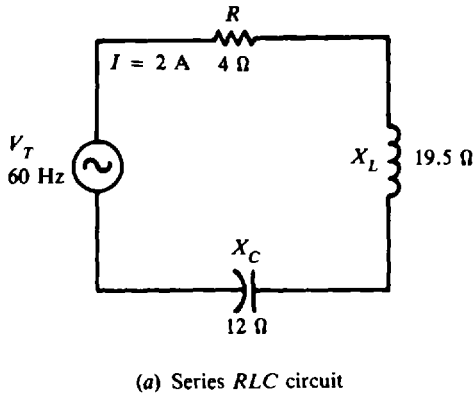


Fig. 14-3

**Impedance in Series RLC**

Impedance  $Z$  is equal to the phasor sum of  $R$ ,  $X_L$ , and  $X_C$ . In Fig. 14-4a:

When  $X_L > X_C$ , 
$$Z = \sqrt{R^2 + (X_L - X_C)^2} \tag{14-5}$$

In Fig. 14-4b:

When  $X_C > X_L$ , 
$$Z = \sqrt{R^2 + (X_C - X_L)^2} \tag{14-6}$$

It is convenient to define net reactance  $X$  as

$$X = X_L - X_C \tag{14-7}$$

Then, from Eqs. (14-5) and (14-6),

$$Z = \sqrt{R^2 + X^2} \tag{14-8}$$

for both inductive and capacitive RLC series circuits (Fig. 14-4).

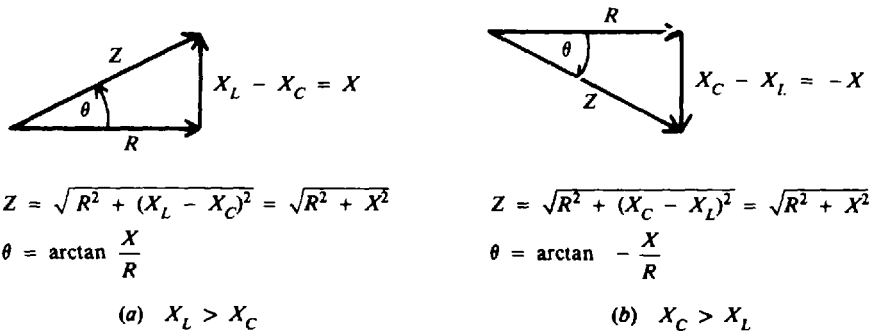


Fig. 14-4 Series RLC impedance-phasor triangle

**Example 14.2** Find the impedance of the series RLC circuit in Example 14.1

$$Z = \sqrt{R^2 + X^2} \tag{14-8}$$

$$X = X_L - X_C = 19.5 - 12 = 7.5 \Omega$$

Then

$$Z = \sqrt{4^2 + (7.5)^2} = 8.5 \Omega \quad \text{Ans.}$$

Or, more simply, by Ohm's law,

$$Z = \frac{V_T}{I} = \frac{17}{2} = 8.5 \Omega \quad \text{Ans.}$$



**Example 14.3** When inductive reactance  $X_L$  and capacitive reactance  $X_C$  are exactly equal in a series RLC circuit, a condition called *series resonance* exists. If in a series circuit  $R = 4 \Omega$  and  $X_L = X_C = 19.5 \Omega$ , find  $Z$  and  $V_T$ .

$$Z = \sqrt{R^2 + X^2} \tag{14-8}$$

$$X = X_L - X_C = 19.5 - 19.5 = 0$$


Then  $Z = \sqrt{R^2} = R = 4 \Omega$       *Ans.*

So  $V_T = IZ = IR = 2(4) = 8 \text{ V}$       *Ans.*

Note that in series resonance, the impedance of the circuit is equal to the resistance of the circuit. This is the minimum value of impedance for the circuit. Therefore at resonance, the highest current will flow.

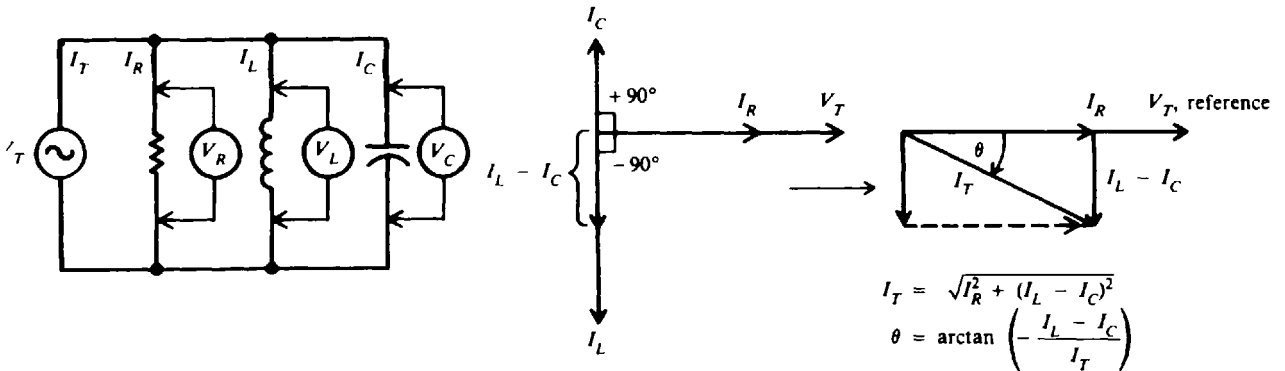**RLC IN PARALLEL**


A three-branch parallel ac circuit (Fig. 14-5a) has resistance in one branch, inductance in the second branch, and capacitance in the third branch. The voltage is the same across each parallel branch, so  $V_T = V_R = V_L = V_C$ . The applied voltage  $V_T$  is used as the reference line to measure phase angle  $\theta$ . The total current  $I_T$  is the phasor sum of  $I_R$ ,  $I_L$ , and  $I_C$ . The current in the resistance  $I_R$  is in phase with the applied voltage  $V_T$  (Fig. 14-5b). The current in the inductance  $I_L$  lags the voltage  $V_T$  by  $90^\circ$ . The current in the capacitor  $I_C$  leads the voltage  $V_T$  by  $90^\circ$ .  $I_L$  and  $I_C$  are exactly  $180^\circ$  out of phase and thus acting in opposite directions (Fig. 14-5b). When  $I_L > I_C$ ,  $I_T$  lags  $V_T$  (Fig. 14-5c) so the parallel RLC circuit is considered inductive.



(a) Parallel RLC circuit diagram      (b) Phasor diagram,  $I_L > I_C$       (c) Current-phasor triangle,  $I_L > I_C$

**Fig. 14-5**  $R$ ,  $X_L$ , and  $X_C$  in parallel;  $I_L > I_C$  for inductive circuit

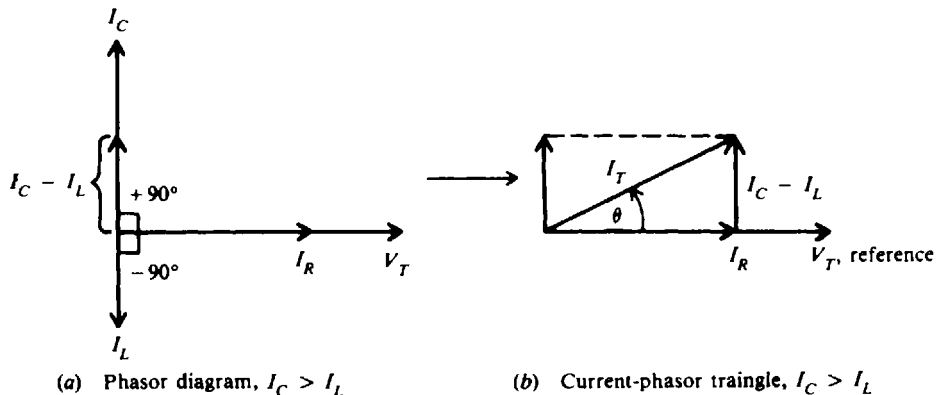If  $I_C > I_L$ , the current relationships and phasor triangle (Fig. 14-6) show that  $I_T$  now leads  $V_T$  so this type of parallel RLC circuit is considered capacitive.



(a) Phasor diagram,  $I_C > I_L$       (b) Current-phasor triangle,  $I_C > I_L$

**Fig. 14-6**  $R$ ,  $X_L$ , and  $X_C$  in parallel;  $I_C > I_L$  for capacitive circuit

When  $I_L > I_C$ , the circuit is inductive and

$$I_T = \sqrt{I_R^2 + (I_L - I_C)^2} \tag{14-9}$$

$$\theta = \arctan \left( -\frac{I_L - I_C}{I_R} \right) \tag{14-10}$$

and when  $I_C > I_L$ , the circuit is capacitive and

$$I_T = \sqrt{I_R^2 + (I_C - I_L)^2} \tag{14-11}$$

$$\theta = \arctan \frac{I_C - I_L}{I_R} \tag{14-12}$$

In a parallel *RLC* circuit, when  $X_L > X_C$ , the capacitive current will be greater than the inductive current and the circuit is capacitive. When  $X_C > X_L$ , the inductive current is greater than the capacitive current and the circuit is inductive. These relationships are opposite to those for a series *RLC* circuit.

**Impedance in Parallel *RLC***

The total impedance  $Z_T$  of a parallel *RLC* circuit equals the total voltage  $V_T$  divided by the total current  $I_T$ .

$$Z_T = \frac{V_T}{I_T} \tag{14-13}$$

**Example 14.4** A 400-Ω resistor, a 50-Ω inductive reactance, and a 40-Ω capacitive reactance are placed in parallel across a 120-V ac line (Fig. 14-7a). Find the phasor branch currents, total current, phase angle, and impedance. Draw the phasor diagram.

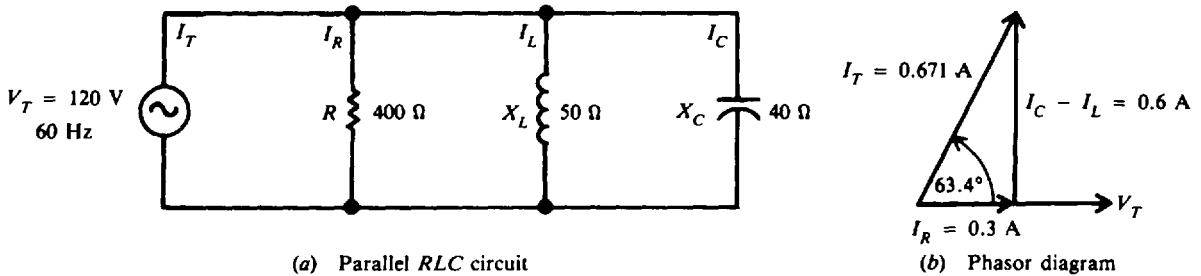


Fig. 14-7

**Step 1.** Find  $I_R, I_L, I_C$ .

$$I_R = \frac{V_T}{R} = \frac{120}{400} = 0.3 \text{ A} \quad \text{Ans.}$$

$$I_L = \frac{V_T}{X_L} = \frac{120}{50} = 2.4 \text{ A} \quad \text{Ans.}$$

$$I_C = \frac{V_T}{X_C} = \frac{120}{40} = 3.0 \text{ A} \quad \text{Ans.}$$

**Step 2.** Find  $I_T, \theta$ . Since  $X_L > X_C$  (50 Ω > 40 Ω) or  $I_C > I_L$  (3.0 A > 2.4 A), the circuit is capacitive.

$$I_T = \sqrt{I_R^2 + (I_C - I_L)^2} \tag{14-11}$$

$$= \sqrt{(0.3)^2 + (3.0 - 2.4)^2} = \sqrt{(0.3)^2 + (0.6)^2} = 0.671 \text{ A} \quad \text{Ans.}$$

$$\theta = \arctan \frac{I_C - I_L}{I_R} \tag{14-12}$$

$$= \arctan \frac{3.0 - 2.4}{0.3} = \arctan \frac{0.6}{0.3} = \arctan 2 = 63.4^\circ \quad I_T \text{ leads } V_T \quad \text{Ans.}$$

Step 3. Find  $Z_T$ , using Eq. (14-13)

$$Z_T = \frac{V_T}{I_T} = \frac{120}{0.671} = 179 \Omega \quad \text{Ans.}$$

Step 4. Draw the phasor diagram (Fig. 14-7b).

**Example 14.5** A parallel  $RLC$  circuit in which  $X_L = X_C$  is said to be in *parallel resonance*. Since  $X_L$  and  $X_C$  are dependent upon the values of  $L$ ,  $C$ , and frequency  $f$ , parallel resonance (that is,  $X_L = X_C$ ) can be obtained by choosing the proper values of  $L$  and  $C$  for a given frequency. If the values of  $L$  and  $C$  are already given, then the frequency can be varied until  $X_L = X_C$ . If in Example 14.4,  $X_L = X_C = 40 \Omega$ , find the values of the same quantities as in that example.

Step 1. Find  $I_R$ ,  $I_L$ ,  $I_C$ .

$$I_R = \frac{V_T}{R} = \frac{120}{400} = 0.3 \text{ A} \quad \text{Ans.}$$

$$I_L = I_C = \frac{V_T}{X_L} = \frac{120}{40} = 3 \text{ A} \quad \text{Ans.}$$

Step 2. Find  $I_T$ ,  $\theta$ . Since  $I_L$  and  $I_C$  are equal and opposite in phase,

$$\begin{aligned} I_T &= \sqrt{I_R^2 + (I_C - I_L)^2} & (14-11) \\ &= \sqrt{I_R^2} = I_R = 0.3 \text{ A} & \text{Ans.} \end{aligned}$$

Note that only 0.3 A comes from the source though the reactive branch currents are each 3 A. At resonance these currents are equal and opposite so that they cancel each other.


$$\theta = \arctan \frac{I_L - I_C}{I_T} \quad (14-12)$$

$$= \arctan \frac{0}{I_T} = \arctan 0 = 0^\circ \quad I_T \text{ in phase with } V_T \quad \text{Ans.}$$

Step 3. Find  $Z_T$ , using Eq. (14-13).

$$Z_T = \frac{V_T}{I_T} = \frac{120}{0.3} = 400 \Omega \quad \text{Ans.}$$

Step 4. Draw the phasor diagram.

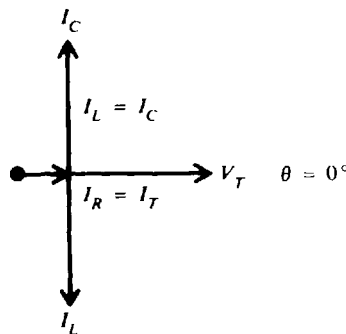

Note that a parallel resonant circuit reduces to a resistive circuit ( $\theta = 0^\circ$ ). Because  $I_L$  and  $I_C$  cancel each other, the current  $I_T$  is a minimum so impedance  $Z_T$  is a maximum.

## RL AND RC BRANCHES IN PARALLEL

Total current  $I_T$  for a circuit containing parallel branches of  $RL$  and  $RC$  (Fig. 14-8) is the phasor sum of the branch currents  $I_1$  and  $I_2$ . A convenient way to find  $I_T$  is to (1) add algebraically

the horizontal components of  $I_1$  and  $I_2$  with respect to the phasor reference  $V_T$ , (2) add algebraically the vertical components of  $I_1$  and  $I_2$ , and (3) form a right triangle with these two sums as legs and calculate the value of the hypotenuse ( $I_T$ ) and its angle to the horizontal.

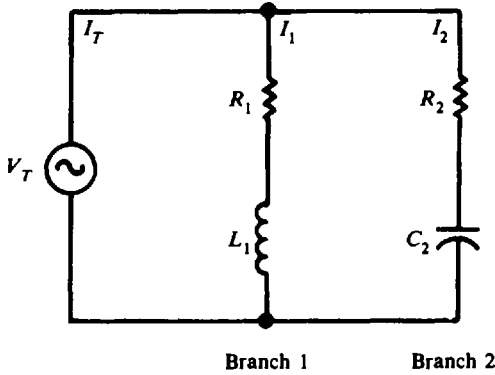


Fig. 14-8 Parallel  $RL$  and  $RC$  branches

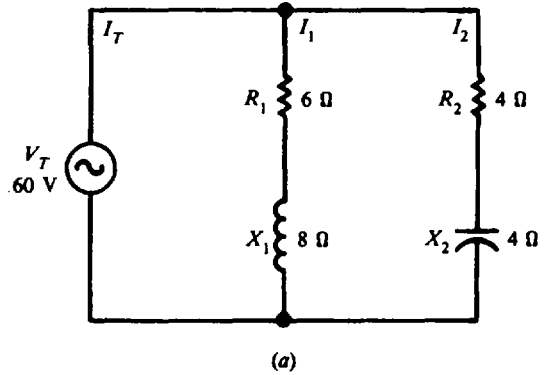


Fig. 14-9a

**Example 14.6** An ac circuit has a  $RL$  branch parallel to a  $RC$  branch (Fig. 14-9a). Find the total current, phase angle, and impedance of this circuit.

**Step 1.** For the  $RL$  branch, find  $Z_1$ ,  $\theta_1$ , and  $I_1$ .


$$Z_1 = \sqrt{R_1^2 + X_1^2} = \sqrt{6^2 + 8^2} = 10 \Omega \quad \theta_1 = \arctan \frac{X_1}{R_1} = \arctan \frac{8}{6} = 53.1^\circ$$

$$I_1 = \frac{V_T}{Z_1} = \frac{60}{10} = 6 \text{ A}$$


$I_1$  lags  $V_T$  in the  $RL$  branch (inductive circuit) by  $53.1^\circ$ . Resolve  $I_1$  into its horizontal and vertical components with respect to  $V_T$  (Fig. 14-9b).

Horizontal component:  $I_1 \cos \theta_1 = 6 \cos (-53.1^\circ) = 3.6 \text{ A}$

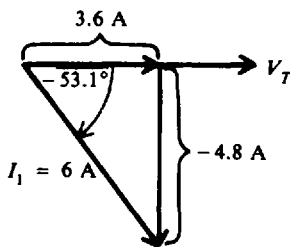Vertical component:  $I_1 \sin \theta_1 = 6 \sin (-53.1^\circ) = -4.8 \text{ A}$



(b)

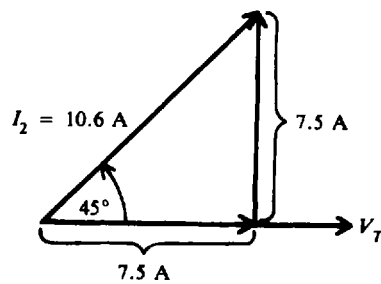

(c)

Fig. 14-9b, c

**Step 2.** For the  $RC$  branch, find  $Z_2$ ,  $\theta_2$ , and  $I_2$ .

$$Z_2 = \sqrt{R_2^2 + X_2^2} = \sqrt{4^2 + 4^2} = 5.66 \Omega \quad \theta_2 = \arctan \left( -\frac{X_2}{R_2} \right) = \arctan -\frac{4}{4} = \arctan -1 = -45^\circ$$

$$I_2 = \frac{V_T}{Z_2} = \frac{60}{5.66} = 10.6 \text{ A}$$

$I_2$  leads  $V_T$  in the RC branch (capacitive circuit) by  $45^\circ$ . Resolve  $I_2$  into its horizontal and vertical components with respect to  $V_T$  (Fig. 14-9c).

Horizontal component:  $I_2 \cos \theta_2 = 10.6 \cos 45^\circ = 7.5 \text{ A}$

Vertical component:  $I_2 \sin \theta_2 = 10.6 \sin 45^\circ = 7.5 \text{ A}$

**Step 3.** Find  $I_T$ .  $I_T$  is the phasor sum of  $I_1$  and  $I_2$ . Add the horizontal components of  $I_1$  and  $I_2$ .

$$3.6 + 7.5 = 11.1 \text{ A}$$

Add the vertical components of  $I_1$  and  $I_2$ .

$$-4.8 + 7.5 = 2.7 \text{ A}$$

The resultant phasor is  $I_T$  (Fig. 14-9d).

$$I_T = \sqrt{(11.1)^2 + (2.7)^2} = \sqrt{130.5} = 11.4 \text{ A}$$

$$\theta = \arctan \frac{2.7}{11.1} = \arctan 0.243 = 13.7^\circ$$

$$Z_T = \frac{V_T}{I_T} = \frac{60}{11.4} = 5.26 \Omega \quad \text{Ans.}$$

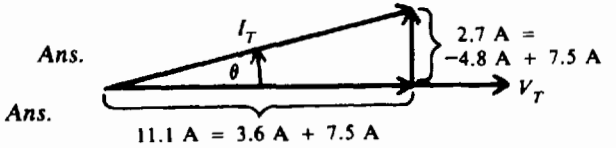


Fig. 14-9d

Note that  $I_T$  leads  $V_T$  (Fig. 14-9d) so that the circuit is leading and thus capacitive.

**POWER AND POWER FACTOR**

The instantaneous power  $p$  is the product of the current  $i$  and the voltage  $v$  at that instant of time  $t$ .

$$p = vi \quad (14-14)$$

When  $v$  and  $i$  are both positive or both negative, their product  $p$  is positive. Therefore, power is being expended throughout the cycle (Fig. 14-10). If  $v$  is negative while  $i$  is positive during any part of the cycle (Fig. 14-11), or if  $i$  is negative while  $v$  is positive, their product will be negative. This "negative power" is not available for work; it is power returned to the line.

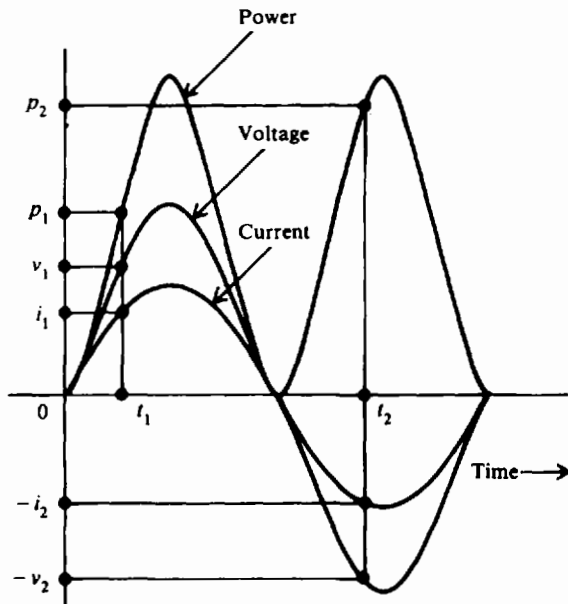


Fig. 14-10 Power-time diagram when voltage and current are in phase

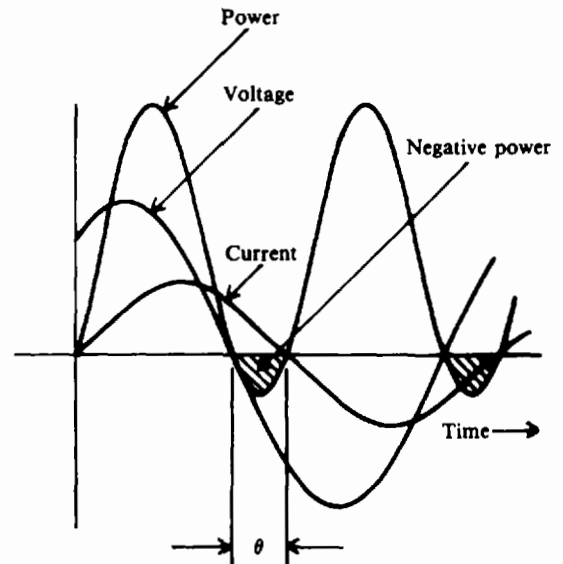


Fig. 14-11 Power-time diagram in series RL circuit where current lags voltage by phase angle  $\theta$

The product of the voltage across the resistance and the current through the resistance is always positive and is called *real power*. Real power can be considered as resistive power that is dissipated as heat. Since the voltage across a reactance is always 90° out of phase with the current through the reactance, the product  $p_x = v_x i_x$  is always negative. This product is called *reactive power* and is due to the reactance of a circuit. Similarly, the product of the line voltage and the line current is known as *apparent power*.

Real power, reactive power, and apparent power can be represented by a right triangle (Fig. 14-12a). From this triangle the power formulas are:

$$\text{Real power } P = V_R I_R = VI \cos \theta, \text{ W} \tag{14-15}$$

or

$$P = I^2 R, \text{ W} \tag{14-16}$$

$$P = \frac{V^2}{R}, \text{ W} \tag{14-17}$$

$$\text{Reactive power } Q = V_X I_X = VI \sin \theta, \text{ VAR} \tag{14-18}$$

$$\text{Apparent power } S = VI, \text{ VA} \tag{14-19}$$

With line voltage  $V$  as reference phasor, in an inductive circuit,  $S$  lags  $P$  (Fig. 14-12b); while in a capacitive circuit,  $S$  leads  $P$  (Fig. 14-12c).

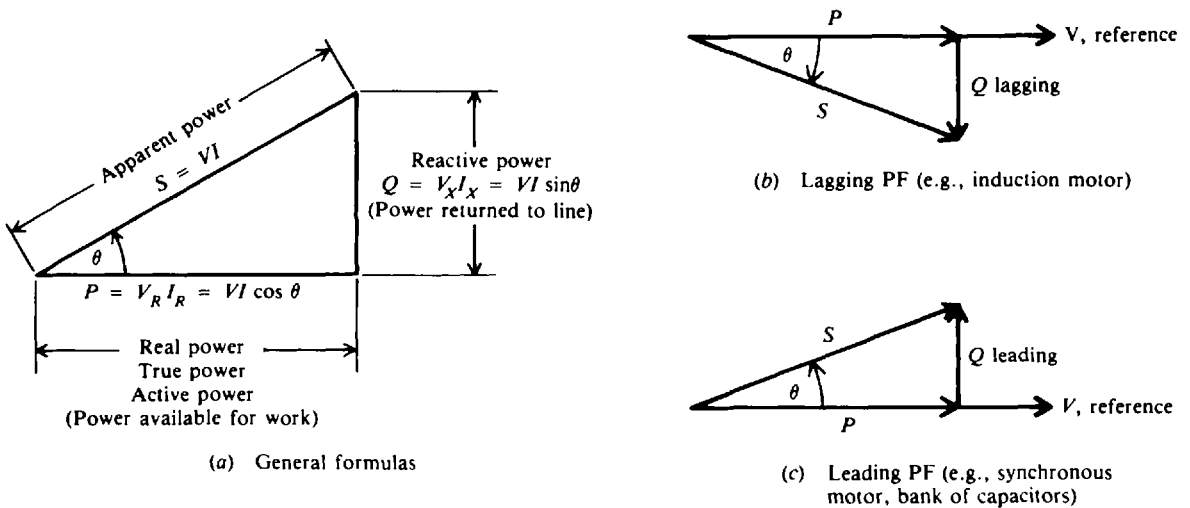


Fig. 14-12 Power triangle

The ratio of real power to apparent power, called the *power factor (PF)*, is

$$\text{PF} = \frac{\text{real power}}{\text{apparent power}} = \frac{V_R I_R}{VI} = \frac{VI \cos \theta}{VI} = \cos \theta \tag{14-20}$$

Also from Eq. (14-15),

$$\text{PF} = \cos \theta = \frac{P}{VI} \tag{14-21}$$

The  $\cos \theta$  of a circuit is the power factor, PF, of the circuit. The power factor determines what portion of the apparent power is real power and can vary from 1 when the phase angle  $\theta$  is 0°, to 0 when  $\theta$  is 90°. When  $\theta = 0^\circ$ ,  $P = VI$ , the formula for voltage and current of a circuit in phase. When  $\theta = 90^\circ$ ,  $P = VI \times 0 = 0$ , indicating that no power is being expended or consumed.

A circuit in which the current lags the voltage (i.e., an inductive circuit) is said to have a *lagging* PF (Fig. 14-12*b*); a circuit in which the current leads the voltage (i.e., a capacitive circuit) is said to have a *leading* PF.

Power factor is expressed as a decimal or as a percentage. A power factor of 0.7 is the same as a power factor of 70 percent. At unity (PF = 1, or 100 percent), the current and voltage are in phase. A 70 percent PF means that the device uses only 70 percent of the voltampere input. It is desirable to design circuits that have a high PF since such circuits make the most efficient use of the current delivered to the load.

When we state that a motor draws 10 kVA (1 kVA = 1000 VA) from a power line, we recognize that this is the apparent power taken by the motor. Kilovoltamperes always refers to the apparent power. Similarly, when we say a motor draws 10 kW, we mean that the real power taken by the motor is 10 kW.

**Example 14.7** A current of 7 A lags a voltage of 220 V by 30°. What is the PF and real power taken by the load?

$$\begin{aligned} \text{PF} &= \cos \theta & (14-20) \\ &= \cos 30^\circ = 0.866 & \text{Ans.} \end{aligned}$$

$$\begin{aligned} P &= VI \cos \theta & (14-15) \\ &= 220(7)(0.866) = 1334 \text{ W} & \text{Ans.} \end{aligned}$$

**Example 14.8** A motor rated at 240 V, 8 A draws 1536 W at full load. What is its PF?  
Use Eq. (14-21).

$$\text{PF} = \frac{P}{VI} = \frac{1536}{240(8)} = 0.8 \quad \text{or} \quad 80\% \quad \text{Ans.}$$

**Example 14.9** In the RLC series ac circuit shown in Fig. 14-3*a*, the line current of 2 A lags the applied voltage of 17 V by 61.9°. Find PF, P, Q, and S. Draw the power triangle.

$$\begin{aligned} \text{PF} &= \cos \theta & (14-20) \\ &= \cos 61.9^\circ = 0.471 \quad \text{or} \quad 47.1\% \text{ lagging} & \text{Ans.} \end{aligned}$$


$$\begin{aligned} P &= VI \cos \theta & (14-15) \\ &= 17(2)(0.471) = 16 \text{ W} & \text{Ans.} \end{aligned}$$

or

$$\begin{aligned} P &= I^2 R & (14-16) \\ &= 2^2(4) = 16 \text{ W} & \text{Ans.} \end{aligned}$$

$$\begin{aligned} Q &= VI \sin \theta & (14-18) \\ &= 17(2)(\sin 61.9^\circ) = 17(2)(0.882) = 30 \text{ VAR lagging} & \text{Ans.} \end{aligned}$$
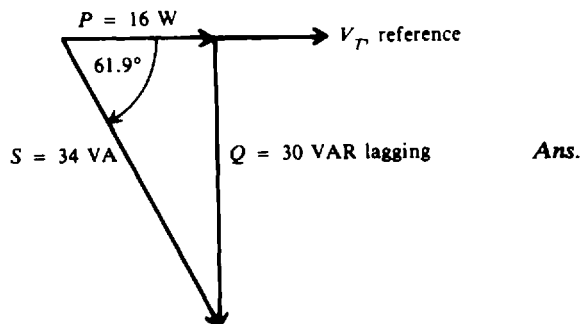
$$\begin{aligned} S &= VI & (14-19) \\ &= 17(2) = 34 \text{ VA} & \text{Ans.} \end{aligned}$$




**Power Factor Correction**


In order to make the most efficient use of the current delivered to a load, we desire a high PF or a PF that approaches unity. A low PF is generally due to the large inductive loads, such as induction motors, which take a lagging current. In order to correct this low PF, it is necessary to bring the current as closely in phase with the voltage as possible. That is, the phase angle  $\theta$  is made as small as possible. This is usually done by placing a capacitive load, which produces a leading current, in parallel with the inductive load.

**Example 14.10** With the use of a phasor diagram show how the PF produced by an inductive motor can be corrected to unity.

We show an induction motor circuit (Fig. 14-13a) and its current-phasor diagram (Fig. 14-13b). Current  $I$  lags the voltage  $V$  by angle  $\theta$  where  $PF = \cos \theta = 0.7$ . We desire to raise the PF to 1.0. We do this by connecting a capacitor across the motor (Fig. 14-14a). If the capacitor current is equal to the inductive current, the two cancel one another (Fig. 14-14b). The line current  $I_1$  is now less than its original value and in phase with  $V$  so that  $PF = \cos 0^\circ = 1$ . Notice that the current through the motor  $I$  remains unchanged. The reactive part of the current to the motor is being supplied by the capacitor. The line now has only to supply the component of current for the resistive part of the motor load.

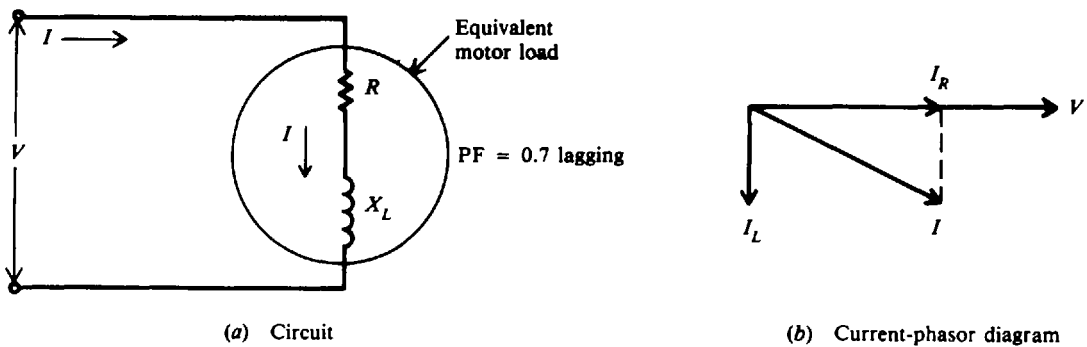

**Fig. 14-13** An induction motor represented by a series  $RL$  circuit

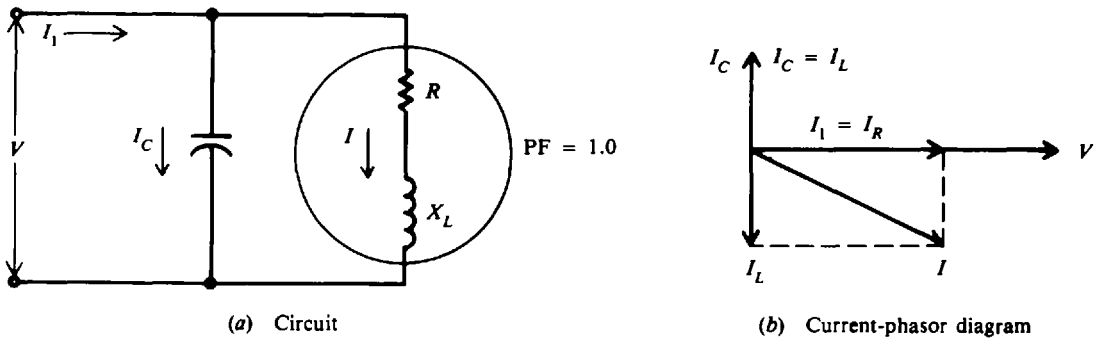

**Fig. 14-14** Induction motor with parallel capacitor added

**Example 14.11** An induction motor draws 1.5 kW and 7.5 A from a 220-V 60-Hz line. What must be the capacitance of a capacitor in parallel in order to raise the total PF to unity (Fig. 14-15a)?

**Step 1.** Find phase angle  $\theta_M$  and then the reactive power  $Q_M$  of the motor load.

$$P_M = V_M I_M \cos \theta_M \tag{14-15}$$

from which


$$\cos \theta_m = \frac{P_M}{V_M I_M} = \frac{1500}{220(7.5)} = 0.909$$

$$\theta_M = \arccos 0.909 = 24.6^\circ$$




From the motor power triangle (Fig. 14-15*b*),
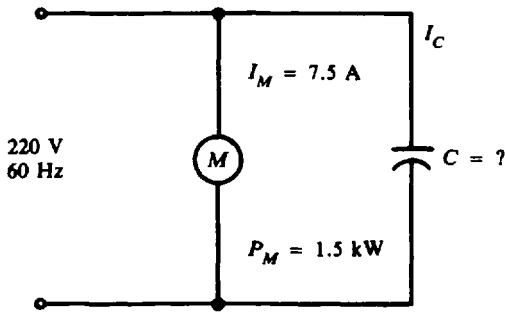
$$Q_M = 1500 \tan 24.6^\circ = 687 \text{ VAR lagging}$$



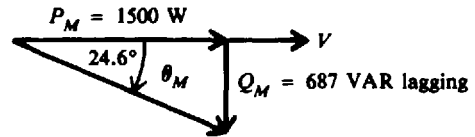(a) Adding parallel capacitor to raise PF to 1



(b)

Fig. 14-15

**Step 2.** Find the current  $I_C$  drawn by the capacitor. For the current to have PF = 1, the capacitor must have a  $Q_C = 687 \text{ VAR}$  leading to balance the  $Q_M = 687 \text{ VAR}$  lagging. Since reactive power in a pure capacitor is also its apparent power,

$$Q_C = S_C = V_C I_C \tag{14-18}$$

$$I_C = \frac{S_C}{V_C} = \frac{687}{220} = 3.12 \text{ A}$$

**Step 3.** Find the reactance of the capacitor.

$$X_C = \frac{V_C}{I_C} = \frac{220}{3.12} = 70.5 \Omega$$

**Step 4.** Find the capacitance of the capacitor, using Eq. (13-9).

$$C = \frac{0.159}{fX_C} = \frac{0.159}{60(70.5)} = 37.6 \times 10^{-6} = 37.6 \mu\text{F} \quad \text{Ans.}$$


**Example 14.12** An induction motor takes 15 kVA at 440 V and 75 percent PF lagging. What must be the PF of a 10-kVA capacitive load connected in parallel in order to raise the total PF to unity?

**Step 1.** Find the reactive power of the induction motor,  $Q_M$ .

$$\text{PF}_M = \cos \theta = 0.75$$

$$\theta = \arccos 0.75 = 41.4^\circ$$
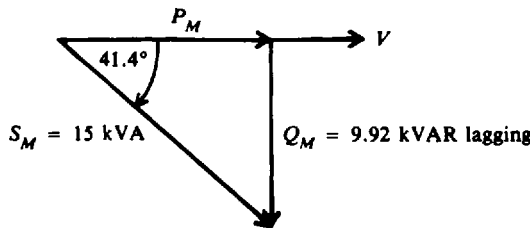
$$Q_M = VI \sin \theta = 15 \sin 41.4^\circ = 9.92 \text{ kVAR lagging}$$




Induction motor

**Step 2.** Find the phase angle and then the PF for the capacitive load. To have a circuit with PF = 1, the total reactive power must equal zero. Since the motor uses 9.92 kVAR lagging, the leading PF load must also use 9.92 kVAR. From the power triangle for leading load,

$$\sin \theta = \frac{Q_S}{S_S} = \frac{9.92}{10} = 0.992$$


$$\theta = \arcsin 0.992 = 82.7^\circ$$
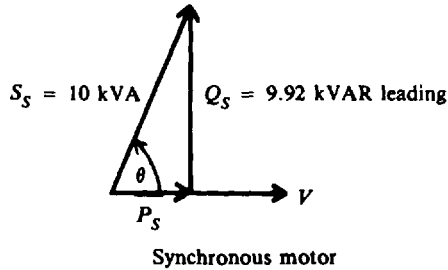
$$\text{PF} = \cos \theta = \cos 82.7^\circ = 0.127 = 12.7\% \text{ leading} \quad \text{Ans.}$$




### Solved Problems

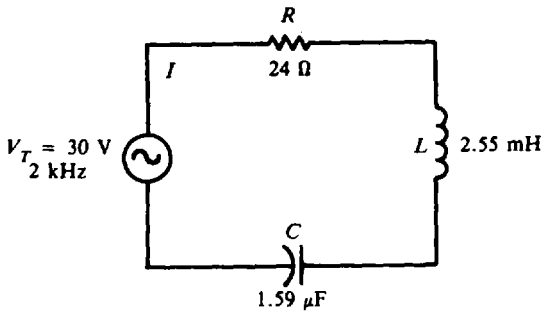**14.1** For the *RLC* series circuit (Fig. 14-16a), find  $X_L$ ,  $X_C$ ,  $Z$ ,  $I$ ,  $V_R$ ,  $V_L$ ,  $V_C$ ,  $P$ , and PF. Draw the voltage-phasor diagram.



(a) Series *RLC* circuit

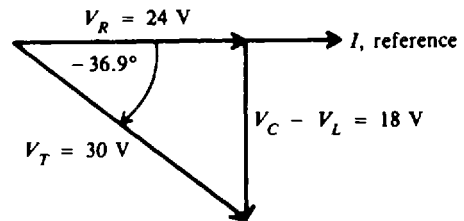

(b)

Fig. 14-16

**Step 1.** Find  $X_L$ ,  $X_C$ , and then  $Z$ .

$$X_L = 6.28 fL \tag{12-4}$$

$$= 6.28(2 \times 10^3)(2.55 \times 10^{-3}) = 32 \Omega \quad \text{Ans.}$$

$$X_C = \frac{0.159}{fC} \tag{13-8}$$

$$= \frac{0.159}{(2 \times 10^3)(1.59 \times 10^{-6})} = 50 \Omega \quad \text{Ans.}$$

$$X = X_L - X_C = 32 - 50 = -18 \Omega$$

Minus indicates the circuit is capacitive ( $X_C > X_L$ ).

$$Z = \sqrt{R^2 + X^2} = \sqrt{24^2 + (-18)^2} = 30 \Omega \quad \text{Ans.}$$

$$\theta = \arctan \frac{X}{R} = \arctan \left( -\frac{18}{24} \right) = -36.9^\circ \quad \text{Ans.}$$

**Step 2.** Find  $I$ ,  $V_R$ ,  $V_L$ , and  $V_C$  by Ohm's law.

$$I = \frac{V_T}{Z} = \frac{30}{30} = 1 \text{ A} \quad \text{Ans.}$$

$$V_R = IR = 1(24) = 24 \text{ V} \quad \text{Ans.}$$

$$V_L = IX_L = 1(32) = 32 \text{ V} \quad \text{Ans.}$$

$$V_C = IX_C = 1(50) = 50 \text{ V} \quad \text{Ans.}$$

Step 3. Find  $P$  and PF.

$$P = I^2R = 1^2(24) = 24 \text{ W} \quad \text{Ans.}$$

$$\text{PF} = \cos \theta = \cos (-36.9^\circ) = 0.8 \text{ leading} \quad \text{Ans.}$$

Step 4. Draw the voltage-phasor diagram (see Fig. 14-16b).

14.2 The output signal of a rectifier is 200 V at 120 Hz. It is fed to a filter circuit consisting of a 30-H filter choke coil and a 20- $\mu\text{F}$  capacitor (Fig. 14-17). How much 120-Hz voltage appears across the capacitor? (The purpose of the filter is to reduce considerably the voltage across the capacitor.)

Step 1. Find  $X_L$ ,  $X_C$ , and  $Z$ .

$$X_L = 6.28 fL = 6.28(120)(30) = 22\,600 \, \Omega$$

$$X_C = \frac{0.159}{fC} = \frac{0.159}{120(20 \times 10^{-6})} = 66 \, \Omega$$

$$X = X_L - X_C = 22\,600 - 66 = 22\,542 \, \Omega = 22\,500 \, \Omega \text{ (rounded to three significant figures)}$$

$$Z = \sqrt{R^2 + X^2}$$

Since  $X \gg R$ ,

$$Z \approx X = 22\,500 \, \Omega$$

Step 2. Find  $I$ .

$$I = \frac{V_T}{Z} = \frac{200}{22\,500} = 8.89 \text{ mA}$$

Step 3. Find  $V_C$ .

$$V_C = IX_C = (8.89 \times 10^{-3})(66) = 0.587 \text{ V} \quad \text{Ans.}$$

This is a satisfactory filter since only 0.587 V out of a total of 200 V ac gets through to the output circuit.

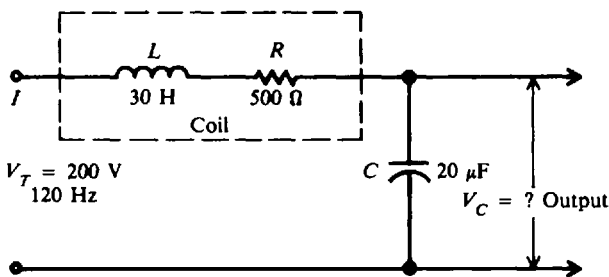


Fig. 14-17 Filter choke coil

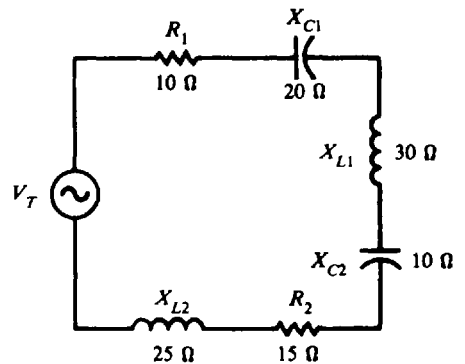


Fig. 14-18

14.3 Find the impedance and current of a  $RLC$  series circuit containing a number of series resistances and reactances (Fig. 14-18).

Add the values of similar circuit elements.

Resistance:  $R_T = R_1 + R_2 = 10 + 15 = 25 \, \Omega$

Capacitance:  $X_{C,T} = X_{C1} + X_{C2} = 20 + 10 = 30 \Omega$   
 Inductance:  $X_{L,T} = X_{L1} + X_{L2} = 30 + 25 = 55 \Omega$   
 Net reactance:  $X_T = X_{L,T} - X_{C,T} = 55 - 30 = 25 \Omega$

$$Z = \sqrt{R_T^2 + X_T^2} = \sqrt{25^2 + 25^2} = 35.4 \Omega \quad \text{Ans.}$$

$$I = \frac{V_T}{Z} = \frac{100}{35.4} = 2.82 \text{ A} \quad \text{Ans.}$$

**14.4** A 30-Ω resistor, a 40-Ω inductive reactance, and a 60-Ω capacitive reactance are connected in parallel across a 120-V 60-Hz ac line (Fig. 14-19a). Find  $I_T$ ,  $\theta$ ,  $Z_T$ , and  $P$ . Is the circuit inductive or capacitive? Draw the current-phasor diagram.

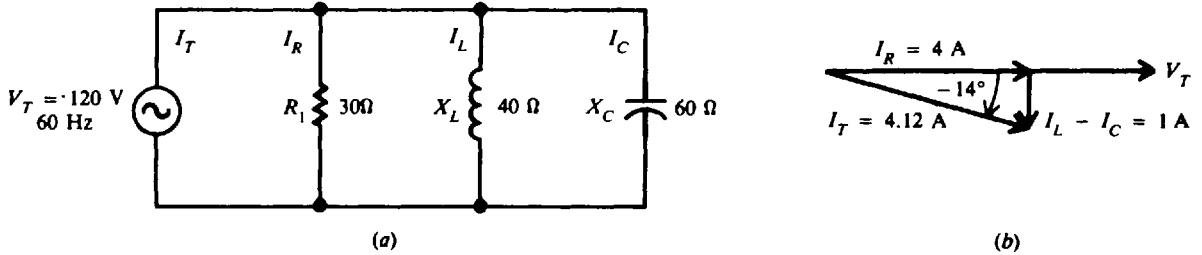


Fig. 14-19

**Step 1.** Find  $I_T$  and  $\theta$ .

$$I_R = \frac{V_T}{R} = \frac{120}{30} = 4 \text{ A} \quad I_L = \frac{V_T}{X_L} = \frac{120}{40} = 3 \text{ A} \quad I_C = \frac{V_T}{X_C} = \frac{120}{60} = 2 \text{ A}$$

Since  $I_L > I_C$ , the circuit is inductive.

$$I_T = \sqrt{I_R^2 + (I_L - I_C)^2} = \sqrt{4^2 + 1^2} = 4.12 \text{ A} \quad \text{Ans.} \quad (14-9)$$

$$\theta = \arctan\left(-\frac{I_L - I_C}{I_R}\right) = \arctan\left(-\frac{1}{4}\right) = -14^\circ \quad \text{Ans.} \quad (14-10)$$

**Step 2.** Find  $Z_T$ .

$$Z_T = \frac{V_T}{I_T} = \frac{120}{4.12} = 29.1 \Omega \quad \text{Ans.}$$

**Step 3.** Find  $P$ .

$$P = V_T I_T \cos \theta = 120(4.12)(\cos 14^\circ) = 480 \text{ W} \quad \text{Ans.}$$

or  $P = I_R^2 R = 4^2(30) = 480 \text{ W} \quad \text{Ans.}$

**Step 4.** Draw the current-phasor diagram (see Fig. 14-19b).  $I_T$  lags  $V_T$  by  $14^\circ$ .

**14.5** An ac circuit can have a number of parallel resistances and reactances (Fig. 14-20). This circuit has more components than Fig. 14-19a (Prob. 14.4). Verify that it has the same value of  $I_T$ ,  $Z_T$ , and  $\theta$ .

$$\begin{aligned} I_{R1} &= \frac{120}{60} = 2 \text{ A} & I_{L1} &= \frac{120}{80} = 1.5 \text{ A} & I_{C1} &= \frac{120}{120} = 1 \text{ A} \\ I_{R2} &= \frac{120}{60} = 2 \text{ A} & I_{L2} &= \frac{120}{80} = 1.5 \text{ A} & I_{C2} &= \frac{120}{120} = 1 \text{ A} \\ I_{R,T} &= 2 + 2 = 4 \text{ A} & I_{L,T} &= 1.5 + 1.5 = 3 \text{ A} & I_{C,T} &= 1 + 1 = 2 \text{ A} \end{aligned}$$

The total resistance branch current is 4 A; total inductive branch current, 3 A; and total capacitive branch current, 2 A. These current values are the same, respectively, in Fig. 14-19a. Therefore,  $I_T$ ,  $Z_T$ , and  $\theta$  have the same values for both circuits.


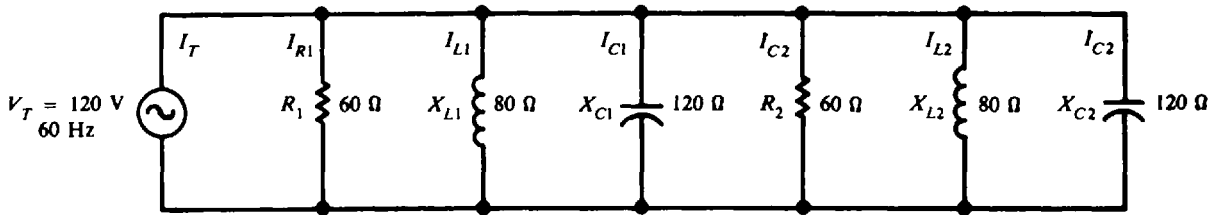


Fig. 14-20

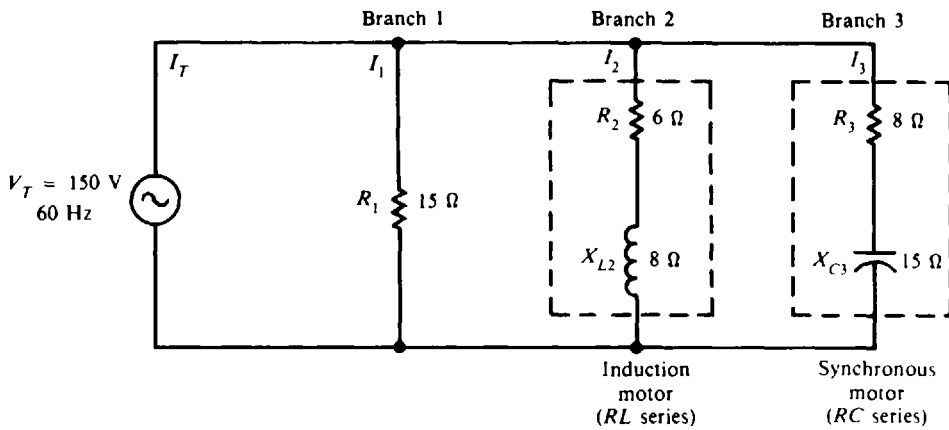14.6 An induction motor of  $6\ \Omega$  resistance and  $8\ \Omega$  inductive reactance is in parallel with a synchronous motor of  $8\ \Omega$  resistance and  $15\ \Omega$  capacitive reactance (Fig. 14-21a). Find the total current drain from a 150-V 60-Hz source, phase angle, total impedance, power factor, and power drawn by the circuit. Find the series impedance, current, and phase angle for each branch.



(a) Three-branch parallel RLC circuit

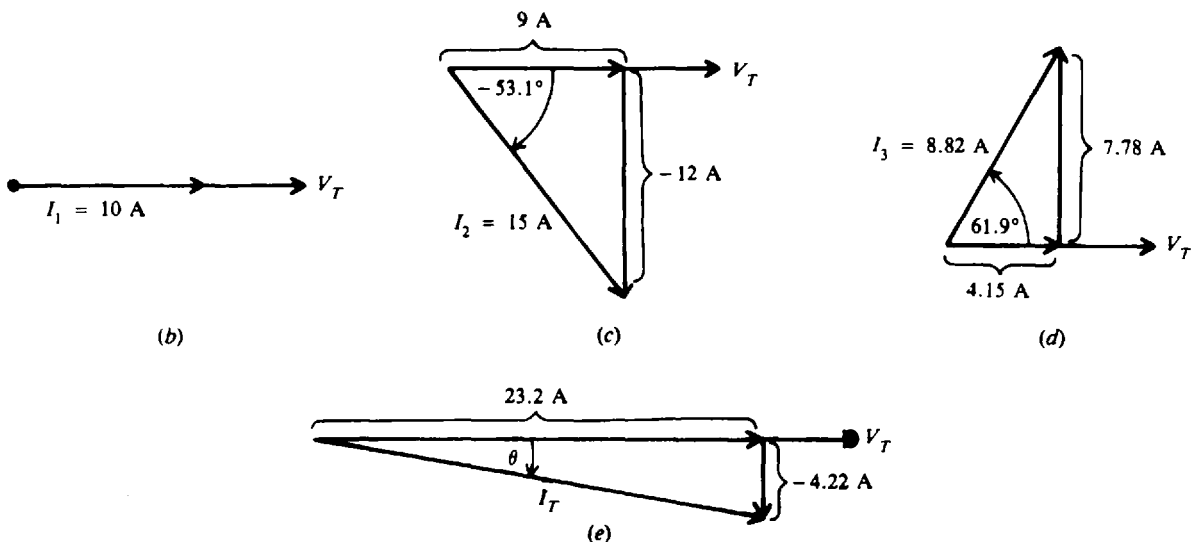


Fig. 14-21

**Step 1.** Find  $Z_1$ ,  $I_1$ , and  $\theta_1$  for branch 1.

$$Z_1 = R_1 = 15 \Omega \quad I_1 = \frac{V_T}{R_1} = \frac{150}{15} = 10 \text{ A}$$

$$\theta_1 = 0^\circ \quad \text{since } I_1 \text{ is in phase with } V_T$$

Calculate horizontal and vertical components of current with respect to  $V_T$  (Fig. 14-21b).

Horizontal component: 10 A

Vertical component: 0 A

**Step 2.** Find  $Z_2$ ,  $I_2$ , and  $\theta_2$  for branch 2.

$$Z_2 = \sqrt{R_2^2 + X_{L2}^2} = \sqrt{6^2 + 8^2} = 10 \Omega \quad I_2 = \frac{V_T}{Z_2} = \frac{150}{10} = 15 \text{ A}$$

$$\theta_2 = \arctan \frac{X_{L2}}{R_2} = \arctan \frac{8}{6} = 53.1^\circ$$

$I_2$  lags  $V_T$  in  $RL$  series branch by  $53.1^\circ$  (Fig. 14-21c).

Horizontal component:  $15 \cos(-53.1^\circ) = 9 \text{ A}$

Vertical component:  $15 \sin(-53.1^\circ) = -12 \text{ A}$

**Step 3.** Find  $Z_3$ ,  $I_3$ , and  $\theta_3$  for branch 3.

$$Z_3 = \sqrt{R_3^2 + X_{C3}^2} = \sqrt{8^2 + 15^2} = 17 \Omega \quad I_3 = \frac{V_T}{Z_3} = \frac{150}{17} = 8.82 \text{ A}$$

$$\theta_3 = \arctan \left( -\frac{X_{C3}}{R_3} \right) = \arctan \left( -\frac{15}{8} \right) = -61.9^\circ$$

$I_3$  leads  $V_T$  in  $RC$  series branch by  $61.9^\circ$  (Fig. 14-21d).

Horizontal component:  $8.82 \cos 61.9^\circ = 4.15 \text{ A}$

Vertical component:  $8.82 \sin 61.9^\circ = 7.78 \text{ A}$

**Step 4.** Find  $L_T$ ,  $\theta$ ,  $Z_T$ , PF, and  $P$  of the circuit.  $I_T$  is the phasor sum of  $I_1$ ,  $I_2$ , and  $I_3$ . The horizontal component of  $I_T$  is the sum of the horizontal components of  $I_1$ ,  $I_2$ , and  $I_3$ , and the vertical component of  $I_T$  is the sum of their vertical components.

$$\text{Horizontal component of } I_T = 10 + 9 + 4.15 = 23.2 \text{ A}$$

$$\text{Vertical component of } I_T = 0 - 12 + 7.78 = -4.22 \text{ A}$$

The resultant phasor is  $I_T$  (Fig. 14-21e).

$$I_T = \sqrt{(23.2)^2 + (-4.22)^2} = 23.6 \text{ A} \quad \text{Ans.}$$

$$\theta = \arctan \left( -\frac{4.22}{23.2} \right) = -10.3^\circ \quad \text{Ans.}$$

$$Z_T = \frac{V_T}{I_T} = \frac{150}{23.6} = 6.36 \Omega \quad \text{Ans.}$$

$$\text{PF} = \cos \theta = \cos(-10.3^\circ) = 0.984 \text{ lagging} \quad (I_T \text{ lags } V_T) \quad \text{Ans.}$$

$$P = V_T I_T \cos \theta = 150(23.6)(0.984) = 3480 \text{ W} \quad \text{Ans.}$$

**14.7** What value of resistance dissipates 800 W of ac power with 5 A rms current?

Use

$$P = I^2 R$$

(14-6)

from which

$$R = \frac{P}{I^2} = \frac{800}{5^2} = \frac{800}{25} = 32 \Omega \quad \text{Ans.}$$

- 14.8 An ac motor operating at 75 percent PF draws 8 A from a 110-V ac line. Find the apparent and real power.

$$\begin{aligned} \text{Apparent power:} \quad S &= VI & (14-19) \\ &= 110(8) = 880 \text{ VA} & \text{Ans.} \end{aligned}$$

$$\begin{aligned} \text{Real (true) power} \quad P &= VI \cos \theta & (14-15) \\ \text{PF} &= \cos \theta = 0.75 \\ P &= 110(8)(0.75) = 660 \text{ W} & \text{Ans.} \end{aligned}$$

- 14.9 A motor operating at 85 percent PF draws 300 W from a 120-V line. What is the current drawn?

$$P = VI \cos \theta \quad (14-15)$$

from which

$$I = \frac{P}{V \cos \theta} = \frac{300}{120(0.85)} = 2.94 \text{ A} \quad \text{Ans.}$$

- 14.10 A 10-kVA induction motor operating at 80 percent lagging PF and a 5-kVA synchronous motor operating at 70 percent leading PF are connected in parallel across a 220-V 60-Hz power line (Fig. 14-22a). Find the total real power  $P_T$ , total reactive power  $Q_T$ , total power factor  $(\text{PF})_T$ , total apparent power  $S_T$ , and total current  $I_T$ .

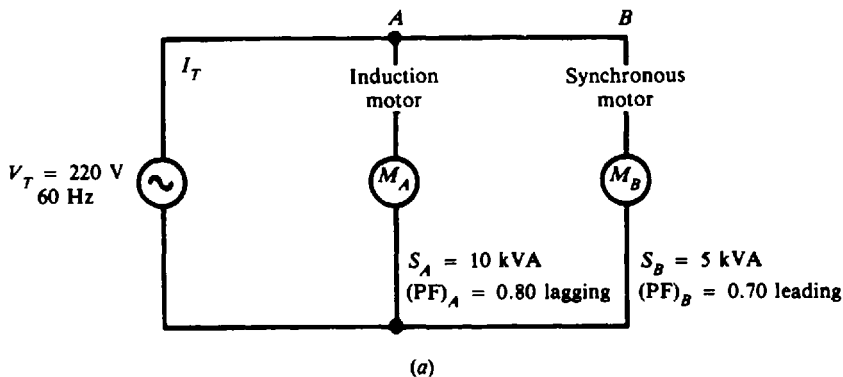


Fig. 14-22a

The approach to this problem with two motors in parallel is first to solve the power triangle for the induction motor, then the power triangle for the synchronous motor, and finally to combine by phasor addition the components of the two power triangles to arrive at the power triangle of the combined motors.

**Step 1.** Find the power relationships of the induction motor.

$$S_A = VI = 10 \text{ kVA, given}$$

$$P_A = VI \cos \theta_A = 10(0.80) = 8 \text{ kW}$$

$$\theta_A = \arccos 0.8 = 36.9^\circ$$

$$Q_A = VI \sin \theta_A = 10(\sin 36.9^\circ) = 10(0.6) = 6 \text{ kVAR lagging because circuit is inductive}$$

The induction motor power triangle is as shown in Fig. 14-22b.

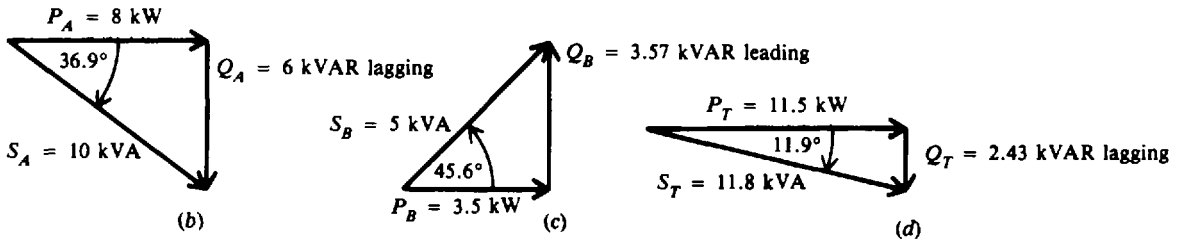


Fig. 14-22b, c, d

**Step 2.** Find power relationships of the synchronous motor.

$$S_B = VI = 5 \text{ kVA, given}$$

$$P_B = VI \cos \theta_B = 5(0.70) = 3.5 \text{ kW}$$

$$\theta_B = \arccos 0.7 = 45.6^\circ$$

$$Q_B = VI \sin \theta_B = 5(\sin 45.6^\circ) = 5(0.71) = 3.57 \text{ kVAR leading because circuit is capacitive}$$

The synchronous motor power triangle is as shown in Fig. 14-22c.

**Step 3.** Find power relations of combined motors. If the power drawn by one branch is not in phase with the power drawn by another branch, power must be added by phasor addition. Therefore,  $P_T$  and  $Q_T$  are the phasor sums of  $P_A$ ,  $P_B$  and  $Q_A$ ,  $Q_B$ , respectively.  $S_T$  is the resultant phasor of  $P_T$  and  $Q_T$ .

$$P_T = P_A + P_B = 8 + 3.5 = 11.5 \text{ kW} \quad \text{Ans.}$$

$$Q_T = Q_A - Q_B = 6 - 3.57 \quad (Q_A > Q_B) \\ = 2.43 \text{ kVAR lagging} \quad \text{Ans.}$$

$$\theta_T = \arctan \frac{Q_T}{P_T} = \arctan \frac{2.43}{11.5} = \arctan 0.211 = 11.9^\circ$$

$$(\text{PF})_T = \cos \theta_T = \cos 11.9^\circ = 0.979 = 97.9\% \text{ lagging} \quad \text{Ans.}$$

$$S_T = \sqrt{P_T^2 + Q_T^2} = \sqrt{(11.5)^2 + (2.43)^2} = 11.8 \text{ kVA} \quad \text{Ans.}$$

The combined motors' power triangle is as shown in Fig. 14-22d. Notice that the addition of the synchronous motor has raised the PF from 0.80 to 0.979.

**14.11** An induction motor takes 7.2 kW at 80 percent PF lagging from a 220-V 60-Hz power line (Fig. 14-23). Find the capacitance of a capacitor placed across the motor terminals in order to increase the PF to 1.

**Step 1.** Find  $S$  and  $Q$  of the induction motor.

$$S = \frac{P}{\text{PF}} = \frac{7.2}{0.8} = 9 \text{ kVA} \quad \text{PF} = \cos \theta = 0.8 \quad \theta = \arccos 0.8 = 36.9^\circ$$

$$Q = P \tan \theta = 7.2 \tan 36.9^\circ = 5.4 \text{ kVAR lagging}$$

**Step 2.** Find the current drawn by the capacitor  $I_C$ . To balance 5.4 kVAR lagging, it is necessary that the capacitor take 5.4 kVAR leading. Since reactive power in a pure capacitor is also its apparent power,

$$S_C = V_C I_C = 5.4 \text{ kVA}$$

$$I_C = \frac{S_C}{V_C} = \frac{5400}{220} = 24.6 \text{ A}$$

**Step 3.** Find the reactance of the capacitor.

$$X_C = \frac{V_C}{I_C} = \frac{220}{24.6} = 8.94 \Omega$$



Step 4. Find the capacitance of the capacitor.

$$C = \frac{0.159}{fX_C} = \frac{0.159}{60(8.94)} = 296 \times 10^{-6} = 296 \mu\text{F} \quad \text{Ans.}$$

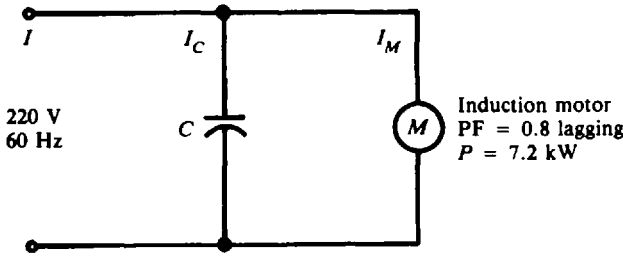


Fig. 14-23

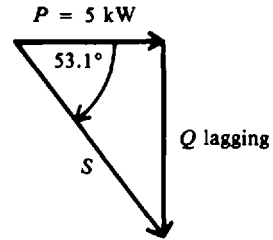


Fig. 14-24

14.12 An inductive load draws 5 kW at 60 percent PF lagging from a 220-V line. Find the kilovoltampere rating of the capacitor needed to raise the total PF unity.

Step 1. Find the power relations of the inductive load (see Fig. 14-24).

$$S = \frac{P}{\text{PF}} = \frac{5}{0.6} = 8.33 \text{ kVA} \quad \text{PF} = \cos \theta = 0.6 \quad \theta = \arccos 0.6 = 53.1^\circ$$

$$Q = 8.33 \sin 53.1^\circ = 6.66 \text{ kVAR lagging}$$

Step 2. Find the kilovoltampere rating of the capacitor. In order to raise the PF to 1, the capacitor must provide 6.66 kVAR of reactive power leading. Since the apparent power in a capacitor is equal to its reactive power,

$$S_C = Q_C = 6.66 \text{ kVA} \quad \text{Ans.}$$

14.13 A plant load draws 2000 kVA from a 240-V line at a PF of 0.7 lagging. Calculate the kilovoltampere required of a capacitor bank in parallel with the plant for the overall PF to be 0.9 lagging.

We use the method of power triangles.

$$\text{PF} = \cos \theta = 0.7 \quad \theta = \arccos 0.7 = 45.6^\circ$$


Real power of the plant load:

$$P = VI \cos \theta = 2000(0.7) = 1400 \text{ kW}$$


Reactive power of the plant load:

$$Q = VI \sin \theta = 2000 \sin 45.6^\circ = 1430 \text{ kVAR lagging}$$

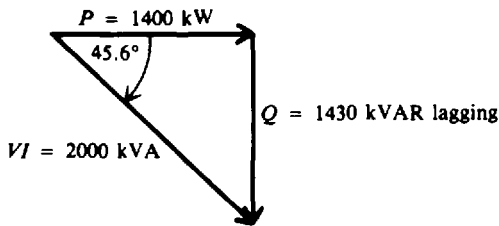Therefore, the power triangle of the original plant is as shown in Fig. 14-25a.



(a) Original plant, PF = 0.7

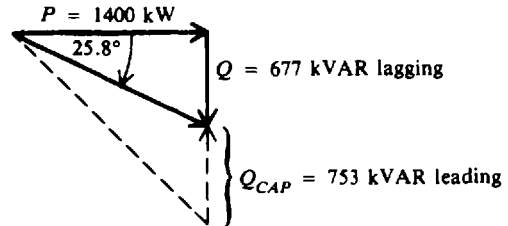

(b) Plant with capacitors added, PF = 0.9

Fig. 14-25 Method of power triangles

We add a parallel capacitor bank to improve the power factor of the plant to 0.9 lagging. The total real power remains the same. We calculate the new  $Q$  of the plant.

$$(PF)_1 = \cos \theta = 0.9 \quad \theta_1 = \arccos 0.9 = 25.8^\circ \quad Q_1 = 1400 \tan 25.8^\circ = 677 \text{ kVAR lagging}$$

The total reactive power of a circuit is equal to the algebraic sum of the reactive powers of each branch. Therefore,

$$\begin{aligned} Q \text{ of the capacitor bank} &= \text{original } Q \text{ of the plant} - \text{new } Q \text{ of the plant} \\ &= 1430 - 677 = 753 \text{ kVAR leading} \end{aligned}$$

Thus  $S$  of the capacitor bank = 753 kVA *Ans.*

The power triangle with the capacitor bank added (Fig. 14-25b) shows how the leading  $Q$  of the capacitors reduces the overall plant  $Q$  to 677 kVAR lagging to produce an improved PF of 0.9.

**14.14** A series  $RL$  combination in an ac circuit has  $R = 10 \Omega$  and  $X_L = 12 \Omega$ . A capacitor is connected across the combination (Fig. 14-26a). What should be the reactance of the capacitor if the circuit is to have a PF of unity?

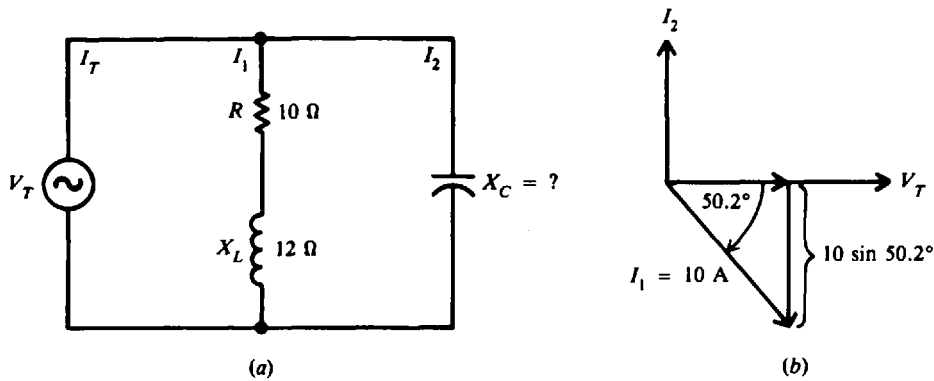


Fig. 14-26

**Step 1.** Find  $I_1$ .

$$Z_1 = \sqrt{R^2 + X_L^2} = \sqrt{10^2 + 12^2} = 15.6 \Omega \quad \theta = \arctan \frac{X_L}{R} = \arctan \frac{12}{10} = 50.2^\circ$$

Assume  $V_T = 156 \text{ V}$ . This choice is arbitrary but is conveniently used because the impedance of the  $RL$  branch is  $15.6 \Omega$ . Then

$$I_1 = \frac{V_T}{Z_1} = \frac{156}{15.6} = 10 \text{ A}$$

The phasor diagram is as shown in Fig. 14-26b.

**Step 2.** Find  $I_2$ . For  $PF = 1$ ,  $I_T$  must be in phase with  $V_T$ .  $I_T$  is the phasor sum of  $I_1$  and  $I_2$ . The current in the capacitor,  $I_2$  (leading  $V_T$  by  $90^\circ$ ), must cancel the vertical component of  $I_1$  in order for  $I_T$  to be in phase with  $V_T$  (Fig. 14-26b). Therefore,

$$I_2 = 10 \sin 50.2^\circ = 7.68 \text{ A}$$


**Step 3.** Find  $X_C$ .

$$X_C = \frac{V_T}{I_2} = \frac{156}{7.68} = 20.3 \Omega \quad \text{Ans.}$$


### Supplementary Problems

- 14.15** In a series circuit,  $R = 12 \Omega$ ,  $X_L = 7 \Omega$ , and  $X_C = 2 \Omega$ . Find the impedance and phase angle of the circuit and the line current when the ac voltage is 110 V. Also find all voltage drops and draw the voltage-phasor diagram.

*Ans.*  $Z = 13 \Omega$ ,  $\theta = 22.6^\circ$ ;  $I = 8.46 \text{ A (lagging)}$ ;  $V_R = 101.5 \text{ V}$ ;  $V_L = 59.2 \text{ V}$ ;  $V_C = 16.9 \text{ V}$ ; phasor diagram: Fig. 14-27.

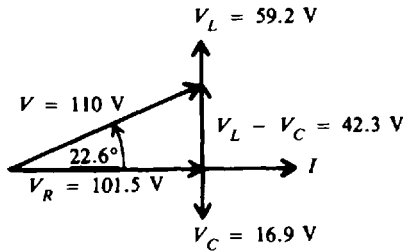


**Fig. 14-27** Phasor diagram

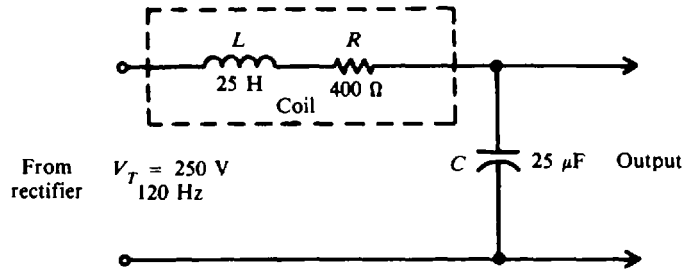

**Fig. 14-28**

- 14.16** In a series circuit,  $R = 6 \Omega$ ,  $X_L = 4 \Omega$ , and  $X_C = 12 \Omega$ . Find  $Z$ ,  $\theta$ ,  $I$ ,  $V_R$ ,  $V_L$ ,  $V_C$ , and  $P$  when the line voltage is 115 V.  
*Ans.*  $Z = 10 \Omega$ ;  $\theta = -53.1^\circ$ ;  $I = 11.5 \text{ A (leading)}$ ;  $V_R = 69 \text{ V}$ ;  $V_L = 46 \text{ V}$ ;  $V_C = 138 \text{ V}$ ;  $P = 794 \text{ W}$
- 14.17** A 130-V 200-Hz power supply is connected across a 10-k $\Omega$  resistor, a 0.05- $\mu\text{F}$  capacitor, and a 10-H coil in series. Find  $X_L$ ,  $X_C$ ,  $Z$ ,  $\theta$ ,  $I$ , and  $P$ .  
*Ans.*  $X_L = 12\,560 \Omega$ ;  $X_C = 15\,900 \Omega$ ;  $Z = 10\,540 \Omega$ ;  $\theta = -18.5^\circ$ ;  $I = 12.3 \text{ mA (leading)}$ ;  $P = 1.51 \text{ W}$
- 14.18** A rectifier delivers 250 V at 120 Hz to a filter circuit consisting of a filter choke coil having 25 H inductance and 400  $\Omega$  resistance, and a 25- $\mu\text{F}$  capacitor (Fig. 14-28). Find the reactance of the coil, the reactance of the capacitor, the impedance of the circuit, the current, and the amount of the 120-Hz voltage that will appear across the capacitor.  
*Ans.*  $X_L = 18\,840 \Omega$ ;  $X_C = 53 \Omega$ ;  $Z = 18\,790 \Omega$ . For practical purposes the circuit is predominantly inductive ( $Z \approx X_L$ ).  $I = 13.3 \text{ mA}$ ;  $V_C = 0.7 \text{ V}$ . Note that only 0.7 V out of a total of 250 V of the 120-Hz ac reaches the output.
- 14.19** A series circuit has  $R = 300 \Omega$ ,  $X_{C1} = 300 \Omega$ ,  $X_{C2} = 500 \Omega$ ,  $X_{L1} = 400 \Omega$ , and  $X_{L2} = 800 \Omega$ , all in series with an applied voltage  $V_T$  of 400 V. Calculate  $Z$ ,  $I$ , and  $\theta$ .  
*Ans.*  $Z = 500 \Omega$ ;  $I = 0.8 \text{ A (lagging)}$ ;  $\theta = 53.1^\circ$
- 14.20** A 10-H coil and a 0.75- $\mu\text{F}$  capacitor are in series with a variable resistor. What must be the value of the resistance in order to draw 0.4 A from a 120-V 60-Hz line?  
*Ans.*  $R = 186 \Omega$ ; ( $X_L - X_C = 235 \Omega$ )
- 14.21** A series resonant circuit ( $X_L = X_C$ ) has a 0.1-H inductance, a 1.013- $\mu\text{F}$  capacitor, and a 5- $\Omega$  resistor connected across a 50-V 500-Hz supply line. Find the inductive and capacitive reactance, impedance, phase angle, current, and voltage across each part of the circuit. Draw the phasor diagram.  
*Ans.*  $X_L = 314 \Omega$ ;  $X_C = 314 \Omega$ ;  $Z = 5 \Omega$ ;  $\theta = 0^\circ$ ;  $I = 10 \text{ A}$ ;  $V_R = 50 \text{ V}$ ;  $V_L = 3140 \text{ V}$ ;  $V_C = 3140 \text{ V}$ ; phasor diagram: Fig. 14-29.

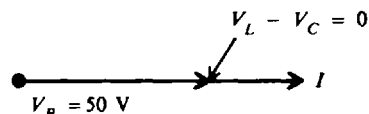

**Fig. 14-29** Phasor diagram

14.22 Fill in the indicated values for a series RLC circuit.

	$V_T, V$	$\theta^\circ$	$I, A$	$R, \Omega$	$X_L, \Omega$	$X_C, \Omega$	$Z, \Omega$	$V_R, V$	$V_L, V$	$V_C, V$	$P, W$	Circuit Type
(a)	?	?	1	3	8	4	?	?	?	?	?	?
(b)	104	?	?	12	2	7	?	?	?	?	?	?
(c)	110	?	?	22	18	18	?	?	?	?	?	?
(d)	?	$45^\circ$	?	15	30	?	?	30	?	?	?	?
(e)	14.1	?	0.1	?	150	250	?	?	?	?	?	?

Ans.

	$V_T, V$	$\theta^\circ$	$I, A$	$R, \Omega$	$X_L, \Omega$	$X_C, \Omega$	$Z, \Omega$	$V_R, V$	$V_L, V$	$V_C, V$	$P, W$	Circuit Type
(a)	5	$53.1^\circ$	.....	.....	.....	.....	5	3	8	4	3	Inductive
(b)	.....	$-22.6^\circ$	8	.....	.....	.....	13	96	16	56	768	Capacitive
(c)	.....	0	5	.....	.....	.....	22	110	90	90	550	Resonant
(d)	42.4	.....	2	.....	.....	15	21.2	.....	60	30	60	Inductive
(e)	.....	$-45^\circ$	.....	99.4	.....	.....	141	10	15	25	1	Capacitive

14.23 A  $30\text{-}\Omega$  resistor, a  $15\text{-}\Omega$  inductive reactance, and a  $12\text{-}\Omega$  capacitive reactance are connected in parallel across a  $120\text{-V}$   $60\text{-Hz}$  line. Find (a) the phasor branch currents, (b) total current and phase angle, (c) impedance, and (d) power drawn by the circuit; and (e) draw the current-phasor diagram.

Ans. (a)  $I_R = 4\text{ A}$ ;  $I_L = 8\text{ A}$ ;  $I_C = 10\text{ A}$ ; (b)  $I_T = 4.47\text{ A}$  (leading);  $\theta = 26.6^\circ$ ; (c)  $Z_T = 26.8\text{ }\Omega$ ; (d)  $P = 480\text{ W}$ ; (e) phasor diagram: Fig. 14-30

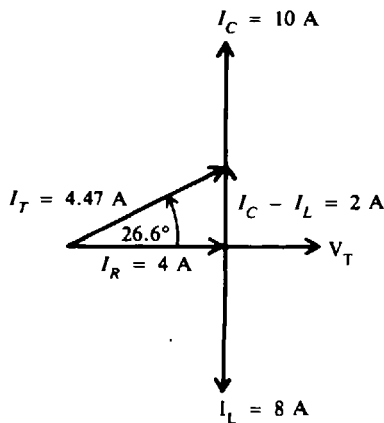


Fig. 14-30 Phasor diagram

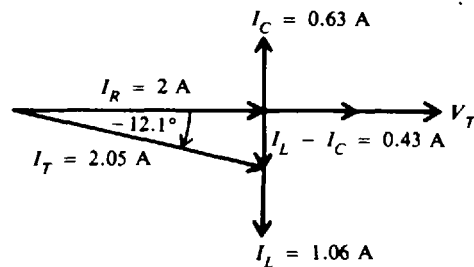


Fig. 14-31 Phasor diagram

14.24 A  $100\text{-}\Omega$  resistor, a  $3\text{-mH}$  coil, and a  $0.05\text{-}\mu\text{F}$  capacitor are in parallel across a  $200\text{-V}$   $10\text{-kHz}$  ac source. Find (a) the reactance of the coil and capacitor, (b) phasor current drawn by each branch, (c) total current, (d) impedance and phase angle, and (e) power drawn by the circuit; and (f) draw the phasor diagram.

Ans. (a)  $X_L = 188\text{ }\Omega$ ;  $X_C = 318\text{ }\Omega$ ; (b)  $I_R = 2\text{ A}$ ;  $I_L = 1.06\text{ A}$ ;  $I_C = 0.63\text{ A}$ ; (c)  $I_T = 2.05\text{ A}$  (lagging); (d)  $Z_T = 97.6\text{ }\Omega$ ;  $\theta = -12.1^\circ$ ; (e)  $P = 400\text{ W}$ ; (f) phasor diagram: Fig. 14-31

14.25 With  $420\text{ mV}$  applied, an ac circuit has the following parallel branches:  $R_1 = 100\text{ }\Omega$ ;  $R_2 = 175\text{ }\Omega$ ;  $X_{L1} = 60\text{ }\Omega$ ;  $X_{L2} = 420\text{ }\Omega$ ;  $X_C = 70\text{ }\Omega$ . Calculate  $I_T$ ,  $Z_T$ , and  $\theta$ .

Ans.  $I_T = 6.9\text{ mA}$  (lagging);  $Z_T = 60.9\text{ }\Omega$ ,  $\theta = -16.9^\circ$

14.26 Repeat Prob. 14.23 but substitute a 15-Ω capacitive reactance for the given 12-Ω capacitive reactance. Because  $X_L = X_C = 15 \Omega$ , we have now a parallel resonant circuit. A parallel resonant circuit has a maximum impedance and a minimum current at the resonant frequency.

Ans. (a)  $I_R = 4 \text{ A}$ ;  $I_L = 8 \text{ A}$ ;  $I_C = 8 \text{ A}$ ; (b)  $I_T = 4 \text{ A}$  (compare with Prob. 14.23);  $\theta = 0^\circ$ ;  
 (c)  $Z_T = 30 \Omega$  (compare with Prob. 14.23); (d)  $P = 480 \text{ W}$ ; (e) phasor diagram: Fig. 14-32

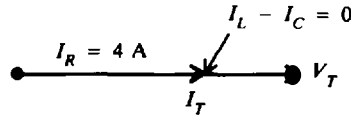


Fig. 14-32 Phasor diagram

14.27 Find the indicated values for a RLC parallel circuit.

	V, V	R, Ω	$X_L, \Omega$	$X_C, \Omega$	$I_R$	$I_L$	$I_C$	$I_T$	$Z_T$	$\theta$	P, W	Circuit Type
(a)	110	27.5	22	55	?	?	?	?	?	?	?	?
(b)	90	45	40	30	?	?	?	?	?	?	?	?
(c)	90	45	40	40	?	?	?	?	?	?	?	?

Ans.

	V, V	R, Ω	$X_L, \Omega$	$X_C, \Omega$	$I_R, \text{ A}$	$I_L, \text{ A}$	$I_C, \text{ A}$	$I_T, \text{ A}$	$Z_T, \Omega$	$\theta^\circ$	P, W	Circuit Type
(a)	....	....	....	....	4	5	2	5	22	-36.9°	440	Inductive
(b)	....	....	....	....	2	2.25	3	2.14	42.1	20.6°	180	Capacitive
(c)	....	....	....	....	2	2.25	2.25	2	45	0	180	Resonant

14.28 Find  $I_T$ ,  $\theta$ , PF, and  $Z_T$  of an ac circuit with a RL branch in parallel to a RC branch (Fig. 14-33).

Ans.  $I_T = 7.82 \text{ A}$ ;  $\theta = -33.5^\circ$ ; PF = 0.834 lagging;  $Z = 3.07 \Omega$

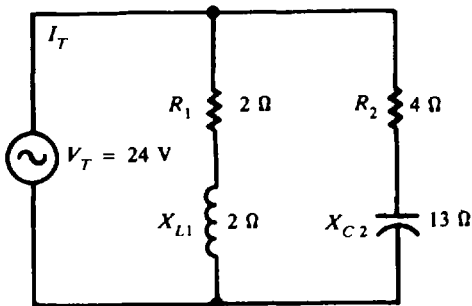


Fig. 14-33

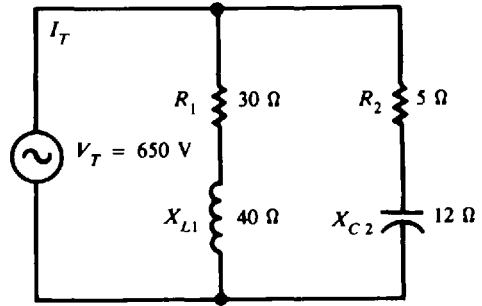


Fig. 14-34

14.29 For the circuit shown, calculate  $I_T$ ,  $\theta$ ,  $Z_T$ , PF, and P (Fig. 14-34).

Ans.  $I_T = 44.8 \text{ A}$ ;  $\theta = 53^\circ$ ;  $Z_T = 14.5 \Omega$ ; PF = 0.602 leading;  $P = 17\,530 \text{ W}$

14.30 With 420 mV applied, an ac circuit has the five following parallel branches:  $R_1 = 100 \Omega$ ;  $R_2 = 175 \Omega$ ;  $X_{L1} = 60 \Omega$ ;  $X_{L2} = 420 \Omega$ ; and  $X_C = 70 \Omega$ . Find  $I_T$ ,  $\theta$ , and  $Z_T$ .

Ans.  $I_T = 6.90 \text{ mA}$  (lagging);  $\theta = -16.9^\circ$ ;  $Z_T = 60.9 \Omega$

14.31 Find the power factor of a washing-machine motor if it draws 4 A and 420 W from a 110-V ac line.

Ans. PF = 0.955, or 95.5%

14.32 Find the PF of a refrigerator motor if it draws 300 W and 3.5 A from a 120-V ac line.

Ans. PF = 71.4%

- 14.33 The lights and motors in a shop draw 20 kW of power. The PF of the entire load is 60 percent. Find the number of kilovoltamperes of power delivered to the load. *Ans.*  $S = 33.3 \text{ kVA}$
- 14.34 A 50-V 60-Hz power supply is connected across a RLC series ac circuit with  $R = 3 \Omega$ ,  $X_L = 6 \Omega$ , and  $X_C = 2 \Omega$ . Find the apparent power, real power, reactive power, and power factor; and draw the power triangle.  
*Ans.*  $S = 500 \text{ VA}$ ;  $P = 300 \text{ W}$ ;  $Q = 400 \text{ VAR lagging}$ ; PF = 0.6, power triangle: Fig. 14.35

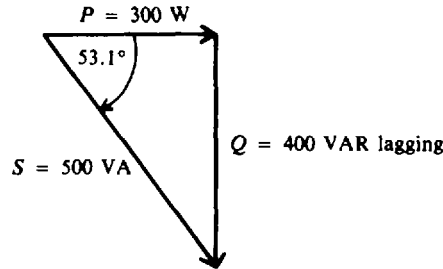


Fig. 14-35 Power triangle

- 14.35 A current of 8 A lags a voltage of 250 V by  $30^\circ$ . What is the power factor and the real power taken by the load? *Ans.* PF = 0.866 lagging;  $P = 1732 \text{ W}$
- 14.36 A motor operating at an 85 percent PF draws 300 W from a 120-V line. What is the current drawn? *Ans.*  $I = 2.94 \text{ A}$
- 14.37 A 220-V line delivers 15 kVA to a load at 80 percent PF lagging. Find the PF of a 12-kVA synchronous motor in parallel to raise the PF to 100 percent.  
*Ans.* PF = 66.1% leading
- 14.38 A bank of motors draws 30 kW at 75 percent PF lagging from a 440-V 60-Hz line. Find the kilovoltamperage and the capacitance of a capacitor placed across the motor terminals if it is to raise the total PF to 1.0. *Ans.*  $S = 26.5 \text{ kVA}$ ;  $C = 363 \mu\text{F}$
- 14.39 A motor draws 2 kW and 10 A from a 220-V 60-Hz line. Find the voltamperage and the capacitance of a capacitor in parallel that will raise the total PF to 1. *Ans.*  $S = 916 \text{ VA}$ ;  $C = 50 \mu\text{F}$
- 14.40 A 220-V 20-A induction motor draws 3 kW of power. A 4-kVA capacitive load is placed in parallel to adjust the PF to unity. What must be the PF of the capacitive load? *Ans.* PF = 59.3% leading
- 14.41 A plant load draws 2000 kVA from a 240-V line at a PF of 0.7 lagging. Find the kilovoltamperage required of a capacitor bank in parallel with the plant for the overall PF to be 0.9 leading.  
*Ans.* 2107 kVA
- 14.42 A series RL branch in an ac circuit has  $R = 8 \Omega$  and  $X_L = 10 \Omega$ . A capacitor is connected in parallel across the branch. What should be the reactance of the capacitor if the unit is to have a PF of unity?  
*Ans.*  $X_C = 16.4 \Omega$
- 14.43 Find  $I_T$ ,  $\theta$ ,  $Z_T$ , PF, and  $P$  for the circuit shown (Fig. 14-36).  
*Ans.*  $I_T = 4.49 \text{ A}$ ;  $\theta = -20.9^\circ$ ;  $Z_T = 22.3 \Omega$ ; PF = 0.934 lagging;  $P = 419 \text{ W}$

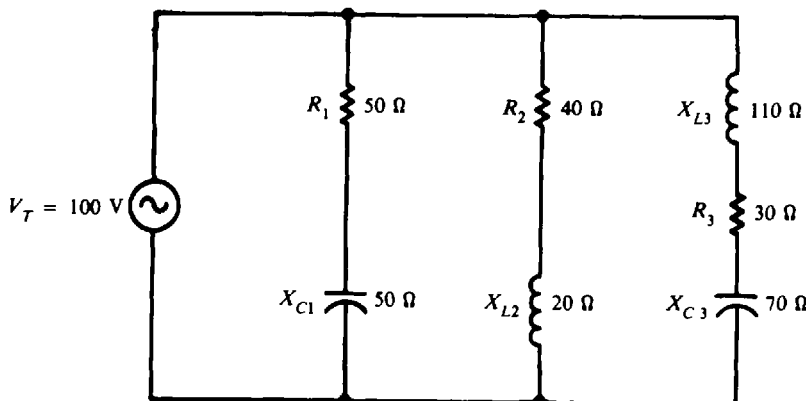


Fig. 14-36

## Alternating-Current Generators and Motors

### ALTERNATORS

Alternating-current generators are also called *alternators*. Almost all electric power for homes and industry is supplied by alternators in power plants. A simple alternator consists of (1) a strong, constant magnetic field; (2) conductors that rotate across the magnetic field; and (3) some means of making a continuous connection to the conductors as they are rotating (Fig. 15-1). The magnetic field is produced by current flowing through the stationary, or stator, field coil. Field-coil excitation is supplied by a battery or other dc source. The armature, or rotor, rotates within the magnetic field. For a single turn of wire around the rotor, each end is connected to a separate slip ring, which is insulated from the shaft. Each time the rotor turn makes one complete revolution, one complete cycle of alternating current is developed (Fig. 15-2). A practical alternator has several hundred turns wound into the slots of the rotor. Two brushes are spring-held against the slip rings to provide the continuous connection between the alternating current induced in the rotor or armature coil and the external circuits.

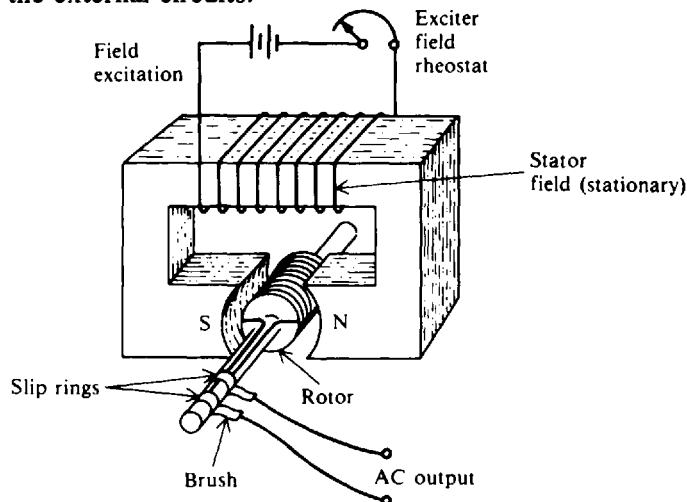


Fig. 15-1 A simple alternator having a stationary field and a rotating armature

The small ac generator usually has a stationary field and a rotating armature (Fig. 15-1). One disadvantage is that the slip-ring and brush contacts are in series with the load. If these parts become worn or dirty, current flow may be interrupted. However, if the dc field excitation is connected to the rotor, the formerly stationary coils will have alternating current induced into them (Fig. 15-3). A load can be connected across these armature coils without the necessity of any moving contacts in the circuit. Field excitation is fed to the rotating field through the slip rings and brushes. Another advantage of this rotating-field and stationary-armature generator is the greater ease of insulating stator fields compared with insulating rotating field coils. Since voltages as high as 18 000 to 24 000 V are commonly generated, this high voltage need not be brought out through slip rings and brushes but can be brought directly to the switch gear through insulated leads from the stationary armature.

The amount of generated voltage of an ac generator depends on the field strength and speed of the rotor. Since most generators are operated at constant speed, the amount of emf depends on field excitation.


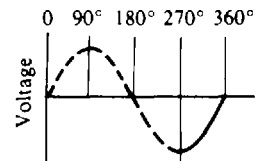
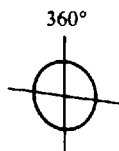
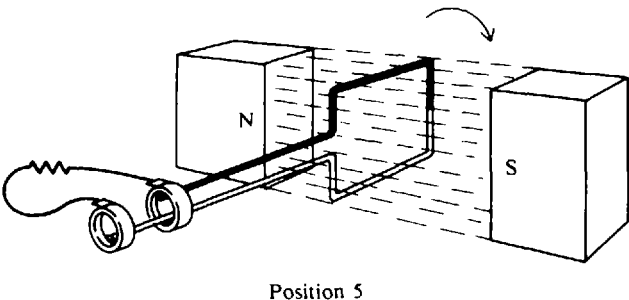
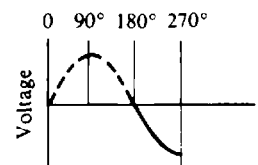
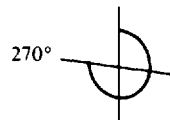
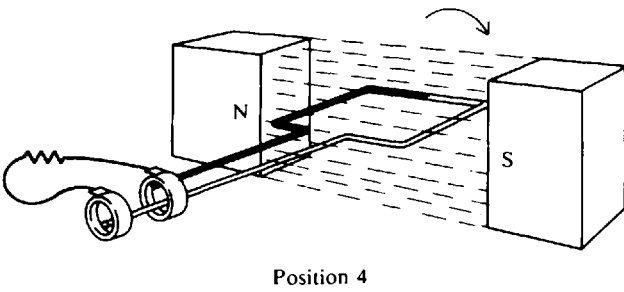
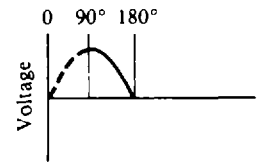
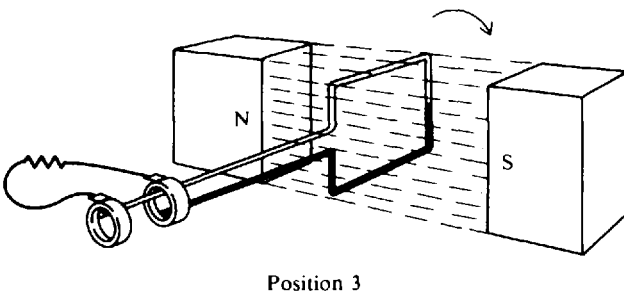
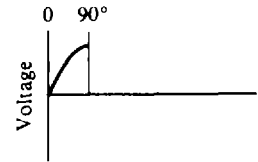
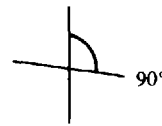
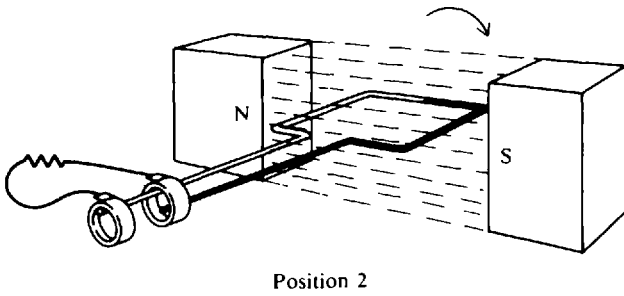
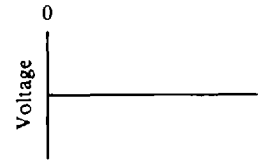
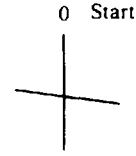


Fig. 15-2 Generating 1 cycle of ac voltage with a single-coil alternator

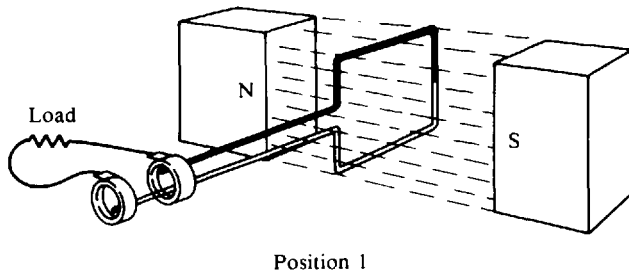

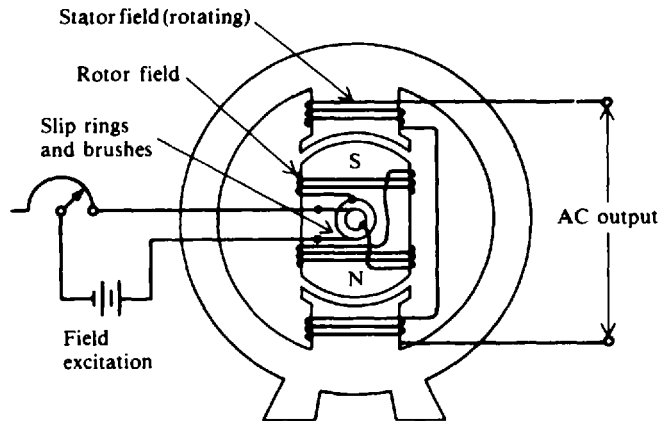


Fig. 15-3 A simple alternator having a rotating field and a stationary armature

The frequency of the generated emf depends on the number of field poles and on the speed at which the generator is operated, or

$$f = \frac{pn}{120} \quad (15-1)$$

where  $f$  = frequency of generated voltage, Hz  
 $p$  = total number of poles  
 $n$  = rotor speed, revolutions per minute (rpm)

Regulation of an ac generator is the percentage rise in terminal voltage as load is reduced from the rated full-load current to zero, with the speed and excitation being constant, or

$$\text{Voltage regulation} = \frac{\text{no-load voltage} - \text{full-load voltage}}{\text{full-load voltage}} \quad (15-2)$$

**Example 15.1** What is the frequency of a four-pole alternator operating at a speed of 1500 rpm?

$$\begin{aligned} f &= \frac{pn}{120} & (15-1) \\ &= \frac{4(1500)}{120} = 50 \text{ Hz} & \text{Ans.} \end{aligned}$$

**Example 15.2** An alternator is operating at 120 V with no load. A load is now applied to the generator. The voltage output drops (the field current remains the same) to 110 V. What is the regulation?

$$\begin{aligned} \text{Voltage regulation} &= \frac{\text{no-load voltage} - \text{full-load voltage}}{\text{full-load voltage}} & (15-2) \\ &= \frac{120 - 110}{110} = \frac{10}{110} = 0.091 = 9.1\% & \text{Ans.} \end{aligned}$$

When the output voltage is not steady, there would be a constant flickering of electric lights, and TV sets would not operate properly. Automatic voltage-regulator devices are used to make up for the drop in output voltage by increasing the field current. Voltage regulation is usually a function external to the alternator.

## PARALLELING GENERATORS

Most power plants have several ac generators operating in parallel in order to increase the power available. Before two generators may be paralleled, their terminal voltages must be equal, their voltages must be in phase, and their frequencies must be equal. When these conditions are met, the two generators are operating in *synchronism*. The operation of getting the generators into synchronism is called *synchronizing*.

## RATINGS

Nameplate data for a typical ac generator (Fig. 15-4) include manufacturer's name, serial, and type number; speed (rpm), number of poles, frequency of output, number of phases, and maximum supply voltage; capacity rating in kilovoltamperes and kilowatts at a specified power factor and maximum output voltage; armature and field current per phase; and maximum temperature rise.

Westinghouse
AC generator air cooled NO. 6750616 Type ATB 3600 RPM
2 poles 60 hertz 3-phase wye-connected for 13 800 volts
Rating 15 625 KVA 12 500 kW 0.80 PF exciter 250 volts
Armature 654 amp field 183 amp
Guaranteed temp. rise not to exceed 60°C on armature by detector 80°C on field by resistance

Fig. 15-4 Nameplate data for typical ac generator

## LOSSES AND EFFICIENCY

Losses of an ac generator are similar to those of a dc generator and include armature copper loss, field-excitation copper loss, and mechanical losses.

Efficiency (Eff) is the ratio of the useful power output to the total power input:

$$\text{Eff} = \frac{\text{output}}{\text{input}} \quad (15-3)$$

**Example 15.3** A 2-hp motor running at rated output acts as the prime mover for an alternator that has a load demand of 1.1 kW. What is the efficiency of the alternator in percent? Neglect field excitation.

$$\text{Input power} = 2 \text{ hp} \times \frac{746 \text{ W}}{\text{hp}} = 1492 \text{ W} \quad \text{Output power} = 1.1 \text{ kW} = 1100 \text{ W}$$

$$\text{Eff} = \frac{\text{output}}{\text{input}} = \frac{1100}{1492} = 0.737 = 73.7\% \quad \text{Ans.}$$

Since the prime mover is supplying 1492 W but the alternator is delivering 1100 W to the load, there must be 392 W of loss in the alternator.


## POLYPHASE INDUCTION MOTORS

### Principle of Operation


The induction motor is the most commonly used type of ac motor because of its simple, rugged construction and good operating characteristics. It consists of two parts: the stator (stationary part) and the rotor (rotating part). The stator is connected to the ac supply. The rotor is not connected electrically to the supply. The most important type of polyphase induction motor is the three-phase motor. (Three-phase machines have three windings and deliver an output between several pairs of wires.) When the stator winding is energized from a three-phase supply, a rotating magnetic field is created. As the field sweeps across the rotor conductors, an emf is induced in these conductors which causes current to flow in them. The rotor conductors carrying current in the stator field thus have a torque exerted upon them that spins the rotor.

### Squirrel-Cage Motor and Wound-Rotor Motor

Three-phase induction motors are classified into two types: squirrel-cage (Fig. 15-5) and wound-rotor motors (Fig. 15-6). Both motors have the same stator construction, but differ in rotor construction. The stator core is built of slotted sheet-steel laminations. Windings are spaced in the stator slots to form the three separate sets of poles.

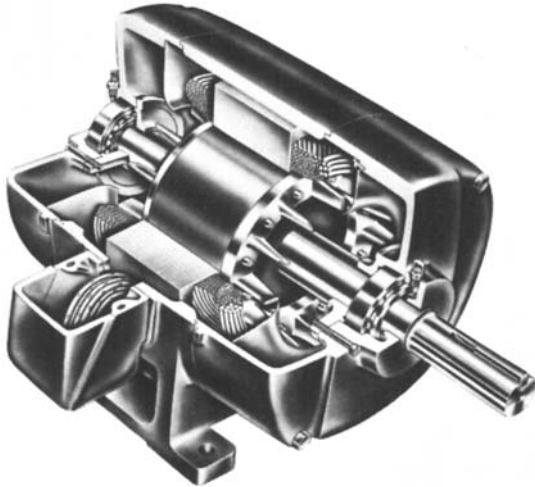


**Fig. 15-5** Cutaway view of a squirrel-cage induction motor (Courtesy of General Electric Company; from *E. C. Lister, Electric Circuits and Machines, 5th ed., McGraw-Hill, New York, 1975, p. 247*)

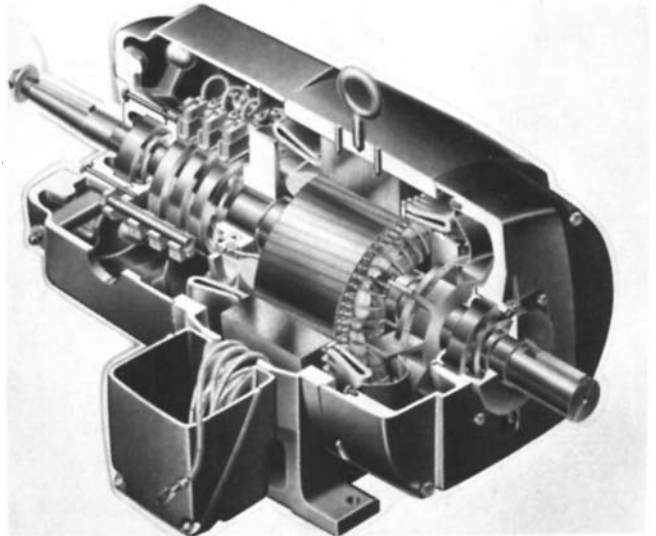

**Fig. 15-6** Cutaway view of a wound rotor induction motor (Courtesy of General Electric Company; from *Lister, p. 248*)

The rotor of a squirrel-cage motor has a laminated core, with conductors placed parallel to the shaft and embedded in slots around the perimeter of the core. The rotor conductors are not insulated from the core. At each end of the rotor, the rotor conductors are all short-circuited by continuous end rings. If the laminations were not present, the rotor conductors and their end rings would resemble a revolving squirrel cage (Fig. 15-7).

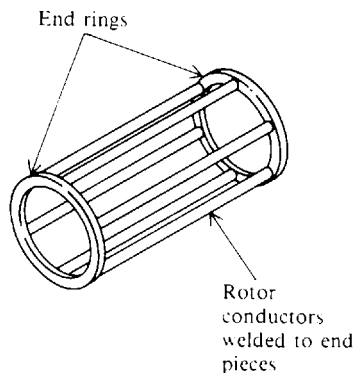

**Fig. 15-7** A simple squirrel-cage rotor with rotor conductors welded to end rings on a shaft

The rotor of a wound-rotor motor is wound with an insulated winding similar to the stator winding. The rotor phase windings are brought out to the three slip rings mounted on the motor shaft (Fig. 15-6). The rotor winding is not connected to the supply. The slip rings and brushes merely provide a means of connecting an external rheostat into the rotor circuit. The purpose of the rheostat is to control the speed of the motor.

**Speed and Slip**

The speed of the rotating magnetic field is called the *synchronous* speed of the motor.

$$n = \frac{120f}{p} \quad (15-4)$$

where  $n$  = speed of rotating magnetic field, rpm  
 $f$  = frequency of rotor current, Hz  
 $p$  = total number of poles

It is noted that the same relation exists between the frequency, number of poles, and synchronous speed of a motor [Eq. (15-4)] as exists between the frequency, number of poles, and speed of rotation of an ac generator [Eq. (15-1)].

An induction motor cannot run at synchronous speed since then the rotor would be standing still with respect to the rotating field and no emf would be induced in the rotor. The rotor speed must be slightly less than synchronous speed in order that current be induced in the rotor to permit rotor rotation. The difference between rotor speed and synchronous speed is called *slip* and is expressed as a percent of synchronous speed.

$$\text{Percent } S = \frac{N_S - N_R}{N_S} 100 \quad (15-5)$$

where  $S$  = slip  
 $N_S$  = synchronous speed, rpm  
 $N_R$  = rotor speed, rpm

**Example 15.4** A four-pole 60-Hz squirrel-cage motor has a full-load speed of 1754 rpm. What is the percent slip at full load?

$$\begin{aligned} \text{Synchronous speed } N_S &= \frac{120f}{p} & (15-4) \\ &= \frac{120(60)}{4} = 1800 \text{ rpm} \end{aligned}$$

$$\text{Slip} = N_S - N_R = 1800 - 1754 = 46 \text{ rpm}$$

$$\begin{aligned} \text{Percent } S &= \frac{N_S - N_R}{N_S} 100 & (15-5) \\ &= \frac{46}{1800} 100 = 2.6\% \quad \text{Ans.} \end{aligned}$$

**Rotor Frequency**

For any value of slip, the rotor frequency is equal to the stator frequency times the percent slip, or

$$f_R = S f_S \quad (15-6)$$

where  $f_R$  = rotor frequency, Hz  
 $S$  = percent slip (written as a decimal)  
 $f_S$  = stator frequency, Hz

**Example 15.5** At a slip of 2.6 percent for the induction motor in Example 15.4, what is the rotor frequency?

$$\begin{aligned} f_S &= 60 \text{ Hz} \quad \text{given} \\ f_R &= S f_S & (15-6) \\ &= 0.026(60) = 1.56 \text{ Hz} \quad \text{Ans.} \end{aligned}$$

### Torque

The torque of an induction motor depends on the strength of the interacting rotor and stator fields and the phase relations between them.

$$T = k\phi I_R \cos \theta_R \quad (15-7)$$

where  $T$  = torque, lb · ft  
 $k$  = constant  
 $\phi$  = rotating stator flux, lines of flux  
 $I_R$  = rotor current, A  
 $\cos \theta_R$  = rotor power factor

Throughout the normal range of operation,  $k$ ,  $\phi$ , and  $\cos \theta_R$  are nearly constant so that  $T$  is directly proportional to  $I_R$ . Rotor current  $I_R$  in turn increases in almost direct proportion to the motor slip. Variation of torque with slip (Fig. 15-8) shows that as slip increases from zero to about 10 percent, the torque linearly increases with the slip. As load and slip are increased beyond rated or full-load torque, the torque reaches a maximum value at about 25 percent slip. This maximum value of torque is called the *breakdown torque* of the motor. If the load is further increased beyond the breakdown point, the motor will quickly come to a stop. For typical squirrel-cage motors, the breakdown torque varies from 200 to 300 percent of full-load torque. The starting torque is the value at 100 percent slip (rotor speed is zero) and is normally 150 to 200 percent of full-load rating. As the rotor accelerates, the torque increases to its maximum value and then decreases to the value required to carry the load on the motor at a constant speed.

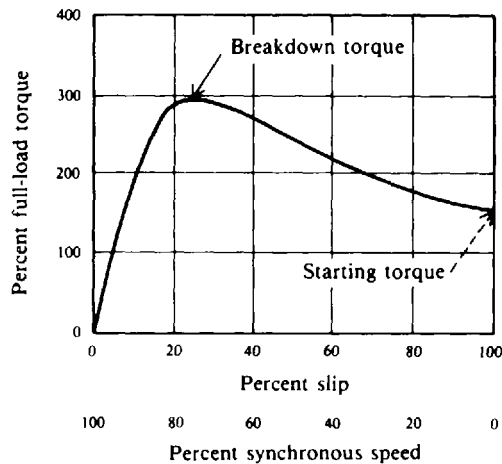


Fig. 15-8 Variation of torque with slip for a typical squirrel-cage motor

### SYNCHRONOUS MOTORS

Like induction motors, synchronous motors have stator windings that produce a rotating magnetic field. But unlike the induction motor, the rotor circuit of a synchronous motor is excited by a dc source. The rotor locks into step with the rotating magnetic field and rotates at the same speed, as given by Eq. (15-4). If the rotor is pulled out of step with the rotating stator field, no torque is developed and the motor stops. Since a synchronous motor develops torque only when running at synchronous speed, it is not self-starting and hence needs some device to bring the rotor to synchronous speed.

**Example 15.6** What is the slip of a synchronous motor?

Since the synchronous speed is equal to the rotor speed,  $N_s = N_R$ ,

$$\begin{aligned} \text{Percent } S &= \frac{N_s - N_R}{N_s} 100 && (15-5) \\ &= \frac{0}{N_s} 100 = 0\% && \text{Ans.} \end{aligned}$$

An ac electric clock uses a synchronous motor to maintain the correct time (as long as the frequency of the ac supply remains constant).

**Starting Synchronous Motors**

A synchronous motor may be started rotating with a dc motor on a common shaft. After the motor is brought to synchronous speed, alternating current is applied to the stator windings. The dc starting motor now acts as a dc generator, which supplies dc field excitation for the rotor. The load then can be coupled to the motor. More often synchronous motors are started by means of a squirrel-cage winding embedded in the face of the rotor poles. The motor is then started as an induction motor and is brought to about 95 percent of synchronous speed. At the proper time, direct current is applied and the motor pulls into synchronism. The amount of torque needed to pull the motor into synchronism is called the *pull-in torque*.

**Effect of Loading Synchronous Motors**

In the synchronous motor the rotor is locked into step magnetically with the rotating magnetic field and must continue to rotate at synchronous speed for all loads. At no load the center lines of a pole of the rotating magnetic field and a dc field pole coincide (Fig. 15-9a). When load is added to the motor, there is a backward shift of the rotor pole relative to the stator pole (Fig. 15-9b). There is no change in speed. The angular displacement between the rotor and stator poles is called the torque angle  $\alpha$ .


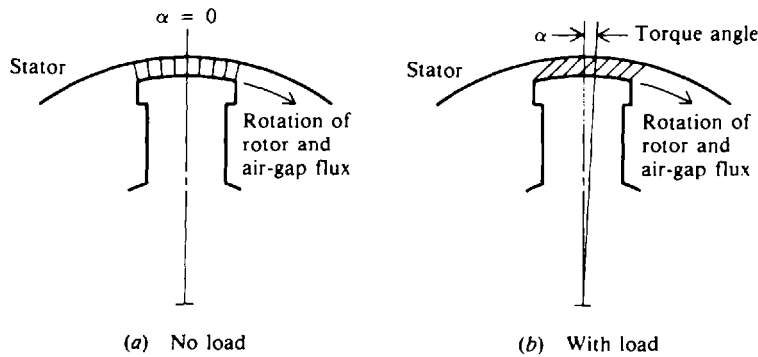


Fig. 15-9 Relative positions of a stator pole and a dc field pole

When a synchronous motor operates at no load (torque angle practically  $0^\circ$ ), the counter emf  $V_g$  is equal to the applied or terminal voltage  $V_t$  (neglecting motor losses) (Fig. 15-10a). With increasing loads and torque angles, the phase position of  $V_g$  changes with respect to  $V_t$ , which allows more stator current to flow to carry the additional load (Fig. 15-10b).  $V_t$  and  $V_g$  are no longer in direct opposition. Their resultant voltage  $V_r$  causes a current  $I$  to flow in the stator windings.  $I$  lags  $V_r$  by nearly  $90^\circ$  because of the high inductance of the stator windings.  $\theta$  is the phase angle between  $V_t$  and  $I$ . An increase in load results in a larger torque angle, which increases  $V_r$  and  $I$  (Fig. 15-10c).

If the mechanical load is too high, the rotor is pulled out of synchronism and comes to a stop. The maximum value of torque that a motor can develop without losing its synchronism is called its *pull-out torque*. If the synchronous motor has a squirrel-cage winding, it will continue to operate as an induction motor.

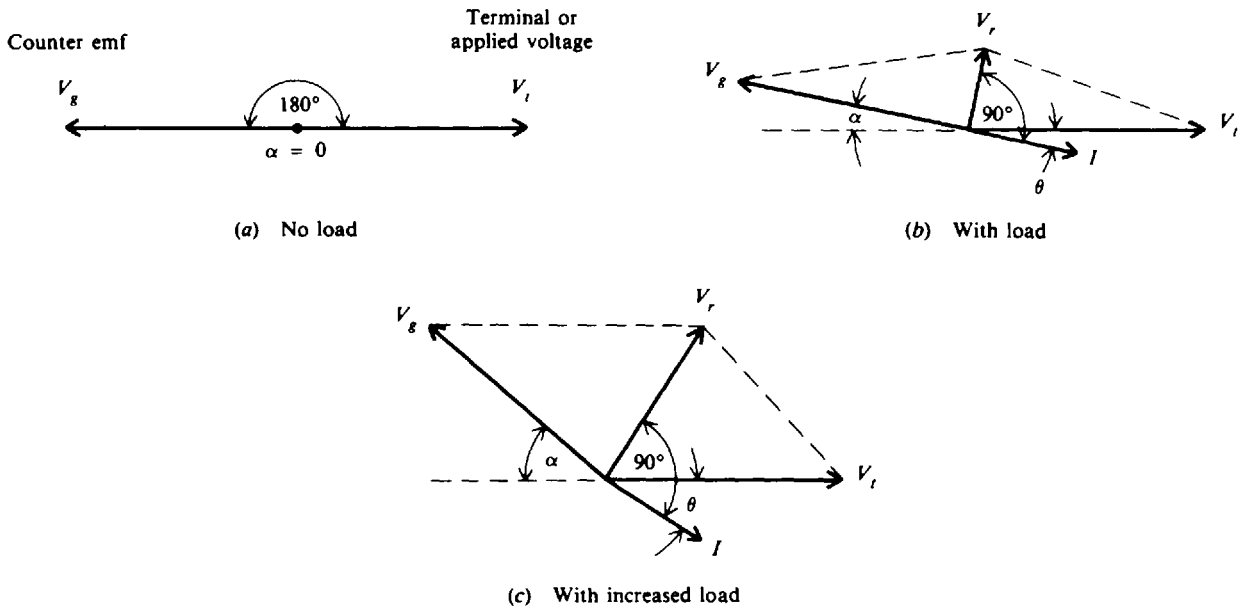

**Fig. 15-10** Phasor diagrams for a synchronous motor for three different load conditions with same dc field excitation

### Ratings and Efficiency

Synchronous-motor nameplate data include the same items found on ac generator nameplates, with the horsepower rating replacing the kilovoltampere rating.

The efficiency of synchronous motors is generally higher than that of induction motors of the same horsepower and speed rating. The losses are the same as those of synchronous generators.


Synchronous motors are used for constant-speed power applications in sizes above 20 hp. A common application is driving air or gas compressors.

### Power Factor Correction with Synchronous Motors


An outstanding advantage of a synchronous motor is that it operates at unity or leading power factor (PF). By varying the strength of the dc field, the overall power factor of a synchronous motor can be adjusted over a considerable range. Thus the motor can be made to appear as a leading load across the line. If an electrical system is operating at a lagging power factor, synchronous motors connected across the line and adjusted for leading PF can improve (that is, raise) the system PF. Any improvement in PF increases supply capacity to the load, raises efficiency, and in general improves the operating characteristics of the system.

### Field Excitation Used to Change Power Factor of Motor

For a constant mechanical load, the PF of a synchronous motor may be varied from a leading value to a lagging value by adjusting its dc field excitation (Fig. 15-11). Field excitation is adjusted so that  $PF = 1$  (Fig. 15-11a). At the same load, when the field excitation is increased, the counter emf  $V_g$  increases. This results in a change in phase between stator current  $I$  and terminal voltage  $V_t$  so that the motor operates at a leading PF (Fig. 15-11b). If the field excitation is reduced below the value represented (Fig. 15-11a), the motor operates at a lagging PF (Fig. 15-11c). An example of a V curve for a synchronous motor, obtained from a manufacturer, shows how stator current varies at a constant load with rotor field excitation (Fig. 15-12). Power factor may also be read when the field current is varied.

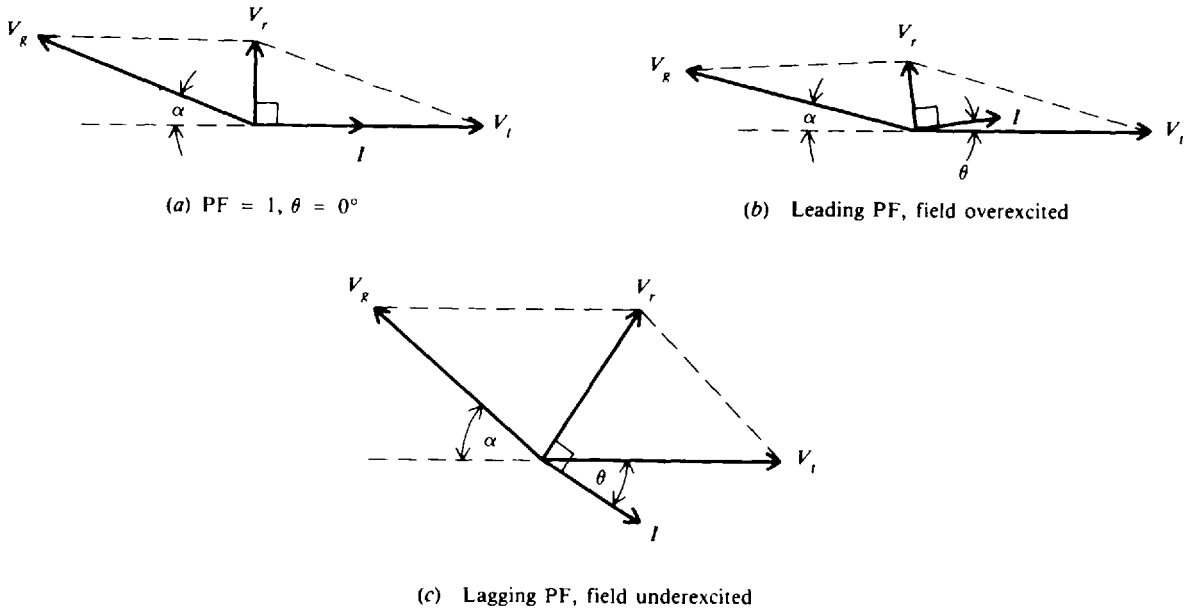

**Fig. 15-11** Phasor diagrams of a synchronous motor with a constant load but different amounts of field excitation

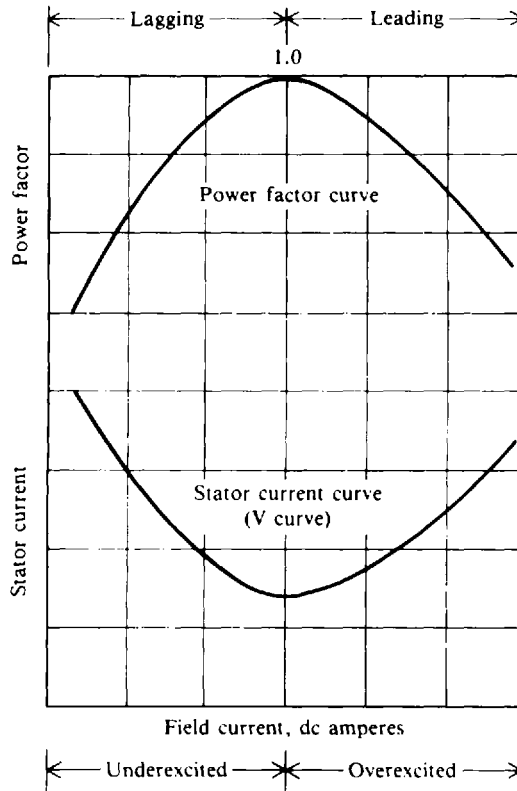

**Fig. 15-12** Variation of stator current and synchronous motor PF with varying dc field excitation at a constant load




**Example 15.7** The load of an industrial plant is 400 kVA at a PF of 75 percent lagging. What must be the PF of the added 100-kW load of a synchronous motor if it improved the overall plant PF to 100 percent?


For PF = 1, the net reactive power of the plant must be equal to zero.

**Step 1.** Find the initial reactive power of the plant (Fig. 15-13a, and b).
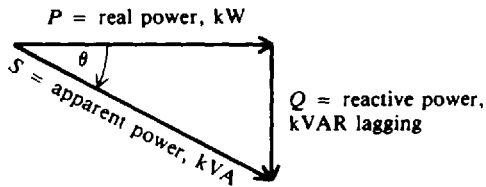
$$\begin{aligned} \text{PF} &= \cos \theta = 0.75 \quad \text{given} \\ \theta &= \arccos 0.75 = 41.4^\circ \quad P = S \cos \theta = 400(0.75) = 300 \text{ kW} \\ Q &= S \sin \theta = 400 \sin 41.4^\circ = 264.5 \text{ kVAR lagging} \end{aligned}$$




(a) General power triangle

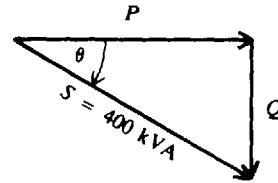


$$\text{PF} = \cos \theta = 0.75 \text{ lagging}$$

(b) Initial plant power triangle

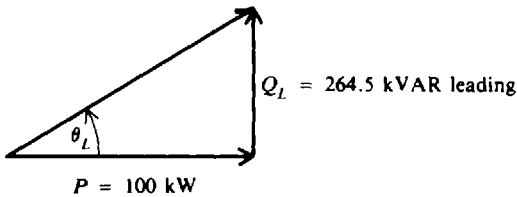

(c) Synchronous motor power triangle

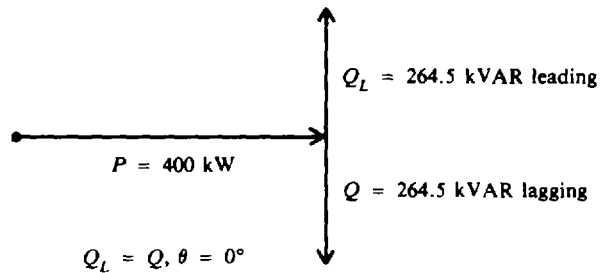

(d) Resultant plant power triangle with PF = 1

**Fig. 15-13** Power-triangle relationships

**Step 2.** Find the PF of the synchronous motor load (Fig. 15-13c). For a net PF = 1, the reactive power of the motor must equal the initial reactive power of the plant in the opposite direction. The  $Q$  of the plant (Step 1) is 264.5 kVAR lagging. So the  $Q_L$  of the added load must be 264.5 kVAR leading.

$$\theta_L = \arctan \frac{264.5}{100} = \arctan 2.64 = 69.3^\circ$$

$$\text{PF} = \cos \theta_L = \cos 69.3^\circ = 0.353 = 35.3\% \text{ leading} \quad \text{Ans.}$$

The resultant power triangle (Fig. 15-13d) shows a plant load of 400 kW (300 kW + 100 kW) at a PF of unity.

## SINGLE-PHASE MOTORS

Single-phase motors are so called because their field windings are connected directly to a single-phase source. Single-phase motors are classified as commutator, induction, or synchronous motors according to the method used to start them, as follows:

1. Commutator motor
  - (a) AC series motor
  - (b) Repulsion motor

2. Induction motor
  - (a) Split-phase motors
    - (1) Capacitor-start motor
    - (2) Capacitor motor
  - (b) Repulsion-start induction motor
  - (c) Shaded-pole motor
3. Synchronous motor

### Commutator Motor

#### AC Series Motor

When an ordinary dc series motor is connected to an ac supply, the current drawn by the motor is low due to the high series-field impedance. The result is low running torque. To reduce the field reactance to a minimum, ac series motors are built with as few turns as possible. Armature reaction is overcome by using compensating windings in the pole pieces.

The operating characteristics are similar to those of dc series motors. The speed increases to a high value with a decrease in load. The torque is high for high armature currents so that the motor has a good starting torque. AC series motors operate more efficiently at low frequencies. Some of the larger sizes used in railroad engines operate at 25 Hz or less. However, fractional horsepower sizes are designed to operate at 50 or 60 Hz.

#### Repulsion Motor

The repulsion motor has an armature and commutator similar to that of a dc motor. However, the brushes are not connected to the supply but are short-circuited (Fig. 15-14). The stator windings produce a current in the rotor windings by induction. This current produces magnetic poles in the rotor. The orientation of these poles is dependent on the position of the brushes. The interaction of the rotor field with the stator field creates the motor torque. The repulsion motor has a high starting torque and a high speed at light loads. It is used where heavy starting loads are expected.

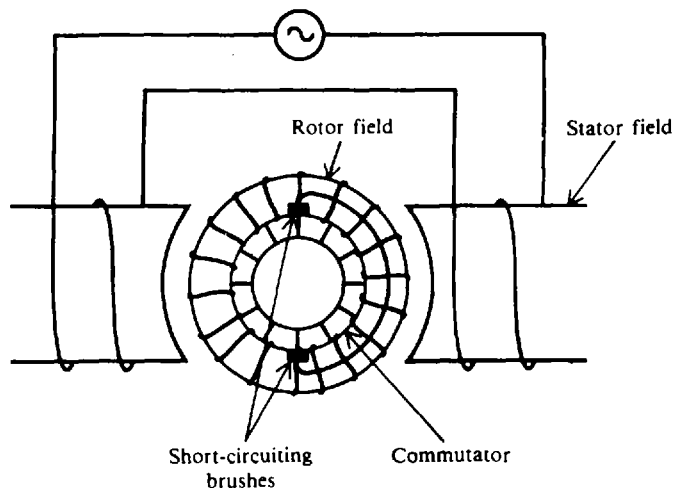


Fig. 15-14 Repulsion motor

### Induction Motor


A single-phase induction motor is not self-starting. The magnetic field set up in the stator by the ac power supply stays lined up in one direction. This magnetic field, though stationary, pulsates as the voltage sine wave does. This pulsating field induces a voltage in the rotor windings,

but the rotor field can only line up with the stator field. With these two fields in direct line, no torque is developed. It is necessary then to turn the rotor by some auxiliary device. Once the rotor is rotating with sufficient speed, the interaction between the rotor and stator fields will maintain rotation. The rotor will continue to increase in speed, trying to lock into synchronous speed. It finally will reach an equilibrium speed equal to the synchronous speed minus slip.

**Split-Phase Motor**

If two stator windings of unequal impedance are spaced 90 electrical degrees apart but connected in parallel to a single-phase source, the field produced will appear to rotate. This is the principle of *phase splitting*.


In the split-phase motor the starting winding has a higher resistance and lower reactance than the main winding (Fig. 15-15a). When the same voltage  $V_t$  is applied to both windings, the current in the main winding  $I_m$  lags behind the current in the starting winding  $I_s$  (Fig. 15-15b). The angle  $\phi$  between the main and starting windings is enough phase difference to provide a weak rotating magnetic field to produce a starting torque. When the motor reaches a predetermined speed, usually 70 to 80 percent of synchronous speed, a centrifugal switch mounted on the motor shaft opens, thereby disconnecting the starting winding.

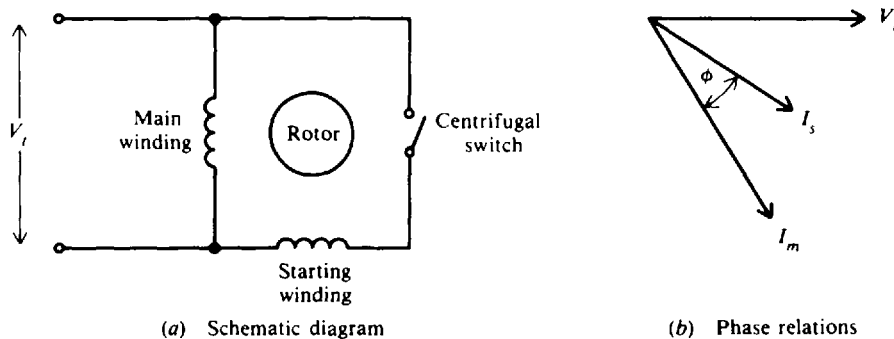


**Fig. 15-15** Split-phase motor

Because it has a low starting torque, this motor type is widely used for easily started loads. It is seldom used in sizes larger than  $\frac{1}{3}$  hp. Common applications include driving washing machines and woodworking tools.

**Capacitor-Start Motor.** By placing a capacitor in series with the starting winding of a split-phase motor (Fig. 15-15a), starting characteristics are improved. The current in the starting winding may be made to lead the voltage (Fig. 15-16).  $\phi$  may be made nearly  $90^\circ$ , resulting in a higher starting torque. This motor also uses a centrifugal switch to disconnect the starting winding. Thus the capacitor is in the circuit only during the starting period.

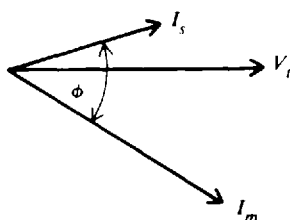

**Fig. 15-16** Phase relations in the capacitor-start motor

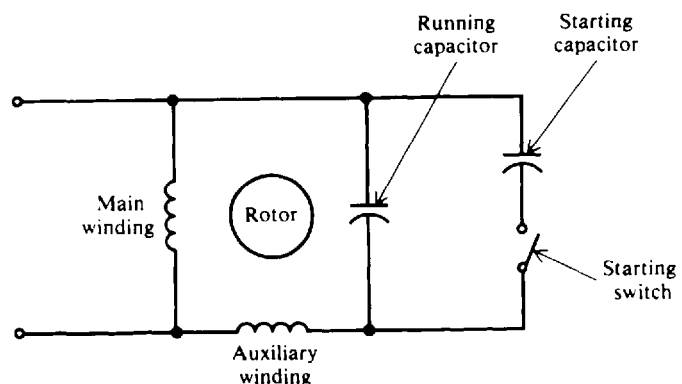

**Fig. 15-17** Capacitor motor


**Capacitor Motor.** The capacitor motor operates with an auxiliary winding and series capacitor permanently connected to the line (Fig. 15-17). The capacitance in series may be of one value for starting and another value for running. As the motor approaches synchronous speed, the centrifugal switch disconnects one section of the capacitor.

#### **Repulsion-Start Induction Motor**

Like a dc motor, the rotor of the repulsion-start induction motor has windings connected to a commutator. Starting brushes make contact with the commutator so the motor starts as a repulsion motor. As the motor nears full speed, a centrifugal device short-circuits all the commutator segments so that it operates as an induction motor. This type of motor is made in sizes ranging from  $\frac{1}{2}$  to 15 hp and is used in applications requiring a high starting torque.

#### **Shaded-Pole Motor**

A shaded pole is produced by a short-circuited coil wound around a part of each pole of a motor. The coil is usually a single band or strap of copper. The effect of the coil is to produce a small sweeping motion of the field flux from one side of the pole piece to the other as the field pulsates (Fig. 15-18). This slight shift in the magnetic field produces a small starting torque. Thus shaded-pole motors are self-starting. As the field in the pole piece increases, a current is induced in the shading coil. This current causes a magnetic field that opposes the main field. The main field therefore will concentrate on the opposite side of the pole pieces (Fig. 15-18a). As the field begins to decrease, the shading-coil field will aid the main field. The concentration of flux then moves to the other edge of the pole piece (Fig. 15-18b). This method of motor starting is used in very small motors, up to about  $\frac{1}{25}$  hp, for driving small fans, small appliances, and clocks.

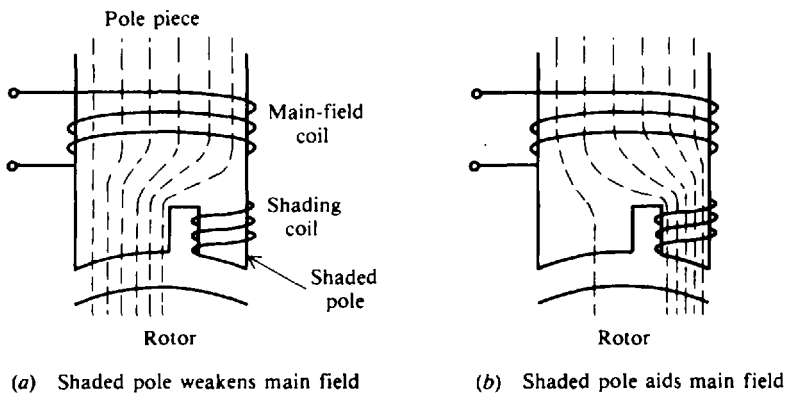

**Fig. 15-18** Action of the magnetic field in a shaded-pole motor

#### **Synchronous Motor**

Several types exist to drive electric clocks, phonograph turntables, and other devices requiring precise rotation. One type is called the Warren synchronous motor. It starts by the use of shading coils in the pole piece. The motor is brought up to synchronous speed from the effects of eddy currents flowing in the rotor iron and of hysteresis. Its principal use is in clocks and other timing devices.

**Example 15.8** List the type of field excitation (dc or ac) and whether the field is usually the stator or the rotor for each of the following: alternator, polyphase induction motor, synchronous motor.

The list is shown in the table below.


Device	Field Excitation	
	Input Field	Output Field
Alternator		
Rotating armature	DC (stator)	Rotor (ac output)
Stationary armature	DC (rotor)	Stator (ac output)
Polyphase induction motor	AC (stator)	
Synchronous motor	DC (rotor) AC (stator)	

**Example 15.9** Fill in the appropriate word to complete each of the following sentences.

- (a) The magnetic field of a single-phase motor does not appear to \_\_\_\_\_.
  - (b) Repulsion motors have \_\_\_\_\_ starting torques.
  - (c) Induction motors are classified by different \_\_\_\_\_ methods.
  - (d) \_\_\_\_\_ must exist so that the stator and rotor fields are not exactly lined up.
  - (e) Split-phase motors have \_\_\_\_\_ separate windings.
- (a) rotate (a three-phase field does appear to rotate), (b) high, (c) starting, (d) Slip, (e) two

### Solved Problems

**15.1** An alternator has a characteristic curve showing percentage of terminal voltage and percentage of full-load ampere output for three types of loading (Fig. 15-19). Calculate the percent regulation for the three types of loading.

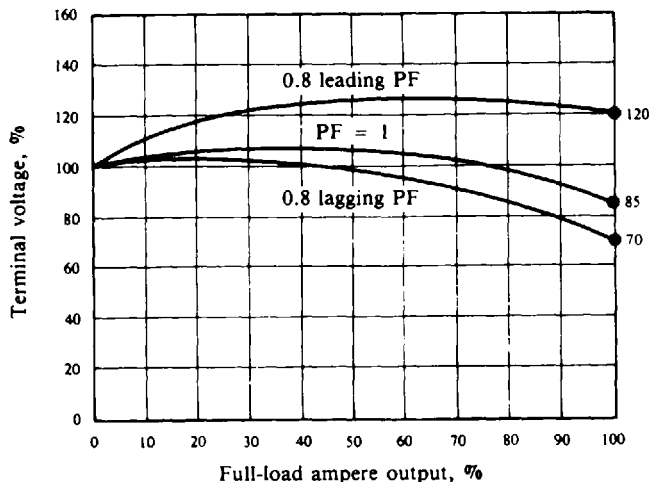

**Fig. 15-19** Effect of power factor on alternator output

When 100 percent rated current is delivered by the alternator, the full-load (FL) voltages are 85, 70, and 120 percent of the no-load (NL) values for PF = 1, 0.8 lagging, and 0.8 leading, respectively (Fig. 15-19).

$$\text{Voltage regulation} = \frac{\text{NL} - \text{FL}}{\text{FL}} \tag{15-2}$$

When PF = 1:

$$\text{Voltage regulation} = \frac{100 - 85}{85} = 0.176 = 17.6\% \quad \text{Ans.}$$

PF = 0.8 lagging:

$$\text{Voltage regulation} = \frac{100 - 70}{70} = 0.429 = 42.9\% \quad \text{Ans.}$$

PF = 0.8 leading:

$$\text{Voltage regulation} = \frac{100 - 120}{120} = -0.167 = -16.7\% \quad \text{Ans.}$$

The negative regulation indicates that the full-load voltage is greater than the no-load voltage.

**15.2 Draw phasor diagrams of an ac generator operating when PF = 1.0, 0.8 lagging, and 0.8 leading.**

Let  $IR$  and  $IX_L$  be voltage drops due to resistance and inductive reactance in the armature winding, respectively.

$$V_g = \text{generated emf} \quad V_t = \text{terminal voltage} \quad I = \text{armature current}$$

$V_g$  is the phasor sum of  $V_t$ , the  $IR$  drop which is in phase with  $I$ , and the  $IX_L$  drop which leads  $I$  by  $90^\circ$  (Fig. 15-20).  $V_g$  is not constant but varies with the amount of load and PF of the load. At lagging PF,  $V_g$  is lowered. The lower the PF in the lagging direction, the less  $V_g$ . At leading PF,  $V_g$  increases with load.

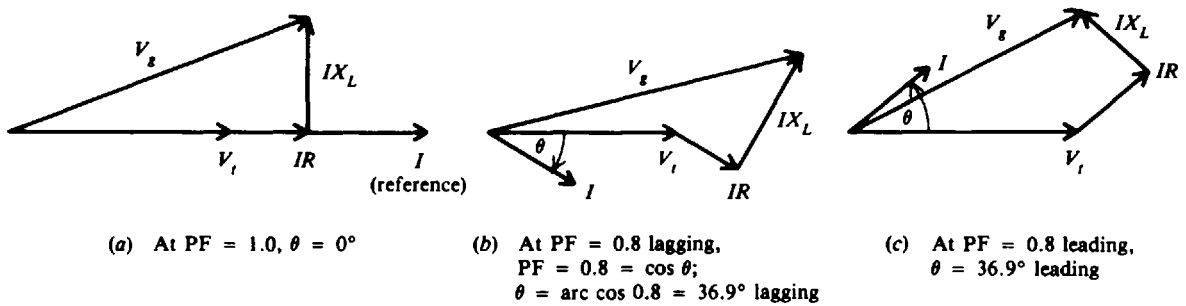


Fig. 15-20 Phasor diagrams of ac generator operating at three different load factors

**15.3 A diesel-driven 60-Hz synchronous generator produces 60 Hz when operated at 200 rpm. How many poles does it have?**

$$f = \frac{pn}{120} \tag{15-1}$$

from which

$$p = \frac{120f}{n} = \frac{120(60)}{200} = 36 \text{ poles} \quad \text{Ans.}$$

- 15.4 At what speed will a two-pole 25-Hz synchronous generator produce 25 Hz?

$$f = \frac{pn}{120} \quad (15-1)$$

from which 
$$n = \frac{120f}{p} = \frac{120(25)}{2} = 1500 \text{ rpm} \quad \text{Ans.}$$

- 15.5 An alternator has a voltage regulation of 10.0 percent. If the full-load voltage is 220 V, what is the no-load voltage?

$$\text{Voltage regulation} = \frac{NL - FL}{FL} \quad (15-2)$$

from which 
$$NL = FL(\text{voltage regulation} + 1) = 220(0.10 + 1) = 242 \text{ V} \quad \text{Ans.}$$

- 15.6 A four-pole 60-Hz induction motor has a full-load slip of 5 percent. What is the full-load rotor speed?

$$N_s = \frac{120f}{p} \quad (15-4)$$

$$= \frac{120(60)}{4} = 1800 \text{ rpm}$$

$$S = \frac{N_s - N_R}{N_s} \quad (15-5)$$

$$SN_s = N_s - N_R$$

$$N_R = N_s - SN_s = N_s(1 - S)$$

Then 
$$N_R = 1800(1 - 0.05) = 1800(0.95) = 1710 \text{ rpm} \quad \text{Ans.}$$

- 15.7 A squirrel-cage motor stator winding is wound for four poles. At full load, the motor operates at 1740 rpm with a slip speed of 60 rpm. What is the supply frequency?

$$\text{Slip} = N_s - N_R$$

$$N_s = N_R + \text{Slip} = 1740 + 60 = 1800 \text{ rpm}$$

$$N_s = \frac{120f}{p} \quad (15-4)$$

from which 
$$f = \frac{pN_s}{120} = \frac{4(1800)}{120} = 60 \text{ Hz} \quad \text{Ans.}$$

- 15.8 What is the rotor frequency of an eight-pole 60-Hz squirrel-cage motor operating at 850 rpm?

$$N_s = \frac{120f}{p} = \frac{120(60)}{8} = 900 \text{ rpm}$$

$$\text{Slip} = N_s - N_R = 900 - 850 = 50 \text{ rpm}$$

$$S = \frac{N_s - N_R}{N_s} \quad (15-5)$$

$$= \frac{50}{900} = 0.056$$

$$f_R = Sf_s \quad (15-6)$$

$$= 0.056(60) = 3.33 \text{ Hz} \quad \text{Ans.}$$

This means that a rotor conductor will have induced in it an emf with a frequency of 3.33 Hz.

- 15.9** How much larger is the rotor reactance of a squirrel-cage motor at start-up (with the rotor at a standstill) than it is when the motor operates at 4 percent slip?

$$\text{Rotor reactance } X_R = 2\pi f_R L_R$$

with  $L_R$  constant,

$$X_R \propto f_R \quad \text{so}$$

rotor reactance is directly proportional to rotor frequency.

At start-up, the speed of the motor  $N_R = 0$  so slip = 1.00. During motor operation slip = 0.04 (given), so

$$f_{R1} = S_1 f_s \tag{15-6}$$

$$f_{R2} = S_2 f_s$$

Dividing,

$$\frac{f_{R1}}{f_{R2}} = \frac{S_1}{S_2}$$

$$f_{R1} = \frac{S_1}{S_2} \times f_{R2} = \frac{1.00}{0.04} \times f_{R2} = 25f_{R2}$$

Since  $X_R \propto f_R$ , the rotor reactance at start is 25 times greater than that at 4 percent slip. Ans.

- 15.10** A motor-generator set used for frequency conversion has a 10-pole 25-Hz synchronous motor and a direct-connected 24-pole synchronous generator. What is the generator frequency?

Synchronous motor:

$$N_s = \frac{120f}{p} = \frac{120(25)}{10} = 300 \text{ rpm}$$

Synchronous generator:

$$f = \frac{pN_s}{120} = \frac{24(300)}{120} = 60 \text{ Hz} \quad \text{Ans.}$$


- 15.11** The load of an industrial plant is 400 kVA at a PF of 75 percent lagging. An additional motor load of 100 kW is needed. Find the new kilovoltampere load and the PF of the load, if the motor to be added is (a) an induction motor with a PF of 90 percent lagging, and (b) a synchronous motor with a PF of 80 percent leading.

The solution is simplified by drawing and solving a series of power triangles.

**Step 1.** Set up a power triangle for current industrial load (IL) (Fig. 15-21a).

$$P_{IL} = 400 \cos \theta = 400(0.75) = 300 \text{ kW}$$
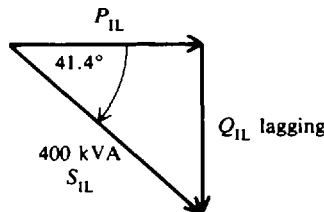
$$Q_{IL} = 400 \sin \theta = 400 \sin 41.4^\circ = 264.5 \text{ kVAR lagging}$$



Given: PF =  $\cos \theta = 0.75$  lagging  
 $\theta = 41.4^\circ$


(a) Industrial load

**Fig. 15-21a**




**Step 2.** Add induction motor (IM) to industrial load (Fig. 15-21b).
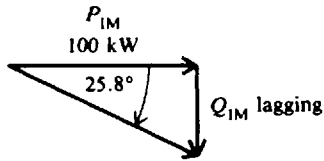
$$Q_{IM} = 100 \tan 25.8^\circ = 48.3 \text{ kVAR lagging}$$



Given:  $PF = \cos \theta = 0.9$  lagging  
 $\theta = 25.8^\circ$

(b) Induction motor

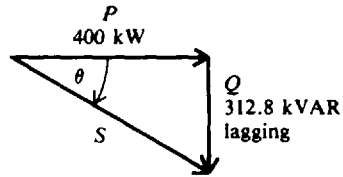

(c) Combined industrial load and induction motor

**Fig. 15-21b, c**

The resultant power triangle is as shown in Fig. 15-21c.

$$P = P_{IL} + P_{IM} = 300 + 100 = 400 \text{ kW}$$

$$Q = Q_{IL} + Q_{IM} = 264.5 + 48.3 = 312.8 \text{ kVAR lagging}$$


$$\theta = \arctan \frac{Q}{P} = \arctan \frac{312.8}{400} = 38^\circ$$

(a)  $PF = \cos \theta = \cos 38^\circ = 0.788 = 78.8\%$  lagging **Ans.**

$$S = \frac{P}{\cos \theta} = \frac{400}{\cos 38^\circ} = 508 \text{ kVA (3 significant figures)} \quad \text{Ans.}$$


**Step 3.** Add synchronous motor (SM) to industrial load (Fig. 15-21d).
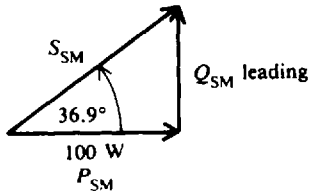
$$Q_{SM} = 100 \tan 36.9^\circ = 75.1 \text{ kVAR leading}$$



Given:  $PF = \cos \theta = 0.80$  leading  
 $\theta = 36.9^\circ$

(d) Synchronous motor

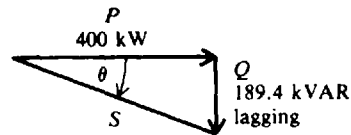

(e) Combined industrial load and synchronous motor

**Fig. 15-21d, e**

The resultant power triangle is as shown in Fig. 15-21e.

$$P = P_{IL} + P_{SM} = 300 + 100 = 400 \text{ kW}$$

$$Q = Q_{IL} - Q_{SM} = 264.5 - 75.1 = 189.4 \text{ kVAR lagging}$$

$$\theta = \arctan \frac{189.4}{400} = 25.3^\circ$$

(b)  $PF = \cos \theta = \cos 25.3^\circ = 0.904 = 90.4\%$  lagging **Ans.**

$$S = \frac{400}{\cos 25.3^\circ} = 442 \text{ kVA} \quad \text{Ans.}$$

15.12 A 220-V 50-A induction motor draws 10 kW of power (Fig. 15-22a). An 8-kVA synchronous motor is placed in parallel with it in order to adjust the PF to unity. What must be the PF of the synchronous motor?

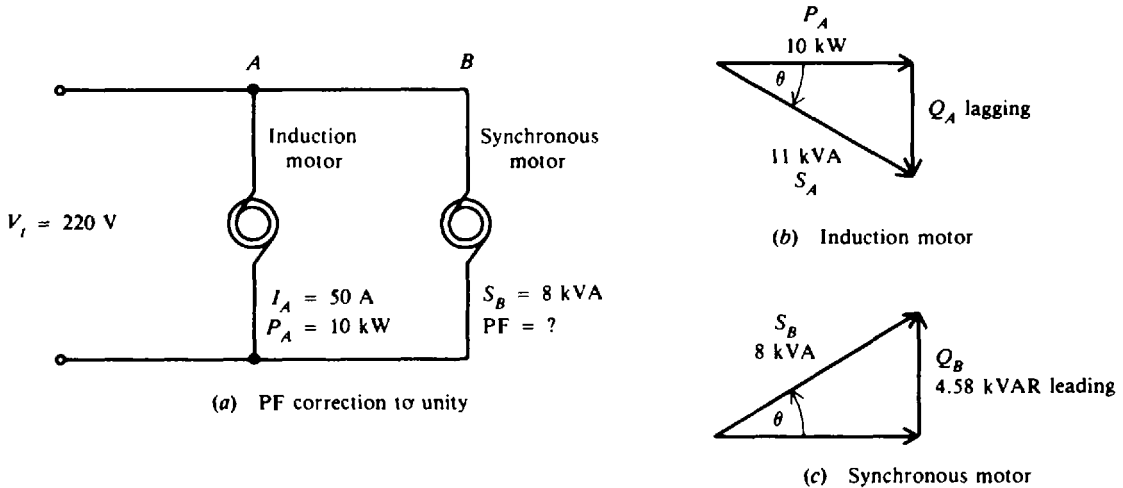


Fig. 15-22

Step 1. Set up a power triangle for the induction motor (Fig. 15-22b).

$$S_A = V_t I_A = 220(50) = 11\,000 \text{ VA} = 11 \text{ kVA}$$

$$\theta = \arccos \frac{P_A}{S_A} = \arccos \frac{10}{11} = 24.6^\circ$$

$$Q_A = S_A \sin \theta = 11 \sin 24.6^\circ = 4.58 \text{ kVAR lagging}$$

Step 2. Set up a power triangle for the synchronous motor (Fig. 15-22c). For the load PF = 1, the net number of kilovoltamperes reactive must be 0. Therefore, the reactive power of the synchronous motor is

$$Q_B = 4.58 \text{ kVAR leading} \quad \theta = \arcsin \frac{Q_B}{S_B} = \arcsin \frac{4.58}{8} = 34.9^\circ$$

$$\text{PF} = \cos \theta = \cos 34.9^\circ = 0.820 = 82.0\% \text{ leading} \quad \text{Ans.}$$

### Supplementary Problems

- 15.13 A 60-Hz alternator operates at 900 rpm. How many poles does it have? **Ans.** Eight poles
- 15.14 How many cycles are generated in 1 revolution of a 12-pole ac generator? How many revolutions per second (rps) must it make to generate a frequency of 60 Hz? How many revolutions per minute? **Ans.** 6 cycles; 10 rps; 600 rpm
- 15.15 (a) At what speed must a six-pole synchronous generator be driven to produce 25 Hz? (b) At what speed must a four-pole 60-Hz synchronous generator be driven to produce 60 Hz? **Ans.** (a) 500 rpm; (b) 1800 rpm
- 15.16 To produce 50 Hz with a two-pole rotating-coil alternator, what must be the prime-mover rpm? **Ans.** 3000 rpm

- 15.17 Find the regulation of an ac generator that has a full-load voltage of 2600 V and a no-load voltage of 3310 V at a PF of 80 percent lagging. Will the percent regulation at a PF of unity be higher than, lower than, or the same as at a PF of 80 percent lagging? *Ans.* 27.3%; lower than
- 15.18 When the load is light, is it more efficient to use one alternator operating at its rated capacity or to share the load between two alternators operating at less than their rated capacity? *Ans.* It is more efficient to use one alternator at rated capacity.
- 15.19 An alternator has a voltage regulation of 10.0 percent. If the no-load voltage is 220 V, what is the full-load voltage? *Ans.* 220 V
- 15.20 A fully loaded 10-hp electric motor is driving a 120-V ac output alternator delivering 6.5 kW to a remote lighting system. If the transmission-line losses are 300 W, what is the approximate loss in the alternator? What is the efficiency of the alternator? *Ans.* 660 W; Eff = 91.2%
- 15.21 A 440-V alternator operating from a 30-hp prime mover turning at full capacity produces 20 kW into a load. Find the efficiency of the alternator. *Ans.* Eff = 89.4%
- 15.22 A 5-kW alternator is known to be 92 percent efficient when it is at full load. What is the power requirement in horsepower for the prime mover? *Ans.* 7.3 hp
- 15.23 Find the synchronous speed of a 60-Hz motor that has an eight-pole stator winding. *Ans.* 900 rpm
- 15.24 Make a table showing the synchronous speeds of 2-, 4-, 6-, 8-, and 12-pole induction motors for frequencies of 25, 50, and 60 Hz.

*Ans.*

$p$	$n, \text{rpm}$		
	$f = 25 \text{ Hz}$	$f = 50 \text{ Hz}$	$f = 60 \text{ Hz}$
2	1500	3000	3600
4	750	1500	1800
6	500	1000	1200
8	375	750	900
12	250	500	600

- 15.25 A six-pole 60-Hz induction motor has a full-load slip of 4 percent. Find the rotor speed at full load. *Ans.* 1152 rpm
- 15.26 What is the rotor frequency of a six-pole 60-Hz squirrel-cage motor operating at 1130 rpm? *Ans.* 3.5 Hz
- 15.27 The three-phase induction motors driving an aircraft carrier have stators that may be connected to either 22 or 44 poles. The frequency of the supply may be varied from 20 to 65 Hz. What are the maximum and minimum speeds available from the motors? *Ans.* Maximum speed, 354.5 rpm; minimum speed, 54.5 rpm
- 15.28 How much greater is the rotor reactance of an induction motor at start-up than it is when operating at 5 percent slip? *Ans.* 20 times greater
- 15.29 What is the speed and speed regulation of a 30-pole 60-Hz 440-V synchronous motor? *Ans.* 240 rpm; 0.0%

- 15.30** The propulsion motors used in a naval vessel are rated 5900 hp, three-phase, 2400 V, 62.5 Hz, and 139 rpm. How many poles do they have? The speed of these motors may be changed by varying the supply frequency between 16 and 62.5 Hz. What are the maximum and minimum speeds?  
*Ans.* 54 poles; maximum speed, 139 rpm; minimum speed, 35.6 rpm
- 15.31** A transmission line delivers a load of 7500 kVA at a PF of 70 percent lagging. If a synchronous condenser is to be located at the end of the line to improve the load power factor to 100 percent, how many kilovoltamperes must it draw from the line. Assume the condenser is 100 percent reactive.  
*Ans.* 5360 kVA
- 15.32** A 440-V line delivers 15-kVA to a load at a PF of 75 percent lagging. To what PF should a 10-kVA synchronous motor be adjusted in order to raise the PF to unity when connected in parallel?  
*Ans.* PF = 12.6% leading
- 15.33** A 220-V 20-A induction motor draws 3 kW of power. A 4-kVA synchronous motor is placed in parallel to adjust the PF to unity. What must be the PF of the synchronous motor?  
*Ans.* PF = 59.3% leading
- 15.34** A 30-kW induction motor operates at a PF of 80 percent lagging. In parallel with it is a 50-kW induction motor operating at a PF of 90 percent lagging. (a) Find the new kilovoltampere load and PF of the load. (b) Find the PF adjustment which must be made on a 20-kW synchronous motor in parallel with the two induction motors in order to raise the PF of the line to unity.  
*Ans.* (a) 92.6 kVA, PF = 86.3% lagging; (b) PF = 39.4% leading
- 15.35** A synchronous motor which has an input of 500 kW is added to a system which has an existing load of 800 kW at a PF of 80 percent lagging. What will be the new system kilowatt load, kilovoltampere load, and PF if the new motor is operated at a PF of (a) 85 percent lagging, (b) 100 percent, and (c) 85 percent leading?  
*Ans.* (a) 1300 kW, 1590 kVA, 81.9% lagging; (b) 1300 kW, 1430 kVA, 90.8% lagging; (c) 1300 kW, 1320 kVA, 97.6% lagging
- 15.36** When is a synchronous motor said to be (a) overexcited, (b) underexcited?  
*Ans.* (a) Operates at leading PF (field excitation greater than that for PF = 1); (b) Operates at lagging PF (field excitation less than that for PF = 1). (See Fig. 15.12.)
- 15.37** For a constant field excitation, what is the effect on a synchronous motor with a lagging PF if the load is increased? *Ans.* Phase angle increases in lagging direction so PF becomes less.
- 15.38** What is meant by (a) pull-in torque, and (b) pull-out torque for a synchronous motor?  
*Ans.* (a) Torque value to pull the motor into synchronous speed; (b) Maximum torque developed without losing synchronous speed (stalling).
- 15.39** Why is a centrifugal switch used in a split-phase motor?  
*Ans.* Starting winding is designed only to help develop starting torque. Once the motor approaches running speed, it is no longer needed. Starting windings are usually wound with lighter-gauge wire, which could overheat and burn out if not disconnected.
- 15.40** How does a shaded-pole motor create a rotating magnetic field?  
*Ans.* Short-circuited coil on one edge of pole piece produces a field that first weakens and then aids the main field.

## Transformers

### IDEAL TRANSFORMER CHARACTERISTICS

The basic transformer consists of two coils electrically insulated from each other and wound upon a common core (Fig. 16-1). Magnetic coupling is used to transfer electric energy from one coil to another. The coil which *receives* energy from an ac source is called the *primary*. The coil which *delivers* energy to an ac load is called the *secondary*. The core of transformers used at low frequencies is generally made of magnetic material, usually sheet steel. Cores of transformers used at higher frequencies are made of powdered iron and ceramics, or nonmagnetic materials. Some coils are simply wound on nonmagnetic hollow forms such as cardboard or plastic so that the core material is actually air.

If a transformer is assumed to be operating under an ideal or perfect condition, the transfer of energy from one voltage to another is accompanied by no losses.

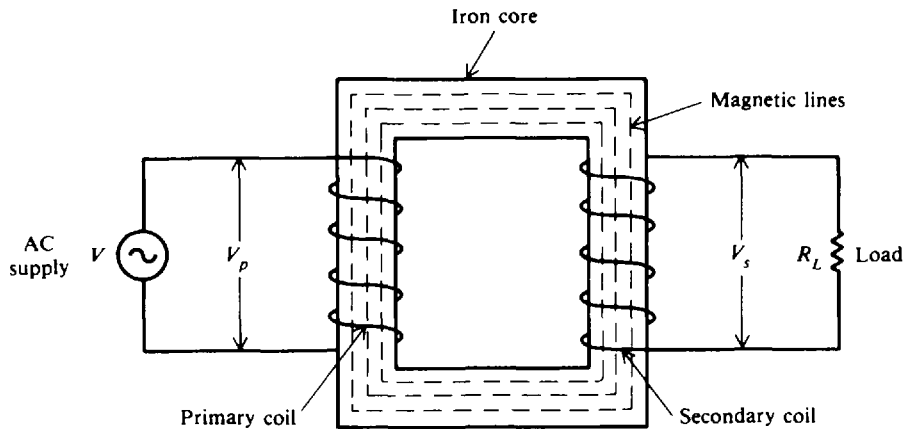


Fig. 16-1 Simple diagram of a transformer

### Voltage Ratio

The voltage on the coils of a transformer is directly proportional to the number of turns on the coils. This relationship is expressed by the formula

$$\frac{V_p}{V_s} = \frac{N_p}{N_s} \quad (16-1)$$

where  $V_p$  = voltage on primary coil, V  
 $V_s$  = voltage on secondary coil, V  
 $N_p$  = number of turns on primary coil  
 $N_s$  = number of turns on secondary coil

The ratio  $V_p/V_s$  is called the *voltage ratio* (VR). The ratio  $N_p/N_s$  is called the *turns ratio* (TR). By substituting these terms into Eq. (16-1), we obtain an equivalent formula

$$\text{VR} = \text{TR} \quad (16-2)$$


A voltage ratio of 1:4 (read as 1 to 4) means that for each volt on the transformer primary, there is 4 V on the secondary. When the secondary voltage is greater than the primary voltage, the transformer is called a *step-up* transformer. A voltage ratio of 4:1 means that for each 4 V on the primary, there is only 1 V on the secondary. When the secondary voltage is less than the primary voltage, the transformer is called a *step-down* transformer.

**Example 16.1** A filament transformer (Fig. 16-2) reduces the 120 V in the primary to 8 V on the secondary. If there are 150 turns on the primary and 10 turns on the secondary, find the voltage ratio and turns ratio.

$$VR = \frac{V_p}{V_s} = \frac{120}{8} = \frac{15}{1} = 15:1 \quad \text{Ans.}$$

$$TR = \frac{N_p}{N_s} = \frac{150}{15} = \frac{15}{1} = 15:1 \quad \text{Ans.}$$

Note that  $VR = TR$  [Eq. (16-2)].

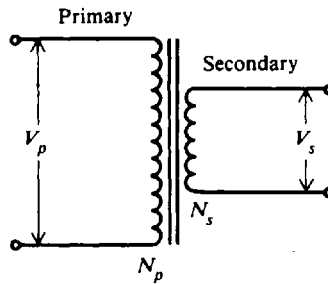

$$V_p = 120 \text{ V} \quad V_s = 8 \text{ V}$$

$$N_p = 150 \text{ turns} \quad N_s = 10 \text{ turns}$$

**Fig. 16-2** Filament transformer

**Example 16.2** An iron-core transformer operating from a 120-V line has 500 turns in the primary and 100 turns in the secondary. Find the secondary voltage.

$$\frac{V_p}{V_s} = \frac{N_p}{N_s} \tag{16-1}$$

Solve for  $V_s$  and substitute known values.

$$V_s = \frac{N_s}{N_p} V_p = \frac{100}{500} 120 = 24 \text{ V} \quad \text{Ans.}$$

**Example 16.3** A power transformer has a turns ratio of 1:5. If the secondary coil has 1000 turns and the secondary voltage is 30 V, find the voltage ratio, the primary voltage, and the number of primary turns.

$$VR = TR = 1:5 \quad \text{Ans.} \tag{16-2}$$

$$\frac{V_p}{V_s} = VR = 1:5 = \frac{1}{5}$$

$$V_p = \frac{1}{5} V_s = \frac{30}{5} = 6 \text{ V} \quad \text{Ans.}$$

$$TR = \frac{N_p}{N_s} = \frac{1}{5}$$

$$N_p = \frac{1}{5} N_s = \frac{1000}{5} = 200 \text{ turns} \quad \text{Ans.}$$

**Current Ratio**

The current in the coils of a transformer is inversely proportional to the voltage in the coils. This relationship is expressed by the equation

$$\frac{V_p}{V_s} = \frac{I_s}{I_p} \tag{16-3}$$

where  $I_p$  = current in primary coil, A  
 $I_s$  = current in secondary coil, A

From Eq. (16-1) we may substitute  $N_p/N_s$  for  $V_p/V_s$ , so we have

$$\frac{N_p}{N_s} = \frac{I_s}{I_p} \quad (16-4)$$

**Example 16.4** Derive the current-ratio equation  $V_p/V_s = I_s/I_p$ .

For an ideal transformer, the power input to the primary is equal to the power output of the secondary. Thus, an ideal transformer is assumed to operate at an efficiency of 100 percent. Therefore,

Power input = power output

$$P_p = P_s$$

Power input =  $P_p = V_p I_p$

Power output =  $P_s = V_s I_s$

Substituting for  $P_p$  and  $P_s$ ,

$$V_p I_p = V_s I_s$$

from which

$$\frac{V_p}{V_s} = \frac{I_s}{I_p} \quad \text{Ans.}$$

**Example 16.5** When the primary winding of an iron-core transformer is operated at 120 V, the current in the winding is 2 A. Find the current in the secondary winding load if the voltage is stepped up to 600 V.

$$\frac{V_p}{V_s} = \frac{I_s}{I_p} \quad (16-3)$$

Solve for  $I_s$  and substitute known values.

$$I_s = \frac{V_p}{V_s} I_p = \frac{120}{600} 2 = 0.4 \text{ A} \quad \text{Ans.}$$

**Example 16.6** A bell transformer with 240 turns on the primary and 30 turns on the secondary draws 0.3 A from a 120-V line. Find the secondary current.

$$\frac{N_p}{N_s} = \frac{I_s}{I_p} \quad (16-4)$$

Solve for  $I_s$  and substitute known values.

$$I_s = \frac{N_p}{N_s} I_p = \frac{240}{30} (0.3) = 2.4 \text{ A} \quad \text{Ans.}$$

### Efficiency

The efficiency of a transformer is equal to the ratio of the power output of the secondary winding to the power input of the primary winding. An ideal transformer is 100 percent efficient because it delivers all the energy it receives. Because of core and copper losses, the efficiency of even the best practical transformer is less than 100 percent. Expressed as an equation,

$$\text{Eff} = \frac{\text{power output}}{\text{power input}} = \frac{P_s}{P_p} \quad (16-5)$$

where Eff = efficiency

$P_s$  = power output from secondary, W

$P_p$  = power input to primary, W

**Example 16.7** What is the efficiency of a transformer if it draws 900 W and delivers 600 W?

$$\begin{aligned} \text{Eff} &= \frac{P_s}{P_p} && (16-5) \\ &= \frac{600}{900} = 0.667 = 66.7\% && \text{Ans.} \end{aligned}$$

**Example 16.8** A transformer is 90 percent efficient. If it delivers 198 W from a 110-V line, find the power input and the primary current.

$$\text{Eff} = \frac{P_s}{P_p} \quad (16-5)$$

Solve for power input  $P_p$ .

$$P_p = \frac{P_s}{\text{Eff}} = \frac{198}{0.90} = 220 \text{ W} \quad \text{Ans.}$$

Write the power input formula.

$$P_p = V_p I_p$$

Solve for  $I_p$ .

$$I_p = \frac{P_p}{V_p} = \frac{220}{110} = 2 \text{ A} \quad \text{Ans.}$$

**Example 16.9** A transformer draws 160 W from a 120-V line and delivers 24 V at 5 A. Find its efficiency.

$$P_p = 160 \text{ W, given}$$

$$P_s = V_s I_s = 24(5) = 120 \text{ W}$$

Then

$$\text{Eff} = \frac{P_s}{P_p} = \frac{120}{160} = 0.75 = 75\% \quad \text{Ans.}$$

## TRANSFORMER RATINGS

Transformer capacity is rated in kilovoltamperes. Since power in an ac circuit depends on the power factor of the load and the current in the load, an output rating in kilowatts must specify the power factor.

**Example 16.10** What is the kilowatt output of a 5-kVA 2400/120-V transformer serving loads with the following power factors: (a) 100 percent, (b) 80 percent, and (c) 40 percent? What is the rated output current of the transformer?

Power output:

(a)  $P_s = \text{kVA} \times \text{PF} = 5(1.0) = 5 \text{ kW} \quad \text{Ans.}$

(b)  $P_s = 5(0.8) = 4 \text{ kW} \quad \text{Ans.}$

(c)  $P_s = 5(0.4) = 2 \text{ kW} \quad \text{Ans.}$

Current output:

$$P_s = I_s V_s$$

Solving for  $I_s$ ,

$$I_s = \frac{P_s}{V_s} = \frac{5000}{120} = 41.7 \text{ A} \quad \text{Ans.}$$

Since rated current is determined by the rated kilovoltamperage, the full-load current of 41.7 A is supplied by the transformer at the three different PFs even though the kilowatt output is different for each case.



### IMPEDANCE RATIO

A maximum amount of power is transferred from one circuit to another when the impedances of the two circuits are equal or *matched*. If the two circuits have unequal impedances, a coupling transformer may be used as an impedance-matching device between the two circuits. By constructing the transformer's winding so that it has a definite turns ratio, the transformer can perform any impedance-matching function. The turns ratio establishes the proper relationship between the ratio of the primary and secondary winding impedances. This relationship is expressed by the equation

$$\left(\frac{N_p}{N_s}\right)^2 = \frac{Z_p}{Z_s} \quad (16-6)$$

Taking the square root of both sides, we obtain

$$\frac{N_p}{N_s} = \sqrt{\frac{Z_p}{Z_s}} \quad (16-7)$$

where  $N_p$  = number of turns on primary  
 $N_s$  = number of turns on secondary  
 $Z_p$  = impedance of primary,  $\Omega$   
 $Z_s$  = impedance of secondary,  $\Omega$

**Example 16.11** Find the turns ratio of a transformer used to match a 14 400- $\Omega$  load to a 400- $\Omega$  load.

$$\begin{aligned} \frac{N_p}{N_s} &= \sqrt{\frac{Z_p}{Z_s}} && (16-7) \\ &= \sqrt{\frac{14\,400}{400}} = \sqrt{36} = \frac{6}{1} = 6:1 && \text{Ans.} \end{aligned}$$

**Example 16.12** Find the turns ratio of a transformer to match a 20- $\Omega$  load to a 72 000- $\Omega$  load.

Use Eq. (16-7).

$$\frac{N_p}{N_s} = \sqrt{\frac{Z_p}{Z_s}} = \sqrt{\frac{20}{72\,000}} = \sqrt{\frac{1}{3600}} = \frac{1}{60} = 1:60 \quad \text{Ans.}$$

**Example 16.13** The secondary load of a step-down transformer with a turns ratio of 5:1 is 900  $\Omega$ . Find the impedance of the primary.

$$\frac{Z_p}{Z_s} = \left(\frac{N_p}{N_s}\right)^2 \quad (16-6)$$

Solve for  $Z_p$  and substitute given values.

$$Z_p = \left(\frac{N_p}{N_s}\right)^2 Z_s = \left(\frac{5}{1}\right)^2 (900) = 22\,500 \, \Omega \quad \text{Ans.}$$

### AUTOTRANSFORMER

An autotransformer is a special type of power transformer. It consists of only one winding. By tapping, or connecting, at points along the length of the winding, different voltages may be obtained. The autotransformer (Fig. 16-3) has a single winding between terminals A and C. The winding is tapped and a wire brought out as terminal B. Winding AC is the primary while winding BC is the secondary. The simplicity of the autotransformer makes it economical and space-saving. However, it does not provide electrical isolation between primary and secondary circuits.

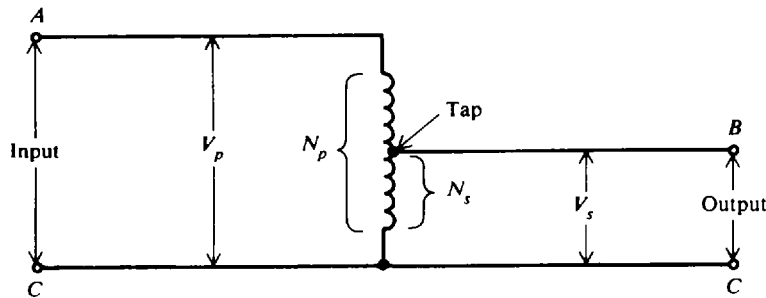


Fig. 16-3 Autotransformer schematic diagram

**Example 16.14** An autotransformer having 200 turns is connected to a 120-V line (Fig. 16-3). To obtain a 24-V output, find the number of turns of the secondary and the turn number at which the transformer should be tapped, counting from terminal A.

$$\frac{V_p}{V_s} = \frac{N_p}{N_s} \tag{16-1}$$

$$N_s = \frac{V_s}{V_p} N_p = \frac{24}{120} 200 = 40 \text{ turns} \quad \text{Ans.}$$

Since the secondary turns include primary, the B tap should be where the turn number is 160 (160 = 200 - 40). If tap B is made movable, the autotransformer becomes a variable transformer. As the tap is moved downward toward C, the secondary voltage decreases.

**TRANSFORMER LOSSES AND EFFICIENCY**

Actual transformers have copper losses and core losses. Copper loss is the power lost in the primary and secondary windings due to the ohmic resistance of the windings. Copper loss in watts is obtained by the formula

$$\text{Copper loss} = I_p^2 R_p + I_s^2 R_s \tag{16-8}$$

- where  $I_p$  = primary current, A
- $I_s$  = secondary current, A
- $R_p$  = resistance of the primary winding,  $\Omega$
- $R_s$  = resistance of the secondary winding,  $\Omega$

Core loss is caused by two factors: hysteresis loss and eddy-current loss. Hysteresis loss is the energy lost by reversing the magnetic field in the core as the magnetizing alternating current rises and falls and reverses direction. Eddy-current loss is the result of induced currents circulating in the core material.

Copper loss in both windings may be measured by means of a wattmeter. The wattmeter is placed in the primary circuit of the transformer while the secondary is short-circuited. The voltage applied to the primary is then increased until the rated full-load current is flowing in the short-circuited secondary. At that point the wattmeter will read the total copper loss. Core loss may be determined also by a wattmeter in the primary circuit by applying the rated voltage to the primary with the secondary circuit open.

The efficiency of an actual transformer is expressed as follows:

$$\begin{aligned} \text{Eff} &= \frac{\text{power output}}{\text{power input}} = \frac{P_s}{P_p} \tag{16-5} \\ &= \frac{\text{power output}}{\text{power output} + \text{copper loss} + \text{core loss}} \end{aligned}$$

and

$$\text{Eff} = \frac{V_s I_s \times \text{PF}}{(V_s I_s \times \text{PF}) + \text{copper loss} + \text{core loss}} \tag{16-9}$$

where PF = power factor of the load

**Example 16.15** A 10:1 step-down 5-kVA transformer has a full-load secondary current rating of 50 A. A short-circuit test for copper loss at a full load gives a wattmeter reading of 100 W. If the resistance of the primary winding is  $0.6 \Omega$ , find the resistance of the secondary winding and the power loss in the secondary. Use Eq. (16-8).

$$\text{Copper loss} = I_p^2 R_p + I_s^2 R_s = 100 \text{ W}$$

To find  $I_p$  at full load, write Eq. (16-4).

$$\frac{N_p}{N_s} = \frac{I_s}{I_p} \quad (16-4)$$

from which

$$I_p = \frac{N_s}{N_p} I_s = \frac{1}{10} 50 = 5 \text{ A}$$

Solve for  $R_s$  from the copper-loss equation above.

$$I_s^2 R_s = 100 - I_p^2 R_p$$

$$R_s = \frac{100 - I_p^2 R_p}{I_s^2} = \frac{100 - 5^2(0.6)}{50^2} = 0.034 \Omega \quad \text{Ans.}$$

$$\text{Power loss in secondary} = I_s^2 R_s = 50^2(0.034) = 85 \text{ W} \quad \text{Ans.}$$

or  $\text{Power loss in secondary} = 100 - I_p^2 R_p = 100 - 5^2(0.6) = 85 \text{ W} \quad \text{Ans.}$

**Example 16.16** An open-circuit test for core loss in the 5-kVA transformer of Example 16.15 gives a reading of 70 W. If the PF of the load is 85 percent, find the efficiency of the transformer at full load.

$$\text{Eff} = \frac{V_s I_s \times \text{PF}}{(V_s I_s \times \text{PF}) + \text{copper loss} + \text{core loss}} \quad (16-9)$$

$$V_s I_s = \text{transformer rating} = 5 \text{ kVA} = 5000 \text{ VA}$$


$$\text{PF} = 0.85 \quad \text{Copper loss} = 100 \text{ W} \quad \text{Core loss} = 70 \text{ W}$$

Substitute known values and solve.

$$\text{Eff} = \frac{5000(0.85)}{5000(0.85) + 100 + 70} = \frac{4250}{4420} = 0.962 = 96.2\% \quad \text{Ans.}$$

## NO-LOAD CONDITION

If the secondary winding of a transformer is left open-circuited (Fig. 16-4a), the primary current is very low and is referred to as the *no-load current*. The no-load current produces the magnetic flux and supplies the hysteresis and eddy-current losses in the core. Therefore, the no-load current  $I_E$  consists of two components: the magnetizing-current component  $I_M$  and the core-loss component  $I_H$ . The magnetizing current  $I_M$  lags the applied primary voltage  $V_p$  by  $90^\circ$ , while the core-loss component  $I_H$  is always in phase with  $V_p$  (Fig. 16-4b). Note also that the primary applied voltage  $V_p$  and the induced secondary voltage  $V_s$  are shown  $180^\circ$  out of phase with each other. Since in practice  $I_H$  is small in comparison with  $I_M$ , the magnetizing current  $I_M$  is very nearly equal to the total no-load current  $I_E$ .  $I_E$  is also called the *exciting current*.

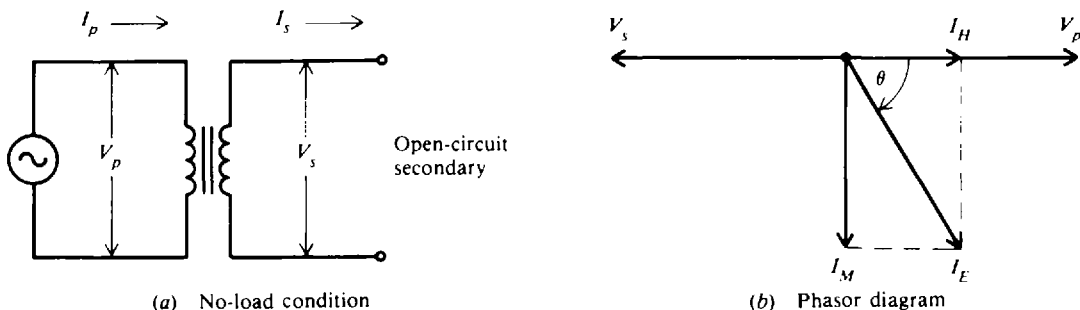

**Fig. 16-4** Iron-core transformer with the secondary open-circuited

**Example 16.17** When the secondary of a 120/240-V transformer is open, the primary current is 0.3 A at a PF of 20 percent. The transformer is rated at 4 kVA. Find (a) the full-load current  $I_p$ , (b) the no-load exciting current  $I_E$ , (c) the core-loss current  $I_H$ , and (d) the magnetizing current  $I_M$ . (e) Determine the percentages of each current with respect to full-load current. (f) Draw the phasor diagram.

(a) Full-load current =  $\frac{\text{transformer kVA rating}}{\text{primary voltage}}$

$$I_p = \frac{4000}{120} = 33.3 \text{ A} \quad \text{Ans.}$$

(b) The primary current measured at no load (secondary open) is the exciting current  $I_E$ . Thus,

$$I_E = 0.3 \text{ A} \quad \text{Ans.}$$

(c) From Fig. 16-4b,

$$I_H = I_E \cos \theta = I_E \times \text{PF} = 0.3(0.2) = 0.06 \text{ A} \quad \text{Ans.}$$

(d) From Fig. 16-4b,

$$I_M = I_E \sin \theta$$

$$\theta = \arccos 0.2 = 78.5^\circ$$

Then  $I_M = 0.3 \sin 78.5^\circ = 0.3(0.980) = 0.294 \text{ A} \quad \text{Ans.}$

(e) Percent no-load primary current (exciting current) to full-load primary current:

$$\frac{0.3}{33.3} = 0.0090 = 0.90\% \quad \text{Ans.}$$

Percent core-loss current to full-load current:


$$\frac{0.06}{33.3} = 0.0018 = 0.18\% \quad \text{Ans.}$$

Percent magnetizing current to full-load current:

$$\frac{0.294}{33.3} = 0.0088 = 0.88\% \quad \text{Ans.}$$

Notice that the magnetizing current (0.294 A) has nearly the same values as the no-load primary current (0.3 A).

(f) Phasor diagram: See Fig. 16-5.

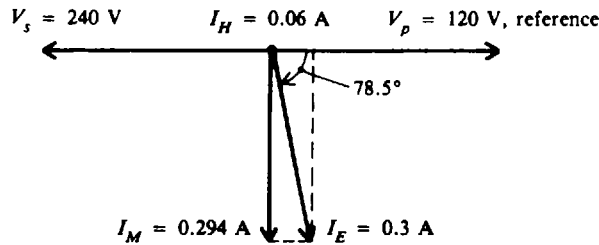

**Fig. 16-5** Phasor diagram

**COIL POLARITY**

The symbol for a transformer gives no indication of the phase of the voltage across the secondary since the phase of that voltage actually depends on the direction of the windings around the core. To solve this problem, polarity dots are used to indicate the phase of primary and secondary signals. The voltages are either in phase (Fig. 16-6a) or 180° out of phase with respect to the primary voltage (Fig. 16-6b).

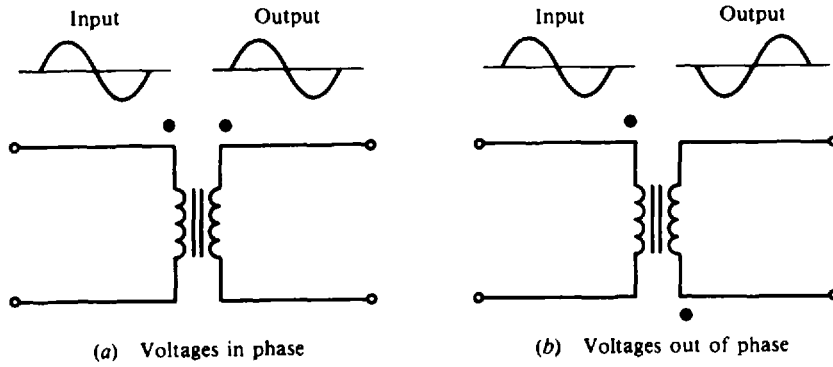


Fig. 16-6 Polarity notation of transformer coils

### Solved Problems

16.1 A power transformer is used to couple electric energy from a power-supply line to one or more components of the system. In one type of power transformer (Fig. 16-7), there are three separate secondary windings, each designed for a different voltage output. The primary of the transformer is connected to a 120-V source of supply and has 100 turns. Find the number of turns on each secondary.

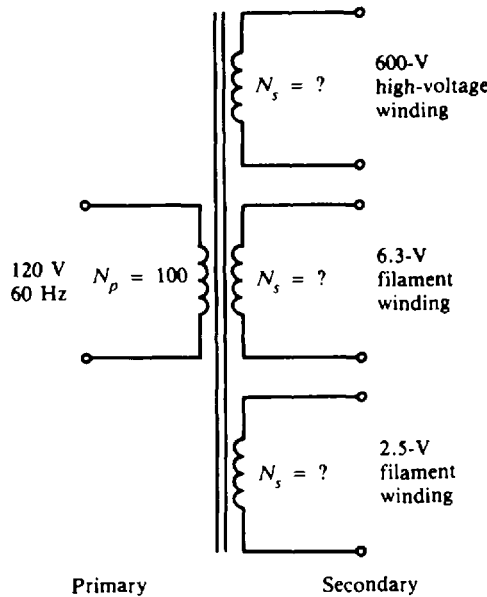


Fig. 16-7 Power transformer schematic diagram

Find  $N_s$  by using Eq. (16-1).

$$\frac{V_p}{V_s} = \frac{N_p}{N_s} \quad \text{from which} \quad N_s = \frac{V_s}{V_p} N_p$$

For the 600-V secondary:  $N_s = \frac{600}{120} 100 = 500 \text{ turns} \quad \text{Ans.}$

For the 6.3-V secondary:  $N_s = \frac{6.3}{120} 100 \approx 5 \text{ turns} \quad \text{Ans.}$

For the 2.5-V secondary:  $N_s = \frac{2.5}{120} 100 \approx 2 \text{ turns} \quad \text{Ans.}$

- 16.2** A transformer whose primary is connected to a 110-V source delivers 11 V. If the number of turns on the secondary is 20 turns, find the number of turns on the primary. How many extra turns must be added to the secondary if it must deliver 33 V?

Find  $N_p$  by using Eq. (16-1).

$$\frac{V_p}{V_s} = \frac{N_p}{N_s} \quad \text{from which} \quad N_p = \frac{V_p}{V_s} N_s = \frac{110}{11} (20) = 200 \text{ turns} \quad \text{Ans.}$$

$$\text{For } V_s = 33 \text{ V}, \quad N_s = \frac{V_s}{V_p} N_p = \frac{33}{110} 200 = 60 \text{ turns}$$

Hence 40 turns (60 - 20) must be added. *Ans.*

- 16.3** A step-down transformer with a turns ratio of 50 000:500 has its primary connected to a 20 000-V transmission line. If the secondary is connected to a 25- $\Omega$  load, find (a) the secondary voltage, (b) the secondary current, (c) the primary current, and (d) the power output.

$$\text{TR} = \frac{N_p}{N_s} = \frac{50\,000}{500} = \frac{100}{1}$$

$$(a) \quad \frac{N_p}{N_s} = \frac{V_p}{V_s} \quad (16-1)$$

$$\text{Then} \quad V_s = \frac{N_s}{N_p} V_p = \frac{1}{100} (20\,000) = 200 \text{ V} \quad \text{Ans.}$$

(b) By Ohm's law,

$$I_s = \frac{V_s}{R_L} = \frac{200}{25} = 8 \text{ A} \quad \text{Ans.}$$

$$(c) \quad \frac{V_p}{V_s} = \frac{I_s}{I_p} \quad (16-3)$$

$$\text{Then} \quad I_p = \frac{200}{20\,000} 8 = 0.08 \text{ A} \quad \text{Ans.}$$

$$(d) \quad P_s = V_s I_s = 200(8) = 1600 \text{ W} \quad \text{Ans.}$$

- 16.4** A 7:5 step-down transformer draws 2 A. Find the secondary current.

$$\text{TR} = \frac{N_p}{N_s} = \frac{7}{5}$$

$$\frac{N_p}{N_s} = \frac{I_s}{I_p} \quad (16-4)$$

$$\text{Then} \quad I_s = \frac{N_p}{N_s} I_p = \frac{7}{5} 2 = 2.8 \text{ A} \quad \text{Ans.}$$

- 16.5** A transformer draws 2.5 A at 110 V and delivers 7.5 A at 24 V to a load with a PF of 100 percent. Find the efficiency of the transformer.

$$\text{Power in} = P_p = V_p I_p = 110(2.5) = 275 \text{ W}$$

$$\text{Power out} = P_s = V_s I_s = 24(7.5) = 180 \text{ W}$$

$$\text{Eff} = \frac{P_s}{P_p} \quad (16-5)$$

$$= \frac{180}{275} = 0.655 = 65.5\% \quad \text{Ans.}$$

- 16.6 A transformer delivers 550 V at 80 mA at an efficiency of 90 percent. If the primary current is 0.8 A, find the power input in voltamperes and the primary voltage.

$$\text{Power out} = P_s = V_s I_s = 550(80 \times 10^{-3}) = 44 \text{ VA}$$

$$\text{Eff} = \frac{P_s}{P_p} \quad (16-5)$$

Then  $\text{Power in} = P_p = \frac{P_s}{\text{Eff}} = \frac{44}{0.9} = 48.9 \text{ VA} \quad \text{Ans.}$

Since the PF of the load is not specified, power is expressed in voltamperes. Also

$$P_p = V_p I_p \quad \text{so} \quad V_p = \frac{P_p}{I_p} = \frac{48.9}{0.8} = 61.1 \text{ V} \quad \text{Ans.}$$

- 16.7 The rating of a power-supply transformer that is to be operated from a 60-Hz 120-V power line may read as follows: 600 V CT (center tap) at 90 mA, 6.3 V at 3 A, 5 V at 2 A. Find the wattage rating of this transformer.

The wattage rating is the total power delivered at 100 percent PF. It is found by adding the power ratings of the individual secondary windings. The general formula to use is  $P_s = V_s I_s$ .

$$\text{At 600 V tap: } P_s = 600(90 \times 10^{-3}) = 54 \text{ W}$$

$$\text{At 6.3 V tap: } P_s = 6.3(3) = 18.9 \text{ W}$$

$$\text{At 5 V tap: } P_s = 5(2) = 10 \text{ W}$$

$$\text{Total power } P_T = 82.9 \text{ W} \quad \text{Ans.}$$

- 16.8 The step-down autotransformer at a power factor of unity is designed to deliver 240 V to a load of 5 kW (Fig. 16-8). The autotransformer's primary winding is connected to a 600-V source. Find the current in (a) the load, (b) the primary winding, and (c) the secondary winding.

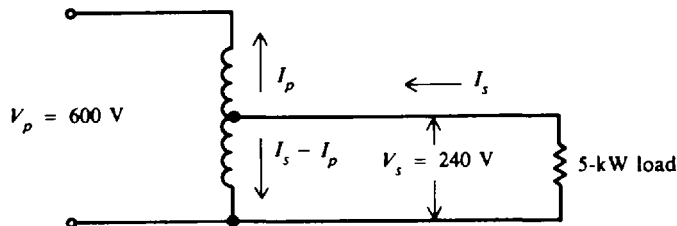


Fig. 16-8 Step-down autotransformer

- (a) Write  $P_s = V_s I_s$  ( $I_s$  in this case is the load current). So

$$I_s = \frac{P_s}{V_s} = \frac{5000}{240} = 20.8 \text{ A} \quad \text{Ans.}$$

- (b) At unity PF and 100 percent efficiency,  $V_p I_p = V_s I_s$ . So

$$I_p = \frac{V_s I_s}{V_p} = \frac{5000}{600} = 8.33 \text{ A} \quad \text{Ans.}$$

- (c) The current in the secondary winding is  $I_s - I_p$  by Kirchhoff's current law.

$$I_s - I_p = 20.8 - 8.3 = 12.5 \text{ A} \quad \text{Ans.}$$

- 16.9** A 60:1 output transformer is used to match an output transistor to a 4- $\Omega$  voice coil. Find the impedance of the output circuit.

$$\frac{Z_p}{Z_s} = \left(\frac{N_p}{N_s}\right)^2 \quad (16-6)$$

In this case the output transistor is in the primary circuit and the voice coil is in the secondary circuit.

$$Z_p = \left(\frac{N_p}{N_s}\right)^2 Z_s = \left(\frac{60}{1}\right)^2 (4) = 14\,400\ \Omega \quad \text{Ans.}$$

- 16.10** A 1:10 step-up transformer is used to match a 500- $\Omega$  line to a circuit. Find the impedance of the circuit.

$$\frac{Z_p}{Z_s} = \left(\frac{N_p}{N_s}\right)^2 \quad (16-6)$$

In this case the circuit is in the secondary.

$$Z_s = \left(\frac{N_s}{N_p}\right)^2 Z_p = \left(\frac{10}{1}\right)^2 (500) = 50\,000\ \Omega = 50\ \text{k}\Omega \quad \text{Ans.}$$

- 16.11** A 240/720-V 5-kVA transformer undergoes a short-circuit test for copper loss. At the start of the test, the primary voltage is varied until the ammeter across the secondary indicates rated full-load secondary current. The measured resistance of the primary winding is 0.05  $\Omega$  and that of the secondary winding is 1.5  $\Omega$ . Calculate the total copper loss.

**Step 1.** Calculate the copper loss in the secondary.

$$\text{Full-load secondary current } I_s = \frac{5000}{720} = 6.94\ \text{A}$$

$$\text{So} \quad I_s^2 R_s = (6.94)^2 (1.5) = 72.2\ \text{W}$$

**Step 2.** Calculate the copper loss in the primary.

$$\text{Full-load primary current } I_p = \frac{5000}{240} = 20.8\ \text{A}$$

$$\text{So} \quad I_p^2 R_p = (20.8)^2 (0.05) = 21.6\ \text{W}$$

**Step 3.** Calculate total copper loss. The total copper loss is the sum of the losses in both windings.

$$\begin{aligned} \text{Total copper loss} &= I_p^2 R_p + I_s^2 R_s \\ &= 21.6 + 72.2 = 93.8\ \text{W} \quad \text{Ans.} \end{aligned} \quad (16-8)$$

The wattmeter in the primary circuit should read 93.8 W.

- 16.12** On an open-circuit test for core loss in the 5-kVA transformer of Prob. 16.11, when the primary voltage is set at the rated voltage of 240 V, the wattmeter in the primary circuit indicates 80 W. If the power factor of the load is 0.8, find the efficiency of the transformer at full load.

Use the efficiency formula:

$$\begin{aligned} \text{Eff} &= \frac{V_s I_s \times \text{PF}}{(V_s I_s \times \text{PF}) + \text{copper loss} + \text{core loss}} \\ &= \frac{5000(0.8)}{5000(0.8) + 93.8 + 80} = \frac{4000}{4174} = 0.958 = 95.8\% \quad \text{Ans.} \end{aligned} \quad (16-9)$$



- 16.13 When the secondary of a power transformer is open, the no-load current in the primary is 0.4 A. If the power factor of the input primary circuit is 0.10, find the exciting current  $I_E$ , the core-loss current  $I_H$ , and the magnetizing current  $I_M$ .

The exciting current is the same as the no-load primary current.

So  $I_E = 0.4 \text{ A}$       Ans.

From the right-triangle relationships (see Fig. 16-9),

$$I_H = I_E \cos \theta = 0.4(0.10) = 0.04 \text{ A} \quad \text{Ans.}$$

$$\text{PF} = \cos \theta = 0.10 \quad \theta = \arccos 0.10 = 84.3^\circ$$

Then  $I_M = I_E \sin \theta = 0.4 \sin 84.3^\circ = 0.4 \text{ A}$       Ans.

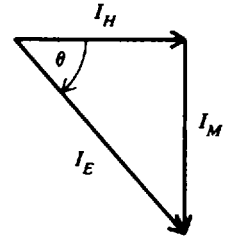


Fig. 16-9

- 16.14 The no-load current taken by a 110/220-V transformer is 0.7 A. The transformer is rated at 2.2 kVA. If the power factors of the primary and secondary circuits are equal, find the primary current when the secondary is supplying its rated 2.2 kVA to the load.

$$\text{Full-load secondary current } I_s = \frac{2200}{220} = 10 \text{ A}$$

Since the PFs for primary and secondary are equal at full load, the main component of load current in the primary is

$$I'_p = \frac{V_s}{V_p} I_s = \frac{220}{110} 10 = 2(10) = 20 \text{ A}$$

To  $I'_p$  we add directly the 0.7-A no-load current. So

$$I_p = 20 + 0.7 = 20.7 \text{ A} \quad \text{Ans.}$$

Because the no-load components  $I_H$  and  $I_M$  of the primary current are much less than the load-current component  $I'_p$ , the no-load current can be added arithmetically instead of vectorially to the total load-current.

- 16.15 Indicate the correct polarity dots for the secondary circuit (Fig. 16-10a).

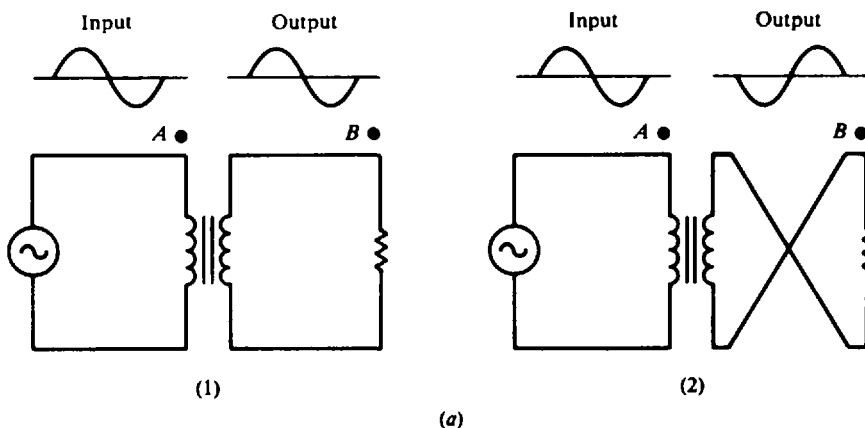


Fig. 16-10a Coil polarity

For diagram (1) (Fig. 16-10a), the voltage at point B with respect to ground has the same phase as the voltage at point A with respect to ground (Fig. 16-10b). For diagram (2) (Fig. 16-10a), the secondary windings are now reversed so that the output voltage at B is now 180° out of phase with the input voltage at A (Fig. 16-10c).

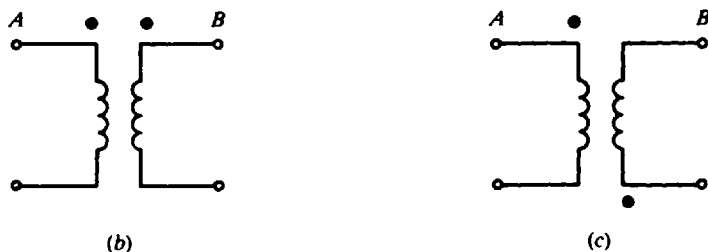



Fig. 16-10b, c

### Supplementary Problems

- 16.16** A bell transformer reduces the voltage from 110 to 11 V. If there are 20 turns in the secondary, find the number of turns on the primary and the turns ratio. *Ans.*  $N_p = 200$  turns; TR = 10:1
- 16.17** Find the voltage at the spark plugs connected to the secondary of a coil with 60 turns on the primary and 36 000 turns on the secondary, if the primary is connected to a 12-V alternator.  
*Ans.*  $V_s = 7200$  V
- 16.18** A coil with a primary winding of 80 turns must supply 4800 V. If the primary is connected to an 8-V source, find the number of turns on the secondary. *Ans.*  $N_s = 48\,000$  turns
- 16.19** The 110-V primary of a power transformer has 220 turns. Three secondaries are to deliver (a) 600 V, (b) 35 V, and (c) 12.5 V. Find the number of turns needed on each secondary.  
*Ans.* (a)  $N_s = 1200$  turns; (b)  $N_s = 70$  turns; (c)  $N_s = 25$  turns
- 16.20** The secondary coil of a transformer has 100 turns and the secondary voltage is 10 V. If the turns ratio is 18:1, find (a) the voltage ratio, (b) the primary voltage, and (c) the number of primary turns.  
*Ans.* (a) VR = 18:1; (b)  $V_p = 180$  V; (c)  $N_p = 1800$  turns
- 16.21** A step-down autotransformer with 55 turns is connected to a 110-V ac line. If a 28-V output is desired, find the secondary turns and the turn number to be tapped.  
*Ans.*  $N_s = 14$  turns; tap at turn 31
- 16.22** A 220/110-V step-down transformer in a stage-lighting circuit draws 12 A from the line. Find the current delivered. *Ans.*  $I_s = 24$  A
- 16.23** An ideal transformer with 2400 turns on the primary and 600 turns on the secondary draws 9.5 A at 100 percent PF from a 220-V line. Find  $I_s$ ,  $V_s$ , and  $P_s$ . *Ans.*  $I_s = 38$  A;  $V_s = 55$  V;  $P_s = 2090$  W
- 16.24** A transformer with 96 percent efficiency is connected to a 2000-V line. If it delivers 10 000 VA, find the power input  $P_p$  in voltamperes and the primary current  $I_p$ . *Ans.*  $P_p = 10\,417$  VA;  $I_p = 5.21$  A
- 16.25** A transformer with an efficiency of 85 percent delivers 650 V and 120 mA at 100 percent PF to a secondary load. The primary current is 0.6 A. Find the power input and the primary voltage.  
*Ans.*  $P_p = 91.8$  W;  $V_p = 153$  V


- 16.26** The three secondary coils of a power-supply transformer deliver 85 mA at 300 V, 1.4 A at 12.6 V, and 1.9 A at 2.5 V. Find the power delivered to the secondary loads. Find also the efficiency if the transformer draws 55 W from a 110-V line. (Assume unity PF in both primary and secondary.)  
*Ans.*  $P_s = 47.9 \text{ W}$ ;  $\text{Eff} = 87.1\%$
- 16.27** Find the current rating of each winding of a 100-kVA 2400/120-V 60-Hz transformer.  
*Ans.* Primary winding, 41.7 A; secondary winding, 833.3 A
- 16.28** Find the turns ratio of a transformer used to match a 50- $\Omega$  load to a 450- $\Omega$  line.     *Ans.*  $\text{TR} = 3:1$
- 16.29** Find the turns ratio of a transformer used to match a 30- $\Omega$  load to a 48 000- $\Omega$  load.  
*Ans.*  $\text{TR} = 1:40$
- 16.30** Find the turns ratio of the transformer needed to match a load of 4000  $\Omega$  to three 12- $\Omega$  speakers in parallel.     *Ans.*  $\text{TR} = 31.6:1 \approx 32:1$
- 16.31** A 1:18 step-up output transformer is used to match a microphone with a grid circuit impedance of 35 k $\Omega$ . Find the impedance of the microphone.     *Ans.*  $Z_p = 108 \Omega$
- 16.32** A 6:1 step-down transformer matches an input load to a secondary load of 800  $\Omega$ . Find the impedance of the input.     *Ans.*  $Z_p = 28.8 \text{ k}\Omega$
- 16.33** A step-up autotransformer requires 100 turns for its 120-V primary. To obtain an output of 300 V, find the number of turns that must be added to the primary.     *Ans.* 150 turns ( $N_s = 250$  turns)
- 16.34** A load of 12 kW at 480 V and 100 percent PF is to be supplied by a step-down autotransformer whose high-voltage winding is connected to a 1200-V source. Find the current in (a) the load, (b) the primary winding, and (c) the secondary winding.  
*Ans.* (a)  $I_s = 25 \text{ A}$ ; (b)  $I_p = 10 \text{ A}$ ; (c)  $I_s - I_p = 15 \text{ A}$
- 16.35** An autotransformer starter used to start an induction motor on a 440-V line applies 70 percent of line voltage to the motor during the starting period. If the motor current is 140 A at start-up, what is the current drawn from the line?     *Ans.* 98 A
- 16.36** A step-down 600/480-V autotransformer supplies a 10-kVA load. Find the primary and secondary line currents and the current in the winding common to both primary and secondary circuits.  
*Ans.*  $I_p = 16.7 \text{ A}$ ;  $I_s = 20.8 \text{ A}$ ;  $I_s - I_p = 4.1 \text{ A}$
- 16.37** A 5-kVA 480/120-V transformer is equipped with high-voltage taps so that it may be operated at 480, 456, or 432 V depending on the tap setting. Find the current in the high-voltage winding for each tap setting. The transformer supplies the rated kVA load at 120 V in each case.  
*Ans.* 10.4 A at 480 V; 11.0 A at 456 V; 11.6 A at 432 V
- 16.38** A transformer with 800 turns in its primary and 160 turns in its secondary is rated 10 kVA at 480 V. Find (a) the VR, (b) the primary voltage, (c) the rated full-load secondary current, and (d) the rated full-load primary current, disregarding the no-load current.  
*Ans.* (a) 5:1; (b) 2400 V; (c) 20.8 A; (d) 4.16 A
- 16.39** A 250-kVA 2400/480-V transformer has copper losses of 3760 W and core losses of 1060 W. What is the efficiency when the transformer is fully loaded at 0.8 PF?     *Ans.*  $\text{Eff} = 97.6\%$
- 16.40** An open-circuit test for core loss in a 240/720-V 10-kVA transformer gives a reading of 60 W. The measured resistance of the low side winding is 0.03  $\Omega$  and that of the high side winding is 1.3  $\Omega$ . Find (a) the total copper loss and (b) the transformer efficiency when the power factor of the load is 0.85.  
*Ans.* (a) Total copper loss = 303 W; (b)  $\text{Eff} = 95.9\%$

- 16.41** A short-circuit test for copper loss at full load gives a wattmeter reading of 175 W. The transformer undergoing the test is a 240/24-V step-down transformer that has a full-load secondary current rating of 60 A. If the resistance of the primary is  $0.7 \Omega$ , find the resistance of the secondary.  
*Ans.*  $R_s = 0.042 \Omega$
- 16.42** On an open-circuit test for core loss, the transformer of Prob. 16.41 takes 1.5 A from a 240-V ac source. The wattmeter reads 95 W. Determine (a) the copper loss at no-load condition and (b) the core loss.  
*Ans.* (a) 1.58 W; (b) 93.4 W (In this case, the wattmeter reading of 95 W indicates core loss plus copper loss at no load.)
- 16.43** A 10-kVA 2400/240-V 60-Hz transformer has a primary winding resistance of  $6 \Omega$  and a secondary winding resistance of  $0.06 \Omega$ . The core loss is 60 W. Find (a) the full-load copper loss and (b) the efficiency of the transformer when it is fully loaded at 0.9 PF.  
*Ans.* (a) 208 W; (b) Eff = 97.1%
- 16.44** If the transformer of Prob. 16.43 had operated at 0.6 PF with the same kilovoltampere loading, what would be its efficiency? *Ans.* Eff = 95.7%
- 16.45** A 10-kVA 7200/120-V transformer has a resistance in the primary winding of  $12 \Omega$  and in the secondary winding of  $0.0033 \Omega$ . Find the copper loss (a) at full load, (b) at half load (5 kVA), and (c) at a load of 2 kVA. *Ans.* (a) 46.0 W; (b) 11.5 W; (c) 1.84 W
- 16.46** A 5-kVA 480/240-V transformer has its secondary open-circuited. Under this no-load condition, the primary current is 0.15 A at a PF of 0.6. Find (a) the full-load current  $I_p$ , (b) the core-loss component  $I_H$ , (c) the magnetizing current  $I_M$ , and (d) the percentage of each current with respect to full-load current; and (e) draw the phasor diagram.  
*Ans.* (a)  $I_p = 10.4 \text{ A}$ ; (b)  $I_H = 0.09 \text{ A}$ ; (c)  $I_M = 0.12 \text{ A}$ ; (d) percent exciting current = 1.44%; percent core-loss current = 0.87%; percent magnetizing current = 1.15%; (e) see Fig. 16-11

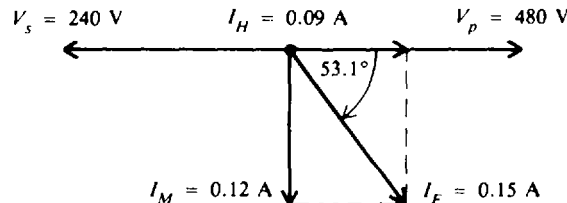

**Fig. 16-11** Phasor diagram

- 16.47** If a transformer circuit has a polarity (Fig. 16-12) where the output is  $180^\circ$  out of phase with the input, show the correct polarity dots when the leads to the load are reversed. *Ans.* See Fig. 16-13.

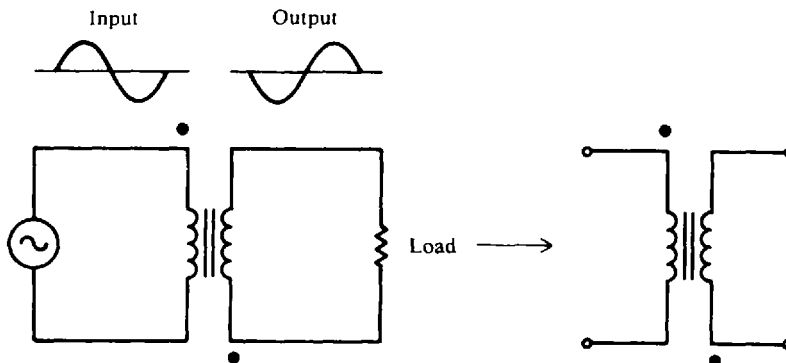

**Fig. 16-12** Transformer polarity

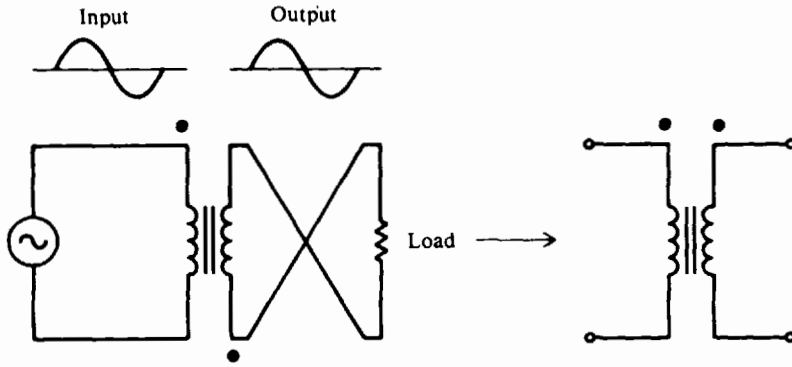


Fig. 16-13

16.48 A secondary center-tapped transformer is shown in Fig. 16-14. Indicate the correct output waveforms at points A and B. Ans. See Fig. 16-15.

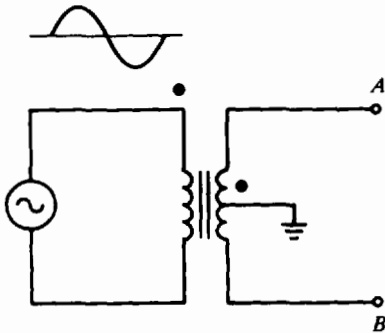


Fig. 16-14 Center-tap secondary

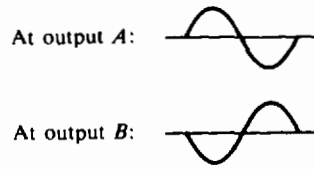


Fig. 16-15

16.49 Two transformers can be connected together to obtain a higher voltage by connecting the primaries together in parallel and connecting their secondaries in series. If the secondaries are properly phased, the output will be the sum of the secondary voltages. If the output is the difference of the secondary voltages, the connection to one of the secondaries may be reversed, or one of the primary windings may be reversed. For a series connection of two transformers, each with a secondary output of 4 V (Fig. 16-16), find the output voltage.

Ans. (a) Output = 8 V; (b) output = 0 V (secondaries "bucking")

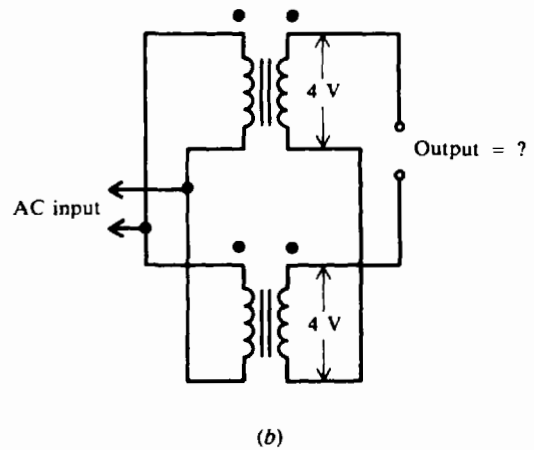
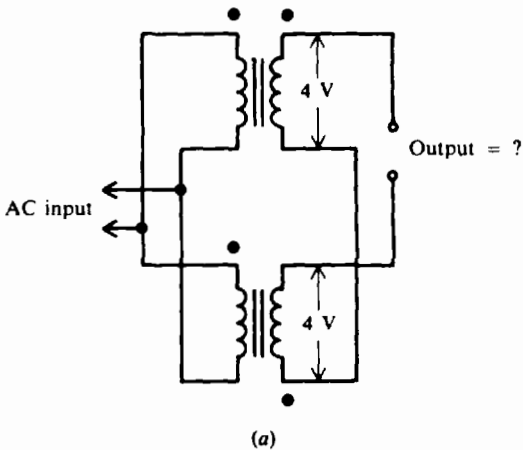


Fig. 16-16 Connection of two transformers

## Three-Phase Systems

### CHARACTERISTICS OF THREE-PHASE SYSTEMS

A three-phase (3- $\phi$ ) system is a combination of three single-phase (1- $\phi$ ) systems. In a 3- $\phi$  balanced system, the power comes from an ac generator that produces three separate but equal voltages, each of which is out of phase with the other voltages by  $120^\circ$  (Fig. 17-1). Although 1- $\phi$  circuits are widely used in electrical systems, most generation and distribution of alternating current is 3- $\phi$ . Three-phase circuits require less weight of conductors than 1- $\phi$  circuits of the same power rating; they permit flexibility in the choice of voltages; and they can be used for single-phase loads. Also, 3- $\phi$  equipment is smaller in size, lighter in weight, and more efficient than 1- $\phi$  machinery of the same rated capacity. The three phases of a 3- $\phi$  system may be connected in two ways. If the three common ends of each phase are connected together at a common terminal marked  $N$  for neutral, and the other three ends are connected to the 3- $\phi$  line, the system is wye- or Y-connected (Fig. 17-2a). If the three phases are connected in series to form a closed loop, the system is delta- or  $\Delta$ -connected (Fig. 17-2b).

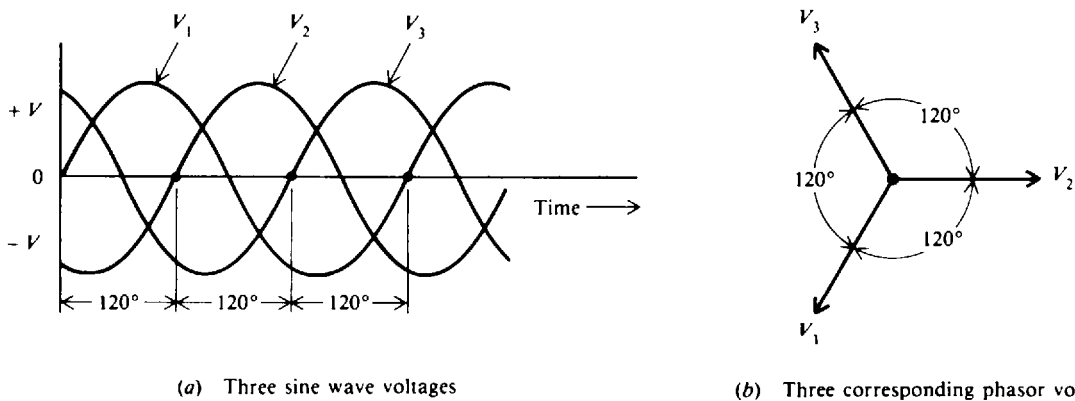


Fig. 17-1 Three-phase alternating voltages with  $120^\circ$  between each phase


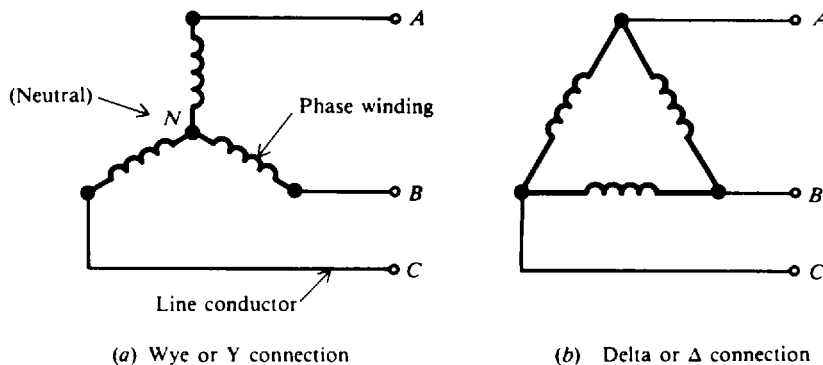


Fig. 17-2 Connections for 3- $\phi$  ac power

**THREE-PHASE TRANSFORMER CONNECTIONS**

Three-phase transformers may consist of three separate but identical 1- $\phi$  transformers or a single 3- $\phi$  unit containing three-phase windings. The transformer's windings (three in the primary and three in the secondary) may be connected to form a 3- $\phi$  bank in any one of four common ways (Fig. 17-3). Each primary winding is matched to the secondary winding drawn parallel to it.

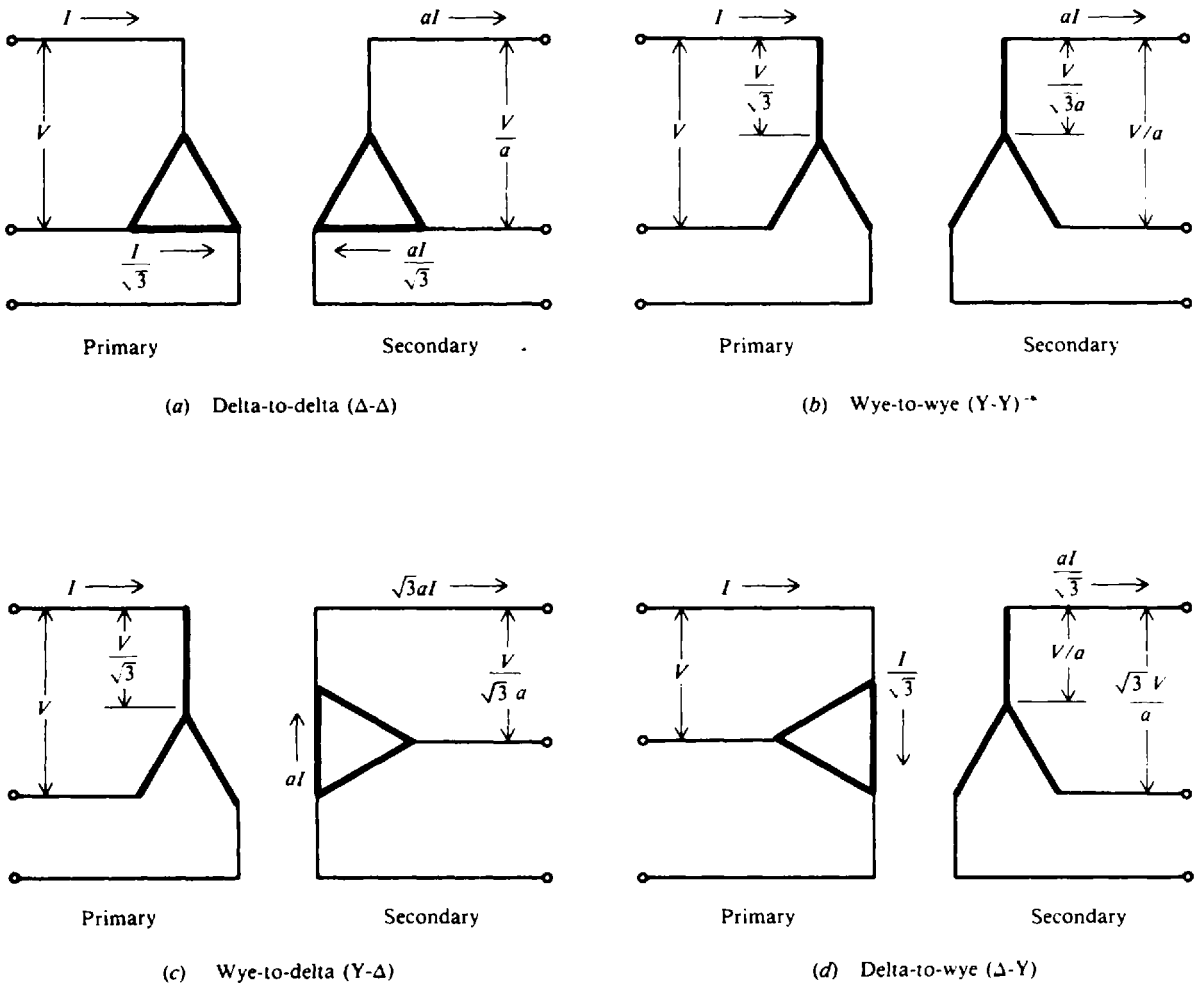

**Fig. 17-3** Common 3- $\phi$  transformer connections. The transformer windings are indicated by the heavy lines.  $a = N_1/N_2$

Shown are the voltages and currents in terms of the applied primary line-to-line voltage  $V$  and line current  $I$ , where  $a = N_1/N_2$ , the ratio of the number of primary to secondary turns. A line voltage is a voltage between two lines, while a phase voltage is a voltage across a transformer winding. A line current is a current in one of the lines, while a phase current is a current in the transformer winding. Voltage and current ratings of the individual transformers depend on the connections shown (Fig. 17-3) and are indicated in tabular form (Table 17-1) for convenience in calculations. Ideal transformers are assumed. The kilovoltampere rating of each transformer is one-third of the kilovoltampere rating of the bank, regardless of the transformer connections used.

**Table 17-1 Voltage and Current Relationships for Common 3- $\phi$  Transformer Connections**

Transformer Connection (Primary to Secondary)	Primary				Secondary			
	Line		Phase		Line		Phase	
	Voltage	Current	Voltage	Current	Voltage*	Current	Voltage	Current
$\Delta$ - $\Delta$	V	I	V	$\frac{I}{\sqrt{3}}$	$\frac{V}{a}$	aI	$\frac{V}{a}$	$\frac{aI}{\sqrt{3}}$
Y-Y	V	I	$\frac{V}{\sqrt{3}}$	I	$\frac{V}{a}$	aI	$\frac{V}{\sqrt{3}a}$	aI
Y- $\Delta$	V	I	$\frac{V}{\sqrt{3}}$	I	$\frac{V}{\sqrt{3}a}$	$\sqrt{3}aI$	$\frac{V}{\sqrt{3}a}$	aI
$\Delta$ -Y	V	I	V	$\frac{I}{\sqrt{3}}$	$\frac{\sqrt{3}V}{a}$	$\frac{aI}{\sqrt{3}}$	$\frac{V}{a}$	$\frac{aI}{\sqrt{3}}$

\*a =  $N_1/N_2$ ;  $\sqrt{3} = 1.73$

**Example 17.1** If the line voltage V is 2200 V to a 3- $\phi$  transformer bank, find the voltage across each transformer primary winding for all four types of transformer connection. Refer to Fig. 17-3 and Table 17-1.

$\Delta$ - $\Delta$ : Primary winding voltage =  $V = 2200$  V      *Ans.*

Y-Y: Primary winding voltage =  $\frac{V}{\sqrt{3}} = \frac{2200}{1.73} = 1270$  V      *Ans.*

Y- $\Delta$ : Primary winding voltage =  $\frac{V}{\sqrt{3}} = \frac{2200}{1.73} = 1270$  V      *Ans.*

$\Delta$ -Y: Primary winding voltage =  $V = 2200$  V      *Ans.*

It is clear that in any  $\Delta$  connection the total voltage across any winding in the primary or secondary equals the line voltage in the primary or secondary, respectively, because each winding is directly across the line. The voltage in each winding will be out of phase by 120° with the voltages in the other windings.

**Example 17.2** If the line current I is 20.8 A to a 3- $\phi$  transformer connection, find the current through each primary winding for all four transformer configurations. Refer to Fig. 17-3 and Table 17-1.

$\Delta$ - $\Delta$ : Primary winding current =  $\frac{I}{\sqrt{3}} = \frac{20.8}{1.73} = 12$  A      *Ans.*

Y-Y: Primary winding current =  $I = 20.8$  A      *Ans.*

Y- $\Delta$ : Primary winding current =  $I = 20.8$  A      *Ans.*

$\Delta$ -Y: Primary winding current =  $\frac{I}{\sqrt{3}} = \frac{20.8}{1.73} = 12$  A      *Ans.*

The current in each winding will be out of phase by 120° with the currents in the other windings.

**Example 17.3** For each type of transformer connection, find the secondary line current and secondary phase current if the primary line current I is 10.4 A and the turns ratio is 2:1. Refer to Fig. 17-3 and Table 17-1.

$\Delta$ - $\Delta$ : Secondary line current =  $aI = 2(10.4) = 20.8$  A      *Ans.*

Secondary phase current =  $\frac{aI}{\sqrt{3}} = \frac{2(10.4)}{1.73} = 12$  A      *Ans.*



Y-Y:	Secondary line current = $aI = 2(10.4) = 20.8 \text{ A}$	Ans.
	Secondary phase current = $aI = 2(10.4) = 20.8 \text{ A}$	Ans.
Y- $\Delta$ :	Secondary line current = $\sqrt{3}aI = 1.73(2)(10.4) = 36 \text{ A}$	Ans.
	Secondary phase current = $aI = 2(10.4) = 20.8 \text{ A}$	Ans.
$\Delta$ -Y:	Secondary line current = $\frac{aI}{\sqrt{3}} = \frac{2(10.4)}{1.73} = 12 \text{ A}$	Ans.
	Secondary phase current = $\frac{aI}{\sqrt{3}} = \frac{2(10.4)}{1.73} = 12 \text{ A}$	Ans.

The current in each secondary line will be out of phase by  $120^\circ$  with the currents in the other secondary lines. Likewise, the current in each secondary winding will be out of phase by  $120^\circ$  with the currents in the other secondary windings.

### POWER IN BALANCED THREE-PHASE LOADS

A balanced load has identical impedance in each secondary winding (Fig. 17-4). The impedance of each winding in the  $\Delta$  load is shown equal to  $Z_\Delta$  (Fig. 17-4a), and in the Y load equal to  $Z_Y$  (Fig. 17-4b). For either connection the lines A, B, and C provide a three-phase system of voltages. The neutral point N in the Y-connection is the fourth conductor of the three-phase four-wire system.

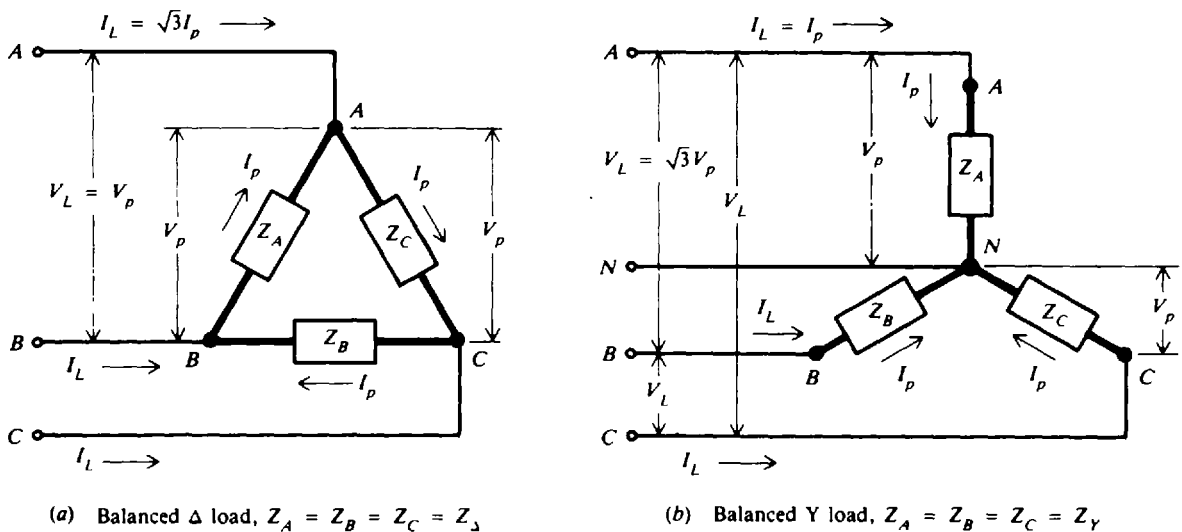


Fig. 17-4 Three-phase balanced load types

In a balanced  $\Delta$ -connected load (Fig. 17-4a), as well as in the windings of a transformer, the line voltage  $V_L$  and the winding or phase voltage  $V_p$  are equal, and the line current  $I_L$  is  $\sqrt{3}$  times the phase current  $I_p$ . That is,

$$\Delta\text{-load: } V_L = V_p \quad (17-1)$$

$$I_L = \sqrt{3}I_p \quad (17-2)$$

For a balanced Y-connected load (Fig. 17-4b), the line current  $I_L$  and the winding or phase current  $I_p$  are equal, the neutral current  $I_N$  is zero, and the line voltage  $V_L$  is  $\sqrt{3}$  times the phase voltage  $V_p$ . That is,

Y load:  $I_L = I_p$  (17-3)

$$I_N = 0 \quad (17-4)$$

$$V_L = \sqrt{3}V_p \quad (17-5)$$

(These relationships are also observed in Fig. 17-3 and Table 17-1.)

Since the phase impedance of balanced Y or Δ loads have equal currents, the phase power or power of one phase is one-third the total power. Phase power  $P_p$  is

$$P_p = V_p I_p \cos \theta \quad (17-6)$$

and total power  $P_T$  is

$$P_T = 3V_p I_p \cos \theta \quad (17-7)$$

Since  $V_L = V_p$  [Eq. (17-1)] and  $I_p = \sqrt{3}I_L/3$  from Eq. (17-2), for a balanced Δ load,

Δ load:  $P_T = \sqrt{3}V_L I_L \cos \theta$  (17-8)

Since  $I_L = I_p$  [Eq. (17-3)] and  $V_p = \sqrt{3}V_L/3$  from Eq. (17-5), for balanced Y loads, substitution in Eq. (17-7) gives

Y load:  $P_T = \sqrt{3}V_L I_L \cos \theta$  (17-8)

Thus the total-power formulas for Δ and Y loads are identical.  $\theta$  is the phase angle between the voltage and current of the load impedance, so  $\cos \theta$  is the power factor of the load.

The total apparent power  $S_T$  in voltamperes and the total reactive power  $Q_T$  in voltamperes reactive are related to total real power  $P_T$  in watts (Fig. 17-5). Therefore, a balanced three-phase load has the real power, apparent power, and reactive power given by the equations

$$P_T = \sqrt{3}V_L I_L \cos \theta \quad (17-8)$$

$$S_T = \sqrt{3}V_L I_L \quad (17-9)$$

$$Q_T = \sqrt{3}V_L I_L \sin \theta \quad (17-10)$$

- where  $P_T$  = total real power, W  
 $S_T$  = total apparent power, VA  
 $Q_T$  = total reactive power, VAR  
 $V_L$  = line voltage, V  
 $I_L$  = line current, A  
 $\theta$  = load phase angle  
 $\sqrt{3}$  = 1.73, a constant

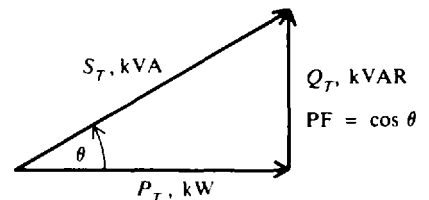


Fig. 17-5 Power-triangle relationships for 3-φ circuit

Transformer ratings are specified generally in kilovoltamperes. The relationships of voltage, current, and power expressed in Eqs. (17-1) to (17-10) are applicable to all balanced 3-φ circuits.

**Example 17.4** How much power is delivered by a balanced 3-φ system if each wire carries 20 A and the voltage between the wires is 220 V at a PF of unity?

Using Eq. (17-8),

$$P_T = \sqrt{3}V_L I_L \cos \theta = 1.73(220)(20)(1) = 7612 \text{ W} \quad \text{Ans.}$$

**Example 17.5** Each phase of a 3-φ Δ-connected generator supplies a full-load current of 100 A at a voltage of 240 V and at a PF of 0.6 lagging (Fig. 17-6). Find the (a) line voltage, (b) line current, (c) 3-φ power in kilovoltamperes, and (d) 3-φ power in kilowatts.

(a) Use Eq. (17-1).

$$V_L = V_p = 240 \text{ V} \quad \text{Ans.}$$

(b) Use Eq. (17-2).

$$I_L = 1.73 I_p = 1.73(100) = 173 \text{ A} \quad \text{Ans.}$$

(c) Use Eq. (17-9).

$$S_T = \sqrt{3} V_L I_L = 1.73(240)(173) = 71\,800 \text{ VA} = 71.8 \text{ kVA} \quad \text{Ans.}$$

(d)  $P_T = S_T \cos \theta = 71.8(0.6) = 43.1 \text{ kW} \quad \text{Ans.}$

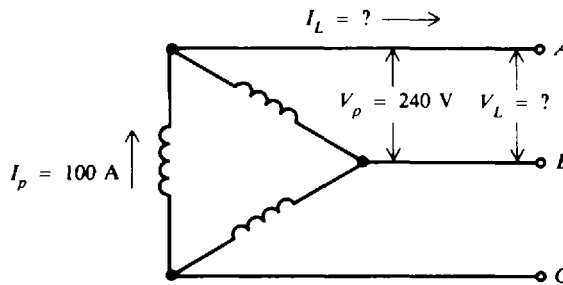


Fig. 17-6 Three-phase  $\Delta$ -connected generator

**Example 17.6** Three resistances of  $20 \Omega$  each are Y-connected to a 240-V 3- $\phi$  line operating at a PF of unity (Fig. 17-7). Find the (a) current through each resistance, (b) line current, and (c) power taken by the three resistances.

(a)  $V_L = \sqrt{3} V_p \quad (17-5)$

$$V_p = \frac{V_L}{\sqrt{3}} = \frac{240}{1.73} = 138.7 \text{ V}$$

$$I_p = \frac{V_p}{Z_p} = \frac{V_p}{R_p} = \frac{138.7}{20} = 6.94 \text{ A} \quad \text{Ans.}$$

(b) Use Eq. (17-3).

$$I_L = I_p = 6.94 \text{ A} \quad \text{Ans.}$$

(c) Use Eq. (17-6).

$$P_T = 3P_p = 3V_p I_p \cos \theta = 3(138.7)(6.94)(1) = 2890 \text{ W} \quad \text{Ans.}$$

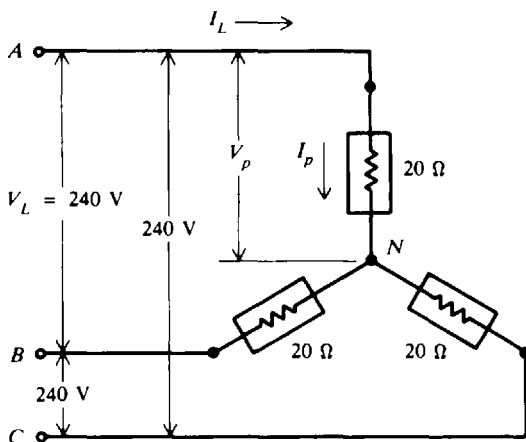


Fig. 17-7 Y-connected load

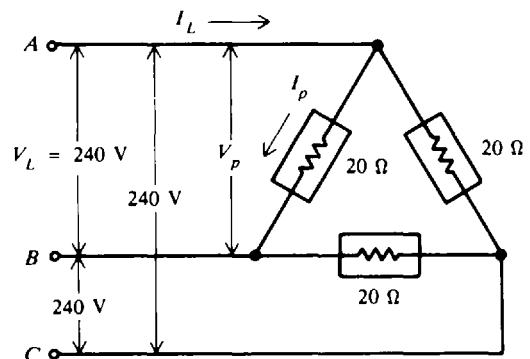


Fig. 17-8  $\Delta$ -connected load

**Example 17.7** Repeat Example 17.6 if the three resistances are reconnected in delta (Fig. 17-8).

(a) Use Eq. (17-1).

$$V_p = V_L = 240 \text{ V}$$

$$I_p = \frac{V_p}{Z_p} = \frac{V_p}{R_p} = \frac{240}{20} = 12 \text{ A} \quad \text{Ans.}$$

(b) Use Eq. (17-2).

$$I_L = \sqrt{3}I_p = 1.73(12) = 20.8 \text{ A} \quad \text{Ans.}$$


(c) Use Eq. (17-6).

$$P_T = 3V_p I_p \cos \theta = 3(240)(12)(1) = 8640 \text{ W} \quad \text{Ans.}$$

Or use Eq. (17-8).

$$P_T = \sqrt{3}V_L I_L \cos \theta = 1.73(240)(20.8)(1) = 8640 \text{ W} \quad \text{Ans.}$$

**Example 17.8** A 3- $\phi$  Y-connected transformer secondary has a four-wire 208-V ABC system (Fig. 17-9). Thirty lamps, each rated at 120 V and 2 A, are to be connected across each phase. Show the connection of the lamp load if the load is to be balanced, and determine the power assumed by each phase and the power consumed by the system. (Assume lamps are resistive.)

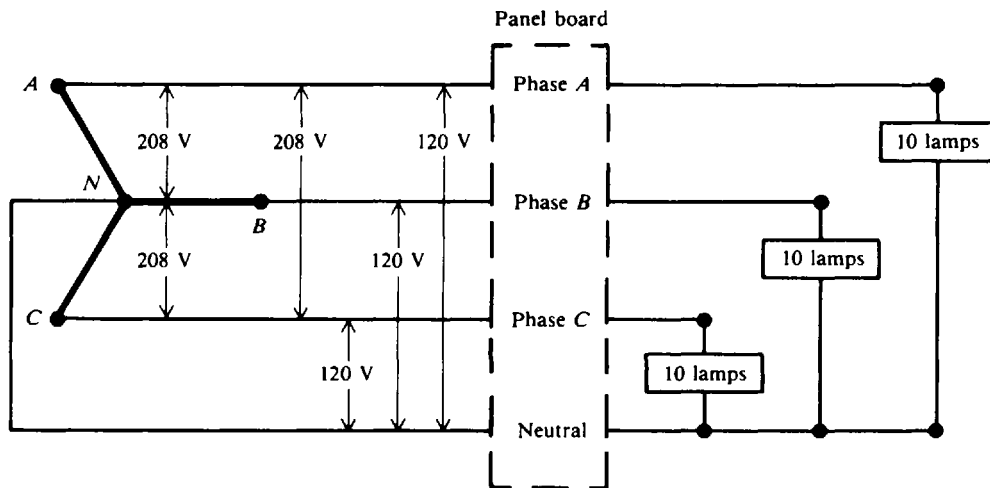

**Fig. 17-9** Load connections for a balanced 3- $\phi$  circuit

The line voltage is given as  $V_L = 208 \text{ V}$ . The line-to-neutral voltage or the phase voltage is  $V_p$ . Using Eq. (17-5),

$$V_L = \sqrt{3}V_p \quad \text{so} \quad V_p = \frac{V_L}{\sqrt{3}} = \frac{208}{1.73} = 120 \text{ V}$$

In order to have a balanced load, 30 lamps must be distributed equally across three 120-V phases. Thus, 10 lamps are connected across each 120-V phase (Fig. 17-9). The power per phase  $P_p$  is found by using Eq. (17-6):

$$P_p = V_p I_p \cos \theta = 120 \left( 10 \text{ lamps} \times \frac{2 \text{ A}}{\text{lamp}} \right) (1) = 120(20)(1) = 2400 \text{ W} \quad \text{Ans.}$$

and the total power is three times the phase power.

$$P_T = 3P_p = 3(2400) = 7200 \text{ W} \quad \text{Ans.}$$

**Example 17.9** A 3- $\phi$  three-wire system has a line current of 25 A and a line voltage of 1000 V. The power factor of the load is 86.6 percent lagging. Find (a) the real power delivered, (b) the reactive power, and (c) the apparent power, and (d) draw the power triangle.

(a) Use Eq. (17-8).

$$P_T = \sqrt{3}V_L I_L \cos \theta = 1.73(1000)(25)(0.866) = 37\,500 \text{ W} = 37.5 \text{ kW} \quad \text{Ans.}$$

(b)  $\theta = \arccos 0.866 = 30^\circ$   
 $\sin \theta = 0.5$

$$Q_T = \sqrt{3}V_L I_L \sin \theta = 1.73(1000)(25)(0.5) = 21\,600 \text{ VAR} = 21.6 \text{ kVAR lagging} \quad \text{Ans.}$$

(c)  $S_T = \sqrt{3}V_L I_L = 1.73(1000)(25) = 43\,250 \text{ VA} = 43.3 \text{ kVA} \quad \text{Ans.}$

(d) See Fig. 17-10.

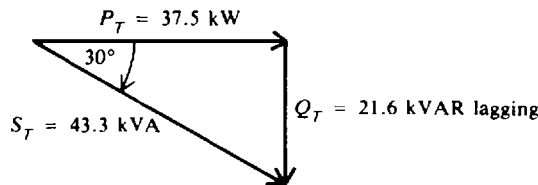


Fig. 17-10 Power triangle

### UNBALANCED THREE-PHASE LOADS

A very important property of a 3- $\phi$  balanced system is that the phasor sum of the three line (or phase) voltages is zero and the phasor sum of the three line (or phase) currents is zero. When the three load impedances are not equal to each other, the phasor sum and the neutral current  $I_N$  are not zero, and we have an unbalanced load. An imbalance occurs when an open or short circuit appears at the load.

If a 3- $\phi$  system has an unbalanced power source and an unbalanced load, the methods for solving them are complex. We will consider an unbalanced load only with a balanced source.

**Example 17.10** Consider a balanced 3- $\phi$  system (Fig. 17-11a) with a Y load. The line-to-line voltage is 173 V and the resistance in each branch is 10  $\Omega$ . Find the line current and neutral current under the following three load conditions: (a) balanced load, (b) open circuit in line A (Fig. 17-11b), and (c) short circuit in line A (Fig. 17-11c).

(a) Balanced 3- $\phi$  load (Fig. 17-11a):

$$V_p = \frac{V_L}{\sqrt{3}} = \frac{173}{1.73} = 100 \text{ V} \quad I_p = \frac{V_p}{R_p} = \frac{100}{10} = 10 \text{ A}$$

$$I_L = I_p = 10 \text{ A} \quad I_N = 0 \text{ A} \quad \text{Ans.}$$

(b) Open Y circuit (Fig. 17-11b): Line voltage  $V_L = 173 \text{ V}$  remains fixed. But current in lines B and C now becomes (two 10- $\Omega$  resistors are in series)

$$I_B = I_C = \frac{173}{2(10)} = 8.66 \text{ A} \quad \text{Ans.}$$

which is less than the current under balanced conditions.

$$I_N = I_B + I_C = 8.66 + 8.66 = 17.3 \text{ A} \quad \text{Ans.}$$

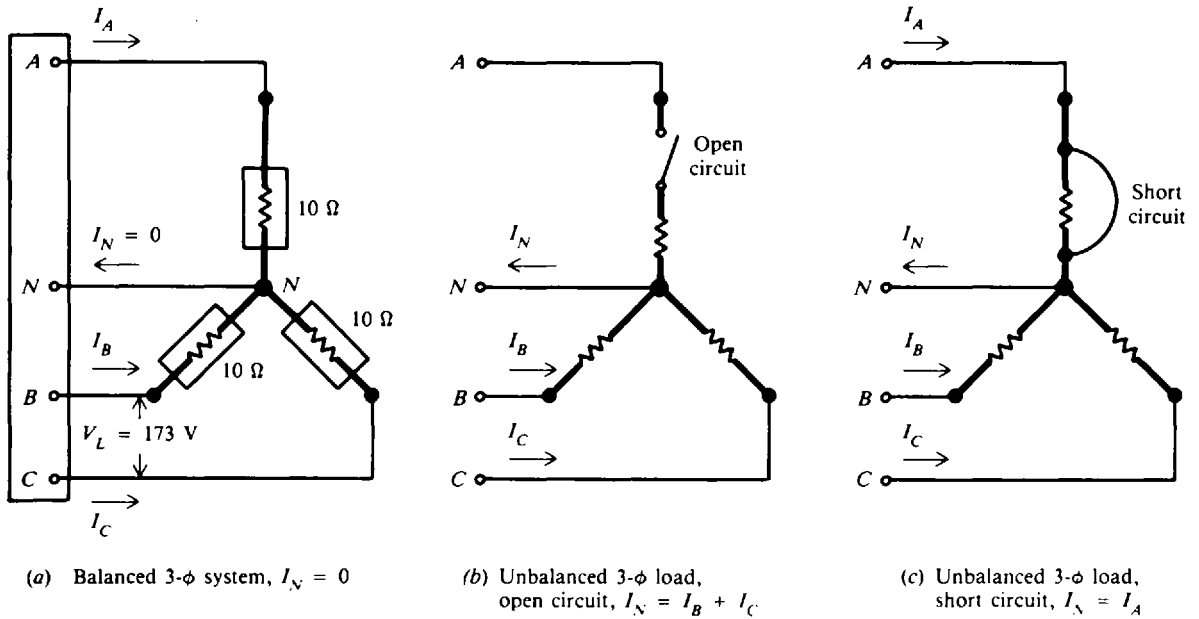


Fig. 17-11 Three-phase unbalanced load conditions

(c) Short Y circuit (Fig. 17-11c): Line voltage  $V_L = 173$  V remains fixed. But current in lines B and C now becomes

$$I_B = I_C = \frac{173}{10} = 17.3 \text{ A} \quad \text{Ans.}$$

which is  $\sqrt{3}$  times the values under balanced conditions. The current in line A is equal to the neutral line current,  $I_A = I_N$ .  $I_N$  is the phasor sum of  $I_B$  and  $I_C$ , which are  $120^\circ$  out of phase, so that

$$I_N = \sqrt{3}I_B = 1.73(17.3) = 30 \text{ A} \quad \text{Ans.}$$

which is three times its value under balanced conditions. Under a fault condition the neutral connector in the Y-connected load carries more current than the line or winding under a balanced load.

### Solved Problems

17.1 Each phase of a Y-connected generator delivers a current of 30 A at a phase voltage of 254 V and a PF of 80 percent lagging (Fig. 17-12). What is the generator terminal voltage? What is the power developed in each phase? What is the 3- $\phi$  power developed?

$$V_L = \sqrt{3}V_p = 1.73(254) = 439 \text{ V} \quad \text{Ans.} \quad (17-3)$$

$$P_p = V_p I_p \cos \theta = 254(30)(0.8) = 6096 \text{ W} \quad \text{Ans.} \quad (17-6)$$

$$P_T = 3V_p I_p \cos \theta = 3P_p = 3(6096) = 18\,288 \text{ W} \quad \text{Ans.} \quad (17-7)$$



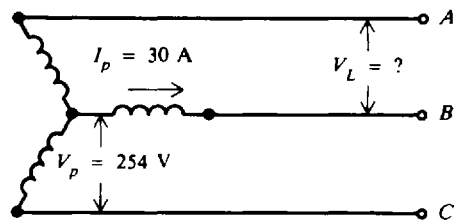


Fig. 17-12 Y-connected generator

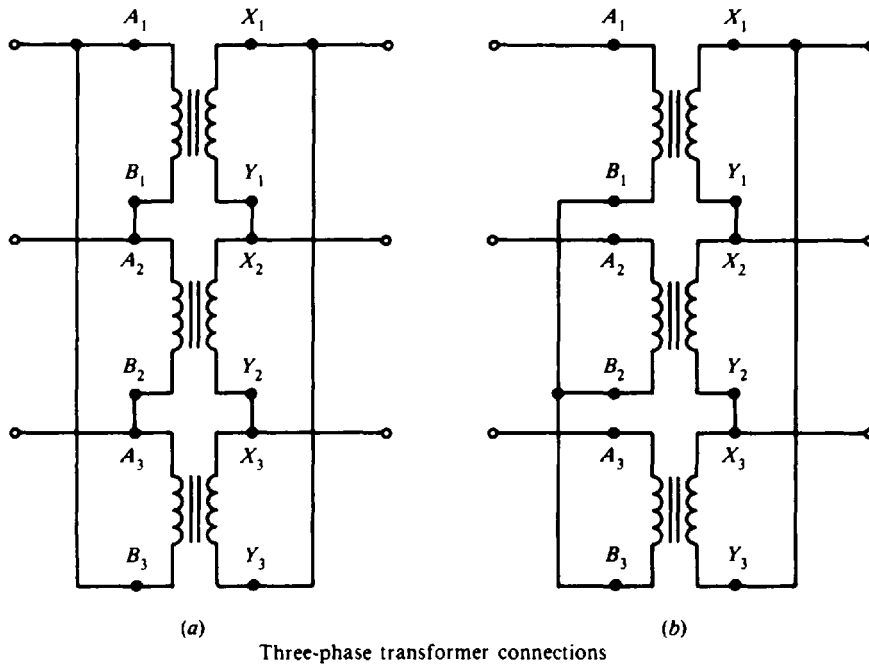17.2 Identify the three-phase transformer connections (Fig. 17-13a and b).



Three-phase transformer connections

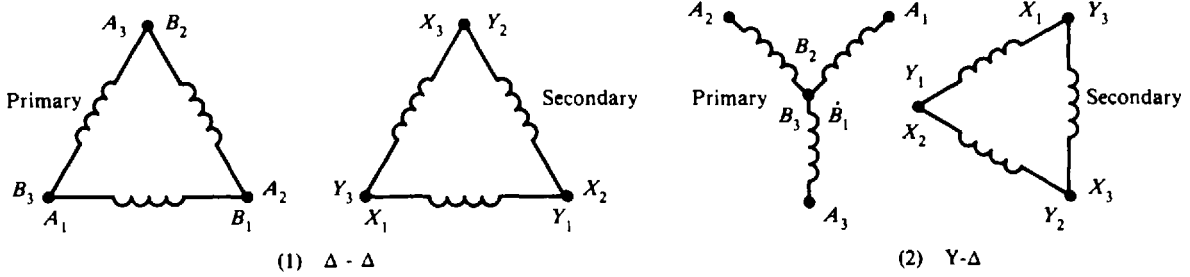

(c) Equivalent transformer connections

Fig. 17-13

If you follow the wiring sequence for the primary winding connection and the secondary winding connection, you obtain the equivalent connections shown in Fig. 17-13c. So (1) is a  $\Delta$ - $\Delta$  connection and (2) is a Y- $\Delta$  connection.

17.3 In a three-phase Y- $\Delta$  connection, each transformer has a voltage ratio of 4:1. If the primary line voltage is 660 V, find (a) the secondary line voltage, (b) the voltage across each primary winding, and (c) the voltage across each secondary winding.

From Fig. 17-3c, the Y- $\Delta$  connection is as shown in Fig. 17-14.

(a) Given are  $V = 660$  V and  $VR = 4 = TR = a$ . Then

$$\text{Secondary line voltage} = \frac{V}{\sqrt{3}a} = \frac{660}{1.73(4)} = 95.4 \text{ V} \quad \text{Ans.}$$

(b) Primary winding voltage =  $\frac{V}{\sqrt{3}} = \frac{660}{1.73} = 382$  V      *Ans.*

(c) Voltage across the secondary winding = voltage of secondary line = 95.4 V      *Ans.*

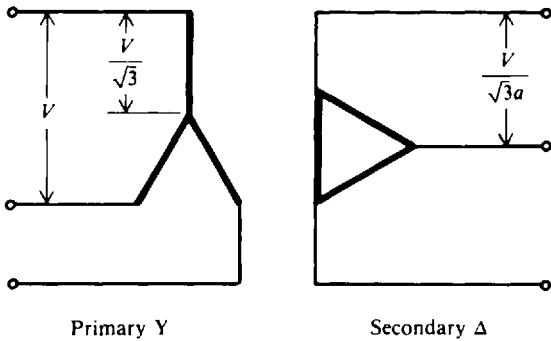


Fig. 17-14 Y-Δ transformer connection

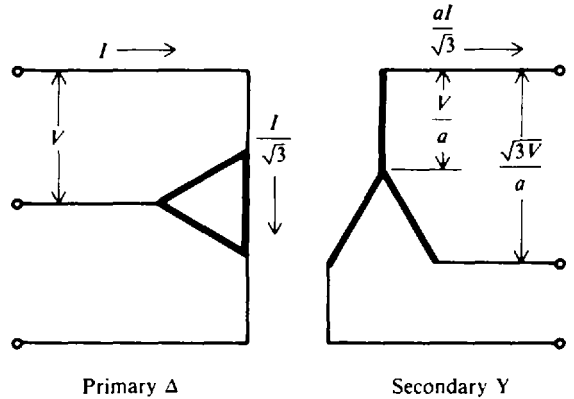


Fig. 17-15 Δ-Y transformer connection

17.4 The secondary line voltage of a Δ-Y transformer bank is 411 V. The transformers have a turns ratio of 3:1. Find (a) the primary line voltage, (b) the current in each secondary winding or coil if the current in each secondary line is 60 A, and (c) the primary line current.

From Fig. 17-3d, the Δ-Y connection is as shown in Fig. 17-15.

(a) Secondary line voltage =  $\frac{\sqrt{3}V}{a} = 411 \text{ V}$  so

Primary line voltage  $V = \frac{411a}{\sqrt{3}} = \frac{411(3)}{1.73} = 713 \text{ V}$  Ans.

(b) When the secondaries are connected in Y, the current in each secondary coil equals the line current, or 60 A.

(c) Secondary line current =  $\frac{aI}{\sqrt{3}} = 60 \text{ A}$  so

Primary line current  $I = \frac{60\sqrt{3}}{a} = \frac{60(1.73)}{3} = 34.6 \text{ A}$  Ans.

17.5 What are the primary and secondary current ratings of a 500-kVA 3-φ transformer stepping down from a 480-V delta to 120/208-V wye (Fig. 17-16). The 120/208-V wye four-wire transformer secondary is used in building electrical systems when both single-phase loads and three-phase motors are to be supplied.

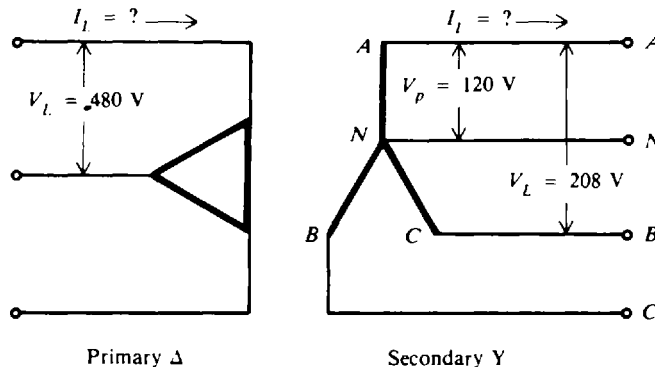


Fig. 17-16 Δ-Y connection for a 3-φ step-down transformer



There are two secondary voltages in the Y transformer four-wire system: the phase voltage  $V_p$  of 120 V and the line voltage  $V_L$  of 208 V ( $120 \times \sqrt{3} = 208$ ). On the primary side:

$$\text{Transformer rating} = \text{apparent power} = \sqrt{3}V_L I_L \tag{17-9}$$

So 
$$I_L = \frac{\text{transformer rating}}{\sqrt{3}V_L} = \frac{500\,000}{1.73(480)} = 602\text{ A} \quad \text{Ans.}$$

On the secondary side:

$$\text{Transformer rating} = \text{apparent power} = \sqrt{3}V_L I_L \tag{17-9}$$

So 
$$I_L = \frac{\text{transformer rating}}{\sqrt{3}V_L} = \frac{500\,000}{1.73(208)} = 1390\text{ A} \quad \text{Ans.}$$

- 17.6 Delta-connected secondaries are generally used for three-phase three-wire loads. Show how a  $\Delta$  connection can be used to supply single-phase loads at two terminal voltages as well as three-phase loads.

A four-wire system is obtained by adding a fourth wire from the midpoint of one of the three  $\Delta$  transformer windings (Fig. 17-17). The normal voltage is 240 V from phase to phase and 120 V from the neutral (or midphase) wire to two of the phasor conductors connected to the winding ends. With this system, single-phase loads are fed from 120-V terminals; and three-phase loads as well as single-phase loads are fed from the 240-V phase terminals A, B, and C.

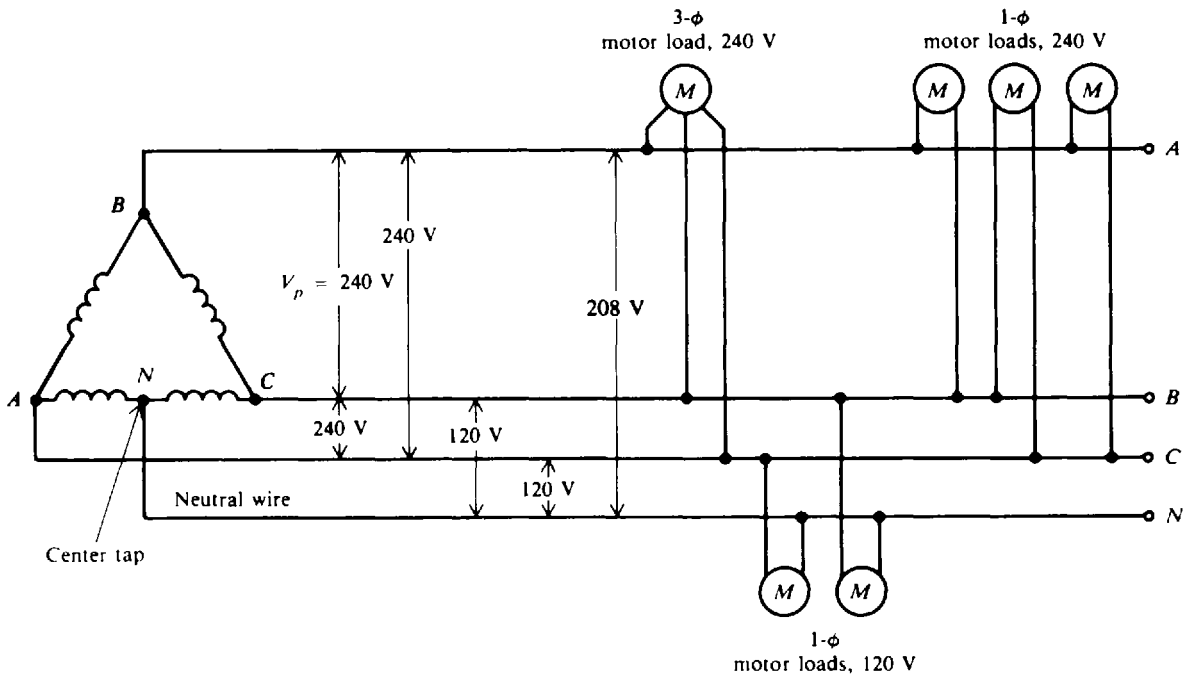



Fig. 17-17  $\Delta$  connections to four-wire line with neutral

- 17.7 A distribution transformer bank of three single-phase transformers is connected  $\Delta$ -Y (Fig. 17-18a). The transformer turns ratio is 100:1. The secondaries of the bank supply power to a 208-V, 3- $\phi$ , four-wire system. The load in the system consists of a 72-kW 3- $\phi$  motor, PF = 1, terminal voltage 208 V; three 12-kW 1- $\phi$  lighting circuits, terminal voltage 120 V; and three 1- $\phi$  10-kVA motors, PF = 0.8 lagging, terminal voltage 208 V. Find (a) the total kilovoltampere load of the circuit; (b) the kilovoltampere rating of the transformer bank if ratings only of 100 kVA, 112.5 kVA, and 150 kVA are available; (c) the kilovoltam-


per rating of the individual transformers; (d) the secondary line current; (e) the primary line voltage, and (f) the primary line current.

**Step 1.** Find the phase-to-neutral voltage  $V_p$  in the Y secondary.

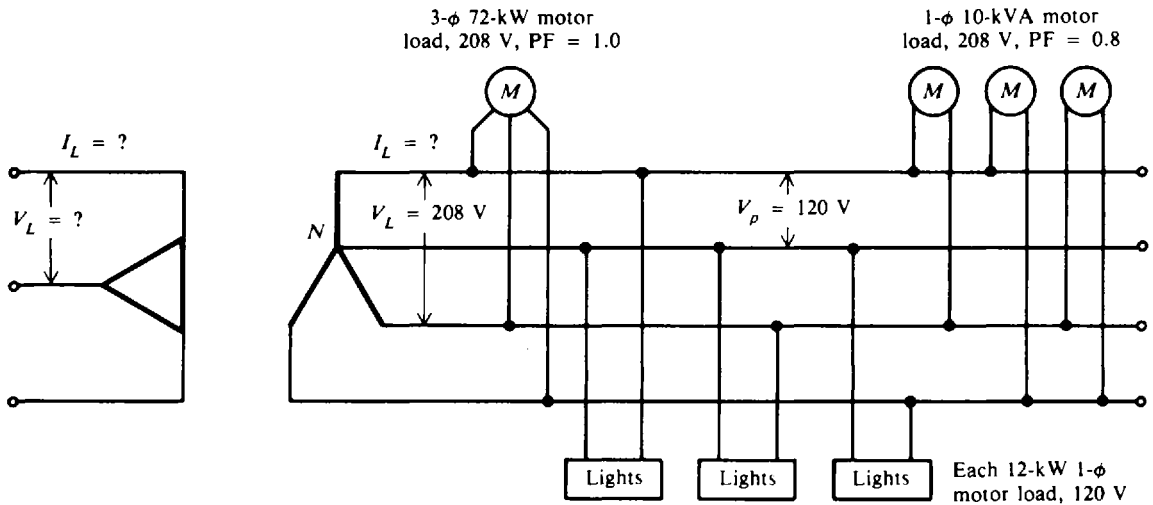
$$V_p = \frac{V_L}{\sqrt{3}} = \frac{208}{\sqrt{3}} = 120 \text{ V}$$



(a) Distribution transformer bank

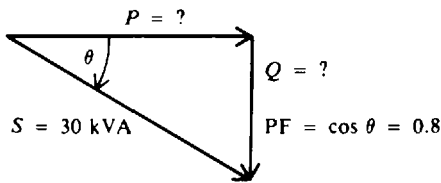

(b) Motor power triangle

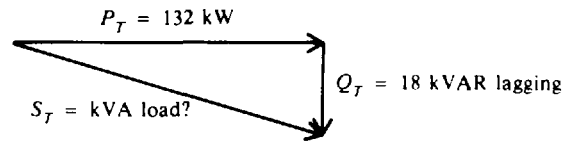

(c) Total power triangle

**Fig. 17-18**

**Step 2.** Find the total kilovoltampere load and then the required kilovoltampere rating of the transformer bank.

Lighting load:  $P = 3 \times 12 \text{ kW} = 36 \text{ kW}$   
 PF = 1, motor load:  $P = 72 \text{ kW}$   
 PF = 0.8, motor load:  $S = 3 \times 10 \text{ kVA} = 30 \text{ kVA}$

In order to find the  $P$  and  $Q$  components of the motor load with PF = 0.8, we use relationships of the power triangle (Fig. 17-18b).

$$P = S \cos \theta = 30(0.8) = 24 \text{ kW} \quad Q = S \sin \theta = 30(0.6) = 18 \text{ kVAR lagging}$$

The total kilowatt load is

$$P_T = 36 + 72 + 24 = 132 \text{ kW}$$

The total kilovoltampere-reactive load  $Q_T$  is

$$Q_T = 18 \text{ kVAR}$$

So the total kilovoltampere load  $S_T$  (Fig. 17-18c) is

$$S_T = \sqrt{132^2 + 18^2}$$

- (a) Kilovoltampere load  $S_T = 133 \text{ kVA}$       *Ans.*  
 (b) The next larger rating available is the 150-kVA transformer bank.      *Ans.*  
 (c) Therefore, this bank requires three 50-kVA single-phase transformers.      *Ans.*

**Step 3.** Find  $I_L$  in the secondary.

$$\text{kilovoltampere load} = \sqrt{3} V_L I_L = 133 \text{ kVA} \quad (17-9)$$

(d) Then 
$$I_L = \frac{133(1000)}{\sqrt{3} V_L} = \frac{133\,000}{1.73(208)} = 370 \text{ A} \quad \textit{Ans.}$$

**Step 4.** Find  $V_L$  in the primary.

(e) Primary  $V_L = (\text{TR})(\text{secondary } V_p) = 100(120) = 12\,000 \text{ V} \quad \textit{Ans.}$

**Step 5.** Find  $I_L$  in the primary.

(f) Then 
$$\text{Kilovoltampere load} = \sqrt{3} V_L I_L = 133 \text{ kVA}$$

$$I_L = \frac{133(1000)}{\sqrt{3} V_L} = \frac{133\,000}{1.73(12\,000)} = 6.41 \text{ A} \quad \textit{Ans.}$$

- 17.8** If the transformer bank of Prob. 17.7 is rated at 150 kVA, find the full-load current on the high side and on the low side.

The low-side (secondary) voltage is given as 208 V.

$$\text{Kilovoltampere rating} = \sqrt{3} V_L I_L = 150 \text{ kVA} \quad (17-9)$$

Low side: 
$$I_L = \frac{150(1000)}{\sqrt{3} V_L} = \frac{150\,000}{1.73(208)} = 417 \text{ A} \quad \textit{Ans.}$$

The high-side (primary) voltage is the product of the turns ratio and the corresponding winding voltage on the low side (secondary), which is the phase voltage  $V_p$ . So

$$V_L = 100(120) = 12\,000 \text{ V}$$

and, assuming ideal transformers without losses, on the high side

$$\text{Kilovoltampere rating} = \sqrt{3} V_L I_L = 150 \text{ kVA} \quad (17-9)$$

High side: 
$$I_L = \frac{150(1000)}{\sqrt{3} V_L} = \frac{150\,000}{1.73(12\,000)} = 7.23 \text{ A} \quad \textit{Ans.}$$

Since maximum currents are present under full-load conditions, the cables connected to the high- and low-voltage windings of the transformer would be sized according to these currents.

- 17.9** A  $\Delta$ -connected load (Fig. 17-19) is drawing 600 kW from a 5000-V line at a lagging power factor. If each wire carries 75 A, what is the power factor and angle of lag?

$$\begin{aligned} \text{PF} &= \cos \theta \\ P_T &= \sqrt{3} V_L I_L \cos \theta \end{aligned} \quad (17-8)$$

Solve for  $\cos \theta$ :

$$\cos \theta = \frac{P_T}{\sqrt{3} V_L I_L}$$

Substitute known values:

$$\text{PF} = \cos \theta = \frac{600(1000)}{1.73(5000)(75)} = 0.925 \text{ lagging} \quad \textit{Ans.}$$

Then 
$$\theta = \arccos 0.925 = 22.4^\circ \quad \textit{Ans.}$$

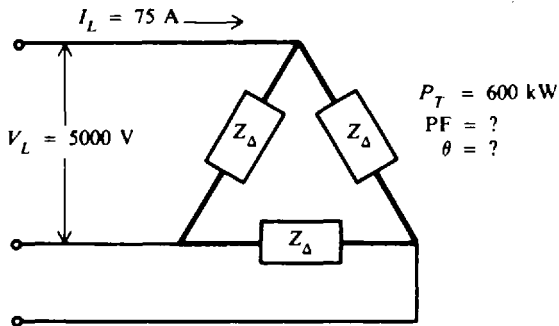


Fig. 17-19 Δ-connected load

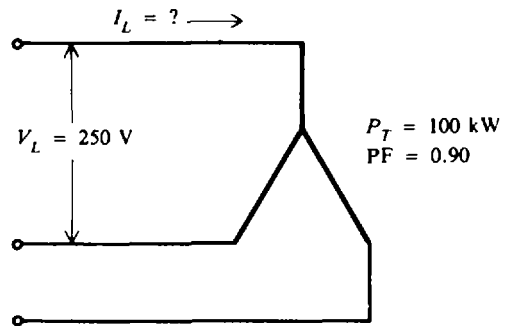


Fig. 17-20 Y-connected generator

17.10 A Y-connected generator (Fig. 17-20) supplies 100 kW at a PF of 0.90. If the line voltage is 250 V, find the line current.

$$\begin{aligned} \text{PF} &= \cos \theta = 0.90 \\ P_T &= \sqrt{3} V_L I_L \cos \theta \end{aligned} \tag{17-8}$$

Solve for  $I_L$ :

$$I_L = \frac{P_T}{\sqrt{3} V_L \cos \theta} = \frac{100(1000)}{1.73(250)(0.90)} = 257 \text{ A} \quad \text{Ans.}$$

17.11 Three loads, each having a resistance of  $16 \Omega$  and an inductive reactance of  $12 \Omega$ , are Δ-connected to a 240-V 3-φ supply (Fig. 17-21). Find the (a) impedance per phase, (b) current per phase, (c) the 3-φ kilovoltampere, (d) PF, and (e) the 3-φ power in kilowatts.


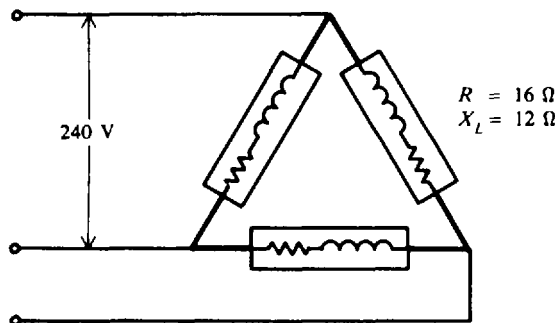



Fig. 17-21 Impedance in Δ-connected load

- (a)  $Z_p = \sqrt{R_p^2 + X_p^2} = \sqrt{16^2 + 12^2} = 20 \Omega \quad \text{Ans.}$   
 $\theta \text{ of load} = \arctan \frac{X_p}{R_p} = \arctan \frac{12}{16} = \arctan 0.75 = 36.9^\circ$
- (b)  $V_p = V_L = 240 \text{ V}$   
 $I_p = \frac{V_p}{Z_p} = \frac{240}{20} = 12 \text{ A} \quad \text{Ans.}$
- (c)  $S_T = 3 V_p I_p = 3(240)(12) = 8640 \text{ VA} = 8.64 \text{ kVA} \quad \text{Ans.}$
- (d)  $\text{PF} = \cos \theta = \cos 36.9^\circ = 0.80 \text{ lagging} \quad \text{Ans.}$
- (e)  $P_T = S_T \cos \theta = 8.64(0.8) = 6.91 \text{ kW} \quad \text{Ans.}$

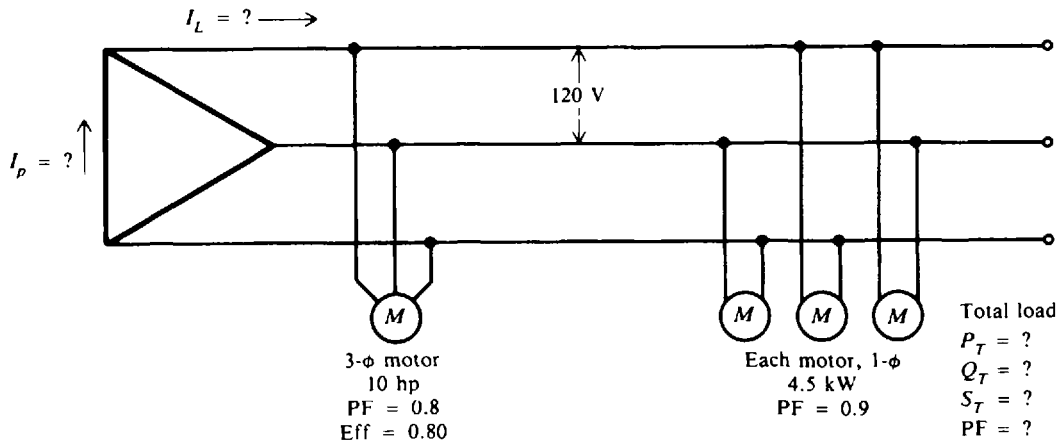
17.12 Find the indicated quantities (Fig. 17-22a), which show the connected loads for a balanced 3- $\phi$   $\Delta$  transformer bank.



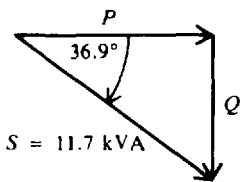
(a) Loads of 3- $\phi$   $\Delta$  transformer bank



(b) Power triangle

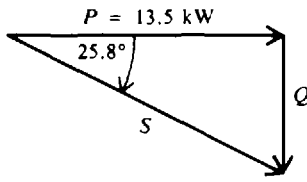

(c) Power triangle

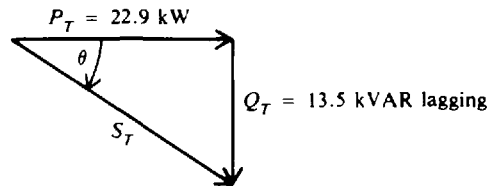

(d) Power triangle

Fig. 17-22

**Step 1.** Find the power relationships for *each* load.

(a) 3- $\phi$  motor (Fig. 17-22b):

$$S = \text{motor load} = \frac{\text{hp} \times 746}{\text{PF} \times \text{Eff}} = \frac{10(746)}{0.8(0.8)} = 11\,656 = 11.7 \text{ kVA} \quad (1 \text{ hp} = 746 \text{ W})$$

$$\theta = \arccos 0.8 = 36.9^\circ$$

$$P = 11.7 \cos 36.9^\circ = 11.7(0.8) = 9.36 \text{ kW}$$

$$Q = 11.7 \sin 36.9^\circ = 11.7(0.6) = 7.02 \text{ kVAR lagging}$$

(b) Three 1- $\phi$  motors (Fig. 17-22c):

$$P = 13.5 \text{ kW given} \quad \theta = \arccos 0.9 = 25.8^\circ$$

$$Q = 13.5 \tan 25.8^\circ = 13.5(0.483) = 6.52 \text{ kVAR lagging}$$

$$S = \sqrt{P^2 + Q^2} = \sqrt{(13.5)^2 + (6.52)^2} = \sqrt{182 + 42.5} = \sqrt{224.5} = 15 \text{ kVA}$$

**Step 2.** Find the power relationships for the *total* load.

$$\text{Total kW load } P_T = 9.36 + 13.5 = 22.9 \text{ kW} \quad \text{Ans.}$$

$$\text{Total kVAR load } Q_T = 7.02 + 6.52 = 13.5 \text{ kVAR lagging} \quad \text{Ans.}$$

From the power-triangle relationships (Fig. 17-22*d*),

$$S_T = \sqrt{P_T^2 + Q_T^2} = \sqrt{(22.9)^2 + (13.5)^2} = \sqrt{524 + 182} = \sqrt{706} = 26.6 \text{ kVA} \quad \text{Ans.}$$

$$\text{PF} = \cos \theta = \frac{P_T}{S_T} = \frac{22.9}{26.6} = 0.861 \text{ lagging} \quad \text{Ans.}$$

**Step 3.** Find the current relationships.

$$S_T = \sqrt{3}V_L I_L \quad (17-9)$$


from which

$$I_L = \frac{S_T}{\sqrt{3}V_L} = \frac{26.5(1000)}{1.73(120)} = 128 \text{ A} \quad \text{Ans.}$$

$$I_L = \sqrt{3}I_p \quad (17-2)$$

from which 
$$I_p = \frac{I_L}{\sqrt{3}} = \frac{128}{1.73} = 74 \text{ A} \quad \text{Ans.}$$

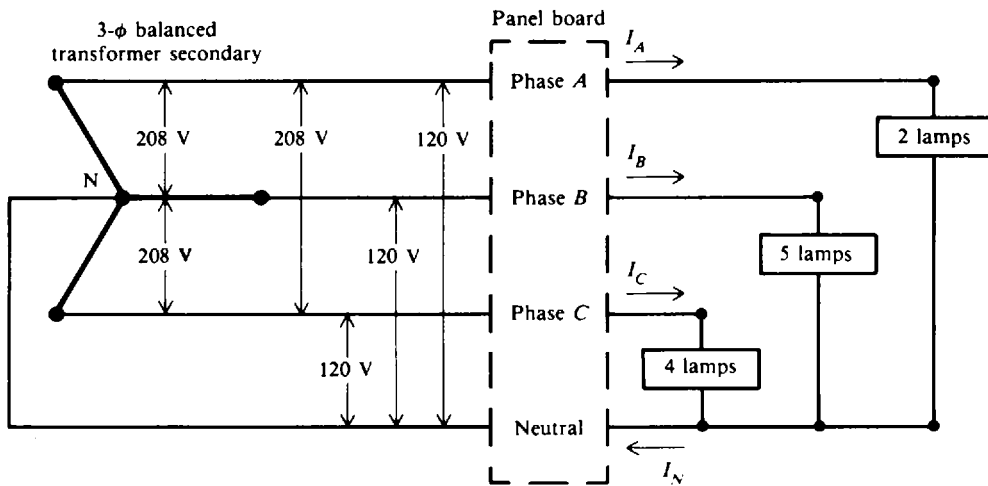**17.13** On a 120/208-V four-wire Y system, two lamps are connected from phase A to neutral, five lamps from phase B to neutral, and four lamps from phase C to neutral (Fig. 17-23*a*). If all the lamps have the same rating and each draws 2 A, find the current in each phase and the neutral current.



(*a*) Unbalanced loading on four-wire, 3- $\phi$  Y circuit  
**Fig. 17-23*a*** Unbalanced loading on four-wire, 3- $\phi$  Y circuit

Since each lamp draws 2 A,

$$I_A = 2 \text{ lamps} \times 2 \text{ A} = 4 \text{ A} \quad \text{Ans.}$$

$$I_B = 5 \text{ lamps} \times 2 \text{ A} = 10 \text{ A} \quad \text{Ans.}$$

$$I_C = 4 \text{ lamps} \times 2 \text{ A} = 8 \text{ A} \quad \text{Ans.}$$

Since the values of the load or phase currents are different, the load is unbalanced and current will flow in the neutral wire. The magnitude of  $I_N$  is the phasor sum of the three phase currents  $I_A$ ,  $I_B$ , and  $I_C$ .

$$I_N = \sqrt{I_x^2 + I_y^2}$$

where  $I_x$  is the sum of the phasor currents along the x axis and  $I_y$  is the sum of the phasor currents along the y axis. We draw the phasor diagram of currents, calculate their component values along the x and y axes, add these components, and then solve for  $I_N$ .

**Step 1.** Draw the current-phasor diagram (Fig. 17-23b).

We show  $I_A$  as the reference phasor and then show each load current  $120^\circ$  out of phase from the others.

**Step 2.** Find the component values of the three load currents and add them. Refer to Fig. 17-23b.

Along the  $x$  axis:  $I_A = 4 \text{ A}$        $I_B = -10 \cos 60^\circ = -5 \text{ A}$        $I_C = -8 \cos 60^\circ = -4 \text{ A}$

Along the  $y$  axis:  $I_A = 0 \text{ A}$        $I_B = 10 \sin 60^\circ = 8.66 \text{ A}$        $I_C = -8 \sin 60^\circ = -6.93 \text{ A}$

Then       $I_x = 4 - 5 - 4 = -5 \text{ A}$        $I_y = 0 + 8.66 - 6.93 = 1.73 \text{ A}$

**Step 3.** Calculate  $I_N$  (Fig. 17-23c).

$$I_N = \sqrt{I_x^2 + I_y^2} = \sqrt{(-5)^2 + (1.73)^2} = 5.29 \text{ A} \quad \text{Ans.}$$

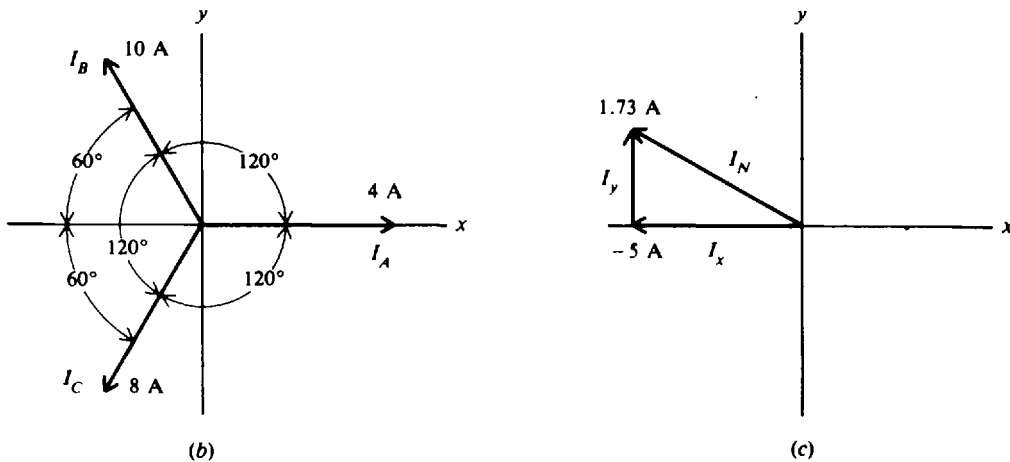


Fig. 17-23b, c

### Supplementary Problems

- 17.14 If the winding or phase voltage in the secondary is 120 V, find the secondary line voltage for Y and  $\Delta$  connections.    *Ans.* Y connection:  $V_L = 208 \text{ V}$ ;  $\Delta$ -connection:  $V_L = 120 \text{ V}$
- 17.15 A  $\Delta$ -connected generator supplies 100 V as line voltage and 25 A as line current. What is the voltage and current for each winding or phase?    *Ans.*  $V_p = 100 \text{ V}$ ;  $I_p = 14.5 \text{ A}$
- 17.16 A Y-connected generator supplies 40 A to each line and has a phase voltage of 50 V. Find the current through each phase and the line voltage.    *Ans.*  $I_p = 40 \text{ A}$ ;  $V_L = 86.5 \text{ V}$
- 17.17 In a Y- $\Delta$  transformer bank, each transformer has a voltage ratio of  $\dot{3}:1$ . If the primary line voltage is 625 V, find (a) the voltage across each primary winding, (b) the secondary line voltage, and (c) the voltage across each secondary winding.    *Ans.* (a) 361 V; (b) 120 V; (c) 120 V
- 17.18 The secondary line voltage of a  $\Delta$ - $\Delta$  transformer bank is 405 V and the secondary line current is 35 A. If each transformer has a turns ratio of 5:1, find (a) the primary line voltage, (b) the secondary winding or phase current, (c) the primary line current, and (d) the primary winding or phase current.    *Ans.* (a) 2025 V; (b) 20.2 A; (c) 7 A; (d) 4.05 A

17.19 Identify the three-phase transformer connections (Fig. 17-24a and b).

Ans. (a)  $\Delta$ -Y connection; (b) Y-Y connection

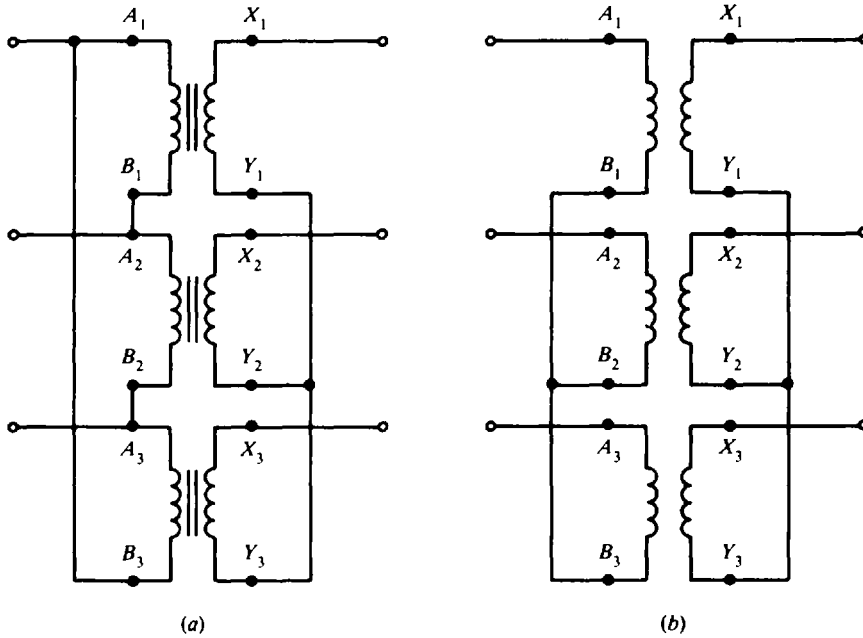


Fig. 17-24

- 17.20 A 3- $\phi$  system with balanced load carries 30 A at 0.75 power factor. If the line voltage is 220 V, find the power delivered. Ans.  $P = 8.56 \text{ kW}$
- 17.21 Find the kW and kVA drawn from a 3- $\phi$  generator when it is delivering 25 A at 240 V to a motor with 86 percent power factor. Ans.  $P = 8.93 \text{ kW}$ ;  $S = 10.4 \text{ kVA}$
- 17.22 Find the full-load line and phase currents for both  $\Delta$ - and Y-connected 3- $\phi$  alternators with ratings of 75 kVA at 480 V.  
 Ans.  $\Delta$ -connected:  $I_L = 90.3 \text{ A}$ ;  $I_p = 52.2 \text{ A}$ ; Y-connected:  $I_L = 90.3 \text{ A}$ ;  $I_p = 90.3 \text{ A}$
- 17.23 Of the four possible ways to connect transformers in three-phase systems, which one will give the highest secondary voltage for a given primary voltage? Ans.  $\Delta$ -Y
- 17.24 Find the line current in a balanced 3- $\phi$  system which delivers 36 kW at 0.95 power factor and 225 V. Ans.  $I_L = 97.4 \text{ A}$
- 17.25 A 3- $\phi$  system supplies 34.2 A at a line voltage of 208 V for a balanced load at 89 percent power factor. Find the kilovoltampere rating of the transformer. Ans.  $S = 12.3 \text{ kVA}$
- 17.26 A balanced 3- $\phi$  line carries 14 A in each line at 1100 V. If the power delivered is 22 kW, find the power factor of the load. Ans.  $\text{PF} = 0.826$
- 17.27 A three-phase system delivers a line current of 50 A at a line voltage of 220 V and 86.6 percent power factor. Find (a) the real power, (b) the reactive power, and (c) the apparent power.  
 Ans. (a)  $P = 16.5 \text{ kW}$ ; (b)  $Q = 9.53 \text{ kVAR}$ ; (c)  $S = 19.1 \text{ kVA}$
- 17.28 How many 60-W 110-V lamps can be connected to a balanced 3- $\phi$  system if the line current is 28.4 A and the line voltage is 110 V on the load side? Ans. 90 lamps



- 17.29 At full load, each of the three phases of a Y-connected generator delivers 150 A and 1329 V at a PF of 75 percent lagging. Find (a) the terminal voltage rating, (b) the kilovoltampere rating, and (c) the kilowatt rating. *Ans.* (a) 2300 V; (b) 598 kVA; (c) 448 kW
- 17.30 It is desired that a 10 000-kVA 3- $\phi$  60-Hz generator have a rated terminal voltage of 13 800 V when it is Y-connected. (a) What must be the voltage rating of each phase? Find (b) the kilovoltampere rating per phase and (c) the rated line current. *Ans.* (a) 7977 V; (b) 3333 kVA; (c) 419 A
- 17.31 A 3- $\phi$  transformer bank is designed to supply a 240-V industrial distribution system. The connected balanced 3- $\phi$  loads are as follows: 50-kW motor at PF = 0.80, 40-kW motor at PF = 0.85, fluorescent lighting load of 10 kW at PF = 0.90, and an incandescent lighting load of 15 kW at PF = 1.0. Find the total real power, total apparent power, total reactive power, and total PF of the load. *Ans.*  $P_T = 115$  kW;  $Q_T = 67.1$  kVAR lagging;  $S_T = 133$  kVA, PF = 86.5%
- 17.32 Find the total line current drawn by the connected loads of Prob. 17.31, assuming balanced conditions. *Ans.*  $I_L = 320$  A
- 17.33 For the distribution transformer bank (Fig. 17-25), find the total kilovoltampere load and the power factor of the load. *Ans.*  $S_T = 170$  kVA ( $P_T = 148$  kW,  $Q_T = 84.5$  kVAR lagging); PF = 0.868 lagging

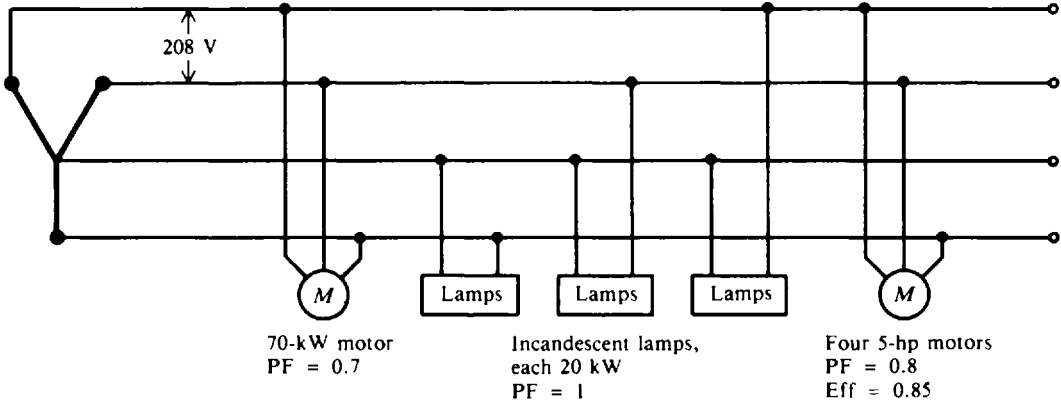


Fig. 17-25

- 17.34 From Fig. 17-26, find  $P_T$ ,  $Q_T$ ,  $S_T$ , PF, and  $I_L$ . *Ans.*  $P_T = 27.8$  kW;  $Q_T = 6.18$  kVAR lagging;  $S_T = 28.5$  kVA; PF = 0.975;  $I_L = 150$  A


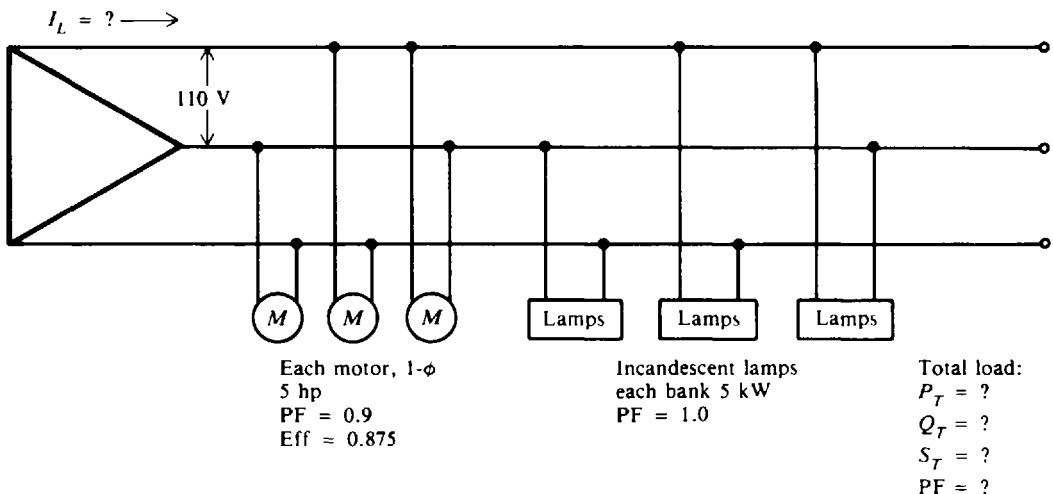


Fig. 17-26

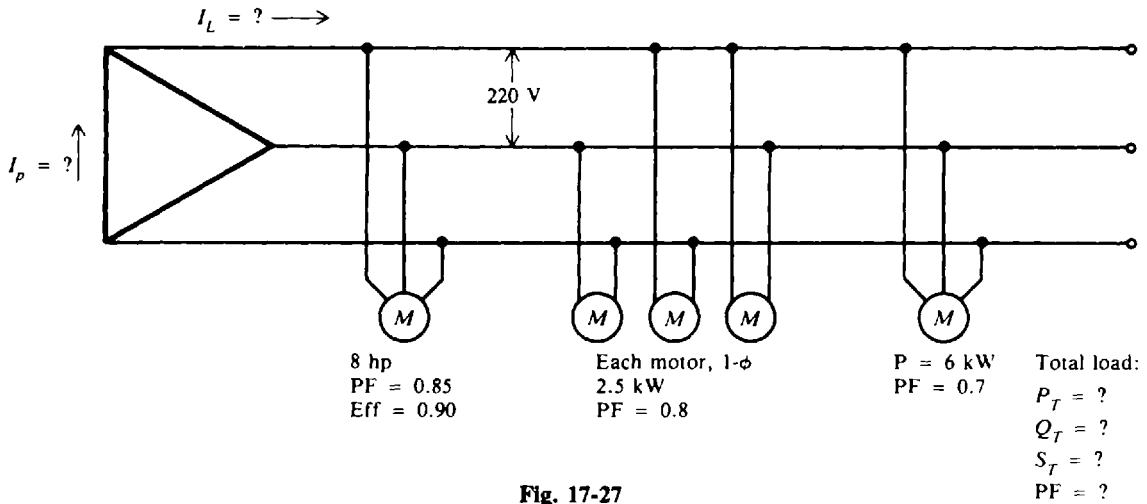
17.35 From Fig. 17-27, find  $P_T$ ,  $Q_T$ ,  $S_T$ , PF,  $I_L$ , and  $I_p$ .

Ans.  $P_T = 20.1$  kW;  $Q_T = 15.9$  kVAR lagging;  $S_T = 25.6$  kVA; PF = 0.785;  $I_L = 67.3$  A;  $I_p = 38.9$  A



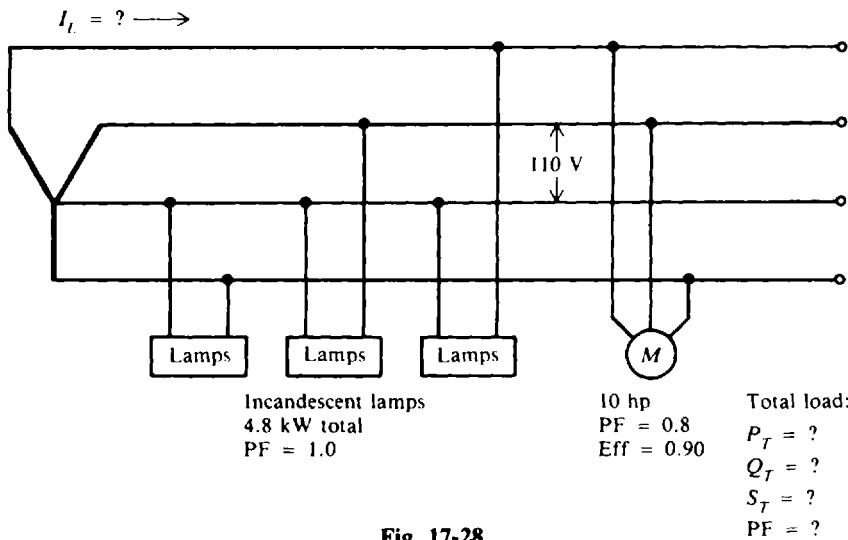17.36 From Fig. 17-28, find  $P_T$ ,  $Q_T$ ,  $S_T$ , PF, and  $I_L$ .

Ans.  $P_T = 13.1$  kW;  $Q_T = 6.24$  kVAR lagging;  $S_T = 14.5$  kVA; PF = 0.903;  $I_L = 43.9$  A



17.37 A 6-hp 3- $\phi$   $\Delta$ -connected motor operates at a power factor of 0.85 with an efficiency of 80 percent. If the line voltage is 220 V, find the line current. Ans.  $I_L = 17.3$  A

17.38 A Y-connected load of three 10- $\Omega$  resistors is connected to a 208-V 3- $\phi$  supply. Find the (a) voltage supplied to each resistor, (b) line current, and (c) total power used.

Ans. (a) 120 V; (b)  $I_L = 12$  A; (c) 4320 W

17.39 Three loads, each having a resistance of 16  $\Omega$  in series with an inductance of 12  $\Omega$ , are Y-connected to a 240-V 3- $\phi$  supply. Find the (a) impedance per phase, (b) current per phase, (c) 3- $\phi$  kilovoltampere, (d) PF, and (e) the 3- $\phi$  power in kilowatts.

Ans. (a)  $Z_p = 20 \Omega$ ; (b)  $I_p = 6.94$  A, (c) 2.89 kVA; (d) 0.80 lagging; (e) 2.31 kW

17.40 A  $\Delta$ -connected load draws 28.8 kVA from a 3- $\phi$  supply. The line current is 69.2 A and the PF of the load is 80 percent, lagging. Find the resistance and reactance of each phase (the kilovoltampere of one phase is one-third of the total). Ans. 4.8  $\Omega$  resistance; 3.6  $\Omega$  reactance

17.41 Find the following indicated quantities:

	Three-Phase Connection	Line Voltage $V_L, V$	Line Current $I_L, A$	Phase Voltage $V_p, V$	Phase Current $I_p, A$
(a)	$\Delta$	90	14	?	?
(b)	Y	?	?	50	10

Ans.

	Three-Phase Connection	$V_L, V$	$I_L, A$	$V_p, V$	$I_p, A$
(a)	$\Delta$	.....	.....	90	8.09
(b)	Y	86.5	10	.....	.....

17.42 Find the following indicated quantities for a  $\Delta$ -connected load:

	$V_L, V$	$I_L, A$	$V_p, V$	$I_p, A$	PF Lagging	$P_T, kW$
(a)	110	?	?	18	0.9	?
(b)	?	32	120	?	0.8	?
(c)	?	?	220	27	?	16

Ans.

	$V_L, V$	$I_L, A$	$V_p, V$	$I_p, A$	PF Lagging	$P_T, kW$
(a)	.....	31.1	110	.....	.....	5.33
(b)	120	.....	.....	18.5	.....	5.31
(c)	220	46.7	.....	.....	0.9	.....

17.43 For the  $\Delta$ -connected transformer secondary (Fig. 17-29), find the total line current.

Ans.  $I_L = 75.1 A$

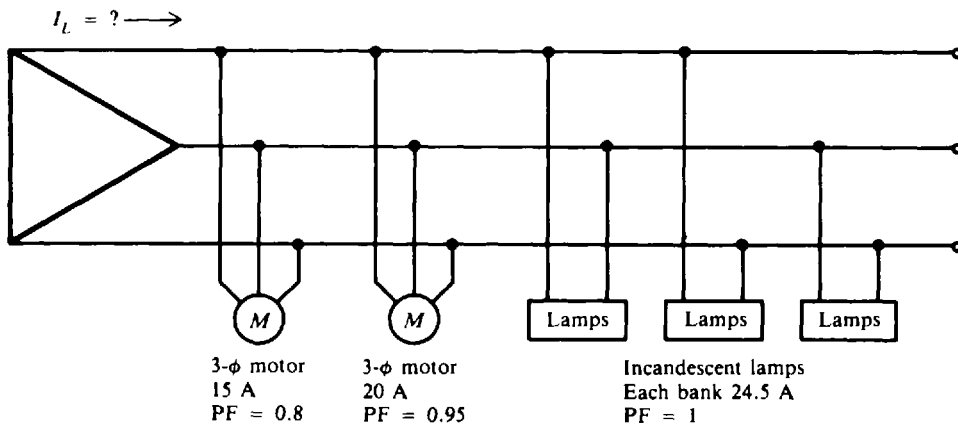


Fig. 17-29

17.44 For the  $\Delta$ -connected loads (Fig. 17-30), find the total line current. *Ans.*  $I_L = 57.7 \text{ A}$

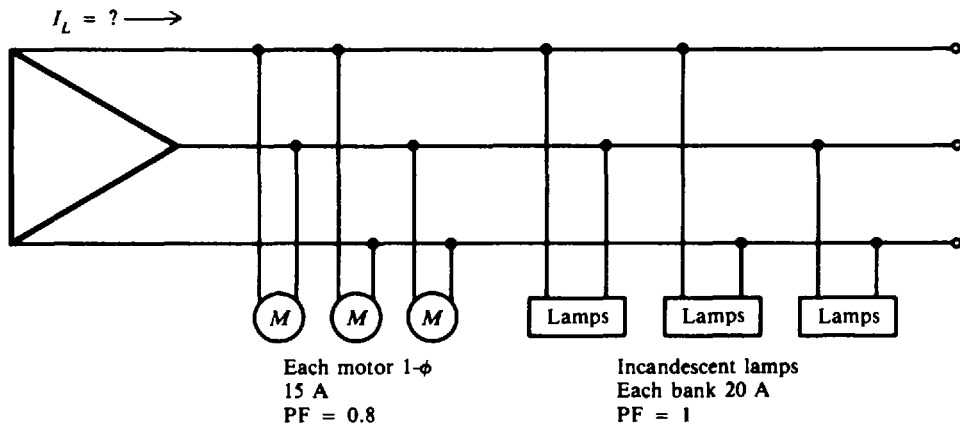


Fig. 17-30

17.45 Individual loads on separate feeders of a large power system are often unbalanced. The loads of a Y-connected generator, consisting of electric heaters, draw 150, 100, and 50 A. Find the neutral current. *Ans.*  $I_N = 86.6 \text{ A}$

17.46 An unbalanced four-wire Y load has load currents of 3, 5, and 10 A. Calculate the value of the neutral current. *Ans.*  $I_N = 6.24 \text{ A}$

## Series and Parallel Resonance

We have observed that in many circuits inductors and capacitors are connected in series or in parallel. Such circuits are often referred to as *RLC* circuits. One of the most important characteristics of a *RLC* circuit is that it can be made to respond most effectively to a single given frequency. When operated in this condition, the circuit is said to be in *resonance* with or *resonant* to the operating frequency.

A series or a parallel *RLC* circuit that is operated at resonance has certain properties that allow it to respond selectively to certain frequencies while rejecting others. A circuit operated to provide frequency selectivity is called a *tuned circuit*. Tuned circuits are used in impedance matching, bandpass filters, and oscillators.

### SERIES RESONANCE

The *RLC* series circuit (Fig. 18-1a) has an impedance  $Z = \sqrt{R^2 + (X_L - X_C)^2}$ . The circuit is at resonance when the inductive reactance  $X_L$  is equal to the capacitive reactance  $X_C$  (Fig. 18-1b).

$$X_L = X_C$$

where  $X_L = 2\pi fL$

$$X_C = \frac{1}{2\pi fC}$$

Then at resonance,

$$2\pi fL = \frac{1}{2\pi fC}$$

Solving for  $f$ ,


$$f^2 = \frac{1}{(2\pi)^2 LC}$$

$$f = f_r = \frac{1}{2\pi\sqrt{LC}} = \frac{0.159}{\sqrt{LC}} \quad (18-1)$$

where  $f_r$  = resonant frequency, Hz

$L$  = inductance, H

$C$  = capacitance, F

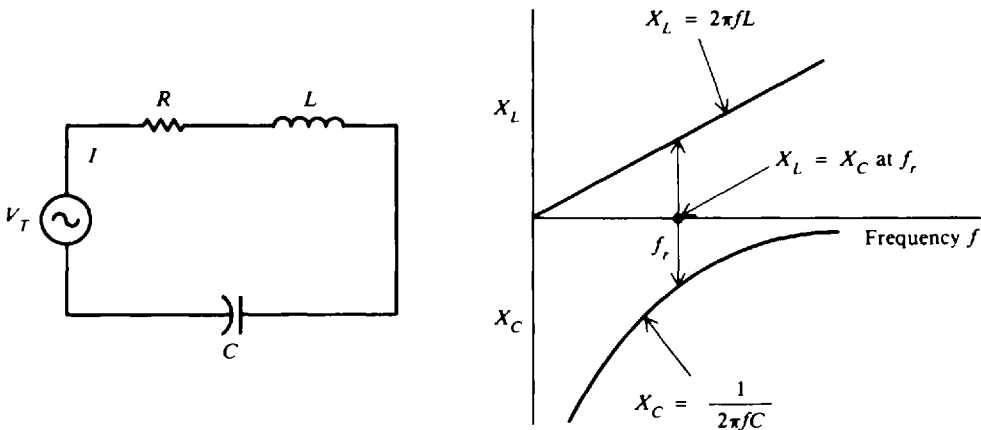

(a) Schematic diagram

(b)  $X_L = X_C$  but are  $180^\circ$  out of phase at  $f_r$

**Fig. 18-1** Series resonance for *RLC* circuit at resonant frequency  $f_r$ .

For any  $LC$  product [Eq. (18-1)] there is only one resonant frequency. Thus, various combinations of  $L$  and  $C$  may be used to achieve resonance if the  $LC$  product remains the same. Equation (18-1) may be solved for  $L$  or  $C$  to find the inductance or capacitance needed to form a series resonant circuit at a given frequency.

$$L = \frac{1}{4\pi^2 f_r^2 C} = \frac{0.0254}{f_r^2 C} \tag{18-2}$$

$$C = \frac{1}{4\pi^2 f_r^2 L} = \frac{0.0254}{f_r^2 L} \tag{18-3}$$

Since  $X_L = X_C$ ,  $X_L - X_C = 0$  so that

$$Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{R^2} = R$$

Since the impedance at resonance  $Z$  equals the resistance  $R$ , the impedance is a minimum. With minimum impedance, the circuit has maximum current determined by  $I = V/R$ . The resonant circuit has a phase angle equal to  $0^\circ$  so that the power factor is unity.

At frequencies below the resonant frequency (Fig. 18-2a),  $X_C$  is greater than  $X_L$  so the circuit consists of resistance and capacitive reactance. However, at frequencies above the resonant frequency (Fig. 18-2a),  $X_L$  is greater than  $X_C$  so the circuit consists of resistance and inductive reactance. At resonance, maximum current is produced for different values of resistance (Fig. 18-2b). With a low resistance, the current increases sharply toward and decreases sharply from its maximum current as the circuit is tuned to and away from the resonant frequency. This condition where the curve is narrow at the resonant frequency provides good selectivity. With an increase of resistance, the curve broadens so that selectivity is less.

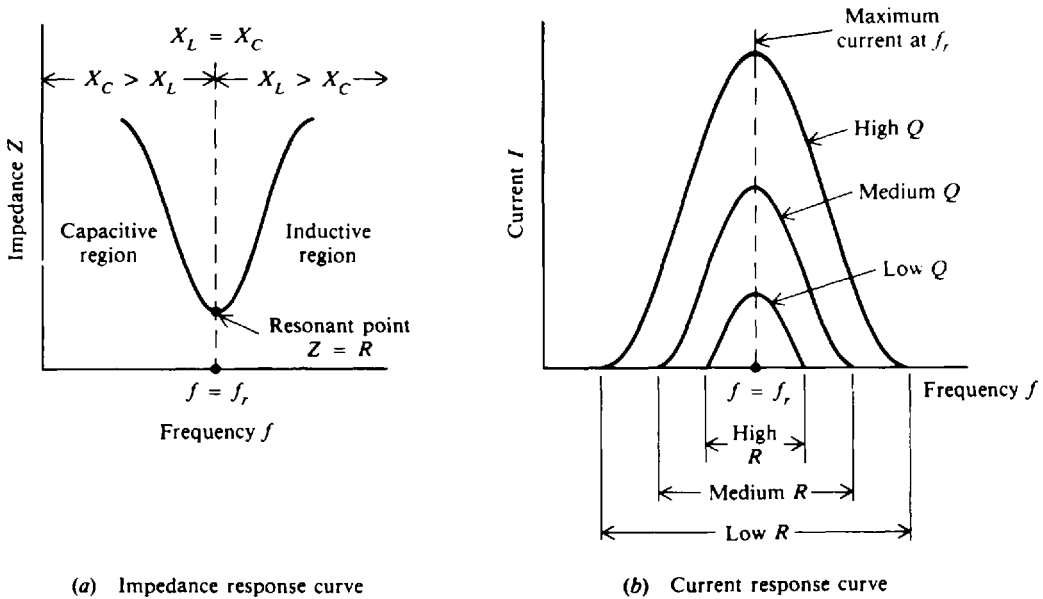


Fig. 18-2 Characteristics of series RLC circuit at resonance

**Example 18.1** Find the resonant frequency of a simple radio receiver tuning circuit (Fig. 18-3) if the inductance is  $200 \mu\text{H}$  and the capacitor is set at  $200 \text{ pF}$ .

$$L = 200 \mu\text{H} = 200 \times 10^{-6} \text{ H} = 2 \times 10^{-4} \text{ H} \quad C = 200 \text{ pF} = 200 \times 10^{-12} \text{ F} = 2 \times 10^{-10} \text{ F}$$

$$f_r = \frac{0.159}{\sqrt{LC}} \tag{18-1}$$

$$= \frac{0.159}{\sqrt{(2 \times 10^{-4})(2 \times 10^{-10})}} = 795\,000 \text{ Hz} = 795 \text{ kHz} \quad \text{Ans.}$$

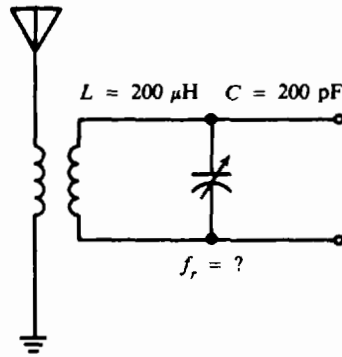


Fig. 18-3 Radio receiver tuning circuit

Notice that the voltage applied to this circuit is the voltage induced across the secondary winding, which is in series with the capacitor. Thus, while the circuit looks like a parallel circuit, it is a series circuit because of the series voltage input.

**Example 18.2** Find the value in picofarads of a tuning capacitor placed in series with a 400-μH inductance in order to provide resonance for a 500-kHz signal.

$$L = 400 \mu\text{H} = 400 \times 10^{-6} \text{H} = 4 \times 10^{-4} \text{H} \quad f_r = 500 \text{ kHz} = 500 \times 10^3 \text{ Hz} = 5 \times 10^5 \text{ Hz}$$

$$C = \frac{0.0254}{f_r^2 L} \tag{18-3}$$

$$= \frac{0.0254}{(5 \times 10^5)^2 (4 \times 10^{-4})} = 2.54 \times 10^{-10} \text{ F} = 254 \times 10^{-12} \text{ F} = 254 \text{ pF} \quad \text{Ans.}$$

**Example 18.3** A voltage of 15 V ac is applied to a 150-μH coil connected in series with a 169-pF capacitor (Fig. 18-4). The total series resistance is 7.5 Ω, which includes the coil winding resistance, the resistance of the connecting leads, and the leakage resistance of the capacitor. This circuit is resonant at 1000 kHz. Find the magnitude of the current and of the voltage drops across each element. Describe the circuit when the frequency of the applied voltage is 800 kHz, 1000 kHz, and 1200 kHz.

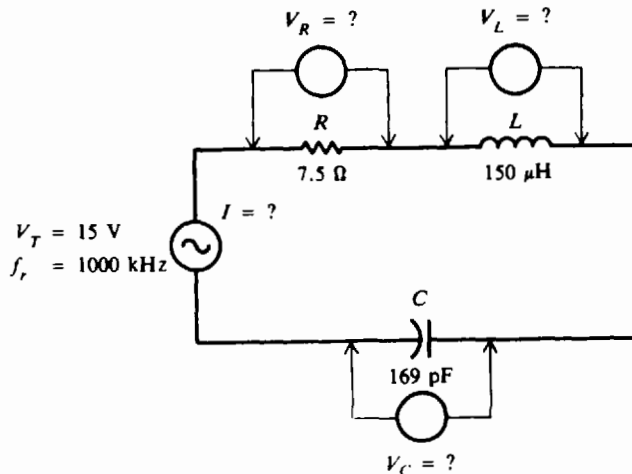


Fig. 18-4 Series RLC circuit

**Step 1.** Find the current at resonance.

At resonance,

$$Z = R = 7.5 \Omega$$

By Ohm's law,

$$I = \frac{V_T}{R} = \frac{15}{7.5} = 2 \text{ A} \quad \text{Ans.}$$

**Step 2.** Find the voltage drops at resonance.

$$X_L = X_C = 2\pi fL = 6.28(10^6)(150 \times 10^{-6}) = 942 \Omega$$

Then  $V_R = IR = 2(7.5) = 15 \text{ V}$       *Ans.*

$$V_L = IX_L = 2(942) = 1884 \text{ V} \quad \text{Ans.}$$

$$V_C = IX_C = 2(942) = 1884 \text{ V} \quad \text{Ans.}$$

Thus we see that the voltage drops across both the inductance and the capacitance are 125 times greater than the applied voltage. Since at resonance the high reactive voltages  $V_L$  and  $V_C$  cancel each other, they have no effect on the load. However, the insulation of the coil connectors and the dielectric of the capacitor must be designed to withstand a voltage about 125 times greater than the applied voltage.

**Step 3.** Describe the behavior of the circuit as a function of frequency. At a frequency  $f = 800 \text{ kHz}$ , which is *below* the resonant frequency:

$$X_L = 6.28fL = 6.28(8 \times 10^5)(150 \times 10^{-6}) = 754 \Omega$$

$$X_C = \frac{1}{6.28fC} = \frac{1}{6.28(8 \times 10^5)(169 \times 10^{-12})} = 1178 \Omega$$

Since  $X_C > X_L$ , the circuit is *capacitive* below the resonant frequency.      *Ans.*

At the resonant frequency  $f_r = 1000 \text{ kHz}$ :

$$X_L = X_C = 942 \Omega$$

Therefore, at resonance the circuit is *purely resistive*.      *Ans.*

At a frequency  $f = 1200 \text{ kHz}$ , which is *above* the resonant frequency:

$$X_L = 6.28fL = 6.28(12 \times 10^5)(150 \times 10^{-6}) = 1130 \Omega$$

$$X_C = \frac{1}{6.28fC} = \frac{1}{6.28(12 \times 10^5)(169 \times 10^{-12})} = 785 \Omega$$

Since  $X_L > X_C$ , the circuit is *inductive* above the resonant frequency.      *Ans.*

Refer to Fig. 18-2a, which confirms the nature of this circuit as a function of frequency.

## Q OF SERIES CIRCUIT

The degree to which a series-tuned circuit is selective is proportional to the ratio of its inductive reactance to its resistance. This ratio  $X_L/R$  is known as the  $Q$  of the circuit and is expressed as follows:

$$Q = \frac{X_L}{R} \quad (18-4)$$

where  $Q$  = quality factor or figure of merit

$X_L$  = inductive reactance,  $\Omega$

$R$  = resistance,  $\Omega$

The lower the resistance, the higher the value of  $Q$ . The higher the  $Q$ , the sharper and more selective is the resonant curve.  $Q$  has the same value if calculated with  $X_C$  instead of  $X_L$  since they are equal at resonance.  $Q = 150$  is a high  $Q$ . Typical values are 50 to 250. Less than 10 is a low  $Q$ ; more than 300 is a very high  $Q$ . See Fig. 18-2b.

The  $Q$  of the circuit is generally considered in terms of  $X_L$  since the coil has the series resistance of the circuit. In this case, the  $Q$  of the coil and the  $Q$  of the series resonant circuit are the same. If extra resistance is added, the  $Q$  of the circuit will be less than the  $Q$  of the coil. The highest possible  $Q$  for the circuit is the  $Q$  of the coil.

The  $Q$  of the resonant circuit can be considered a magnification factor that determines how much the voltage across  $L$  or  $C$  is increased by the resonant rise of current in a series circuit.

$$V_L = V_C = QV_T \quad (18-5)$$



**Example 18.4** Find the  $Q$  for the series resonant circuit and the rise of voltage across  $L$  or  $C$  due to resonance (Fig. 18-4).

Use Eq. (18-4) to find  $Q$ .

$$Q = \frac{X_L}{R} = \frac{942}{7.5} = 125.6 \quad \text{Ans.}$$

Use Eq. (18-5) to find  $V_L$  or  $V_C$ .

$$V_L = V_C = QV_T = 125.6(15) = 1884 \text{ V} \quad \text{Ans.}$$

This is the same value calculated for  $V_L$  or  $V_C$  at resonance in Example 18.3.

## PARALLEL RESONANCE

### Pure Parallel LC Circuit

In the pure  $LC$  parallel-tuned circuit (that is, one in which there is no resistance), the coil and capacitor are placed in parallel and the applied voltage  $V_T$  appears across these circuit components (Fig. 18-5). In this parallel-tuned circuit, as in the series-tuned circuit, resonance occurs when the inductive reactance is equal to the capacitive reactance.

$$X_L = X_C$$


Because the applied voltage is common to both branches,

$$V_L = V_C$$

so that

$$\frac{V_L}{X_L} = \frac{V_C}{X_C}, \quad I_L = I_C$$

The current in the inductive branch  $I_L$  equals the current in the capacitive branch  $I_C$ .  $I_L$  lags the applied voltage  $V_T$  by  $90^\circ$ , while  $I_C$  leads the voltage by  $90^\circ$  (Fig. 18-5b). Since the phasor currents  $I_L$  and  $I_C$  are equal and out of phase by  $180^\circ$ , their vector sum is zero so that the total current  $I_T$  is zero. Under this condition the impedance of the circuit at the resonant frequency must be infinite in value.

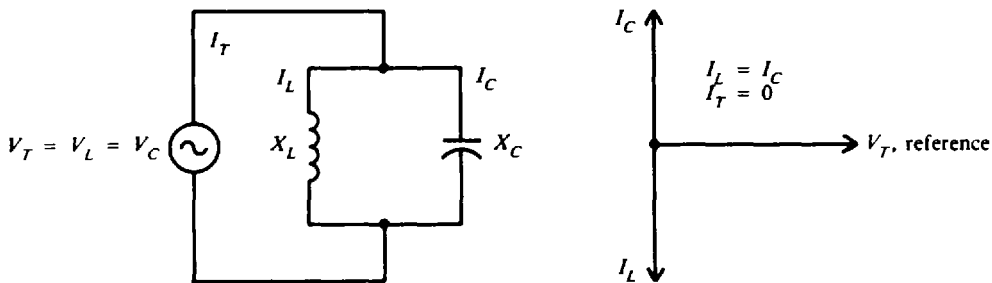

(a) Schematic diagram

(b) Current-phasor diagram at resonance

Fig. 18-5 Pure  $LC$  parallel circuit

The formula for the resonant frequency of a pure  $LC$  parallel-tuned circuit is the same as that for a series tuned circuit.

$$f_r = \frac{1}{2\pi\sqrt{LC}} = \frac{0.159}{\sqrt{LC}} \quad (18-1)$$

If the resonant frequency is known, then the inductance or capacitance for a parallel resonant LC circuit can be found by formulas.

$$L = \frac{0.0254}{f_r^2 C} \tag{18-2}$$

$$C = \frac{0.0254}{f_r^2 L} \tag{18-3}$$

**Example 18.5** A parallel resonant circuit appears as an infinite impedance (or open circuit) at the resonant frequency. This makes it possible to reject or “trap” a wave of a definite frequency in antenna circuits. A 400-μH coil and a 25-pF capacitor are placed in parallel to form a “wave trap” in an antenna. Find the resonant frequency that the circuit will reject. The resistance of the circuit is negligible.

$$L = 400 \mu\text{H} = 4 \times 10^{-4} \text{ H} \quad C = 25 \text{ pF} = 25 \times 10^{-12} \text{ F}$$

$$f_r = \frac{0.159}{\sqrt{LC}} \tag{18-1}$$

$$= \frac{0.159}{\sqrt{(4 \times 10^{-4})(25 \times 10^{-12})}} = 1590 \text{ kHz} \quad \text{Ans.}$$

**Example 18.6** The capacitance of a parallel resonant circuit used as a wave trap in an antenna circuit is 400 pF. Find the value of the parallel inductance in order to reject an 800-kHz wave.


$$f = 800 \text{ kHz} = 8 \times 10^5 \text{ Hz} \quad C = 400 \text{ pF} = 400 \times 10^{-12} \text{ F}$$

$$L = \frac{0.0254}{f^2 C} \tag{18-2}$$

$$= \frac{0.0254}{(8 \times 10^5)(400 \times 10^{-12})} = 9.92 \times 10^{-5} = 99.2 \mu\text{H} \quad \text{Ans.}$$

**Practical Parallel LC Circuit**

In a practical LC parallel-tuned circuit (Fig. 18-6a), there is some resistance, most of which is due to the resistance of the inductor wire. The resonant frequency of a parallel circuit also is defined as that frequency at which the parallel circuit acts as a pure resistance. Therefore, the line current  $I_T$  must be in phase with the applied voltage  $V_T$  (unity power factor) (Fig. 18-6b). This means that the out-of-phase or quadrature component of the current through the inductive branch  $I_L$  must be equal to the current through the capacitive branch  $I_C$ ; and the total line current  $I_T$  equals the in-phase component of the current through the inductive branch, or  $I_T = I_R$  (Fig. 18-6b). Since the impedance is maximum,  $I_T$  is minimum.

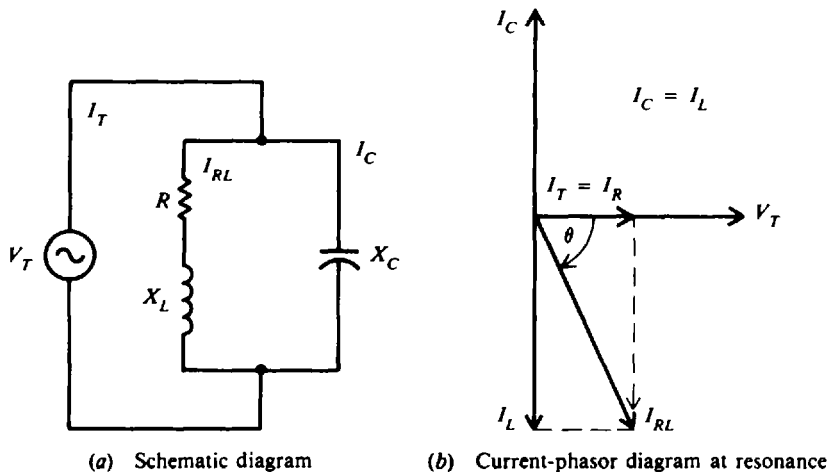

**Fig. 18-6** Practical parallel LC circuit

The resonant frequency for the circuit (Fig. 18-6a) is

$$f_r = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}} \tag{18-6}$$

- where  $f_r$  = resonant frequency, Hz
- $L$  = inductance, H
- $C$  = capacitance, F
- $R$  = resistance,  $\Omega$

If the  $Q$  of the coil is high, say greater than 10, or the term  $1/LC \gg R^2/L^2$ , then, for practical purposes, the term  $R^2/L^2$  can be disregarded. The result is that Eq. (18-6) becomes Eq. (18-1), the resonant-frequency formula for series resonance.

$$f_r = \frac{1}{2\pi\sqrt{LC}} \tag{18-1}$$

The total impedance at resonance of the practical  $LC$  parallel circuit is

$$Z_T = \frac{L}{RC} \tag{18-7}$$

In terms of quality factor  $Q$ ,  $Z_T$  at resonance can also be found by

$$Z_T = X_L Q = 2\pi f_r L Q \tag{18-8}$$

or

$$Z_T = \frac{Q}{2\pi f_r C} \tag{18-9}$$

The impedance  $Z_T$  of a practical parallel circuit is maximum at the resonant frequency and decreases at frequencies below and above the resonant frequency (Fig. 18-7a). An increase in resistance decreases the impedance and causes the impedance to vary less “sharply” as the circuit is tuned over a band of frequencies below and above the resonant frequency (Fig. 18-7b). At frequencies below resonance,  $X_C > X_L$  and  $I_L > I_C$  so that the parallel-tuned circuit is inductive (Figs. 18-7a and c). At frequencies above resonance, the reverse condition is true,  $X_L > X_C$  and  $I_C > I_L$ , so that now the circuit is capacitive (Figs. 18-7a and c). Since the impedance  $Z_T$  is maximum at parallel resonance,  $I_T$  is minimum (Fig. 18-7c).

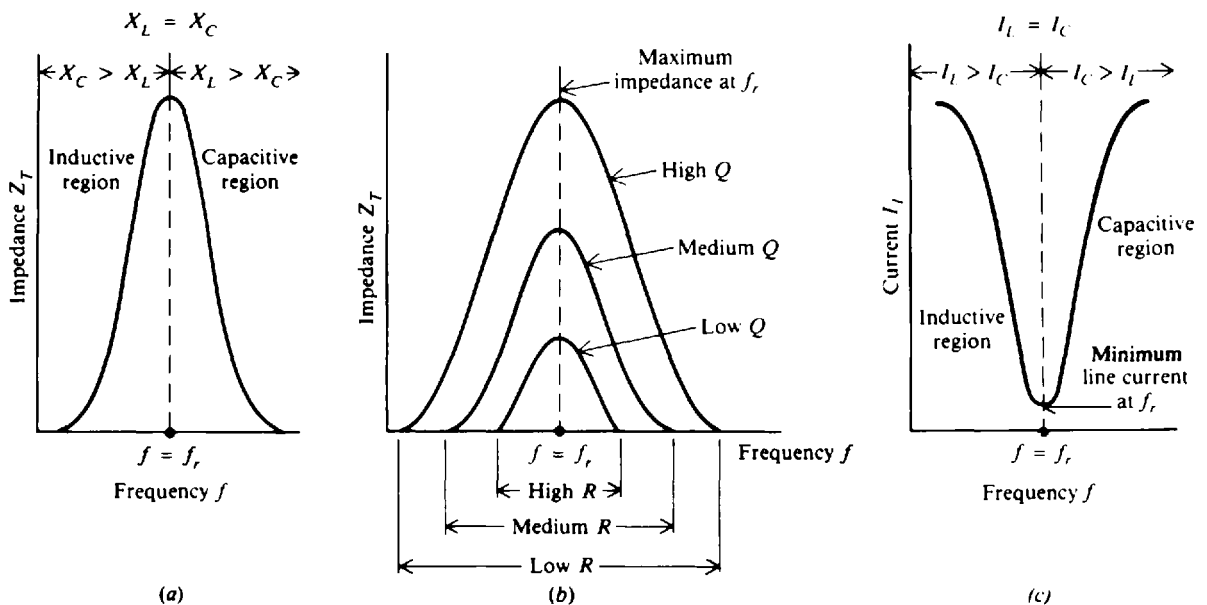


Fig. 18-7 Impedance and current response curves of practical parallel  $LC$  circuit at resonance

**Q OF PARALLEL CIRCUIT**

For a parallel resonant circuit in which  $R$  is very low compared with  $X_L$ ,

$$Q = \frac{X_L}{R} \tag{18-4}$$

where  $R$  is the resistance of the coil in series with  $X_L$  (Fig. 18-6a). If the resistance of the source supply is very high and there is no other resistance branch shunting the tuned circuit, the  $Q$  of the parallel resonant circuit is the same as the  $Q$  of the coil.

**Example 18.7** In the circuit shown (Fig. 18-8a), find (a) the resonant frequency of the circuit, (b) the impedance of the circuit, and (c) the total current at resonance; and (d) draw the phasor diagram.

(a) Find  $f_r$ .

$$f_r = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}} \tag{18-6}$$


Compare  $1/LC$  with  $R^2/L^2$ .

$$\frac{1}{LC} = \frac{1}{(203 \times 10^{-6})(500 \times 10^{-12})} = 9.85 \times 10^{12}$$

$$\frac{R^2}{L^2} = \frac{(6.7)^2}{203 \times 10^{-6}} = \frac{44.9}{4.12 \times 10^{-8}} = 10.9 \times 10^8$$

Because  $9.85 \times 10^{12} \gg 10.9 \times 10^8$  or  $1/LC \gg R^2/L^2$ , the  $R^2/L^2$  term can be disregarded and Eq. (18-1) can be used.

$$f_r = \frac{1}{2\pi} \sqrt{\frac{1}{LC}} = \frac{1}{6.28} \sqrt{9.85 \times 10^{12}} = 500\,000 \text{ Hz} = 500 \text{ kHz} \quad \text{Ans.}$$

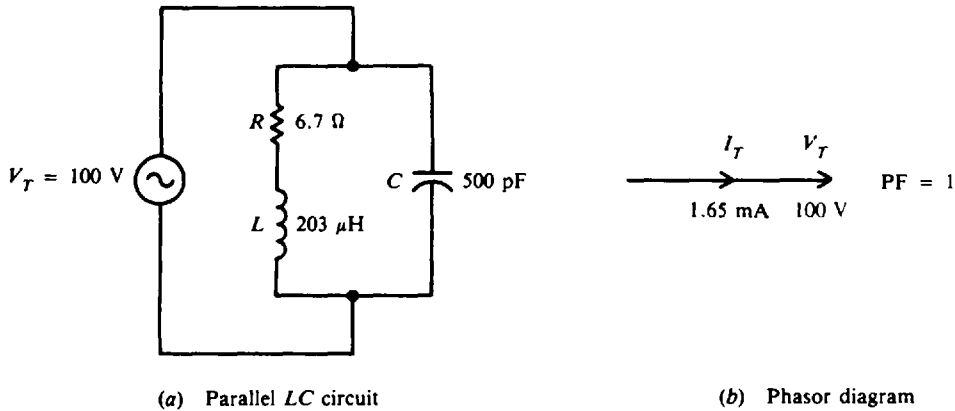

**Fig. 18-8**

(b) Find  $Z_T$ . Use Eq. (18-7).

$$Z_T = \frac{L}{RC} = \frac{203 \times 10^{-6}}{6.7(500 \times 10^{-12})} = 60\,600 \Omega = 60.6 \text{ k}\Omega \quad \text{Ans.}$$

(c) Find  $I_T$  by Ohm's law.

$$I_T = \frac{V_T}{Z_T} = \frac{100}{60.6 \times 10^3} = 1.65 \text{ mA} \quad \text{Ans.}$$

(d) Draw the phasor diagram (see Fig. 18-8b).


**Example 18.8** A coil with a  $Q$  of 71.6 is connected in parallel with a capacitor to produce resonance at 356 kHz. The impedance at resonance is found to be  $64\text{ k}\Omega$ . Find the value of the capacitor. Assume the  $Q$  of the resonant circuit is the same as the  $Q$  of the coil.

$$Z_T = \frac{Q}{2\pi f_r C} \quad (18-9)$$

from which  $C = \frac{Q}{2\pi f_r Z_T} = \frac{71.6}{6.28(356 \times 10^3)(64 \times 10^3)} = 5 \times 10^{-10}\text{ F} = 500\text{ pF}$     *Ans.*

### BANDWIDTH AND POWER OF RESONANT CIRCUIT

The width of the resonant band of frequencies centered around  $f_r$  is called the *bandwidth* of the tuned circuit. In Fig. 18-9a, the group of frequencies with a response of 70.7 percent of maximum or more is considered the bandwidth of the tuned circuit. For a series resonant circuit, the bandwidth is measured between the two frequencies  $f_1$  and  $f_2$ , producing 70.7 percent of the maximum current at  $f_r$  (Fig. 18-9b). For a parallel resonant circuit, the bandwidth is measured between the two frequencies, allowing 70.7 percent of the maximum total impedance at  $f_r$  (Fig. 18-9c).

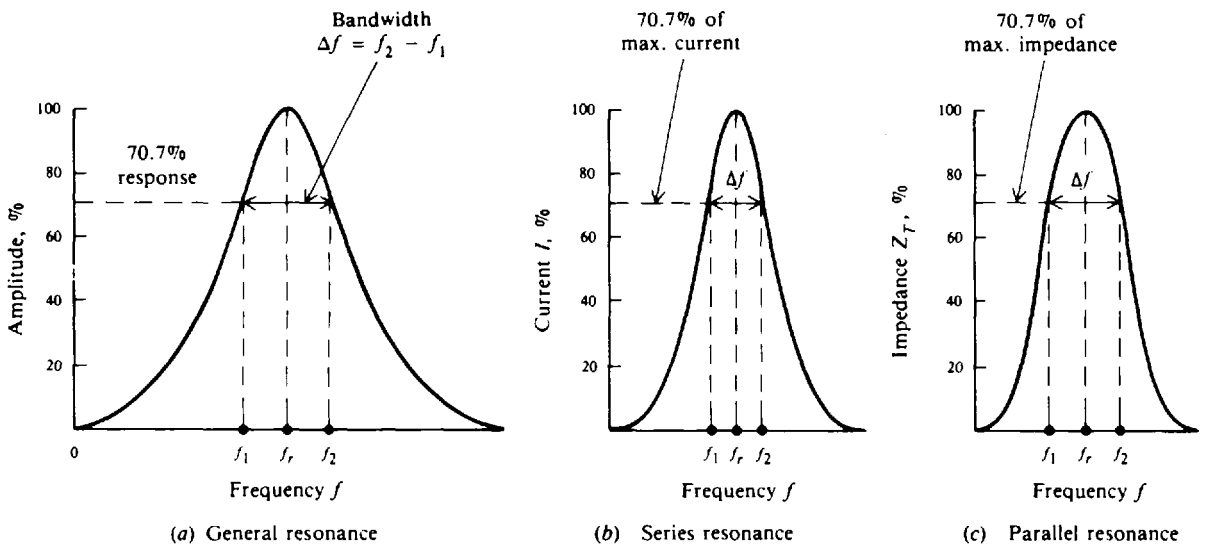

**Fig. 18-9** Bandwidth of a tuned LC circuit

At each frequency  $f_1$  and  $f_2$ , the net capacitive or net inductive reactance equals the resistance. Then  $Z_T$  of the series RLC resonant circuit is  $\sqrt{2}$  or 1.4 times greater than  $R$ . The current then is  $I/\sqrt{2} = 0.707I$ . Since power is  $I^2R$  or  $V^2/R$  and  $(0.707)^2 = 0.50$ , the bandwidth at 70.7 percent response in current or voltage is also the bandwidth of *half-power* points.

Bandwidth (BW) in terms of  $Q$  is


$$\text{BW} = f_2 - f_1 = \Delta f = \frac{f_r}{Q} \quad (18-10)$$

High  $Q$  means narrow bandwidth, whereas low  $Q$  yields greater bandwidth (Fig. 18-10).

Either  $f_1$  or  $f_2$  is separated from  $f_r$  by one-half of the total bandwidth (Fig. 18-9), so these edge frequencies can be calculated.

$$f_1 = f_r - \frac{\Delta f}{2} \quad (18-11)$$

$$f_2 = f_r + \frac{\Delta f}{2} \quad (18-12)$$

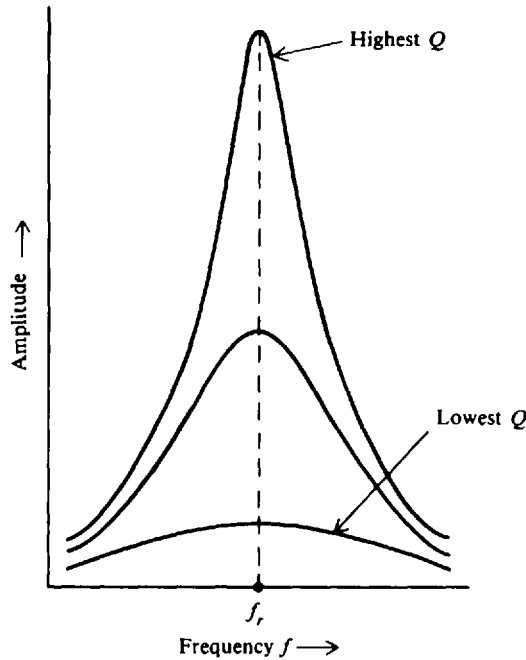

**Fig. 18-10** Resonant response curves: higher  $Q$  provides sharper resonance, lower  $Q$  provides broader response

**Example 18.9** An  $LC$  circuit resonant at 1000 kHz has a  $Q$  of 100. Find the total bandwidth  $\Delta f$  and the edge frequencies  $f_1$  and  $f_2$ .

$$\begin{aligned} \Delta f &= \frac{f_r}{Q} && (18-10) \\ &= \frac{1000 \times 10^3}{100} = 10 \times 10^3 = 10 \text{ kHz} && \text{Ans.} \end{aligned}$$

Since  $f_1$  and  $f_2$  have the same frequency spacing on each side of the resonant frequency, bandwidth can also be expressed as

$$\Delta f = \pm 5 \text{ kHz} \quad \text{Ans.}$$


Use Eq. (18-11) to find  $f_1$ .

$$f_1 = f_r - \frac{\Delta f}{2} = 1000 \times 10^3 - (5 \times 10^3) = 995 \times 10^3 = 995 \text{ kHz} \quad \text{Ans.}$$

Use Eq. (18-12) to find  $f_2$ .

$$f_2 = f_r + \frac{\Delta f}{2} = 1000 \times 10^3 + 5 \times 10^3 = 1005 \times 10^3 = 1005 \text{ kHz} \quad \text{Ans.}$$

**Example 18.10** For a series resonant circuit (Fig. 18-11), what is the real power consumed at resonance and at an edge frequency?

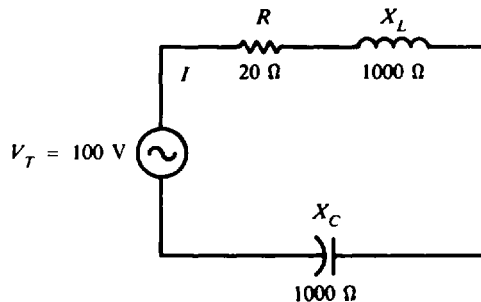

**Fig. 18-11** Series resonant circuit

At resonance: 
$$I = \frac{V_T}{R} = \frac{100}{20} = 5 \text{ A}$$

Power at resonance: 
$$P_r = I^2 R = 5^2(20) = 500 \text{ W} \quad \text{Ans.}$$

or 
$$P_r = V_T I = 100(5) = 500 \text{ W} \quad \text{Ans.}$$

Power at  $f_1$  or  $f_2$ : 
$$P_{f_1} = \left(\frac{I}{\sqrt{2}}\right)^2 R = \frac{I^2 R}{2} = \frac{5^2(20)}{2} = 250 \text{ W} \quad \text{Ans.}$$

or, since  $f_1$  and  $f_2$  are at the half-power points,

$$P_{f_1} = P_{f_2} = \frac{P_r}{2} = \frac{500}{2} = 250 \text{ W} \quad \text{Ans.}$$

## SUMMARY

Series and parallel resonance are compared in Table 18-1.

**Table 18-1 Comparison of Series and Parallel Resonance**

Series Resonance	Parallel Resonance ( $Q > 10$ )
$f_r = \frac{1}{2\pi\sqrt{LC}}$	$f_r = \frac{1}{2\pi\sqrt{LC}}$
$I$ maximum at $f_r$ with $\theta = 0^\circ$	$I_T$ minimum at $f_r$ with $\theta = 0^\circ$
Impedance $Z$ minimum at $f_r$	Impedance $Z_T$ maximum at $f_r$
$Q = \frac{X_L}{R}$	$Q = \frac{X_L}{R}$
$Q$ rise in voltage = $QV_T$	$Q$ rise in impedance = $QX_L$
Bandwidth $\Delta f = \frac{f_r}{Q}$	Bandwidth $\Delta f = \frac{f_r}{Q}$
Capacitive below $f_r$ , but inductive above $f_r$	Inductive below $f_r$ , but capacitive above $f_r$

## Solved Problems

- 18.1** What value of inductance must be connected in series with a 300-pF capacitor in order that the circuit be resonant to a frequency of 500 kHz?

$$C = 300 \text{ pF} = 300 \times 10^{-12} \text{ F} = 3 \times 10^{-10} \text{ F} \quad f = 500 \text{ kHz} = 500 \times 10^3 \text{ Hz} = 5 \times 10^5 \text{ Hz}$$

$$L = \frac{0.0254}{f_r^2 C} \quad (18-2)$$

$$= \frac{0.0254}{(5 \times 10^5)^2 (3 \times 10^{-10})} = 339 \mu\text{H} \quad \text{Ans.}$$

- 18.2** Prepare a table of various combinations of  $L$  and  $C$  required to produce resonance in a series  $RLC$  circuit at a frequency of 600 kHz.

Find the  $LC$  product for  $f_r = 600 \text{ kHz}$ .

$$L = \frac{0.0254}{f_r^2 C} \quad (18-2)$$

$$LC = \frac{0.0254}{f_r^2} = \frac{0.0254}{(6 \times 10^5)^2} = 7 \times 10^{-14}$$

If  $L$  is to be specified in microhenrys and  $C$  in microfarads, then

$$LC = \frac{7 \times 10^{-14}}{10^{-12}} = 0.07$$

Assume various values of  $L$  and solve for resulting values of  $C$  by Eq. (18-3). The result is the following table.

Ans.

Resonant Frequency, kHz	$L, \mu\text{H}$	$C, \mu\text{F}$	$LC$ Product
600	100	0.0007	0.07
600	50	0.0014	0.07
600	10	0.007	0.07
600	1	0.07	0.07
600	0.2	0.35	0.07
600	0.05	1.4	0.07
600	0.005	14	0.07
600	0.0005	140	0.07

- 18.3 A 4-mH coil and a 50-pF capacitor form the secondary side of a transformer (Fig. 18-12). Find the resonant frequency.

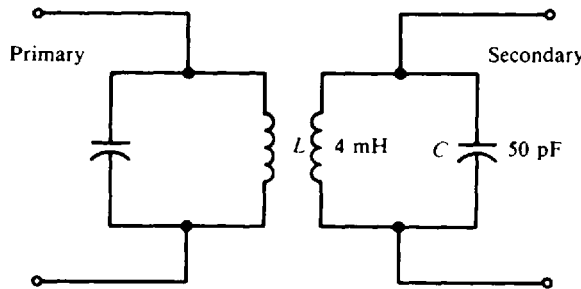


Fig. 18-12 Resonance in transformer secondary

$$L = 4 \text{ mH} = 4 \times 10^{-3} \text{ H} \quad C = 50 \text{ pF} = 50 \times 10^{-12} \text{ F}$$

Using Eq. (18-1),

$$f_r = \frac{0.159}{\sqrt{LC}} = \frac{0.159}{\sqrt{(4 \times 10^{-3})(50 \times 10^{-12})}} = 356 \text{ kHz} \quad \text{Ans.}$$

- 18.4 A series circuit has  $R = 40 \Omega$ ,  $L = 0.5 \text{ H}$ , and  $C = 0.2 \mu\text{F}$ . Find (a) the impedance and  $Q$  of the circuit to a frequency of 400 Hz, (b) the capacitance that must be added in parallel with the  $0.2 \mu\text{F}$  to produce resonance at this frequency, and (c) the impedance and  $Q$  of the coil at resonance.

(a) Find  $Z$  at  $f = 400 \text{ Hz}$ .

$$X_L = 6.28 fL = 6.28(400)(0.5) = 1256 \Omega$$

$$X_C = \frac{1}{2\pi fC} = \frac{1}{6.28(400)(0.2 \times 10^{-6})} = 1990 \Omega$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{40^2 + (1256 - 1990)^2} = \sqrt{40^2 + (-734)^2} = 735 \Omega \quad \text{Ans.}$$

At nonresonance, 
$$Q = \frac{X_L - X_C}{R} = \frac{734}{40} = 18.4 \quad \text{Ans.}$$



(b) Find the  $C$  that will produce resonance.

$$\begin{aligned}
 f &= 400 \text{ Hz} & L &= 0.05 \text{ H} \\
 C &= \frac{0.0254}{f_r^2 L} & & \\
 &= \frac{0.0254}{400^2(0.05)} = 0.3175 \mu\text{F} \approx 0.318 \mu\text{F}
 \end{aligned} \tag{18-3}$$

Since  $0.318 \mu\text{F}$  is needed for resonance and we have only  $0.2 \mu\text{F}$ , we must add  $0.118 \mu\text{F}$  ( $0.318 \mu\text{F} - 0.2 \mu\text{F}$ ) in parallel with  $0.2 \mu\text{F}$ , so

$$C = 0.118 \mu\text{F} \quad \text{Ans.}$$

(c) Find  $Z$  and  $Q$  at resonance.

$$Z = R = 40 \Omega \quad \text{Ans.}$$

Find  $X_C$  at resonance.

$$X_C = \frac{1}{2\pi f_r C} = \frac{1}{6.28(400)(0.3175 \times 10^{-6})} = 1254 \Omega \approx 1256 \Omega$$

Due to rounding off,  $X_C$  is not exactly equal to  $X_L$  ( $1256 \Omega$ ).  $X_L = X_C$  at resonance, so

$$Q = \frac{X_L}{R} = \frac{X_C}{R} = \frac{1256}{40} = 31.4 \quad \text{Ans.}$$

**18.5** A  $RLC$  series circuit with  $R = 5 \Omega$ ,  $C = 10 \mu\text{F}$ , and a variable inductance  $L$  has an applied voltage  $V_T = 110 \text{ V}$  with a frequency of  $60 \text{ Hz}$ .  $L$  is adjusted until the voltage across the resistor is a maximum. Find the current and voltage across each element.

The maximum voltage across the resistor occurs at resonance. At resonance,

$$X_C = \frac{1}{2\pi f C} = \frac{1}{6.28(60)(10 \times 10^{-6})} = 265 \Omega$$

$$X_L = X_C = 265 \Omega \quad \text{and} \quad Z = R = 5 \Omega$$

Then 
$$I = \frac{V_T}{Z} = \frac{110}{5} = 22 \text{ A} \quad \text{Ans.}$$

and 
$$V_R = IR = 22(5) = 110 \text{ V} \quad \text{Ans.}$$

$$V_L = IX_L = 22(265) = 5830 \text{ V} \quad \text{Ans.}$$

$$V_C = IX_C = 22(265) = 5830 \text{ V} \quad \text{Ans.}$$

**18.6** Find the minimum and maximum values of the capacitor needed to obtain resonance with a  $300\text{-}\mu\text{H}$  coil to frequencies between  $500$  and  $1500 \text{ kHz}$ .

For a minimum  $C$ ,  $f_r$  is equal to its maximum value of  $1500 \text{ kHz}$ .

$$C_{\min} = \frac{0.0254}{f_{r,\max}^2 L} = \frac{0.0254}{(1.5 \times 10^6)^2(300 \times 10^{-6})} = 3.76 \times 10^{-11} \text{ F} = 37.6 \text{ pF} \quad \text{Ans.}$$


For a maximum  $C$ ,  $f_r$  is equal to its minimum value of  $500 \text{ kHz}$ .

$$C_{\max} = \frac{0.0254}{f_{r,\min}^2 L} = \frac{0.0254}{(5 \times 10^5)^2(300 \times 10^{-6})} = 3.39 \times 10^{-10} \text{ F} = 339 \text{ pF} \quad \text{Ans.}$$

**18.7** A series  $RLC$  circuit with  $R = 25 \Omega$  and  $L = 0.6 \text{ H}$  has a leading phase angle of  $60^\circ$  at a frequency of  $40 \text{ Hz}$ . Find the frequency at which this circuit will be resonant.

**Step 1.** Draw the impedance triangle (Fig. 18-13) and solve for the net reactance  $X$ .

$$X = X_C - X_L = 25 \tan 60^\circ = 25(1.73) = 43.3 \Omega$$

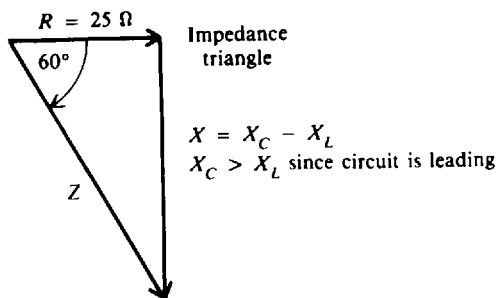

**Fig. 18-13** Impedance triangle

**Step 2.** Find  $X_L$  and then  $X_C$ .

$$X_L = 6.28 fL = 6.28(40)(0.6) = 151 \Omega$$

$$X_C - X_L = 43.3 \quad \text{from Step 1}$$

Then

$$X_C = 43.3 + X_L = 43.3 + 151 = 194 \Omega$$

**Step 3.** Find  $C$ .

$$C = \frac{1}{2\pi f X_C} = \frac{1}{6.28(40)(194)} = 20.5 \mu\text{F}$$

**Step 4.** Knowing  $L$  and  $C$ , find  $f_r$ , using Eq. (18-1).

$$f_r = \frac{0.159}{\sqrt{LC}} = \frac{0.159}{\sqrt{0.6(20.5 \times 10^{-6})}} = 45.3 \text{ Hz} \quad \text{Ans.}$$

**Step 5.** As a check, determine whether  $X_L = X_C$  at  $f_r = 45.3$  Hz.

$$X_L = 6.28 f_r L = 6.28(45.3)(0.6) = 171 \Omega$$

$$X_C = \frac{1}{2\pi f_r C} = \frac{1}{6.28(45.3)(20.5 \times 10^{-6})} = 171 \Omega$$

Therefore,  $X_L = X_C = 171 \Omega$ .

**18.8** A common application of resonant circuits is tuning a receiver to the carrier frequency of a desired radio station. The tuning is done by the air capacitor  $C$ , which can be varied with the plates completely in mesh (maximum capacitance) to out of mesh (minimum capacitance). Calculate the capacitance of the variable capacitor to tune for radio stations broadcasting at 500, 707, 1000, 1410, and 2000 kHz (Fig. 18-14).


$$C = \frac{0.0254}{f_r^2 L} \tag{18-3}$$

At  $f_r = 500$  kHz:  $C = \frac{0.0254}{(5 \times 10^5)^2 (239 \times 10^{-6})} = 4.25 \times 10^{-10} = 425 \text{ pF} \quad \text{Ans.}$

Since  $C \propto \frac{1}{f_r^2} \quad C_n = C_o \left( \frac{f_{r,o}}{f_{r,n}} \right)^2$

Let  $C_o = 425$  pF,  $f_{r,o} = 500$  kHz.

At  $f_r = 707$  kHz:  $C = 425 \left( \frac{500}{707} \right)^2 = 213 \text{ pF} \quad \text{Ans.}$

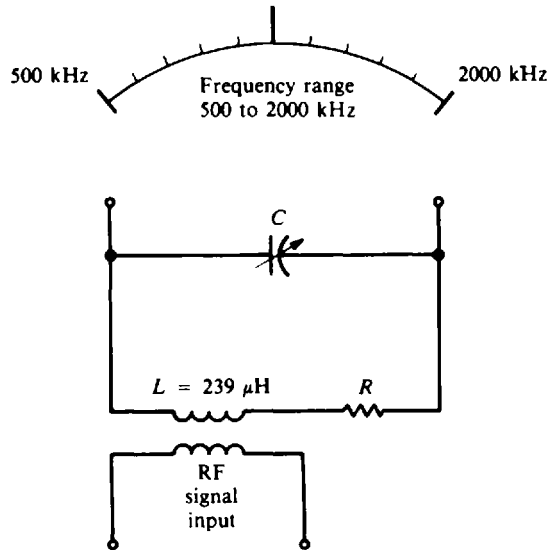

**Fig. 18-14** Tuning  $LC$  circuit through the AM radio band of 500 to 2000 kHz

At  $f_r = 1000$  kHz:  $C = 425 \left( \frac{500}{1000} \right)^2 = 106$  pF      *Ans.*

At  $f_r = 1410$  kHz:  $C = 425 \left( \frac{500}{1410} \right)^2 = 53.4$  pF      *Ans.*

At  $f_r = 2000$  kHz:  $C = 425 \left( \frac{500}{2000} \right)^2 = 26.6$  pF      *Ans.*

- 18.9** The  $Q$  of a coil in a series resonant circuit can be determined experimentally by measuring the  $Q$  rise in voltage across  $L$  or  $C$  and comparing this voltage with the generator or input voltage. As a formula

$$Q = \frac{V_{\text{out}}}{V_{\text{in}}} = \frac{V_L}{V_{\text{in}}} = \frac{V_C}{V_{\text{in}}}$$

This method is better than the  $X_L/R$  formula for determining  $Q$  because  $R$  is the ac resistance of the coil, which is not easily measured. A series circuit resonant at 400 kHz develops 100 mV across a 250- $\mu$ H coil with a 2-mV input. Calculate the  $Q$  and ac resistance of the coil.

$$Q = \frac{V_{\text{out}}}{V_{\text{in}}} = \frac{100 \text{ mV}}{2 \text{ mV}} = 50 \quad \textit{Ans.}$$

$$X_L = 2\pi f_r L = 6.28(4 \times 10^5)(250 \times 10^{-6}) = 628 \Omega$$

$$Q = \frac{X_L}{R} \quad (18-4)$$

$$R = \frac{X_L}{Q} = \frac{628}{50} = 12.6 \Omega \quad \textit{Ans.}$$

- 18.10** A 0.1-mH coil and a 1200-pF capacitor are connected in parallel to form the primary of an IF transformer (Fig. 18-15). What is the resonant frequency?

Since this is a case of a pure  $LC$  parallel tuned circuit,

$$f_r = \frac{0.159}{\sqrt{LC}} \quad (18-1)$$

$$L = 0.1 \text{ mH} = 0.1 \times 10^{-3} \text{ H} \quad C = 1200 \text{ pF} = 1200 \times 10^{-12} \text{ F} = 1.2 \times 10^{-9} \text{ F}$$

$$f_r = \frac{0.159}{\sqrt{(0.1 \times 10^{-3})(1.2 \times 10^{-9})}} = 459 \text{ kHz} \quad \text{Ans.}$$

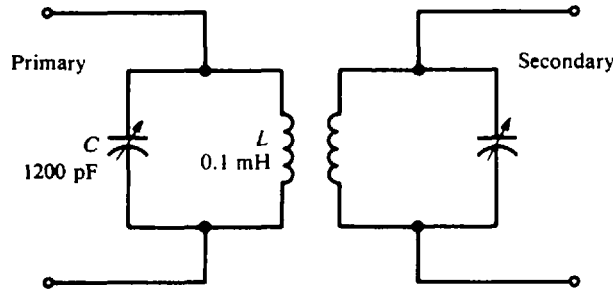


Fig. 18-15 LC tuning on the primary side of an IF transformer

18.11 The parallel tank circuit of an oscillator contains a coil of  $320 \mu\text{H}$ . Find the value of the capacitance at the resonant frequency of  $1 \text{ MHz}$ . Resistance is negligible.

Use Eq. (18-3).

$$C = \frac{0.0254}{f^2 L} = \frac{0.0254}{(1 \times 10^6)^2 (320 \times 10^{-6})} = 7.9 \times 10^{-11} \text{ F} = 79 \text{ pF} \quad \text{Ans.}$$

18.12 For the practical LC parallel circuit (Fig. 18-16), the formula for the equivalent or total impedance  $Z_T$  is

$$Z_T = \frac{1}{R^2 + X^2} \sqrt{(RX_L X_C - RX_C X)^2 + (R^2 X_C + X_L X_C X)^2} \quad \text{where} \quad X = X_L - X_C$$

Find the total impedance  $Z_T$  when  $f = 1000 \text{ kHz}$ ,  $R = 4 \Omega$ ,  $L = 100 \mu\text{H}$ , and  $C = 200 \text{ pF}$ . Round off  $Z_T$  to three significant figures.

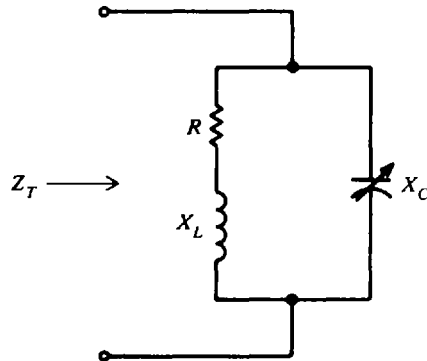


Fig. 18-16 Equivalent impedance of an LC parallel circuit

Step 1. Calculate  $X_L$ ,  $X_C$ , and  $X$ .

$$X_L = 2\pi fL = 6.28(1 \times 10^6)(100 \times 10^{-6}) = 628 \Omega$$

$$X_C = \frac{1}{2\pi fC} = \frac{1}{6.28(1 \times 10^6)(200 \times 10^{-12})} = 796 \Omega$$

$$X = X_L - X_C = 628 - 796 = -168 \Omega$$

**Step 2.** Substitute values of  $R$ ,  $X$ ,  $X_L$ , and  $X_C$  to calculate  $Z_T$ .

$$R^2 + X^2 = 4^2 + (-168)^2 = 2.82 \times 10^4$$

$$RX_LX_C - RX_CX = 4(628)(796) - 4(796)(-168) = 2.54 \times 10^6$$

$$R^2X_C + X_LX_CX = 4^2(796) + 628(796)(-168) = -84 \times 10^6$$

$$Z_T = \frac{1}{2.82 \times 10^4} \sqrt{(2.54 \times 10^6)^2 + (-84 \times 10^6)^2} = \frac{84 \times 10^6}{2.82 \times 10^4} = 2979 \Omega = 2980 \Omega \quad \text{Ans.}$$

In this case  $X_C > X_L$  ( $796 \Omega > 628 \Omega$ ) so that the circuit is inductive (more inductive current than capacitive current).

A simpler method for evaluating  $Z_T$  when  $R \ll X_L$ ,  $R \ll X_C$ , and  $R \ll X$  is by reducing the formula for  $Z_T$ . For these conditions,  $X_LX_CX$  is the dominating term so that the other terms under the square root sign can be disregarded. The result is

$$Z_T \cong \frac{1}{X^2} \sqrt{(X_LX_CX)^2} \cong \frac{X_LX_CX}{X^2} \cong \frac{X_LX_C}{X}$$

Since the inequality conditions hold true for this circuit ( $10 \Omega \ll 628 \Omega$ ,  $10 \Omega \ll 796 \Omega$ , and  $10 \Omega \ll 168 \Omega$ ),

$$Z_T \cong \frac{628(796)}{168} \cong 2976 \Omega \cong 2980, \text{ rounded off to three significant figures} \quad \text{Ans.}$$

which equals the value previously calculated.

**18.13** Find the resonant frequency and total impedance  $Z_T$  of the circuit (Fig. 18-16) when the component values remain the same as those in Prob. 18.12,  $R = 4 \Omega$ ,  $L = 100 \mu\text{H}$ , and  $C = 200 \text{ pF}$ .

**Step 1.** Find  $f_r$ .

$$f_r = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}} \quad (18-6)$$

Compare  $1/LC$  with  $R^2/L^2$ .

$$\frac{1}{LC} = \frac{1}{(100 \times 10^{-6})(200 \times 10^{-12})} = 5 \times 10^{13}$$

$$\frac{R^2}{L^2} = \frac{4^2}{(100 \times 10^{-6})^2} = \frac{16}{10^{-8}} = 16 \times 10^8$$

Since  $1/LC \gg R^2/L^2$ , the  $R^2/L^2$  term can be disregarded so  $f_r$  can be found by using Eq. (18-1).

$$f_r = \frac{1}{2\pi} \sqrt{\frac{1}{LC}} = \frac{1}{6.28} \sqrt{5 \times 10^{13}} = 1.13 \times 10^6 \text{ Hz} = 1130 \text{ kHz} \quad \text{Ans.}$$

**Step 2.** Find  $Z_T$  at resonance, using Eq. (18-7).

$$Z_T = \frac{L}{RC} = \frac{100 \times 10^{-6}}{4(200 \times 10^{-12})} = 125 \text{ k}\Omega \quad \text{Ans.}$$

**18.14** Find the total impedance of  $Z_T$  of the circuit (Fig. 18-16) when  $f = 1300 \text{ kHz}$  and the component values remain the same as those in Prob. 18.12,  $R = 4 \Omega$ ,  $L = 100 \mu\text{H}$ , and  $C = 200 \text{ pF}$ . Round off  $Z_T$  to three significant figures.

**Step 1.** Calculate  $X_L$ ,  $X_C$ , and  $X$ .

$$X_L = 2\pi fL = 6.28(1.3 \times 10^6)(100 \times 10^{-6}) = 816 \Omega$$

$$X_C = \frac{1}{2\pi fC} = \frac{1}{6.28(1.3 \times 10^6)(200 \times 10^{-12})} = 612 \Omega$$

$$X = X_L - X_C = 816 - 612 = 204 \Omega$$

**Step 2.** Substitute in the formula for  $Z_T$  given in Prob. 18.12.

$$R^2 + X^2 = 4^2 + 204^2 = 4.16 \times 10^4$$

$$RX_LX_C - RX_CX = 4(816)(612) - 4(612)(204) = 1.5 \times 10^6$$

$$R^2X_C + X_LX_CX = 4^2(612) + 816(612)(204) = 1.02 \times 10^8$$

$$Z_T = \frac{1}{4.16 \times 10^4} \sqrt{(1.5 \times 10^6)^2 + (1.02 \times 10^8)^2} = \frac{1.02 \times 10^8}{4.16 \times 10^4} = 2452 \Omega = 2450 \Omega \quad \text{Ans.}$$

In this case  $X_L > X_C$  ( $816 \Omega > 612 \Omega$ ) so that the circuit is capacitive (more capacitive current than inductive current).

A simpler method is to use the formula developed in Prob. 18.12.

$$Z_T \cong \frac{X_LX_C}{X} \cong \frac{816(612)}{204} \cong 2448 \Omega$$

$$\cong 2450 \Omega, \text{ rounded off to three significant figures}$$

which equals the value calculated by the exact formula.

In summary, the accompanying table shows the nature of a practical LC parallel circuit below the resonant frequency, at the resonant frequency, and above the resonant frequency.

Problem Number	Frequency	$Z_T$	Nature of LC Parallel Circuit
18.12	1000 kHz: Below resonant frequency	2980 $\Omega$	Inductive ( $X_C > X_L$ )
18.13	1130 kHz: At resonant frequency	125 k $\Omega$	Resistive, ( $X_C = X_L$ ) maximum impedance, minimum current
18.14	1300 kHz: Above resonant frequency	2450 $\Omega$	Capacitive ( $X_L > X_C$ )

**18.15** A parallel LC circuit tuned to 200 kHz with a 350- $\mu$ H coil has a measured impedance  $Z_T$  of 19 800  $\Omega$ . Calculate Q.

$$X_L = 2\pi fX_L = 6.28(2 \times 10^5)(350 \times 10^{-6}) = 440 \Omega$$

$$Z_T = X_LQ \tag{18-8}$$

$$Q = \frac{Z_T}{X_L} = \frac{19\,800}{440} = 45 \quad \text{Ans.}$$

### Supplementary Problems

- 18.16** Find the resonant frequency of a series circuit if the inductance is 300  $\mu$ H and the capacitance is 0.005  $\mu$ F. *Ans.*  $f_r = 130$  kHz
- 18.17** Find the resonant frequency of a transmitting antenna that has a capacitance of 300 pF, a resistance of 40  $\Omega$ , and an inductance of 300  $\mu$ H. *Ans.*  $f_r = 530$  kHz
- 18.18** Find the resonant frequency of a series resonant section of a bandpass filter when  $L = 350 \mu$ H and  $C = 20$  pF. *Ans.*  $f_r = 1500$  kHz

- 18.19 What is the resonant frequency of a series circuit that consists of an inductance of  $500\ \mu\text{H}$  and a capacitance of  $400\ \text{pF}$ ? *Ans.*  $f_r = 356\ \text{kHz}$
- 18.20 How much capacitance is needed to obtain resonance at  $1500\ \text{kHz}$  with an inductance of  $45\ \mu\text{H}$ ? *Ans.*  $C = 251\ \text{pF}$
- 18.21 Find the value of inductance that will produce resonance to  $50\ \text{Hz}$  if it is placed in series with a  $20\text{-}\mu\text{F}$  capacitor. *Ans.*  $L = 0.508$
- 18.22 What is the capacitance of an antenna circuit whose inductance is  $50\ \mu\text{H}$  if it is resonant to  $1200\ \text{kHz}$ ? *Ans.*  $C = 353\ \text{pF}$
- 18.23 What is the inductance of a series resonant circuit with a  $300\text{-pF}$  capacitor at a frequency of  $1000\ \text{kHz}$ ? *Ans.*  $L = 84.7\ \mu\text{H}$
- 18.24 A voltage of  $100\ \text{V ac}$  at a frequency of  $10\ \text{kHz}$  is impressed across a series circuit that consists of a  $220\text{-pF}$  capacitor and an  $800\text{-mH}$  coil with an internal resistance of  $125\ \Omega$ . Find (a) the current in the circuit, (b) the voltage drops across the capacitor and the coil, (c) the power dissipated by the circuit, and (d) the  $Q$  of the coil.  
*Ans.* (a)  $I = 4.52\ \text{mA}$  ( $Z = 22\ 100\ \Omega$ ); (b)  $V_C = 327\ \text{V}$ ;  $V_L = 227\ \text{V}$ ;  
 (c)  $P = 2.55\ \text{mW}$ ; (d)  $Q = 402$
- 18.25 Find (a) the resonant frequency of the circuit in Prob. 18.24. As a series resonant circuit, find (b) the current in the circuit, (c) the voltage drops across the capacitor and the coil, (d) the power dissipated by the resonant circuit, (e) the  $Q$  of the coil, (f) the total bandwidth and edge frequencies, and (g) the power dissipated by the circuit operating at the edge frequency.  
*Ans.* (a)  $f_r = 12.0\ \text{kHz}$ ; (b)  $I = 0.8\ \text{A}$ ; (c)  $V_C = 48\ 230\ \text{V}$ ;  $V_L = 48\ 230\ \text{V}$ ; (d)  $P = 80\ \text{W}$ ;  
 (e)  $Q = 482$ ; (f)  $\Delta f = 25\ \text{Hz}$ ;  $f_1 = 11\ 988\ \text{Hz}$ ;  $f_2 = 12\ 012\ \text{Hz}$ . Rounding off has distorted these answers. If  $f_r$  were rounded to unit hertz,  $f_r = 11\ 985\ \text{Hz}$  (five significant figures). Then  $f_1 = 11\ 973\ \text{Hz}$  and  $f_2 = 11\ 997\ \text{Hz}$ . (g)  $P = 40\ \text{W}$
- 18.26 What type and value of "pure reactance" must be added to the circuit in Prob. 18.24 to make it resonant at  $10\ \text{kHz}$ ? *Ans.*  $L = 355\ \text{mH}$  added in series
- 18.27 A series circuit has a resistance of  $30\ \Omega$ , an inductance of  $0.382\ \text{H}$ , and a capacitance of  $0.2\ \mu\text{F}$ . Find (a) the impedance of the circuit to a frequency of  $500\ \text{Hz}$ , (b) the  $Q$  of the circuit, (c) the capacitance that must be added in parallel with the  $0.2\text{-}\mu\text{F}$  capacitor to produce resonance at this frequency, (d) the impedance of the circuit at resonance, (e) the  $Q$  of the resonant circuit, and (f) the bandwidth.  
*Ans.* (a)  $Z = 391\ \Omega$ ; (b)  $Q = 13$ ; (c)  $C = 0.065\ \mu\text{F}$  (Total  $C = 0.265\ \mu\text{F}$  at resonance);  
 (d)  $Z = 30\ \Omega$ ; (e)  $Q = 40$ ; (f)  $\Delta f = 12.5\ \text{Hz}$
- 18.28 A tuning capacitor is continuously variable between  $20$  and  $350\ \text{pF}$ . Find (a) the inductance that must be connected in series with it to produce a lowest resonant frequency of  $550\ \text{kHz}$ , and then (b) the highest resonant frequency. *Ans.* (a)  $L = 0.239\ \text{mH}$ ; (b)  $f_r = 2300\ \text{kHz}$
- 18.29 A  $0.1\text{-H}$  inductance, a  $1\text{-}\mu\text{F}$  capacitor, and a  $5\text{-}\Omega$  resistor are connected in series across a supply voltage of  $50\ \text{V}$  at a frequency of  $503\ \text{Hz}$ . (a) Is the circuit resonant? (b) Find the impedance of the circuit, and (c) find the amount of voltage across each component.  
*Ans.* (a) Yes ( $X_C = X_L = 316\ \Omega$ ); (b)  $Z = 5\ \Omega$ ; (c)  $V_R = 50\ \text{V}$ ;  $V_L = 3160\ \text{V}$ ;  $V_C = 3160\ \text{V}$
- 18.30 In a series  $RLC$  circuit,  $R = 10\ \Omega$ ,  $L = 20\ \text{mH}$ , and  $C = 1.26\ \mu\text{F}$ . Fill in the indicated quantities in the accompanying table, and plot the impedance as a function of frequency.

$f$	$X_L$	$X_C$	$Z$	Nature*	$Q$
800 Hz	?	?	?	?	?
900 Hz	?	?	?	?	?
1 kHz	?	?	?	?	?
1.1 kHz	?	?	?	?	?
1.2 kHz	?	?	?	?	?

\*Inductive, capacitive, or resistive (resonant)

Ans.

$f, \text{Hz}$	$X_L, \Omega$	$X_C, \Omega$	$Z, \Omega$	Nature	$Q$
800	101	158	57.9	Capacitive	5.7
900	113	140	28.8	Capacitive	2.7
1000	126	126	10	Resonant, resistive	12.6
1100	138	115	25.1	Inductive	2.4
1200	151	105	47.1	Inductive	4.6

See Fig. 18-17 for plot of impedance as a function of frequency.

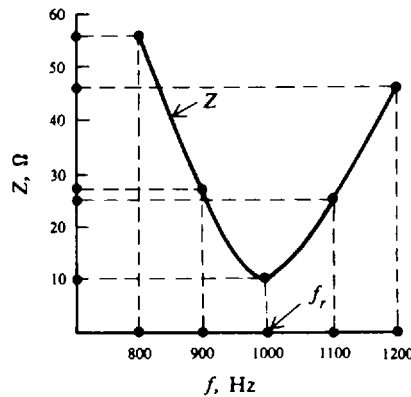


Fig. 18-17

- 18.31 A series RLC circuit with  $R = 250 \Omega$  and  $L = 0.6 \text{ H}$  has a lagging phase angle of  $30^\circ$  at a frequency of 60 Hz. Find the frequency at which this circuit will be resonant. *Ans.*  $f_r = 36.1 \text{ Hz}$
- 18.32 A series RLC circuit with  $R = 10 \Omega$  and  $C = 10 \mu\text{F}$  has a leading phase angle at  $45^\circ$  at a frequency of 500 Hz. Find the frequency at which this circuit will be resonant. *Ans.*  $f_r = 604 \text{ Hz}$
- 18.33 A series resonant circuit produces 240 mV across the coil with a 2-mV input. (a) What is the  $Q$  of the coil? (b) Find  $R$  if the coil is 5 mH and  $f_r$  is 300 kHz. (c) How much  $C$  is needed for this  $f_r$ ? (d) What are the bandwidth and edge frequencies?  
*Ans.* (a)  $Q = 120$ ; (b)  $R = 78.5 \Omega$ ; (c)  $C = 56.4 \text{ pF}$ ; (d)  $\Delta f = 2.5 \text{ kHz}$ ;  $f_1 = 298.75 \text{ kHz}$ ;  $f_2 = 301.25 \text{ kHz}$
- 18.34 For  $f_r = 450 \text{ kHz}$  and  $Q = 50$ , determine the bandwidth  $\Delta f$  and the edge frequencies  $f_1$  and  $f_2$ .  
*Ans.*  $\Delta f = 9 \text{ kHz}$ ;  $f_1 = 445.5 \text{ kHz}$ ;  $f_2 = 454.5 \text{ kHz}$



- 18.35 Find the lowest and highest values of  $C$  needed with  $0.1\text{-}\mu\text{H}$  coil to tune through the commercial FM broadcast band of 88 to 108 MHz. *Ans.*  $C_{\min} = 21.7\text{ pF}$ ;  $C_{\max} = 32.7\text{ pF}$
- 18.36 Find the resonant frequency of a filter made of a  $150\text{-}\mu\text{H}$  coil and  $40\text{-pF}$  capacitor in parallel. *Ans.*  $f_r = 2053\text{ kHz}$
- 18.37 A  $0.001\text{-}\mu\text{F}$  capacitor and a coil are connected in parallel to form the primary of an IF transformer. Find the inductance of the coil so that the circuit is resonant to a frequency of  $460\text{ kHz}$ . *Ans.*  $L = 120\text{ }\mu\text{H}$
- 18.38 A  $16\text{-}\mu\text{H}$  coil and a  $50\text{-pF}$  capacitor are connected in parallel (Fig. 18-18). If the effective resistance of the coil is  $25\text{ }\Omega$ , find the resonant frequency, the  $Q$  of the coil at resonance, the bandwidth, and the edge frequencies. *Ans.*  $f_r = 5620\text{ kHz}$ ;  $Q = 22.6$ ;  $\Delta f = 249\text{ kHz}$ ;  $f_1 = 5495.5\text{ kHz}$ ;  $f_2 = 5744.5\text{ kHz}$

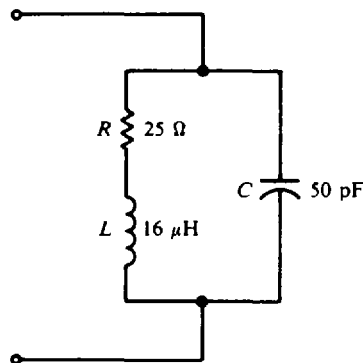


Fig. 18-18

- 18.39 An inductor is connected in parallel with a  $200\text{-pF}$  capacitor so that the circuit is resonant to  $113\text{ kHz}$ . A circuit magnification meter indicates that the  $Q$  of the inductor is  $800$ . Find (a) the value of the inductance, (b) the effective resistance of the inductor, and (c) the impedance of the circuit at resonance. *Ans.* (a)  $L = 9.91\text{ mH}$ ; (b)  $R = 8.79\text{ }\Omega$ ; (c)  $Z_T = 5.64\text{ M}\Omega$
- 18.40 An inductor with a measured  $Q$  of  $100$  resonates with a capacitor at  $7500\text{ kHz}$  with an impedance of  $65.9\text{ k}\Omega$ . Find the value of the inductance and the capacitance of the test capacitor. *Ans.*  $L = 14\text{ }\mu\text{H}$ ;  $C = 32.2\text{ pF}$
- 18.41 An inductor of  $0.1\text{ mH}$  with a  $Q$  of  $90$  is connected in parallel with a  $253\text{-pF}$  capacitor. Find (a) the resonant frequency and bandwidth, (b) the impedance of the circuit at resonance, and (c) the effective resistance of the inductor. *Ans.* (a)  $f_r = 1000\text{ kHz}$ ;  $\Delta f = 11.1\text{ kHz}$ ; (b)  $Z_T = 56.5\text{ k}\Omega$ ; (c)  $R = 7\text{ }\Omega$
- 18.42 Find the resonant frequency of the parallel circuit (Fig. 18-19). (Note that this is a very low  $Q$  circuit.) *Ans.*  $f_r = 159\text{ Hz}$  [use Eq. (18-6)]

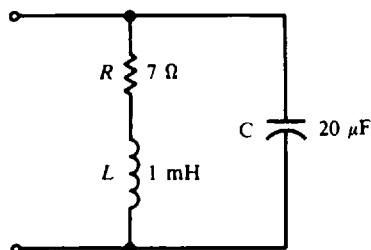


Fig. 18-19

18.43 Fill in the indicated quantities for the low-Q circuit (Fig. 18-19) for the various given frequencies. Round off  $Z_T$  to three significant figures. (See Prob. 18.12.) What is the Q of the circuit at resonance?

	$f, \text{ Hz}$	$Z_T, \Omega$	Nature
(a)	127	?	?
(b)	159	?	?
(c)	191	?	?

Ans.

	$f, \text{ Hz}$	$Z_T, \Omega$	Nature
(a)	127	7.09	20% below $f_r$ , essentially resistive
(b)	159	7.14	At $f_r$ , purely resistive
(c)	191	7.21	20% above $f_r$ , essentially resistive

$Q = 7.14$

18.44 Find the resonant frequency of the parallel LC circuit (Fig. 18-20). (Note that this is a high-Q circuit.)  
 Ans.  $f_r = 500 \text{ kHz}$

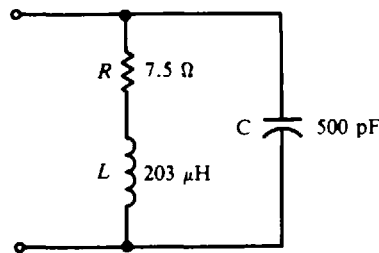


Fig. 18-20

18.45 Fill in the indicated quantities for the high-Q circuit (Fig. 18-20) for the given frequencies. Round off  $Z_T$  to three significant figures. (See Probs. 18.12, 18.13, and 18.14.)

	$f, \text{ kHz}$	$Z_T, \Omega$	Nature	Q
(a)	400	?	?	?
(b)	500	?	?	?
(c)	600	?	?	?

Ans.

	$f, \text{ kHz}$	$Z_T, \Omega$	Nature	Q
(a)	400	1420	20% below $f_r$ , highly inductive	38.0
(b)	500	54.1 k	At $f_r$ , high resistance	84.9
(c)	600	1730	20% above $f_r$ , highly capacitive	31.3

18.46 In a parallel resonant circuit with  $X_L = 500 \Omega$  and  $Q = 50$ , calculate  $Z_T$ . Ans.  $Z_T = 25 \text{ k}\Omega$

## Waveforms and Time Constants

### RL SERIES CIRCUIT WAVEFORMS

When a switch  $S$  is closed in a circuit having only resistance  $R$  (Fig. 19-1a), the readings on the ammeter  $A$  and the voltmeter  $V$  both rise quickly to a value and remain steady at that value (Fig. 19-1b and c). If the resistance  $R$  and the current  $I$  are known, the voltage  $V$  can be found by Ohm's law,

$$V = IR \quad (19-1)$$

When switch  $S$  is opened, the current and voltage drop quickly to zero.

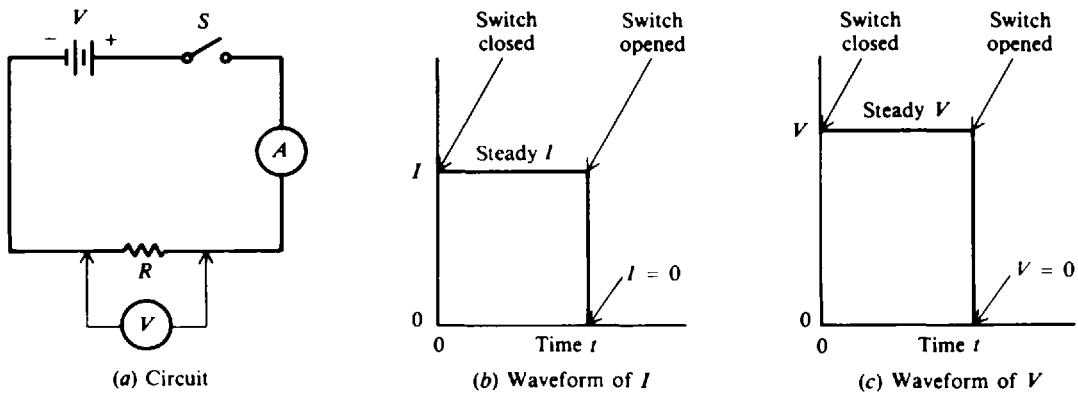


Fig. 19-1 Response of circuit with  $R$  only

When a coil of wire is added in series with a resistor, we have a  $RL$  series circuit (Fig. 19-2a), where  $V$  is the dc voltage,  $i$  is the instantaneous current,  $v_R$  is the instantaneous voltage across the resistor, and  $v_L$  is the instantaneous voltage across the coil. When the switch  $S$  is closed, the current begins to rise rapidly from zero until it reaches a steady value  $I$  determined by the resistance  $R$  of the circuit and the dc voltage  $V$  of the source (Fig. 19-2b). The shape that the current curve takes is exponential. When the switch is opened, the voltage source is removed and the current decays to zero at an exponential rate (Fig. 19-2b). With regard to voltage waveforms across  $R$  and  $L$ , when the switch is closed, the full dc voltage  $V$  appears across the coil and  $v_L$  decays to zero at an exponential rate; and  $v_R$  begins at zero and rises exponentially to a steady value of  $V$  (Fig. 19-2c). When the switch is opened, the net series voltage across  $R$  and  $L$ ,  $v_R + v_L$ , must equal zero. Because  $v_R$  cannot change quickly,  $v_L$  drops to  $-V$  and decays to  $0$  V (Fig. 19-2c).


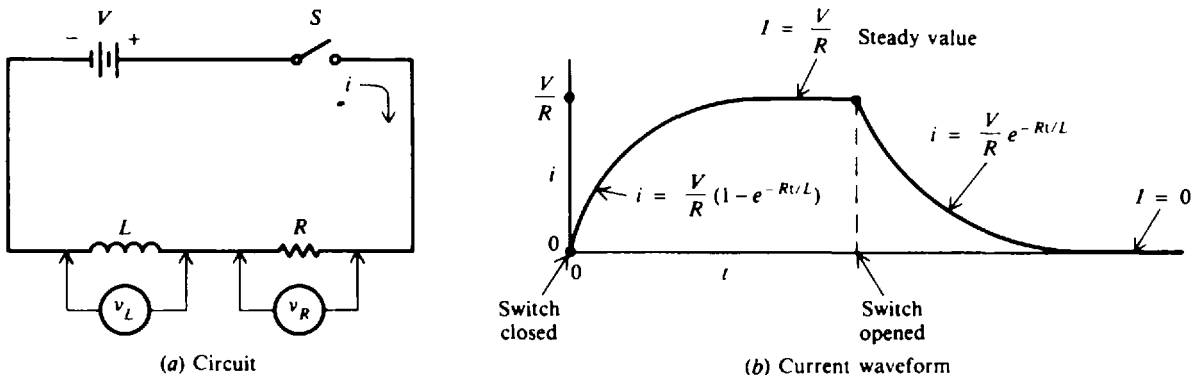


Fig. 19-2 Response of circuit with  $R$  and  $L$  in series

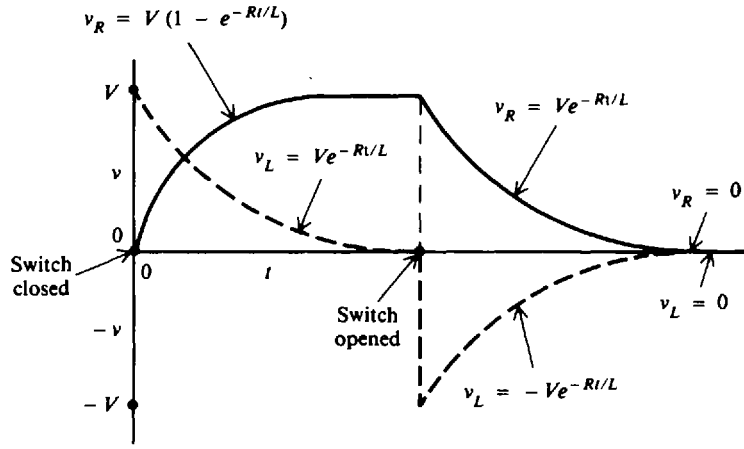

(c) Voltage waveforms of  $v_R$  and  $v_L$  ( $V = v_R + v_L$ )

Fig. 19-2(cont.)

The term *exponential* is used to describe the current and voltage waveforms because the formulas for calculating  $i$ ,  $v_R$ , and  $v_L$  when time  $t$  is given contain an exponent of  $e$  (constant equal to 2.718). The specific formulas to describe the *RL* waveforms follow:

**RL Series Charging Formulas When Switch Is Closed**

**Current** (Fig. 19-2b) 
$$i = \frac{V}{R}(1 - e^{-Rt/L}) \tag{19-2}$$

$$I = \frac{V}{R} \quad \text{when } t \text{ is large} \tag{19-3}$$

**Voltage** (Fig. 19-2c) 
$$V = v_R + v_L \tag{19-4}$$

$$v_R = V(1 - e^{-Rt/L}) \tag{19-5}$$

$$v_L = Ve^{-Rt/L} \tag{19-6}$$

**RL Series Discharging Formulas When Switch Is Opened**

**Current** (Fig. 19-2b) 
$$i = \frac{V}{R}e^{-Rt/L} \tag{19-7}$$

$$I = 0 \quad \text{when } t \text{ is large} \tag{19-8}$$

**Voltage** (Fig. 19-2c) 
$$0 = v_R + v_L \tag{19-9}$$

$$v_R = Ve^{-Rt/L} \tag{19-10}$$

$$v_L = -Ve^{-Rt/L} \tag{19-11}$$

- where
- $i$  = instantaneous current, A
  - $V$  = applied dc voltage, V
  - $R$  = resistance of the circuit,  $\Omega$
  - $L$  = inductance of the circuit, H
  - $t$  = time, s
  - $e$  = natural log base, constant equal to 2.718
  - $I$  = final or steady-state value of current, A
  - $v_R$  = instantaneous voltage across the resistor, V
  - $v_L$  = instantaneous voltage across the coil, V

**Example 19.1** Find the value of  $e^{-Rt/L}$  for the following values of  $R$ ,  $L$ , and  $t$ .

	$R, \Omega$	$L, \text{H}$	$t, \text{s}$
(a)	15	15	0
(b)	15	15	1
(c)	30	15	1
(d)	15	30	1
(e)	15	15	3
(f)	30	20	1

The simplest way to evaluate exponentials is by use of an electronic calculator. First calculate  $-Rt/L$  and then  $e^{-Rt/L}$ . Round off numerical answers to three significant digits.

$$(a) \quad -\frac{Rt}{L} = \frac{-15(0)}{15} = 0$$

$$e^{-Rt/L} = e^0 = 1 \quad \text{Ans.}$$

Any quantity raised to a zero exponent equals 1.

$$(b) \quad -\frac{Rt}{L} = \frac{-15(1)}{15} = -1$$

$$e^{-1} = 0.368 \quad \text{Ans.}$$

$$(c) \quad -\frac{Rt}{L} = \frac{-30(1)}{15} = -2$$

$$e^{-2} = 0.135 \quad \text{Ans.}$$

$$(d) \quad -\frac{Rt}{L} = \frac{-15(1)}{30} = -0.5$$

$$e^{-0.5} = 0.607 \quad \text{Ans.}$$

$$(e) \quad -\frac{Rt}{L} = \frac{-15(3)}{15} = -3$$

$$e^{-3} = 0.050 \quad \text{Ans.}$$

$$(f) \quad -\frac{Rt}{L} = \frac{-30(1)}{20} = -1.5$$

$$e^{-1.5} = 0.223 \quad \text{Ans.}$$

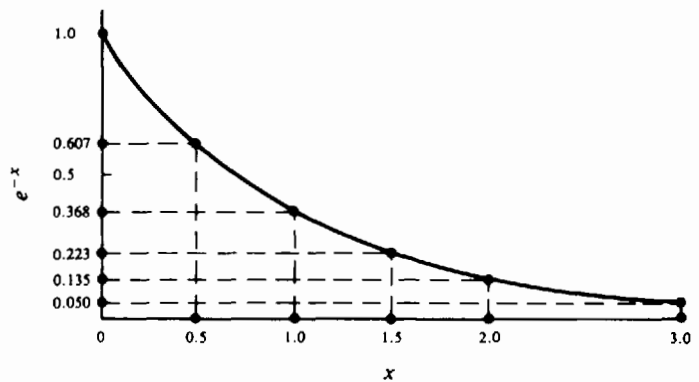


Fig. 19-3 Plot of exponential curve  $e^{-x}$

If we let  $x = (R/L)t$  and plot these values, we obtain the curve  $e^{-x}$  (Fig. 19-3).

**Example 19.2** A 20-H coil and a 20- $\Omega$  resistor are connected in series across a 120-V dc source (Fig. 19-4a). (a) What is the current 1, 2, 3, 4, and 5 s after the circuit is closed? (b) What is the initial current at the instant the circuit is closed? (c) What is the voltage across the coil and across the resistor at 1 s after the circuit is closed? (d) Plot the curve of current versus time from  $t = 0$  to  $t = 5$  s.

(a) **Step 1.** Write the formula for series  $RL$  current when the switch is closed.

$$i = \frac{V}{R} (1 - e^{-Rt/L}) \quad (19-2)$$

**Step 2.** Find the value of  $e^{-Rt/L}$  for  $t = 1, 2, 3, 4,$  and  $5$  s.

For  $t = 1$  s:

$$-\frac{Rt}{L} = \frac{-20(1)}{20} = -1$$

$$e^{-1} = 0.368 \quad \text{Ans.}$$

For  $t = 2$  s:  $-\frac{Rt}{L} = \frac{-20(2)}{20} = -2$

$e^{-2} = 0.135$       *Ans.*

For  $t = 3$  s:  $-\frac{Rt}{L} = \frac{-20(3)}{20} = -3$


$e^{-3} = 0.050$       *Ans.*

For  $t = 4$  s:  $-\frac{Rt}{L} = \frac{-20(4)}{20} = -4$

$e^{-4} = 0.018$       *Ans.*

For  $t = 5$  s:  $-\frac{Rt}{L} = \frac{-20(5)}{20} = -5$

$e^{-5} = 0.007$       *Ans.*

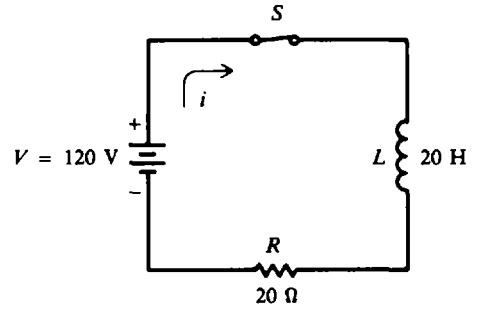

(a) Series  $RL$  circuit with switch closed

**Fig. 19-4a** Series  $RL$  circuit with switch closed

**Step 3.** Find  $i$  by substituting values for  $e^{-Rt/L}$ ,  $V$ , and  $R$ .

$$i = \frac{V}{R}(1 - e^{-Rt/L}) \tag{19-2}$$

For  $t = 1$  s:  $i = \frac{120}{20}(1 - 0.368) = 6(0.632) = 3.79$  A      *Ans.*

For  $t = 2$  s:  $i = \frac{120}{20}(1 - 0.135) = 6(0.865) = 5.19$  A      *Ans.*

For  $t = 3$  s:  $i = \frac{120}{20}(1 - 0.050) = 6(0.950) = 5.70$  A      *Ans.*

For  $t = 4$  s:  $i = \frac{120}{20}(1 - 0.018) = 6(0.982) = 5.89$  A      *Ans.*

For  $t = 5$  s:  $i = \frac{120}{20}(1 - 0.007) = 6(0.993) = 5.96$  A      *Ans.*

(b) The initial current is that current when  $t = 0$  s. So

$$-\frac{Rt}{L} = \frac{-20(0)}{20} = 0 \quad \text{and} \quad e^0 = 1$$

Then  $i = \frac{120}{20}(1 - 1) = 6(0) = 0$  A      *Ans.*

(c) Write Eqs. (19-5) and (19-6) and substitute proper values when  $t = 1$  s.

$$V_R = V(1 - e^{-Rt/L}) = 120(1 - 0.368) = 120(0.632) = 75.8 \quad \text{Ans.}$$

$$v_L = Ve^{-Rt/L} = 120(0.368) = 44.2 \text{ V} \quad \text{Ans.}$$

As a check, substitute values for  $v_R$  and  $v_L$  into Eq. (19-4).

$$\begin{aligned} V &= v_R + v_L \\ 120 &= 75.8 + 44.2 \\ 120 \text{ V} &= 120 \text{ V} \end{aligned}$$

(d) Plot of current curve is shown in Fig. 19-4b. Note that at  $t = 5$  s, the current has almost reached its steady-state value of 6 A.

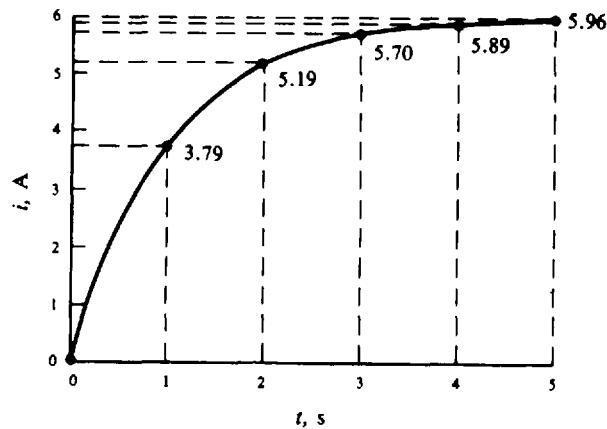


Fig. 19-4b

**Example 19.3** In Example 19.2, the switch is opened after having been closed for 7 s. What is the value of current 2 s after the switch is opened?

For practical purposes, at time  $t = 7$  s, the value of current has reached 6 A, its steady-state value. See Fig. 19-4b. So write Eq. (19-7) and substitute values for  $t = 2$  s.

$$i = \frac{V}{R} e^{-Rt/L} \quad \text{or} \quad i = I e^{-Rt/L}$$

$$-\frac{Rt}{L} = -\frac{20(2)}{20} = -2$$

$$e^{-2} = 0.135$$

$$i = \frac{120}{20} (0.135) = 6(0.135) = 0.81 \text{ A} \quad \text{Ans.}$$

### RL TIME CONSTANTS

Any value of  $t$  can be inserted in the formula for current [Eq. (19-2)], and a corresponding value of the current  $i$  can be found. Theoretically, the current never reaches the steady-state value of  $V/R$  on rise, zero, or decay. However, from a practical standpoint, the ammeter does show steady current values a finite number of seconds after the circuit is closed or opened.

A convenient unit of time measurement is the time constant  $T$ , which is equal to the ratio  $L/R$  in a  $RL$  circuit.

$$t = T = \frac{L}{R} \quad (19-12)$$

We say that

$$\text{One time constant} = 1T = \frac{L}{R}$$

$$\text{Two time constants} = 2T = \frac{2L}{R}$$

$$\text{Three time constants} = 3T = \frac{3L}{R}$$

and so on.

By substituting one time constant,  $t = 1T = L/R$ , in Eq. (19-2),

$$i = \frac{V}{R}(1 - e^{-(R/L)t}) \tag{19-2}$$

we obtain 
$$i = \frac{V}{R}(1 - e^{-(R/L)(L/R)}) \quad \text{or} \quad i = \frac{V}{R}(1 - e^{-1})$$

Since 
$$e^{-1} = 0.368$$

then 
$$i = \frac{V}{R}(1 - 0.368) = (0.632)\frac{V}{R}$$

Therefore, one time constant is the time in seconds required for the current in a *RL* circuit to rise to 0.632 times its steady-state value  $V/R$ , or at  $t = L/R$  the current is 63.2 percent of its final value.

Table 19-1 shows the value of the quantities  $e^{-Rt/L}$  and  $1 - e^{-Rt/L}$  for the number of time constants ranging from 0 to 6.

**Table 19-1 Time Constant Factors**

Number of time constants	$e^{-Rt/L}$	$1 - e^{-Rt/L}$
0	1.000	0.000
0.5	0.607	0.393
1.0	0.368	0.632
1.5	0.223	0.777
2.0	0.135	0.865
2.5	0.082	0.918
3.0	0.050	0.950
3.5	0.030	0.970
4.0	0.018	0.982
4.5	0.011	0.989
5.0	0.007	0.993
5.5	0.004	0.996
6.0	0.002	0.998

The table shows that the current reaches more than 99 percent (0.993) of its steady-state value in five time constants. Since the rise during the sixth time constant is only 0.005 (0.998 - 0.993), the current is considered, from a practical standpoint, to have reached its steady-state value at the end of five time constants.

**Example 19.4** A circuit has total resistance of 10 Ω and an inductance of 50 H. In how many seconds will the current reach its steady-state value?

Write the formula for a time constant [Eq. (19-12)] and substitute  $L = 50$  H and  $R = 10$  Ω.

$$T = L/R = 50/10 = 5 \text{ s, one time constant}$$

The total time to reach the steady-state value is equal to five time constants.

$$\text{Total time} = 5T = 5(5) = 25 \text{ s} \quad \text{Ans.}$$



**Example 19.5** Draw a plot of a rising current versus time constants in a  $RL$  series circuit.

Refer to Table 19-1 for values of  $1 - e^{-Ri/L}$  or  $1 - e^{-t/T}$  and the corresponding time constants. The plot is shown in Fig. 19-5. Compare the similarity of this plot with that in Fig. 19-4b of Example 19.2d, where  $V/R = 6$  A and one time constant equals  $L/R = 20/20 = 1$  s. In that example, therefore, the horizontal scale of time is the same as that of time constants for this example. To illustrate, at  $t = 4$  s,  $i = 5.89$  A (Fig. 19-4b); in this example,  $t = 4 = T$ , so  $i = 0.982(V/R) = 0.982(6) = 5.89$  A.


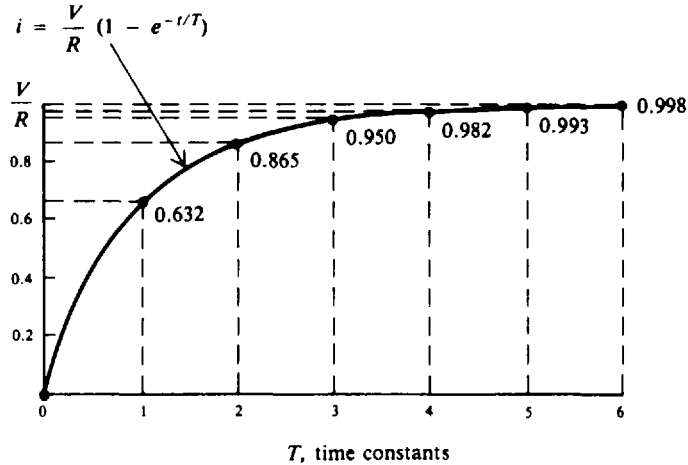


Fig. 19-5

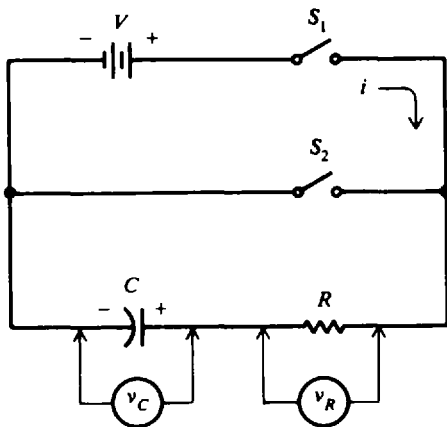
**RC SERIES CIRCUIT WAVEFORMS**

When a capacitor is added in series with a resistor, we have the  $RC$  series circuit (Fig. 19-6a), where  $V$  is the dc voltage,  $i$  is the instantaneous current,  $v_R$  is the instantaneous voltage across the resistor, and  $v_C$  is the instantaneous voltage across the capacitor.

When switch  $S_1$  is closed and switch  $S_2$  is opened, the current rises instantly to its maximum value of  $V/R$  and then decays exponentially until it reaches zero, its steady-state or final value (Fig. 19-6b). Also, the full voltage  $V$  of the battery is across the resistor,  $V = v_R$ . As the current decreases, the voltage across the resistance  $v_R$  decreases and the voltage across the capacitance  $v_C$  rises so that the sum of the voltages  $v_R$  and  $v_C$  is equal to  $V$ ;  $v_R$  reduces to zero and the capacitor charges to  $v_C = V$  (Fig. 19-6c).




(a) Circuit

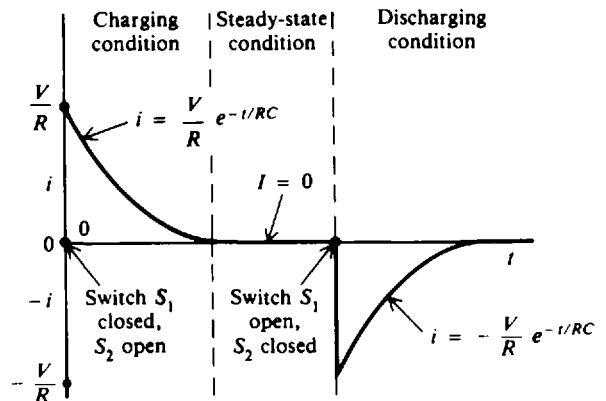

(b) Current waveform

Fig. 19-6 Response of circuit with  $R$  and  $C$  in series

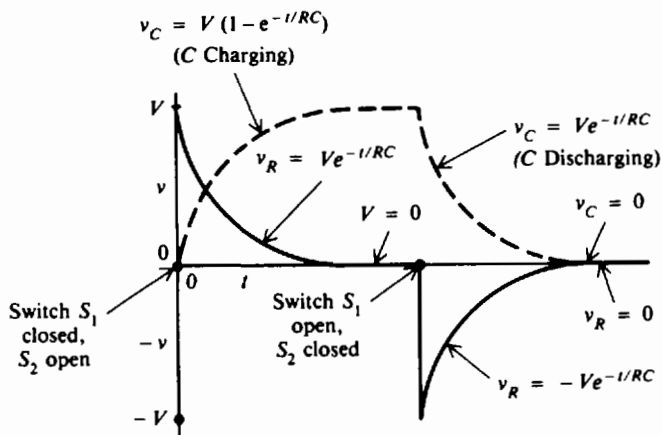

(c) Voltage waveforms of  $v_R$  and  $v_C$  ( $V = v_R + v_C$ )

Fig. 19-6 (cont.)

After steady-state conditions are reached ( $i = 0$ ,  $v_R = 0$ ,  $v_C = V$ ), switch  $S_1$  is opened and switch  $S_2$  is closed. Current now flows out of the capacitor in the direction opposite to the direction it flowed while the capacitor was being charged. The current drops instantly to  $-V/R$  and gradually decays to zero (Fig. 19-6b). Also, the voltage  $V$  appears across the resistance with opposite polarity, that of  $-V$  (Fig. 19-6c). Then the two voltages  $v_R$  and  $v_C$  decay exponentially to zero.

The specific formulas to describe the  $RL$  waveforms follow:

**RC Series Charging Formulas When Switch  $S_1$  Is Closed and Switch  $S_2$  Is Opened**

**Current** (Fig. 19-6b)

$$i = \frac{V}{R} e^{-t/RC} \tag{19-13}$$

$$I = 0 \quad \text{when } t \text{ is large} \tag{19-14}$$

**Voltage** (Fig. 19-6c)

$$V = v_R + v_C \tag{19-15}$$

$$v_R = Ve^{-t/RC} \tag{19-16}$$

$$v_C = V(1 - e^{-t/RC}) \tag{19-17}$$

**RC Series Discharging Formulas When Switch  $S_1$  Is Opened and Switch  $S_2$  Is Closed**

**Current** (Fig. 19-6b)

$$i = -\frac{V}{R} e^{-t/RC} \tag{19-18}$$

$$I = 0 \quad \text{when } t \text{ is large} \tag{19-19}$$

**Voltage** (Fig. 19-6c)

$$0 = v_R + v_C \tag{19-20}$$

$$v_R = -Ve^{-t/RC} \tag{19-21}$$

$$v_C = Ve^{-t/RC} \tag{19-22}$$

- where  $i$  = instantaneous current, A  
 $V$  = applied dc voltage, V  
 $R$  = resistance of the circuit,  $\Omega$   
 $C$  = capacitance of the circuit, F  
 $t$  = time, s  
 $e$  = natural log base, constant equal to 2.718  
 $I$  = final or steady-state value of current, A  
 $v_R$  = instantaneous voltage across the resistor, V  
 $v_C$  = instantaneous voltage across the capacitor, V

**Example 19.6** Find the value of  $e^{-t/RC}$  for the following values of  $R$ ,  $C$ , and  $t$ .

	$R$	$C$	$t$
(a)	2 $\Omega$	0.5 F	1 s
(b)	1 M $\Omega$	10 $\mu$ F	5 s
(c)	1 k $\Omega$	500 $\mu$ F	2 s
(d)	200 $\Omega$	1000 $\mu$ F	0.3 s

The simplest way to find values of exponential expressions is to use an electronic calculator.

$$(a) \quad -\frac{t}{RC} = -\frac{1}{2(0.5)} = -1$$

$$e^{-t/RC} = e^{-1} = 0.368 \quad \text{Ans.}$$

$$(b) \quad -\frac{t}{RC} = -\frac{5}{(1 \times 10^6)(10 \times 10^{-6})} = -\frac{5}{10} = -0.5$$

Remember to convert  $R$  into ohms and  $C$  into farads before you calculate.

$$e^{-0.5} = 0.607 \quad \text{Ans.}$$


$$(c) \quad -\frac{t}{RC} = -\frac{2}{(1 \times 10^3)(500 \times 10^{-6})} = -4$$

$$e^{-4} = 0.018 \quad \text{Ans.}$$

$$(d) \quad -\frac{t}{RC} = -\frac{0.3}{(2 \times 10^2)(10^3 \times 10^{-6})} = -\frac{0.3}{0.2} = -1.5$$

$$e^{-1.5} = 0.223 \quad \text{Ans.}$$

**Example 19.7** For a  $RC$  series circuit (Fig. 19-7), find (a) the current 1 s after the circuit is closed and (b) the voltage across the resistance and the capacitor at that instant of time.

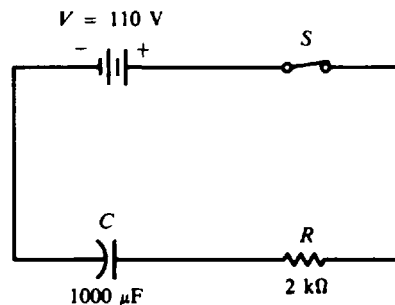

**Fig. 19-7** Series  $RC$  circuit with switch closed

(a) **Step 1.** Write the formula for series  $RC$  current when the switch is closed.

$$i = \frac{V}{R} e^{-t/RC} \tag{19-13}$$

**Step 2.** Find the value of  $e^{-t/RC}$  for  $t = 1$  s.

$$-\frac{t}{RC} = -\frac{1}{(2 \times 10^3)(10^3 \times 10^{-6})} = -\frac{1}{2} = -0.5 \quad e^{-0.5} = 0.607$$

**Step 3.** Find  $i$  by substituting values in Eq. (19-13).

$$i = \frac{110}{2000} (0.607) = 0.0334 \text{ A} = 33.4 \text{ mA} \quad \text{Ans.}$$

(b) Write the formulas for voltage when the switch is closed and then substitute the proper values.

$$\begin{aligned} v_R &= V e^{-t/RC} & (19-16) \\ &= 110(0.607) = 66.8 \text{ V} \quad \text{Ans.} \end{aligned}$$

$$\begin{aligned} v_C &= V(1 - e^{-t/RC}) & (19-17) \\ &= 110(1 - 0.607) = 110(0.393) = 43.2 \text{ V} \quad \text{Ans.} \end{aligned}$$

Check by using Eq. (19-15).

$$\begin{aligned} V &= v_R + v_C \\ 110 &= 66.8 + 43.2 \\ 110 \text{ V} &= 110 \text{ V} \end{aligned}$$

**Example 19.8** After the circuit (Fig. 19-7) has reached steady state when the capacitor has charged to 110 V, the switch is opened. Find now (a) the current 1 s after the circuit is opened and (b) the voltages across the resistance and the capacitor at that time.

(a) **Step 1.** Write the formula for series  $RC$  current when the switch is opened.

$$i = -\frac{V}{R} e^{-t/RC} \tag{19-18}$$

**Step 2.** Find  $e^{-t/RC}$ .

$$e^{-t/RC} = e^{-0.5} = 0.607$$

**Step 3.** Find  $i$  by substituting values in Eq. (19-18).

$$i = -\frac{110}{2000} (0.607) = -0.0334 \text{ A} = -33.4 \text{ mA} \quad \text{Ans.}$$

(b) Write the formulas for voltage when the switch is opened and then substitute proper values.

$$\begin{aligned} v_R &= -V e^{-t/RC} & (19-21) \\ &= -110(0.607) = -66.8 \text{ V} \quad \text{Ans.} \end{aligned}$$

$$\begin{aligned} v_C &= V e^{-t/RC} & (19-22) \\ &= 110(0.607) = 66.8 \text{ V} \quad \text{Ans.} \end{aligned}$$

Check:

$$\begin{aligned} 0 &= v_R + v_C \\ 0 &= -66.8 + 66.8 \\ 0 \text{ V} &= 0 \text{ V} \end{aligned}$$

### RC TIME CONSTANTS

The time constant  $T$  for a capacitive circuit is

$$T = RC \tag{19-23}$$

We say that

$$\begin{aligned}\text{One time constant} &= 1T = RC \\ \text{Two time constants} &= 2T = 2RC \\ \text{Three time constants} &= 3T = 3RC\end{aligned}$$

and so on.

The time constant of a capacitive circuit is usually very short because the capacitance of a circuit may be only a few microfarads or even picofarads.

Voltage and current values in capacitive circuits are assumed to reach their steady-state or final values after five time constants, just as in inductive circuits. Table 19-1 applies also to capacitive circuits if  $e^{-Rt/L}$  is replaced by  $e^{-t/RC}$ .

### CALCULATION FOR TIME $t$

The time required for a specific voltage decay can be calculated by transposing Eq. (19-21) or Eq. (19-22).

$$v = Ve^{-t/RC}$$

where  $V$  is the higher voltage at the start and  $v$  ( $v_R$  or  $v_C$ ) is the lower voltage at the finish.

$$e^{-t/RC} = \frac{v}{V}$$

Take the natural logarithm (ln) of each side.

$$\begin{aligned}-\frac{t}{RC} \ln e &= \ln \frac{v}{V} \\ \ln e &= 1\end{aligned}$$

So

$$\begin{aligned}-\frac{t}{RC} &= \ln \frac{v}{V} = \ln v - \ln V \\ \frac{t}{RC} &= -\ln v + \ln V = \ln \frac{V}{v} \\ t &= RC \ln \frac{V}{v}\end{aligned}\tag{19-24}$$

**Example 19.9** A dc circuit of source voltage  $V$  has a 10-M $\Omega$  resistance in series with a 1- $\mu$ F capacitor. What is the time constant of the circuit and how long will current flow in the circuit when the RC combination is short-circuited?

Write the formula for time constant in a capacitive circuit, Eq. (19-23).

$$T = RC = (10 \times 10^6)(1 \times 10^{-6}) = 10 \text{ s} \quad \text{Ans.}$$

Since the steady-state current is assumed to be zero after five time constants, the time that current will flow is

$$5T = 5(10) = 50 \text{ s} \quad \text{Ans.}$$

**Example 19.10** Find the resistance necessary in a RC series circuit if the circuit has a capacitance of 10  $\mu$ F and a time constant of 1 s is desired.

Rewrite Eq. (19-23) and solve for  $R$ .

$$R = \frac{T}{C} = \frac{1}{10 \times 10^{-6}} = 10^5 = 100 \text{ k}\Omega \quad \text{Ans.}$$

**Example 19.11** One time constant for a series RC circuit is also defined as the time in seconds required for the capacitor to charge to 63.2 percent of its final value. Show that this statement is true.

Write the capacitance voltage equation  $v_C$  when the capacitor is being charged.

$$v_C = V(1 - e^{-t/RC}) \tag{19-17}$$

One time constant  $T = RC$ . Substitute  $RC$  for  $t$ .

$$v_C = V(1 - e^{-RC/RC}) = V(1 - e^{-1}) = V(1 - 0.368) = 0.632 V$$

So  $v_C$  is 63.2 percent of  $V$  in one time constant.

**Example 19.12** If a RC circuit has a time constant of 1 s, how long will it take for  $v_R$  to drop from 100 to 50 V? Write the time equation for voltage decay, Eq. (19-24).

$$t = RC \ln \frac{V}{v} = 1 \left( \ln \frac{100}{50} \right) = \ln 2 = 0.693 \text{ s} \quad \text{Ans.}$$

### Solved Problems

**19.1** A series circuit contains a resistance of 20 Ω and an inductance of 10 H connected across a voltage source of 110 V. (a) What is the current 1 s after the circuit is closed? (b) What are  $v_R$  and  $v_C$  at this time?

Some time after the current reaches a steady value, the switch is opened. When the series circuit is open, the RL circuit opposes the decay of current toward the steady-state value of zero. (c) What is the current 2 s after the circuit is opened? (d) What are  $v_R$  and  $v_C$  at this time?

(a) **Step 1.** Write the formula for charging or rising current when the switch is closed.

$$i = \frac{V}{R} (1 - e^{-Rt/L}) \tag{19-2}$$

**Step 2.** Find the value of  $e^{-Rt/L}$  for  $t = 1$  s.

$$-\frac{Rt}{L} = -\frac{20(1)}{10} = -2 \quad e^{-2} = 0.135$$

**Step 3.** Substitute values for  $e^{-Rt/L}$ ,  $V$ , and  $R$  in Eq. (19-2).

$$i = \frac{110}{20} (1 - 0.135) = 5.5(0.865) = 4.76 \text{ A} \quad \text{Ans.}$$

(b) Write the formulas for  $v_R$  and  $v_L$  after the switch is closed and solve them when  $t = 1$  s.

$$\begin{aligned} v_R &= V(1 - e^{-Rt/L}) \\ &= 110(0.865) = 95.2 \text{ V} \quad \text{Ans.} \end{aligned} \tag{19-5}$$

Also  $v_R = iR = 4.76(20) = 95.2 \text{ V}$ .

$$\begin{aligned} v_L &= Ve^{-Rt/L} \\ &= 110(0.135) = 14.8 \text{ V} \quad \text{Ans.} \end{aligned}$$

Check:

$$\begin{aligned} V &= v_R + v_L \\ 110 &= 95.2 + 14.8 \\ 110 \text{ V} &= 110 \text{ V} \end{aligned} \tag{19-4}$$

(c) The steady-state value of current is

$$I = \frac{V}{R} = \frac{110}{20} = 5.5 \text{ A}$$

Write the formula for discharging or decaying current when the switch is opened and substitute values with  $t = 2 \text{ s}$ .

$$i = \frac{V}{R} e^{-Rt/L} \tag{19-7}$$

$$-\frac{Rt}{L} = -\frac{20(2)}{10} = -4$$

$$e^{-4} = 0.018$$

$$i = 5.5(0.018) = 0.10 \text{ A} \quad \text{Ans.}$$

(d) Write the formulas for  $v_R$  and  $v_L$  after the switch is opened and solve them when  $t = 2 \text{ s}$ .

$$v_R = V e^{-Rt/L} \tag{19-10}$$

$$= 110(0.018) = 1.98 \text{ V} \quad \text{Ans.}$$

$$v_L = -V e^{-Rt/L} \tag{19-11}$$

$$= -110(0.018) = -1.98 \text{ V} \quad \text{Ans.}$$

Check:

$$0 = v_R + v_L \tag{19-9}$$

$$0 = 1.98 - 1.98$$

$$0 \text{ V} = 0 \text{ V}$$

**19.2** A  $RL$  series circuit has the following values:  $V = 75 \text{ V}$  dc,  $R = 50 \Omega$ , and  $L = 15 \text{ H}$ . (a) Find the time constant. (b) How long after the circuit is energized will the current reach a steady value? (c) What is the steady-state value of current?

(a) Write the formula for the time constant, Eq. (19-12), and substitute given values.


$$T = \frac{L}{R} = \frac{15}{50} = 0.3 \text{ s} \quad \text{Ans.}$$

(b) A steady-state value of current is reached after five time constants.

$$5T = 5(0.3) = 1.5 \text{ s} \quad \text{Ans.}$$

(c)  $I = \frac{V}{R} = \frac{75}{50} = 1.5 \text{ A} \quad \text{Ans.}$

**19.3** In the circuit shown (Fig. 19-8), find (a) the total inductance and (b) the time constant. Assume that a current of  $10 \text{ A}$  is flowing when the switch  $S$  is opened. Find (c) the current  $2 \text{ s}$  later.

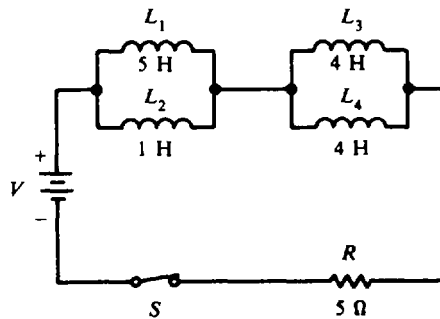

**Fig. 19-8** Circuit with branch inductances in series with  $R$

(a) Reduce the series-parallel combination of inductances to its equivalent.

Parallel: 
$$L_a = \frac{L_1 L_2}{L_1 + L_2} = \frac{5(1)}{5 + 1} = \frac{5}{6} = 0.83 \text{ H}$$

Parallel: 
$$L_b = \frac{L_3 L_4}{L_3 + L_4} = \frac{4(4)}{4 + 4} = \frac{16}{8} = 2.0 \text{ H}$$

Then series: 
$$L_T = L_a + L_b = 0.83 + 2.0 = 2.83 \text{ H} \quad \text{Ans.}$$

(b) The time constant of the circuit is the ratio of total inductance to the total resistance of the circuit.

$$T = \frac{L_T}{R} = \frac{2.83}{5} = 0.57 \text{ s} \quad \text{Ans.}$$

(c) Write the formula for decaying current. The  $V/R$  value is 10 A.


$$i = \frac{V}{R} e^{-Rt/L} \tag{19-7}$$

$$-\frac{Rt}{L_T} = -\frac{5(2)}{2.83} = -3.5$$

$$e^{-3.5} = 0.030$$

Then 
$$i = 10(0.030) = 0.30 \text{ A} \quad \text{Ans.}$$

**19.4** A  $RL$  circuit (Fig. 19-9) is used to generate a high voltage to light a neon bulb, which requires 90 V for ionization at which time it glows. When the circuit is open, the high resistance  $R_2$  produces a low time constant  $L/R$  so that the current drops toward zero much faster than the rise of current when the switch is closed. The result is a high value of self-induced voltage across a coil when the  $RL$  circuit is open. This voltage can be greater than the applied voltage. (a) Find the time constants of the circuit when the switch is opened and when the switch is closed. (b) When the switch is closed, find the voltage across the neon bulb. Is it sufficient to start ionization? (c) When the switch is open, what is the voltage across the neon bulb, and is it great enough to light it?

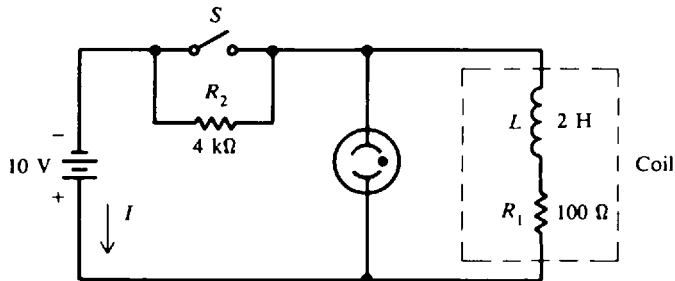

**Fig. 19-9**  $RL$  circuit produces a high voltage when switch is opened

(a) The time constant is the ratio of total inductance to the total resistance.

Switch open:

$$T = \frac{L}{R_1 + R_2} = \frac{2}{4000 + 100} = \frac{2}{4100} = 4.9 \times 10^{-4} = 0.49 \text{ ms} \quad \text{Ans.}$$

Switch closed ( $R_2$  short-circuited):

$$T = \frac{L}{R_1} = \frac{2}{100} = 2 \times 10^{-2} = 20 \text{ ms} \quad \text{Ans.}$$

When the switch is open, there is a much shorter time constant for current decay. The current decays practically to zero after five time constants, or 2.5 ms.



- (b) When the switch is closed, there is 10 V across the neon bulb, which is far less than the 90 V needed to ionize it to glow.
- (c) When the switch is closed,  $R_2$  is short-circuited so that the 100- $\Omega$   $R_1$  is the only resistance. The steady-state current  $I = V/R_1 = 10/100 = 0.10$  A. When the switch is opened, the rapid drop in current results in a magnetic field collapsing at a fast rate, inducing a high voltage across  $L$ . The energy stored in the magnetic field maintains  $I$  at 0.10 A for an instant before the current decays. With 0.10 A in the 4-k $\Omega$   $R_2$ , its potential difference is  $0.10(4000) = 400$  V. This 400-V pulse is sufficient to light the bulb.

**19.5** For a  $RC$  series circuit (Fig. 19-10), find (a) the time constant of the circuit; (b)  $v_C$  and  $v_R$  one time constant after the switch is closed and at 5 s, and (c)  $v_C$  and  $v_R$  one time constant after discharge starts, assuming the capacitor is fully charged to 10 V.

- (a) Write Eq. (19-23) for the time constant in a  $RC$  series circuit and substitute values for  $R$  and  $C$ .

$$T = RC = (100 \times 10^3)(20 \times 10^{-6}) = 2 \text{ s} \quad \text{Ans.}$$

- (b) Write the formulas for charging voltage, substitute values, and solve for  $v_C$  and  $v_R$ .

$$v_C = V(1 - e^{-t/RC}) \quad (19-17)$$

When  $t = T = 2$  s:

$$v_C = 10(1 - e^{-2/2}) = 10(1 - e^{-1}) = 10(1 - 0.368) = 10(0.632) = 6.32 \text{ V} \quad \text{Ans.}$$

$$V = v_R + v_C \quad (19-15)$$

$$v_R = V - v_C = 10 - 6.32 = 3.68 \text{ V} \quad \text{Ans.}$$

When  $t = 5$  s:

$$v_C = 10(1 - e^{-5/2}) = 10(1 - e^{-2.5}) = 10(1 - 0.082) = 10(0.918) = 9.18 \text{ V} \quad \text{Ans.}$$

$$v_R = V - v_C = 10 - 9.18 = 0.82 \text{ V} \quad \text{Ans.}$$

- (c) Write the formula for discharging voltage, substitute values, and solve for  $v_C$  and  $v_R$ .


$$v_C = Ve^{-t/RC} \quad (19-22)$$

When  $t = T = 2$  s:


$$v_C = Ve^{-2/2} = Ve^{-1} = 10(0.368) = 3.68 \text{ V} \quad \text{Ans.}$$

$$0 = v_R + v_C \quad (19-20)$$

$$v_R = -v_C = -3.68 \text{ V} \quad \text{Ans.}$$

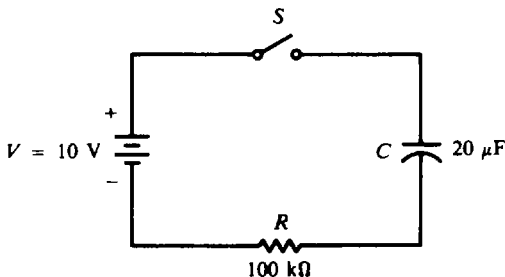

**Fig. 19-10**  $RC$  circuit

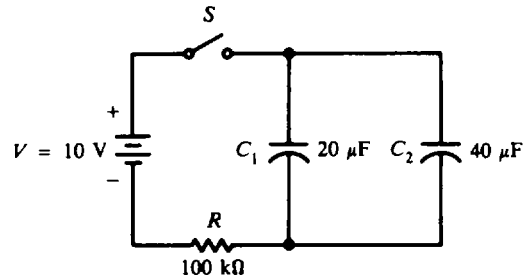

**Fig. 19-11** Circuit with  $C$  branch in series with  $R$

**19.6** For the circuit shown (Fig. 19-11), a 40- $\mu\text{F}$  capacitor is added across the 20- $\mu\text{F}$  capacitor in the circuit of Fig. 19-10. Find the time constant of this circuit and the voltage across this circuit 3 s after the start of charge.

Find the total capacitance for two capacitors in parallel.

Parallel:  $C_T = C_1 + C_2 = 20 + 40 = 60 \mu\text{F}$


Then  $T = RC_T = (100 \times 10^3)(60 \times 10^{-6}) = 6 \text{ s}$      *Ans.*

Write the formula for charging voltage and substitute values to find  $v_C$ .

$$v_C = V(1 - e^{-t/RC}) \tag{19-17}$$

$$= 10(1 - e^{-3/6}) = 10(1 - e^{-0.5}) = 10(1 - 0.607) = 10(0.393) = 3.93 \text{ V} \quad \text{Ans.}$$

- 19.7** A simple switching circuit for producing a sawtooth wave is shown (Fig. 19-12a). The switch  $S$  is closed and then opened very quickly so that the capacitor is not fully charged but only charged to the linear portion of its charging exponential curve (Fig. 19-12b). (The linear portion is the straightest portion at the start of the charge cycle.) The switch is opened and closed at specific intervals to produce a sawtooth voltage wave across the capacitor. Find the magnitude of the  $v_C$  curve when the switching time interval is one-fifth the time constant of the circuit. What is the time interval?

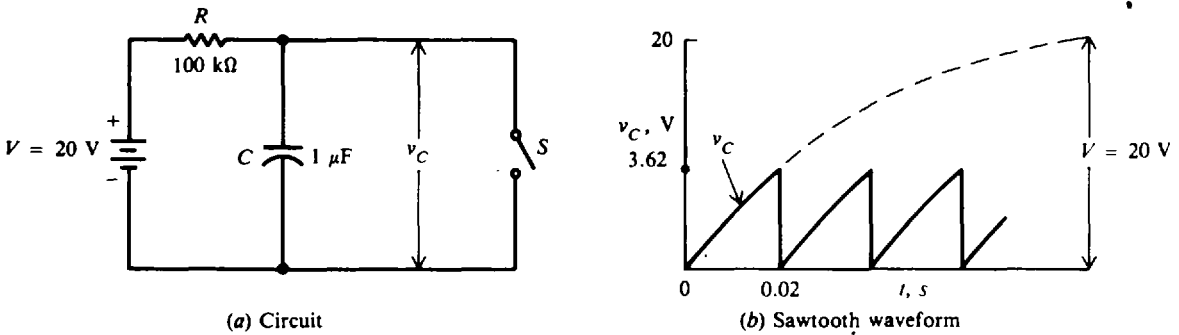

**Fig. 19-12** RC circuit for generating a sawtooth waveform

Write the voltage formula for charging the capacitor.

$$v_C = V(1 - e^{-t/RC}) \tag{19-17}$$


If  $t = \frac{1}{5}RC$ , then

$$e^{-t/RC} = e^{-(1/5)RC/RC} = e^{-1/5} = e^{-0.2} = 0.819$$

Then  $v_C = 20(1 - 0.819) = 20(0.181) = 3.62 \text{ V}$      *Ans.*

Time interval  $t = \frac{1}{5}RC = \frac{(100 \times 10^3)(1 \times 10^{-6})}{5} = 0.02 \text{ s}$      *Ans.*

- 19.8** A RC series circuit with a rectangular pulse input is shown (Fig. 19-13). A rectangular pulse is a special case of a constant dc source because the voltage is a constant  $V$  when the pulse is on and a constant zero when the pulse is off. If a single pulse is applied to the circuit, find the voltage across the resistance at the time of 0.5, 1, and 2 ms. The pulse has a maximum voltage of 10 V and lasts for 1 ms.

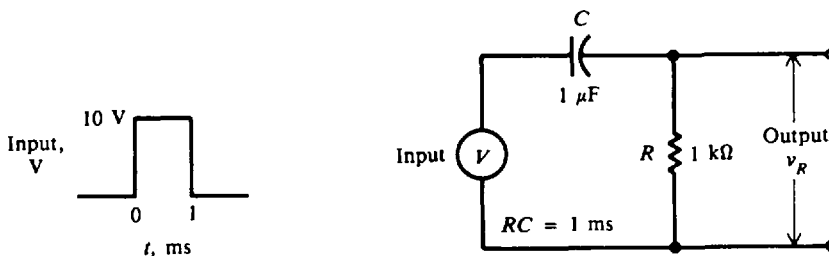

**Fig. 19-13** RC circuit with rectangular pulse of applied voltage

Find the time constant of the circuit.

$$T = RC = (1 \times 10^3)(1 \times 10^{-6}) = 1 \times 10^{-3} = 1 \text{ ms}$$

Write the formula for  $v_R$  when the circuit is charging.

$$v_R = Ve^{-t/RC} \quad (19-16)$$

When  $t = 0.5$  ms,

$$v_R = 10e^{-0.5/1} = 10e^{-0.5} = 10(0.607) = 6.07 \text{ V} \quad \text{Ans.}$$

When  $t = 1$  ms,

$$v_R = 10e^{-1/1} = 10e^{-1} = 10(0.368) = 3.68 \text{ V} \quad \text{Ans.}$$

At  $t = 1$  ms, the pulse is turned off. At that instant the source voltage is zero, so

$$\begin{aligned} v_R + v_C &= 0 \\ v_R &= -v_C \end{aligned}$$

Since the voltage across the capacitor  $v_C$  cannot change instantly, the voltage across the resistor becomes  $-v_C$ . Now at an instant *before*  $t = 1$  ms,

$$\begin{aligned} v_R + v_C &= 10 \\ v_C &= 10 - v_R = 10 - 3.68 = 6.32 \text{ V} \end{aligned}$$

Therefore, at  $t = 1$  ms,  $v_R = -v_C = -6.32$  V and then  $v_R$  decays to zero. So the formula for  $v_R$  at  $t = 1$  ms is:

$$v_R = -6.32e^{-t/RC}$$

Then in the next 1 ms or when  $t = 2$  ms measured from the origin,

$$v_R = -6.32e^{-1} = -6.32(0.368) = -2.33 \text{ V} \quad \text{Ans.}$$

The plot for  $v_R$  is as shown in Fig. 19-14.

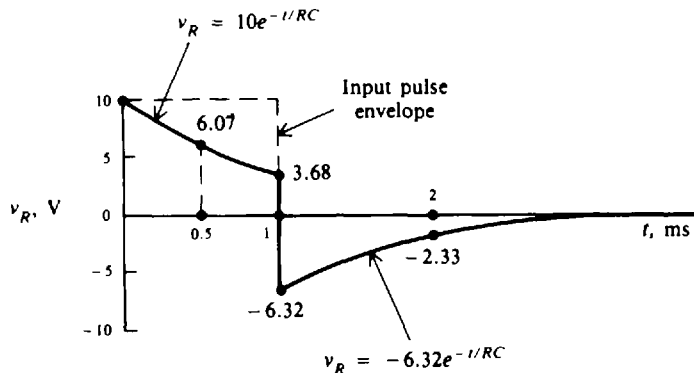


Fig. 19-14 Charge and discharge of an RC circuit

- 19.9 A RC series circuit with a square-wave input is shown (Fig. 19-15). The input is a periodic train of pulses with an amplitude of 10 V and a width of 1 ms, with each pulse generated every 2 ms. Plot the output voltage curve across the resistor.

$$T = RC = (1 \times 10^3)(0.1 \times 10^{-6}) = 0.1 \times 10^{-3} = 0.1 \text{ ms}$$

Find some values of  $v_R$  within the 0 to 1 ms that the pulse is on, say at  $T = 0.1$  ms,  $2T = 0.2$  ms, and  $3T = 0.3$  ms. First, write the formula for  $v_R$  when the circuit is charging.

$$v_R = Ve^{-t/RC} \quad (19-16)$$

When  $t = T = 0.1$  ms,  $v_R = 10e^{-1} = 10(0.368) = 3.68$  V

When  $t = 2T = 0.2$  ms,  $v_R = 10e^{-2} = 10(0.135) = 1.35$  V

When  $t = 3T = 0.3$  ms,  $v_R = 10e^{-3} = 10(0.05) = 0.5$  V

At  $t = 5T$  or 0.5 ms,  $v_R$  will reach its steady-state value of 0 V.

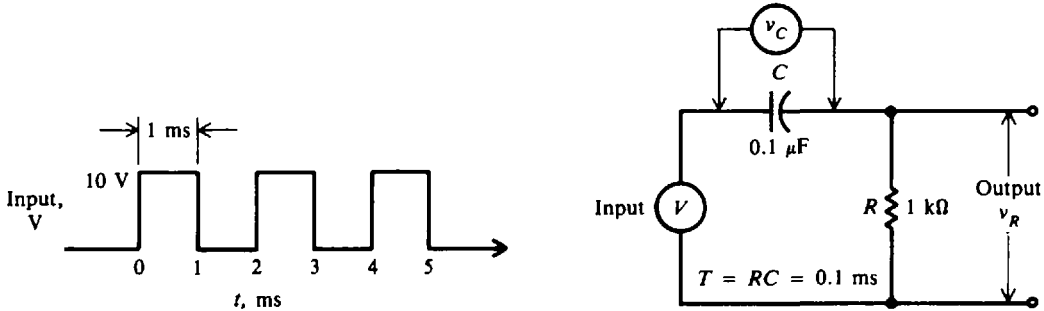


Fig. 19-15 RC circuit with square wave for input voltage

When the pulse is turned off between 1 and 2 ms,  $v_R$  will instantly drop to  $-10$  V because the capacitor charged to 10 V requires a finite time to discharge. Then  $v_R$  will gradually rise to 0 V.

The formula for  $v_R$  when the circuit is discharging is

$$v_R = -Ve^{-t/RC} \tag{19-21}$$

where  $t$  represents time from 1 to 2 ms. So when  $t = 1.1$  ms from origin,

$$v_R = -3.68$$
 V

When  $t = 1.2$  ms,

$$v_R = -1.35$$
 V

When  $t = 1.3$  ms,

$$v_R = -0.5$$
 V

When  $t = 1.5$  ms,

$$v_R = 0$$
 V

The symmetry of the output curve is shown in the plot (Fig. 19-16). Because the circuit has changed the waveform of input pulses to peaks, it is called a *RC peaker*. It is called also a *differentiating circuit* because  $v_R$  can change instantaneously. We obtain a peak output when the circuit time constant is small compared with the half-period of the input waveform. In this case  $T = 0.1$  ms compared with the half-period of 1 ms, so the ratio of the time constant to the half-period is 1 to 10.

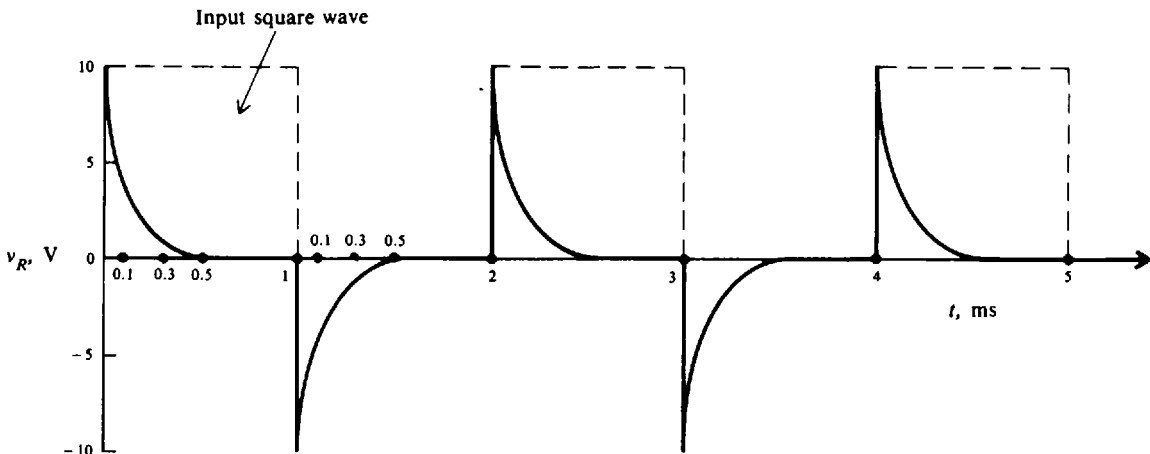


Fig. 19-16 Charge and discharge of a RC circuit with a short time constant

In summary, to explain a short  $RC$  time circuit, a 10-V input is applied for 1 ms (10 time constants of the  $RC$  circuit), allowing  $C$  to become completely charged and  $v_R$  to be 0 V (Figs. 19-15 and 19-16). After  $C$  is charged,  $v_C$  remains at 10 V with  $v_R$  at 0 V ( $V = v_C + v_R$ ). After 1 ms, the total voltage  $V$  drops to zero,  $C$  discharges completely in five time constants, and  $v_C$  and  $v_R$  remain at 0 V while there is no applied voltage. On the next cycle,  $C$  charges and discharges completely again. The interval between pulses when the input voltage is 0 V acts as a "short" to the  $RC$  circuit.

- 19.10 For the circuit shown (Fig. 19-17), (a) find the time constant. (b) If at time  $t = 0$ , the voltage across the capacitor  $C_1$  is  $v_1 = 10$  V and the voltage across the capacitor  $C_2$  is  $v_2 = 20$  V with the polarity shown, find the current when  $t = 0.26$  s.

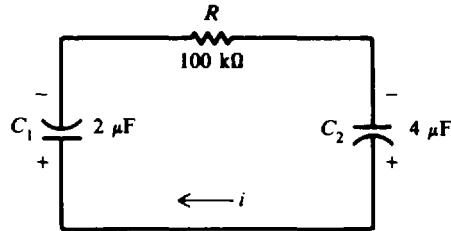


Fig. 19-17  $RC$  circuit during discharge

- (a) First, find the total capacitance for two capacitors in series with a single discharge path.

$$C_T = \frac{C_1 C_2}{C_1 + C_2} = \frac{2(4)}{2 + 4} = 1.33 \mu\text{F}$$

The time constant is

$$T = RC_T = (100 \times 10^3)(1.33 \times 10^{-6}) = 0.133 \text{ s} \quad \text{Ans.}$$

- (b) The net voltage  $V$  is  $v_2 - v_1 = 20 - 10 = 10$  V so  $C_1$  is being charged in the direction of  $i$  as shown.

$$\begin{aligned} i &= \frac{V}{R} e^{-t/RC} \quad (\text{Here } V \text{ is the net voltage at } t = 0) \\ &= \frac{10}{100 \times 10^3} e^{-0.26/0.133} = 10^{-4} e^{-1.95} = (0.1 \times 10^{-3})(0.142) = 0.0142 \text{ mA} \quad \text{Ans.} \end{aligned}$$

### Supplementary Problems

- 19.11 Find the value of  $e^{-Rt/L}$  for the following values of  $R$ ,  $L$ , and  $t$ .

	$R, \Omega$	$L, \text{H}$	$t, \text{s}$
(a)	10	10	1
(b)	5	10	1
(c)	5	10	2
(d)	10	5	1
(e)	10	5	2

Ans. (a) 0.368, (b) 0.607; (c) 0.368; (d) 0.135; (e) 0.018

19.12 Calculate the time constants of the following inductive circuits:

	L	R
(a)	20 H	400 Ω
(b)	20 μH	500 kΩ
(c)	50 mH	50 Ω
(d)	40 μH	5 Ω
(e)	20 mH	100 Ω

Ans. (a) 50 ms; (b) 40 μs; (c) 1 ms; (d) 8 μs; (e) 0.2 ms

19.13 In the circuit shown (Fig. 19-18), find (a) the current 1 s after the switch is closed, (b) the time constant, and (c) the steady-state or final value of the current.

Ans. (a)  $i = 1.11$  A; (b)  $T = 4$  s; (c)  $I = 5$  A

19.14 The circuit (Fig. 19-18) is closed for 20 s. Then the switch is opened so that current decays through  $L$  and  $R$ . Calculate  $i$ ,  $v_R$ , and  $v_L$  after 2 s.

Ans.  $i = 3.03$  A;  $v_R = 15.2$  V;  $v_L = -15.2$  V

19.15 A current of 20 A is flowing in a  $RL$  series circuit the instant before the switch is opened. If  $R = 10$  Ω and  $L = 10$  H, find the current after 3 s has elapsed. Also find  $v_R$  and  $v_L$  at that time.

Ans.  $i = 0.996$  A;  $v_R = 9.96$  V;  $v_L = -9.96$  V

19.16 A 5-Ω resistor and a 10-H inductor are connected in series across a 60-V dc line. Find the time constant, steady-state current, and time to reach the steady-state current value.

Ans.  $T = 2$  s;  $I = 12$  A;  $5T = 10$  s

19.17 A series circuit has the following values:  $V = 80$  V,  $R = 20$  Ω, and  $L = 10$  H. (a) What is the time constant? (b) What is the current 1 s after the circuit is closed? (c) What are  $v_R$  and  $v_L$  at that time? (d) How long after the circuit is closed will the current reach a constant value?

Ans. (a)  $T = 0.5$  s; (b)  $i = 3.46$  A; (c)  $v_R = 69.2$  V;  $v_L = 10.8$  V; (d)  $t = 2.5$  s

19.18 A circuit contains three inductances in series with a resistance across a 120-V source. If each inductor is 8 H and the resistor is 12 Ω, find (a) the time constant. Find the value of the current (b) 1 s, (c) 2 s, and (d) 3 s after the circuit is closed.

Ans. (a)  $T = 2$  s; (b)  $i = 3.94$  A; (c)  $i = 6.32$  A; (d)  $i = 7.77$  A

19.19 A circuit (Fig. 19-19) contains two inductances in parallel, a series inductance, and a series resistance across a 110-V source. Find the time constant and the current 0.45 s after the circuit is closed.

Ans.  $T = 0.895$  s ( $L_T = 13.43$  H);  $i = 2.90$  A

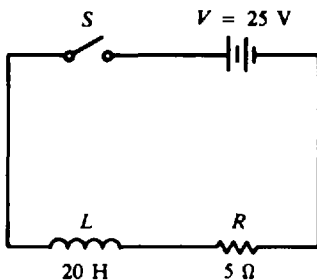


Fig. 19-18  $RL$  circuit

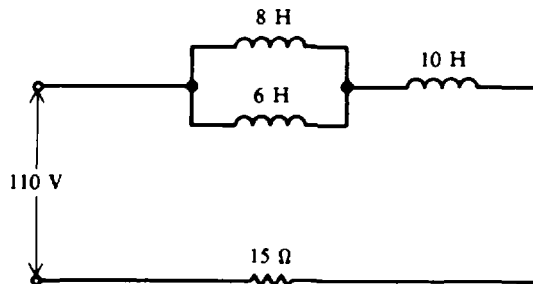


Fig. 19-19 Combination  $RL$  circuit

19.20 A *RL* series circuit is shown (Fig. 19-20a).



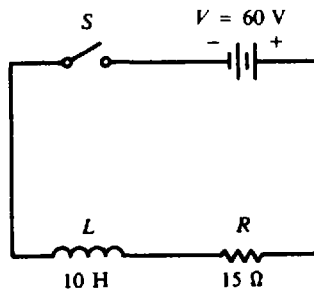


Fig. 19-20a *RL* circuit

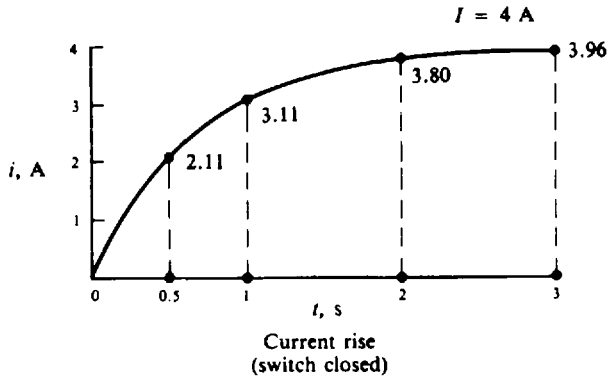
- (a) Plot the rise of current after the switch is closed when time is equal to 0.5, 1, 2, and 3 s.
- (b) After the current reaches its final value, the switch is opened. Plot the decay of current when time is equal to 0.5, 1, 2, and 3 s after the switch is closed.
- (c) Plot the voltages across the resistance and inductance when the switch is closed and opened for the same time values at 0.5, 1, 2, and 3 s. *Ans.* See Fig. 19-20b, parts 1, 2, 3, and 4.




(1)

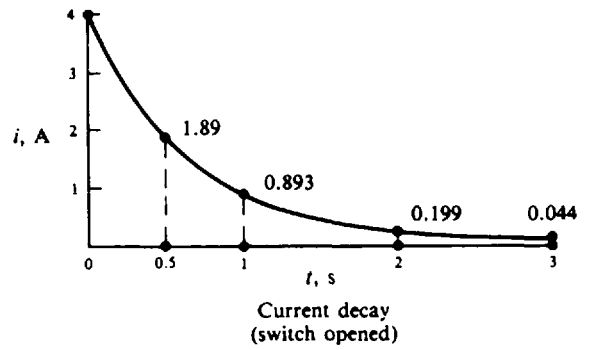

(2)

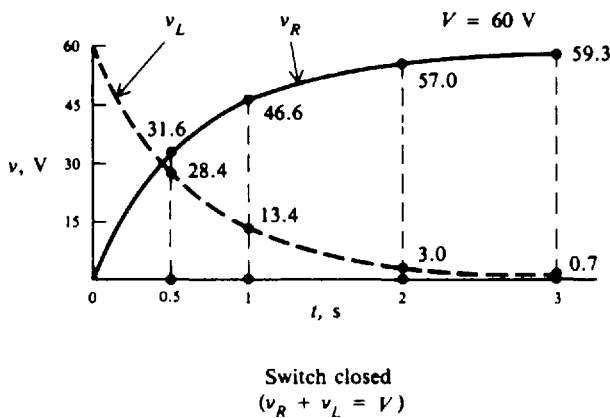

(3)

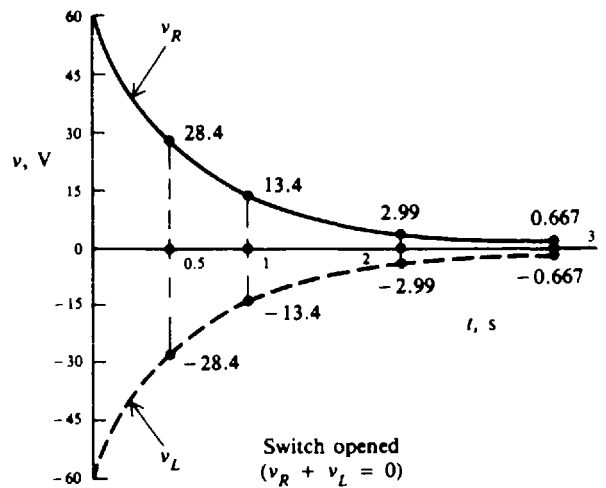

(4)

Fig. 19-20b

19.21 Find the value of  $e^{-t/RC}$  for the following values of  $R$ ,  $C$ , and  $t$ .

	$R$	$C$	$t$
(a)	1 M $\Omega$	1 $\mu$ F	1 s
(b)	1 M $\Omega$	0.5 $\mu$ F	1 s
(c)	100 k $\Omega$	1 $\mu$ F	0.1 s
(d)	100 k $\Omega$	10 $\mu$ F	0.5 s
(e)	10 k $\Omega$	2 $\mu$ F	10 ms

Ans. (a) 0.368; (b) 0.135; (c) 0.368; (d) 0.607; (e) 0.607

19.22 Calculate the time constants of the following capacitive circuits:

	$R$	$C$
(a)	1 M $\Omega$	0.001 $\mu$ F
(b)	1 M $\Omega$	1 $\mu$ F
(c)	250 k $\Omega$	0.05 $\mu$ F
(d)	110 k $\Omega$	100 pF
(e)	5 k $\Omega$	300 pF

Ans. (a) 1 ms; (b) 1 ms; (c) 12.5 ms; (d) 1  $\mu$ s; (e) 1.5  $\mu$ s

19.23 In the circuit shown (Fig. 19-21), what are (a) the current 1 s after the circuit is closed, and (b)  $v_R$  and  $v_C$  at that instant of time? Ans. (a)  $i = 36$  mA; (b)  $v_R = 72.8$  V; (c)  $v_C = 47.2$  V

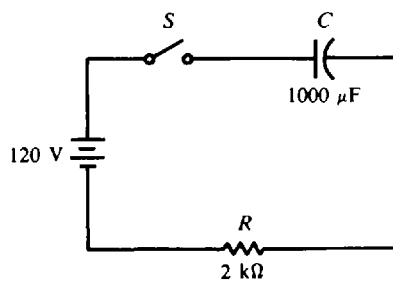


Fig. 19-21 RC circuit

19.24 After the circuit (Fig. 19-21) has reached its steady-state condition where the capacitor has been charged to 120 V, the switch is opened. Find (a) the time required for the circuit to have reached steady state, (b) the current 1.5 s after the circuit is opened, and (c)  $v_R$  and  $v_C$  at that time.

Ans. (a)  $t = 10$  s; (b)  $i = -28$  mA; (c)  $v_R = -56.7$  V;  $v_C = 56.7$  V

19.25 In a series RC circuit with the capacitor *charging*, fill in the missing values. Time  $t$  is measured at the instant the switch is closed.



	V, V	R	C, $\mu\text{F}$	T	t	I	i	$v_R$	$v_C$
(a)	115	100 k $\Omega$	1	?	0.1 s	?	?	?	?
(b)	220	1 k $\Omega$	?	1 ms	2 ms	?	?	?	?
(c)	110	?	10	10 s	5 s	?	?	?	?
(d)	115	10 k $\Omega$	100	?	6 s	?	?	?	?

Ans.

	V, V	R	C, $\mu\text{F}$	T	t	I	i	$v_R$ , V	$v_C$ , V
(a)	....	....	....	0.1 s	....	1.15 mA	0.42 mA	42.3	72.7
(b)	....	....	1	....	....	0.22 A	29.8 mA	29.8	190.2
(c)	....	1 M $\Omega$	....	....	....	0.11 mA	0.067 mA	66.8	43.2
(d)	....	....	....	1 s	....	11.5 mA	0 A	0	115

19.26 In a series RC circuit with the capacitor *discharging*, fill in the same missing values as in the table accompanying Prob. 19.25. Time  $t$  is measured at the instant the switch is opened. The circuit constants of  $V$ ,  $R$ , and  $C$  are the same as those in Prob. 19.25.

Ans.

	V, V	R	C, $\mu\text{F}$	T	t	I	i	$v_R$ , V	$v_C$ , V
(a)	....	....	....	0.1 s	....	-1.15 mA	-0.42 mA	-42.3	42.3
(b)	....	....	1	....	....	-0.22 A	-29.8 mA	-29.8	29.8
(c)	....	1 M $\Omega$	....	....	....	-0.11 mA	-0.067 mA	-66.8	66.8
(d)	....	....	....	1 s	....	-11.5 mA	0 A	0	0

19.27 Find the time constant of the circuits shown (Fig. 19-22).

- Ans. (a)  $T = 1$  s  
 (b)  $T = 8.33 \mu\text{s}$  ( $R_T = 8.33 \Omega$ )  
 (c)  $T = 0.2$  ms ( $C_T = 0.2 \mu\text{F}$ )  
 (d)  $T = 90 \mu\text{s}$  ( $C_T = 0.09 \mu\text{F}$ )

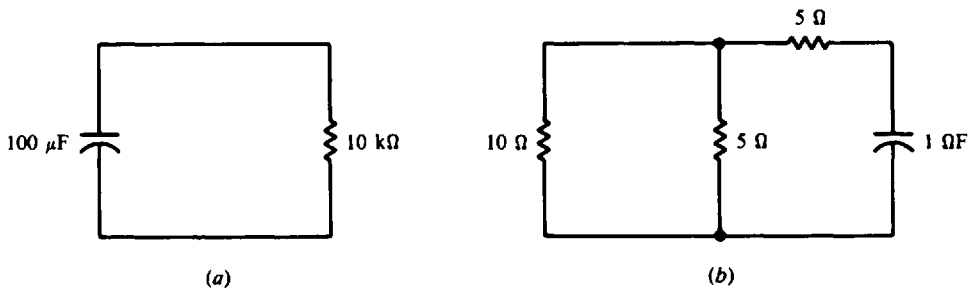


Fig. 19-22 RC circuit configurations



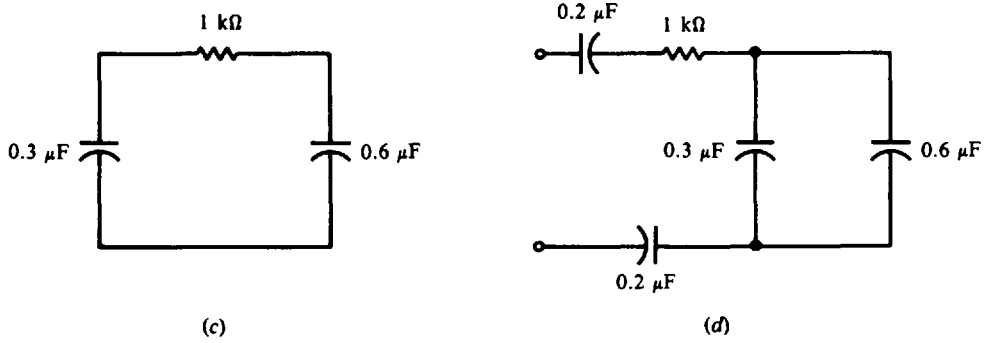
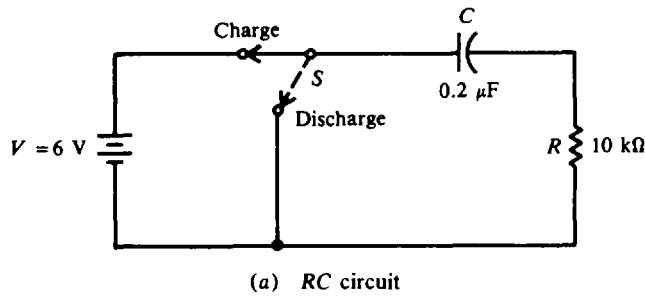
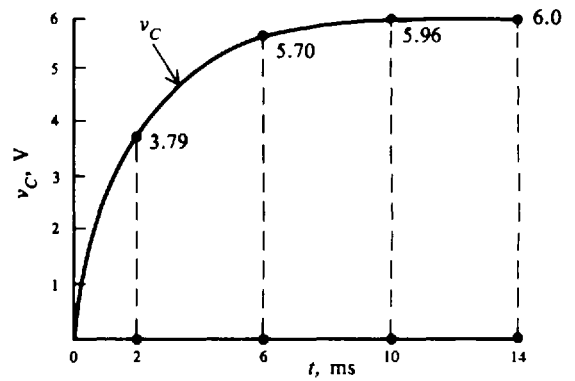


Fig. 19-22(cont.)

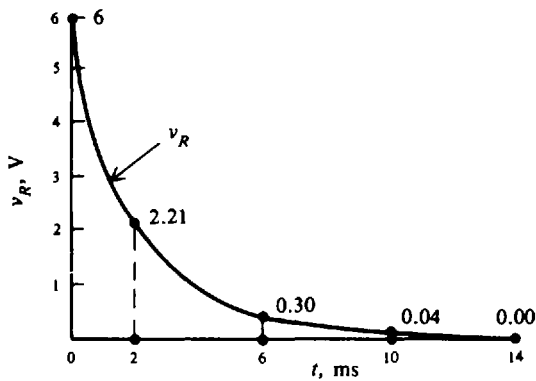19.28 The RC circuit (Fig. 19-23a) has its switch closed at time  $t = 0$ . Plot curves for  $i$ ,  $v_R$ , and  $v_C$  for  $t = 0, 2, 6, 10,$  and  $14$  ms during the charging cycle. Ans. See Fig. 19-23b.



(a) RC circuit

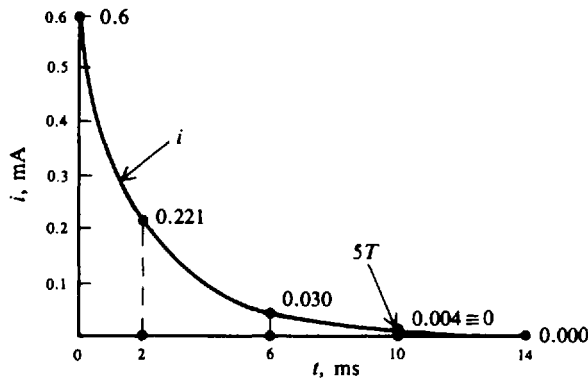

(b)  $i$ ,  $v_R$ ,  $v_C$  curves during charging cycle

Fig. 19-23a, b

19.29 After the circuit (Fig. 19-23a) has reached steady-state values, the switch is opened. Plot curves for  $i$ ,  $v_R$ , and  $v_C$  for  $t = 0, 2, 6, 10,$  and  $14$  ms during this discharging cycle. *Ans.* See Fig. 19-23c.

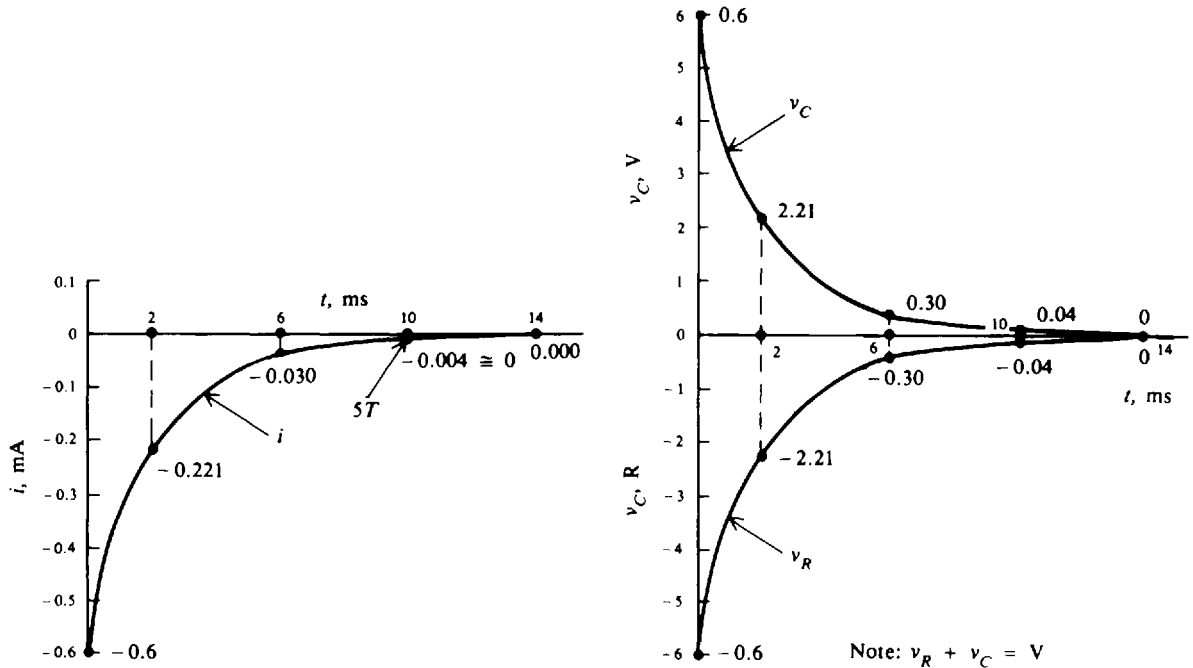


Fig. 19-23c  $i$ ,  $v_R$ ,  $v_C$  curves during discharging cycle

19.30 The dc source of 6 V in the circuit (Fig. 19-23a) is replaced by a single pulse of 6 V amplitude lasting 2 ms (Fig. 19-24a). Plot the voltage across the 10-k $\Omega$  resistance for  $t = 0, 2, 4, 6, 10,$  and  $14$  ms after the switch is closed. (Round off answers to two significant figures.) *Ans.* See Fig. 19-24b.

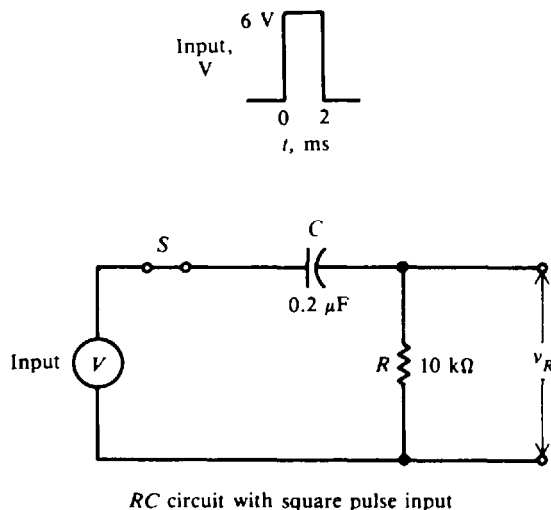


Fig. 19-24a RC circuit with square pulse input


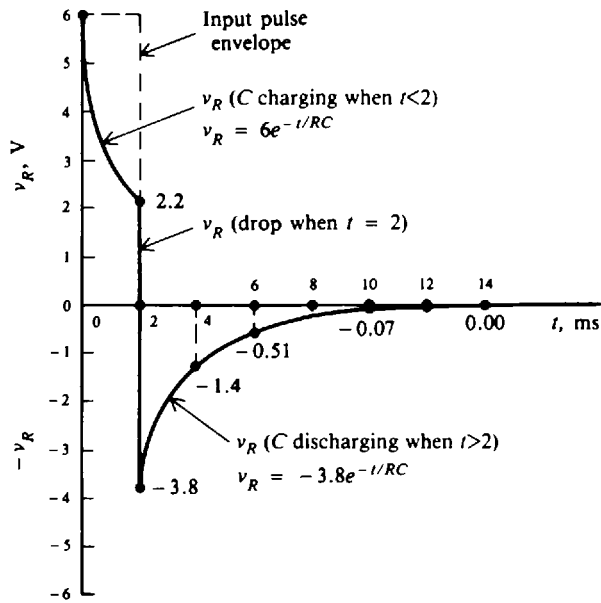
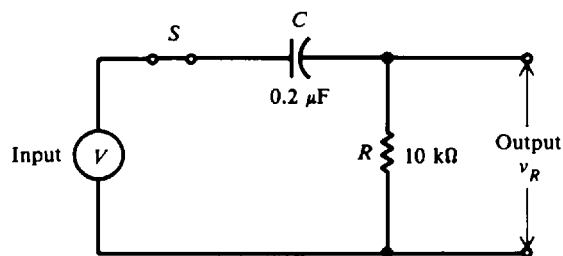


Fig. 19-24b

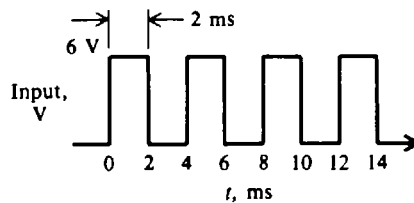19.31 The source voltage for the circuit (Fig. 19-24a) is now replaced by a train of repetitive pulses (Fig. 19-25a). Each pulse has a 6-V amplitude and a pulse width of 2 ms. The period of the pulse train is 4 ms. Draw the plot of  $v_R$  for  $t = 0, 2, 4, 6, 8, 10, 12$  and  $14$  ms. (Round off answers to two significant figures.) Ans. See Fig. 19-25b.



RC circuit with square wave input

Fig. 19-25a RC circuit with square wave input

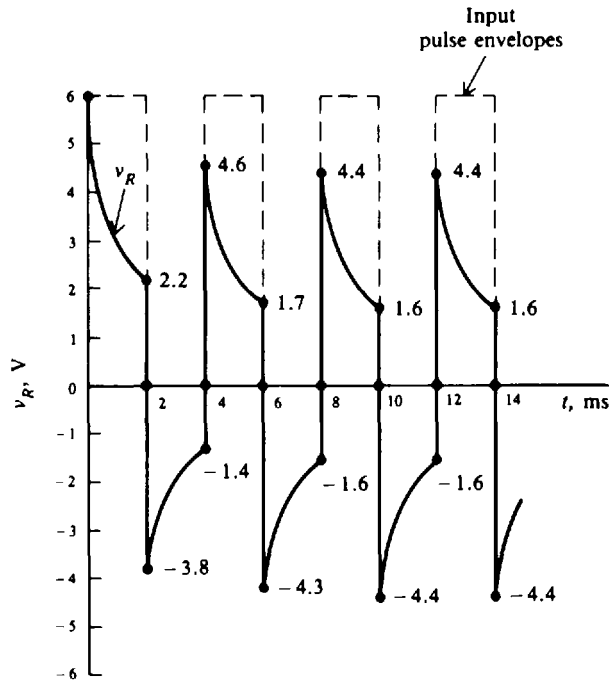


Fig. 19-25b

- 19.32 For the circuit shown (Fig. 19-26), find (a) the time constant, and (b) the current at  $t = 10$  ms when the voltage across  $C_1$  is 15 V and the voltage across  $C_2$  is 25 V, with the polarity as indicated at  $t = 0$ .  
 Ans. (a)  $T = 5$  ms; (b)  $i = 0.541$  mA

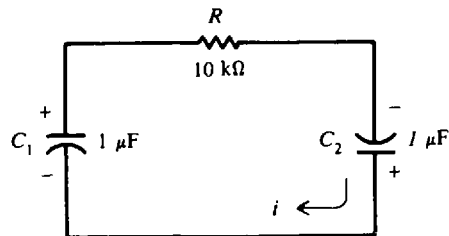


Fig. 19-26 RC discharging circuit

- 19.33 If the polarity of capacitor  $C_2$  is reversed (Fig. 19-26), find the current at  $t = 10$  ms.  
 Ans.  $i = -0.135$  mA
- 19.34 A  $0.05\text{-}\mu\text{F}$  capacitor is charged to 264 V. It discharges through a  $40\text{-k}\Omega$  resistor. How much time is required for  $v_C$  to discharge down to 66 V?    Ans.  $t = 2.77$  ms
- 19.35 A 100-V source is in series with a  $2\text{-M}\Omega$  resistor and a  $2\text{-}\mu\text{F}$  capacitor. How much time is required for  $v_C$  to charge to 63.2 V?    Ans.  $t = 4$  s (1T)

# Chapter 20

## Electrical Measurements

### BASIC MEASURING INSTRUMENTS

Ammeters, voltmeters, ohmmeters, and wattmeters are instruments used for measuring current, voltage, resistance, and power, respectively. The simplest instruments commonly used to measure voltage and current are the electromechanical direct-current (dc) and the alternating-current (ac) meters.

The most common sensing mechanism used in basic dc ammeters, voltmeters, and ohmmeters is a current-sensing device called the *D'Arsonval meter movement* or the permanent-magnetic-moving-coil movement (Fig. 20-1). The moving coil has a permanent magnet and a coil of wire that carries current. The coil is in the field of the permanent magnet. When there is current in the coil, a torque results that tends to rotate the coil. Rotation of the coil is restrained by helical springs so that the motion of the coil and hence of the pointer is proportional to the current in the coil.

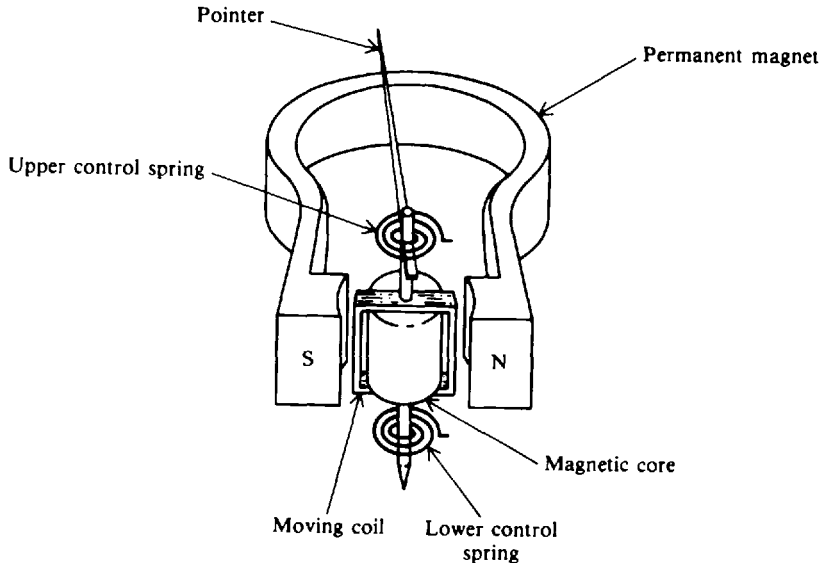


Fig. 20-1 D'Arsonval meter mechanism

### AMMETERS


An *ammeter* measures electric current. Its scale may be calibrated in amperes, milliamperes, or microamperes. To measure current an ammeter is inserted in series with the circuit being tested (Fig. 20-2). The addition of the ammeter increases the resistance of the circuit by an amount equal to the internal resistance of the meter  $R_M$ .

From Ohm's law, the current *without* the meter is

$$I_o = \frac{V}{R_o} \quad (20-1)$$

and *with* the meter added is
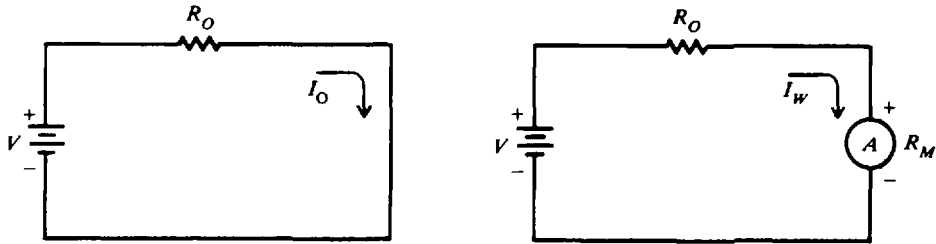
$$I_w = \frac{V}{R_o + R_M} \quad (20-2)$$



(a)  $I_O$  true current, without ammeter in circuit      (b)  $I_w$  measured current, with ammeter in circuit

Fig. 20-2 Circuit for current measurement

The *accuracy* of the meter  $K_A$  is the ratio of the current when the meter is in the circuit (measured current),  $I_w$ , to the current without the meter (true current),  $I_O$ , or

$$K_A = \frac{I_w}{I_O} \quad (20-3)$$

Also, by substitution,

$$\begin{aligned} K_A &= \frac{V}{R_O + R_M} \frac{R_O}{V} \\ &= \frac{R_O}{R_O + R_M} \end{aligned} \quad (20-4)$$

The percent of *loading error* is the percent error in the ammeter reading due to loading effects that result from the added resistance of the meter.

$$\text{Loading error (\%)} = (1 - K_A)(100) \quad (20-5)$$

A reading which is 100 percent accurate means that the loading error is 0 percent. A 99 percent accurate reading means that the loading error is 1 percent.

A second error in a real ammeter is *calibration error* that arises from the fact that the meter face may not be accurately marked. The specification for this error is in terms of full-scale current. Typical values are about 3 percent of full-scale current.

**Example 20.1** A 1-mA meter has a calibration error of  $\pm 3$  percent. If the currents are 1 and 0.25 mA, what are the ranges for each reading of the ammeter?

The deviation from true current is  $(\pm 0.03)(1 \text{ mA}) = \pm 0.03 \text{ mA}$ . At 1 mA, the ammeter would read between

$$1 \text{ mA} \pm 0.03 \text{ mA} = 0.97 \text{ to } 1.03 \text{ mA} \quad \text{Ans.}$$

The off-scale reading of 1.03 mA means that 1.03 mA can produce a 1-mA reading. At 0.25 mA, the reading would be between

$$0.25 \text{ mA} \pm 0.03 \text{ mA} = 0.22 \text{ to } 0.28 \text{ mA} \quad \text{Ans.}$$

**Example 20.2** Find the accuracy and percent loading error of a 10-mA ammeter with a 200- $\Omega$  resistance (Fig. 20-3). Also find the true current  $I_O$  and the measured current  $I_w$ .

Use Eq. (20-4).

$$K_A = \frac{R_O}{R_O + R_M} = \frac{1000}{1000 + 200} = 0.833 \text{ or } 83.3\% \quad \text{Ans.}$$

The accuracy value of 83.3 percent tells us that the ammeter reading is 83.3 percent of the true current. The accuracy is low because the meter resistance is close in value to that of the resistor. To have a high degree of accuracy, the meter resistance should be much less than the circuit resistance.

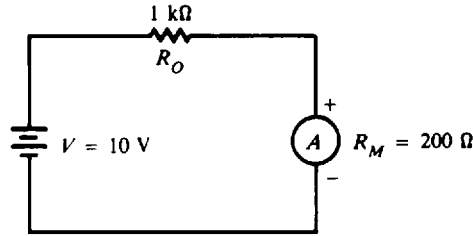


Fig. 20-3 Measuring current through a 1-kΩ resistor

$$\begin{aligned} \text{Loading error (\%)} &= (1 - K_A)(100) & (20-5) \\ &= (1 - 0.833)(100) = 16.7\% & \text{Ans.} \end{aligned}$$

$$\begin{aligned} I_O &= \frac{V}{R_O} & (20-1) \\ &= \frac{10}{1000} = 0.01 \text{ A} = 10 \text{ mA} & \text{Ans.} \end{aligned}$$

$$\begin{aligned} I_w &= \frac{V}{R_O + R_M} & (20-2) \\ &= \frac{10}{1000 + 200} = \frac{10}{1200} = 8.33 \times 10^{-3} \text{ A} = 8.33 \text{ mA} & \text{Ans.} \end{aligned}$$

or 
$$K_A = \frac{I_w}{I_O} \quad (20-3)$$

from which  $I_w = K_A I_O = 0.833(10) = 8.33 \text{ mA}$ , which checks

**Ammeter Shunts**

An ammeter with a full-scale current  $I_M$  can be shunted by a resistor  $R_{SH}$  in order to measure currents greater than  $I_M$  (Fig. 20-4). The purpose of a shunt is to extend the *range* of the ammeter by allowing it to measure current higher than its original full-scale value. By Kirchoff's current law,

$$I_{SH} = I_T - I_M \quad (20-6)$$

Since the voltage across the shunt resistor must equal the voltage across the ammeter,

$$\begin{aligned} I_{SH} R_{SH} &= I_M R_M \\ \text{or } R_{SH} &= \frac{I_M R_M}{I_{SH}} \end{aligned} \quad (20-7)$$

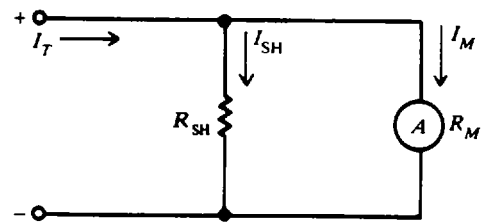


Fig. 20-4 Ammeter with a shunt

Substituting  $I_{SH}$  from Eq. (20-6) into Eq. (20-7),

$$R_{SH} = \frac{I_M R_M}{I_T - I_M} \quad (20-8)$$

The input resistance of the shunted ammeter is

$$R'_M = \frac{R_M R_{SH}}{R_M + R_{SH}} \quad (20-9)$$

Also 
$$R'_M = \frac{V_{in}}{I_{in}} = \frac{I_M R_M}{I_T} \quad (20-10)$$

When computing the accuracy [Eq. (20-4)] for a shunted ammeter, use  $R'_M$  instead of  $R_M$ .



**Example 20.3** An ammeter with a meter resistance of  $50\ \Omega$  and a full-scale deflection current of  $1\ \text{mA}$  is to be shunted to enable it to measure currents up to  $5\ \text{mA}$ . Find the value of the shunt resistor and the value of the input resistance of the shunted ammeter.

Use Eq. (20-8).

$$R_{SH} = \frac{I_M R_M}{I_T - I_M} = \frac{1(50)}{5 - 1} = \frac{50}{4} = 12.5\ \Omega \quad \text{Ans.}$$

(Note that we did not convert current from milliamperes to amperes since the unit milliampere appears both in the numerator and denominator of the  $R_{SH}$  formula and thus cancels out.)

$$R'_M = \frac{I_M R_M}{I_T} \tag{20-10}$$

$$= \frac{1(50)}{5} = 10\ \Omega \quad \text{Ans.}$$

The meter's ability to measure current was extended from  $1$  to  $5\ \text{mA}$  by shunting with a  $12.5\text{-}\Omega$  resistor. This is a factor of  $5$  so the ammeter resistance effectively is reduced by a factor of  $5$  ( $R_M/R'_M = 50/10 = 5$ ).

**VOLTMETERS**

A simple dc voltmeter can be constructed by placing a resistor  $R_S$ , called a *multiplier*, in series with the ammeter meter movement, and by marking the meter face to read voltage  $V$  across the resistor and voltmeter (Fig. 20-5).

By Ohm's law,

So, 
$$V = I_M R_S + I_M R_M \tag{20-11}$$

$$I_M R_S = V - I_M R_M$$

from which 
$$R_S = \frac{V}{I_M} - R_M \tag{20-12}$$

When  $R_M$  is negligibly low,

$$R_S \cong \frac{V}{I_M}$$

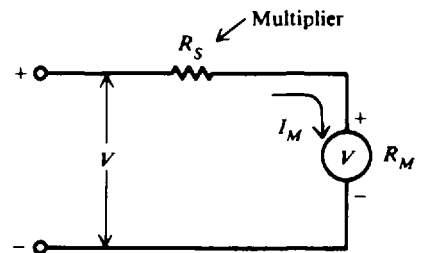


Fig. 20-5 Simple dc voltmeter

**Example 20.4** A  $1\text{-mA}$  meter movement (ammeter with a full-scale deflection of  $1\ \text{mA}$ ) with internal resistance of  $50\ \Omega$  is to be constructed as a voltmeter. What is the value of the series resistor needed to measure a full-scale voltage of  $50\ \text{V}$ ?

Use Eq. (20-12).

$$R_S = \frac{V}{I_M} - R_M = \frac{50}{1 \times 10^{-3}} - 50 = 50\ \text{k}\Omega \quad \text{Ans.}$$

**Example 20.5** We desire to construct a multirange voltmeter from a  $50\text{-}\mu\text{A}$  meter movement with an internal resistance of  $2\ \text{k}\Omega$  (Fig. 20-6). The ranges are to be  $5, 10,$  and  $25\ \text{V}$ . Find the multiplier resistance  $R_S$  for each range.

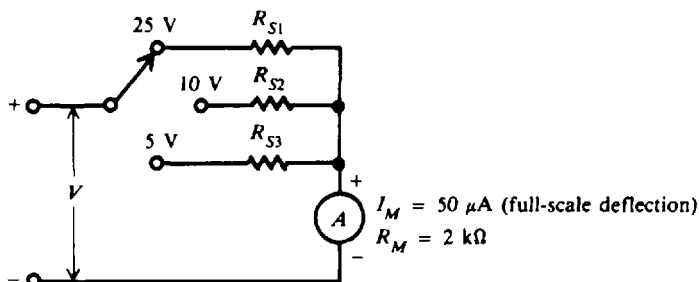


Fig. 20-6 Multirange voltmeter

$$R_S = \frac{V}{I_M} - R_M \quad (20-12)$$

$$\text{25-V range:} \quad R_{S1} = \frac{25}{50 \times 10^{-6}} - 2000 = 498 \text{ k}\Omega \cong 500 \text{ k}\Omega \quad \text{Ans.}$$

$$\text{10-V range:} \quad R_{S2} = \frac{10}{50 \times 10^{-6}} - 2000 = 198 \text{ k}\Omega \cong 200 \text{ k}\Omega \quad \text{Ans.}$$

$$\text{5-V range:} \quad R_{S3} = \frac{5}{50 \times 10^{-6}} - 2000 = 98 \text{ k}\Omega \cong 100 \text{ k}\Omega \quad \text{Ans.}$$

### Sensitivity

The input resistance of a simple voltmeter (Fig. 20-5) is

$$R_{in} = R_S + R_M$$

$$\text{Also} \quad R_{in} = \frac{V}{I_M} \quad (20-13)$$

where  $V$  is full-scale voltage and  $I_M$  is full-scale current of the meter movement.

A *sensitivity factor*  $S$  is defined as the reciprocal of the full-scale current.

$$S = \frac{1}{I_M} \quad (20-14)$$

$$\text{In units,} \quad S = \frac{1}{\text{A}} = \frac{1}{\text{V}/\Omega} = \Omega/\text{V} \quad (\text{ohms per volt})$$

Thus, a voltmeter with a full-scale current of 1 mA has a sensitivity of  $S = 1/10^{-3} = 1000 \Omega/\text{V}$ . Equation (20-13) can be modified to

$$R_{in} = SV \quad (20-15)$$

The value of  $S$  is generally printed on the meter face.

**Example 20.6** A voltmeter uses a 1-mA movement. Find the input resistance on the 10-, 50-, and 500-V ranges.

$$S = \frac{1}{I_M} \quad (20-14)$$

$$= \frac{1}{1 \text{ mA}} = \frac{1}{10^{-3}} = 1000 \Omega/\text{V}$$

$$R_{in} = SV \quad (20-15)$$

$$\text{10-V range:} \quad R_{in} = 1000 \times 10 = 10 \text{ k}\Omega \quad \text{Ans.}$$

$$\text{50-V range:} \quad R_{in} = 1000 \times 50 = 50 \text{ k}\Omega \quad \text{Ans.}$$

$$\text{500-V range:} \quad R_{in} = 1000 \times 500 = 500 \text{ k}\Omega \quad \text{Ans.}$$

### Voltmeter Loading Effect

When a voltmeter is connected to a circuit, the voltmeter draws current from the circuit. This current produces a voltage drop across the resistance of the coil, which is subtracted from the voltage being measured. This reduction in voltage is called the *loading effect*.

The *accuracy* of the voltmeter,  $K_V$ , is defined as the ratio of the voltage when the voltmeter is in the circuit (measured voltage),  $V_w$ , to the voltage without the voltmeter (true voltage),  $V_o$ . To determine  $K_V$  (Fig. 20-7), use Ohm's law

$$I = \frac{V_o}{R_o + R_{in}}$$

where  $V_O$  is the true voltage being measured,  $R_O$  is the resistance of the circuit, and  $R_{in}$  is the input resistance of the voltmeter. The voltage indicated by the meter is

$$V_w = IR_{in}$$

so 
$$V_w = \frac{R_{in}}{R_O + R_{in}} V_O \quad (20-16)$$

and 
$$K_v = \frac{V_w}{V_O} = \frac{R_{in}}{R_O + R_{in}} \quad (20-17)$$

As with the ammeter,

$$\text{Loading error (\%)} = (1 - K_v)(100) \quad (20-5)$$

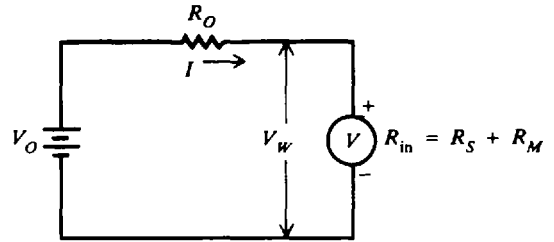


Fig. 20-7 Voltmeter measuring circuit

**Example 20.7** The voltmeter in the 50-V range is to measure the voltage across terminals  $ab$  (Fig. 20-8). Find the true voltage  $V_O$  across  $ab$  (voltmeter is not in the circuit), measured voltage  $V_w$  (voltmeter is in the circuit), and the accuracy  $K_v$  of the voltmeter reading.

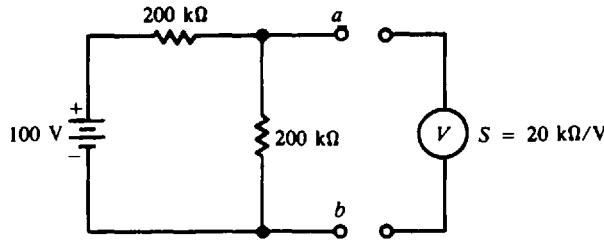


Fig. 20-8 Measuring voltage in a circuit

$$V_O = \left( \frac{200 \text{ k}\Omega}{200 \text{ k}\Omega + 200 \text{ k}\Omega} \right) (100 \text{ V}) = 50 \text{ V} \quad \text{Ans.}$$

$R_O$  is the equivalent (Thevenin) resistance of the circuit looking into terminals  $ab$ .

$$R_O = \frac{(200 \text{ k}\Omega)(200 \text{ k}\Omega)}{200 \text{ k}\Omega + 200 \text{ k}\Omega} = 100 \text{ k}\Omega$$

On the 50-V range the voltmeter has an input resistance of

$$\begin{aligned} R_{in} &= SV \\ &= (20 \text{ k}\Omega/\text{V})(50) = 1 \text{ M}\Omega \end{aligned} \quad (20-15)$$

$$\begin{aligned} V_w &= \frac{R_{in}}{R_O + R_{in}} V_O \\ &= \frac{10^6}{100 \times 10^3 + 10^6} (50) = \frac{50}{1.1} = 45.5 \text{ V} \quad \text{Ans.} \end{aligned} \quad (20-16)$$

$$\begin{aligned} K_v &= \frac{V_w}{V_O} \\ &= \frac{45.5}{50} = 0.910 \quad \text{or} \quad 91\% \quad \text{Ans.} \end{aligned} \quad (20-17)$$

The accuracy is 91 percent, so the voltmeter reading is 91 percent of the true voltage, or  $0.91(50 \text{ V}) = 45.5 \text{ V}$ .

**OHMMETERS**

An instrument to determine resistance is the *ohmmeter*. The ohmmeter (Fig. 20-9) consists of a battery, a meter movement calibrated to read ohms, and a resistor.  $R_O$  is a current-limiting resistance and includes the meter resistance  $R_M$ .  $R_O$  is shown as an adjustable resistor for zeroing

and for correcting the aging of the battery.  $R_x$  is the unknown resistance to be measured. Zeroing is done by first short-circuiting the ohmmeter terminals  $ab$  and adjusting  $R_O$  to produce full-scale deflection.

The full-scale deflection in current is

$$I_M = \frac{V}{R_O} \quad (20-18)$$

When  $R_x$  is connected across the ohmmeter terminals, the current is

$$I = \frac{V}{R_O + R_x} \quad (20-19)$$

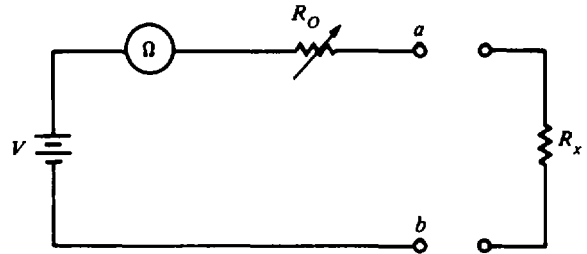


Fig. 20-9 A simple ohmmeter

A convenient way of determining ohmmeter deflection is using a deflection factor  $D$ , which is the ratio of  $I$  to  $I_M$ .

$$D = \frac{I}{I_M} = \frac{R_O}{R_O + R_x} \quad (20-20)$$

$$I = DI_M \quad (20-21)$$

Solving for  $R_x$  in Eq. (20-20), we obtain

$$R_x = \frac{1 - D}{D} R_O \quad (20-22)$$

If half-scale deflection occurs, that is  $D = 1/2$ ,  $R_x = R_O$  so that we mark the value of  $R_O$  at mid-scale on the ohmmeter face.

**Example 20.8** An ohmmeter (Fig. 20-10) has a meter movement with a full-scale deflection of  $50 \mu\text{A}$ . The open-circuit voltage  $V$  at terminals  $ab$  is  $6 \text{ V}$ . The ohmmeter is zeroed and then an unknown resistor  $R_x$  is measured, which produces quarter-scale deflection. Find the value of the unknown resistor.

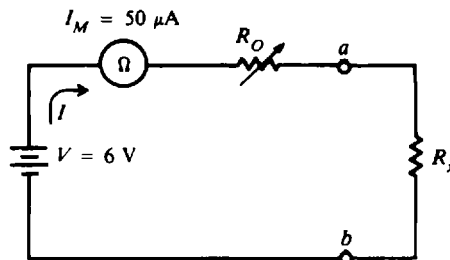


Fig. 20-10 Measuring resistance with an ohmmeter

First, find  $R_O$  from Eq. (20-18).

$$R_O = \frac{V}{I_M} = \frac{6}{50 \times 10^{-6}} = 120 \text{ k}\Omega$$

Then solve for  $R_x$ , using Eq. (20-22).

$$R_x = \frac{1 - D}{D} R_O = \frac{1 - 1/4}{1/4} 120 = 3(120) = 360 \text{ k}\Omega \quad \text{Ans.}$$

Therefore, the quarter scale of this ohmmeter face would read  $360 \text{ k}\Omega$ .

**Example 20.9** Assume an ohmmeter with  $R_O = 15 \Omega$  and full-scale current  $I_M = 500 \mu\text{A}$ . Determine the meter current with  $0$ -,  $5$ -,  $10$ -,  $15$ - $\Omega$ , and  $1\text{-M}\Omega$  resistors across the meter terminal.

Find the deflection factor for each resistor:

$$D = \frac{R_o}{R_o + R_x} \tag{20-20}$$

$R_x = 0 \Omega:$   $D = \frac{15}{15} = 1$

$R_x = 5 \Omega:$   $D = \frac{15}{15 + 5} = 0.75$

$R_x = 10 \Omega:$   $D = \frac{15}{15 + 10} = 0.60$

$R_x = 15 \Omega:$   $D = \frac{15}{15 + 15} = 0.50$

$R_x = 1 \text{ M}\Omega:$   $D = \frac{15}{15 + 15 \times 10^6} \cong 1 \times 10^{-6} \cong 0$

Next, find the current values corresponding to each resistor:

$$I = DI_M \tag{20-21}$$

$R_x = 0 \Omega:$   $I = 1(500 \times 10^{-6}) = 500 \mu\text{A}$  (full-scale deflection) *Ans.*

$R_x = 5 \Omega:$   $I = 0.75(500 \times 10^{-6}) = 375 \mu\text{A}$  *Ans.*

$R_x = 10 \Omega:$   $I = 0.60(500 \times 10^{-6}) = 300 \mu\text{A}$  *Ans.*

$R_x = 15 \Omega:$   $I = 0.50(500 \times 10^{-6}) = 250 \mu\text{A}$  *Ans.*

$R_x = 1 \text{ M}\Omega:$   $I = 0(500 \times 10^{-6}) = 0 \mu\text{A}$  (zero deflection) *Ans.*

Notice that when the resistance is increased from 0 to 5  $\Omega$ , the meter current decreased by 125  $\mu\text{A}$  ( $500 \mu\text{A} - 375 \mu\text{A}$ ). Similarly when the resistance is increased from 5 to 10  $\Omega$ , the current decreases by only 75  $\mu\text{A}$  ( $375 \mu\text{A} - 300 \mu\text{A}$ ). Thus an ammeter scale used to measure resistance is *nonlinear* (Fig. 20-11). Also, the ohmmeter scale is a reversal of the usual ammeter and voltmeter scales. That is, the zero resistance ( $R_x = 0$ ) is at the right end of the scale and the infinite resistance is at the left end ( $R_x = 1 \text{ M}\Omega \gg R_o$ ).


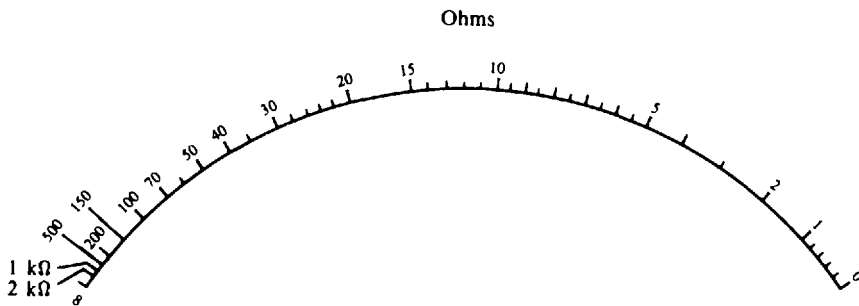


Fig. 20-11 Ohmmeter scale

**Continuity Tests**

A wire conductor that is continuous without a break has practically 0  $\Omega$  resistance. Thus, the ohmmeter can be used to test for continuity. This test should be conducted on the lowest ohms range. A break in the wire will give a reading of infinite resistance, indicating an open circuit.

**Example 20.10** Suppose there is a cable of wires harnessed together (Fig. 20-12) in which the individual wires cannot be seen. How would you proceed to find the wire that connects to terminal A?

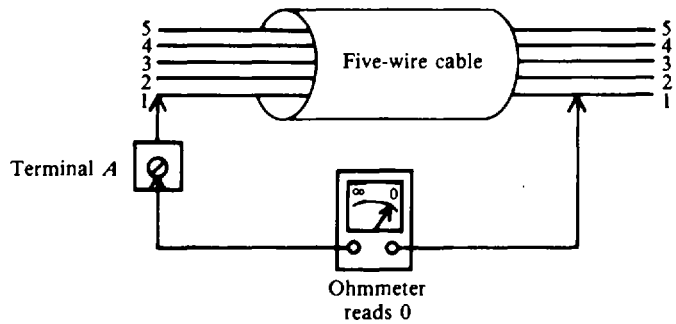

**Fig. 20-12** Continuity from A to 1 shows this wire connected to terminal A

Connect one terminal of the meter to terminal A to which wire 1 is connected (Fig. 20-12). The other meter test lead is then brought in contact with each of the wire ends marked 1', 2', 3', 4', and 5'. A 0-Ω reading on the meter indicates continuity of a direct electrical path between the two ends of the wire. Unless a short-circuit exists between wires, the continuity test will identify the two ends of the same wire.

**MULTIMETERS**

A *multimeter* is a single instrument capable of measuring voltage, resistance, and current. The volt-ohm-milliammeter (VOM) is the most common multimeter. A typical VOM has a meter movement with a full-scale current of 50 μA or a sensitivity of 20 kΩ/V when used as a dc voltmeter. One meter movement is used to measure milliamperes, dc voltage, ac voltage, and ohms.

**Example 20.11** Generally a VOM has voltage ranges that extend from 2.5 V on the lowest range to about 5000 V on the highest range. If the VOM has a sensitivity of 20 kΩ/V, what is the input resistance for these two extreme ranges of voltage?

$$R_{in} = SV \tag{20-15}$$

For 2.5 V:  $R_{in} = \frac{20 \text{ k}\Omega}{V} (2.5 \text{ V}) = 50 \text{ k}\Omega \quad \text{Ans.}$

For 5000 V:  $R_{in} = \frac{20 \text{ k}\Omega}{V} (5000 \text{ V}) = 100\,000 \text{ k}\Omega = 100 \text{ M}\Omega \quad \text{Ans.}$

**Example 20.12** When used as an ohmmeter, the VOM typically has three ranges: R × 1, R × 100, and R × 10 000. Explain.

The R × 1 is the lowest range, making this range scale suitable for measuring low resistance. If the reading is 15 on the R × 1 scale, the resistance measured is 15 Ω. The R × 100 is the medium-range scale. A reading of 15 on the R × 100 scale means the measured resistance is 1500 Ω. The R × 10 000 is the highest range, where a reading of 15 on that scale means 150 000 Ω resistance.

If the resistance to be measured is known approximately, switch the ohmmeter to the scale that will indicate this value most accurately. If the resistance is not known, set the various scales from highest on down until approximately a half-scale deflection is reached. A half-scale deflection gives the most accurate reading.

**ALTERNATING-CURRENT METERS**

AC meters measure electrical quantities of current and voltage that change in amplitude and direction periodically with time (Fig. 20-13). However, for frequencies greater than a few hertz, the moving-coil assembly cannot follow the rapid changes because of inertia and damping. The coil responds on the basis of the average value of the alternating quantities. Although the scale of

an ac meter can be calibrated in average values, the scale for general applications is calibrated in terms of rms or effective values.

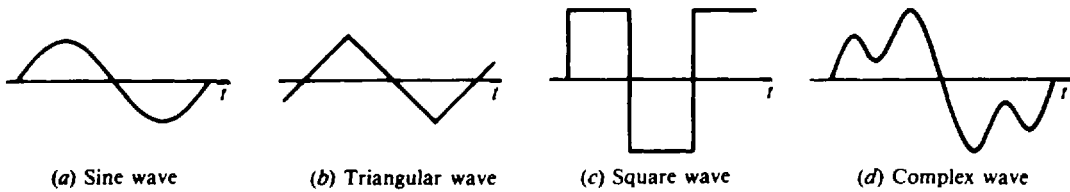


Fig. 20-13 Examples of ac waveforms

AC meters generally use one of two methods for measuring ac current or voltage. For frequencies below several hundred hertz, electromechanical meter movements that respond directly to ac excitation can be used. For higher frequencies, the ac quantities are first converted to dc and then applied to a D'Arsonval movement.


**Half-Wave Rectifier Circuit**

The simplest type of ac voltmeter is the half-wave rectifier circuit (Fig. 20-14a). The *ab* terminals are the measuring terminals. The signal to be measured is a sine wave with peak values of  $V_p$ . The diode permits current to flow in one direction during the positive half-cycle, and presents a very high resistance to current in the other direction during the negative half-cycle. The resulting current through the meter (Fig. 20-14b) results in an rms calibrated reading (Fig. 20-13c). The ammeter actually indicates the average value, which is

$$I_{av} = 0.318 I_p \tag{20-23}$$

However, generally ac meters are marked off to indicate the effective or rms value, which is

$$I_{rms} = 0.707 I_p \tag{20-24}$$

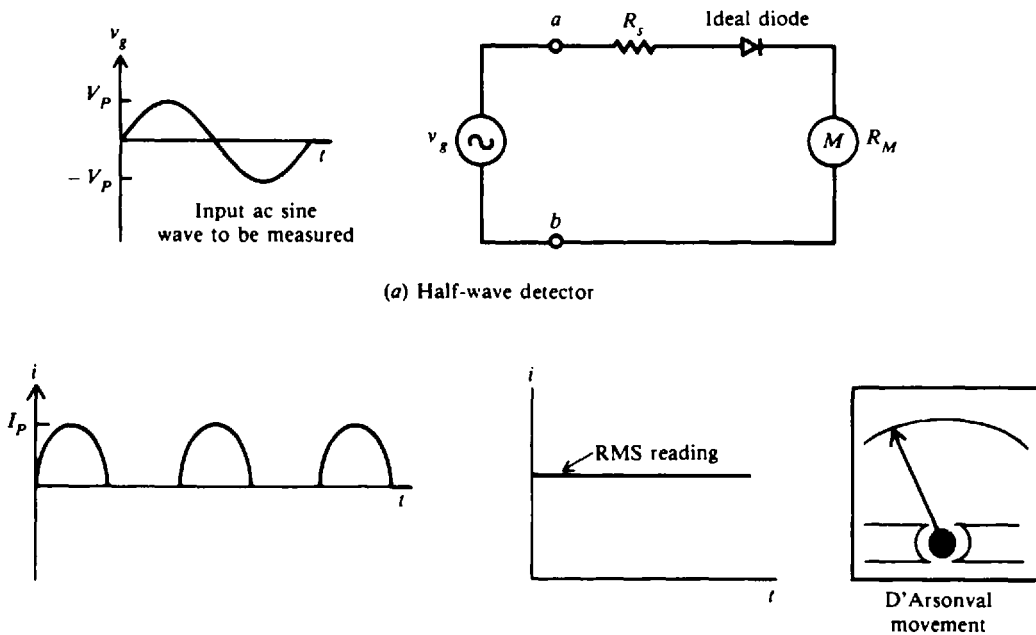

(b) Ammeter current output

(c) Output rms scale reading

Fig. 20-14 AC meter with half-wave bridge detector. Meter reads rms of input.

The rms scale is valid only for a sine wave input. If we measure a square wave or a sawtooth, the rms reading is not correct. Assume that the rms scale of any ac meter applies only to sine wave inputs unless it is known that the instrument is a true rms voltmeter.

For the half-wave rectifier circuit (Fig. 20-14a),

$$\begin{aligned} V_p &= I_p(R_S + R_M) \\ V_{rms} &= 0.707 V_p \end{aligned} \tag{20-25}$$

Substitute  $V_p$  in Eq. (20-25),

$$\begin{aligned} V_{rms} &= 0.707(R_S + R_M)I_p = 0.707(R_S + R_M)\left(\frac{I_{av}}{0.318}\right) \\ \text{so } V_{rms} &= 2.22(R_S + R_M)I_{av} \end{aligned} \tag{20-26}$$

This equation shows how the rms value of the input sine wave is related to the average current in this type of ac ammeter.

The input resistance is  $R_S + R_M$  during the positive half-cycle and  $R_S$  during the negative half-cycle. Since  $R_M \ll R_S$  in any practical design, the input resistance is approximately  $R_S$  throughout the entire cycle.

$$V_{rms} \cong 2.22 R_{in} I_{av} \cong 2.22 R_S I_{av} \tag{20-27}$$

For the full-scale deflection, Eq. (20-27) becomes

$$V_M = 2.22 R_{in} I_M$$

where  $V_M$  is the full-scale rms value and  $I_M$  is the full-scale dc current. Solving for  $R_{in}$ ,

$$R_{in} = 0.45 \frac{V_M}{I_M} \tag{20-28}$$

Define sensitivity  $S_{ac}$  as follows:

$$S_{ac} = \frac{0.45}{I_M} \tag{20-29}$$

So

$$R_{in} = S_{ac} V_M \tag{20-30}$$

On commercial ac voltmeters of the half-wave rectifier type, the value of  $S_{ac}$  is printed on the meter face.

**Example 20.13** A half-wave rectifier type of ac meter has a sine wave input voltage of 100 V peak (Fig. 20-15a). Calibrate the meter face at two readings each for  $V_p$  and  $V_{rms}$ .

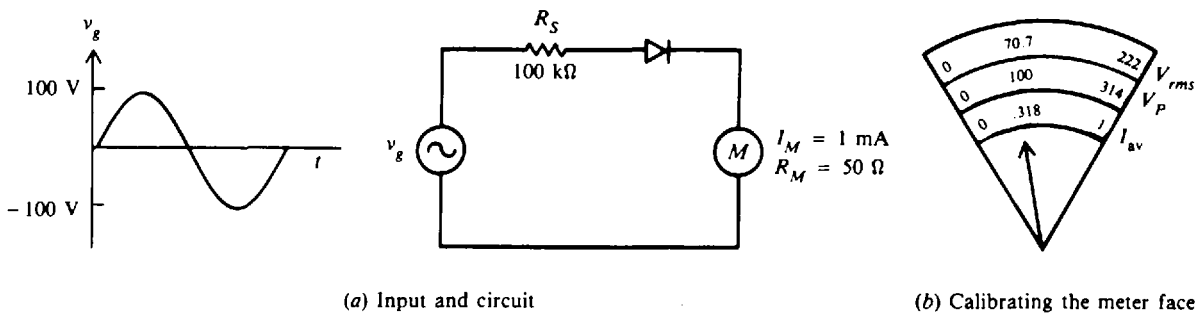


Fig. 20-15 AC meter with half-wave rectifier circuit

By Ohm's law,

$$I_p = \frac{V_p}{R_S + R_M} = \frac{100}{100 \times 10^3 + 50} \cong 1 \times 10^{-3} \text{ A} = 1 \text{ mA}$$



The ammeter actually indicates the average value, so

$$I_{av} = 0.318 I_P \tag{20-23}$$

$$= 0.318 \times 1 \text{ mA} = 0.318 \text{ mA}$$

$$V_{rms} = 0.707 V_P \tag{20-25}$$

$$= 0.707(100) = 70.7 \text{ V}$$

So an average current of 0.318 mA is produced by an input peak voltage of 100 V, which is 70.7  $V_{rms}$ . For an average value of 1 mA to represent a full-scale deflection of 1 mA, the input voltage is raised to 314 V peak ( $1/0.318 \times 100$ ) and 222  $V_{rms}$  ( $314 \times 0.707$ ). (See Fig. 20-15b.) The rest of the peak-voltage scale and rms-voltage scale can be marked off in a similar manner.

**Example 20.14** If  $R_S$  is 1 M $\Omega$  and the meter movement has a full-scale current of 50  $\mu$ A, find the rms value of an input sine wave that produces full-scale deflection (Fig. 20-16).

Use Eq. (20-27).

$$V_{rms} \cong 2.22 R_S I_{av} \cong 2.22(10^6)(50 \times 10^{-6}) \cong 111 \text{ V} \quad \text{Ans.}$$

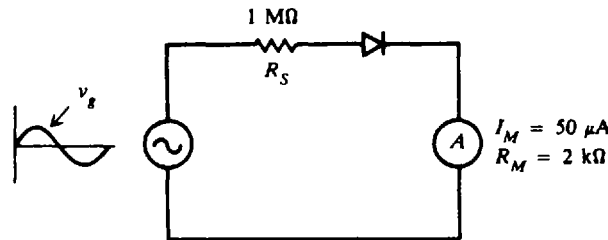


Fig. 20-16 Simple ac voltmeter


**Example 20.15** A VOM has a dc sensitivity of 20 k $\Omega$ /V and ac sensitivity of 5 k $\Omega$ /V. Find the input resistance of the VOM in the 10-V dc range and in the 10-V rms range.

10-V dc range:  $R_{in} = SV \tag{20-15}$   
 $= (20 \times 10^3)(10) = 200 \text{ k}\Omega \quad \text{Ans.}$

10-V ac range:  $R_{in} = S_{ac} V_M \tag{20-30}$   
 $= (5 \times 10^3)(10) = 50 \text{ k}\Omega \quad \text{Ans.}$

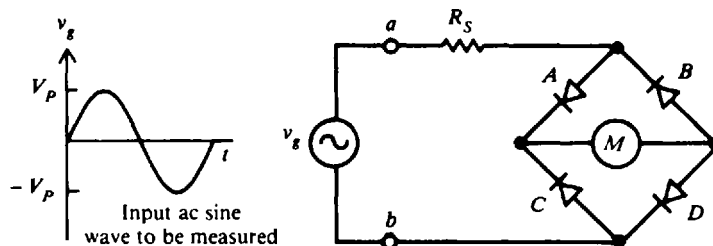**Full-Wave Rectifier Circuit**

One way of improving the sensitivity of a rectifier type of ac meter is to use full-wave rectification (Fig. 20-17a). Diodes A and D conduct during the positive half-cycle. During the negative cycle, diodes B and C conduct. As a result, the current flows from left to right throughout the entire cycle (Fig. 20-17a). The resulting wave shapes are half-sine waves above the axis (Fig. 20-17b) and give a rms reading (Fig. 20-17c).



(a) Full-wave detector

Fig. 20-17 AC meter with full-wave bridge detector. Meter reads rms of input.

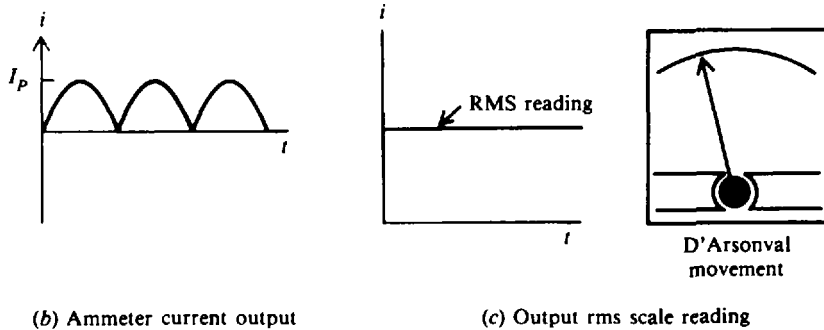


Fig. 20-17 (cont.)

The average value of the meter current is

$$I_{av} = 0.636 I_p \tag{20-31}$$

which is exactly double that of a half-wave-rectified sine wave. Similarly, the ac sensitivity for a full-wave rectifier becomes

$$S_{ac} = \frac{0.90}{I_M} \tag{20-32}$$

**Example 20.16** The bridge (Fig. 20-17a) is connected to 1-mA meter movement. What is the ac sensitivity? Use Eq. (20-32).

$$S_{ac} = \frac{0.90}{I_M} = \frac{0.90}{1 \times 10^{-3}} = 900 \Omega/V \quad \text{Ans.}$$

**Example 20.17** If a 100- $\mu$ A meter movement with a resistance of 1 k $\Omega$  is used to a full-wave bridge detector, what should the size of  $R_S$  be for a 50-V rms sine wave to produce full-scale deflection?

For half-wave detector,  $V_{rms} = 2.22(R_S + R_M)I_{av}$  (20-26)

Then for full-wave detector,  $V_{rms} = 1.11(R_S + R_M)I_{av}$

from which  $R_S = 0.90 \frac{V_{rms}}{I_{av}} - R_M$

If  $R_M \ll R_S$ ,

$$R_S \cong 0.90 \frac{V_{rms}}{I_{av}} \cong 0.90 \left( \frac{50}{100 \times 10^{-6}} \right) \cong 450 \times 10^3 \cong 450 \text{ k}\Omega \quad \text{Ans.}$$

**True RMS Voltmeters**

To prevent error in measuring ac voltage or current, rms values of nonsinusoidal waveforms should be measured with true rms instruments. The rms value, expressed as a function of peak value, is noted for each waveform (Fig. 20-18). The meter error is given by the following equation:

$$\text{Meter error} = \frac{\text{true value} - \text{indicated value}}{\text{true value}} \tag{20-33}$$

One type of true rms voltmeter uses a thermocouple (Fig. 20-19a). The input signal (e.g., sine wave, square wave, or sawtooth) is applied to the heater, which raises the temperature of the thermocouple and produces an output dc voltage  $V$ . This output voltage is proportional to the square of the rms voltage input and can be read by a dc voltmeter. The indicator of the dc voltmeter must be marked according to the square relation, resulting in a nonlinear scale (Fig. 20-19b).

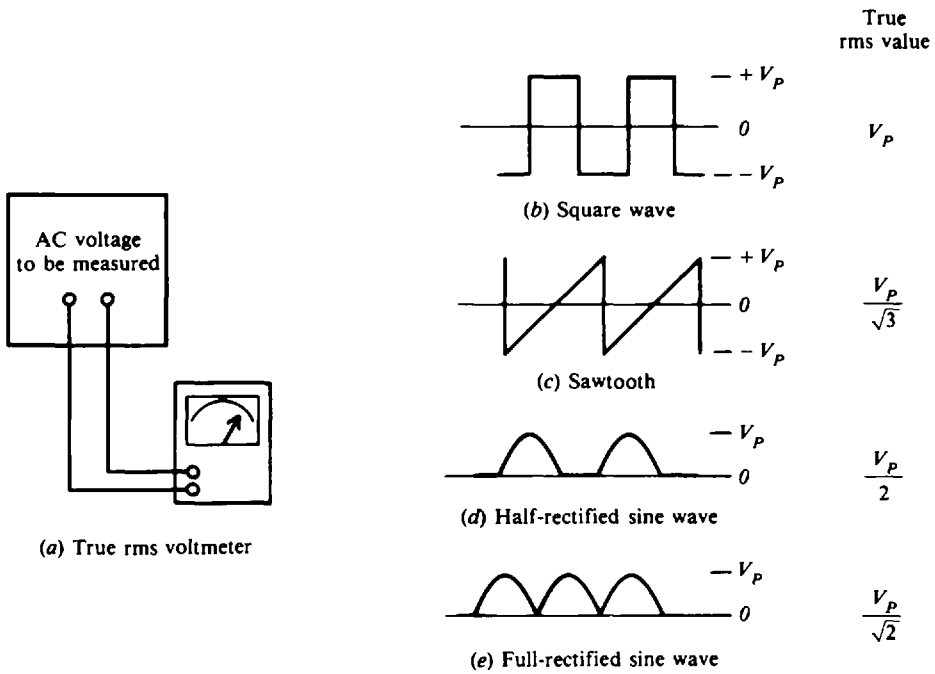


Fig. 20-18 Using a true rms voltmeter

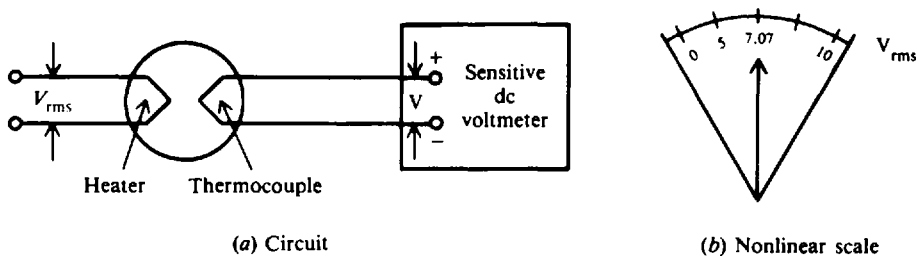


Fig. 20-19 Simple thermocouple circuit for measuring true rms voltage

**Example 20.18** A full-wave rectifier type of ammeter indicates a current of 4.44 mA rms when measuring the triangular wave current (Fig. 20-20). What is the true rms value of the waveform? Calculate the error of the ac meter.

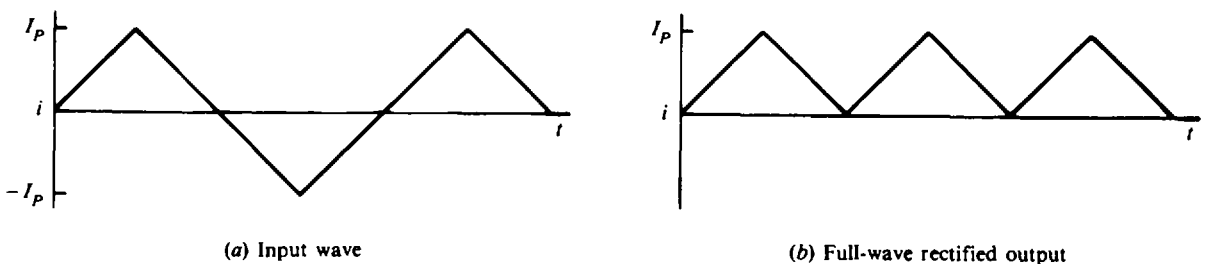


Fig. 20-20 Input and output waveforms of a triangular wave

First, find the average value of current since the ac meter responds accurately to this value. For a full-rectified wave,

$$\frac{\text{rms value}}{\text{Average value}} = \frac{0.707}{0.636} = 1.11$$

$$\text{Average value} = \frac{\text{rms value}}{1.11} = \frac{4.44}{1.11} = 4 \text{ mA}$$

$$\text{True peak value} = 2(\text{average value}) = 2(4) = 8 \text{ mA}$$

For a triangular wave (Fig. 20-18c),

$$V_{\text{rms}} = \frac{V_P}{\sqrt{3}}$$

or 
$$I_{\text{rms}} = \frac{I_P}{\sqrt{3}} = \frac{8}{\sqrt{3}} = 4.62 \text{ mA} \quad \text{Ans.}$$

$$\text{Meter error} = \frac{\text{true value} - \text{indicated value}}{\text{true value}} \tag{20-33}$$

$$= \frac{4.62 - 4.44}{4.62} = \frac{0.18}{4.62} = 0.039 \quad \text{or} \quad 3.9\% \text{ low} \quad \text{Ans.}$$

### WATTMETERS AND WATTHOUR METERS

#### Wattmeter

A wattmeter is an instrument that measures dc power or real ac power. The wattmeter uses fixed coils to indicate current in the circuit, while the movable coil indicates voltage (Fig. 20-21). The coils  $L_{I1}$  and  $L_{I2}$  in series are the fixed coils serving as an ammeter to measure current. The two  $I$  terminals are connected in series with the load. The movable coil  $L_V$  and its multiplier resistance  $R_S$  are used as a voltmeter, with the  $V$  terminals connected across the line in parallel with the load. Then the current in the fixed coils is proportional to  $I$ , while the current in the movable coil is proportional to  $V$ . The deflection of the pointer then is proportional to the  $VI$  product, which is power.

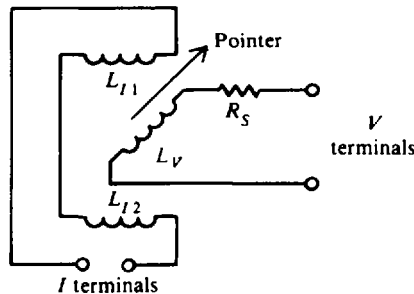


Fig. 20-21 Schematic diagram of a wattmeter

The wattmeter is rated in terms of its maximum current, voltage, and power. Each of these ratings must be observed to prevent damage to the wattmeter.

Power dissipated in a dc circuit is

$$P = VI \quad \text{or} \quad P = I^2R$$

Power dissipated in an ac circuit is

$$P = V_{\text{rms}}I_{\text{rms}} \cos \theta \quad \text{or} \quad P = I^2R \tag{20-34}$$


where  $\theta$  is the phase angle between  $V$  and  $I$ .

**Two-Wattmeter Method**


Since the total power in a 3- $\phi$  circuit is the sum of the powers of the separate phases, the total power could be measured by placing a wattmeter in each phase (Fig. 20-22). This method is not feasible since it is often impossible to break into the phases of a  $\Delta$  load. Nor may it be feasible for the Y load since the neutral point  $N$  to which the wattmeters must be connected is not always accessible. Therefore, only two wattmeters are generally used in making 3- $\phi$  power measurements (Fig. 20-23). In a balanced 3- $\phi$  system of any power factor, the total power measured is

$$P_T = W_A + W_B \tag{20-35}$$

where  $W_A$  and  $W_B$  are the wattage readings of wattmeters  $A$  and  $B$ , respectively. It is important in the two-wattmeter method that the proper sign be given to the wattmeter readings and that the sum be taken algebraically. One method to determine whether a wattmeter reading shall be taken as positive or negative is presented. Disconnect from the common potential point  $C$  (Fig. 20-23) the potential coil of that wattmeter which has the lower reading and connect it to the line containing the current coil of the other wattmeter. If the meter pointer swings down scale, the wattmeter reading is negative.

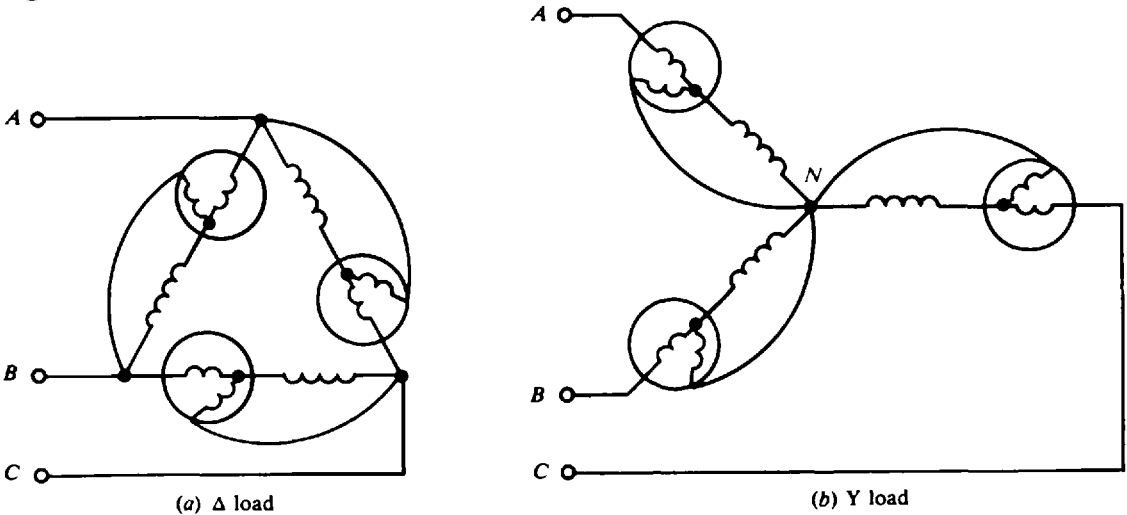

**Fig. 20-22** A wattmeter in each phase may be used to measure 3- $\phi$  power

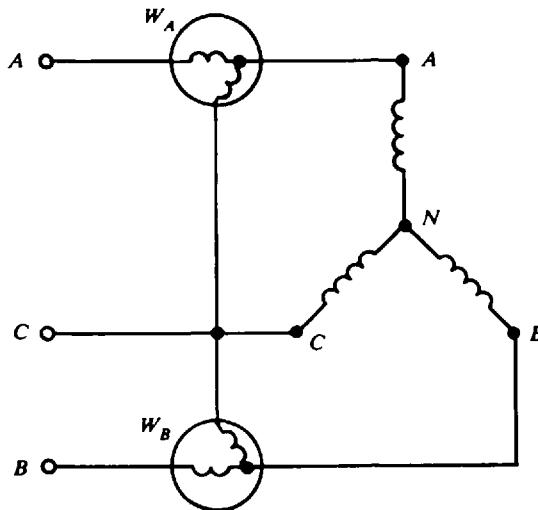


**Fig. 20-23** Connection of two wattmeters to measure 3- $\phi$  power

**Watt-hour Meter**

When the power being dissipated in a load is calculated in terms of time, the amount of energy consumed by the load can be found. The unit commonly used for electric energy calculation is the kilowatt-hour (kWh). It is the product of kilowatts and hours. For example,

$$1 \text{ kWh} = 1000 \text{ W} \times 1 \text{ h} = 200 \text{ W} \times 5 \text{ h} = 1 \text{ W} \times 1000 \text{ h} = 500 \text{ W} \times 2 \text{ h}$$

The most common energy-measuring device is the watt-hour meter (Fig. 20-24). The speed of the rotating aluminum disk (rotor of an ac motor) is determined by the magnetic fields set up by the current and voltage coils. The greater the power passing through the meter, the faster the disk turns. The number of turns is a measure of the energy consumed by the load. The shaft on which the disk is mounted is geared to a group of indicators with clocklike faces. By reading the values on their faces at different times, you can determine how much energy passed through the meter during the interval between readings.

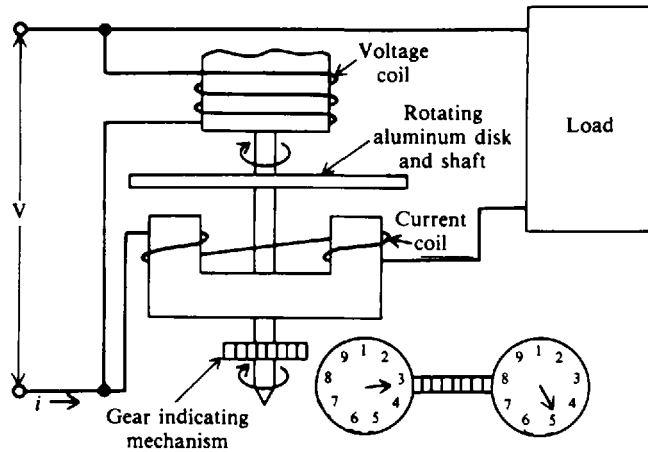

**Fig. 20-24** Typical watt-hour meter

**Example 20.19** The voltage and current being supplied to a load are sinusoidal waveforms whose peak values are 162 V and 5 A. The phase angle between them is 30°. What is the reading of the wattmeter?

$$V_{rms} = \frac{V_P}{\sqrt{2}} = \frac{162}{\sqrt{2}} = 115 \text{ V} \quad I_{rms} = \frac{I_P}{\sqrt{2}} = \frac{5}{\sqrt{2}} = 3.54 \text{ A}$$

$$\cos \theta = \cos 30^\circ = 0.866$$

$$P = V_{rms} I_{rms} \cos \theta \tag{20-34}$$

$$= 115(3.54)(0.866) = 353 \text{ W} \quad \text{Ans.}$$

**Example 20.20** In a circuit (Fig. 20-23),  $W_A$  reads 800 W and  $W_B$  reads 400 W. When the potential coil of  $W_B$  is disconnected at C and connected at A, the needle moves down the scale. What is the total ac power consumed by the 3- $\phi$  load?

The test indicates that the  $W_B$  reading is -400 W. Use Eq. (20-35).

$$P_T = W_A + W_B = 800 - 400 = 400 \text{ W} \quad \text{Ans.}$$

**ANALOG ELECTRONIC METERS**

Electronic meters belonging to the analog class consist of an amplifier connected to a D'Arsonval meter movement. In a meter designed to measure dc quantities, the amplifier receives the signal being measured, amplifies it, and feeds it to the D'Arsonval movement (Fig. 20-25a). The D'Arsonval movement converts the amplified signal to a reading by causing a pointer to move

along a calibrated scale. If the meter is designed to measure ac quantities, a rectifier is connected into the circuit along with the amplifier and D'Arsonval movement (Fig. 20-25b). The amplifier circuits use transistors and are known as TVMs (transistor voltmeters) or FETVMs (field-effect transistor voltmeters).

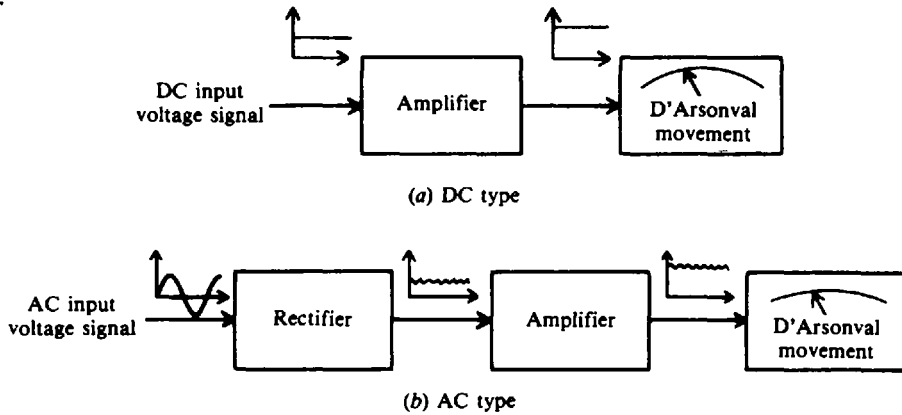


Fig. 20-25 Block diagram of electronic analog meters

**Example 20.21** A basic transistor voltmeter circuit has a base-current input  $I = 100 \mu\text{A}$ , which produces full-scale deflection of the 1-mA meter movement (Fig. 20-26a). Resistors  $R_1$ ,  $R_2$ , and  $R_3$  provide dc voltage ranges of 1, 3, and 10 V. The base-emitter junction of the transistor has a resistance of  $1000 \Omega$ , shown as  $R_O$  (Fig. 20-26b). The input resistance changes on each position of the range switch in the same manner as for a VOM. Calculate the values of  $R_1$ ,  $R_2$ , and  $R_3$  and the sensitivity of the TVM at each voltage range.

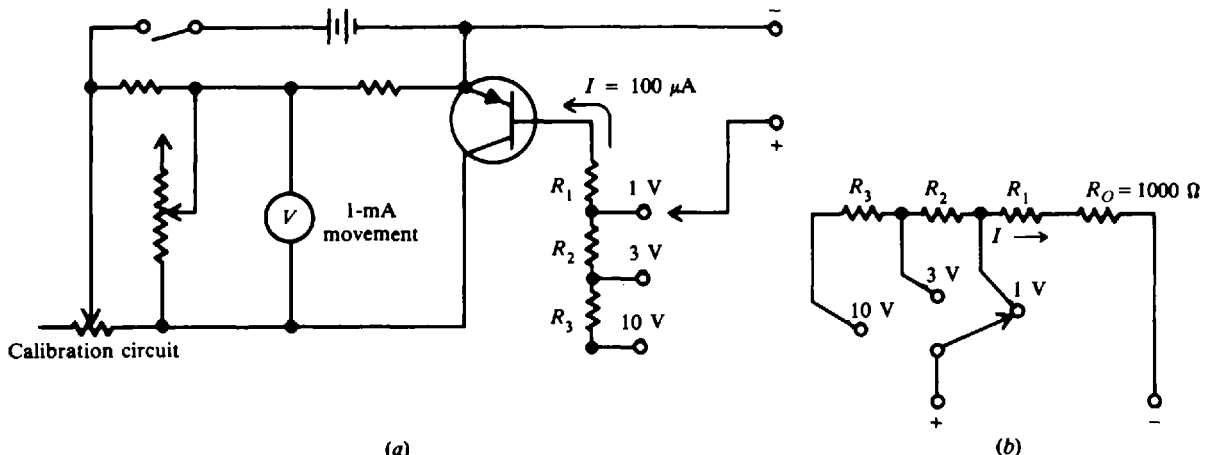


Fig. 20-26 Basic TVM configuration

Refer to the equivalent resistive network (Fig. 20-26b). Use Ohm's law.

1-V range:

$$I = \frac{V}{R_1 + R_O}$$

$$100 \times 10^{-6} = \frac{1}{R_1 + 1000}$$

$$10^{-4} = \frac{1}{R_1 + 10^3}$$

$$10^{-4}R_1 + 10^{-1} = 1$$

$$10^{-4}R_1 = 0.9$$

$$R_1 = \frac{0.9}{10^{-4}} = 9000 \Omega \quad \text{Ans.}$$

The total input resistance in the 1-V range is  $R_O + R_1 = 10\,000\ \Omega$ . Thus

$$\text{Sensitivity} = 10\,000\ \Omega/\text{V} \quad \text{Ans.}$$

3-V range:

$$I = \frac{V}{R_2 + R_1 + R_O}$$

$$100 \times 10^{-6} = \frac{3}{R_2 + 9000 + 1000}$$

$$10^{-4} = \frac{3}{R_2 + 10^4}$$

$$R_2 = \frac{2}{10^{-4}} = 20\,000\ \Omega \quad \text{Ans.}$$

$$\text{Sensitivity} = \frac{20\,000\ \Omega}{3\ \text{V} - 1\ \text{V}} = \frac{20\,000}{2} = 10\,000\ \Omega/\text{V} \quad \text{Ans.}$$

10-V range:

$$I = \frac{V}{R_3 + R_2 + R_1 + R_O}$$

$$100 \times 10^{-6} = \frac{10}{R_3 + 20\,000 + 9000 + 1000}$$

$$10^{-4} = \frac{10}{R_3 + 3 \times 10^4}$$

$$R_3 = \frac{7}{10^{-4}} = 70\,000\ \Omega \quad \text{Ans.}$$

$$\text{Sensitivity} = \frac{70\,000\ \Omega}{10\ \text{V} - 3\ \text{V}} = \frac{70\,000}{7} = 10\,000\ \Omega/\text{V} \quad \text{Ans.}$$

## DIGITAL METERS

A digital voltmeter (DVM) is an instrument that displays a measured dc voltage in discrete numerals, such as +10.93 V. A decimal-point placement is included so that the exact value is evident. In some models, a plus or minus sign appears to the left of the numbers to indicate the polarity of the voltage being measured. The conventional meter with a pointer is an analog meter because its deflection corresponds directly to the measured quantity. Digital readout has several advantages over analog display: There are no observational errors such as parallax and estimation; there are fewer range scales; and it allows faster reading of numerical values, greater accuracy, and capability of feeding output directly to recorders for processing by digital computers.

The display of +10.93 consists of four digits, which means that the maximum display number is 9999. It is possible to provide an additional digit in front of the above four. This added digit can be either unlighted (no reading) or a 1, and is referred to as  $\frac{1}{2}$  digit. Thus the  $\frac{1}{2}$  digit can increase the above reading from 9999 to 19 999, or practically double the original reading. For example, a 1-V range could now read 1.9999, or a 1000-V range could now read 19 999. When the  $\frac{1}{2}$  digit is added to a 4-digit display, it is called a  $4\frac{1}{2}$ -digit display. The display generally uses light-emitting diodes (LEDs).

### Specifications

Common types of specifications relate to sensitivity, resolution, and accuracy. *Sensitivity* is the capability of the DVM to respond to the smallest changes of measured voltage. A rule of thumb is that the sensitivity is approximately equal to the least significant digit (extreme right-hand digit) of the reading. For example, if we are reading +10.93 V, the sensitivity would be 0.03 V. *Resolution* is the ability of a display to resolve one digit out of the the total number capable of being displayed. For example, in a four-digit display, the largest number which can be



displayed is 9999 (for practical purposes, 10 000). Since the display can resolve 1 digit (least significant) out of 10 000, the resolution is 1 part in 10 000, or 0.01 percent. Accuracy is expressed in two parts: the first part is a percentage of the actual reading; the second part, a percentage of the full-scale reading or a number of digits (least significant digit).

**Example 20.22** 5.000 V is measured with a 4-digit DVM whose accuracy is  $\pm 0.01$  percent of reading,  $\pm 1$  digit. What is the maximum error of the DVM reading?

A 4-digit resolution for this display means that 1-digit accuracy is 0.001. So

$$\text{Error} = \pm 0.0001(5 \text{ V}) \pm 0.001 \text{ V}$$

$$\text{Maximum error} = 0.0001(5 \text{ V}) + 0.001 \text{ V} = \pm 0.0015 \text{ V} \quad \text{Ans.}$$

Error is calculated to one more significant digit than the total number of digits displayed.

**Example 20.23** A multipurpose DVM can be designed to measure resistance. It displays 685  $\Omega$ . Its accuracy is  $\pm 0.15$  percent of the reading,  $+0.1$  percent of full scale. What is the maximum error of this reading?

Full scale for this meter reading is 1000  $\Omega$ . So

$$\text{Maximum error} = 0.0015(685 \Omega) + 0.001(1000 \Omega) = 1.0 + 1.0 = \pm 2.0 \Omega \quad \text{Ans.}$$

Therefore, the true value of resistance may be between 683 and 687  $\Omega$ .

## Solved Problems

**20.1** Find the true current  $I_O$  and the current  $I_w$  that the ammeter reads when connected (Fig. 20-27).

Use Eq. (20-1) to find  $I_O$ .

$$I_O = \frac{V}{R_O} = \frac{2}{1000} = 2 \times 10^{-3} = 2 \text{ mA} \quad \text{Ans.}$$

$$K_A = \frac{I_w}{I_O} \quad (20-3)$$

from which 
$$I_w = K_A I_O = \frac{R_O}{R_O + R_M} I_O = \frac{1000}{1050} (2 \times 10^{-3}) = 1.90 \times 10^{-3} = 1.90 \text{ mA} \quad \text{Ans.}$$

**20.2** What approximate value of ammeter resistance (Fig. 20-27) is required to produce a 99 percent accurate reading?

Accuracy is  $K_A$ , and

$$K_A = \frac{R_O}{R_O + R_M} \quad (20-4)$$

$$0.99 = \frac{1000}{1000 + R_M}$$

$$R_M = \frac{1000 - 990}{0.99} = \frac{10}{0.99} = 10 \Omega \quad \text{Ans.}$$

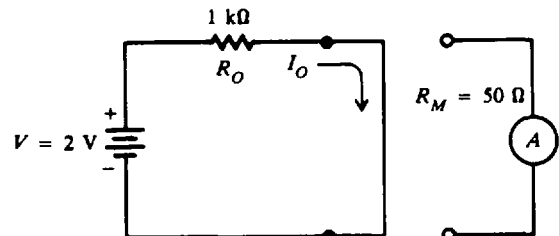


Fig. 20-27 Ammeter measurement

20.3 We wish to measure the true current  $I_O$  through the 500- $\Omega$  resistor (Fig. 20-28). Terminal  $ab$  is opened and then the ammeter is placed in series with the 500- $\Omega$  resistor. Once this is done the current through the 500- $\Omega$  resistor is reduced to a new value  $I_w$ . Calculate  $I_O$ ,  $K_A$ , and  $I_w$ .

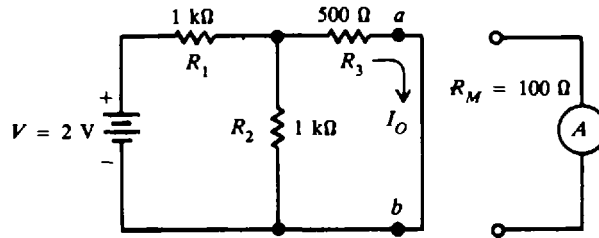


Fig. 20-28 Measuring current in a resistive network

Step 1. Find  $I_O$ .  $R_1$  is in series with the two parallel resistors  $R_2$  and  $R_3$ .

$$R_{eq} = R_1 + \frac{R_2 R_3}{R_2 + R_3} = 1000 + \frac{1000(500)}{1500} = 1333 \Omega$$

$$I_T = \frac{V}{R_{eq}} = \frac{2}{1333} = 1.5 \times 10^{-3} = 1.5 \text{ mA}$$

$I_O$  is the current through  $R_3$ , 500- $\Omega$  resistor.

$$I_O = \frac{R_2}{R_2 + R_3} I_T = \frac{1000}{1500} (1.5) = 1 \text{ mA} \quad \text{Ans.}$$

Step 2. Find  $K_A$ . First, we must find  $R_O$ , the Thevenin resistance (Chap. 8) looking back into terminals  $a$  and  $b$ .  $R_O$  is the 500  $\Omega$  plus the value of the two 1-k $\Omega$  resistors in parallel.

$$R_O = R_3 + \frac{R_1 R_2}{R_1 + R_2} = 500 + \frac{1000(1000)}{(2000)} = 1000 \Omega$$

To find  $K_A$ , use Eq. (20-4).

$$K_A = \frac{R_O}{R_O + R_M} = \frac{1000}{1000 + 100} = \frac{1000}{1100} = 0.909 \quad \text{or} \quad 90.9\% \quad \text{Ans.}$$

Step 3. Find  $I_w$ .

$$I_w = K_A I_O = 0.909(1) = 0.91 \text{ mA} \quad \text{Ans.}$$

The current that is actually measured is 91 percent of the true current in the original circuit. The true current is 1 mA. When the meter is connected, the measured current is 0.91 mA.

20.4 The size of  $R_M$  compared with  $R_O$  determines the accuracy of the reading of an ammeter. Find the value of  $R_O$  with respect to  $R_M$  to ensure a 99 percent accuracy.

$$K_A = \frac{R_O}{R_O + R_M} = 0.99 \tag{20-4}$$

Solve explicitly for  $R_O$ .

$$R_O = 0.99 R_O + 0.99 R_M$$

$$R_O - 0.99 R_O = 0.99 R_M$$

$$0.01 R_O = 0.99 R_M$$

$$R_O = \frac{0.99}{0.01} R_M = 99 R_M$$

$R_O$  must be equal to or greater than  $99R_M$ . A practical rule to remember for at least 99 percent accuracy is  $R_O \geq 100R_M$ .

**20.5** An ammeter with a meter resistance of  $1000 \Omega$  and a full-scale current of  $100 \mu A$  is shunted (Fig. 20-29). The various current ranges are 1, 10, and 100 mA. Find the input resistance of the shunted ammeter in each range.

$$R'_M = \frac{I_M R_M}{I_T} \tag{20-10}$$

1-mA range:  $R'_M = \frac{(100 \times 10^{-6})(1 \times 10^3)}{1 \times 10^{-3}} = 100 \Omega$      *Ans.*

10-mA range:  $R'_M = \frac{1}{10}(100 \Omega) = 10 \Omega$      *Ans.*

100-mA range:  $R'_M = \frac{1}{100}(100 \Omega) = 1 \Omega$      *Ans.*

Note that this circuit (Fig. 20-29) has a serious deficiency because as we switch from one range to another, the switch is momentarily open. For example, if the switch is in the 100-mA position and the current reading is around 10 mA, we would switch to the lower reading. As we switch to the 10-mA range, the ammeter is momentarily unshunted so that the entire 10 mA passes through the  $100\text{-}\mu A$  movement. This may burn out the meter movement.

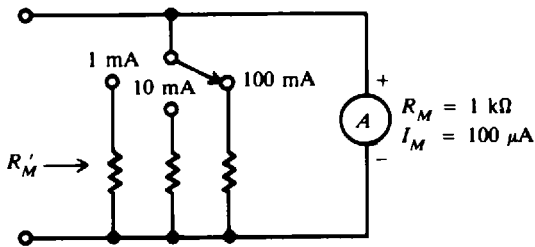


Fig. 20-29 Multirange ammeter

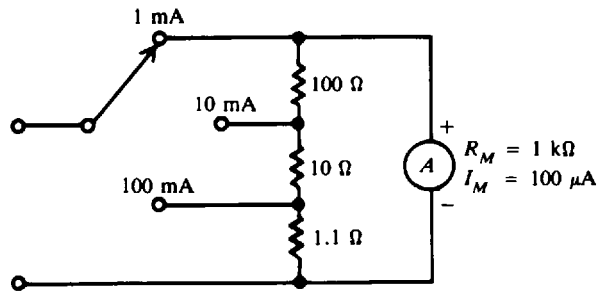


Fig. 20-30 Ayrton shunt

**20.6** To avoid having an unshunted meter during switching, as described by Prob. 20.5, an *Ayrton shunt* may be used (Fig. 20-30). No matter what the switch position is, the meter movement is always shunted. Show that the total current capacity is 1, 10, and 100 mA as indicated.

Find the correct values for  $R_{SH}$  and then compare them with those indicated (Fig. 20-30).

$$R_{SH} = \frac{I_M R_M}{I_T - I_M} \tag{20-8}$$

1-mA range:

$$R_{SH} = \frac{(100 \times 10^{-6})(1 \times 10^3)}{1 \times 10^{-3} - 100 \times 10^{-6}} = \frac{10^{-1}}{10 \times 10^{-4} - 1 \times 10^{-4}} = \frac{10^{-1}}{9 \times 10^{-4}} = 111.1 \Omega$$

The value of  $111.1 \Omega$  agrees with that shown:

$$100 + 10 + 1.1 = 111.1 \Omega \quad \text{Ans.}$$

10-mA range:

Note the  $100\text{-}\Omega$  resistance is now in series with the  $1000\text{-}\Omega$  meter resistance to give  $1100 \Omega$  for the total resistance in that branch.

$$R_M = 1000 + 100 = 1100 \Omega$$

$$R_{SH} = \frac{(100 \times 10^{-6})(1.1 \times 10^3)}{10 \times 10^{-3} - 100 \times 10^{-6}} = \frac{1.1 \times 10^{-1}}{100 \times 10^{-4} - 1 \times 10^{-4}} = \frac{1.1 \times 10^{-1}}{99 \times 10^{-4}} = 11.1 \Omega$$

The value of 11.1 Ω agrees with that shown:

$$10 + 1.1 = 11.1 \Omega \quad \text{Ans.}$$

100-mA range: At this range 10 Ω, 100 Ω, and the meter resistance, 1000 Ω are in series.

$$R_M = 1000 + 100 + 10 = 1110 \Omega$$

$$R_{SH} = \frac{(100 \times 10^{-6})(1.11 \times 10^3)}{100 \times 10^{-3} - 100 \times 10^{-6}} = \frac{1.1 \times 10^{-1}}{1000 \times 10^{-4} - 1 \times 10^{-4}} \frac{1.11 \times 10^{-1}}{999 \times 10^{-4}} = 1.1 \Omega$$

The value of 1.1 Ω agrees with that indicated.

20.7 What is the half-scale current of an ammeter with a sensitivity of 10 kΩ/V?

$$S = \frac{1}{I_M} \tag{20-14}$$

$$I_M = \frac{1}{S} = \frac{1}{10 \times 10^3} = 0.1 \times 10^{-3} = 0.1 \text{ mA}$$

If 0.1 mA represents full-scale current, then half-scale current is

$$\frac{1}{2}(0.1) = 0.05 \text{ mA} \quad \text{or} \quad 50 \mu\text{A} \quad \text{Ans.}$$

20.8 Find the voltmeter reading in the 50-V range and in the 100-V range (Fig. 20-31).

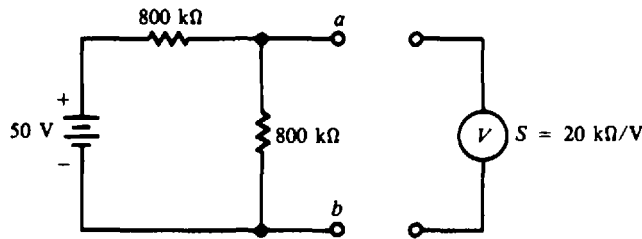


Fig. 20-31 Finding voltmeter reading

Find true voltage across terminals *ab*.

$$V_O = \frac{800 \text{ k}\Omega}{1600 \text{ k}\Omega} (50 \text{ V}) = 25 \text{ V}$$

Find equivalent resistance, looking into terminals *ab*.

$$R_O = \frac{(800 \text{ k}\Omega)(800 \text{ k}\Omega)}{800 \text{ k}\Omega + 800 \text{ k}\Omega} = 400 \text{ k}\Omega$$

50-V range:

$$\begin{aligned} R_{in} &= SV \\ &= \frac{20 \text{ k}\Omega}{V} (50 \text{ V}) = 1 \text{ M}\Omega \end{aligned} \tag{20-15}$$


$$\begin{aligned} V_w &= \frac{R_{in}}{R_O + R_{in}} V_O \\ &= \frac{1 \times 10^6}{400 \times 10^3 + 1 \times 10^6} (25) = \frac{1}{1.4} 25 = 17.9 \text{ V} \quad \text{Ans.} \end{aligned} \tag{20-16}$$

100-V range:

$$\begin{aligned} R_{in} &= \frac{20 \text{ k}\Omega}{V} (100 \text{ V}) = 2 \text{ M}\Omega \\ V_w &= \frac{2 \times 10^6}{400 \times 10^3 + 2 \times 10^6} (25) = \frac{2}{2.4} 25 = 20.8 \text{ V} \quad \text{Ans.} \end{aligned}$$

We have obtained two different readings. Both readings are incorrect since the true voltage across  $ab$  is 25 V. When we obtain different voltage readings as we change ranges, we immediately know that the voltmeter is loading the circuit excessively and hence the readings are erroneous. Conversely, if we change ranges without obtaining different readings, we can assume that the loading is negligible.

- 20.9** We desire to measure the voltage across the 10-k $\Omega$  resistor (Fig. 20-32). We have two voltmeters,  $A$  and  $B$ , to measure this voltage. Voltmeter  $A$  has a sensitivity of 1 k $\Omega$ /V and voltmeter  $B$  has a sensitivity of 20 k $\Omega$ /V. Both use their 50-V scales. Find the reading and accuracy of each meter.

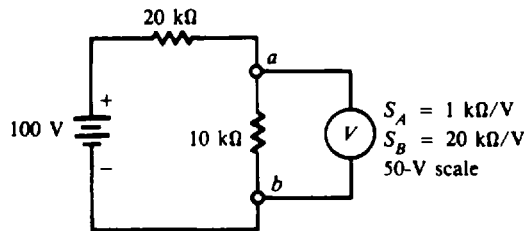

**Fig. 20-32** Finding voltmeter accuracy

$$\text{True voltage } V_O = \frac{10 \text{ k}\Omega}{10 \text{ k}\Omega + 20 \text{ k}\Omega}(100 \text{ V}) = 33.3 \text{ V}$$

$$\text{Equivalent resistance } R_O = \frac{(10 \text{ k}\Omega)(20 \text{ k}\Omega)}{10 \text{ k}\Omega + 20 \text{ k}\Omega} = 6.67 \text{ k}\Omega$$

$$\text{Voltmeter A: } R_{in} = S_A V = \frac{1 \text{ k}\Omega}{\text{V}}(50 \text{ V}) = 50 \text{ k}\Omega$$

$$V_w = \frac{R_{in}}{R_O + R_{in}} V_O \quad (20-16)$$

$$= \frac{50 \times 10^3}{6.67 \times 10^3 + 50 \times 10^3}(33.3) = \frac{50}{56.7}(33.3) = 29.4 \text{ V} \quad \text{Ans.}$$

$$K_v = \frac{V_w}{V_O} = \frac{29.4}{33.3} = 0.883 \quad \text{or} \quad 88.3\% \quad \text{Ans.}$$

$$\text{Voltmeter B: } R_{in} = S_B V = \frac{20 \text{ k}\Omega}{\text{V}}(50 \text{ V}) = 1 \text{ M}\Omega$$

$$V_w = \frac{1 \times 10^6}{6.67 \times 10^3 + 1 \times 10^6}(33.3) = \frac{1}{1.007}33.3 = 33.1 \text{ V} \quad \text{Ans.}$$

$$K_v = \frac{V_w}{V_O} = \frac{33.1}{33.3} = 0.994 \quad \text{or} \quad 99.4\%, \text{ very accurate} \quad \text{Ans.}$$

This problem shows that the meter with the highest sensitivity will yield the most accurate reading in terms of the possible loading error. As a rule of thumb, to reduce the loading error of the voltmeter reading to less than 1 percent, the input resistance of the voltmeter should be at least 100 times higher than the resistance of the path across which the voltage is being measured, or  $R_{in} > 100R_O$ . A similar rule holds for the ammeter reading (Prob. 20.4).

- 20.10** A dc voltmeter connected to terminals  $ab$  reads 5 V on the 5-V range (Fig. 20-33). What is the value of the battery voltage?

First, we find the true voltage  $V_O = V_{ab}$  and then  $V_B$ .

$$\text{Equivalent resistance } R_O = \frac{(60 \text{ k}\Omega)(30 \text{ k}\Omega)}{60 \text{ k}\Omega + 30 \text{ k}\Omega} = 20 \text{ k}\Omega \quad R_{in} = S V = \frac{20 \text{ k}\Omega}{\text{V}}(5 \text{ V}) = 100 \text{ k}\Omega$$

$$V_w = \frac{R_{in}}{R_o + R_{in}} V_o \tag{20-16}$$

from which,  $V_o = \frac{R_o + R_{in}}{R_{in}} V_w = \frac{20 \times 10^3 + 100 \times 10^3}{100 \times 10^3} (5) = 1.2(5)$

$$V_{ab} = V_o = 6 \text{ V}$$

$$I = \frac{V_{ab}}{60 \text{ k}\Omega} = \frac{6}{60 \times 10^3} = 0.1 \times 10^{-3} = 0.1 \text{ mA}$$

$$V_B = I(30 \text{ k}\Omega + 60 \text{ k}\Omega) = (0.1 \times 10^{-3})(90 \times 10^3) = 9 \text{ V} \quad \text{Ans.}$$

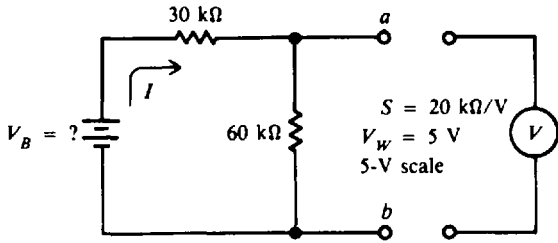


Fig. 20-33 Calculating source voltage

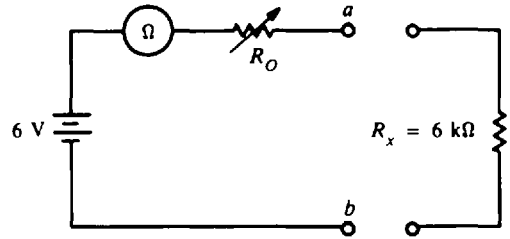


Fig. 20-34 Finding ohmmeter reading

**20.11** The meter movement of an ohmmeter (Fig. 20-34) has a full-scale current of 1 mA. What is the midscale value of ohms? If the battery ages down to 5 V, what will a 6 kΩ-resistor actually read?

Note at midscale ( $D = \frac{1}{2}$ ),

$$R_x = \frac{1 - D}{D} R_o \tag{20-22}$$

$$= \frac{1 - 1/2}{1/2} R_o = R_o$$

$$R_o = \frac{V}{I_M} = \frac{6}{1 \times 10^{-3}} = 6 \text{ k}\Omega \quad \text{Ans.}$$

Thus midscale value is 6 kΩ.

At 5 V with  $R_x = 6 \text{ k}\Omega$  at terminals *ab*,

$$I = \frac{V}{R_o + R_x} \tag{20-19}$$

$$= \frac{5}{6 \times 10^3 + 6 \times 10^3} = \frac{5}{12 \times 10^3} = 0.417 \times 10^{-3} = 0.417 \text{ mA}$$

If we assume a linear scale reading between midscale, 0.500, and 0.417 mA, the ohmmeter reading will be

$$\frac{0.500 \times 10^{-3} \text{ A}}{0.417 \times 10^{-3} \text{ A}} (6 \times 10^3 \Omega) = 7.2 \times 10^3 \Omega = 7.2 \text{ k}\Omega \quad \text{Ans.}$$

**20.12** Prepare a table to show how the meter face of an ohmmeter must be marked in terms of the value of  $R_o$ .

Let  $R_x$  take on the values indicated in the table in order to find the corresponding deflection factor  $D$  by

$$D = \frac{R_o}{R_o + R_x} \tag{20-20}$$

$R_x$	$D$
0	1
$R_O/3$	$\frac{3}{4}$
$R_O$	$\frac{1}{2}$
$3R_O$	$\frac{1}{4}$
$7R_O$	$\frac{1}{8}$
$\infty$	0

Observe the following:

1.  $R_x = 0$  produces a deflection of 1, or full-scale deflection. This makes sense since a zeroed ohmmeter means full-scale current. So  $0 \Omega$  is marked at full scale.
2. For  $R_x = \infty$ , or open circuit, no current can flow, so deflection is zero. Infinity is marked at the zero-current point on the meter face.
3. For  $R_x = R_O$ , half-scale deflection occurs, so  $R_O$  is indicated in the midscale on the meter face. Continuing in this way, the entire meter can be correctly marked to read ohms.
4. A partially marked meter face is shown (Fig. 20-35). The ohms scale increases from right to left. This arrangement is called a *back-off scale*.

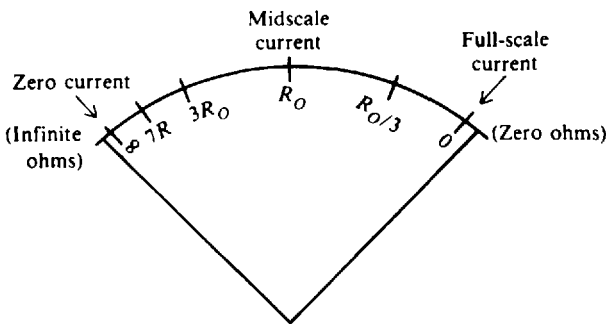


Fig. 20-35 Marking the ohmmeter scale

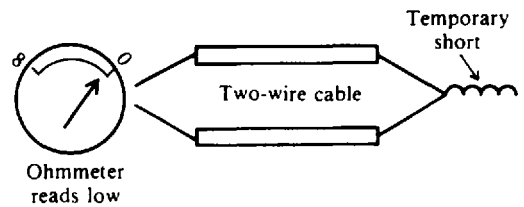


Fig. 20-36 Short-circuit at one end of two-wire line to check continuity from opposite end

**20.13** It is desired to check the continuity of a long two-wire line (Fig. 20-36), but its ends are too far apart for the ohmmeter leads to read. How would you check its continuity?

Short-circuit the ends that are far apart and check the continuity of both wires at the other end (Fig. 20-36). If the wires are long, there may be a readable deflection. If the ohmmeter has a low reading close to zero, the cable is continuous; if it reads close to infinity, the cable is open.

**20.14** A VOM provides six dc voltage ranges (Fig. 20-37). The instrument is switched to its 2.5-V range. The test leads are plugged into the positive and negative terminals. The meter movement ( $M$ ) has an internal resistance of  $2000 \Omega$ . What is the full-scale current and sensitivity of the multimeter?

$$\text{Total resistance} = R_{in} = R_S + R_M$$

At 2.5-V range:

$$R_{in} = 48 \text{ k}\Omega + 2 \text{ k}\Omega = 50 \text{ k}\Omega$$

$$I_M = \frac{V}{R_{in}} = \frac{2.5}{50 \times 10^3} = 0.05 \times 10^{-3} = 50 \mu\text{A} \quad \text{Ans.}$$

$$S = \frac{1}{I_M} = \frac{1}{50 \times 10^{-8}} = 20\,000 = 20 \text{ k}\Omega/\text{V} \quad \text{Ans.}$$

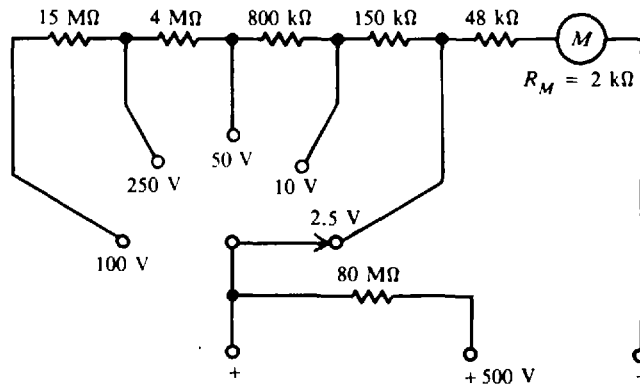


Fig. 20-37 A VOM configuration with six voltage ranges

20.15 Find the full-scale current of the VOM (Fig. 20-37) when the switch is at 250-V range.

$$R_{in} = R_S + R_M$$

At 250-V range:  $R_{in} = (4 \times 10^6 + 800 \times 10^3 + 150 \times 10^3 + 48 \times 10^3) + 2 \times 10^3 = 5000 \times 10^3 = 5 \text{ M}\Omega$

$$I_M = \frac{V}{R_{in}} = \frac{250}{5 \times 10^6} = 50 \times 10^{-6} = 50 \mu\text{A} \quad \text{Ans.}$$

The instrument circuit draws 50 μA at full-scale indication for each voltage range of 2.5 and 250 V.

20.16 If the circuit (Fig. 20-38) is to have full-scale deflection for an input sine wave of 50 V rms, what size should  $R_S$  be? The meter movement has  $I_M = 50 \mu\text{A}$  and meter resistance  $R_M = 2 \text{ k}\Omega$ .

$$V_{rms} = 2.22(R_S + R_M)I_{av}$$

from which  $R_S = 0.45\left(\frac{V_{rms}}{I_{av}}\right) - R_M = 0.45\left(\frac{50}{50 \times 10^{-6}}\right) - 2 \times 10^3 = 448 \times 10^3 = 448 \text{ k}\Omega \quad \text{Ans.}$

An approximation with  $R_M \ll R_S$  is

$$V_{rms} \cong 2.22 R_S I_{av} \tag{20-27}$$

from which  $R_S \cong 0.45\left(\frac{V_{rms}}{I_{av}}\right) \cong 0.45\left(\frac{50}{50 \times 10^{-6}}\right) \cong 0.45 \times 10^6 \cong 450 \text{ k}\Omega \quad \text{Ans.}$

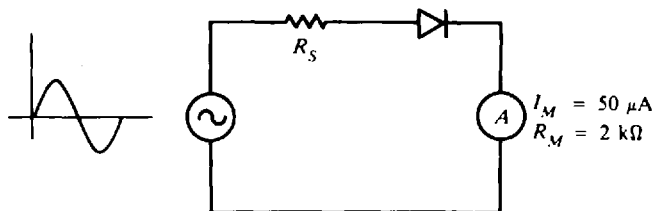


Fig. 20-38 Simple ac voltmeter with half-wave detector

20.17 A simple dc voltmeter uses a meter movement with a full-scale current of 50 μA and a meter resistance of 2 kΩ. By means of a switching arrangement, the same meter movement can be connected to the output of a simple half-wave rectifier. Find the value of the multiplier resistance that is used on the 100-V dc range and on the 100-V rms range.



DC voltmeter [use Eq. (20-12)]:

$$R_S = \frac{V}{I_M} - R_M = \frac{100}{50 \times 10^{-6}} - 2 \times 10^3 = 2 \times 10^6 - 2 \times 10^3 \cong 2 \text{ M}\Omega \quad \text{Ans.}$$

AC voltmeter:

$$R_S \cong 0.45 \left( \frac{V_{rms}}{I_{av}} \right) \cong 0.45 \left( \frac{100}{50 \times 10^{-6}} \right) \cong 0.9 \times 10^6 \cong 900 \text{ k}\Omega \quad \text{Ans.}$$

Note that the input resistance is approximately equal to  $R_S$ . On the 100-V dc range,  $R_S = 2 \text{ M}\Omega$ ; while on the 100-V ac range,  $R_S = 900 \text{ k}\Omega$ . This reduction in input resistance is typical for all rectifier types of ac voltmeters.

- 20.18** A VOM on the 10-V range is used to measure the voltage of the circuit (Fig. 20-39). Find the accuracy as far as the loading effects are concerned for dc and ac voltage measurements.

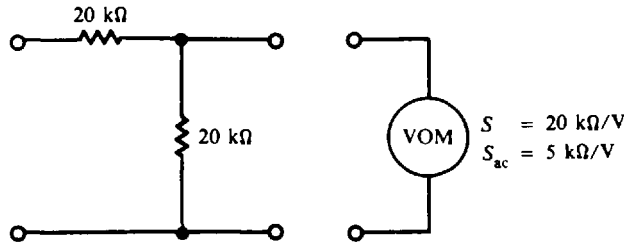


Fig. 20-39 Measuring voltage by VOM

DC measurement:

$$\text{Accuracy} = K_V = \frac{V_w}{V_O} = \frac{R_{in}}{R_O + R_{in}} \quad (20-17)$$

$$\begin{aligned} R_{in} &= SV \\ &= (20 \times 10^3)(10) = 200 \text{ k}\Omega \end{aligned} \quad (20-15)$$

$R_O$  is the equivalent resistance of the two 20-k $\Omega$  resistors in parallel.

$$R_O = \frac{20(20)}{20 + 20} = 10 \text{ k}\Omega$$

$$K_V = \frac{200 \times 10^3}{10 \times 10^3 + 200 \times 10^3} = 0.952 \quad \text{or } 95.2\% \quad \text{accuracy} \quad \text{Ans.}$$

AC measurement:

$$\begin{aligned} R_{in} &= S_{ac} V_M \\ &= 5(10) = 50 \text{ k}\Omega \end{aligned} \quad (20-30)$$

$$R_O = 10 \text{ k}\Omega \quad (\text{same calculation as before})$$

$$K_V = \frac{50 \times 10^3}{10 \times 10^3 + 50 \times 10^3} = 0.833 \quad \text{or } 83.3\% \text{ accuracy} \quad \text{Ans.}$$

More loading error can be expected for ac measurements than for dc measurements.

- 20.19** A VOM uses a 50- $\mu\text{A}$ , 2-k $\Omega$  meter movement. On dc voltage ranges a full-wave detector is used. Also, the ammeter is shunted by 2 k $\Omega$  on ac ranges. What are the dc and ac sensitivities of the VOM?

DC measurement:

$$\begin{aligned} S &= \frac{1}{I_M} \\ &= \frac{1}{50 \times 10^{-6}} = 0.02 \times 10^6 = 20 \text{ k}\Omega/\text{V} \end{aligned} \quad (20-14) \quad \text{Ans.}$$

AC measurement:

$$S_{ac} = \frac{0.90}{I_M} \tag{20-32}$$

At full-scale deflection, the meter and shunt will each draw  $50 \mu A$ .

$$I_M = 50 \mu A + 50 \mu A = 100 \mu A$$

$$S_{ac} = \frac{0.90}{100 \times 10^{-6}} = 0.9 \times 10^4 = 9 \text{ k}\Omega/\text{V} \quad \text{Ans.}$$

The sensitivity has been considerably reduced in the ac measurements.

**20.20** An ac meter uses an unshunted  $50\text{-}\mu A$  movement. Find the input resistance on the 5-, 50-, and 500-V rms ranges if a half-wave detector is used.

$$S_{ac} = \frac{0.45}{I_M} \tag{20-29}$$

$$= \frac{0.45}{50 \times 10^{-6}} = 0.9 \times 10^4 = 9 \text{ k}\Omega/\text{V}$$

$$R_{in} = S_{ac} V_M \tag{20-30}$$

5-V range:  $R_{in} = 9(5) = 45 \text{ k}\Omega \quad \text{Ans.}$

50-V range:  $R_{in} = 9(50) = 450 \text{ k}\Omega \quad \text{Ans.}$

500-V range:  $R_{in} = 9(500) = 4.5 \text{ M}\Omega \quad \text{Ans.}$

**20.21** If a thermocouple ammeter reads 5 A at full scale, what will be the current passing through the meter when the meter deflection is one-half of full scale?

Since the heating effect is proportional to  $i^2R$ , the resulting current which activates the D'Arsonval movement gives a true rms reading. Thus deflection is proportional to the square of the current, and conversely the current is proportional to the square root of deflection. So

$$I_{rms} = \sqrt{D} I_M = \sqrt{\frac{1}{2}}(5) = 3.54 \text{ A} \quad \text{Ans.}$$

**20.22** A dc voltmeter and ammeter are connected to measure dc power (Fig. 20-40), where  $R_v$  is the resistance of the voltmeter,  $V_L$  is the voltage across the load,  $I_v$  is the current in the voltmeter,  $I_L$  is the current in the load, and  $I_T$  is the current being read by the ammeter. Develop an expression for dc power in terms of  $V_L$ ,  $I_T$ , and  $R_v$ .


$$P = V_L I_L$$

By Kirchhoff's current law,

$$I_L = I_T - I_v = I_T - \frac{V_L}{R_v}$$

Substitute  $I_L$  into the first equation.

$$P = V_L \left( I_T - \frac{V_L}{R_v} \right) = V_L I_T - \frac{V_L^2}{R_v} \quad \text{Ans.}$$

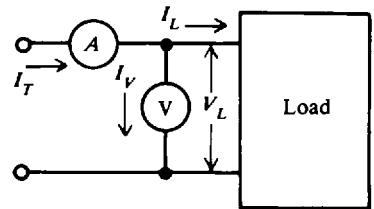

**Fig. 20-40** Meter connections for measuring dc power

This expression shows that useful power  $P$  is equal to the total power consumed by the meter and load minus the power consumed by the meter.

**20.23** A 50-V dc voltmeter with a  $1000 \Omega/\text{V}$  sensitivity, and a 100-mA dc ammeter are connected to measure the power in a load (Fig. 20-40). The voltmeter reads 40 V and the ammeter reads 50 mA. How much power is being dissipated by the load?

Use Eq. (20-15).

$$R_v = R_{in} = SV = (1 \times 10^3)(50) = 50\,000\ \Omega = 50\ \text{k}\Omega$$

$$P = V_L I_T - \frac{V_L^2}{R_v} \quad (\text{See Prob. 20.22})$$

$$= 40(50 \times 10^{-3}) - \frac{40^2}{50 \times 10^3} = 2.00 - 0.032 = 1.97\ \text{W} \quad \text{Ans.}$$

- 20.24** Two wattmeters properly connected to measure 3- $\phi$  power read +1000 and +800 W, respectively. What is the total power supplied?

The total power is the sum of the two readings [Eq. (20-35)].

$$P_T = W_A + W_B = 1000 + 800 = 1800\ \text{W} \quad \text{Ans.}$$

- 20.25** If the cost of electric power is 6 cents per kilowatt-hour, what is the cost of using (a) a 145-W solid-state color television for 4 h, and (b) a 400-W clothes dryer for 1 h 20 min?

- (a) 145 W = 0.145 kW

$$\text{Energy (kWh)} = \text{power (kW)} \times \text{time (h)} = 0.145(4) = 0.58\ \text{kWh}$$


$$\text{Cost} = \text{energy (kWh)} \times \text{unit cost (cents/kWh)} = 0.58(6) = 3.5\ \text{cents} \approx 4\ \text{cents} \quad \text{Ans.}$$

- (b) 400 W = 0.4 kW      1 h 20 min =  $\frac{80}{60} = 1.33\ \text{h}$

$$\text{Energy} = 0.4(1.33) = 0.532\ \text{kWh}$$

$$\text{Cost} = 0.532(6) = 3.2\ \text{cents} \approx 3\ \text{cents} \quad \text{Ans.}$$

- 20.26** A transistorized volt-ohmmeter (TVOM) has a very high input impedance (usually about 20 M $\Omega$ ), which is higher than that of the volt-ohm-milliammeter (VOM). Explain the advantage of having a high input impedance in the measuring circuit by referring to Fig. 20-41.

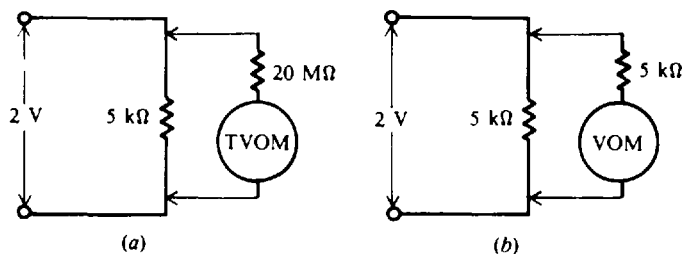

**Fig. 20-41** Importance of a high-impedance voltmeter

A load of 5 k $\Omega$  has 2 V across it. When the TVOM is placed across the load, we have 5 k $\Omega$  and 20 M $\Omega$  in parallel, which is equivalent to 5 k $\Omega$  (Fig. 20-41a). Thus for all practical purposes, the TVOM is an open circuit, and only 5 k $\Omega$  is in the circuit during measurement.

We now measure the voltage across the 5-k $\Omega$  load with a VOM that has only 5 k $\Omega$  resistance (Fig. 20-41b). The two resistances in parallel have a combined resistance of (5 k $\Omega$ )/2, or 2.5 k $\Omega$ . Since the circuit resistance is decreased by the VOM, both the voltage across the resistor and the circuit current are changed during measurement. In general, the higher the input resistance of the measuring device, the more accurate the measurement. (See Prob. 20.9.)

- 20.27** A multipurpose DVM measures dc and ac voltages; 80.00 V is measured with 4-digit resolution. The dc measurement accuracy is  $\pm 0.05$  percent of reading  $\pm 1$  digit, while the ac

measurement accuracy is  $\pm 0.1$  percent of reading  $\pm 2$  digits. Compare the accuracies of the two measurements.

DC measurement:

$$\text{Maximum error} = 0.0005(80 \text{ V}) + 0.01 \text{ V} = 0.04 + 0.01 = \pm 0.05 \text{ V} \quad \text{Ans.}$$

AC measurement:

$$\text{Maximum error} = 0.001(80 \text{ V}) + 0.02 \text{ V} = 0.08 + 0.02 = \pm 0.10 \text{ V} \quad \text{Ans.}$$

Generally the accuracy of ac voltage measurements is lower than that of dc voltage measurements.

### Supplementary Problems

- 20.28** An ammeter with a full-scale deflection of 1 mA has a calibration error of  $\pm 5$  percent of the full-scale current. If the ammeter reads 0.40 mA, what is the possible range in the true current through the ammeter? *Ans.* 0.35 to 0.45 mA
- 20.29** The ammeter has a resistance of  $200 \Omega$  (Fig. 20-42). (a) What does the ammeter read? (b) If the ammeter is ideal (no resistance), what will it read? (c) What is the accuracy of the meter? (d) What is the percent loading error?  
*Ans.* (a) 0.83 mA; (b) 1.0 mA; (c) 0.833 or 83.3%, (d) 16.7%
- 20.30** The ammeter has a resistance of  $50 \Omega$  (Fig. 20-42) and a full-scale current of 1 mA. If the calibration error is  $\pm 3$  percent of the full-scale reading, what is the possible range of ammeter readings?  
*Ans.* 0.922 to 0.982 mA

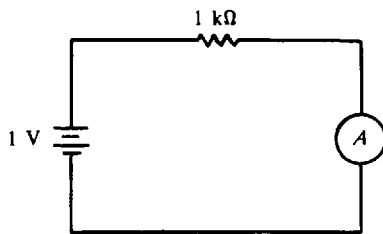


Fig. 20-42

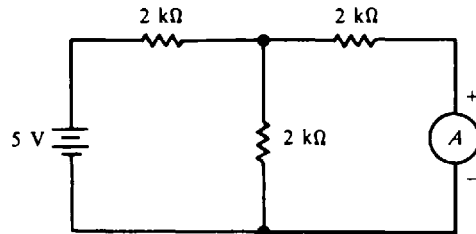


Fig. 20-43

- 20.31** If the ammeter has a resistance of  $100 \Omega$  (Fig. 20-43), what is its accuracy and percent loading error?  
*Ans.* 96.8% ( $R_O = 3 \text{ k}\Omega$ ); 3.2%
- 20.32** If the accuracy is to be greater than 99 percent (Fig. 20-43), what should the ammeter resistance be?  
*Ans.*  $R_M < 30 \Omega$
- 20.33** Show that for a minimum 95 percent accurate reading of an ammeter  $R_O$  should be greater than  $20R_M$ .  
*Ans.*  $K_A = \frac{R_O}{R_O + R_M} = 0.95$ ;  $R_O = 19R_M$  so that  $R_O > 20R_M$  (thumb rule).
- 20.34** Suppose that the Thevenin resistance of a complex resistive network under test is  $20 \text{ k}\Omega$ . What is the highest value of meter resistance permissible if 99 percent accuracy is desired. (See Prob. 20.4).  
*Ans.*  $R_M = 200 \Omega$
- 20.35** What is the value of the shunt resistance needed to convert a  $50\text{-}\mu\text{A}$  meter movement with a  $2\text{-k}\Omega$  internal resistance into a  $100\text{-}\mu\text{A}$  meter? *Ans.*  $R_{SH} = 2 \text{ k}\Omega$

- 20.36 Given a 1-mA meter movement with a resistance of  $50\ \Omega$ , we desire to convert it to an ammeter capable of measuring up to 150 mA. What is the required shunt resistance? *Ans.*  $R_{SH} = 0.336\ \Omega$
- 20.37 A 1-mA ammeter with an internal resistance of  $50\ \Omega$  is to be shunted so as to allow a total current of 1 A. Find the value of shunt resistance and the input resistance of the shunted ammeter.  
*Ans.*  $R_{SH} = 0.05\ \Omega$ ;  $R'_M = 0.05\ \Omega$
- 20.38 An ammeter with a meter resistance of  $2\ \text{k}\Omega$  and full-scale current of  $50\ \mu\text{A}$  is shunted (Fig. 20-44). The various current ranges are 5, 50, and 500 mA. Find the input resistance of the shunted ammeter in each range.  
*Ans.* 5-mA range:  $R'_M = 20\ \Omega$ ; 50-mA range:  $R'_M = 2\ \Omega$ ; 500-mA range:  $R'_M = 0.2\ \Omega$

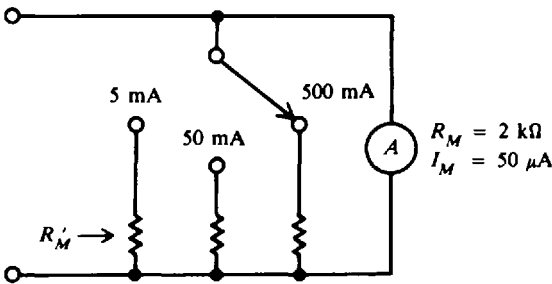


Fig. 20-44

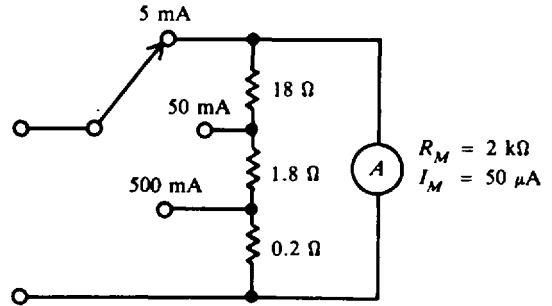


Fig. 20-45

- 20.39 Show that the total current capacity is 5, 50, and 500 mA as indicated for each position of the range switch for the Ayrton shunt circuit (Fig. 20-45). (See Prob. 20.38.)  
*Ans.* Solve Eq. (20-8) for  $I_T$ :  $I_T = \frac{R_M + R_{SH}}{R_{SH}} I_M$ .  
Confirm 5 mA:  $I_T = \left(\frac{2 \times 10^3 + 20}{20}\right) (50 \times 10^{-6}) = 5\ \text{mA}$
- 20.40 Convert a  $50\text{-}\mu\text{A}$  ammeter with  $R_M = 2\ \text{k}\Omega$  to a voltmeter with a full-scale voltage of 100 V.  
*Ans.*  $R_S = 2\ \text{M}\Omega$
- 20.41 A  $50\text{-}\mu\text{A}$  ammeter with a resistance of  $2\ \text{k}\Omega$  is to be converted into a multirange voltmeter with the following ranges: 1, 15, 50, and 150 V (Fig. 20-46). Find the multiplier resistances for each range.  
*Ans.* 1-V range:  $R_{S1} = 18\ \text{k}\Omega$ ; 15-V range:  $R_{S2} = 298\ \text{k}\Omega \cong 300\ \text{k}\Omega$ ; 50-V range:  $R_{S3} = 998\ \text{k}\Omega \cong 1\ \text{M}\Omega$ ; 150-V range:  $R_{S4} = 3\ \text{M}\Omega$

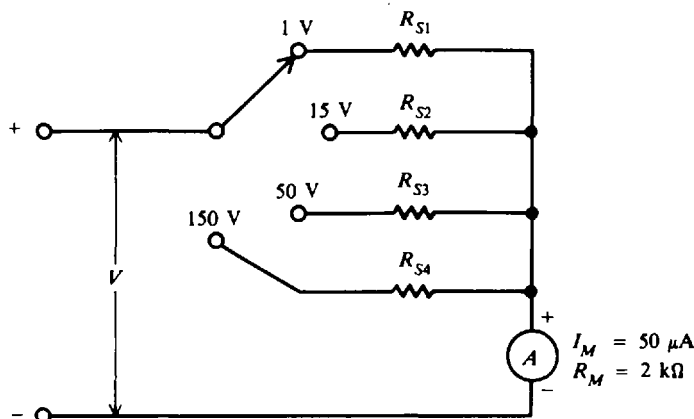


Fig. 20-46

**20.42** Find the values of multiplier resistance needed to provide the following voltage ranges: 1.5, 5, 15, 50, 150, and 500 V. The meter is a  $20\text{-}\mu\text{A}$ ,  $5\text{-k}\Omega$  movement.  
 Ans. 1.5-V range:  $70\text{ k}\Omega$ ; 5-V range:  $245\text{ k}\Omega$ ; 15-V range:  $745\text{ k}\Omega$ ; 50-V range:  $2.5\text{ M}\Omega$ ; 150-V range:  $7.5\text{ M}\Omega$ ; 500-V range:  $25\text{ M}\Omega$

**20.43** A voltmeter with a  $50\text{-}\mu\text{A}$  movement has ranges of 5, 50, and 500 V. What is the meter sensitivity? What is the input resistance on each range?  
 Ans.  $S = 20\text{ k}\Omega/\text{V}$ ; 5-V:  $R_{in} = 100\text{ k}\Omega$ ; 50-V:  $R_{in} = 1\text{ M}\Omega$ ; 500-V:  $R_{in} = 10\text{ M}\Omega$

**20.44** A voltmeter has a sensitivity of  $20\text{ k}\Omega/\text{V}$ . What is its input resistance on the 5-V range? On the 5000-V range?  
 Ans. 5-V:  $R_{in} = 100\text{ k}\Omega$ ; 5000-V:  $R_{in} = 100\text{ M}\Omega$

**20.45** What would the voltmeter read on the following ranges: 50, 15, and 5 V (Fig. 20-47)?  
 Ans. 50-V: 8 V; 15-V: 5.45 V; 5-V: 2.86 V

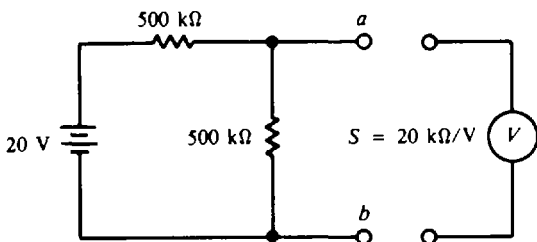


Fig. 20-47

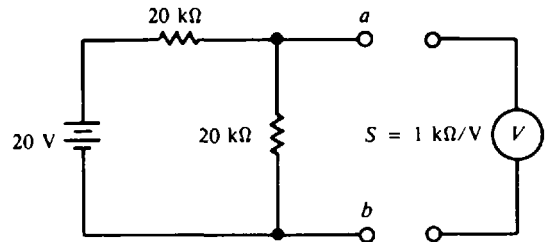


Fig. 20-48

**20.46** A dc voltmeter connected to the  $ab$  terminals reads 5 V (Fig. 20-48). It has the following ranges: 1, 3, 5, 10, 30, 100, and 300 V. What range is the voltmeter on? Ans. 10-V scale

**20.47** In order to measure the voltage across the  $ab$  terminals (Fig. 20-47) with a loading accuracy of 99 percent, what is the minimum voltmeter input resistance permissible? (See Prob. 20.9.)  
 Ans.  $R_{in} = 25\text{ M}\Omega$

**20.48** For the simple ohmmeter (Fig. 20-49), which uses a 1-mA  $50\text{-}\Omega$  meter movement, what is the value of  $R_O$  that produces full-scale current? Ans.  $R_O = 6\text{ k}\Omega$

**20.49** If a  $50\text{-}\mu\text{A}$  movement is used (Fig. 20-49), what value of ohms is marked at midscale? At quarter scale? Ans.  $120\text{ k}\Omega$ ,  $360\text{ }\Omega$

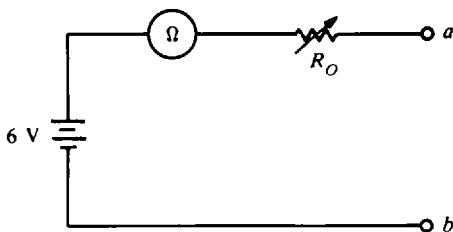


Fig. 20-49

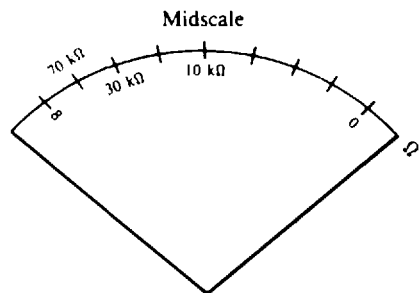


Fig. 20-50

**20.50** An ohmmeter has a 10-V battery and a 1-mA movement. To zero the ohmmeter,  $R_O$  is adjusted to  $10\text{ k}\Omega$  in order to allow a full-scale current of 1 mA to flow. Prepare an ohmic scale for this ohmmeter. Ans. See Fig. 20-50.

- 20.51 If the 10-V battery of Prob. 20.50 ages to 9 V and no further adjustment is made, what will a 10-kΩ resistor actually read? *Ans.* 11.1 kΩ
- 20.52 It is desired to calibrate an ohmmeter (Fig. 20-51).  $R_O$  has been adjusted to produce full-scale deflection. Determine the meter current and deflection for each external resistor  $R_X$ : 0, 750, 1500, 3000, 150 000, and 500 000 Ω.

*Ans.*

mA	Deflection
1	Full scale
0.67	$\frac{2}{3}$ scale
0.5	$\frac{1}{2}$ scale
0.33	$\frac{1}{3}$ scale
0.01	$\frac{1}{100}$ scale
0	None

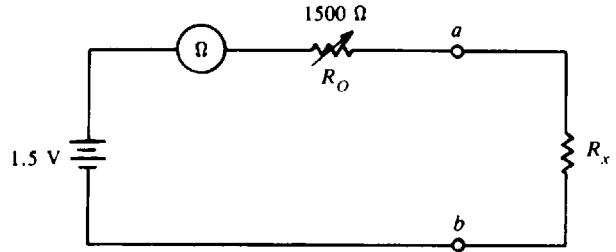


Fig. 20-51

- 20.53 A VOM is capable of measuring dc and ac voltages. As an ac voltmeter, the VOM has a sensitivity of 5000 Ω/V and full-scale ranges of 2.5 to 1000 V. Find the input resistances for these voltage ranges. *Ans.* 12.5 kΩ, 5 MΩ
- 20.54 Verify that the VOM circuit (Fig. 20-37) draws 50 μA at full scale for voltage ranges of 10, 50, 100, and 500 V. (See Probs. 20.14 and 20.15.)  
*Ans.* Example, 10-V range:  $\frac{V}{R_{in}} = \frac{10}{200 \times 10^3} = 50 \mu A$
- 20.55 The current through an ammeter is a half-wave rectified sine wave with a peak value of 25 mA. What is the dc value of this circuit? *Ans.* 7.95 mA
- 20.56 An input sine wave is being measured by an ac meter (Fig. 20-52).  $R_M = 2 \text{ k}\Omega$ ,  $R_S = 48 \text{ k}\Omega$ . If the ammeter reads 30 μA, what is the rms value of the input sine wave? *Ans.* 30 μA
- 20.57 A meter is a 50 μA, 2-kΩ movement (Fig. 20-52). What is the size of  $R_S$  required on the 100-V rms range? *Ans.*  $R_S \cong 900 \text{ k}\Omega$
- 20.58 Calculate the ac sensitivity (Fig. 20-52) if the ammeter has a full-scale deflection current of 50 μA. What are the input resistances of the 5-V, 50-V, and 100-V ranges?  
*Ans.*  $S_{ac} = 9 \text{ k}\Omega/\text{V}$ ; 45 kΩ, 450 kΩ, 900 kΩ

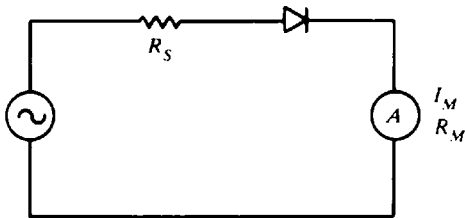


Fig. 20-52

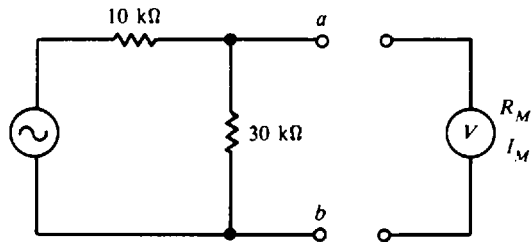


Fig. 20-53

- 20.59 An ac voltmeter on its 10-V range is used to measure the voltage across the 30-kΩ resistor (Fig. 20-53).  $S_{ac} = 5 \text{ k}\Omega/\text{V}$ . If the voltmeter reads 5 V, what is the true voltage across the 30-kΩ resistor without the voltmeter connected? *Ans.* 5.75 V rms

- 20.60** A 100- $\mu$ A movement is shunted so that the total current capacity is 1 mA. What is the ac sensitivity of this shunted ammeter if it uses a half-wave detector? Full-wave detector?  
*Ans.* 450  $\Omega$ /V, 900  $\Omega$ /V
- 20.61** A half-wave rectifier type of ac voltmeter has the usual rms scale based upon the assumption that only sine waves will be measured. If this voltmeter is used to measure a square wave, a false rms reading results. However, if a reading of 100 V is obtained for the square wave, what are: (a) the actual peak value, and (b) the actual rms value of the square wave at the measuring terminals? (c) What is the meter error that results from this square wave measurement?  
*Ans.* (a) 90.1 V peak; (b) 90.1 V rms; (c) 11.1%
- 20.62** A 50- $\mu$ A movement, 2-k $\Omega$  meter resistance is used in a full-wave bridge detector. What should the size of  $R_s$  be for a 50-V rms sine wave to produce full-scale deflection? *Ans.* 900 k $\Omega$
- 20.63** An ac voltmeter has a sensitivity of 5 k $\Omega$ /V. What is the input resistance on the 2.5-V range? If this voltmeter is used to measure the voltage across the 30-k $\Omega$  resistor (Fig. 20-54), what will the voltmeter read on its 2.5-V range if the generator voltage is 4 V rms? What is the percent loading error of the meter? *Ans.*  $R_{in} = 12.5$  k $\Omega$ ; 1.22 V rms; 49.2%

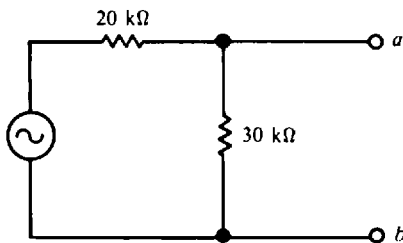


Fig. 20-54

- 20.64** An ac voltmeter uses a full-wave bridge circuit. The meter is a 1-k $\Omega$  100- $\mu$ A movement. What is the input resistance on the 50-V range? *Ans.* 450 k $\Omega$
- 20.65** For the circuit (Fig. 20-54), what size should the input resistance of an ac voltmeter be in order to ensure 99 percent loading accuracy? *Ans.* 1.2 M $\Omega$
- 20.66** An ac voltmeter has a half-wave detector. If 1.5 V dc is applied to the meter, what will the pointer indicate? *Ans.* 3.33 V rms
- 20.67** What will be the reading of a full-wave rectified ac voltmeter if the waveform shown (Fig. 20-55) is applied to the meter? What will be the meter error? *Ans.* 6.97 V rms; 8.67%

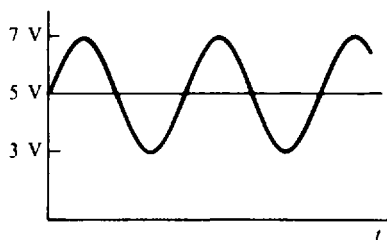


Fig. 20-55



- 20.68 A full-wave rectifier type of ac voltmeter indicates a reading of 6.66 V when measuring the sawtooth wave voltage (Fig. 20-56). Find (a) the true rms value of the waveform and (b) the percent error of the meter. *Ans.* (a) 6.93 V; (b) 3.9%

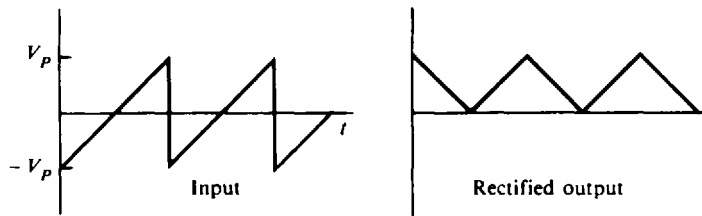


Fig. 20-56

- 20.69 The voltage and current being supplied for a single-phase load are in the form of sine waves with peak amplitudes of 250 V and 3.5 A. The power factor of the load is 0.32. What will the wattmeter connected across the load read? *Ans.* 140 W
- 20.70 A 250-V voltmeter with a 20 000  $\Omega/V$  rating and a 5-A ammeter are used to measure the power being dissipated in a dc circuit. The voltmeter reads 180 V and the ammeter 4.5 A. What is the real power being dissipated by the circuit? *Ans.*  $P = 810$  W
- 20.71 Two wattmeters are used to measure 3- $\phi$  power to a Y load. Wattmeter A reads 1500 W and wattmeter B reads 900 W. When the voltage coil of wattmeter B is disconnected from the common potential point and connected at A, the reading of wattmeter B is "up-scale." What is the total power supplied? If the reading were off the scale, what would be the total power supplied? *Ans.* 2400 W; 600 W
- 20.72 The cost of electric power is 5 cents per kilowatt-hour. What is the cost of using (a) a 1200-W toaster for 30 min; (b) six 150-W flood lamps for 12 h; (c) a 1100-W electric iron for 45 min; and (d) a 70-W radio for 2 h? *Ans.* (a) 3 cents; (b) 54 cents; (c) 4.1 or 4 cents; (d) 0.7 or 1 cent
- 20.73 If we employ the meter movement of the basic TVM configuration (Fig. 20-26, Example 20.21) in a VOM configuration, what is the new sensitivity value? *Ans.*  $S = 1000 \Omega/V$
- 20.74 For the TVM circuit (Fig. 20-26), find the values of  $R_1$ ,  $R_2$ , and  $R_3$  that are required to produce dc voltage ranges of 5, 50, and 250 V. Also, find the sensitivity of the TVM. *Ans.*  $R_1 = 49 \text{ k}\Omega$ ;  $R_2 = 450 \text{ k}\Omega$ ;  $R_3 = 2 \text{ M}\Omega$ ;  $S = 10\,000 \Omega/V$
- 20.75 Given three DVMs with the following accuracy specifications, what will be the maximum error for each of these instruments if 3.50 V is indicated by each of the meters?
- (a) Resolution = 3 digits (3.50); accuracy =  $\pm 0.1\%$  of reading and  $\pm 0.1\%$  of full scale
  - (b) Resolution = 5 digits (3.5000); accuracy = 0.005% of reading and  $\pm 0.005\%$  of full scale
  - (c) Resolution = 4 digits (3.500); accuracy =  $\pm 0.01\%$  of reading and  $\pm 2$  digits
- Ans.* (a)  $\pm 0.0135$  V; (b)  $\pm 0.00068$  V; (c)  $\pm 0.00235$  V
- 20.76 Three commercial digital voltmeters have the following DCV (dc voltage) accuracies specified:
- DVM 1:  $\pm 1\%$  of reading,  $\pm 1$  digit
  - DVM 2:  $\pm 0.1\%$  of reading,  $\pm 0.05$  percent of full scale
  - DVM 3:  $\pm 0.1\%$  of reading,  $\pm 1$  digit
- If each DVM displays  $\pm 17.76$  V, what is the maximum error for each instrument?
- Ans.* DVM 1:  $\pm 0.188$  V; DVM 2:  $\pm 0.068$  V; DVM 3:  $\pm 0.028$  V

# Index

The letter *p* following a page number refers to a problem.

- AC circuits, 213
  - parallel, 219 (*See also* Parallel ac circuits)
  - series, 213 (*See also* Series ac circuits)
  - series-parallel, 219
- AC generators, 300–303 (*See also* Generators, ac)
- AC meters, 410
- AC motors, 303–313 (*See also* Motors, ac)
- AC series motor, 301
- AC voltage:
  - angle, 205, 206
  - definition, 9
  - effective value, 212
  - frequency, 208
  - generation, 205
  - instantaneous value, 207
  - maximum value, 207
  - period, 208
  - phase angle, 209
  - wave length, 209
- AC voltmeters, 419–423
- Accuracy:
  - ammeter, 412
  - digital meter, 430
  - voltmeter, 415
- Alkaline cell, 92, 96
- Alternating current:
  - average value, 212
  - effective (rms) value, 212
  - peak (maximum) value, 212
  - peak-to-peak value, 212
- Alternator, 91, 205, 300
- American Wire Gauge (AWG), 54, 55
- Ammeter, 411
  - accuracy, 412
  - calibration error, 412
  - extending range, 413
  - loading error, 412
- Ampere (A), 5
- Ampere-turn (At), 167, 174
- Ampere-turn per meter (At/m), 167, 174
- Ampere-turn per weber (At/Wb), 170, 174
- Analog electronic meter, 427
- Analysis:
  - mesh, 104–106
  - nodal, 106–108
- Angle, phase, 209
- Apparent power, 238, 262, 283, 343
- Armature, 184
- Armature coil, 185
- Armature windings, 186
  - duplex lap, 186
  - simplex lap, 186
  - triplex lap, 187
  - wave, 187
- Atom, 1–3
  - energy levels, 1, 2
  - inert, 3
  - neutral, 1
  - unstable, 1
- Atomic number, 1
- Autotransformer, 326, 327
- Ayrton shunt, 432*p*
- Balanced bridge, 128
- Balanced three-phase load, 342
- Balanced three-wire system, Edison, 133
- Bandwidth, 370
- Battery, 7, 88–96
  - capacity, 95
  - internal resistance, 94
  - lead-acid, 90
  - shell life, 95
  - specific gravity, 95
  - (*See also* Cell)
- BH magnetization, 168
- Bilateral circuit, 120
- Block diagram, 31
- Bridge circuit:
  - two deltas, 119, 120
  - Wheatstone, 128, 129, 141*p*
- Brush (generator, motor), 185
- Capacitance, 252, 253
- Capacitive circuits, 257–262
  - parallel, 260
  - series, 257
- Capacitive resistance, 256
- Capacitor motor, 313
- Capacitor-start motor, 312
- Capacitors, 251
  - parallel, 255
  - series, 254
  - types, 254
  - working voltage, 255
- Capacity, battery, 95
- Carbon-zinc cell, 92, 96
- Cell:
  - alkaline, 92

- Cell (*continued*)
- carbon-zinc, 92, 96
  - dry, 89
  - Edison, 93
  - internal resistance, 94
  - lead-acid, 91
  - manganese-alkaline, 92, 93
  - mercury, 93
  - nickel-cadmium, 93
  - parallel, 89, 90
  - primary, 90
  - recharging, 90
  - secondary, 90
  - series, 89
  - solar, 8
  - types, 96
  - voltaic chemical, 7, 88, 89
  - wet, 89
- Charge, 3, 4
- law of charges, 3
- Choke coil, 240*p*, 242*p*
- Choke coil filter, 288*p*
- Circle, Ohm's law, 41
- Circuit:
- ac, 213
  - capacitive, 257
  - dc, 38
  - inductive, 231
  - magnetic, 170
  - open, 38, 74
  - resonant, 362
  - short, 38, 74
  - three-phase, 339
- Circular mils (CM), 54, 55
- Coercive force, 169
- Coils, 165
- characteristics, 226
  - inductance, 225
  - quality, 237
- Commutator, 185
- Commutator motor, 310
- Compound, 1
- Compound dc generator, 187
- Conductance, 75
- Conductor, 53, 54
- Conductor properties, 56
- Continuity test, 418, 436*p*
- Conventional current flow direction, 7
- Conversion:
- $\Delta$  to Y, 116
  - Y to  $\Delta$ , 117
  - source, 125
- Copper loss, 190, 303, 327
- Copper wire table, 55
- Core loss, magnetic, 226, 327
- Coulomb (C), 4, 253
- Coupling capacitor, 265*p*
- Cumulative-compound dc generator, 187
- Current, 5, 6
- conventional flow direction, 7
- Current (*continued*)
- electron flow direction, 6, 7
  - exciting, 328
  - full-load, 329
  - mesh, 104
  - no-load, 328
  - RC series, 391
  - RL series, 385
  - source, 124
  - three-phase, 341
- Current division rule, 75
- Current-phasor triangle, 235, 261, 278, 279
- Cycle, 205
- D'Arsonval meter movement, 411, 427, 428
- DC (direct current), 8, 9
- DC circuits:
- parallel, 69–74
  - series, 50–53
  - series-parallel, 126
- DC generator, 184–191 (*See also* Generator, dc)
- DC motors, 184, 185, 189–196 (*See also* Motors, dc)
- DC voltmeter, 414–416 (*See also* Voltmeters, dc)
- Deflection factor, ohmmeter, 417
- Delta ( $\Delta$ ) connection, 116, 339, 342
- $\Delta$  to Y conversion, 116
- Diagram:
- block, 31
  - one-line, 28–30
  - pictorial, 27
  - schematic, 27, 28, 30
  - wiring, 31, 32
- Diamagnetic materials, 164
- Dielectric, 251
- Dielectric constant, 253
- Differentiating circuit (*see* Peaker circuit)
- Digital meters, 429
- accuracy, 430
  - resolution, 429
  - sensitivity, 429
- Digital voltmeter (DVM), 429
- Diode, 420, 422
- Direction of current, 7
- Division of current, 75
- Dot convention, 230, 329
- Dry cell, 89
- Duplex lap winding, 186
- Earth's magnetic field, 175*p*
- Eddy-current, 226, 227, 313, 328
- Edison cell, 93, 96
- Edison system, 132, 133
- Effective value, 212
- Efficiency:
- ac generator, 303
  - dc generator, 190
  - motor, 46
  - synchronous motor, 308
  - transformer, 324, 327
- Electric charge, 3, 4

- Electric circuit, 38
- Electric energy, 44, 427
- Electrical degrees, 206
- Electrical plan, 31, 32
- Electrical symbols, 28, 29
- Electrodes, 88, 89
- Electrolyte, 88, 89
- Electromagnetic applications, 166
- Electromagnetic induction, 172
- Electromagnetism, 164
- Electromotive force (emf), 5
- Electrons, 1
  - flow, 5–7
  - free, 6, 7
  - shells, 2, 3
- Electrostatic field, 4, 5
- Elements, 1
- Energy:
  - electric, 44, 427
  - cost, 47
  - levels, atom, 1, 2
  - thermal, 7
- Equivalent circuit:
  - dc generator, 188
  - dc motor, 192
  - Norton's, 124
  - resistive, 126
  - Thevenin's, 122
- Equivalent sources, 125
- Exponential form ( $e^x$ ), 385, 389
  
- Farad (F), 16, 252
- Faraday's law, 172, 173
- Ferrites, 163
- Ferromagnetic materials, 163
- Field-effect transistor voltmeter (FETVM), 428
- Field intensity, 167, 174
- Field winding, 185
- Filter:
  - choke coil, 288*p*
  - high-pass, 240*p*, 243*p*
  - low-pass, 269*p*
- Flux:
  - density, 163, 174
  - magnetic, 162, 163, 170, 174
  - mutual, 226
- Force:
  - coercive, 169
  - electromotive, 5
  - magnetomotive, 167
- Frequency, 208
  - resonant, 362, 368
- Full-wave rectifier, 422
- Fuse, 38
  
- Gauge number (wire size), 54–55
- Generator, 7, 184
- Generator, ac, 300–303
  - alternator, 300
  - efficiency, 303
- Generator, ac (*continued*)
  - frequency, 302
  - generated voltage, 301
  - losses, 303
  - parallel operation, 302
  - ratings, 303
  - three-phase, 339
  - voltage regulation, 302
- Generator, dc, 184–191
  - components, 184, 185
  - compound, 187
  - cumulative-compound, 187
  - efficiency, 190, 191
  - equivalent circuit, 188
  - generated voltage, 189
  - long-shunt compound, 187, 188
  - losses, 190, 191
  - self-excited, 187
  - separated excited, 187
  - series, 187, 188
  - short-shunt compound, 187, 188
  - shunt, 187, 188
  - voltage regulation, 189
- Geometric degrees, 206
- Ground, 34*p*, 38
  
- Half-power points, 370
- Half-wave rectifier, 420
- Henry (H), 16, 225
- Hertz (Hz), 16, 208
- High-pass filter, 240*p*, 243*p*
- Horsepower, 43, 193
- Hydrometer, 95
- Hysteresis, 169, 190, 226, 227, 313, 327, 328
  
- Ideal transformer, 322, 324
- Impedance:
  - coil, 237, 242*p*
  - parallel *LC* circuit, 368
  - parallel *RC* circuit, 261
  - parallel *RL* circuit, 236
  - parallel *RLC* circuit, 279
  - resonant circuit, 363
  - series *RC* circuit, 260
  - series *RL* circuit, 234
  - series *RLC* circuit, 277
- Impedance ratio, 326
- Induced voltage, 172
- Inductance, 225
  - coil, 225, 226
  - mutual, 226
  - self-, 225
  - total, 228, 230
- Induction, electromagnetic, 172
- Induction motor, 310, 311, 313
- Inductive circuits, 231–239
  - parallel, 235–236
  - series, 231–235
- Inductive reactance, 227

- Inductors:
  - parallel, 230
  - polarity, 229
  - series, 228
  - series-aiding, 229
  - series-opposing, 229
- Inert atom, 3
- Instantaneous power, 282
- Instantaneous value, 207
- Instruments:
  - digital, 429, 430
  - electrical, 411–427
  - electronic, 427, 428
- Insulator, 90
- Internal resistance, 94, 237, 411
- International System of Units (SI), 15, 16
- Ionization, 3
- Ions, 3, 88
- IR* drop, 52
  
- Joule (J), 16, 44
  
- Kilo- (metric prefix), 15, 16, 19
- Kilowatt hour, 44, 427
- Kirchhoff's laws:
  - current law (KCL), 103
  - voltage law (KVL), 101, 102
  
- Lagging phase angle, 210
- Lagging power factor, 284
- Law:
  - charges, 3, 4
  - Faraday's, 172, 173
  - Lenz's, 173
  - Ohm's, 41, 170
- LC circuit, 366, 367
- Lead-acid cell, 90, 96
- Leading phase angle, 210
- Leading power factor, 284
- Left-hand rule (motor), 191
- Lenz's law, 173
- Line current, 340, 341
- Line drop, 130
- Line power loss, 131
- Line voltage, 340, 341
- Linear circuit, 120
- Load:
  - balanced, 133, 342
  - $\Delta$ -connected, 342
  - unbalanced, 346, 347
  - Y-connected, 342
- Lodestones, 162
- Long-shunt compound dc generator, 187, 188
- Loop, 104
- Loop analysis, 104
- Loop current, 104
- Losses:
  - ac generator, 303
  - dc generator, motor, 189, 190
  - Losses (*continued*)
    - transformer, 327
  - Low-pass filter, 269*p*
  
  - Magnetomotive force (mmf), 167, 170, 174
  - Magnetic circuit, 170, 171
  - Magnetic field, 162, 164, 165, 175
  - Magnetic flux, 162, 163, 170, 174
  - Magnetic flux density, 163, 174
  - Magnetic materials, 163
    - diamagnetic, 164
    - ferrites, 163
    - ferromagnetic, 163
    - paramagnetic, 164
  - Magnetic poles, 162, 175
  - Magnetic units, 167, 174
  - Magnetite, 162
  - Magnetization curve, 168
  - Magneto hydrodynamic (MHD) conversion, 7
  - Magnets:
    - artificial, 162
    - natural, 162
    - permanent, 163
    - temporary, 163
  - Manganese-alkaline cell, 92, 93, 96
  - Matter, 1
  - Maximum power transfer theorem, 129
  - Maximum (peak) value, 212
  - Mega- (metric prefix), 16
  - Mercury cell, 93, 96
  - Mesh current, 104–106
  - Meter error:
    - calibration, 412
    - formula, 423
    - loading, 412, 415
  - Metric prefixes, 15–16, 19
  - Micro- (metric prefix), 16
  - Milli- (metric prefix), 16
  - Mils, 54
    - circular, 54, 55
  - Molecule, 1
  - Motors, 184
  - Motors, ac, 303–314
    - polyphase induction, 303
      - rotor frequency, 305
      - slip, 305
      - squirrel-cage, 304
      - synchronous speed, 305
      - torque, 306
    - single-phase, 310
      - ac series, 311
      - capacitor, 313
      - capacitor-start, 312
      - commutator, 310
      - induction, 310, 311
      - repulsion, 311
      - shaded-pole, 313
      - split-phase, 312
      - synchronous, 310, 313

- Motors, ac (*continued*)  
 synchronous, 306  
 efficiency, 308  
 field excitation, 308, 309  
 loading, 307  
 power factor correction, 308  
 ratings, 308  
 single-phase, 311, 313  
 synchronous speed, 305  
 torque, 307
- Motors, dc, 184, 185, 191–196  
 components, 184, 185  
 compound, 195  
 equivalent circuit, 192  
 series, 194  
 shunt, 194  
 speed regulation, 193  
 starting resistance, 196  
 torque, 192
- Multimeter, 419
- Multiplier, 414
- Mutual inductance, 226
- Nano- (metric prefix), 16
- Negative charge, 1
- Network (*see* Circuit)
- Network theorem (*see* Theorem)
- Neutral atom, 1
- Neutral wire, 132, 133
- Neutron, 1
- Nickel-cadmium cell, 93, 96
- Nodal analysis, 106–108
- Node, 107  
 principal, 106, 107  
 reference, 106
- Node voltage, 106–108
- No-load voltage, 94
- Nonsinusoidal waveform, 218
- Norton's theorem, 124
- Nucleus, 1
- Ohm ( $\Omega$ ), 16, 39
- Ohmmeter, 416  
 continuity test, 418  
 deflection factor, 417
- Ohm's law:  
 electric circuit, 41  
 magnetic circuit, 170
- One-line diagram, 28, 30
- Open circuit, 38, 74
- Open-circuit test, transformer, 327
- Open-circuit voltage, 94, 122
- Parallel ac circuits:  
 LC, 366–368  
 resistances, 219p  
 RC, 260, 261
- Parallel ac circuits (*continued*)  
 RL, 235, 236  
 RLC, 278–281
- Parallel dc circuits, 69–77  
 conductance, 75  
 distribution of current, 69  
 division of current, 75  
 equal resistors, 72  
 power, 77  
 total current, 69  
 total resistance, 71, 73  
 voltage, 69
- Parallel operation (generators), 302
- Parallel resonance, 366, 372
- Paramagnetic material, 164
- Peak (maximum) value, 212
- Peak-to-peak value, 212
- Peaker (RC) circuit, 400p
- Period, 208
- Permeability, 163, 168, 169, 174
- Phase angle, 209  
 capacitive circuit, 257, 258, 260, 261, 276, 279  
 inductive circuit, 231, 232, 235, 236, 276, 279  
 lagging, 210  
 leading, 210  
 resistive circuit, 213
- Phase current, 340
- Phase splitting, 312
- Phase voltage, 340
- Phasor, 209–211
- Phasor diagram, 209–211  
 current triangle, 235, 261, 278, 279  
 voltage triangle, 232, 258, 275, 276
- Photoelectric effect, 8
- $\Pi$  to T conversion, 116
- Pico- (metric prefix), 16
- Piezoelectric effect, 8
- Polarity:  
 battery, 88  
 coil, 165  
 induced voltage, 173  
 inductors, 230  
 single conductor, 164  
 transformer, 329, 330  
 voltage drop, 53
- Poles, magnetic, 162, 175
- Polyphase induction motor (*see* Motors, ac)
- Positive charge, 1
- Potential difference, 5
- Potentiometer, 40, 41
- Power:  
 apparent, 238, 262, 283, 343  
 half-, 370  
 instantaneous, 282  
 maximum transfer of, 129  
 reactive, 237, 262, 283, 343  
 real, 237, 262, 283, 343  
 resistor, 42, 43  
 three-phase, 343

- Power (*continued*)
  - total dc, 57, 77
  - wattmeter, 425
- Power factor (PF), 237, 283, 308, 327
  - lagging, 284
  - leading, 284
- Power factor correction, 285
  - synchronous motor, 308
- Power measurement:
  - dc, 439*p*
  - single-phase, 425
  - three-phase, 426
  - two-wattmeter method, 426
- Power transformer, 330*p*
- Power triangle, 237, 283, 343
- Powers of ten, 16–19
- Primary cell, 90
- Primary winding, transformer, 322
- Principal node, 106, 107
- Proton, 1
  
- $Q$  of coil, 237, 244*p*
  - measurement, 376*p*
- $Q$  of parallel circuit, 369
- $Q$  of resonant circuit, 370–372
- $Q$  of series circuit, 365
  
- Radian, 15, 206
- RC circuit:
  - parallel, 260, 261
  - peaker, 400*p*
  - series, 257–260, 390, 391
  - time constant, 393, 394
- Reactance:
  - capacitive, 256
  - inductive, 227
- Reactive power, 237, 262, 283, 343
- Real power, 237, 262, 283, 343
- Rectifier circuits:
  - full-wave, 422
  - half-wave, 420
- Reference node, 106
- Reference phasor, 210
- Relative permeability, 163, 169, 174, 226
- Relay circuit, 166, 167
- Reluctance, 170, 171, 174
- Repulsion motor, 311
- Resistance, 39
  - copper wire, 54, 55
  - internal, 94
  - measurement:
    - multimeter, 419
    - ohmmeter, 416–417
    - Wheatstone bridge, 128, 129
  - parallel, 71, 72
  - series, 50, 51, 57
  - specific, 55, 56
  - temperature coefficient, 56, 57
  - Thevenin, 122
- Resistivity, 55
- Resistor, 39
  - carbon-composition, 39
  - fixed, 39
  - power rating, 40
  - tolerance, 39
  - variable, 40
  - wire-wound, 39
- Resolution, digital meter, 429
- Resonance:
  - parallel, 366–369
  - series, 362–365
- Resonant frequency, 362, 368
- Retentivity, 169
- Rheostat, 40
- Right-hand rule, 164–166
- RL circuit:
  - high-voltage, 397*p*
  - parallel, 235–236
  - series, 231–235, 384, 385
  - time constant, 388–389
- RLC circuit:
  - parallel, 278–280
  - parallel branches, *RL* and *RC*, 280, 281
  - resonant, 362–363
  - series, 275–278
- rms (root-mean-square) value, 212
- Rotor, 184, 304
- Rounding-off numbers, 20, 21
- Rule:
  - current division, 75
  - equal resistors in parallel, 72
  - left-hand, 191
  - Ohm's law circle, 41
  - powers of ten, 16–19
  - right-hand, 164–166
  - voltage division, 58
- Sawtooth waveform, 399*p*
- Schematic diagram, 27, 28, 30
- Scientific notation, 20, 21
- Secondary winding, transformer, 322
- Self-excited dc generator, 187'
- Self-inductance, 225
- Sensitivity:
  - ac meter, 421
  - digital meter, 429
  - multimeter, 419
  - voltmeter, 415, 434*p*
- Separated excited dc generator, 187
- Separators, 90
- Series ac circuits:
  - C* only, 257
  - L* only, 231
  - R* only, 213
  - RC*, 257–260
  - RL*, 231–235
  - RLC*, 275–278
- Series dc circuits, 50–53
- Series dc generator, 187

- Series dc motor, 194
- Series-parallel dc circuits, 126–128
- Series resonance, 362, 372
- Shaded-pole motor, 313
- Shelf life, battery, 95
- Short circuit, 38, 74
- Short-circuit test, transformer, 327, 333*p*
- Short-shunt compound dc generator, 187, 188
- Shunt dc generator, 187, 188
- Shunt dc motor, 194
- SI (International System of Units), 15, 16
- Siemens (S), 16, 75
- Significant digit, 20
- Simplex lap winding, 186
- Sine wave, 206, 207
- Single-line diagram, 28
- Single-phase motors, 310–313
- Sinusoid, 209
  - average value, 212
  - effective (rms) value, 212
  - peak (maximum) value, 212
  - peak-to-peak value, 212
  - table for conversions, 212
- Slip, 305
- Slip rings, 300
- Solar cell, 8
- Solenoid, 167
- Sources, 7, 8
  - ac, 9, 205
  - current, 124
  - dc, 8
  - equivalent current and voltage, 125
  - Norton, 124
  - Thevenin, 122
  - voltage, 8, 9
- Specific gravity, cell, 95
- Specific resistance, 55, 56
- Speed, synchronous, 305
- Speed-load characteristic:
  - compound motor, 195
  - induction motor, 306
  - series motor, 194, 195
  - shunt motor, 194
- Speed regulation, dc motor, 193, 194
- Split-phase motor, 312
- Squirrel-cage motor, 304
- Starting resistor, dc motor, 196
- Step-down transformer, 322
- Step-up transformer, 322
- Storage battery, 90–92
- Superposition theorem, 120
- Switch, 31, 32, 34*p*
- Symbols, electrical, 28, 29
- Synchronizing ac generators, 302
- Synchronous motors (*see* Motors, ac, synchronous)
  
- T to  $\Pi$  conversion, 117
- Temperature coefficient of resistance, 56, 57
- Tesla (T), 16, 163
  
- Theorem:
  - maximum power transfer, 129
  - Norton's, 124
  - superposition, 120
  - Thevenin's, 122
- Thermal energy, 7
- Thermionic emission, 7
- Thermocouple, 8, 423
- Thevenin's theorem, 122
- Three-phase systems, 339–347
  - balanced load, 342
  - $\Delta$ -connected, 339
  - power, 343
  - unbalanced load, 346
  - Y-connected, 339
- Three-wire distribution system, 131–133
- Time constant, 388
  - RC circuit, 393
  - RL circuit, 388
- Time diagram:
  - C only, 257
  - L only, 231
  - R only, 213
  - RC peaker, 400, 401*p*
  - RC series, 259, 390, 391
  - RL parallel, 236
  - RL series, 233, 384, 385
  - sawtooth, 399*p*
  - power, 282
- Time, exponential voltage decay or rise, 394, 395
- Tolerance, resistance, 39, 40
- Torque:
  - dc motor, 191, 192
  - induction motor, 306
  - synchronous motor, 307
- Torque-load characteristic:
  - compound motor, 195
  - series motor, 195
  - shunt motor, 194
- Transformers, 322–330
  - autotransformer, 326, 327
  - basic construction, 322
  - current ratio, 323
  - efficiency, 324, 327
  - ideal, 322, 324
  - impedance ratio, 326
  - losses, 327
  - no-load condition, 328
  - polarity, 329, 330
  - power type, 330*p*
  - primary winding, 322
  - ratings, 325
  - secondary winding, 322
  - step-down, 322
  - step-up, 322
  - three-phase connections, 340
  - three-phase voltage, current table, 341
  - turns ratio, 322
  - voltage ratio, 322



- Transistor:
  - radio receiver, 28, 30
  - symbol, 28, 29
- Transistor voltmeter (TVM), 428
- Triplex lap winding, 187
- True rms voltmeter, 423, 424
- Tuned circuit, 362, 370
- Turns ratio, 322
- Two-wattmeter method, 426
  
- Unbalanced three-phase load, 346
- Unbalanced three-wire system, Edison, 132, 133
- Units, SI, 15, 16
- Unstable atom, 1
  
- VA (voltamperes), 238
- Valence electrons, 2
- VAR (voltamperes reactive), 237
- Vector, 209, 210
- Volt (V), 2, 5
- Voltage, 5
  - induced, 172
  - node, 106
  - open-circuit, 94, 122
  - polarity, 101, 102
  - RC series circuit, 391
  - RL series circuit, 385
  - three-phase, 341
  - (*See also* AC voltage)
- Voltage-divider circuit, 138*p*
- Voltage division rule, 58
- Voltage drop, 52, 58
- Voltage-phasor triangle, 232, 258, 275, 276
- Voltage ratio, 322
- Voltage regulation:
  - ac generator, 302
  - dc generator, 189
- Voltaic chemical cell, 7, 88, 89
- Voltmeters:
  - ac, 419–423
    - sensitivity, 421
  - dc, 414–416
    - accuracy, 415
    - loading error, 416, 433*p*
    - multiplier, 414
  - digital, 429
  - true rms, 423, 424
- Watt (W), 16, 42
- Wattage rating, 40
- Watt-hour meter, 427
- Wattmeter, 327, 425
  - measurement, 426
- Wave winding, 187
- Waveforms:
  - RC peaker circuit, 400, 401*p*
  - RC series circuit, 390–392
  - RL series circuit, 384, 385
  - sawtooth, 399*p*
- Wavelength, 209
- Weber (Wb), 16, 163
- Wet cell, 89
- Wheatstone bridge, 128, 129, 141*p*
- Winding, transformer:
  - primary, 322
  - secondary, 322
- Wire Gauge, American (AWG), 54, 55
- Wire measurement, 54
- Wire resistance, 55
- Wiring diagram, 31, 32
- Work, 5
  
- Y (Wye) connection, 116, 339, 342
- Y to  $\Delta$  conversion, 117